

Electrical Machinery Laboratory: Final Test (2022.06.15, 15:30-18:00)

A. Power Electronics

1. The commonly used power devices include **diode**, **SCR**, **MCT**, **BJT**, **MOSFET**, **IGBT**, **TRIAC**, etc.


- (1) Which device is uncontrolled turn-on and turn-off: diode . (2%)
- (2) Give the devices that requires continuous gate signal: MOSFET, BJT, IGBT . (6%)
- (3) Give the devices that requires pulse gate signals: SCR, MCT, TRIAC . (6%)

2. The wide-bandgap devices can be turn-on and turn-off faster than Si-based devices. There are two kinds of wide-bandgap devices: SiC and GaN . (4%)

3. Which device has **negative** temperature coefficient and is **not** suitable for parallel operation?
MOSFET or BJT: BJT . (2%)

4. A IGBT is the combination of MOSFET and BJT . (4%)

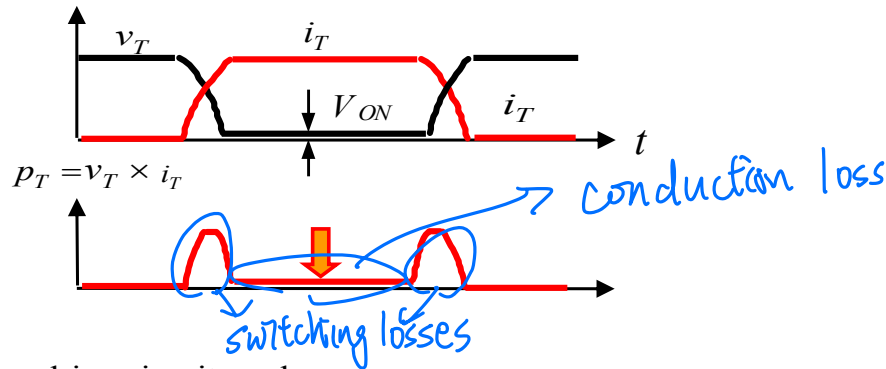
5. Indicate the conduction loss and switching losses for a power semiconductor switch: (6%)



B. Stepping Motors

1. For the stepping motor drive circuit as shown:

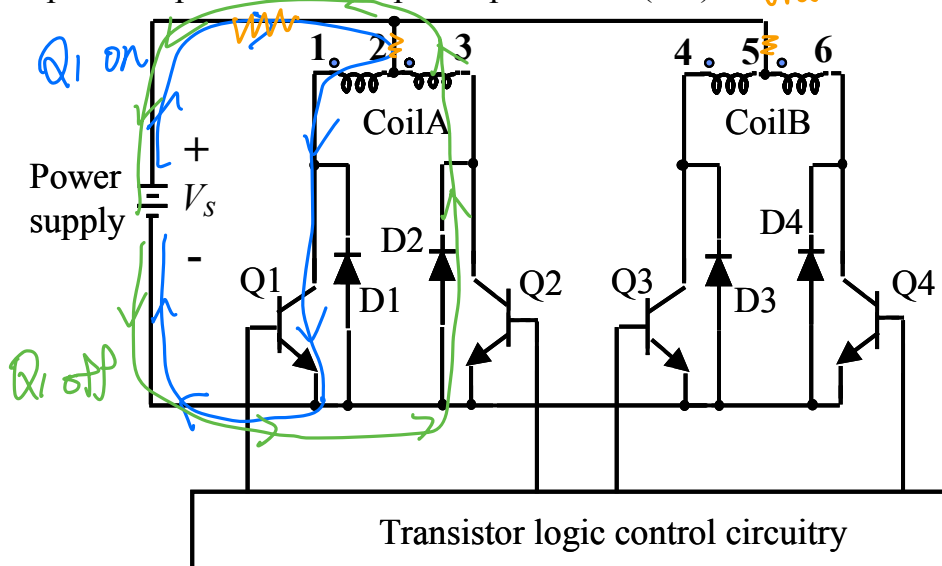- (1) The winding is bifilar or unifilar? bifilar . (2%)
- (2) The drive is bipolar or unipolar? unipolar . (2%)
- (3) Draw or describe the current paths as: (a) Q1 is ON; and (b) Q1 is off. (6%)
- (4) Indicate the possible places for the speed up resistor. (6%) → 橘色部份.




C. Electronic Fluorescent Lamp

1. For the half-bridge electronic fluorescent lamp circuit as shown:

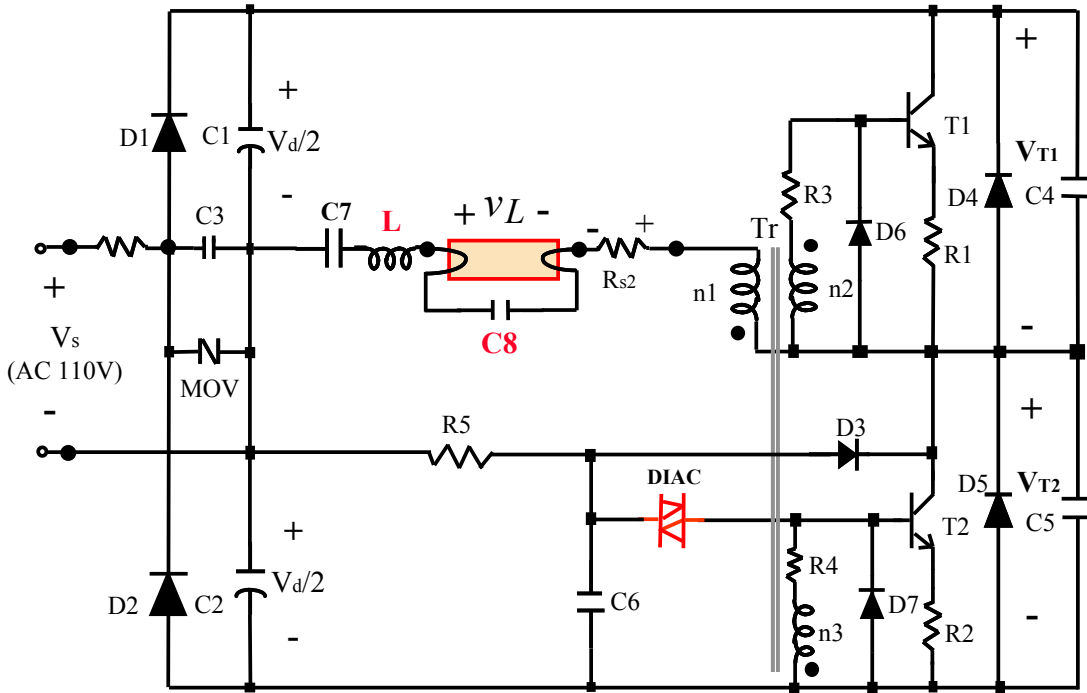(1) Briefly describe its operation principle. (10%)

首先, C_1, C_2 執行半波整流的动作, 接著對 C_6 充電至 $break\ down\ voltage$, DIAC 導通, T_2 ON. 電流開始互感耦合, 產生諧振.



(2) Refer to given schematic, give the purposes of the following circuit components: (9%)

MOV: 突波电压抑制元件

D4, C4, D5, C5: T_1, T_2 の 諧振电路, 防開關損壞


DIAC: 电压超過 $break\ down\ voltage$ 時會導通, 引發諧振电路開始諧振

D. Cold Cathode Fluorescent Lamp (CCFL)


1. Briefly describe operation principle of this experiment circuit (given below). (8%)

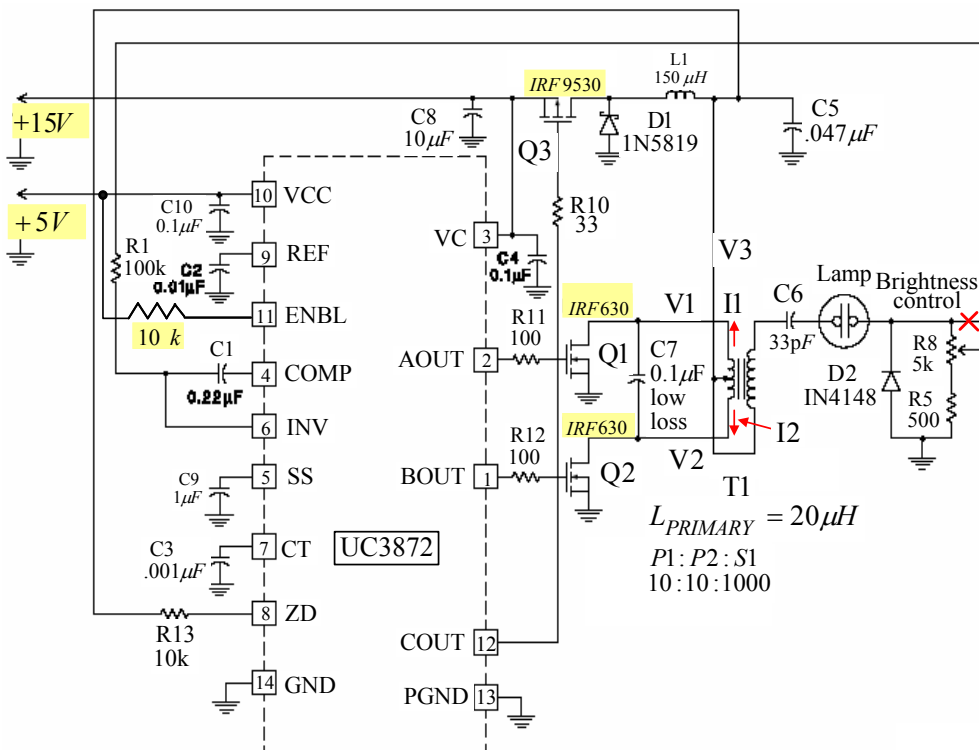2. IRF 9530 is P-channel or N-channel power MOSFET? P-channel. (2%)

AOUT, BOUT 產生的訊号讓 Q1, Q2 push-pull 之後 Buck converter 電流 灌入, 產生諧振, 使燈炮發光。



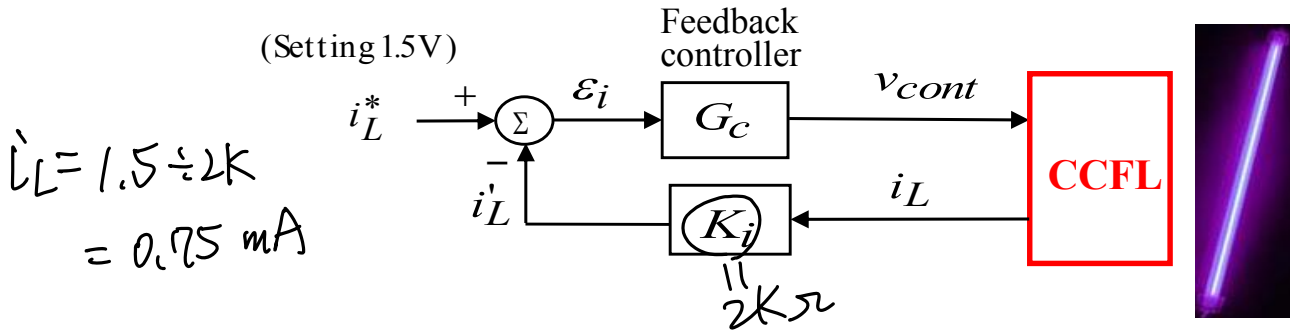3. For the brightness control scheme as given, $K_i = 2k\Omega$ is set, find the set current $i_L = \underline{0.75 \text{ mA}}$. (6%)



4. The devices (Q3, D1, L1) form what type of DC-DC converter? (4%)

DC-DC Buck converter

E. Power Transformers and Power Quality

1. Some test data of the given transformer are measured as follows:

OCT: $V_{oc} = \underline{220}$ (V), $I_{oc} = 2.5$ (A), $P_{oc} = 150$ (W)

SCT: $V_{sc} = 150$ (V), $I_{sc} = \underline{4.445}$ (A), $P_{sc} = 250$ (W)

(1) For a correct measurement procedure being made, fill in the values of V_{oc} and I_{sc} . (6%)

(2) Find efficiencies at (full load, PF= 0.8 lagging) and at (50% rated load PF = 0.8 lagging): (8%)

$$\eta_{1.0} = \frac{P_{rated}}{P_{rated} + P_{oc} + P_{sc}} = \frac{10k \times 0.8}{10k \times 0.8 + 150 + 250} = 95.24\%$$

$$\eta_{0.5} = \frac{\frac{1}{2} P_{rated}}{\frac{1}{2} P_{rated} + P_{oc} + \frac{1}{4} P_{sc}} = \frac{\frac{1}{2} \times 10k \times 0.8}{\frac{1}{2} \times 10k \times 0.8 + 150 + \frac{1}{4} \times 250} = 94.96\%$$

2. At the a given load, its measured no-load and full-load terminal voltages respectively are:

120V/60Hz and 108V/60Hz. Find the voltage regulation: (4%)

$$VR = \frac{|120 - 108|}{|108|} = 11.11\%$$

3. The rating of a Delta-Delta connected three-phase transformers is 10kVA. Now a single-phase transformer is removed to form the V-V connection, find its VA rating. (6%)

$$\frac{10k}{\sqrt{3}} \doteq 5.77 \text{ KVA}$$


4. (1) Explain the inrush current generation process of a transformer. (6%)

當按下開關時，电压產生磁通 ($\phi(t) = \frac{1}{\omega N} \int v(t) dt$)，磁通產生激磁电流

$I_f v(t) = \sqrt{2} V \sin \omega t \Rightarrow \phi(t)$ 為 \cos func. 且如果是在 A、C 點按下開關時


(2) In what case the inrush current will be minimum? (4%)

在 V 的峰值時開啟。如圖 B、D 點

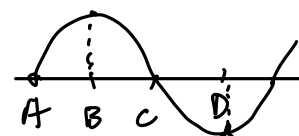

ϕ 會很大，此時這很大的磁通產生的激磁电流就是 inrush current

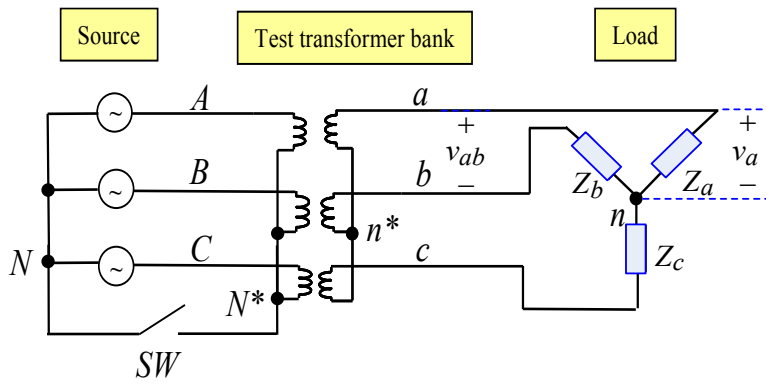5. For the Y-Y connected transformer system as shown:



(1) In which case $v_a(t)$ possesses 3rd-order harmonics: SW is closed or opened? opened. (2%)

(2) If SW is closed, $Z_a=Z_b=Z_c$ and $i_A(t) = 5\sin 377t + 1.5\sin(3 \times 377t)$, find: (4%)

$i_{N^*-N} = \underline{3 \times 1.5 \sin(3 \times 377t) = 4.5 \sin(3 \times 377t)}$ (A)

(3) Explain what is roving ground? (6%)

線电压雖相同, 但有若不平衡負載時中性點會移動, 相电压會不同。
則稱為 moving ground.

6. For the 18-pulse rectifier system applied by multi-phase transformers:

(1) What phase shifts of the output voltage are provided by this system? $-20^\circ, 0^\circ, +20^\circ$. (4%)

(2) If the frequency of input AC voltage is 60Hz. What is the frequency of the DC-link voltage ripple? $60 \times 18 = 1080$ Hz. (3%)

7. For an incandescent lamp (白熾燈) load:

(1) Its power factor PF = 1; (2%)

(2) Describe why it possesses inrush current? (4%)

1. 白熾燈的电阻會隨時間改變
在一開始啟動時电阻較小, 所以啟動瞬間有
inrush current. 之後時間久了白熾燈的电阻↑
电流會趨於穩定。

F. Industrial Control Distribution:


1. How to change the rotational direction of a three-phase induction motor. (3%)

將三條輸入の電源線の其中2條對調。



2. For the circuit as shown, as the push button REV is pushed down, describe all the events (including the operations of contacts, lamps, motor, ...) to occur. (15%)

馬達反轉，按 FWD 無效 (1) 井 MCR 2_{open}，亮黃燈，TR 激磁


3. What is the component TH-RY? 熱動電斷器 (Thermal Relay) (5%) 過載即自動跳掉。

4.  belongs to a-contact or b-contact? b-contact. (3%)

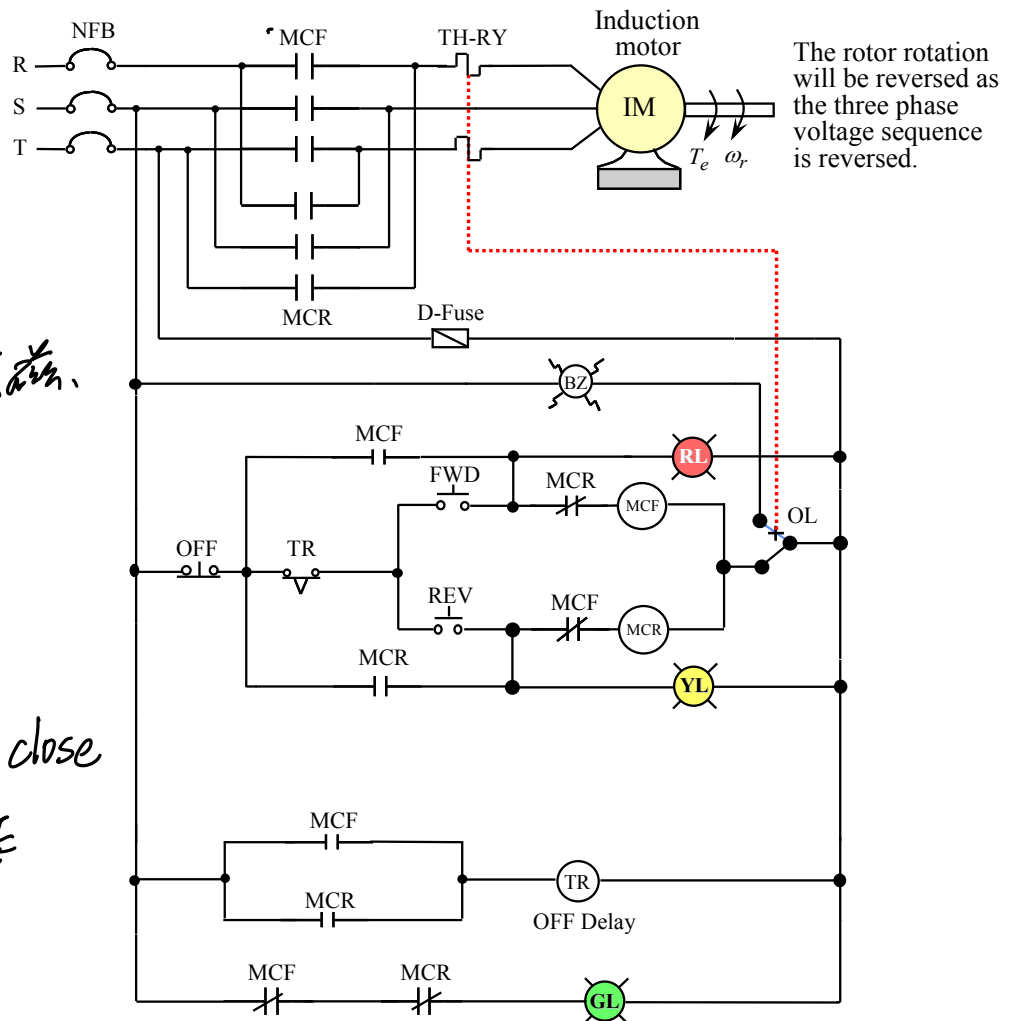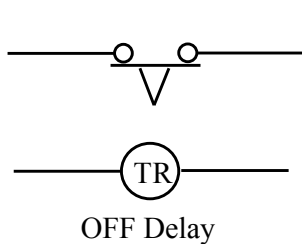
5. Describe the operation of the off-delay relay TR. (6%)



馬達轉動時，(TR) 激磁。


 馬上 open

按下時，(TR) 消磁。


等 delay 時間到， close 才能執行下一個動作

DC Machines:

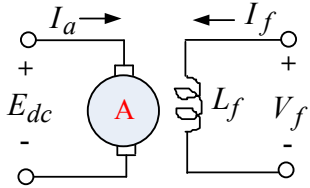1. Give the name of the following DC machines: (4%)





它激式

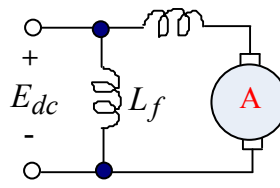


自激複激式
(長並聯)

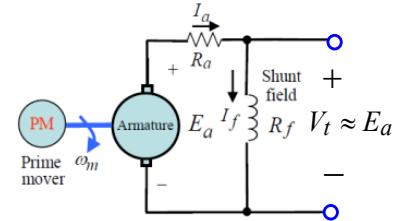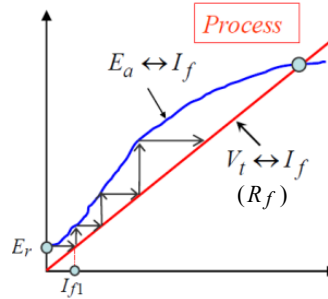2. (1) Describe the voltage buildup process of a DC shunt generator. (5%)


利用一剩磁產生一小電樞電壓 E_r 。
由 E_r 產生一小磁場電流 I_f ，進而產生較高電壓，直至磁化曲線與場阻線相交所決定之電壓。



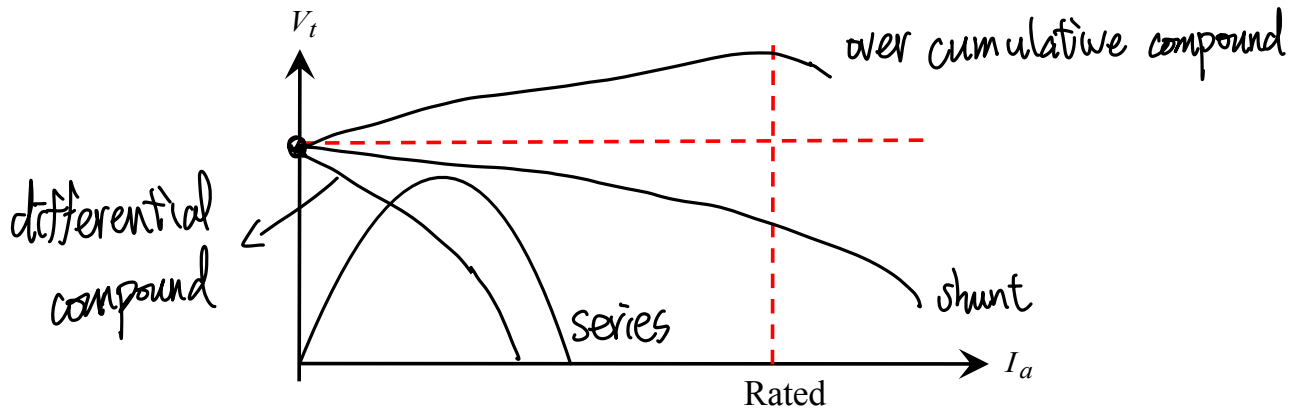3. (1) Sketch the terminal voltage vs. load (armature current) curves of the following DC generators in the same figure: *Shunt, series, over cumulative compound, differential compound.* (8%)



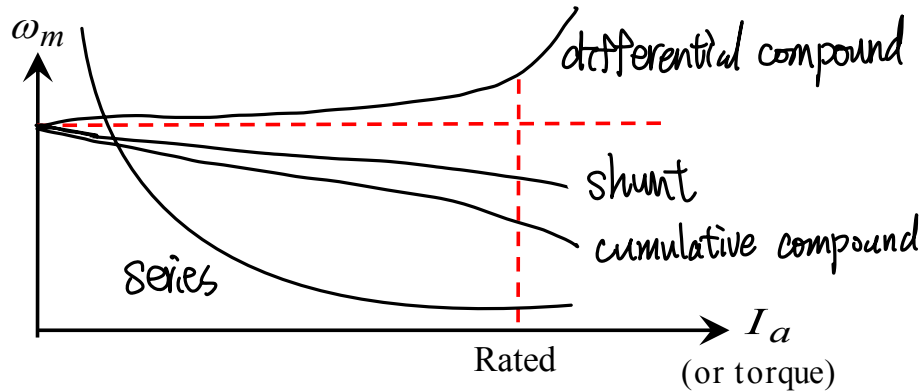
(2) Sketch the speed vs. load (armature current) curves of the following DC motors in the same figure: *Shunt, series, cumulative compound, differential compound.* (8%)



SCR Phase Speed Control of DC Motors:

1. Why we can not add a filtering capacitor between nodes (A) and (N)? (4%)

加了之後，會沒有 zero crossing 提供 SCR 無線換相。

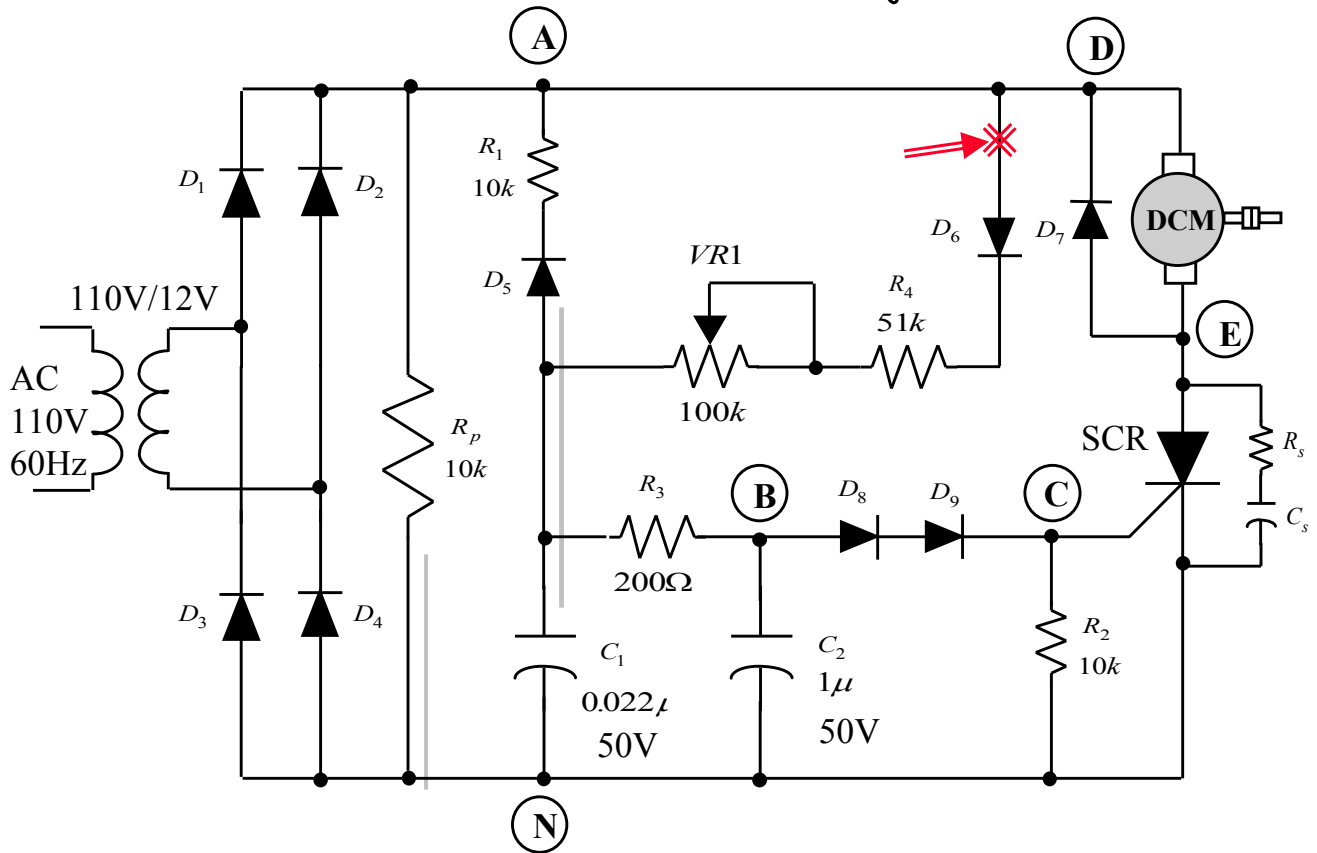

3. Describe the purpose of D_7 . (3%)

此為飛輪 diode，與電樞反並聯，一般係用以提供電樞電流延續流通路徑，使電樞電流較為連續， D_7 另亦可減少因電樞電流之變化所生電感負感反電動勢 (L di/dt) 對 SCR 耐壓之危害。

4. Describe the purpose of VR_1 . (3%)

調整 VR_1 可改變 C_2 充電速度，就可改變 SCR 導通角，控制轉速。

5. Describe the difference for the anode D_6 being connected to point (D) and (E). (5%)

D_6 接 (D) \Rightarrow 轉速較易受負載改變而影響。

D_6 接 (E) $\Rightarrow C_1$ 之充電電壓由 SCR 之陽極電壓供給，具有較佳調節特性，轉速較不易受負載影響。