
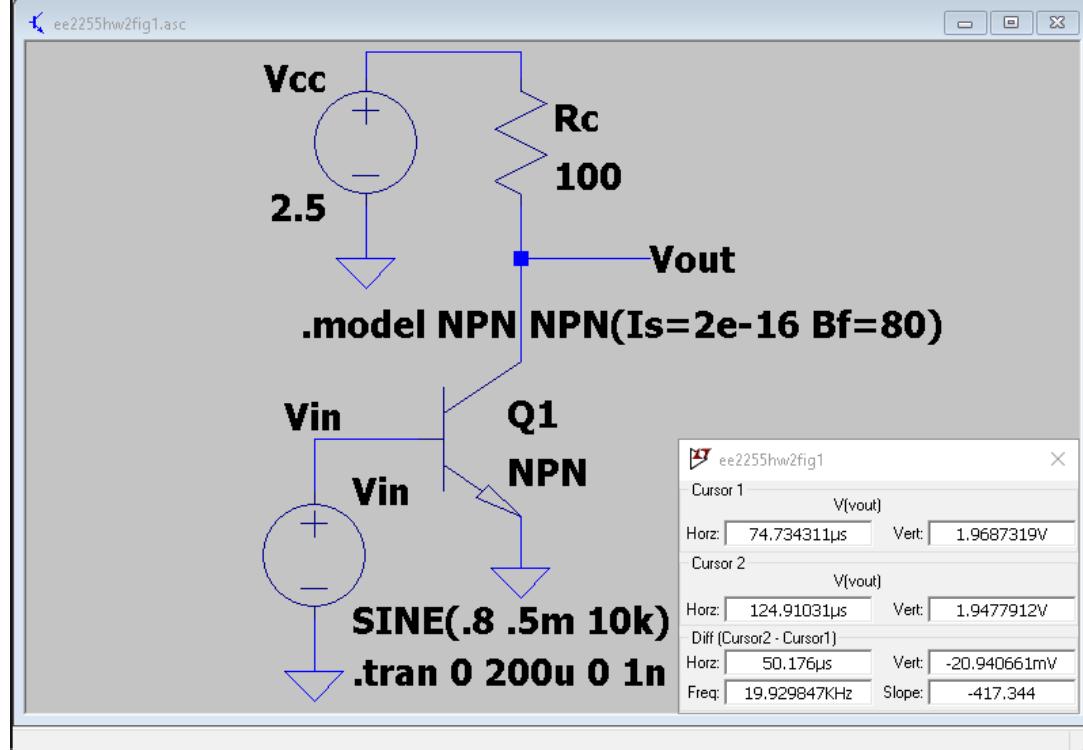


108061112 林靖 hw2

1.(a)(b)

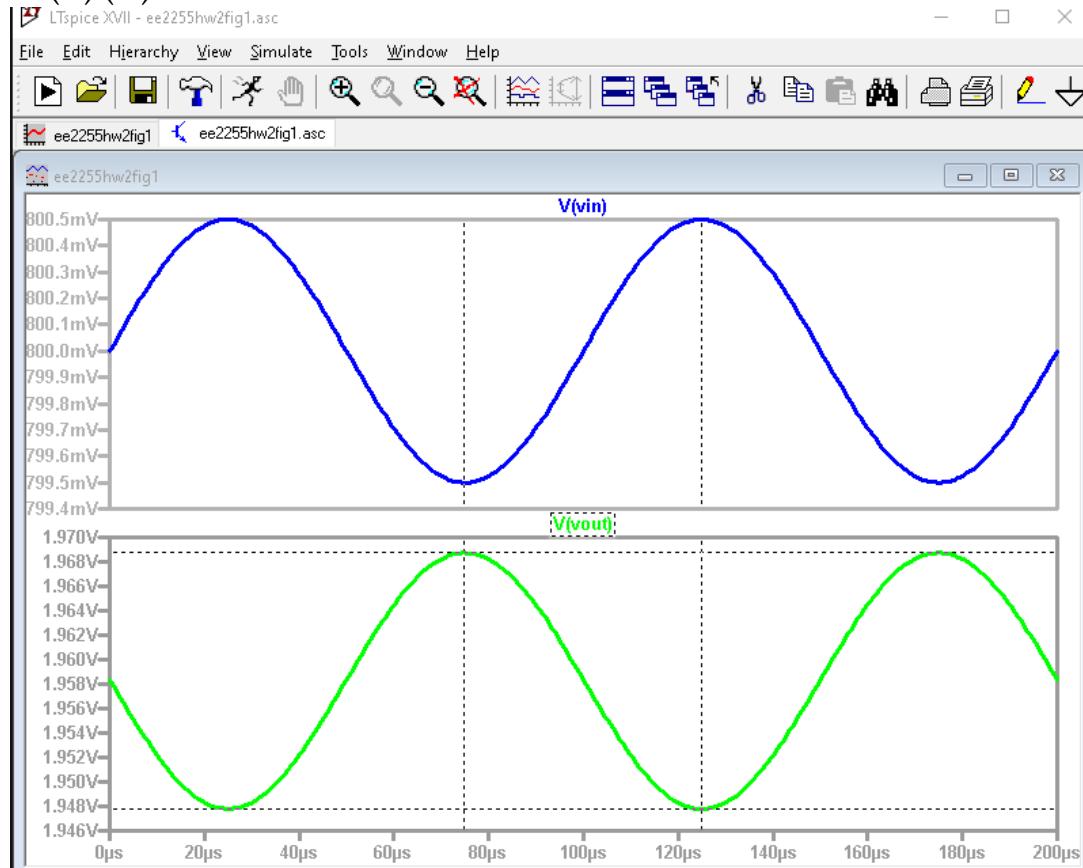

1.(c)

$$g_m \cdot R_c$$

$$= -\frac{I}{V_T} I_S \exp \frac{V_{BE}}{V_T} \cdot R_c$$

$$= \frac{1}{26mV} 2 \cdot 10^{-16} A \exp \frac{0.8V}{26mV} \cdot 100 \Omega$$

$$= 17.740$$


1.(d)

SPICE voltage gain =  $(1.9687319 - 1.9477912) / 0.001 = 20.941$

small signal model voltage gain = 17.740

relative error =  $(20.941 - 17.740) / 20.941 = 0.15$

2.(a)(b)

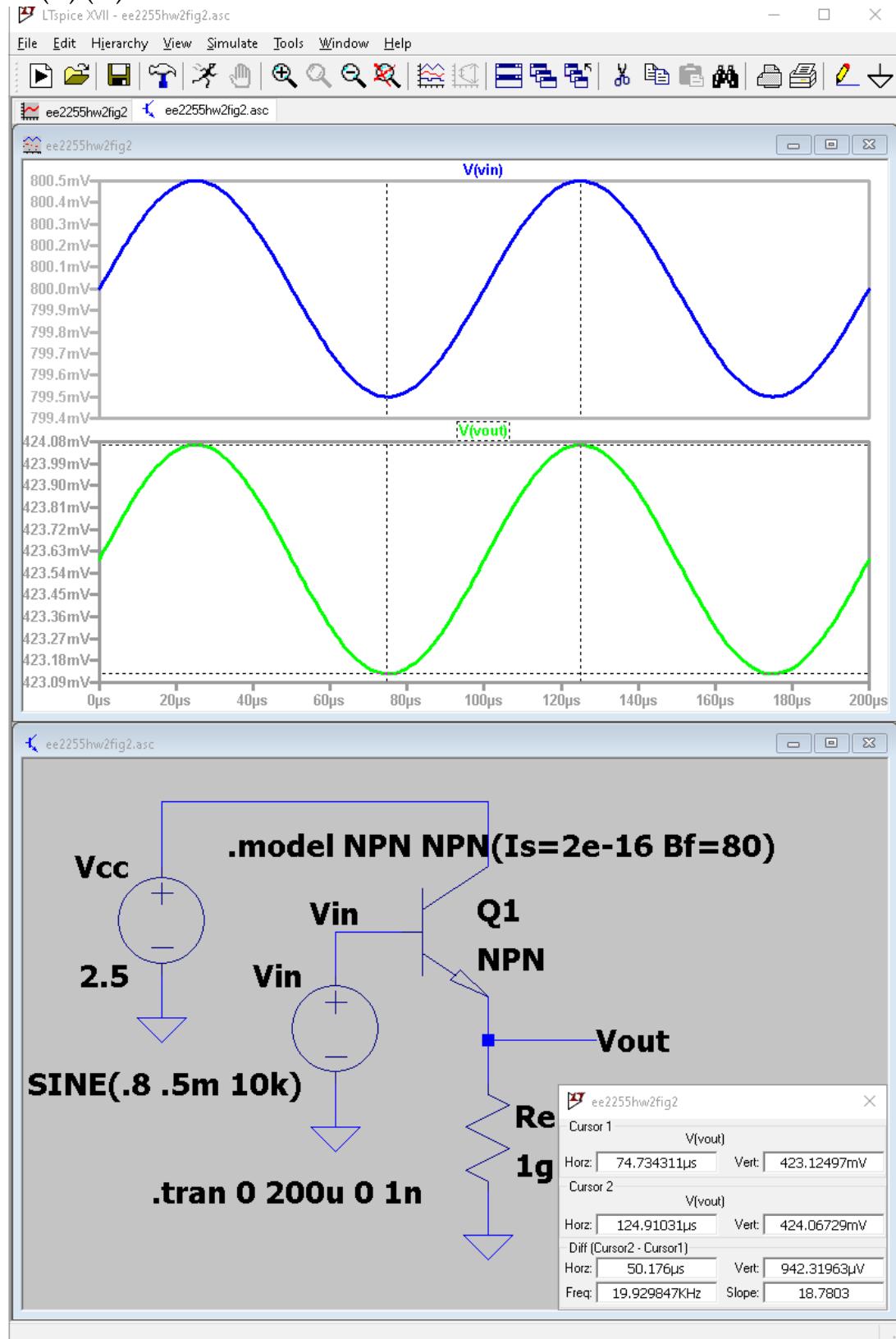

2.(c)

$$\frac{R_E}{R_E + \frac{1}{g_m}}$$

$$= \frac{R_E}{R_E + \frac{1}{\frac{1}{V_T} I_s \exp - \frac{V_{BE}}{V_T}}}$$

| GΩ

$$= \frac{| GΩ + \frac{1}{\frac{1}{26mV} 2 \cdot 10^{-16} A \exp - \frac{0.8V}{26mV}}}{| GΩ + }$$

$$= 0.99999$$

2.(d)

SPICE voltage gain =  $(0.42406729 - 0.42312497) / 0.001 = 0.94232$

small signal model voltage gain = 0.99999

relative error =  $(0.94232 - 0.99999) / 0.94232 = -0.06$