


1. (a)

$W = L = 0.2 \mu\text{m}$

Gate bias = 0.6 V

Loading resistor = 1 M Ω

Voltage gain = 26.765 > 10

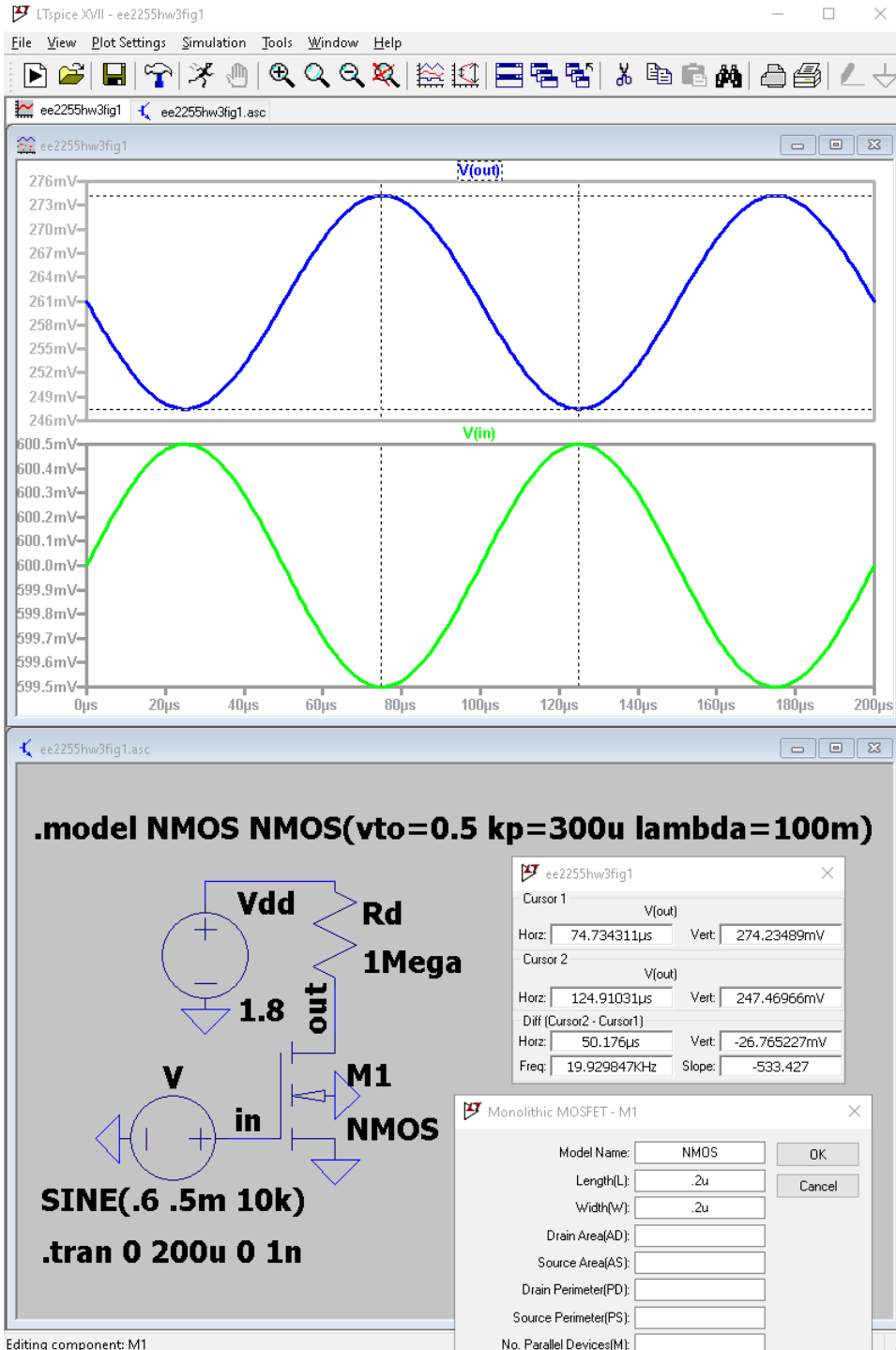

1. (b)

$V_{ds} = 0.260869 \text{ V}$

$V_{gs} = 0.6 \text{ V}$

$V_{th} = 0.5 \text{ V}$

$0.260869 > 0.6 - 0.5$

NMOS is in saturation region

--- Operating Point ---

| | | |
|-----------------|----------------------|-----------------------|
| V(n001): | 1.8 | voltage |
| V(out): | 0.260869 | voltage |
| V(in): | 0.6 | voltage |
| Id(M1): | 1.53913e-006 | device_current |
| Ig(M1): | 0 | device_current |
| Ib(M1): | -2.70869e-013 | device_current |
| Is(M1): | -1.53913e-006 | device_current |
| I(Rd): | 1.53913e-006 | device_current |
| I(Vdd): | -1.53913e-006 | device_current |
| I(V): | 0 | device_current |

1. (c)

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$I_D = \frac{1}{2} 300 \cdot 10^{-6} \frac{0.2 \cdot 10^{-6}}{0.2 \cdot 10^{-6}} (0.6 - 0.5)^2 (1 + 100 \cdot 10^{-3} \times V_{DS}) \quad \text{①}$$

$$V_{DD} - V_{DS} = I_D R_D$$

$$1.8 - V_{DS} = I_D \cdot 10^6 \quad \text{②}$$

解聯立①② 得 $V_{DS} = 0.26087 \text{ V}$

$$r_o = \left[\frac{\partial}{\partial V_{DS}} I_D \right]^{-1}$$

$$= \left[\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda \right]^{-1}$$

$$= \left[\frac{1}{2} 300 \cdot 10^{-6} \frac{0.2 \cdot 10^{-6}}{0.2 \cdot 10^{-6}} (0.6 - 0.5)^2 100 \cdot 10^{-3} \right]^{-1}$$

$$= 6666667 \quad \Omega$$

1. (d)

$$\begin{aligned}
 g_m &= \frac{\partial}{\partial V_{GS}} I_D \\
 &= \frac{\partial}{\partial V_{GS}} \left[\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \right] \\
 &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) \\
 &= 300 \cdot 10^{-6} \frac{0.2 \cdot 10^{-6}}{0.2 \cdot 10^{-6}} (0.6 - 0.5) (1 + 100 \cdot 10^{-3} \times 0.26087) \\
 &= 0.00003078261 \quad \Omega^{-1}
 \end{aligned}$$

$$\begin{aligned}
 A_v &= -g_m (R_D \parallel r_o) \\
 &= -0.00003078261 \times \frac{10^6 \times 6666667}{10^6 + 6666667} \\
 &= -26.767
 \end{aligned}$$

26.765 和 26.767 的誤差為 0.7‰
很準確


2. (a)

$$W = L = 0.2 \mu\text{m}$$

$$\text{Gate bias} = 0.6 \text{ V}$$

$$\text{Loading resistor} = 1 \text{ M}\Omega$$

$$\text{Voltage gain} = 0.88082 > 0.8$$

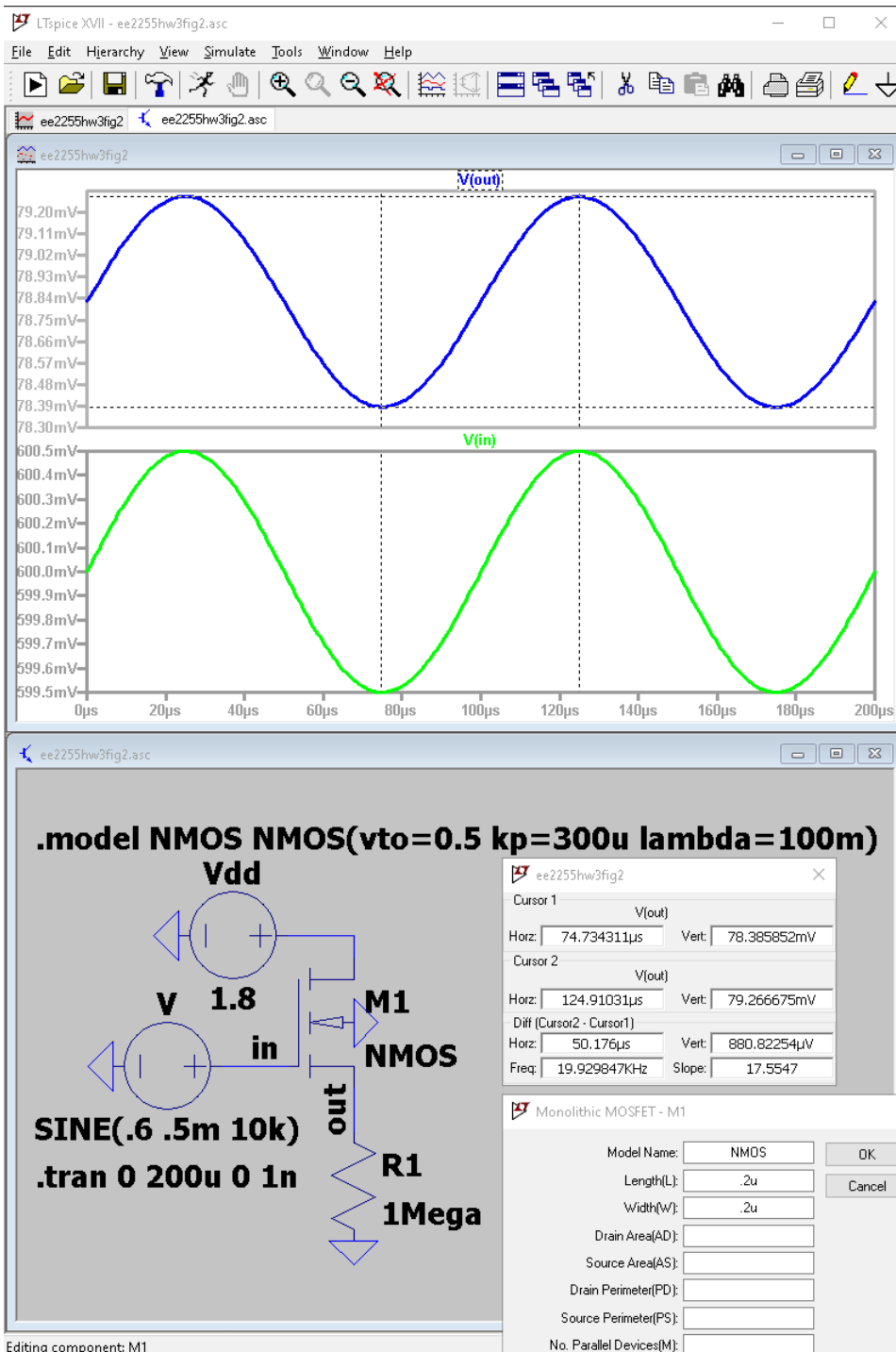

2. (b)

$$V_{ds} = 1.8 - 0.078826 = 1.721174 \text{ (V)}$$

$$V_{gs} = 0.6 - 0.078826 = 0.521174 \text{ (V)}$$

$$V_{th} = 0.5 \text{ V}$$

$$1.721174 > 0.521174 - 0.5$$

NMOS is in saturation region

--- Operating Point ---

| | | |
|-----------------|----------------------|-----------------------|
| V(n001): | 1.8 | voltage |
| V(in): | 0.6 | voltage |
| V(out): | 0.0788262 | voltage |
| Id(M1): | 7.88282e-008 | device_current |
| Ig(M1): | 0 | device_current |
| Ib(M1): | -1.89835e-012 | device_current |
| Is(M1): | -7.88263e-008 | device_current |
| I(R1): | 7.88262e-008 | device_current |
| I(Vdd): | -7.88281e-008 | device_current |
| I(V): | 0 | device_current |

2. (c)

$$V_{DD} = V_{DS} + V_S$$

$$1.8 = V_{DS} + V_S \quad \text{①}$$

$$V_S = I_D \times R_S$$

$$V_S = I_D \times 10^6 \quad \text{②}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$I_D = \frac{1}{2} 300 \cdot 10^{-6} \frac{0.2 \cdot 10^{-6}}{0.2 \cdot 10^{-6}} (0.6 - V_S - 0.5)^2 (1 + 100 \cdot 10^{-3} V_{DS}) \quad \text{③}$$

解聯立 ① ② ③ 得 $V_{DS} = 1.72117 \text{ V}$, $V_S = 0.078826 \text{ V}$

$$r_o = \left[\frac{\partial I_D}{\partial V_{DS}} \right]^{-1}$$

$$= \left[\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_S - V_{TH})^2 \lambda \right]^{-1}$$

$$= \left[\frac{1}{2} 300 \cdot 10^{-6} \frac{0.2 \cdot 10^{-6}}{0.2 \cdot 10^{-6}} (0.6 - 0.078826 - 0.5)^2 100 \cdot 10^{-3} \right]^{-1}$$

$$= 1.48697 \cdot 10^8$$

2. (d)

$$\begin{aligned}
 g_m &= \frac{\partial}{\partial V_{GS}} I_D \\
 &= \mu_n C_{ox} \frac{W}{L} (V_G - V_S - V_{TH}) (1 + \lambda V_{DS}) \\
 &= 300 \cdot 10^{-6} \frac{0.2 \cdot 10^{-6}}{0.2 \cdot 10^{-6}} (0.6 - 0.078826 - 0.5) (1 + 100 \cdot 10^{-3} \times 1.72117) \\
 &= 7.4455 \cdot 10^{-6}
 \end{aligned}$$

$$\begin{aligned}
 A_v &= \frac{R_D \parallel r_o}{g_m^{-1} + (R_D \parallel r_o)} \\
 &= \frac{\frac{10^6 \times 1.48697 \cdot 10^8}{10^6 + 1.48697 \cdot 10^8}}{(7.4455 \cdot 10^{-6})^{-1} + \frac{10^6 \times 1.48697 \cdot 10^8}{10^6 + 1.48697 \cdot 10^8}} \\
 &= 0.88089
 \end{aligned}$$

0.88082 和 0.88089 的誤差為 0.8‰
很準確