

# 1 AC Analysis

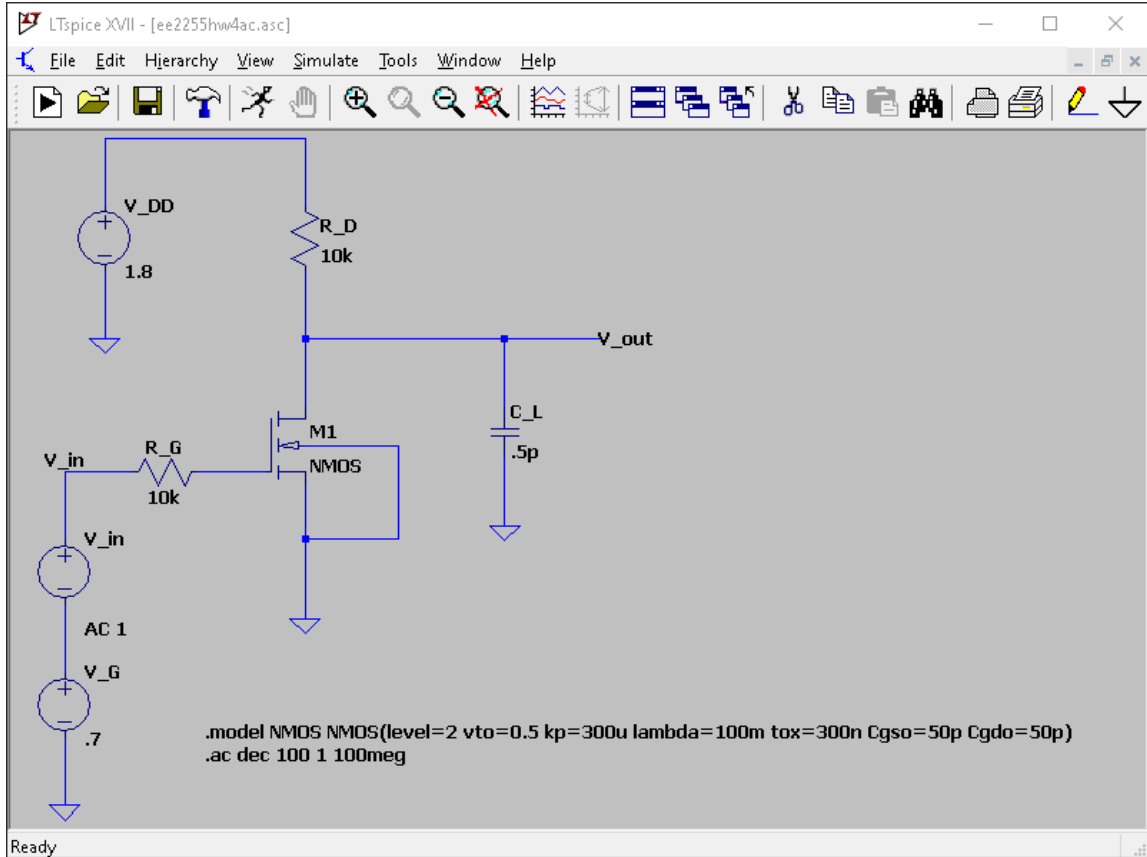


Figure 1: This is the schematic for the AC analysis. I designed the gate voltage and the drain resistor to be  $V_G = 0.7V$  and  $R_D = 10k\Omega$  respectively.

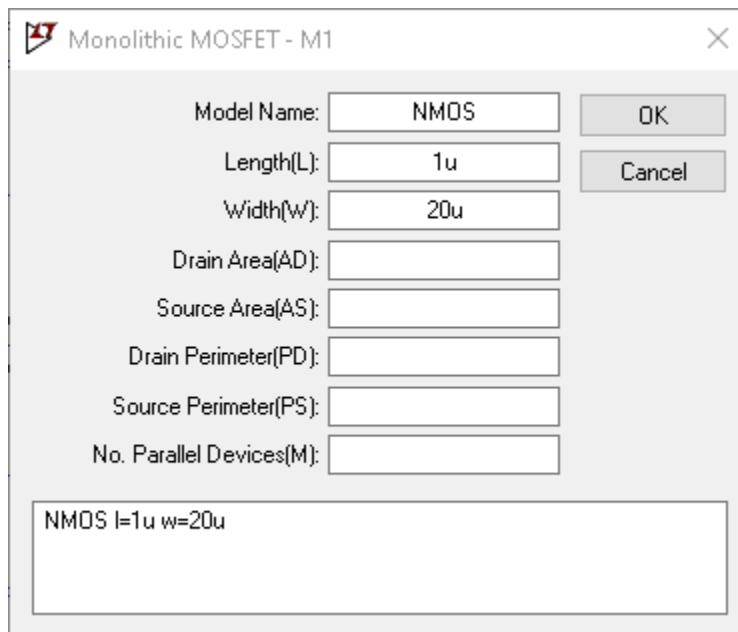


Figure 2: I designed the width of the NMOS to be  $W = 20\mu m$ .

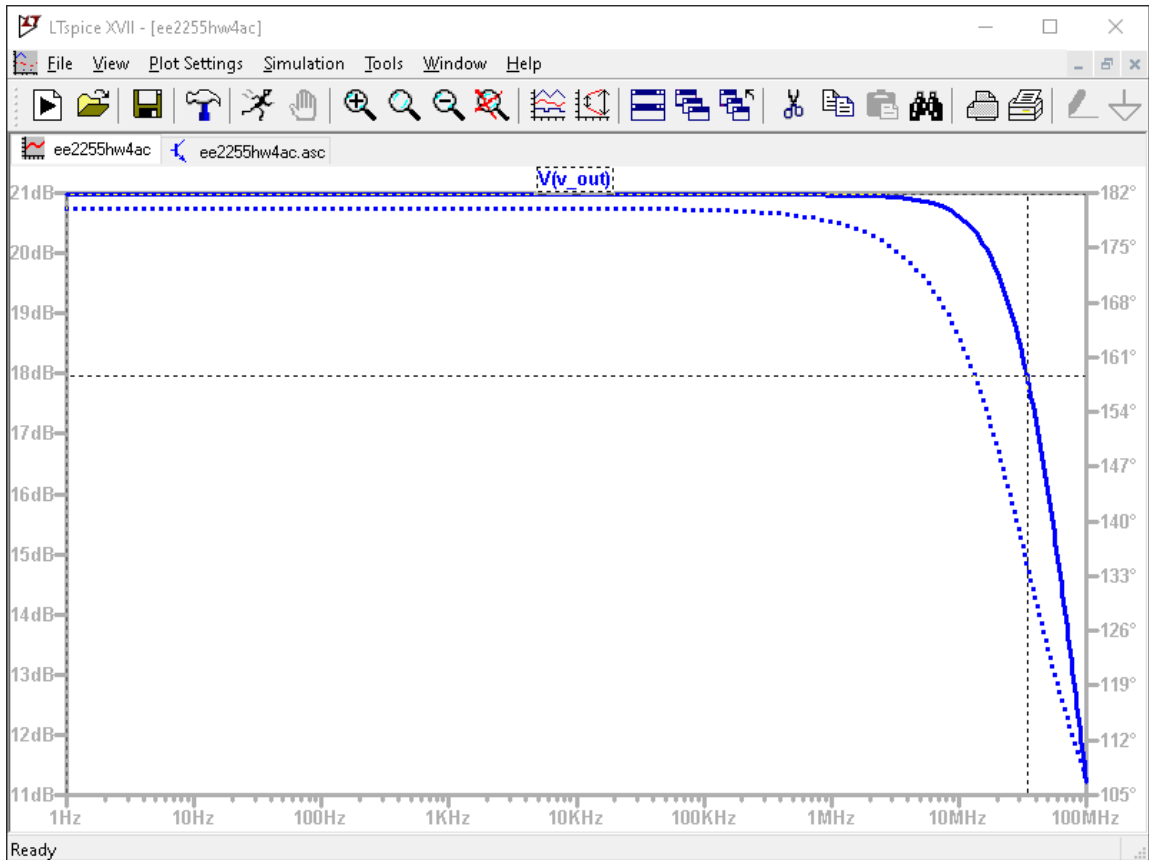


Figure 3: Cursor 1 and 2 in the bode plot are placed at 1Hz and 34.35MHz respectively.

 


Figure 4: The data extracted by cursor 1 show that the small-signal gain at low frequency is larger than 20dB. The ratio shows that the -3dB-bandwidth is wider than 30MHz.

$$\text{small-signal gain } (V/V) = 10^{\frac{20.967592\text{dB}}{20\text{dB}}} = 11.178 > 10$$

## 2 Transient Analysis

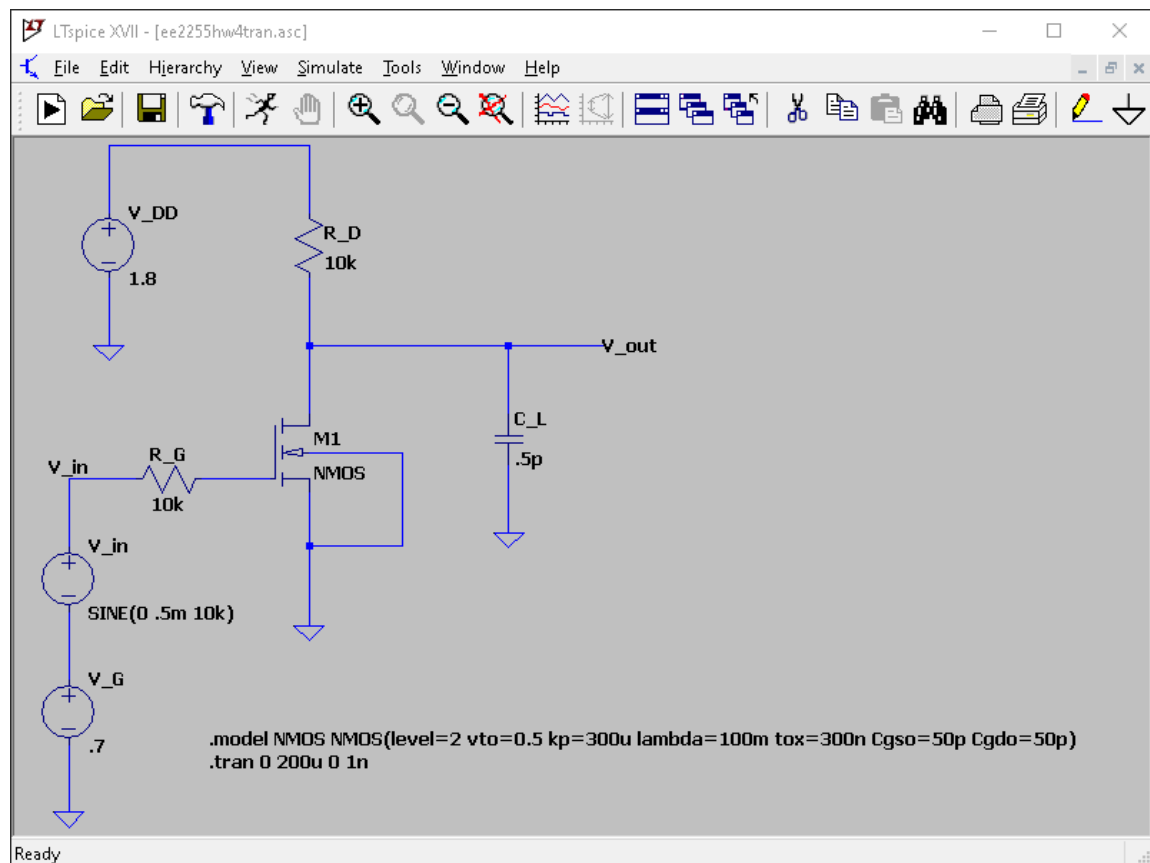


Figure 5: This is the schematic for the transient analysis. The only differences from Figure 1 are the voltage source syntax SINE(0 .5m 10k) and the simulation command .tran 0 200u 0 1n set.

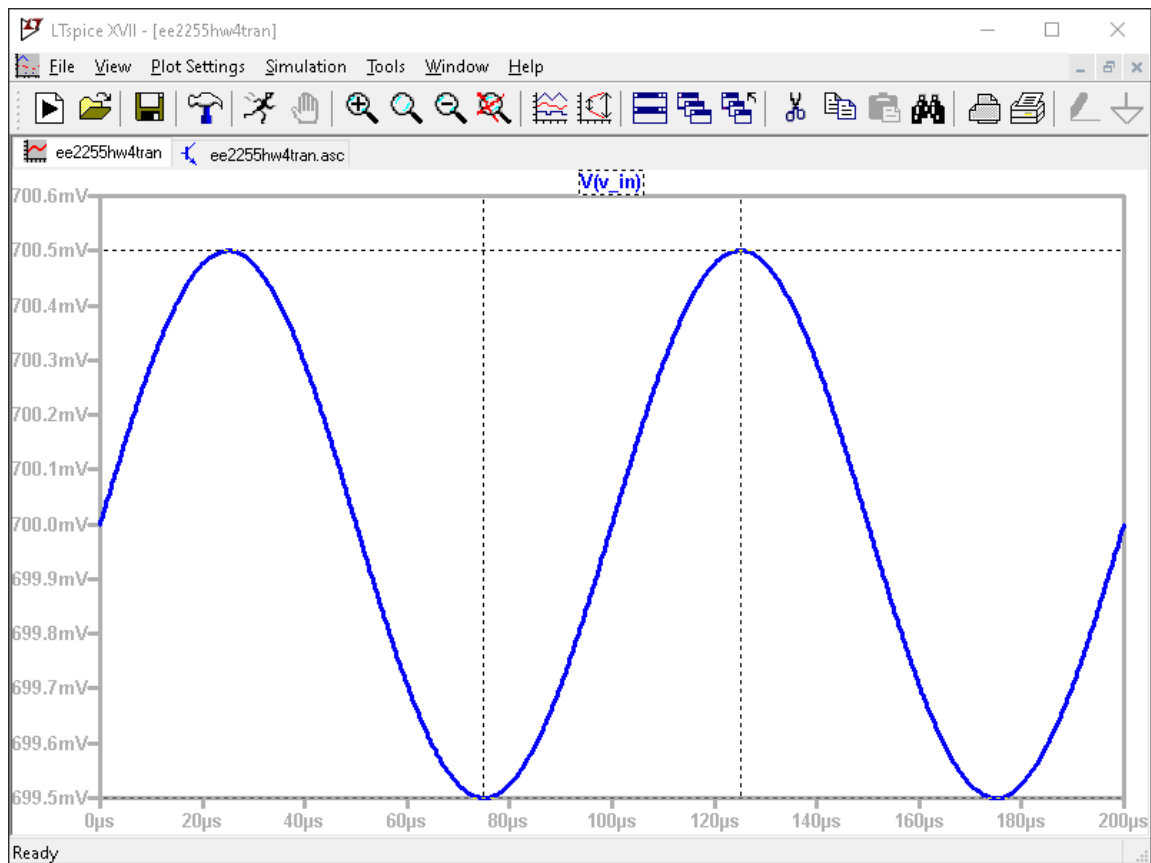


Figure 6: Cursor 1 and 2 are placed at the wave trough and the wave crest respectively.

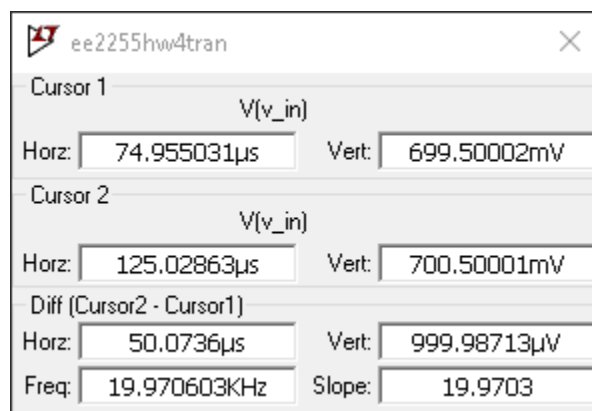


Figure 7:  $V_{in}$  is a sine wave with frequency  $f = 10kHz$  and peak-to-peak amplitude  $V_{p-p} = 1mV$ .

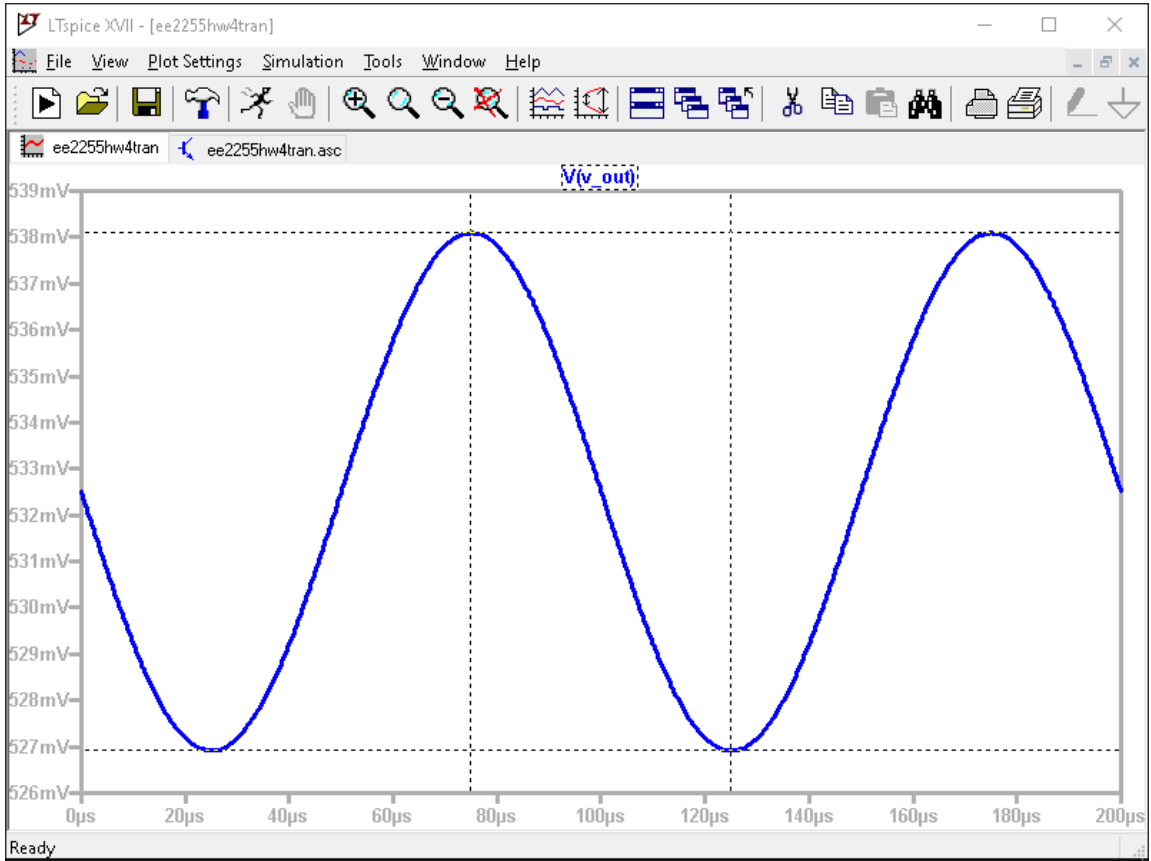


Figure 8: Cursor 1 and 2 are placed at the wave crest and the wave trough respectively.

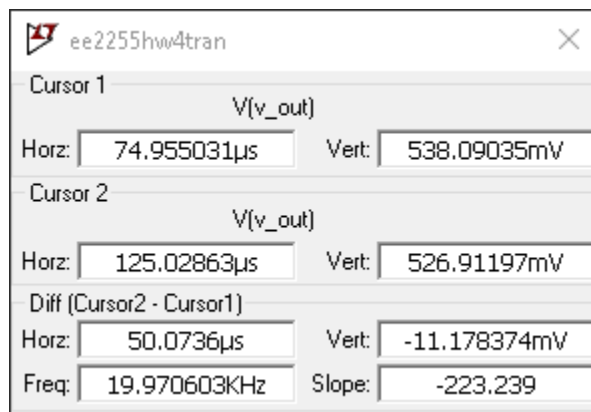


Figure 9: The diff shows that the small-signal voltage gain is larger than 10V/V.

The SPICE directive in Figure 5 sets  $V_{TH} = v_{to} = 500.0mV$ . The data extracted by cursor 1 in Figure 7 show that  $\min(V_{GS}) = 699.5mV$ . The gate voltage exceeds the threshold voltage so

$$V_{GS} > V_{TH}$$

holds. The data extracted by cursor 2 in Figure 7 show that  $\max(V_{GS}) = 700.5mV$ . The data extracted by cursor 2 in Figure 9 show that  $\min(V_{DS}) = 526.9mV$ . In the worse case scenario,  $\max(V_{OV}) = \max(V_{GS}) - V_{TH} = 200.5mV$ . The drain voltage exceeds the overdrive voltage so

$$V_{DS} > V_{OV}$$

holds. Hence the NMOS operates in saturation region.

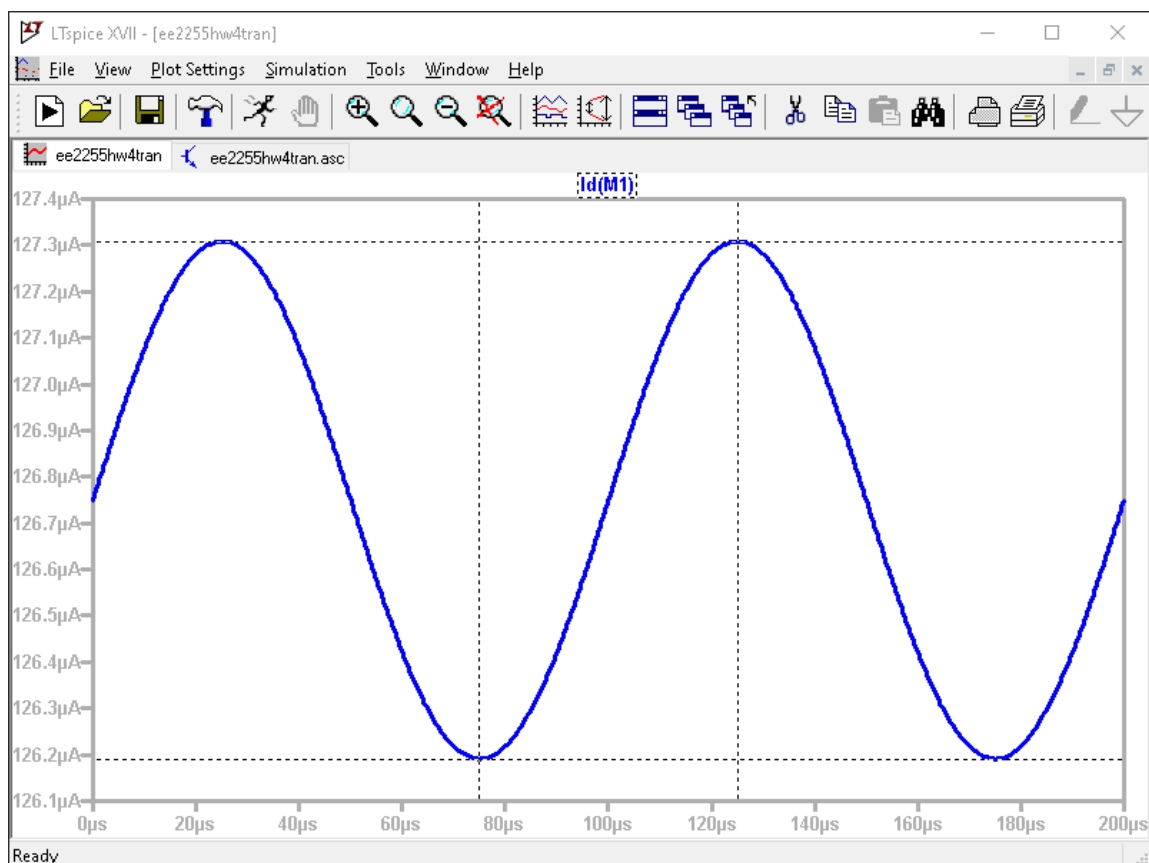


Figure 10: Cursor 1 and 2 are placed at the wave trough and the wave crest respectively.

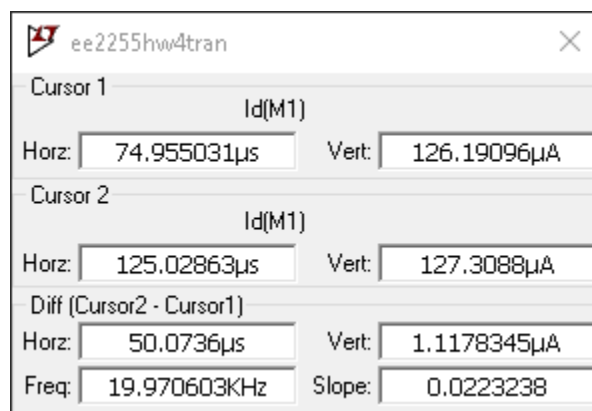


Figure 11: The data extracted by cursor 1 and 2 show that  $\min(I_D) = 126.2 \mu A$  and  $\max(I_D) = 127.3 \mu A$  respectively. The DC offset of the drain current is  $[\min(I_D) + \max(I_D)]/2 = 126.75 \mu A$ .

### 3 Figure of Merit

The figure of merit of the common-source amplifier with gate voltage  $V_G = 0.7V$ , drain resistor  $R_D = 10k\Omega$ , and NMOS width  $W = 20\mu m$  is

$$\begin{aligned} \text{FoM} &= \frac{\text{gain}(V/V) \times \text{bandwidth}(MHz)}{\text{drain-current}(mA)} \\ &= \frac{11.178 \times 34.35}{0.12675} \approx 3029 > 800. \end{aligned}$$

### Appendix

For the interested reader, I provide here a brief introduction to my attempt to maximize the figure of merit, although these are not referred to elsewhere in the homework assignment. Through some tedious fine-tuning, I found a local maximum for the function

$$\text{FoM}(V_G, R_D, W)$$

at

$$V_G \approx 0.5135V$$

$$R_D \approx 7.2863k\Omega$$

$$W \approx 282.5\mu m$$

subject to the specifications

$$\text{gain}(V_G, R_D, W) > 20dB$$

$$\text{bandwidth}(V_G, R_D, W) > 30MHz.$$

The figure of merit of the common-source amplifier with gate voltage  $V_G = 0.5135V$ , drain resistor  $R_D = 7.2863k\Omega$ , and NMOS width  $W = 282.5\mu m$  is

$$\begin{aligned} \text{FoM} &= \frac{\text{gain}(V/V) \times \text{bandwidth}(MHz)}{\text{drain-current}(mA)} \\ &= \frac{10.000^+ \times 30.000^+}{0.0093528} \approx 32076 \gg 800, \end{aligned}$$

where the data were extracted by the cursors as shown in Figure 12 and Figure 13.

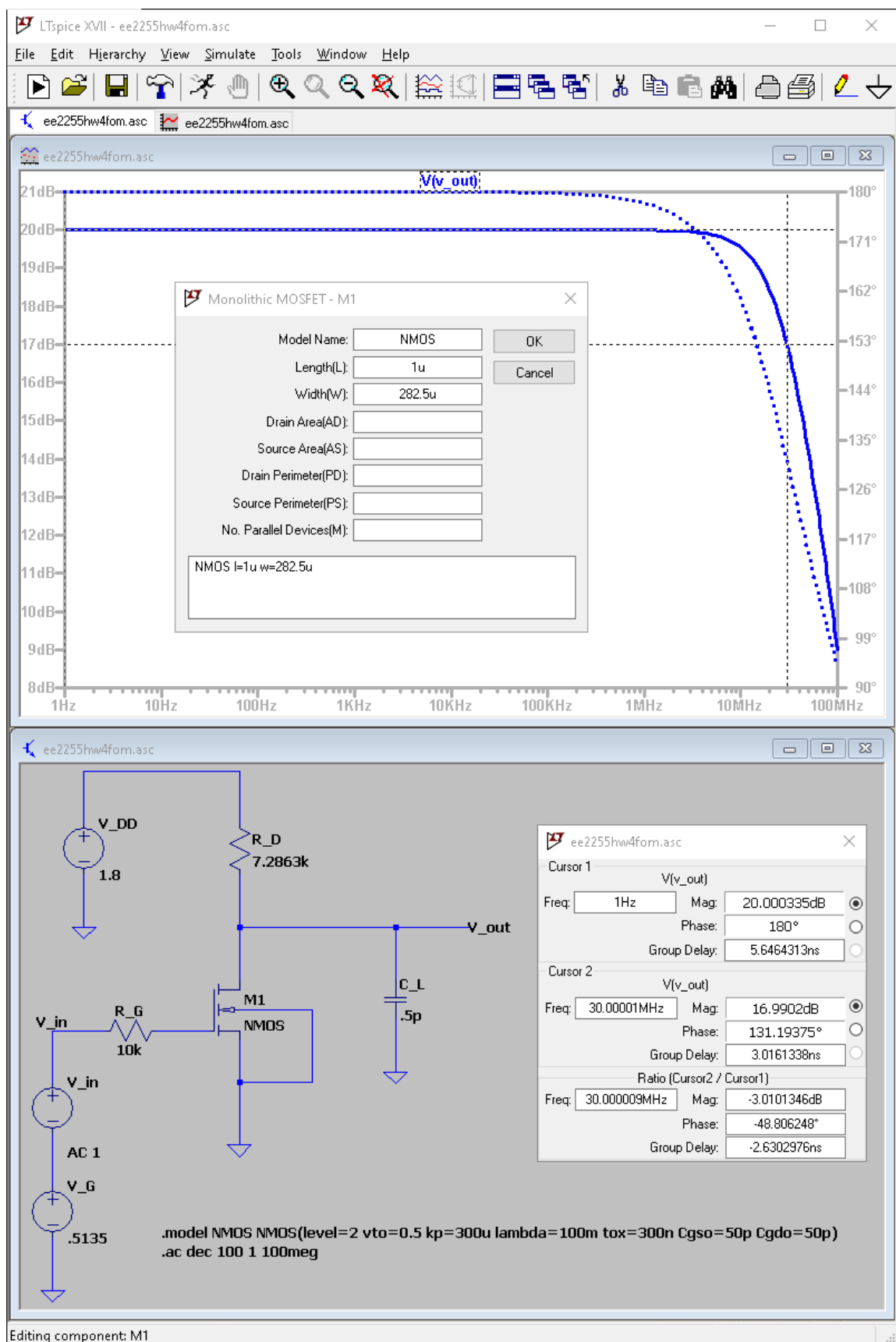


Figure 12: After fine-tuning, the data extracted by cursors show that the small-signal gain is a little bit larger than 20dB and the -3dB-bandwidth is a little bit wider than 30MHz. Note that the exact value of the half-power bandwidth is  $20 \log_{10} \frac{1}{\sqrt{2}} \approx -3.0103$ .



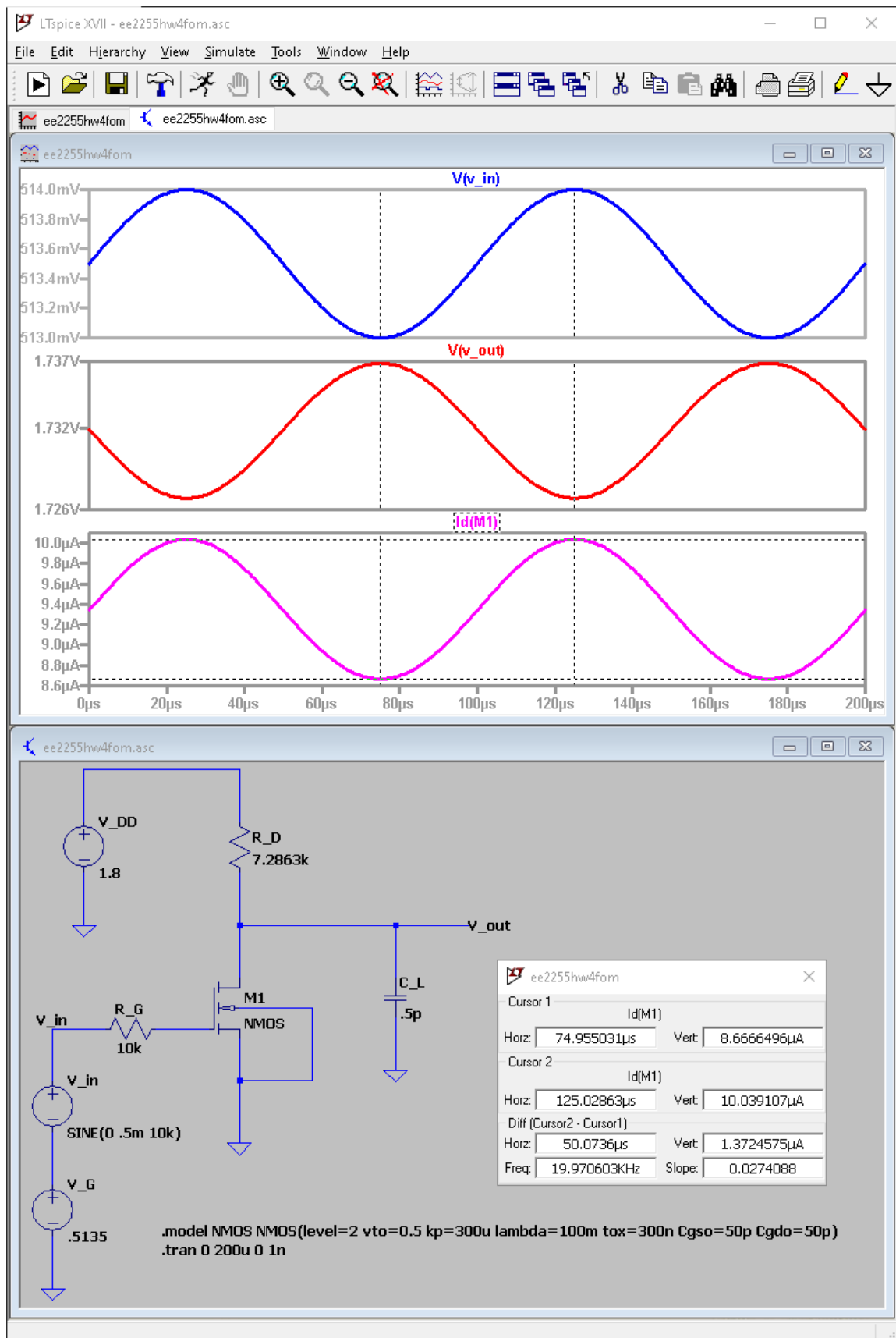


Figure 13: The data extracted by cursor 1 and 2 show that  $\min(I_D) = 8.6666\mu A$  and  $\max(I_D) = 10.039\mu A$  respectively. The DC offset of the drain current is  $[\min(I_D) + \max(I_D)]/2 = 9.3528\mu A$ . Note that  $1726mV > 514mV - 500mV$  and  $513mV > 500mV$  so the threshold voltage, the gate voltage, and the drain voltage satisfy  $V_{DS} > V_{OV}$  and  $V_{GS} > V_{TH}$  in the worst case scenario. Hence the NMOS operates in saturation region.