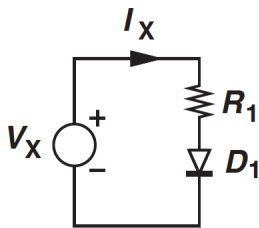


Student ID:

Name:

1. There is a circuit as shown in Fig. 1. When we input the  $V_x$  as 1V, the current  $I_x$  is 0.2mA. When we input the  $V_x$  as 2V,  $I_x$  is 0.5mA.
  - (a) Please calculate the values of resistance of  $R_1$  and  $I_s$  of diode  $D_1$ .
  - (b) Please use the large signal model to calculate the  $I_x$  current, when we input the  $V_x$  as 2.05V.
  - (c) Please use the small signal model to repeat (b) and compare the  $I_x$  results of (b) and (c).
  - (d) Please use the  $R_1$  value and  $I_s$  of diode  $D_1$  in (a), and like (b) use LTspice operation point analysis to get the  $I_x$  with  $V_x$  as 2.05V.



2. Fig. 2 is a full-wave rectifier. In this circuit  $R_1=100\text{ K}\Omega$ ,  $C_1=50\text{pF}$ , and  $V_{in}$  is a 1MHz sinusoidal waveform from +3V to -3V.
  - (a) Please plot the input and differential output voltage, when constant voltage model ( $V_{D,on}=0.8\text{V}$ ) are used for diodes  $D_1$ - $D_4$ .
  - (b) Please calculate the peak and the ripple voltages and mark them at the output waveform of (a).
  - (c) Please use the constant voltage model in (a) for LTspice transient analysis to simulate this circuit. And compare the simulation results with (b).

