

Student ID:

Name:

Notice

- (1) Delay is not allowed. (-100pt)
- (2) We use LTspice transient analysis to simulate both cases. You must set **stop time = 200u** and **maximum timestep = 1n**. (-5pt)
- (3) The BJT model is set by the directive: **.model NPN NPN(Is=2e-16 Bf=80)**. (-10pt)
- (4) You must attach screenshots of circuit and output waveform. (-10pt)
- (5) You must extract the output amplitude by cursor. (-10pt)
- (6) Please check the hand-writing result in your photo is clear. (-5pt or -10pt)

1. Fig. 1 shows the common-emitter amplifier with V_{CC} as 2.5 V. V_{in} is a 10 KHz sinusoidal waveform with amplitude equal to 0.5 mV ($V_{p-p} = 1$ mV).
 - (a) Please design your V_B and R_C to make the voltage gain larger than 10 V/V. Note that voltage gain is the ratio of output amplitude to input amplitude.
 - (b) Please check the BJT operates in "active mode," and display it ($V_{CE} > V_{BE} > 0$).
 - (c) Please use small signal model to calculate its small signal gain.
 - (d) Compare (a) and (c) results.

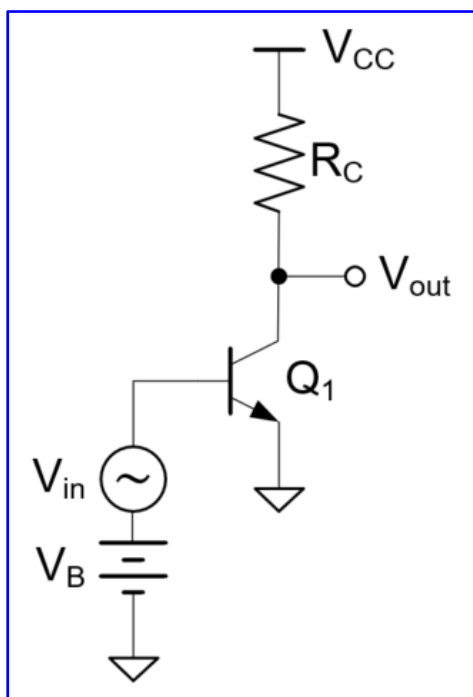


Fig. 1

2. Fig. 2 shows the common-collector amplifier (emitter follower) with V_{CC} as 2.5 V. V_{in} is a 10 KHz sinusoidal waveform with amplitude equal to 0.5 mV ($V_{p-p} = 1$ mV).
- Please design your V_B and R_E to make the voltage gain larger than 0.8 V/V. Note that voltage gain is the ratio of output amplitude to input amplitude.
 - Please check the BJT operates in "active mode," and display it ($V_{CE} > V_{BE} > 0$).
 - Please use small signal model to calculate its small signal gain.
 - Compare (a) and (c) results.


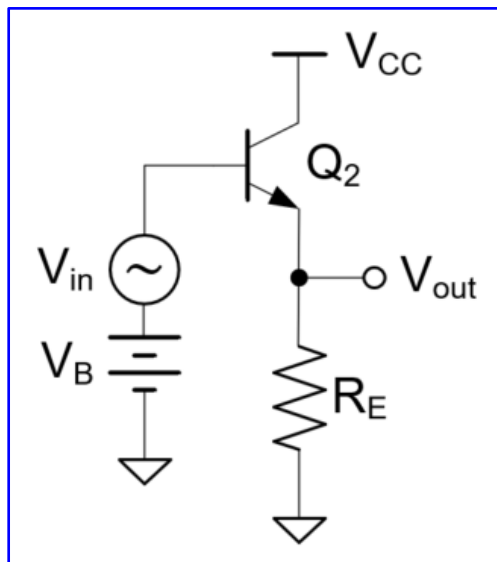



Fig. 2

Appendix

(1) Setup of Transient Analysis

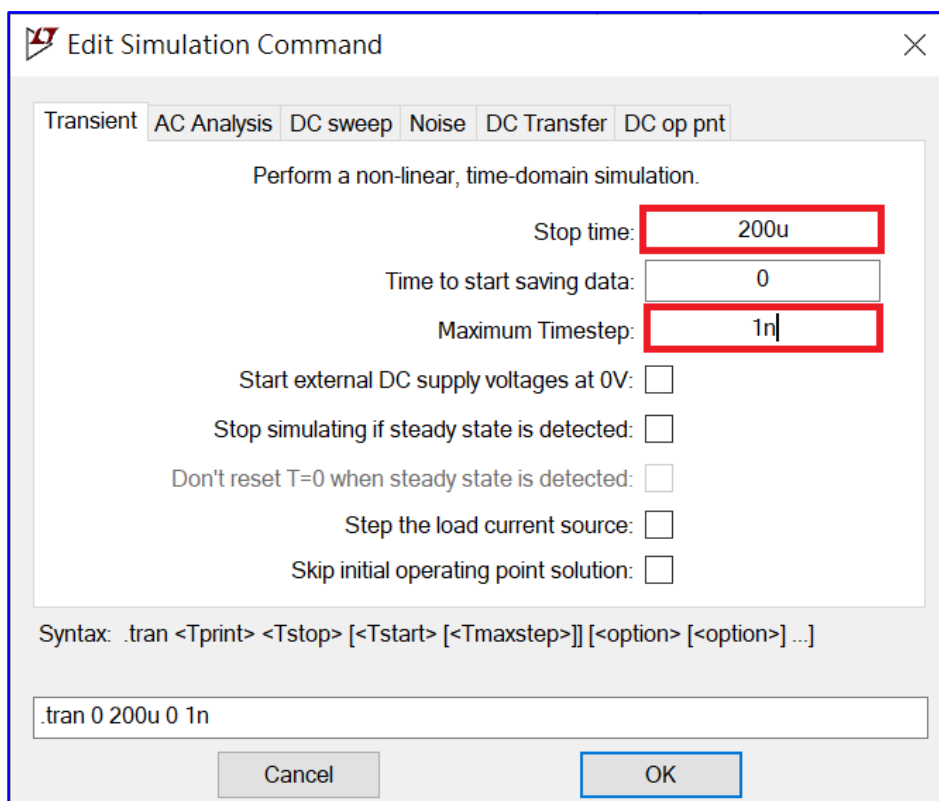

(2) Waveform of Sinusoidal Input

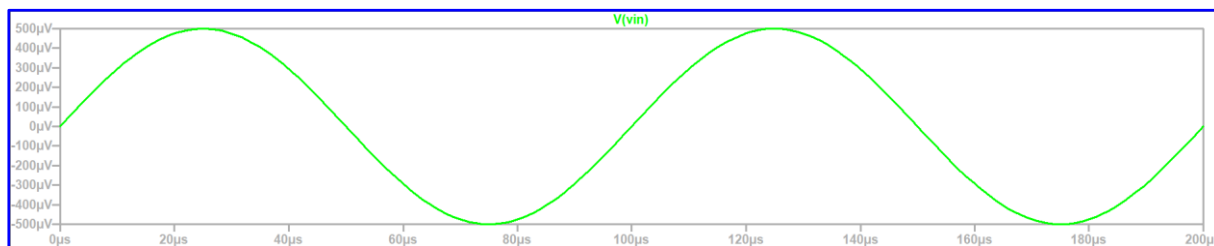

(3) Setup of BJT Model

