

HW3 (Chapter 6, 7)

Student ID: _____

Name: _____

Notice

- (1) Delay is not allowed. (-100pt)
- (2) We use LTspice **transient** analysis to see the voltage gain of signal. You must set **stop time= 200u** and **maximum timestep = 1n**. (-5pt)
- (3) The NMOS model is set by the directive:
.model NMOS NMOS(vto=0.5 kp=300u lambda=100m). (-10pt)
- (4) You must attach the **screenshots of your NMOS size** (like Fig. 5). (-10pt)
- (5) You must attach screenshots of circuit and output waveform. (-10pt)
- (6) You must extract the output amplitude by cursor. (-10pt)
- (7) Please check the hand-writing result in your photo is **clear**. (-5pt or -10pt)

1. Fig. 1 shows the common-source amplifier with V_{DD} as 1.8 V. V_{in} is a 10KHz sinusoidal waveform with 0.5mV amplitude ($V_{p-p} = 1$ mV) .

 


Fig. 1

- (a) Please design your

W and L of NMOS (for 0.18 μ m technology both W and L should be longer than 0.18 μ m)

Gate bias V_G

Loading resistor R_D

You should achieve the voltage gain larger than 10 V/V. Note that the voltage gain means the

ratio of output amplitude to input amplitude.

- (b) Please use **.OP** to show your output operating point and check your NMOS must be operating in “saturation region” ($V_{DS} > V_{GS} - V_{TH}$).
- (c) Base on λ and I_D . Please hand-calculate r_o of NMOS.
- (d) Please use small signal model to calculate its voltage gain (r_o is NOT neglectable). Compare the results between hand-calculation and your simulation in (a).

2. Fig. 2 shows the common-drain amplifier (source follower) with V_{DD} as 1.8 V. V_{in} is a 10KHz sinusoidal waveform with 0.5mV amplitude ($V_{p-p} = 1$ mV).

 


Fig. 2

- (a) Please design your
W and L of NMOS (for 0.18 μ m technology both W and L should be longer than 0.18 μ m)
Gate bias V_G
Loading resistor R_S

You should achieve the voltage gain larger than 0.8 V/V. Note that the voltage gain means the ratio of output amplitude to input amplitude.

- (b) Please use **.OP** to show your output operating point and check your NMOS must be operating in “saturation region” ($V_{DS} > V_{GS} - V_{TH}$).
- (c) Please use small signal model to calculate its voltage gain. Compare the results between hand-calculation and your simulation in (a).

Appendix

(1) How to find NMOS schematic

Please choose **nmos4** and short the “body port” to ground

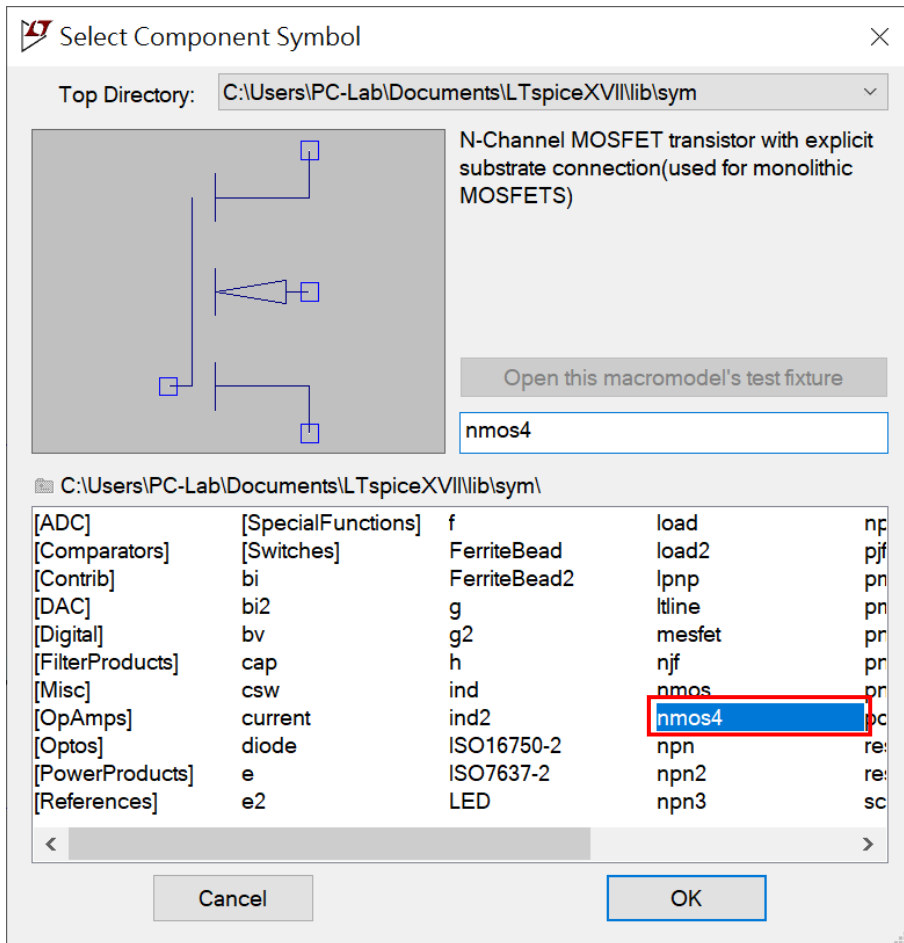


Fig. 3

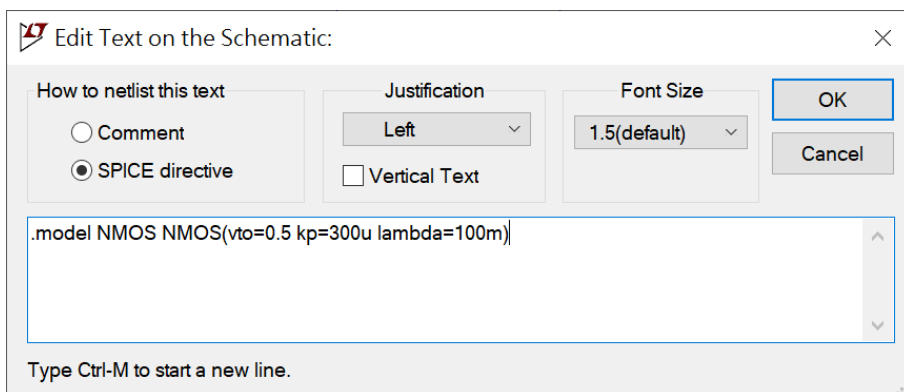


Fig. 4

In the model, vto means V_{TH} , kp means $\mu_n C_{ox}$, lambda means λ .

(2) How to change W and L of NMOS?

Right click on the NMOS schematic

Monolithic MOSFET - M1

Model Name:

Length(L):

Width(W):

Drain Area(AD):

Source Area(AS):

Drain Perimeter(PD):

Source Perimeter(PS):

No. Parallel Devices(M):

NMOS l=2u w=20u

Fig. 5