

Part1_B卷

姓名: 林靖 交卷時間 (IP): 2021-06-22 10:55 分數: 35 / 40

恭喜您，通過測驗的及格門檻 24 分!

溫馨小提醒

- (0) 此考卷為**B卷** 請確認自己學號為**偶數**
- (1) 建議同學準備好**計算紙** 寫考卷時自己標記題號並書寫計算過程
除了方便同學檢查自己答案是否有填寫正確之外
當題目有連貫性時 也可以幫助同學快速回顧之前答題時的想法
- (2) 請同學**把握考試時間**
不像現場考試 助教沒辦法提醒同學再過幾分鐘收卷
建議同學先把會寫的題目寫完 再回頭處理比較困難的題目
- (3) 填充題務必將答案四捨五入到**小數點第一位** (整數也請表示到小數第一位)
有特別標記需要填**正負號**的題目 請不要忘記
單位和**科學記號**都需要特別注意
- (4) 測試題範例
 $1+10 = 11.0$
 $10-2-8 = 0.0$ (add +/-)
 $1.5*1.5 = +2.3$ (add+/-)
 $1.2*1.2 = 1.4$


題組 (共 4 題)

Problem Set 1-1

單選題 [8pts]

Please answer **problem 1~4** according to Circuit A.

Circuit A is a common gate circuit. If all the transistors are in saturation region and ignore the channel length modulation, V_{DD} , V_B , V_G voltages are fixed, to **decrease the voltage gain $|(V_{out}/V_{in})|$,**

 

Circuit A

The load resistor R_D has to

- A. increase
- B. decrease
- C. no change

2

The common gate size $(W/L)_2$ has to

- A. increase
- B. decrease
- C. no change

2

The bias transistor size $(W/L)_1$ has to

- A. increase
- B. decrease
- C. no change

2

The source impedance R_S has to

- A. increase
- B. decrease
- C. no change

2


題組 (共 4 題)

Problem Set 1-2

單選題 [8pts]

Please answer **problem 5~8** according to Circuit B.

 Circuit B is an emitter degenerated amplifier. If the transistor Q_1 is in active region, V_{CC} , V_B voltages are fixed, when the **degeneration resistor R_E decreases**,



Circuit B

The voltage gain will

- A. increase
- B. decrease
- C. no change

The input impedance will

- A. increase
- B. decrease
- C. no change

The output impedance will

- A. increase
- B. decrease
- C. no change

The output swing range will

- A. increase
- B. decrease
- C. no change

正確答案: **C**

題組 (共 4 題)

Problem Set 2:

填充題 [21pts]

單選題 [3pts]

Please answer **problem 9-12** according to Circuit C.


Please use the following parameters.

$$\mu_n C_{ox} = 0.125 \text{ mA/V}^2, \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 100, V_{TH} = 0.4V,$$

$$\lambda_1 = \lambda_2 = 0, \lambda_3 = \lambda_4 = 0.1 \text{ V}^{-1},$$

$$V_{DD} = 2.0\text{V}, R_{D1} = R_{D2} = 4\text{k}\Omega, I_{REF} = 0.1\text{mA}, \text{ and } \left(\frac{W}{L}\right)_3 : \left(\frac{W}{L}\right)_4 = 5:1$$

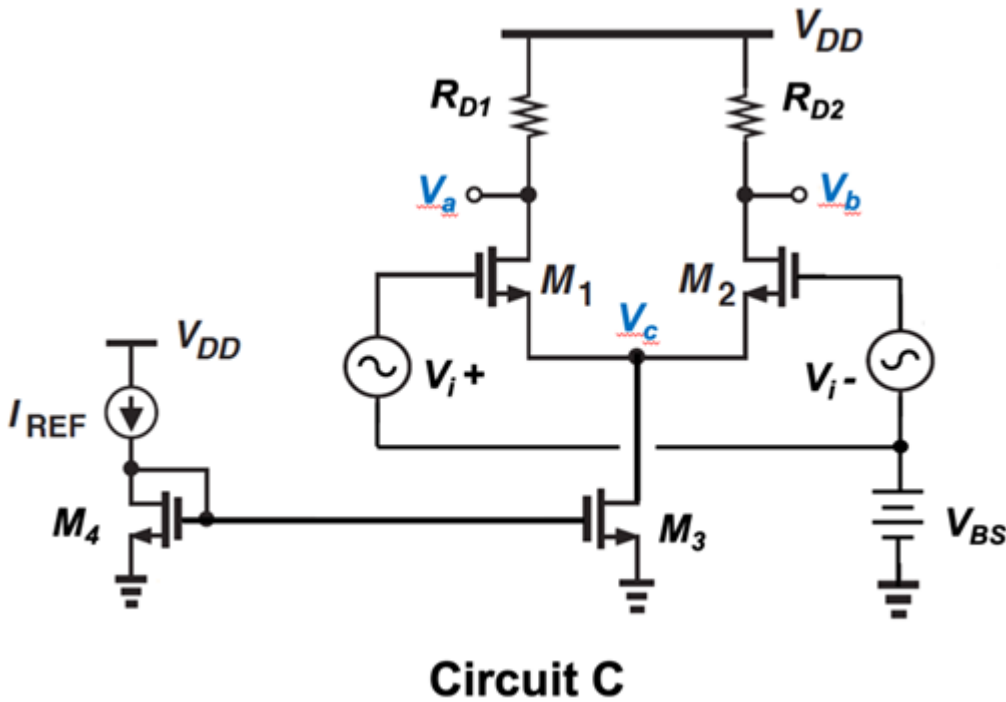In Circuit C, all the transistors are with no body effect.



If the output common mode level is 1V, and the V_{GS3} is 0.5V, the input common mode level V_{BS} has to be 0.5 **1.1** (3 分) V to make the M_1 DC current 2.5 (3 分) $\times 10^{-1}$ mA, and M_3 DC current is 5.0 (3 分) $\times 10^{-1}$ mA. (e.g, 2.19 => 2.2, 0.34 => 0.3).

The small signal differential mode voltage gain $(V_a)/(V_{i+})$ is -10.0 (3 分) V/V, voltage gain $(V_b)/(V_{i+})$ is +10.0 (3 分) V/V, voltage gain $(V_c)/(V_{i+})$ is +0.0 (3 分) V/V. (add + or - in each answer).

The small signal common mode voltage gain is -9.9 (3 分) $\times 10^{-2}$ V/V. (add + or -).

In this circuit, which is the possible way to increase the input differential mode linear range?

- A. increase RD
- B. decrease VDD
- C. increase W/L of M1 and M2
- D. increase IREF

3

Copyright © 2021 National Tsing Hua University. All rights reserved.

本網站僅作學術研究用途，不得從事商業用途，請**尊重智慧財產權**，避免任何侵權行為，勿上傳/下載未經授權之檔案資料，並依授權規範合理使用。

Please respect the intellectual property rights.

線上：172 人