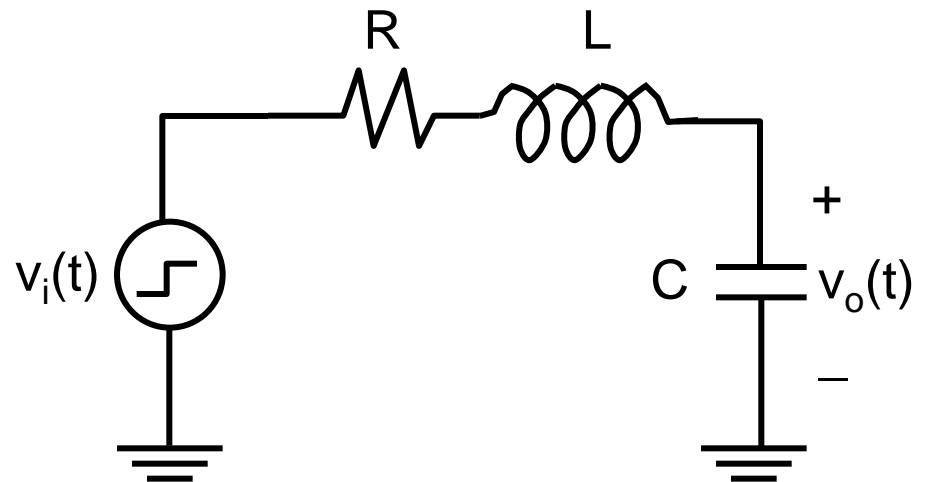
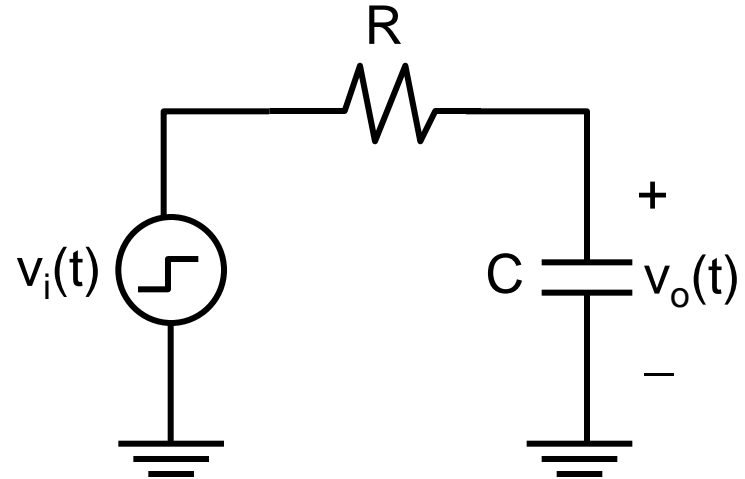
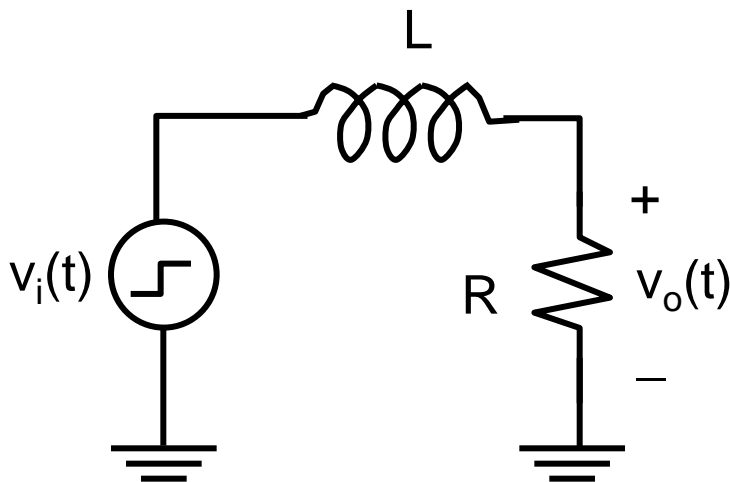

Time-Domain Responses of 1st- and 2nd-Order Circuits

張孟凡
清華大學電機系

幾個RLC組成的1st and 2nd-Order Circuits

- 如何判斷1st or 2nd-order?
 - 將 $v_o(s)/v_i(s)$ 寫出來，觀察分母的次數
 - 也可以由 $v_o(s)/v_i(s)$ 得回原本的differential equation



Example

- RLC impedances in Laplace Transform:

$$R, \frac{1}{sC} \text{ and } sL$$


- 經由阻抗分壓:

$$\frac{v_o(s)}{v_i(s)} = \frac{R}{Ls + R} \quad (\text{1st order})$$

- The original differential eqn. therefore is:


$$sL \cdot v_o(s) + R \cdot v_o(s) = R \cdot v_i(s)$$
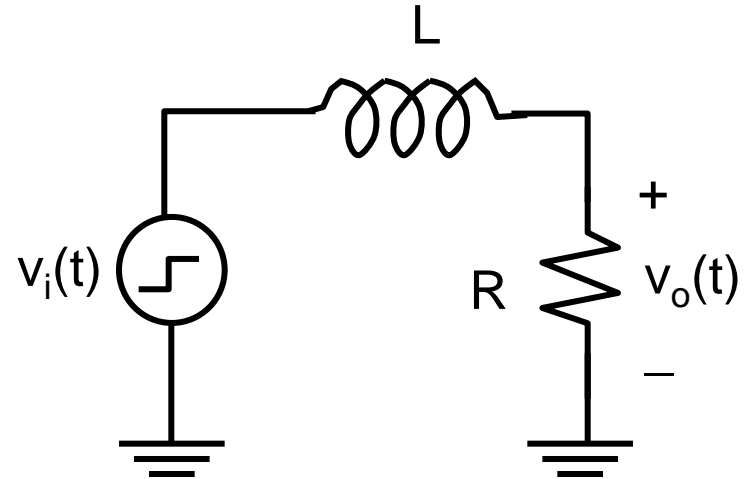
$$\text{I.L.T.} \Rightarrow L\dot{v}_o(t) + Rv_o(t) = Rv_i(t)$$



Step Response of 1st-Order RC Circuit

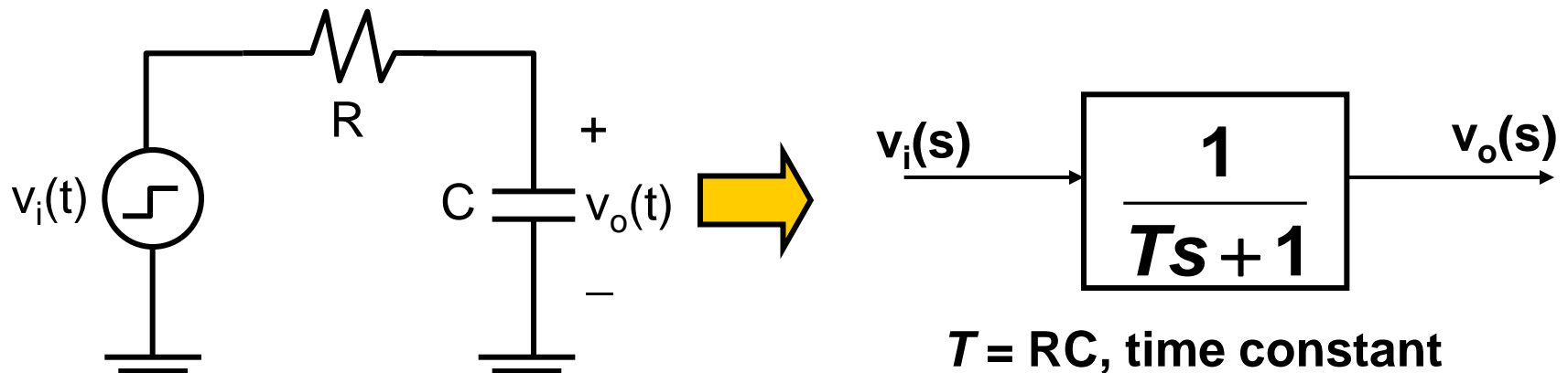- Given a unit-step input $v_i(t)$, assume $v_o(0) = 0$:




$$\frac{v_o(s)}{v_i(s)} = \frac{1}{RCs + 1}$$

$$\Rightarrow v_o(s) = \frac{1}{RCs + 1} \cdot \frac{1}{s} = \frac{1}{s} - \frac{RC}{RCs + 1} = \frac{1}{s} - \frac{1}{s + (1/RC)}$$

$$\text{Solve } v_o(t) = \left(1 - e^{-\frac{t}{RC}} \right) \cdot u(t)$$



Cont'd

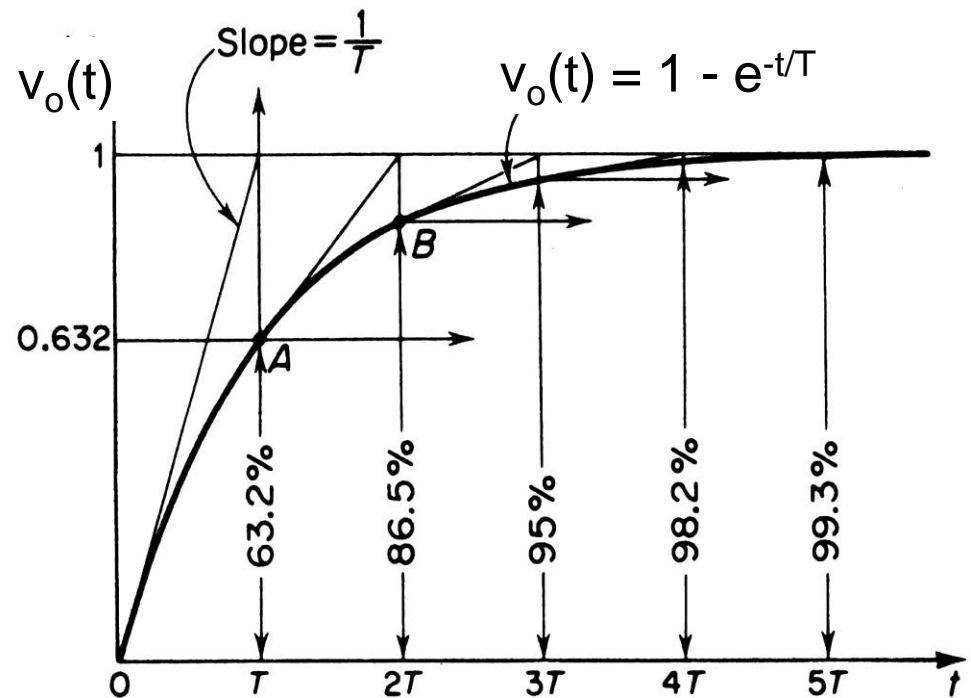- For $t = T$ ($T = RC$), the response reaches 63% of the steady state
- The error is around 0.7% after $t = 5T$



Step Response: R and C Interchanged

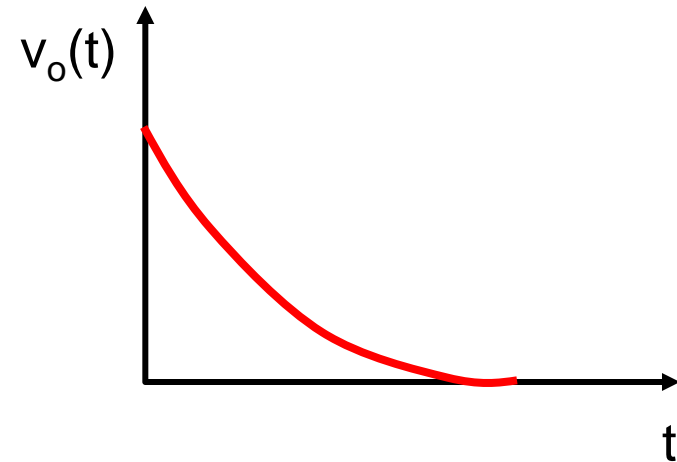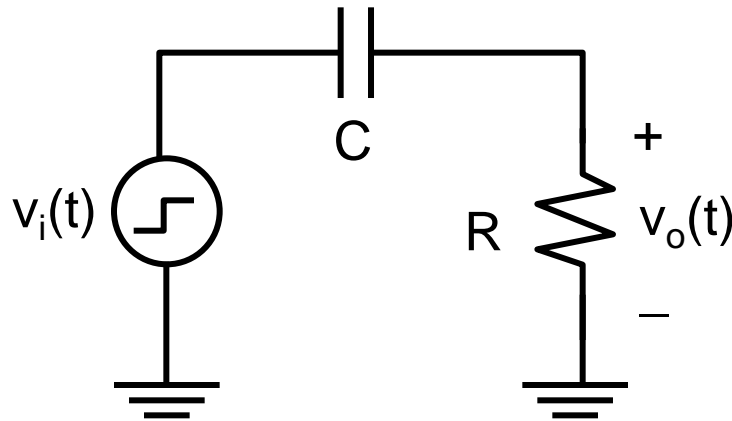- Given a step input $v_i(t)$, assume $v_o(0) = 0$:



$$\frac{v_o(s)}{v_i(s)} = \frac{RCs}{RCs + 1}$$

$$\Rightarrow v_o(s) = \frac{RCs}{RCs + 1} \cdot \frac{1}{s} = \frac{RC}{RCs + 1} = \frac{1}{s + (1/RC)}$$

$$\text{Solve } v_o(t) = e^{-\frac{t}{RC}}$$


2nd-Order RLC Circuit

- By KVL:

$$v_i = iR + L \frac{di}{dt} + v_o$$

- Substituting $i = C \cdot dv_o/dt$ gives:
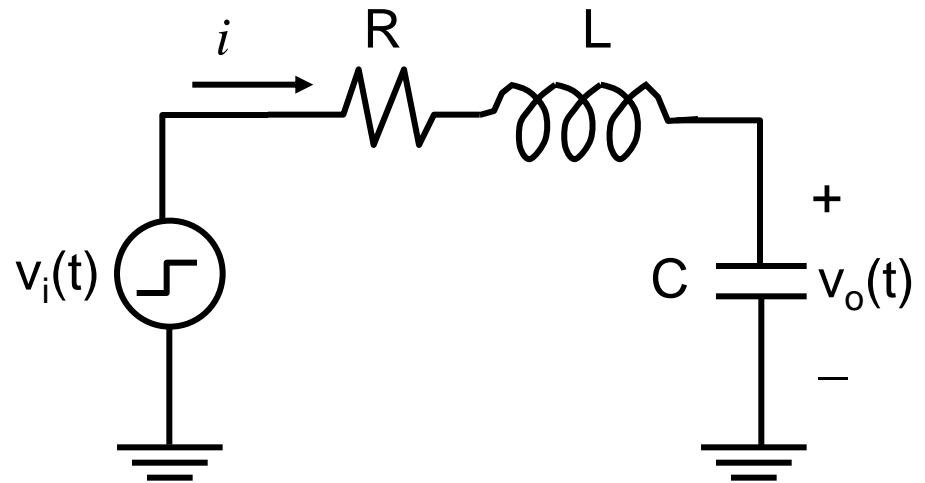
$$LC \frac{d^2 v_o}{dt^2} + RC \frac{dv_o}{dt} + v_o = v_i$$



- By Laplace transform (assume $v_o(0) = v_o'(0) = 0$):

$$\frac{v_o(s)}{v_i(s)} = \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Introducing Damping Ratio and Natural Frequency

- 為便於分析二階系統的step response，the transfer function is re-written as:

$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$


$$\text{where } \omega_n = \frac{1}{\sqrt{LC}} \text{ (natural frequency) and } \xi = \frac{R}{L} \cdot \frac{1}{2\omega_n} = \frac{R}{2} \sqrt{\frac{C}{L}}$$

- ξ : **damping ratio, dimensionless (無單位)** ; 攸關於系統中能量的損失
 - $\xi < 1$, underdamped, producing two complex roots
 - $\xi = 1$, critically damped, producing two repeated real roots
 - $\xi > 1$, overdamped, producing two distinct real roots
- 二階系統的step response在damping ratio小於1時會有振盪行為
 - The roots of the denominator for $\zeta < 1$ are:

$$s_{1,2} = -\xi\omega_n \pm j\omega_n \sqrt{1 - \xi^2}$$

Step Responses of the 2nd-Order Circuit

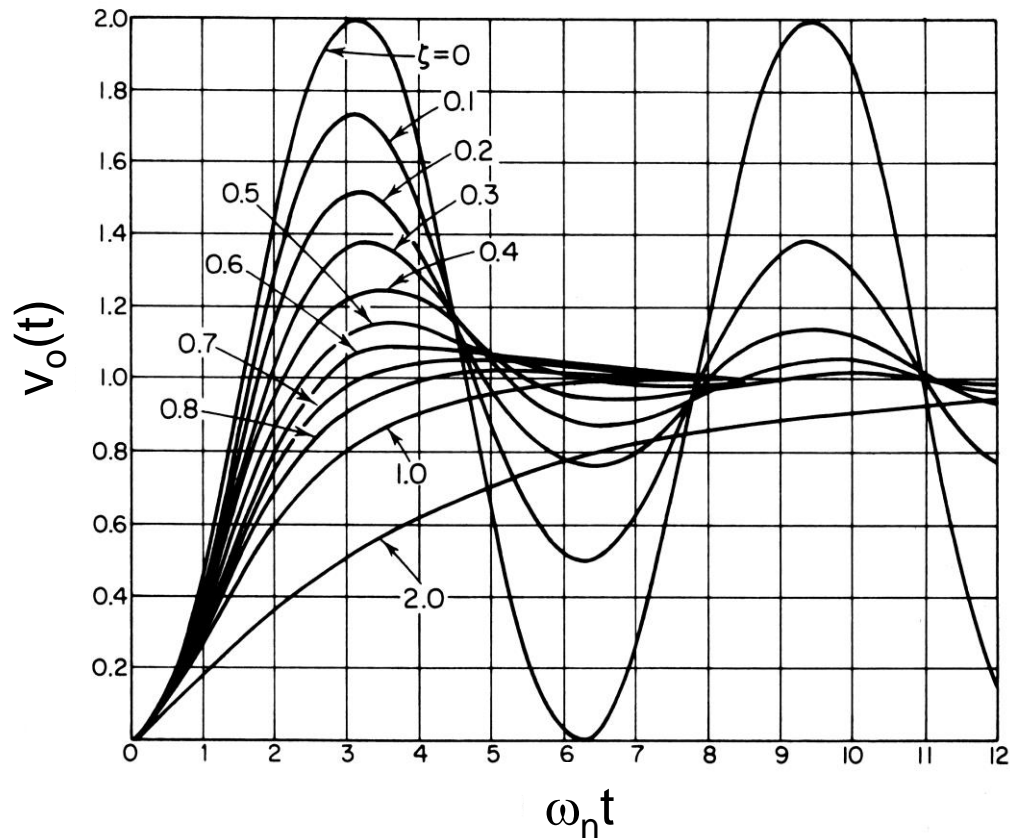- The output grows exponentially without oscillation for $\xi \geq 1$
- 注意： $\xi < 1$ 則有振盪， $\xi = 0$ 則振盪不會衰減(due to no energy loss)




Example: Underdamped Step Response

- Given $v_i(t)$ is a unit step, and

$$\frac{v_o(s)}{v_i(s)} = \frac{100}{s^2 + 10s + 100}$$

- First: $\omega_n = 10$, and $\xi = 0.5$
- To solve:
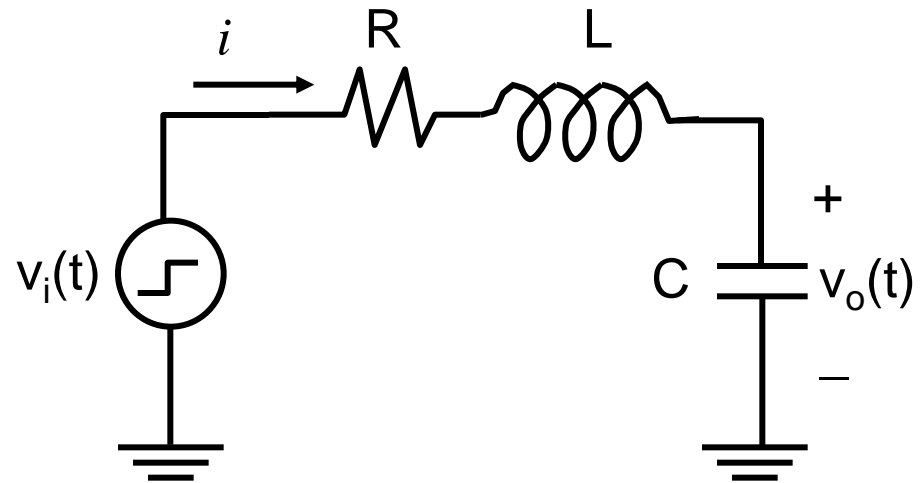
$$\begin{aligned} v_o(s) &= \frac{1}{s} \frac{100}{s^2 + 10s + 100} \\ &= \frac{1}{s} \frac{s+10}{s^2 + 10s + 100} \\ &= \frac{1}{s} \frac{s+5}{(s+5)^2 + (5\sqrt{3})^2} - \frac{5}{(s+5)^2 + (5\sqrt{3})^2} \\ &= \frac{1}{s} \frac{s+5}{(s+5)^2 + (5\sqrt{3})^2} - \frac{1}{\sqrt{3}} \frac{5\sqrt{3}}{(s+5)^2 + (5\sqrt{3})^2} \end{aligned}$$



$$\therefore v_o(t) = \left(1 - e^{-5t} \cos 5\sqrt{3}t - \frac{1}{\sqrt{3}} e^{-5t} \sin 5\sqrt{3}t \right) \cdot u(t)$$

Underdamped Step Response


- Two complex poles: $s_{1,2} = -\xi\omega_n \pm \underbrace{j\omega_n\sqrt{1-\xi^2}}_{\omega_d}$

- 可以歸納成一個公式（不建議一定要背，但有些關鍵的物理意義要瞭解）：

$$v_o(t) = 1 - e^{-\xi\omega_n t} \left(\cos \omega_d t + \frac{\xi}{\sqrt{1-\xi^2}} \sin \omega_d t \right)$$


$$\omega_d = \omega_n \sqrt{1-\xi^2} \quad \text{damped natural frequency}$$
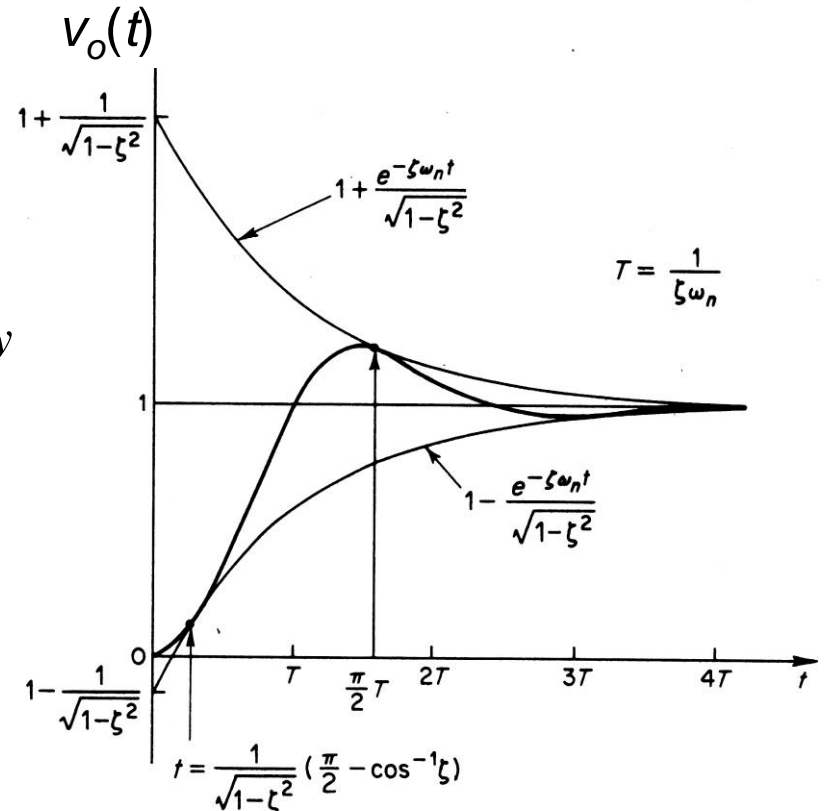
$$\text{Time constant: } \tau = \frac{1}{\xi\omega_n}$$



Unit-Step Response Specifications (規格) for Underdamped Case

- 定義規格，便於之後設計我們所需的 $v_o(t)$

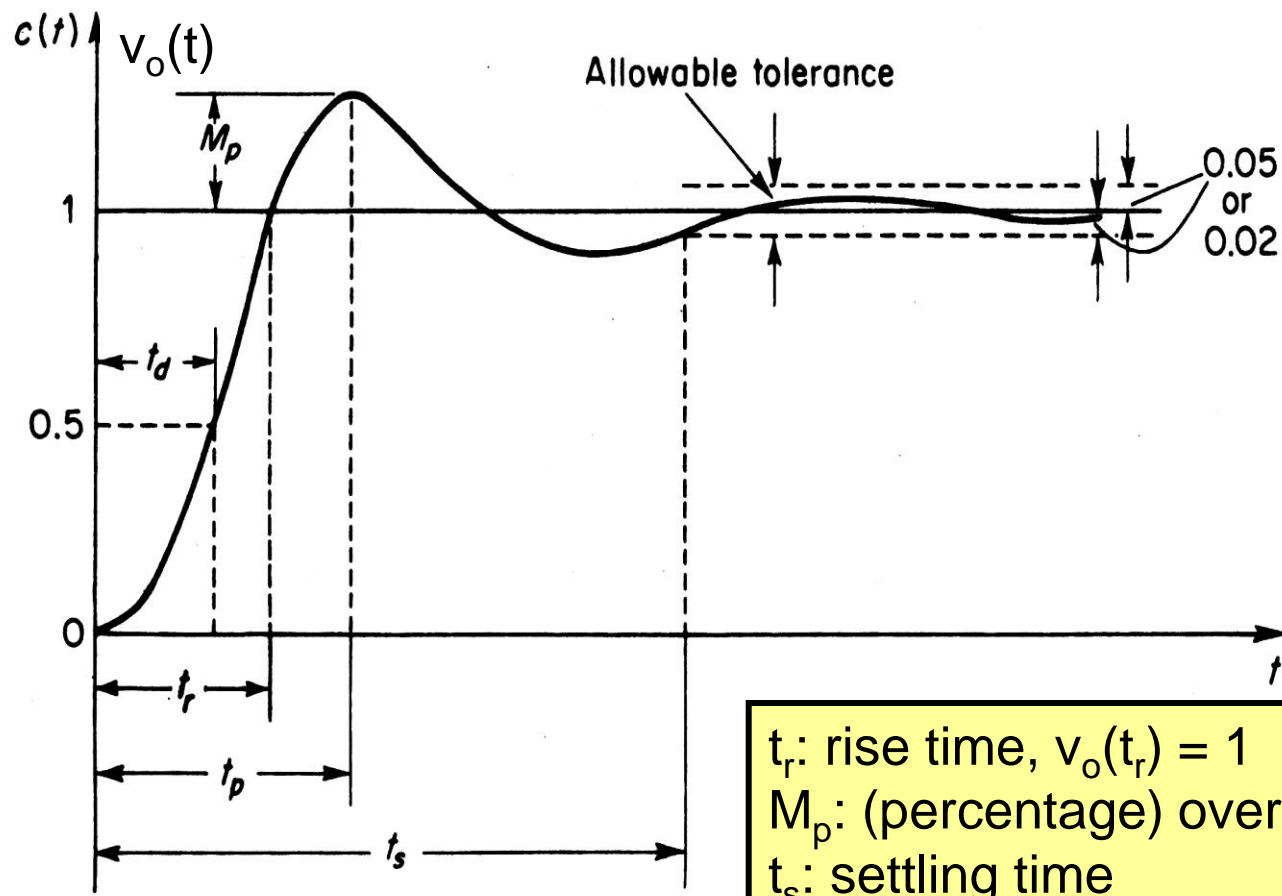

t_r : rise time, $v_o(t_r) = 1$
 M_p : (percentage) overshoot, 最大超越量
 t_s : settling time

Rise Time t_r

- Rise time t_r occurs at output $v_o(t) = 1$:

$$v_o(t_r) = 1 = 1 - e^{-\xi\omega_n t_r} \underbrace{\left(\cos \omega_d t_r + \frac{\xi}{\sqrt{1-\xi^2}} \sin \omega_d t_r \right)}_{=0}$$

$$\therefore t_r = \frac{\tan^{-1}\left(\frac{-\sqrt{1-\xi^2}}{\xi}\right)}{\omega_d}$$


Note: unit = radian, between $\pi/2$ and π

- 舉例： $\tan^{-1}(-1) = \frac{3}{4}\pi$

Peak Time t_p and Maximum Overshoot M_p

- t_p occurs at the first peak of $v_o(t)$:

$$\left. \frac{dv_o(t)}{dt} \right|_{t=t_p} = 0$$
$$\therefore t_p = \frac{\pi}{\omega_d}$$

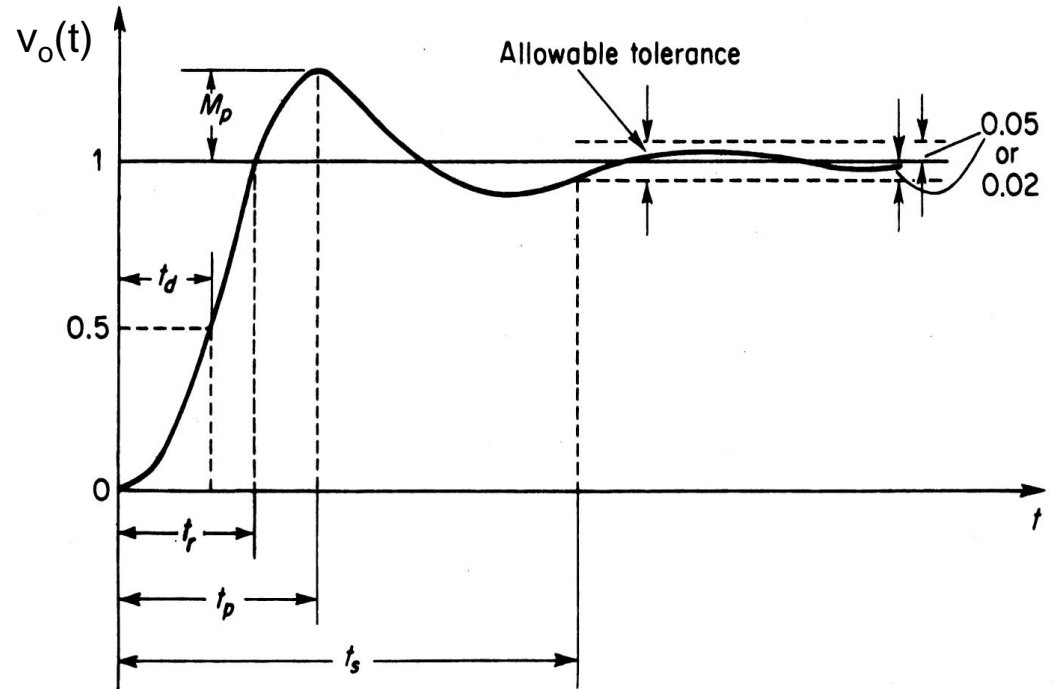


- So:

$$M_p = v_o(t_p) - 1 = e^{-\left(\frac{\xi}{\sqrt{1-\xi^2}}\right)\pi}$$

也請記得overshoot公式

Overshoot M_p vs. Damping Ratio ξ

這張圖對你實驗設計會有幫助

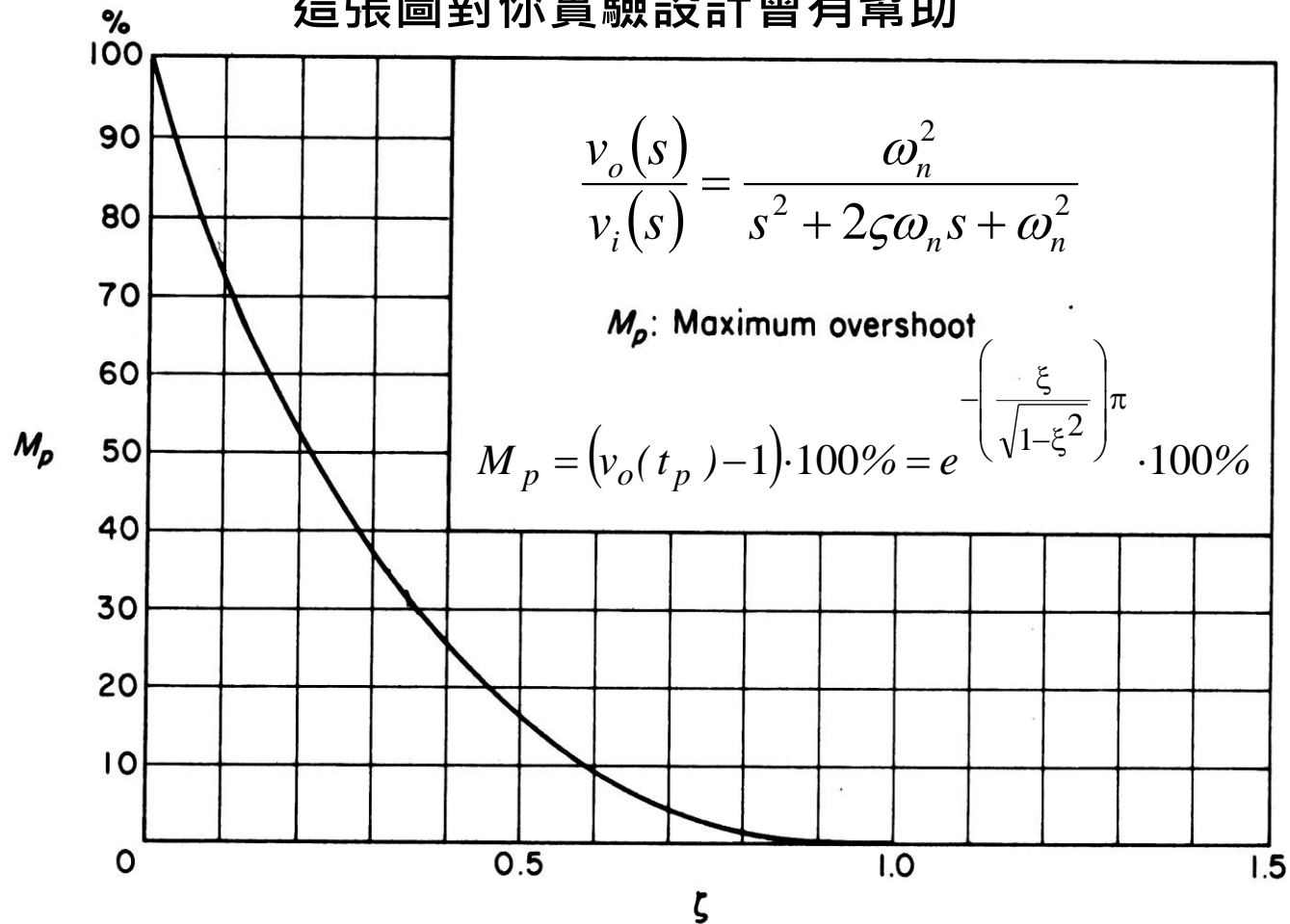

Some Skills with the Oscilloscope: Averaging

- Purpose: to reduce noise and smooth the measured waveforms
(波形變得較漂亮清楚，對於你紀錄波形有幫助)



Some Skills with the Oscilloscope: Cursor

- Purpose: 藉由二游標來量測波形中任兩點相對的時間差及電壓差(對於你紀錄波形有幫助)

