


# Lab 3: Passive Filters ( 被動式濾波電路 )

---



- Filter types
- Frequency Response: Bode Diagram
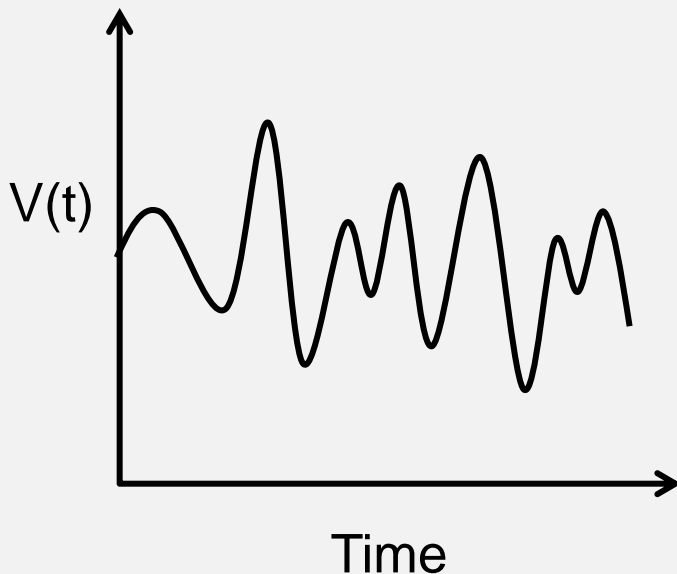
# Signals: Time Domain ( 時域 ) vs. Frequency Domain ( 頻域 )

- The spectrum ( 頻譜 ) of a time-domain signal can be obtained by Fourier analysis
- Filters of various types can keep or attenuate signals at different frequency ranges
- What are passive and active filters?




Fourier analysis

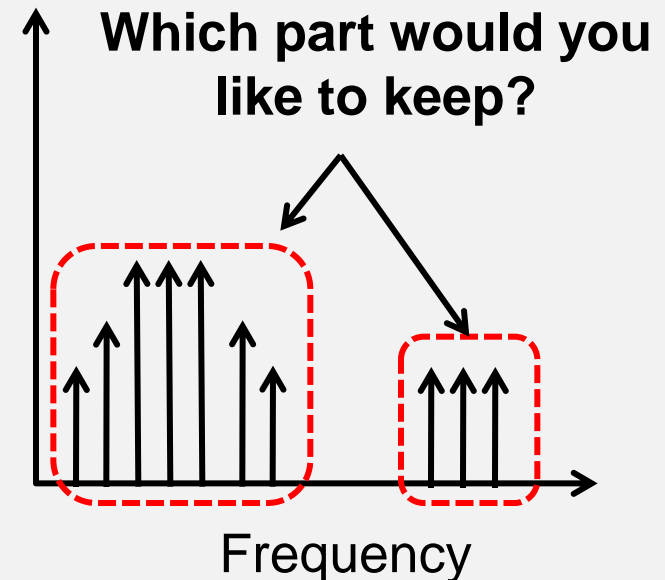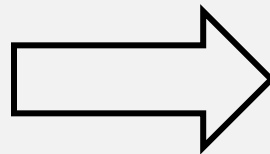



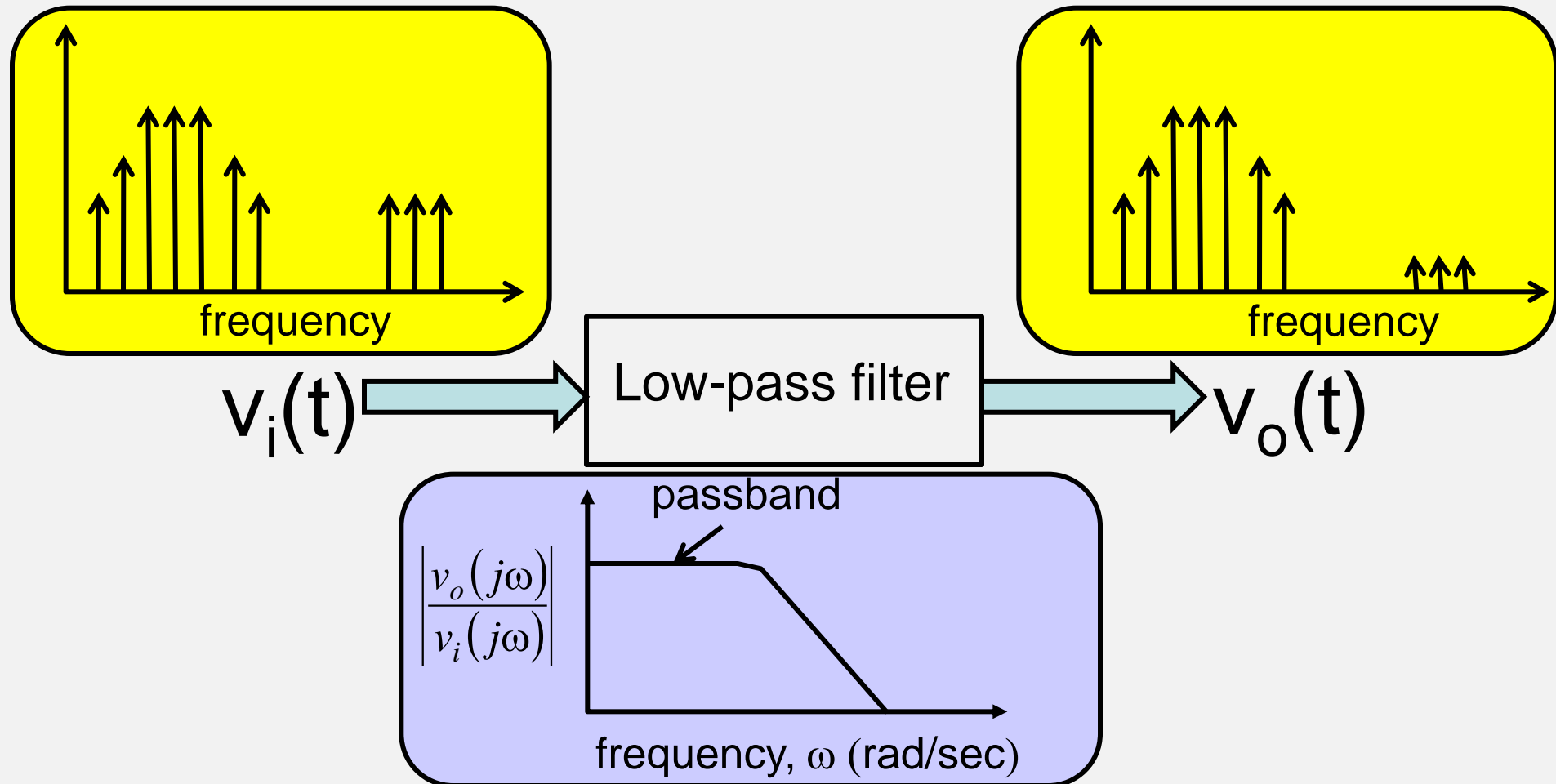
# Filter Types: First, a Low-Pass Filter ( 低通濾波器 )

- The frequency response of a low-pass filter as shown attenuates high-frequency components of the signal



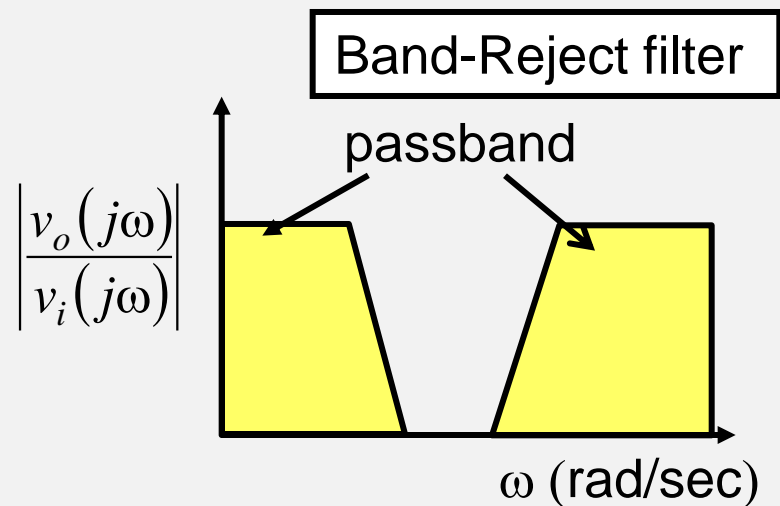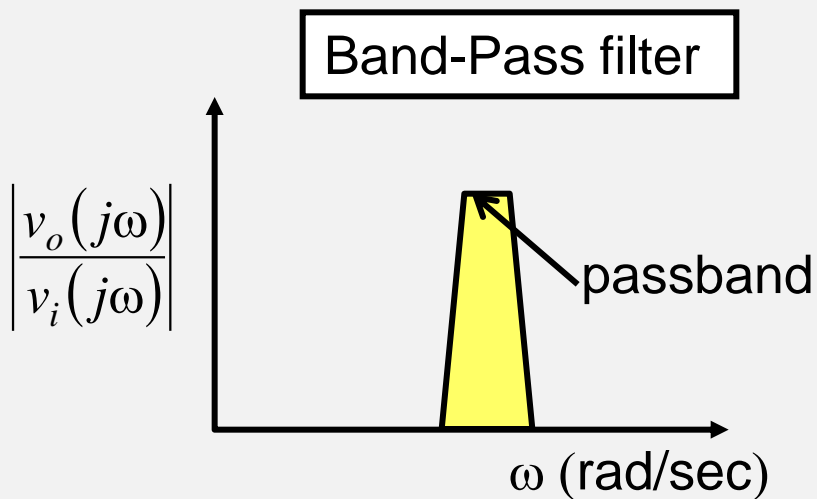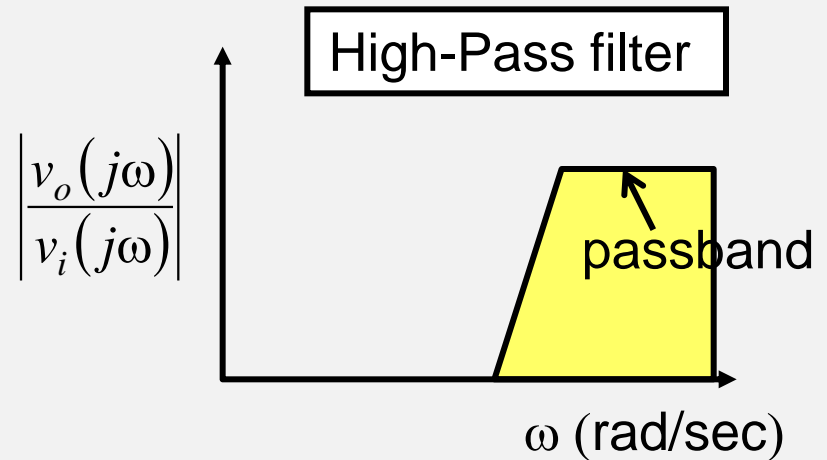
# Cont'd: Frequency Responses of Other Types of Filters

- High-pass filter
- Band-pass filter
- Band-reject filter
- 我們稍後會講解何謂 frequency response，以下先講解如何以 LRC 來製作 filter




# Low-Pass and High-Pass Filters

Low-Pass

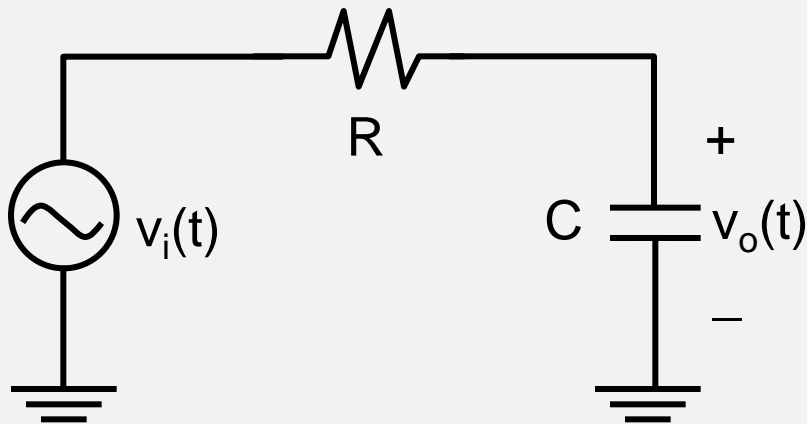

$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{RCs + 1}$$


High-Pass

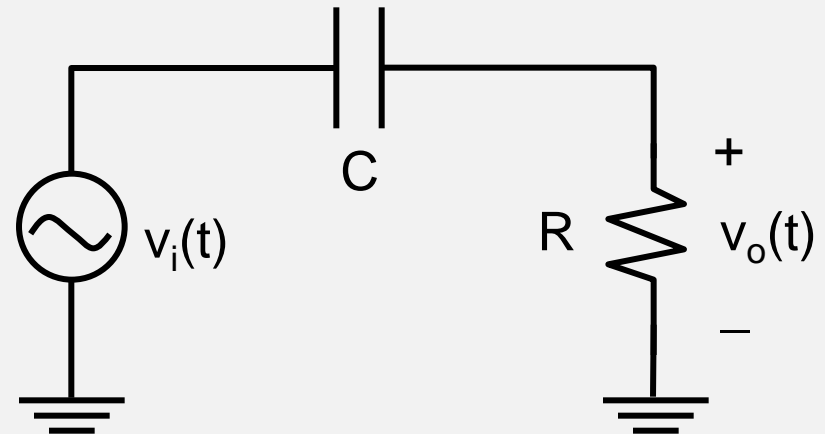

$$\frac{v_o(s)}{v_i(s)} = \frac{R}{R + \frac{1}{sC}} = \frac{RCs}{RCs + 1}$$


從impedance的觀點來導出不同的濾波電路

# Band-Pass Filters

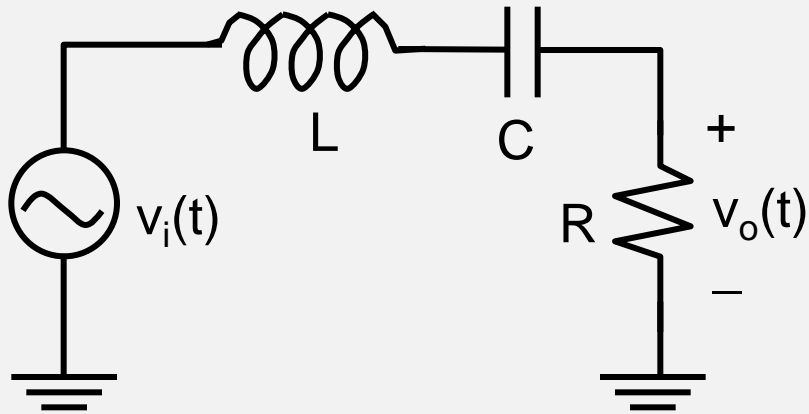


$$\frac{v_o(s)}{v_i(s)} = \frac{R}{R + \left( sL + \frac{1}{sC} \right)}$$

$$= \frac{RCs}{LCs^2 + RCs + 1}$$

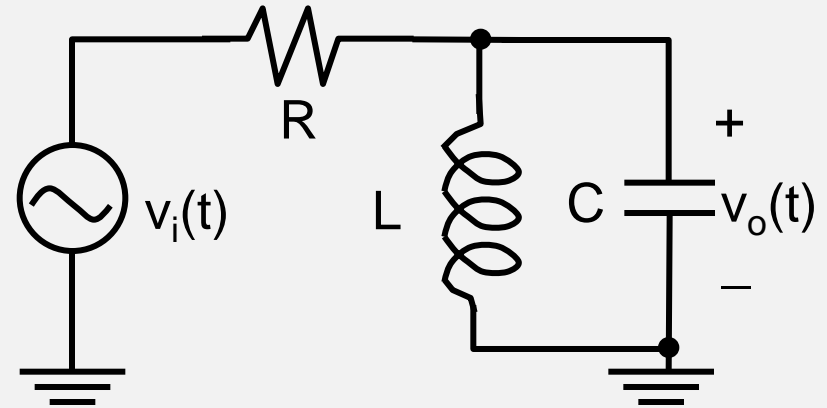


$$\frac{v_o(s)}{v_i(s)} = \frac{Ls}{LRCs^2 + Ls + R}$$

# Band-Reject Filters

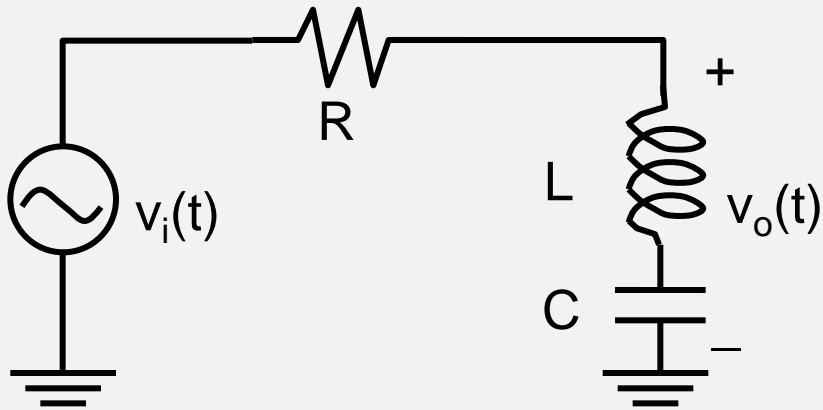

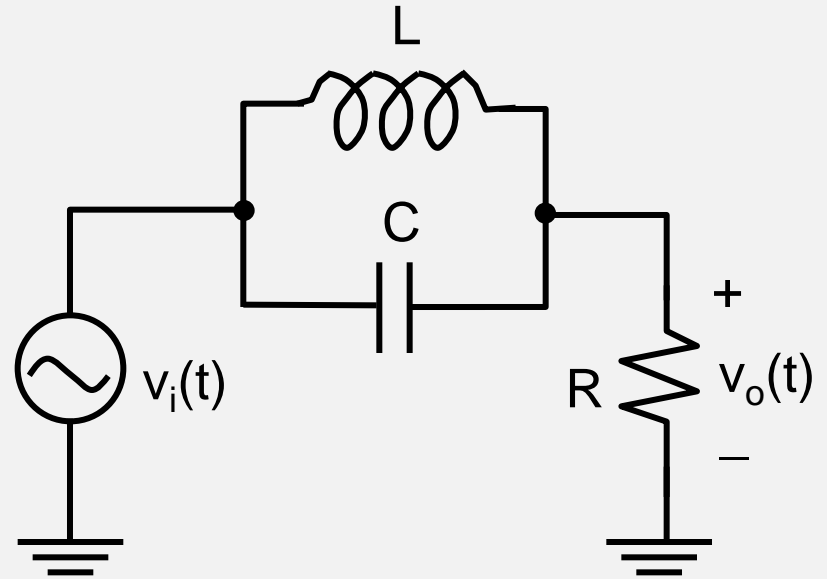
$$\frac{v_o(s)}{v_i(s)} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$



$$\frac{v_o(s)}{v_i(s)} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$
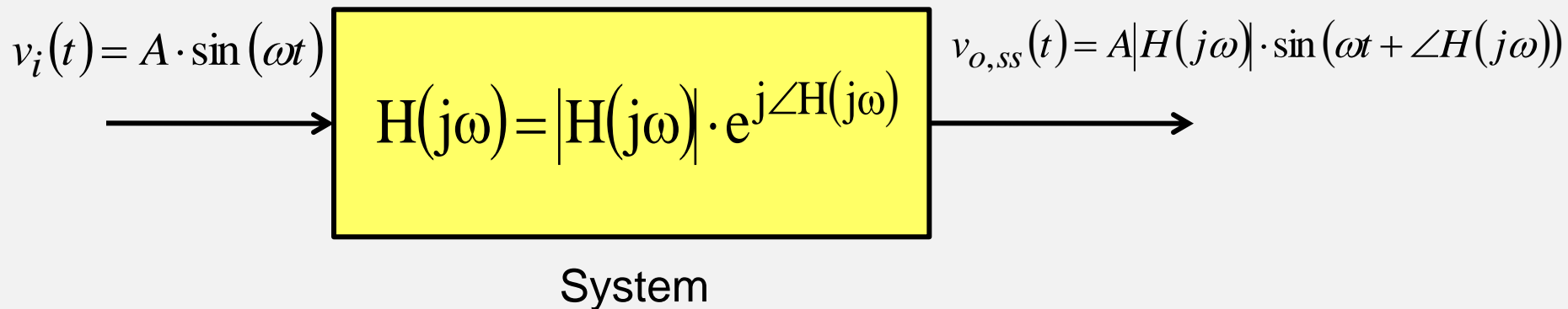
# What is the Frequency Response of a Circuit/System?

- Given a sinusoidal input to a system (for example, a circuit), the steady-state output (記得，強調的是穩態輸出) is modified by the gain and phase of system's frequency response
- Frequency response of a system can be represented by Bode diagram, and used in filtering problems (this lab) and control system problems (大三下控制系統)






# Example: a Low-Pass Filter

- Here is a RC circuit:  $v_i = \sin(t)$

$$\frac{v_o(s)}{v_i(s)} = \frac{1}{s+1} \quad v_i(s) = \frac{1^2}{s^2 + 1^2}$$

$$v_o(s) = \frac{1}{s+1} \cdot \frac{1}{s^2 + 1} = \frac{a}{s+1} + \frac{bs+c}{s^2 + 1}$$
$$= \frac{0.5}{s+1} + \frac{-0.5s+0.5}{s^2 + 1}$$


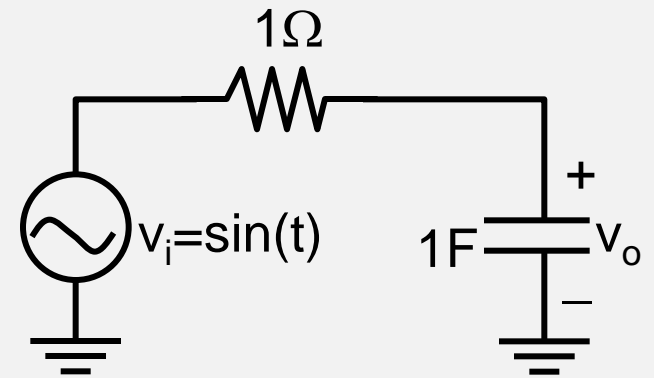
$$v_o(t) = 0.5e^{-t} - 0.5 \cos t + 0.5 \sin t$$
$$= 0.5e^{-t} + \frac{\sqrt{2}}{2} \left( \frac{1}{\sqrt{2}} \sin t - \frac{1}{\sqrt{2}} \cos t \right)$$
$$= 0.5e^{-t} + 0.707 \sin(t - 45^\circ)$$



$$v_{o,ss}(t) = 0.707 \sin(t - 45^\circ)$$

**0.707 and  $-45^\circ$  are the magnitude and phase of the frequency response at  $\omega = 1$  rad/sec**
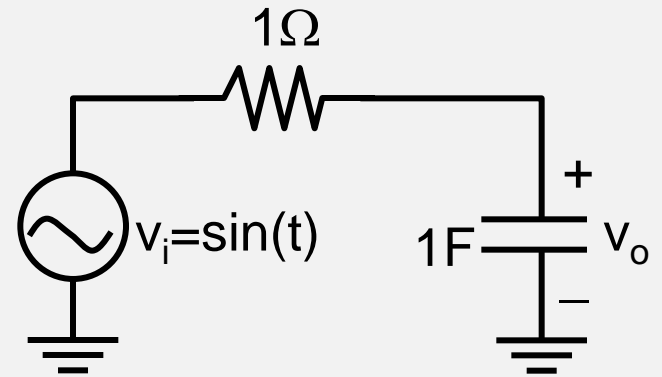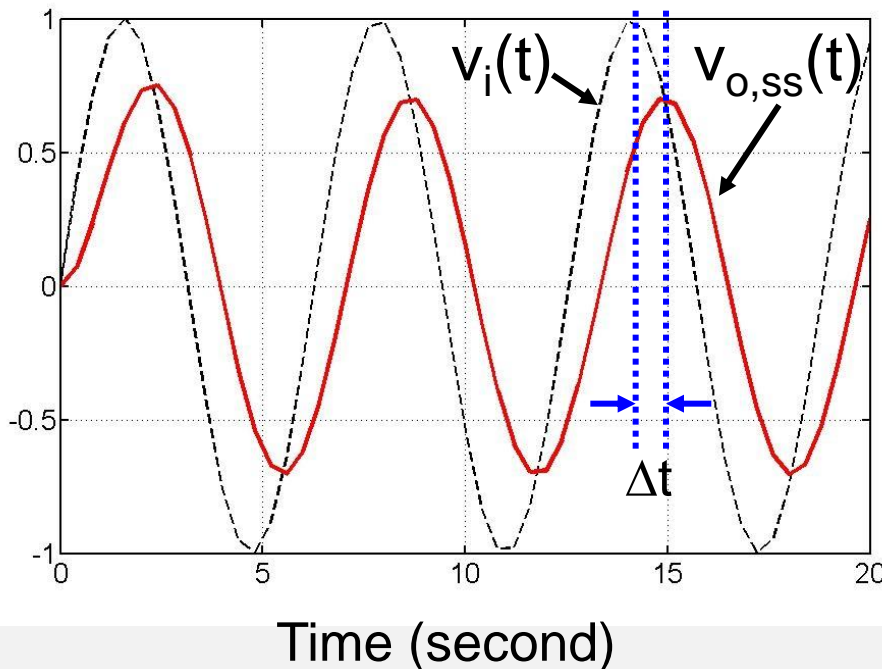
# Cont'd: Obtain the Phase from Waveforms




$$T = \frac{1}{f} = \frac{2}{\omega/2\pi} = 2\pi \text{ for } \omega = 1 \text{ rad/sec}$$

$$\Delta t = \frac{\theta}{360^\circ} \cdot T = 0.785 \text{ sec}$$

$$\Rightarrow \theta = 45^\circ (+ \text{ or } - ?)$$

$-45^\circ$  means  $v_{o,ss}(t)$  lags  $v_i(t)$  by 0.785 sec.

## Cont'd : Verify $|H(j\omega)|$ and $\angle H(j\omega)$ at $\omega = 1$ rad/sec

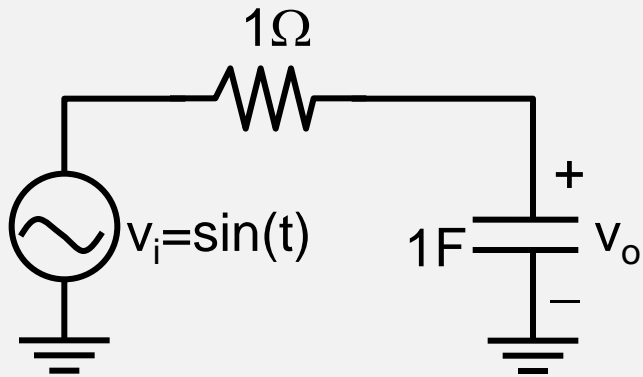

$$v_{o,ss}(t) = 0.707 \sin(t - 45^\circ)$$

$$H(s) = \frac{v_o(s)}{v_i(s)} = \frac{1}{s+1}$$

$$H(j\omega)\Big|_{\omega=1} = \frac{1}{j+1} = 0.707 e^{-j\frac{\pi}{4}}$$

# Example: a High-Pass Filter

- Input  $v_i = \sin(t)$


$$\frac{v_o(s)}{v_i(s)} = \frac{s}{s+1} \Rightarrow v_o(s) = \frac{s}{s+1} \cdot \frac{1^2}{s^2+1^2}$$

- 類似前例，以下請自行驗證：

$$v_o(t) = 0.5(\sin t + \cos t) - 0.5e^{-t}$$
$$= 0.707 \sin(t + 45^\circ) - 0.5e^{-t}$$


Steady-state part

Transient part

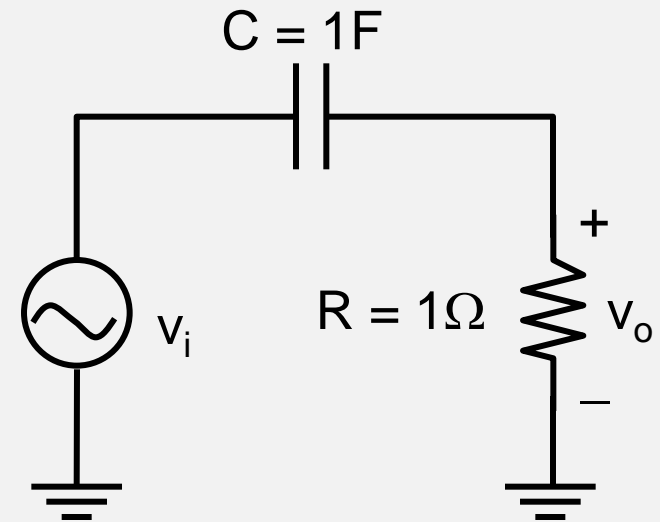


**0.707 and  $+45^\circ$  are the magnitude and phase of the frequency response at  $\omega = 1$  rad/sec**
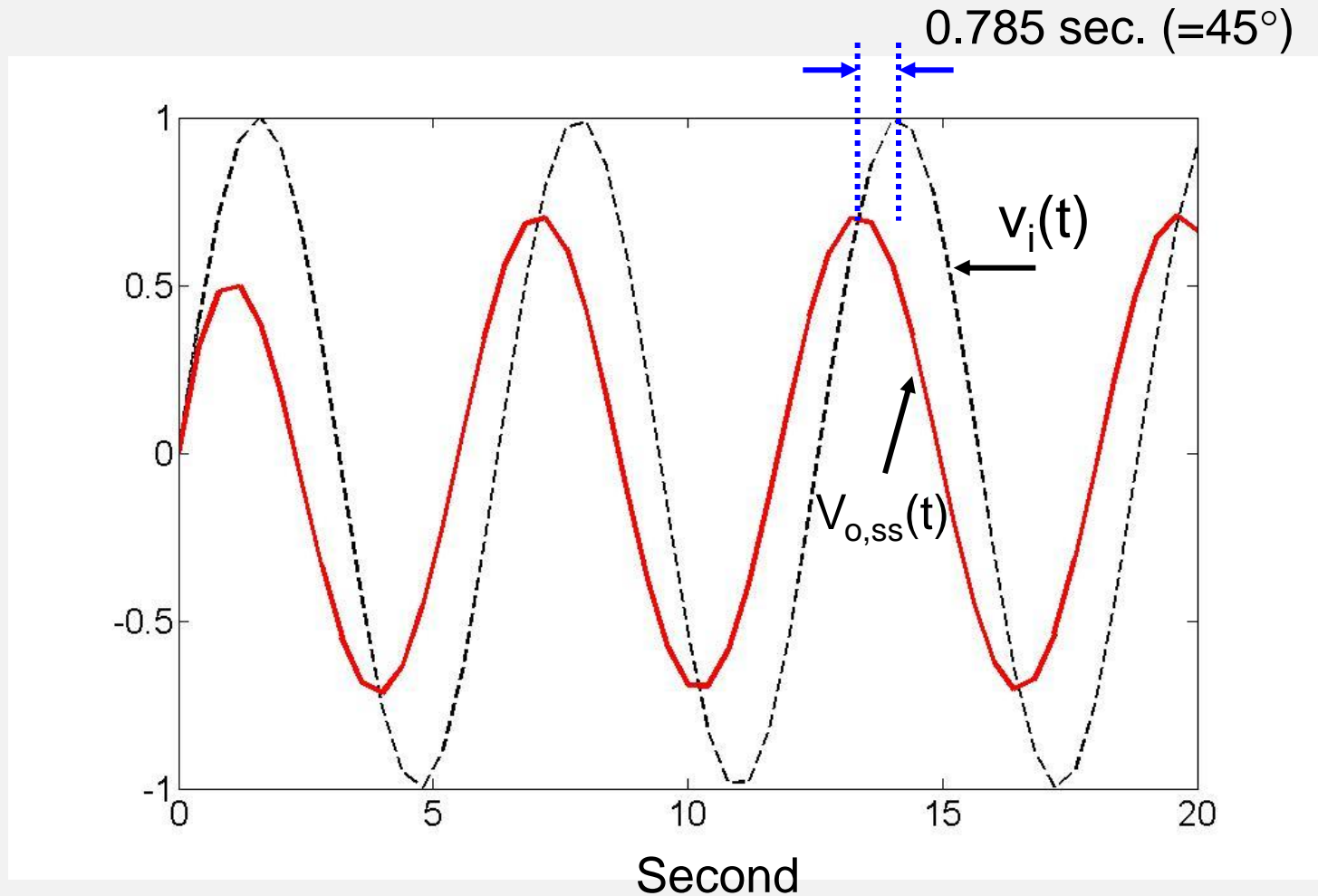
# Cont'd : 觀察波形及相角 -- The Steady-State Output $V_{o,ss}$ Leads by $45^\circ$


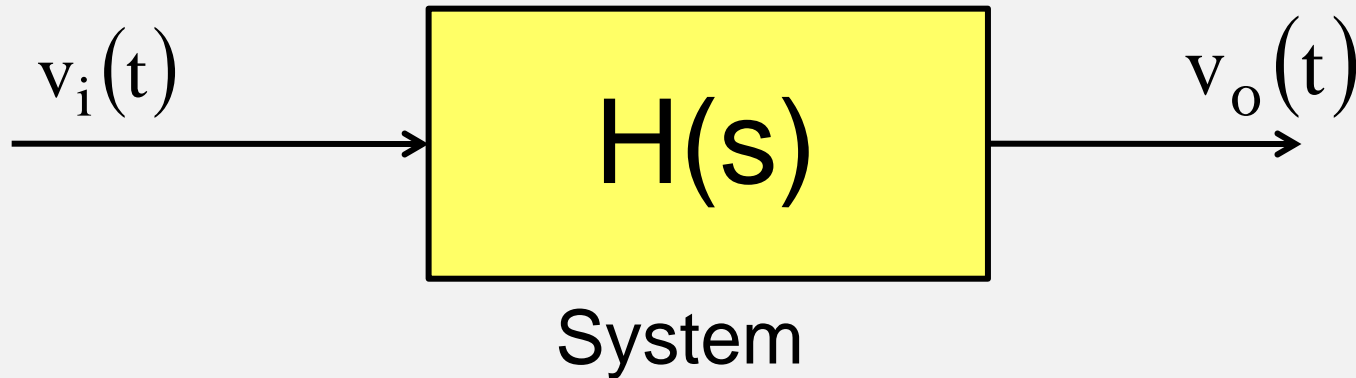
# Summary : Establish System's Frequency Response



- 方法一、當你不知道系統表示式 $H(s)$ 時：建議用剛剛例子所示範，輸入不同頻率的弦波，然後觀察相對應輸出弦波的值以及相角，來求得 $|H(j\omega)|$ 及 $\angle H(j\omega)$
- 方法二、當知道系統表示式 $H(s)$ 時：以 $s = j\omega$ 代入 $H(s)$  (why? 如果有機會修控制系統時會提到 )

$$H(j\omega) = |H(j\omega)| \cdot e^{j\angle H(j\omega)}$$


# Frequency Response Represented by the Bode Diagram

- Bode diagram contains gain and phase plots with frequency represented by logarithmic scale
- By replacing  $s = j\omega$  to get frequency-domain representation
- Example: a low-pass filter

$$H(s) = \frac{v_o(s)}{v_i(s)} = \frac{1}{RCs + 1}$$

$$= \frac{1}{Ts + 1} \quad \text{where } T = RC = 1 \text{ sec}$$
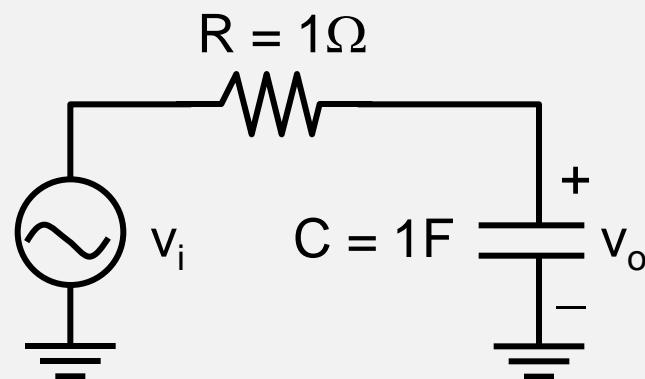
$$s = j\omega \Rightarrow H(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = \frac{1}{j\omega T + 1}$$



# Cont'd: Magnitude of a LPF

$$|H(j\omega)| = \left| \frac{v_o(j\omega)}{v_i(j\omega)} \right| = \frac{1}{\sqrt{\omega^2 T^2 + 1}}$$



- Unit of magnitude: Decibel (dB)

$$20 \text{Log}_{10} |H(j\omega)|$$

$$|H(j\omega)|_{\omega=0} = 1 = 0 \text{ dB}$$

$$|H(j\omega)|_{\omega=1/T} = \frac{1}{\sqrt{2}} = 0.707 = -3 \text{ dB}$$

$$|H(j\omega)|_{\omega=\infty} = 0 = -\infty \text{ dB}$$

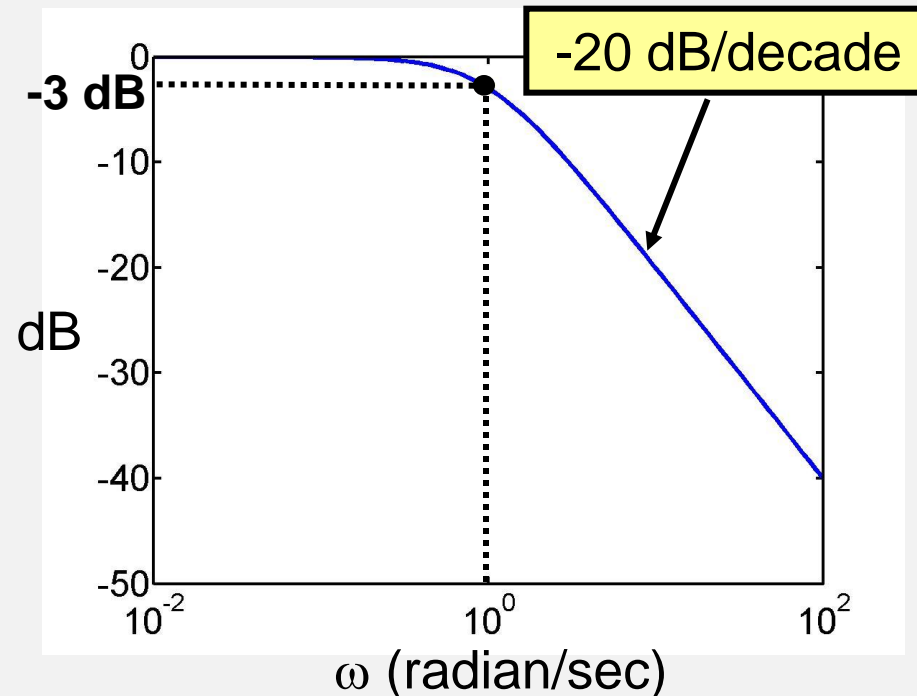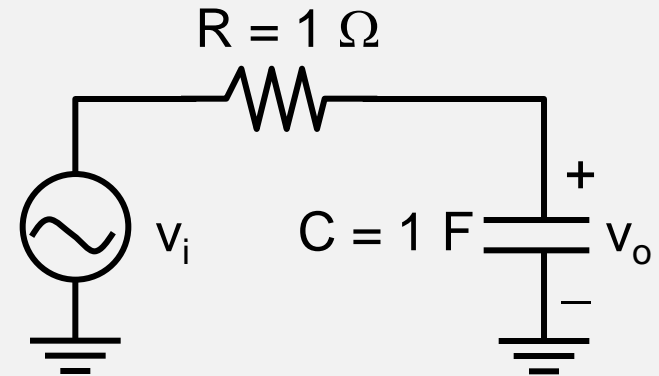



# Cont'd: Phase of a LPF


$$H(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = \frac{1}{j\omega T + 1}$$

$$\angle H(j\omega) = \angle \frac{1}{j\omega T + 1} = -\tan^{-1}(\omega T)$$


$$\angle H(j0) = -\tan^{-1}(0T) = 0^\circ$$

$$\angle H\left(j\frac{1}{T}\right) = -\tan^{-1}(1) = -45^\circ$$
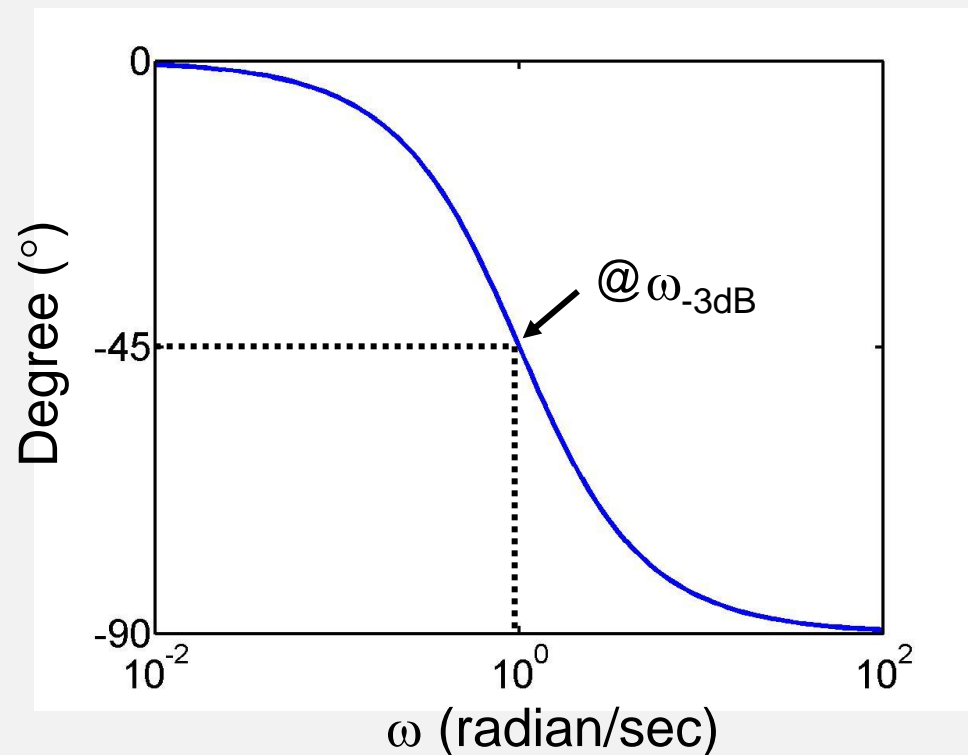
$$\angle H(j\infty) = -\tan^{-1}(\infty) = -90^\circ$$



# Example: A High-Pass Filter

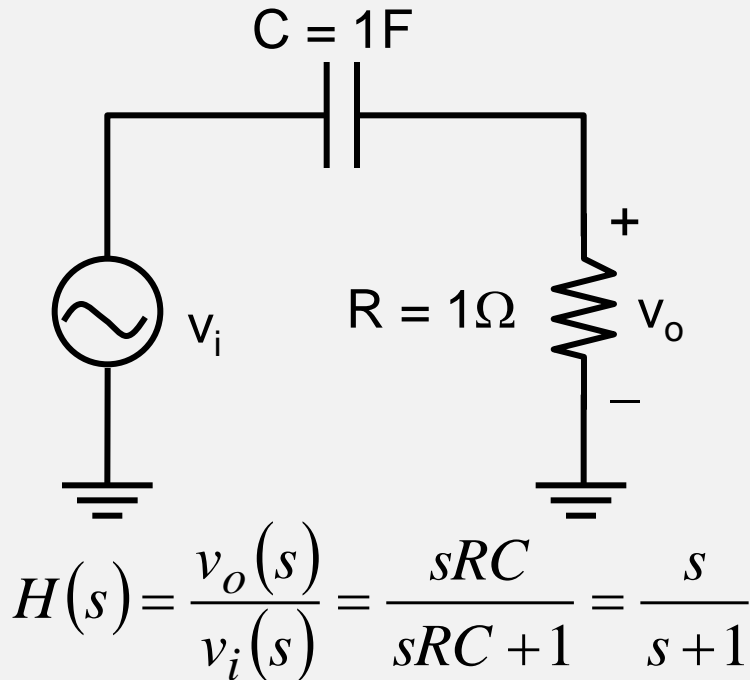


## ■ Magnitude:


$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + 1}}$$

$$|H(j0)| = 0 = -\infty\text{dB}; \left|H\left(j\frac{1}{T}\right)\right| = 0.707 = -3\text{dB}; |H(j\infty)| = 1 = 0\text{dB};$$

-3-dB frequency ( $1/(RC) = 1$  rad/sec)

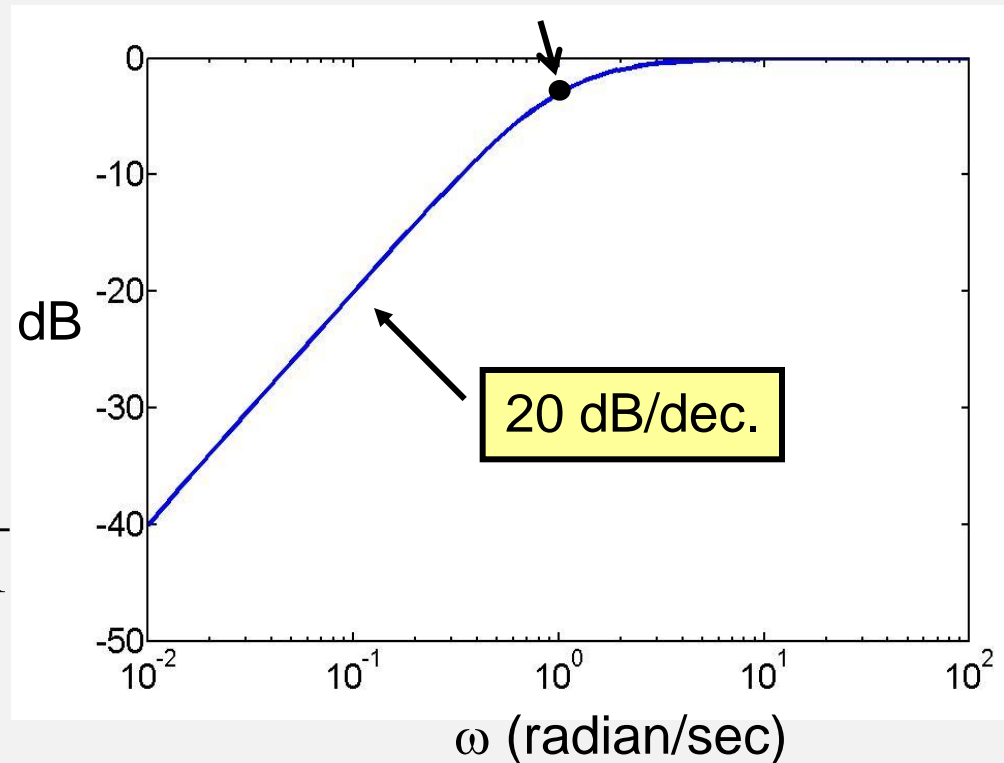


# Cont'd: Phase of a HPF

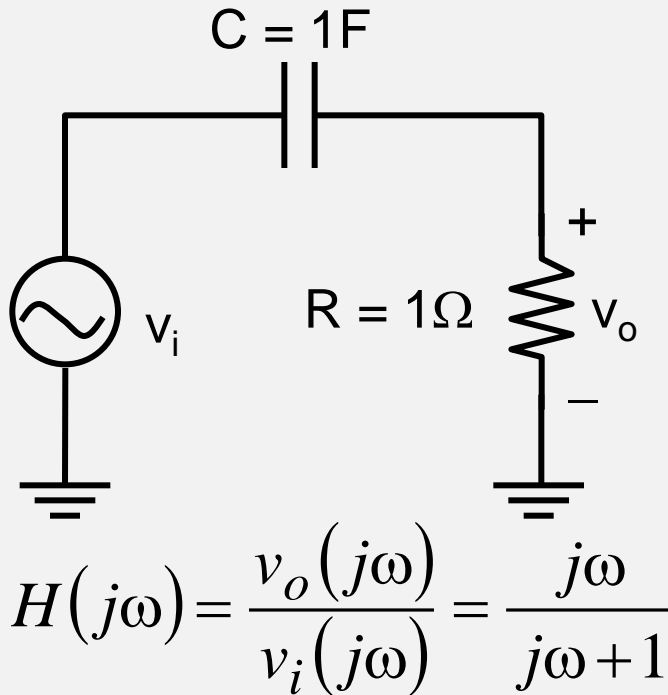

■ Phase:

$$\angle H(j\omega) = 90^\circ - \tan^{-1} \omega$$

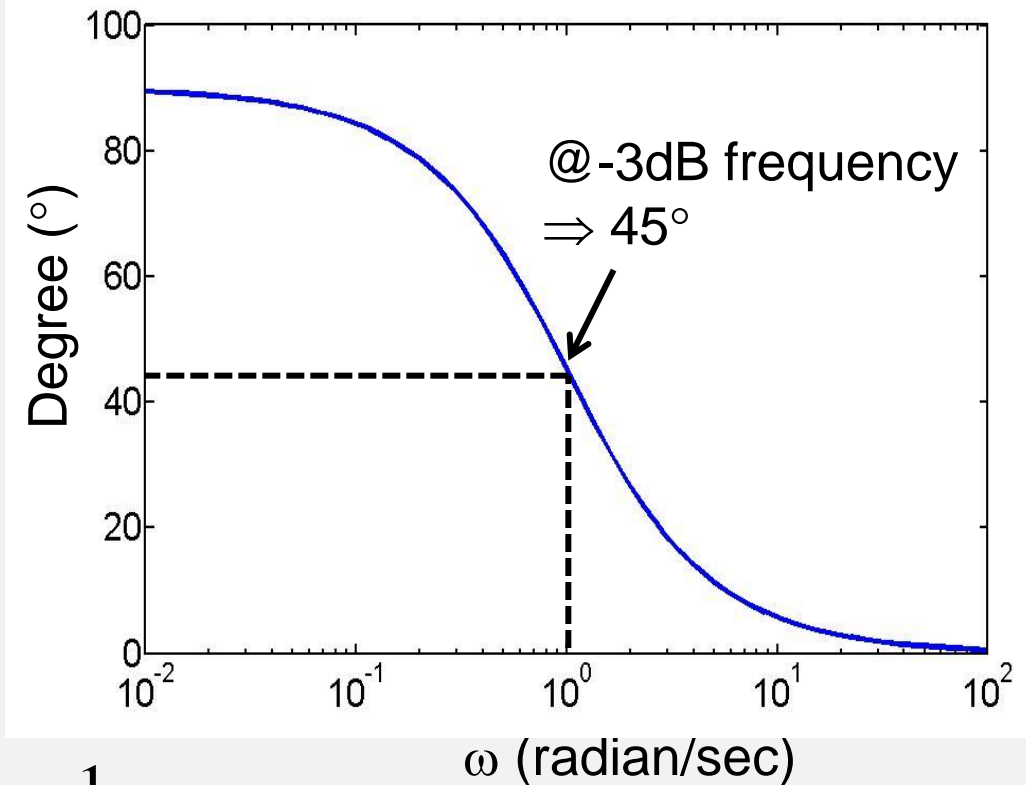
$$\angle H(j0) = 90^\circ; \angle H\left(j\frac{1}{T}\right) = 45^\circ; \angle H(j\infty) = 0^\circ$$



# Bode Diagram: 2nd-Order Systems


- 相較於RC組成的一階電路，經LRC組成的電路其分母可達到二階，如之前提到的band-pass及band-reject filters

Band-Pass

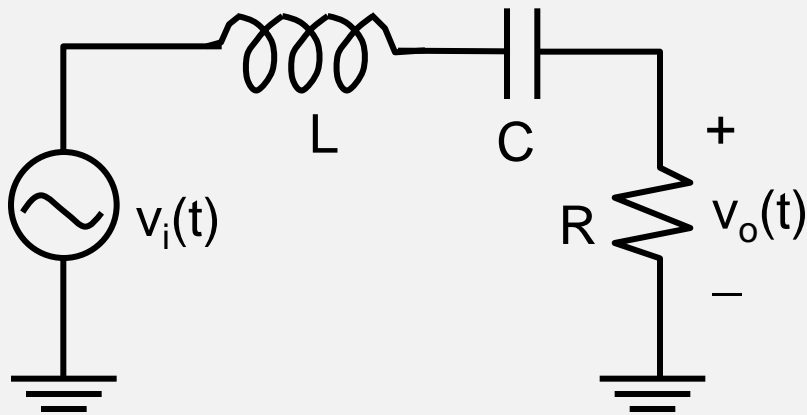

$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Band-Reject

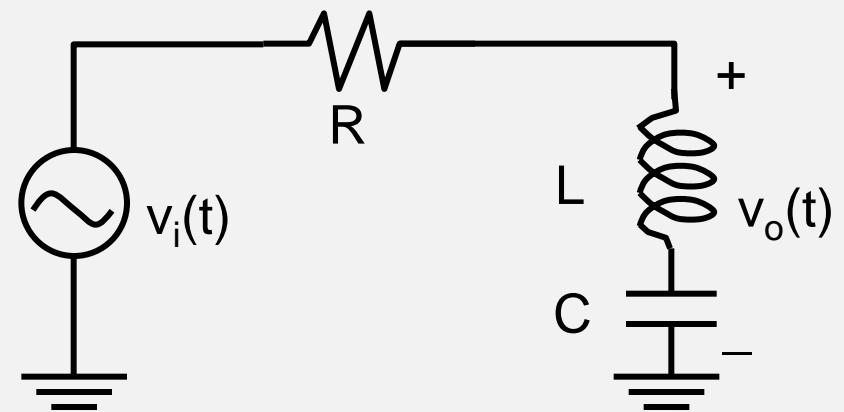


$$\frac{v_o(s)}{v_i(s)} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

# 2<sup>nd</sup>-Order Low-Pass Filter

- 如圖，這是一個二階的low-pass filter，瞭解它的frequency response將有助於瞭解band-pass及band-reject filters之frequency responses

$$H(s) = \frac{v_o(s)}{v_i(s)} = \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$
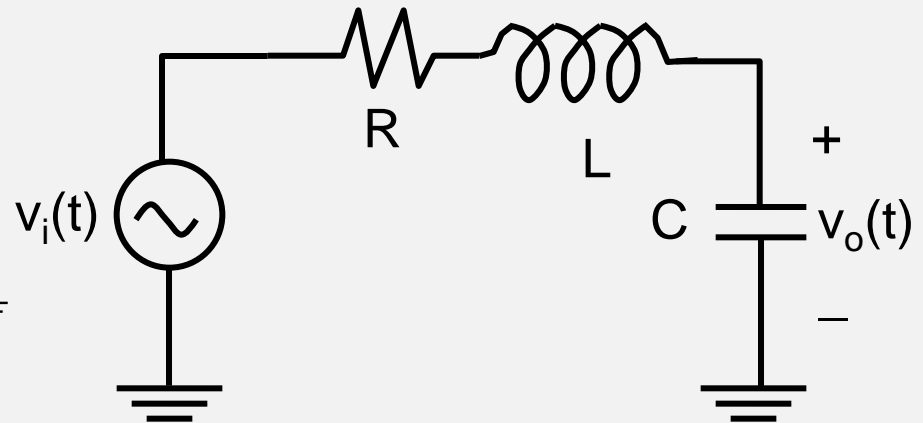
$$= \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2} \quad \omega_n = \frac{1}{\sqrt{LC}}$$



- Replace  $s = j\omega$ :

$$H(j\omega) = \frac{\omega_n^2}{(j\omega)^2 + 2\xi\omega_n(j\omega) + \omega_n^2} = \frac{\omega_n^2}{(\omega_n^2 - \omega^2) + j2\xi\omega_n\omega}$$
$$= \frac{1}{\left(1 - \frac{\omega^2}{\omega_n^2}\right) + j2\xi\frac{\omega}{\omega_n}}$$


# Cont'd: Magnitudes for Different Damping Ratios $\xi$

■ Magnitude:  $|H(j\omega)| = \frac{1}{\sqrt{\left(1 - \frac{\omega^2}{\omega_n^2}\right)^2 + \left(2\xi \frac{\omega}{\omega_n}\right)^2}}$

$$|H(j\omega)|_{\omega=0} = 1$$

$$|H(j\omega)|_{\omega=\omega_n} = \frac{1}{2\xi}$$

$$|H(j\omega)|_{\omega=\infty} = 0$$

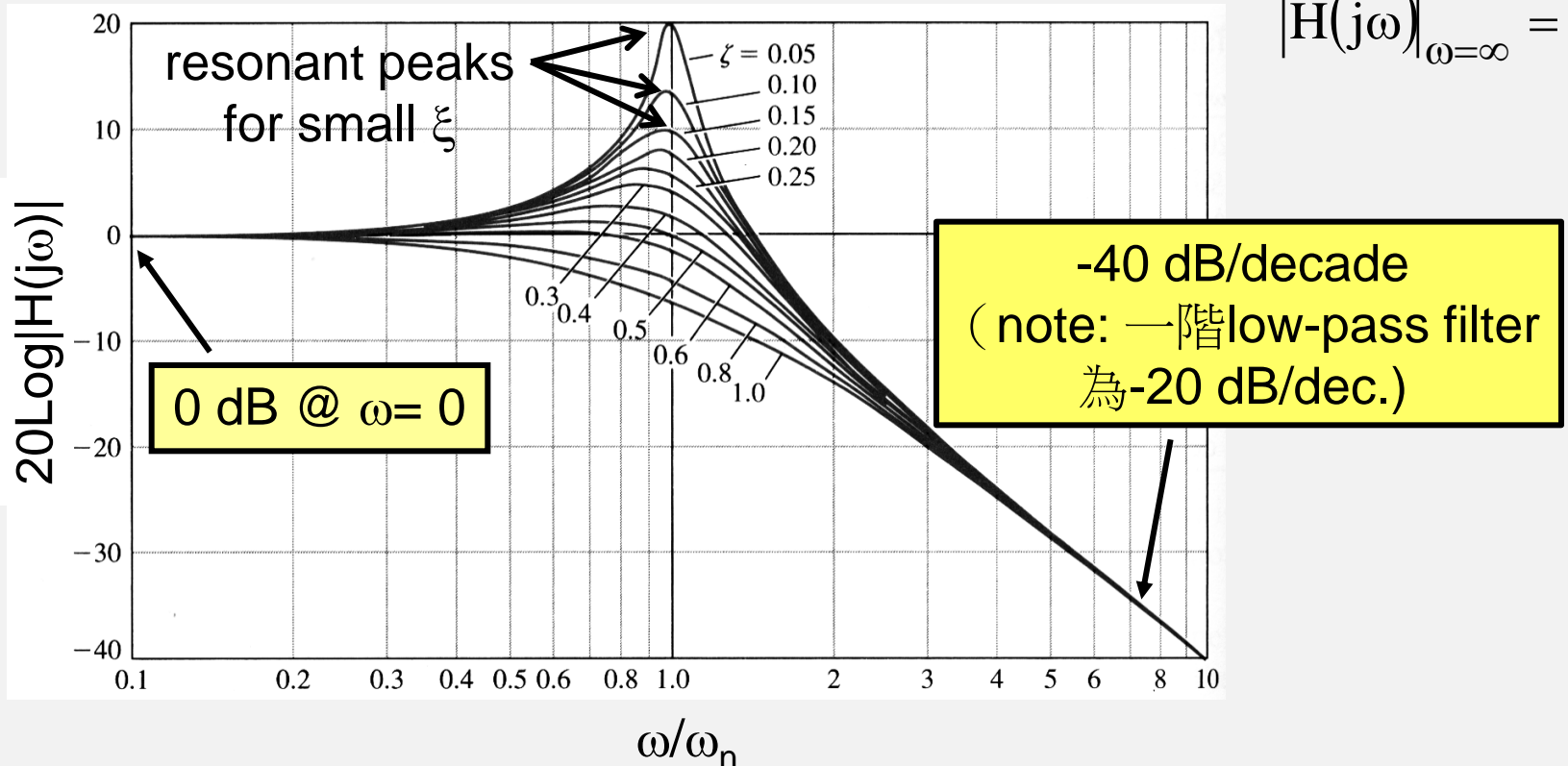

# Cont'd: Phases for Different Damping Ratios $\xi$

- The transfer function:


$$H(j\omega) = \frac{1}{\left(1 - \frac{\omega^2}{\omega_n^2}\right) + j2\xi \frac{\omega}{\omega_n}}$$

$$\Rightarrow \angle H(j\omega) = -\tan^{-1} \underbrace{\frac{2\xi \frac{\omega}{\omega_n}}{\left(1 - \frac{\omega^2}{\omega_n^2}\right)}}_{0 \rightarrow 180^\circ}$$

- Note:


- $\angle H(j\omega)|_{\omega=0} = 0^\circ$ ;
- $\angle H(j\omega)|_{\omega=\infty} = -180^\circ$

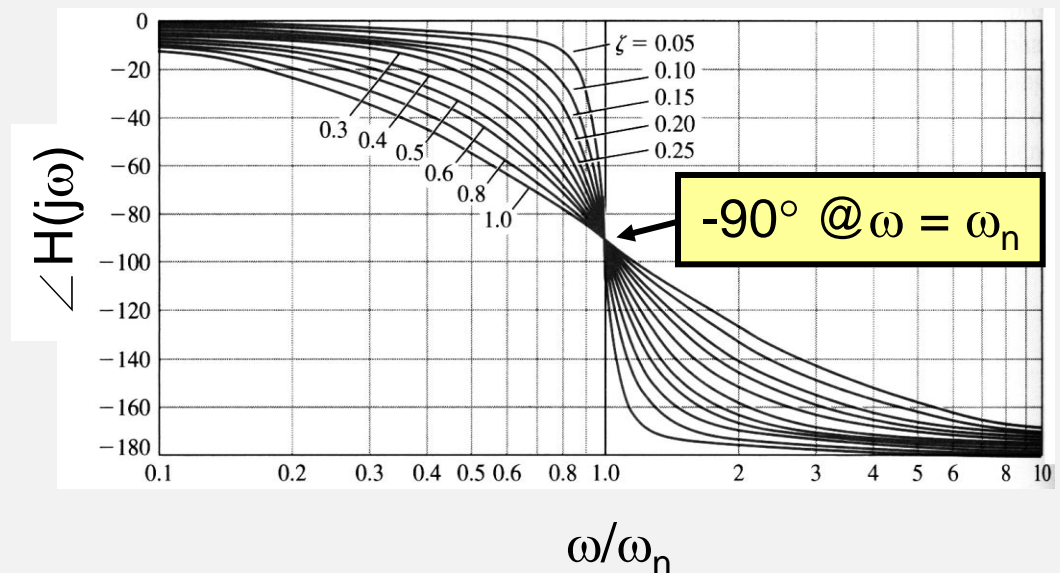- Note:  $\angle H(j\omega_n) = -90^\circ$  for all  $\xi$  values


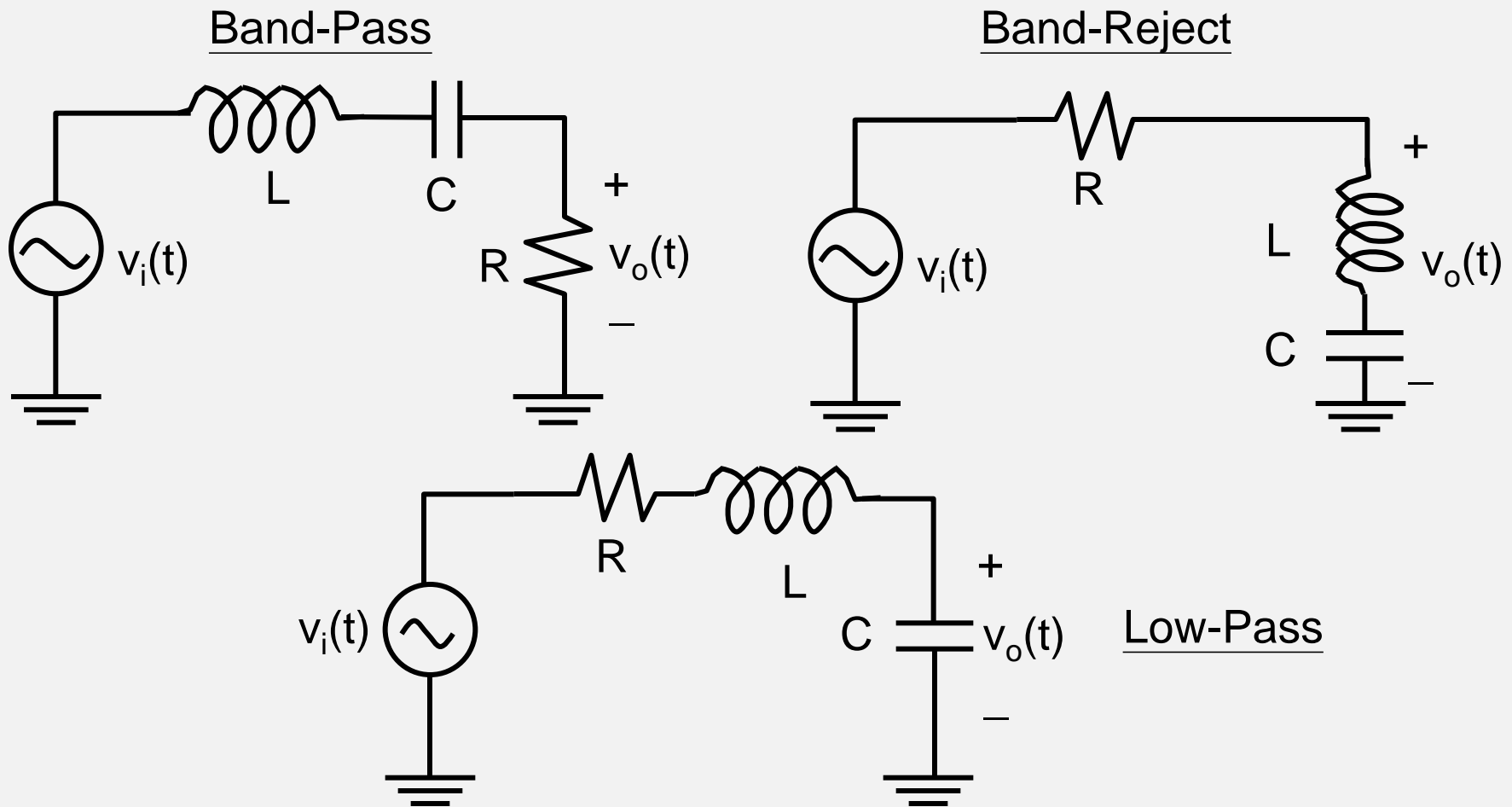
# Bode Diagrams for Band-Pass, Band-Reject, and Low-Pass Filters

- 假設 $R = 1 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1 \text{ F}$ , 比較此三種filters的Bode diagrams





# Cont'd: 假設 $R = 1 \Omega$ , $L = 1 \text{ H}$ , $C = 1 \text{ F}$

- 想想看：low-pass, band-pass及band-reject filters在自然振頻 ( $\omega_n = 1/\sqrt{LC}$ ) 的增益各是多少？

Band-Pass:


$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Band-Reject:

$$\frac{v_o(s)}{v_i(s)} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$


Low-Pass:
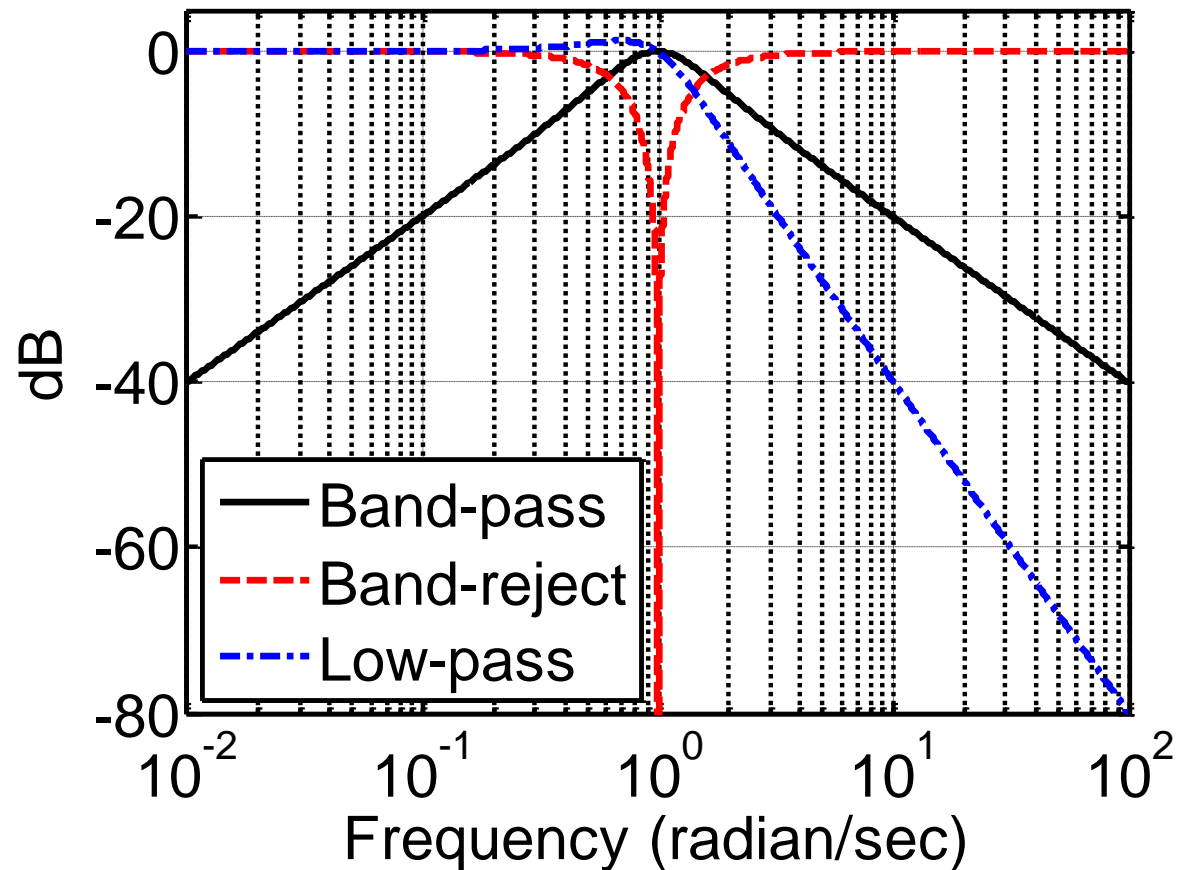
$$\frac{v_o(s)}{v_i(s)} = \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$


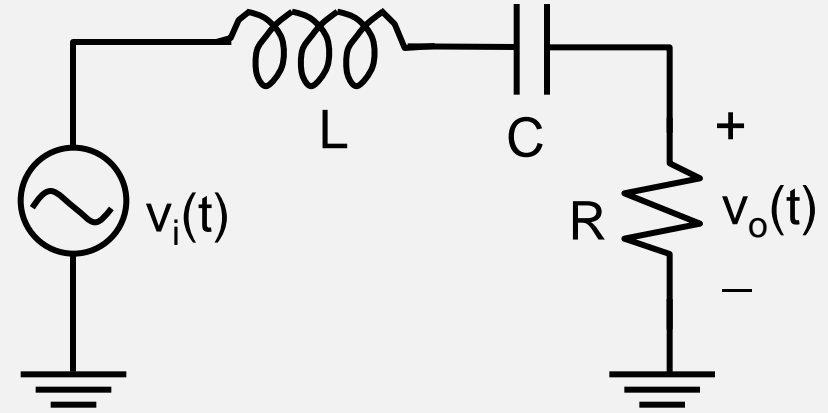
# Band-Pass Filter: the Effect of Adjusting the Value of R

- Let  $L = 1 \text{ H}$ ,  $C = 1 \text{ F}$
- In this case, the damping ratio reduces when the resistor value decreases




$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}, \quad \omega_n = \frac{1}{\sqrt{LC}}$$

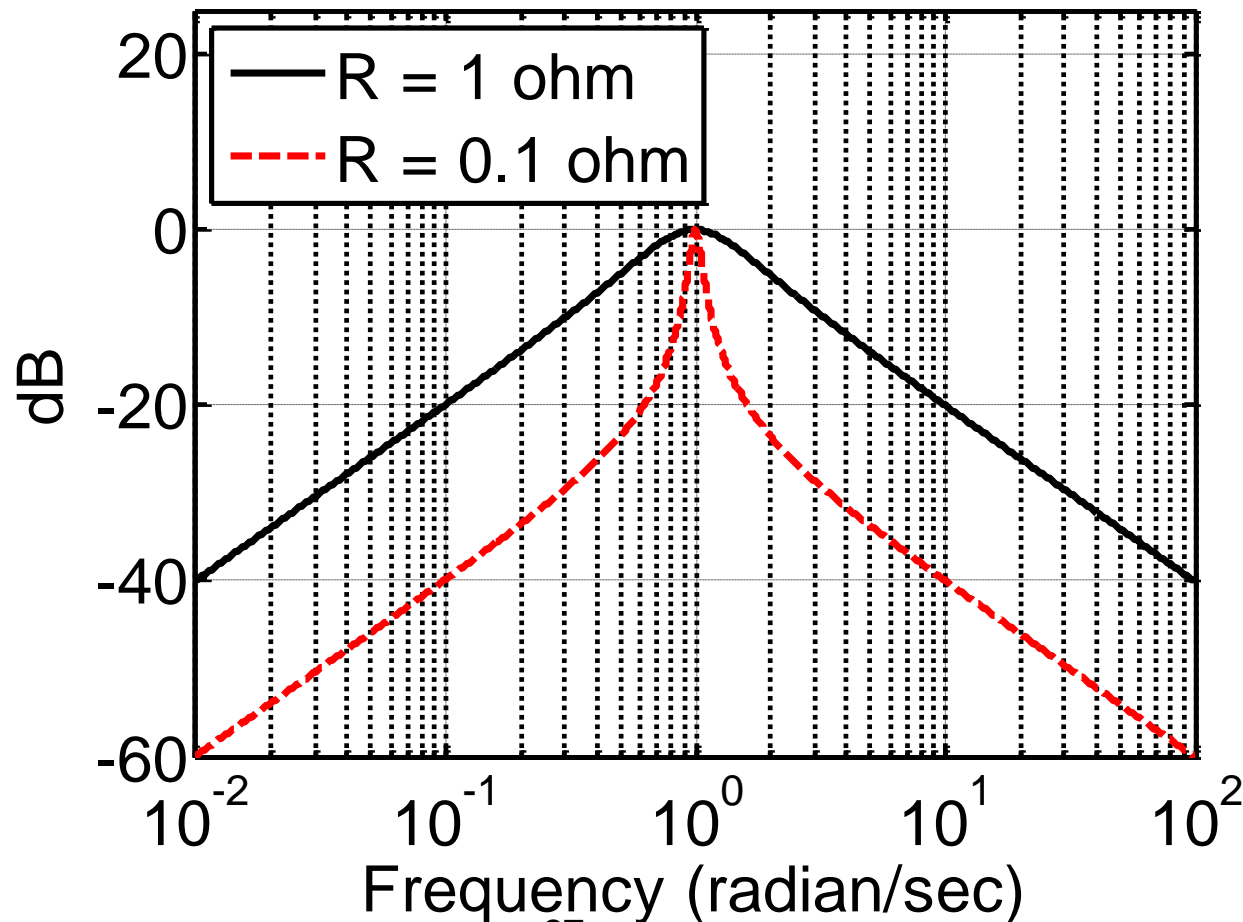
# Cont'd: Frequency Responses for Different Values of R

- Damping ratio降低使得passband 的頻寬變窄，濾波的效果變好（可以更選擇性地讓所需的頻率訊號通過而衰減其他頻率訊號）


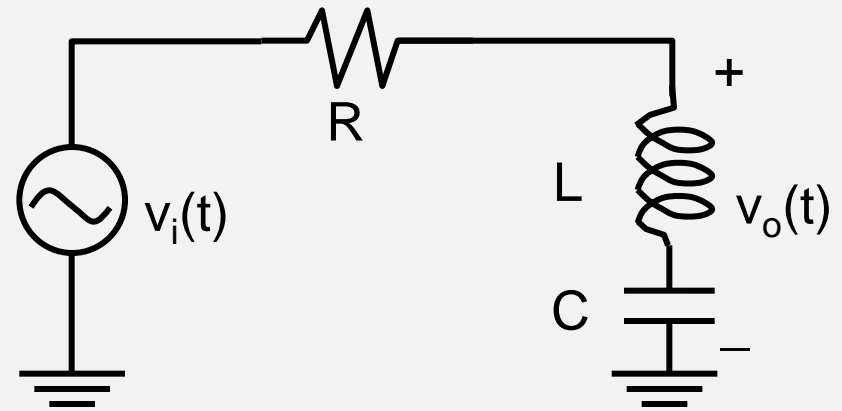
# Band-Reject Filter: the Effect of Adjusting the Value of R

- 假設  $L = 1 \text{ H}$ ,  $C = 1 \text{ F}$
- In this case, the damping ratio reduces when the resistor value decreases



$$\frac{v_o(s)}{v_i(s)} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}, \quad \omega_n = \frac{1}{\sqrt{LC}}$$

# Cont'd: Frequency Responses for Different Values of R

- Damping ratio降低使得濾波的效果變好，可以更選擇性地衰減不要的頻率訊號而留下想要的部分

