

# Lab 4: Active Filters

---


- Operational amplifier (Op-amp)
- Quality factor
- First-order active filters
- Second-order active filters
- Design problem for Electrocardiogram (ECG)
- Implementation using the LM348 and TLC2264 chips

# The Ideal Op-amp


- An op-amp has
  - Differential inputs:  $V_1$  and  $V_2$
  - Single-ended output:  $V_3$
  - So:

$$V_3 = A \cdot (V_2 - V_1)$$

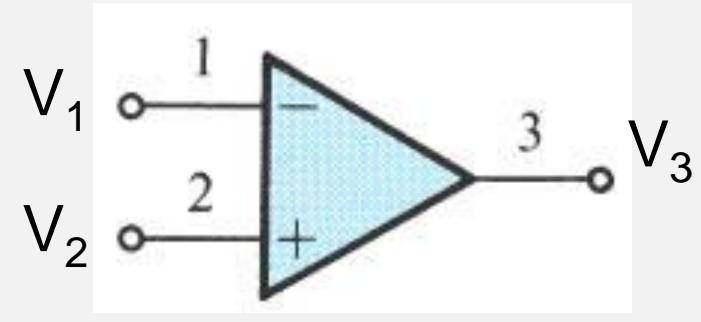- For an ideal op-amp:  $A = \infty$  ( $A = 10^3$  to  $10^5$  for typical op-amps)
  - What is the large gain for?
- An op-amp needs DC power supplies, either positive  $V_{CC}$  and negative  $V_{EE}$ , or  $V_{dd}$  and 0




Gain =  $A$

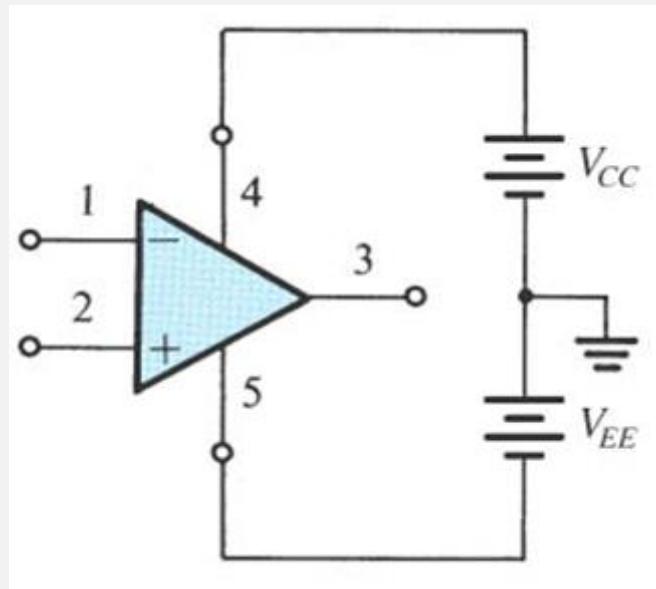

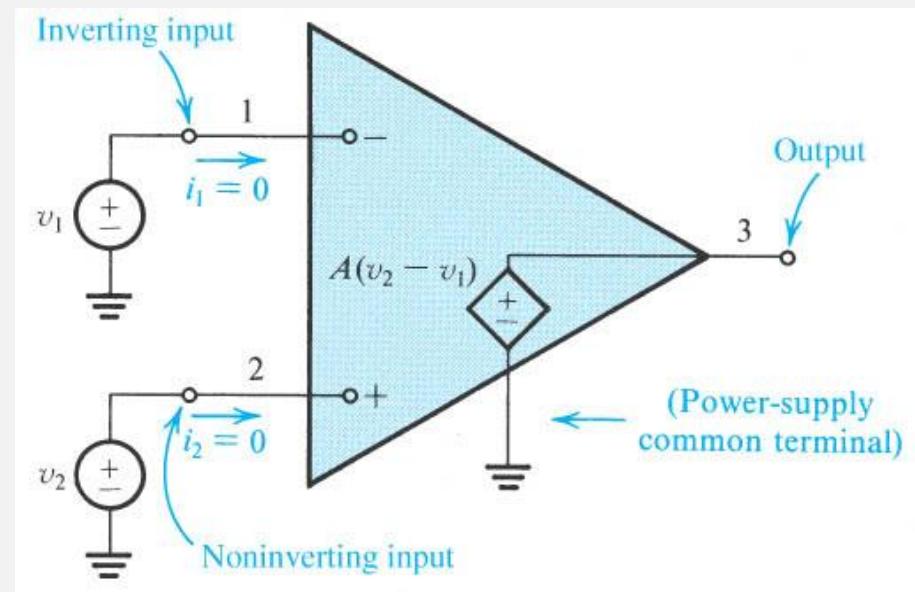
# The Ideal Op-amp


- An ideal op-amp can be used conveniently to implement both linear and nonlinear circuits. It features:
  - Infinite input impedance
    - » No current flowing in
  - Zero output impedance
  - Common-mode inputs produce no output
    - » Infinite common-mode rejection ratio (CMRR)
  - Infinite open-loop gain,  $A$
  - Infinite bandwidth



# Example of Op-amp Design (類比電路設計)

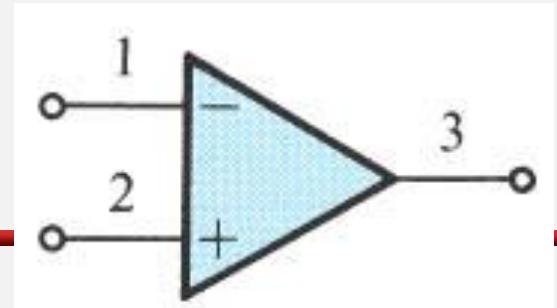


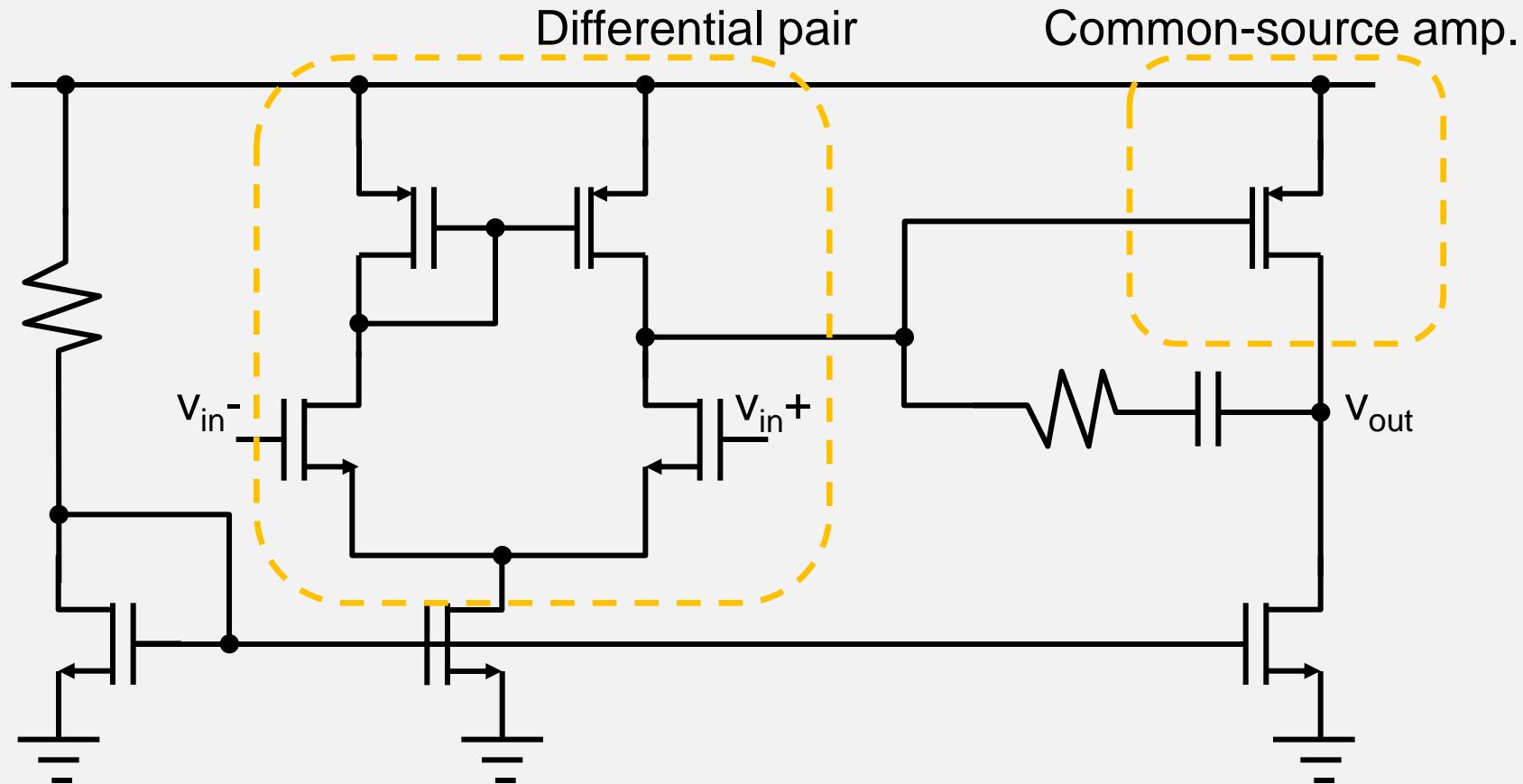- This is a typical “Two-stage Op-amp”, and there are other types.



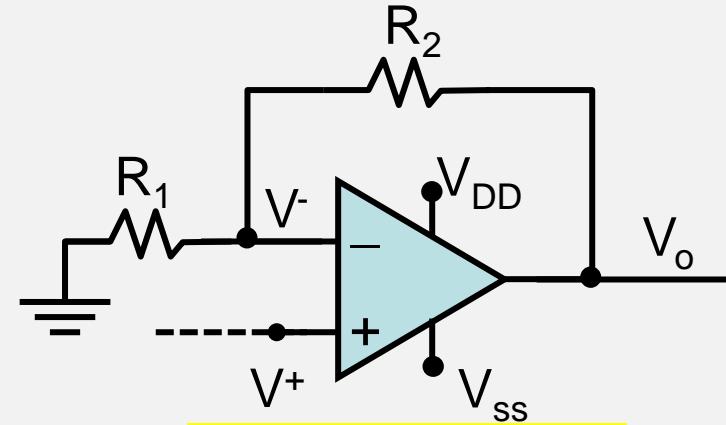
# Negative or Positive Feedback around an Opamp

- 請注意：Op-amp的增益太大，不能直接拿來作為放大器
- An op-amp is typically operated by "negative feedback" (負迴授) to build various circuits
  - 負迴授可達到在輸入端 $V^+ = V^-$ , 即所謂virtual short (虛擬短路), 是建構電路的重要性質
- Positive feedback can be used for making oscillators while virtual short does not necessarily exist



Negative feedback

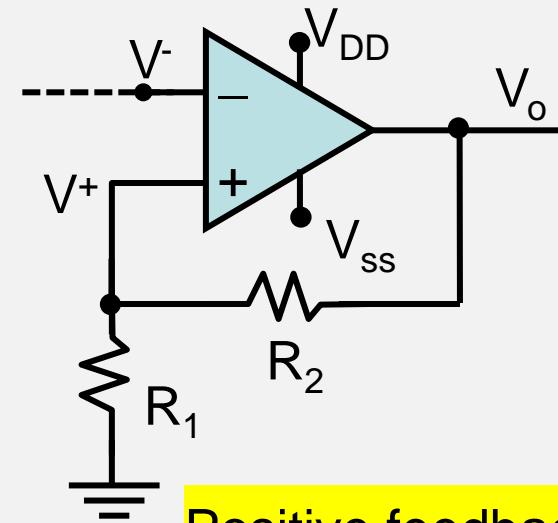

Positive feedback


# How is Virtual Short ( $V^+ = V^-$ ) achieved using Negative Feedback?

- By derivation , we have  $V^+ = V^-$  when op-amp's gain is  $\infty$ 
  - 實際上op-amp的增益一般在60 dB (1,000) 到 ~100 dB
  - 合理假設op-amp輸入電阻夠大，電流無法流入

$$V_o = A \cdot (V^+ - V^-)$$


$$V^- = \frac{R_1}{R_1 + R_2} V_o$$
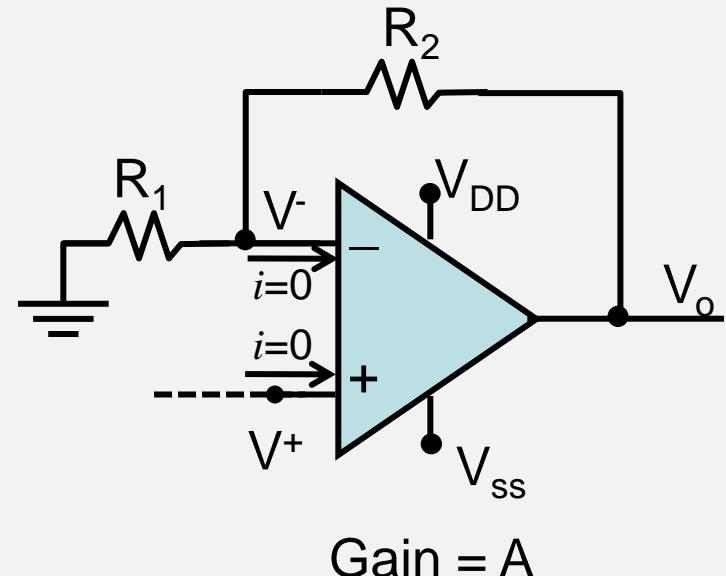
$$\Rightarrow V^+ = \left( \underbrace{\frac{R_2}{R_1} + 1}_{\approx 0} \right) \cdot V^-$$


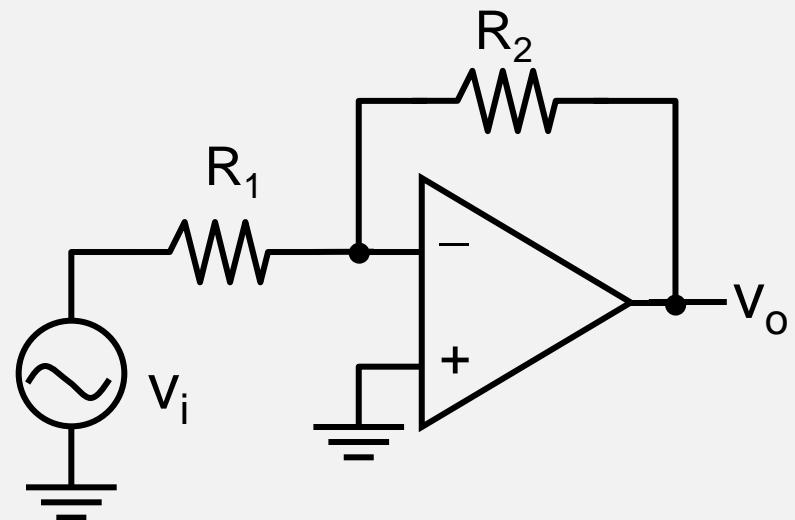
# Op-amp電路（一）：Inverting Amplifier

- It is not easy to make an amplifier with accurate gain using single transistors (for example, a common-source amplifier)
- 以op-amp製作放大器的基本觀念：op-amp的gain很大，使得能以負回授達到”虛擬短路”；在此基礎下，只要電阻值 ( $R_1, R_2$ ) 準確，便能有準確的增益 ( $v_o/v_i$ )
- “Inverting” means the achieved gain has a negative sign



# Cont'd : Inverting Amplifier

■ Virtual short, so:


$$V^- = V^+ = 0$$

$$i_1 = \frac{V_i - V^-}{R_1} = \frac{V_i}{R_1}$$

$$V_o = V^- - i_1 R_2 = -\frac{R_2}{R_1} V_i$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

$$R_{in} = R_1$$

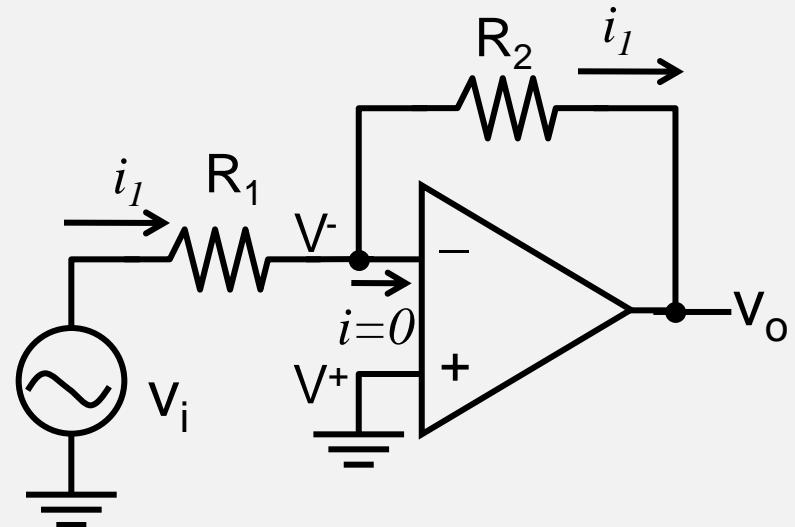

# (重要) Inverting Configuration

- In general:


$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2}{Z_1}$$

- For example:  $Z_1 = R$ ,  $Z_2 = 1/(sC)$ :


$$\frac{V_o(s)}{V_i(s)} = -\frac{1}{sRC} \quad (\text{integrator})$$

$$\frac{V_o(s)}{V_i(s)} = -\frac{1}{sRC} \Rightarrow V_o(s) = -\frac{1}{sRC} V_i(s)$$
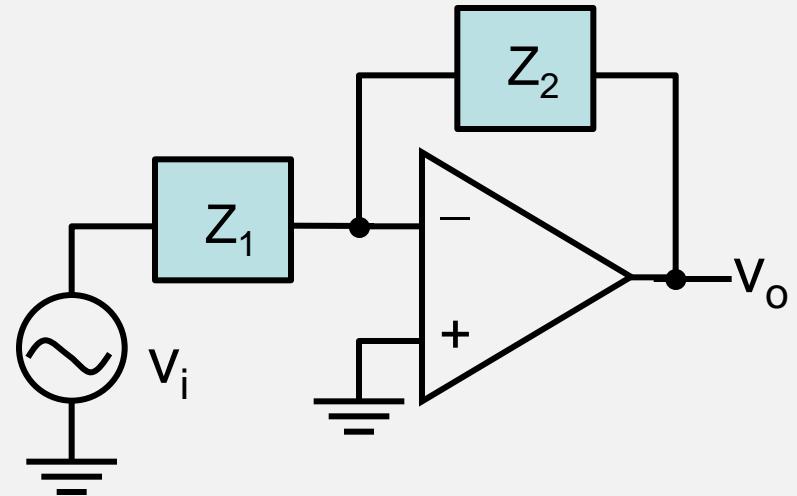
$$\Rightarrow V_o(t) = -\frac{1}{RC} \int V_i(t) \cdot dt$$



# Example: Weighted Summer

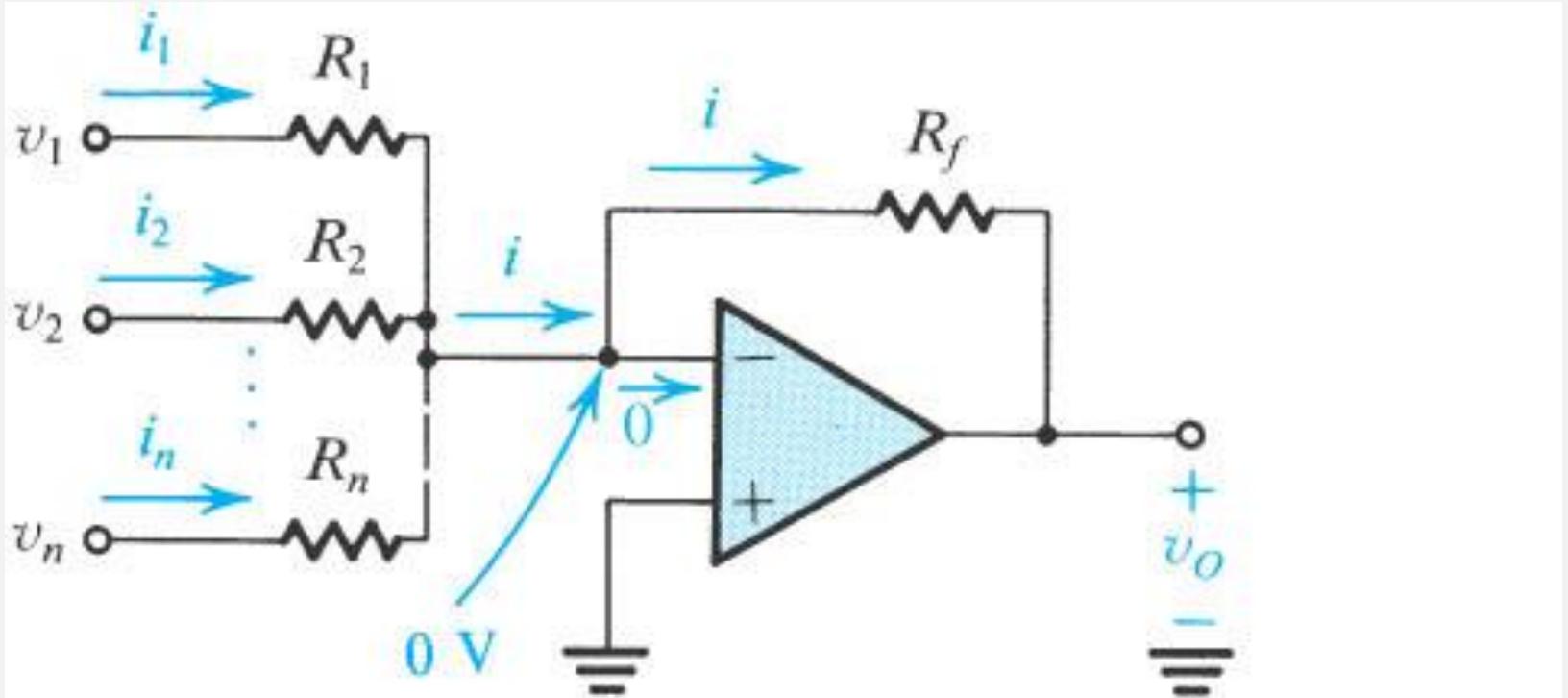

$$v_o = -\left( \frac{R_f}{R_1} \cdot v_1 + \frac{R_f}{R_2} \cdot v_2 + \dots + \frac{R_f}{R_n} \cdot v_n \right)$$

# Opamp電路（二）：Non-Inverting Amplifier


- “Non-inverting” means the gain is positive
- Virtual short, so:

$$V^- = V^+ = V_i$$

$$i_1 = \frac{V^-}{R_1} = \frac{V_i}{R_1}$$



$$V_o = V^- + i_1 \cdot R_2 = V_i + \frac{V_i}{R_1} \cdot R_2$$
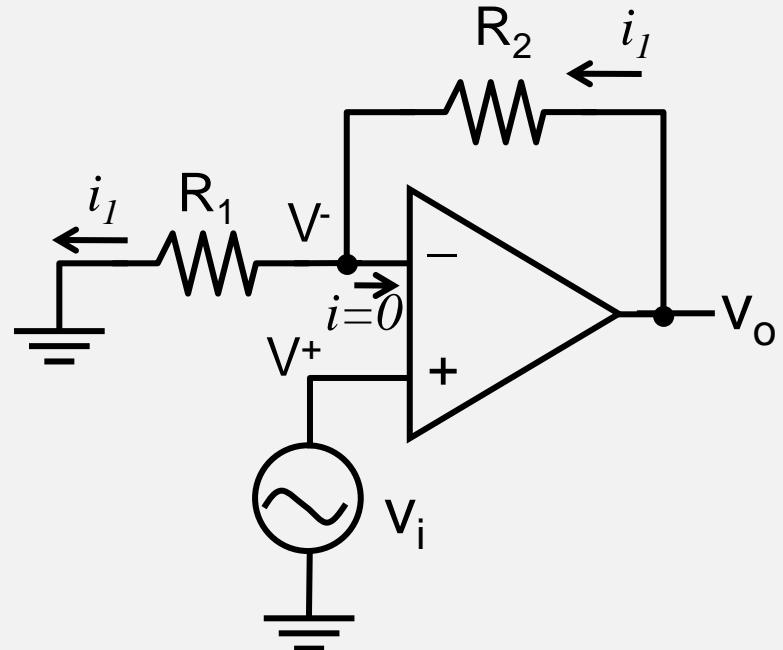
$$\Rightarrow \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$



$R_{in}$  is very large, which is good

# ( 重要 ) Non-Inverting Configuration

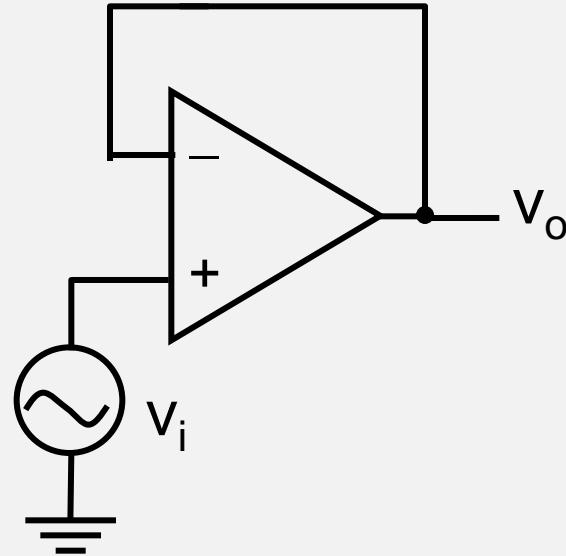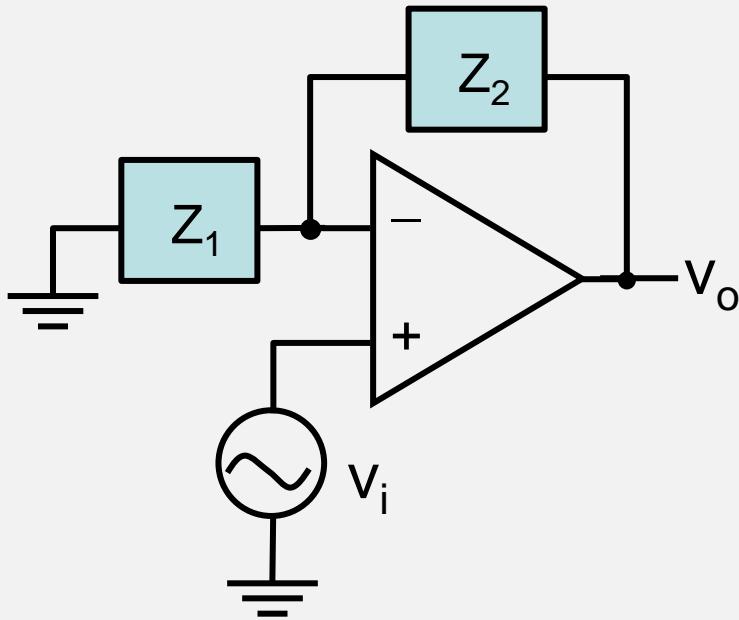

■ Similarly:

$$\frac{V_o(s)}{V_i(s)} = 1 + \frac{Z_2}{Z_1}$$

■ Voltage follower ( $Z_1 = \infty$ ,  $Z_2 = 0$ ) with a gain of 1 and better driving capability

$$\frac{V_o(s)}{V_i(s)} = 1$$

# Difference Amplifier

- It can remove the common-mode signal, and subtract and amplify the differential signal
- By superposition:


$$v_o = \left(1 + \frac{R_4}{R_3}\right) \cdot \left(\frac{R_2}{R_1 + R_2}\right) \cdot v_1 - \frac{R_4}{R_3} \cdot v_2$$

■ For  $R_1 = R_2 = R_3 = R_4$

$$v_o = v_1 - v_2$$

$$\Delta v_i - (R_1 + R_3) \cdot \Delta i + \underbrace{(v^+ - v^-)}_{\approx 0} = 0$$
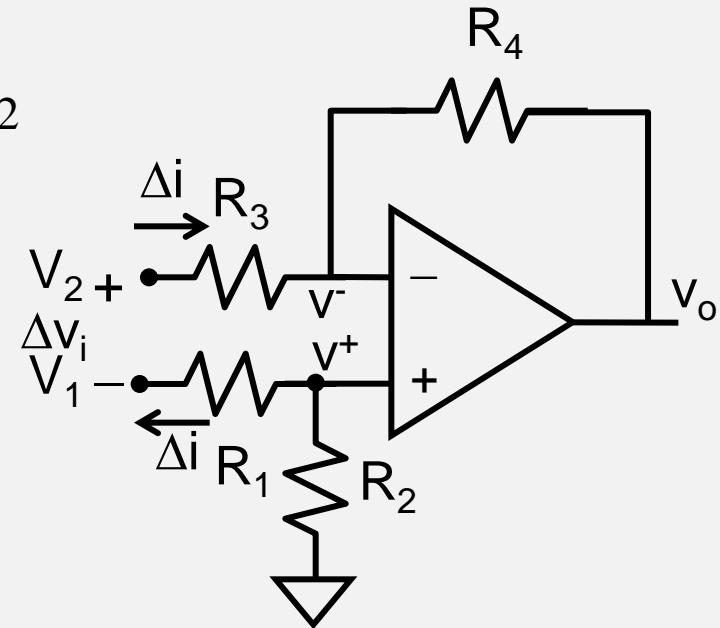
$$R_{in} = \frac{\Delta v_i}{\Delta i} = R_1 + R_3 \quad (\text{Drawback})$$



# High-Input-Impedance Differential-Mode Instrumentation Amplifier

- 提供很大的輸入阻抗


$$v_o = \left(1 + \frac{R_4}{R_3}\right) \cdot \left(\frac{R_2}{R_1 + R_2}\right) \cdot v_1 - \frac{R_4}{R_3} \cdot v_2$$

when  $\frac{R_4}{R_3} = \frac{R_2}{R_1}$

$$v_o = \frac{R_2}{R_1} \cdot (v_1 - v_2)$$

when  $R_1 = R_2 = R_3 = R_4$

$$v_o = v_1 - v_2$$

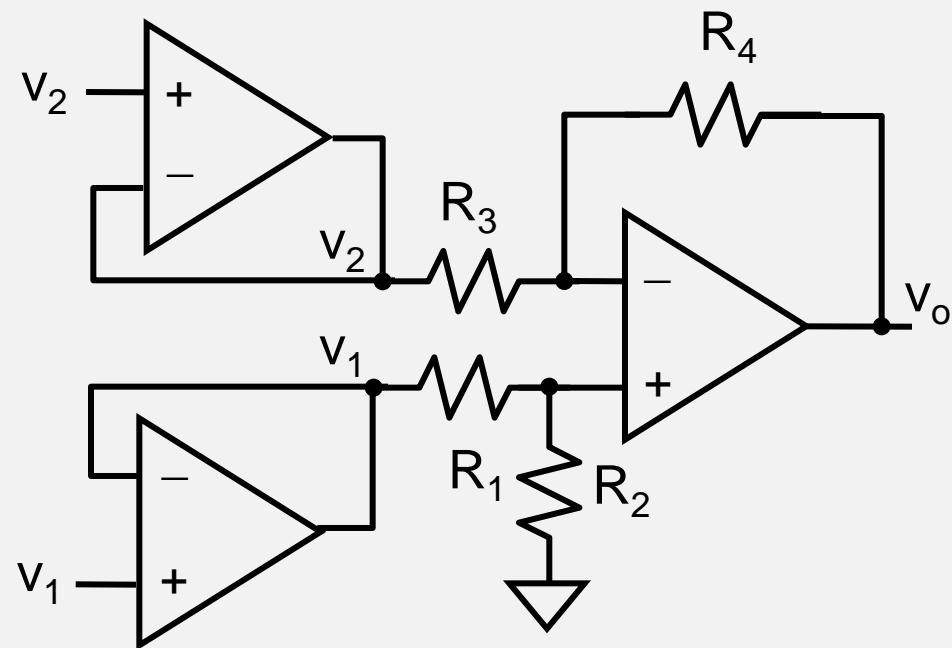

# Variable-Gain Differential-Mode Instrumentation Amplifier (Design Problem IV)

The gain can be conveniently adjusted by tuning  $R_G$


$$v_o = v'_1 - v'_2 \quad (1)$$

$$v'_1 = \left(1 + \frac{R_1}{R_G}\right) \cdot v_1 - \frac{R_1}{R_G} \cdot v_2 \quad (2)$$

$$v'_2 = \left(1 + \frac{R_1}{R_G}\right) \cdot v_2 - \frac{R_1}{R_G} \cdot v_1 \quad (3)$$


Substitute (2)(3) into (1):
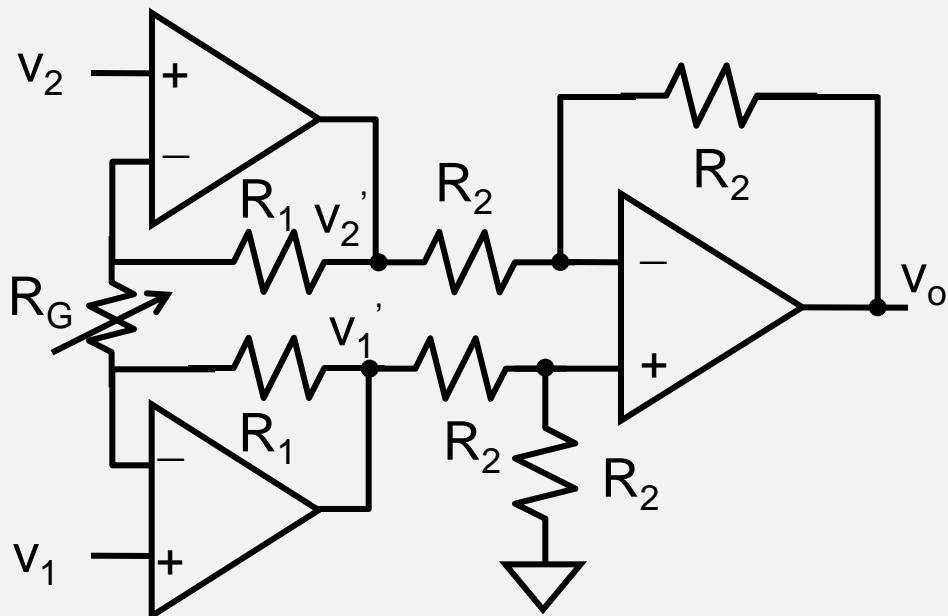
$$v_o = \left(1 + \frac{2R_1}{R_G}\right) \cdot (v_1 - v_2)$$


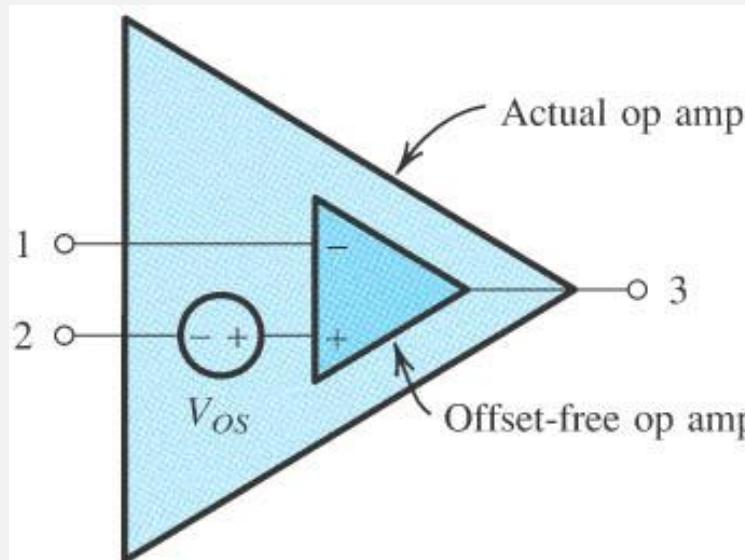
# Non-Ideal Effect in Op-amp: Offset Voltage

- Input offset voltage  $V_{os}$  occurs due to internal imbalances in the input differential amplifier
  - Result: Real op-amps have a non-zero output even if the DC level of two inputs are the same
  - How to reduce the non-zero output to avoid output saturation in an amplifier?






# Reduce the Output Change due to $V_{os}$

- In a non-inverting amplifier, the input dc offset is amplified by:


$$V_o = \left(1 + \frac{R_2}{R_1}\right) \cdot V_{os}$$

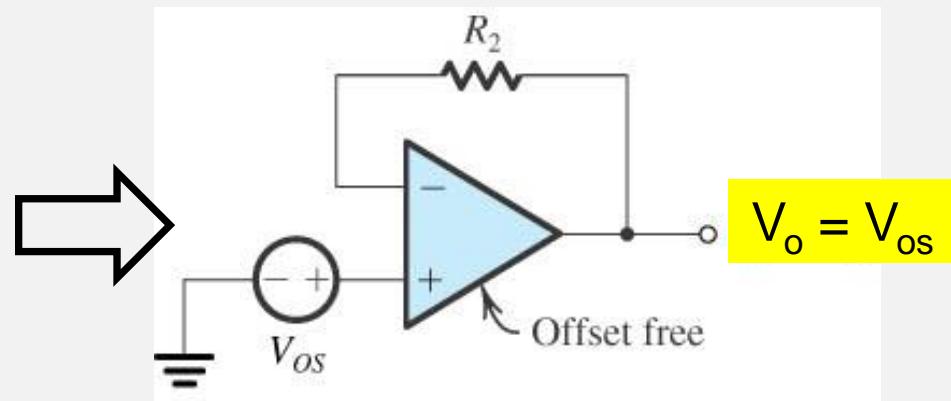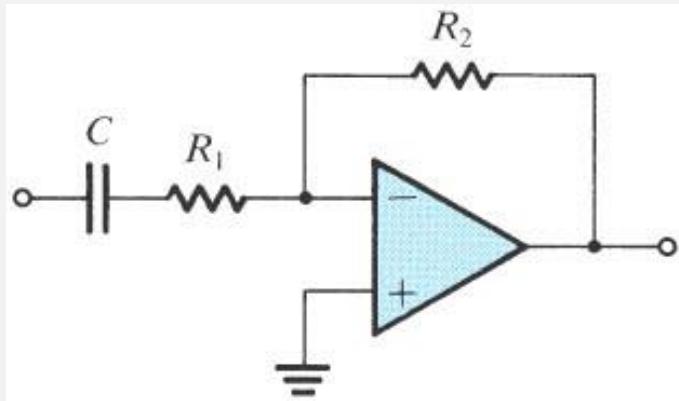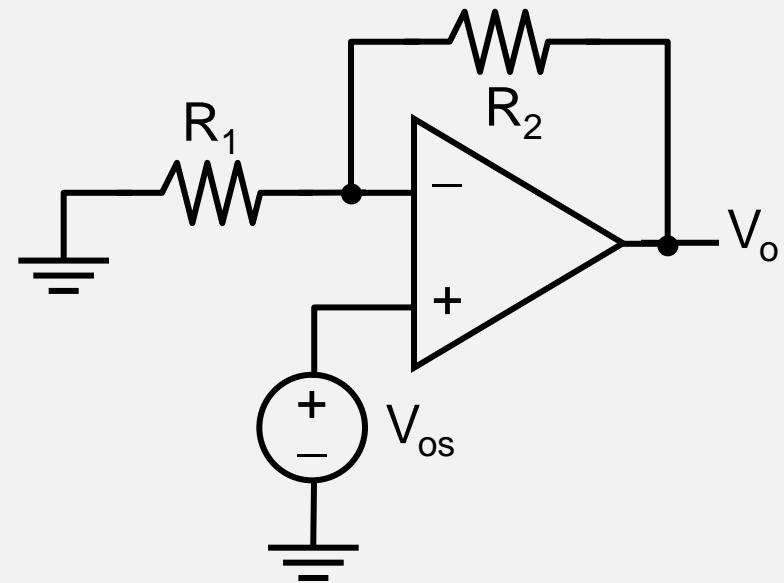- Add a capacitor to reduce the output due to  $V_{os}$


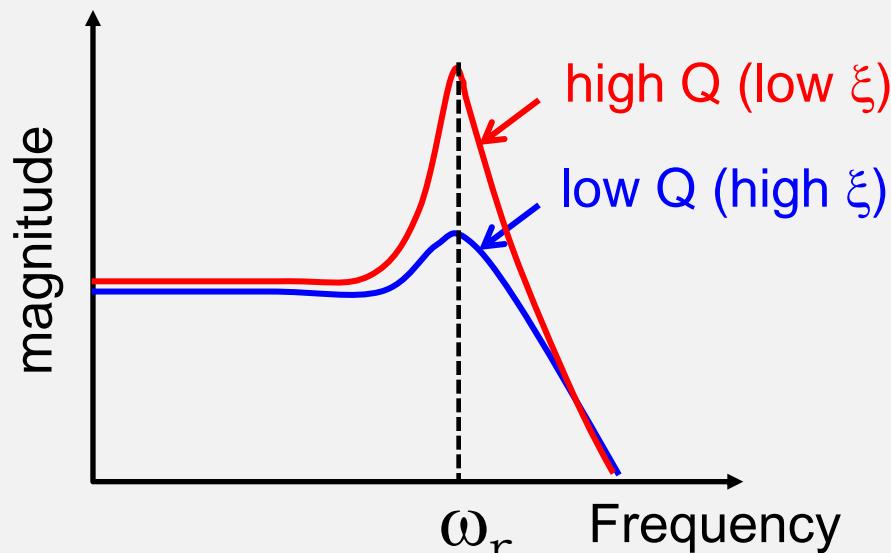
# Quality Factor (Q) of a Frequency Response

- A parameter to evaluate the energy-dissipating behavior of a circuit near its resonant frequency
  - High Q: a large resonant peak and thus low energy dissipation
  - Low Q: a small resonant peak and thus high energy dissipation
- As shown, frequency responses of a low-Q and a high-Q filters:




# Reminder: the Frequency Response (Magnitude) of a 2<sup>nd</sup>-Order System for Different Damping Ratios $\xi$

$$H(s) = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$|H(j\omega)|_{\omega=0} = 1$$

$$|H(j\omega)|_{\omega=\omega_n} = \frac{1}{2\xi}$$

$$|H(j\omega)|_{\omega=\infty} = 0$$

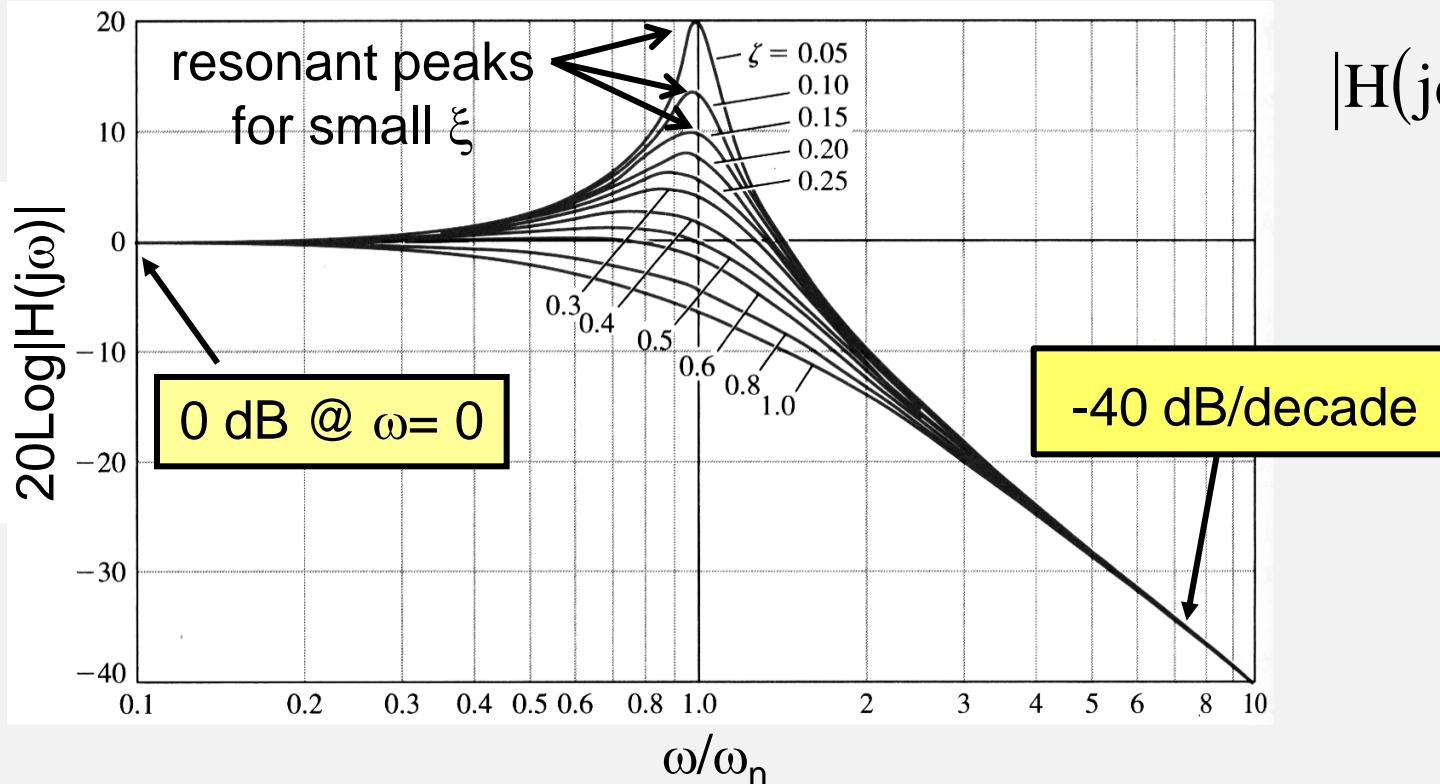

# Definition : Quality Factor (Q)

---


- The resonant peak magnitude is related to energy dissipation
- Definition:

$$Q \equiv \frac{\text{Energy stored}}{\text{Average energy dissipated per radian}}$$

- Q is a dimensionless parameter and related to the damping ratio by  $Q \approx 1 / (2\xi)$
- $Q = \infty$  implies there is no energy dissipation when a circuit oscillates
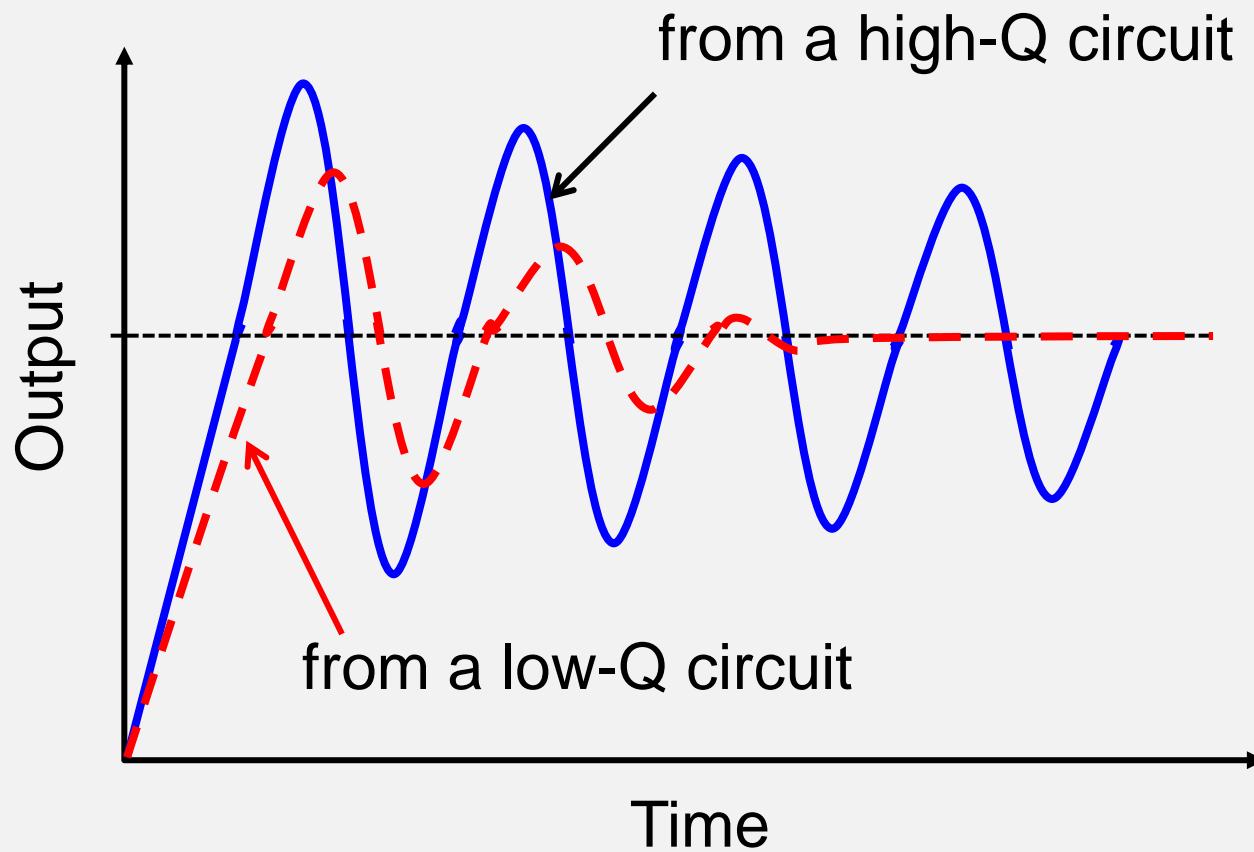
# Step Response vs. Q


- A high-Q circuit has low energy dissipation, and long oscillation time in its step response


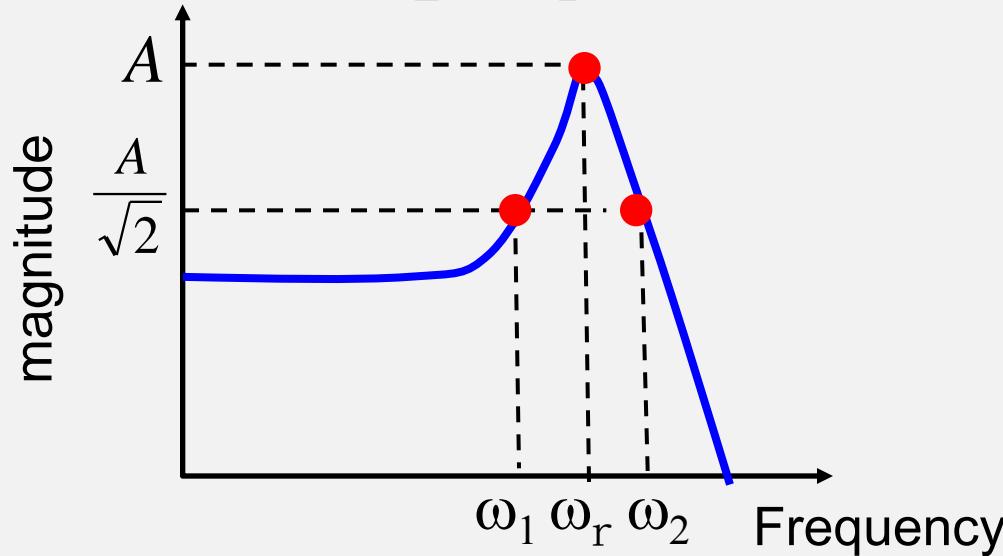
# Obtain Q by Analysis or Experiment

- Q can be obtained by analysis:
  - For  $\xi << 1$ , Q is related to the damping ratio by  $Q \approx 1 / (2\xi)$ 。  
Remember: Q and  $\xi$  are both dimensionless
- Q can be obtained by experiment using the half-power bandwidth (defined by  $\omega_1$  and  $\omega_2$ ):

$$Q = \frac{\omega_r}{\omega_2 - \omega_1} \quad (\text{重要！你實驗demo Q值要用到})$$




# Example: Q of a Low-Pass Filter

Transfer function is given by:

$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

where  $\omega_n = \frac{1}{\sqrt{LC}}$  natural frequency

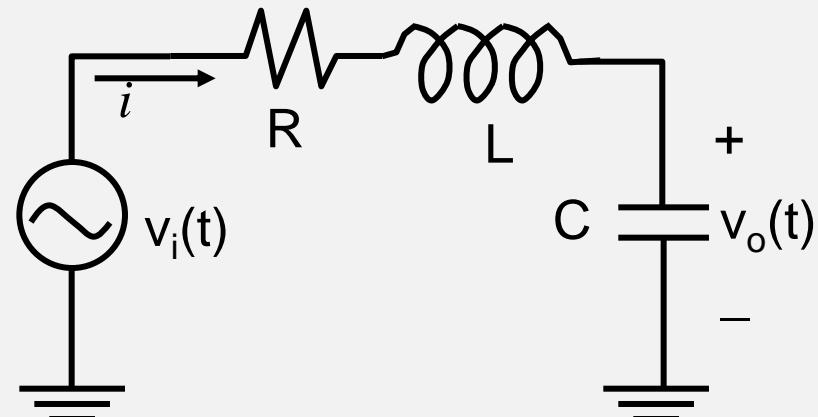and  $\xi = \frac{R}{L} \cdot \frac{1}{2\omega_n} = \frac{R}{2} \sqrt{\frac{C}{L}}$



$$So Q = \frac{1}{2\xi} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


# Active Filters

---

- In addition to passive elements, operational amplifiers are used to build an “active” filter
- 特色：
  - A voltage gain more than one can be achieved
  - An active filter can achieve the frequency response of a standard 2nd-order R-L-C circuit without the use of an inductor
  - An active filter can achieve higher-order filters ( $> 2^{\text{nd}}$  order) with better attenuation
    - » Note: 1<sup>st</sup>-order filter: -20 dB/decade, 2<sup>nd</sup>-order filter: -40 dB/decade, nth-order =  $-20 \times n$  dB/decade
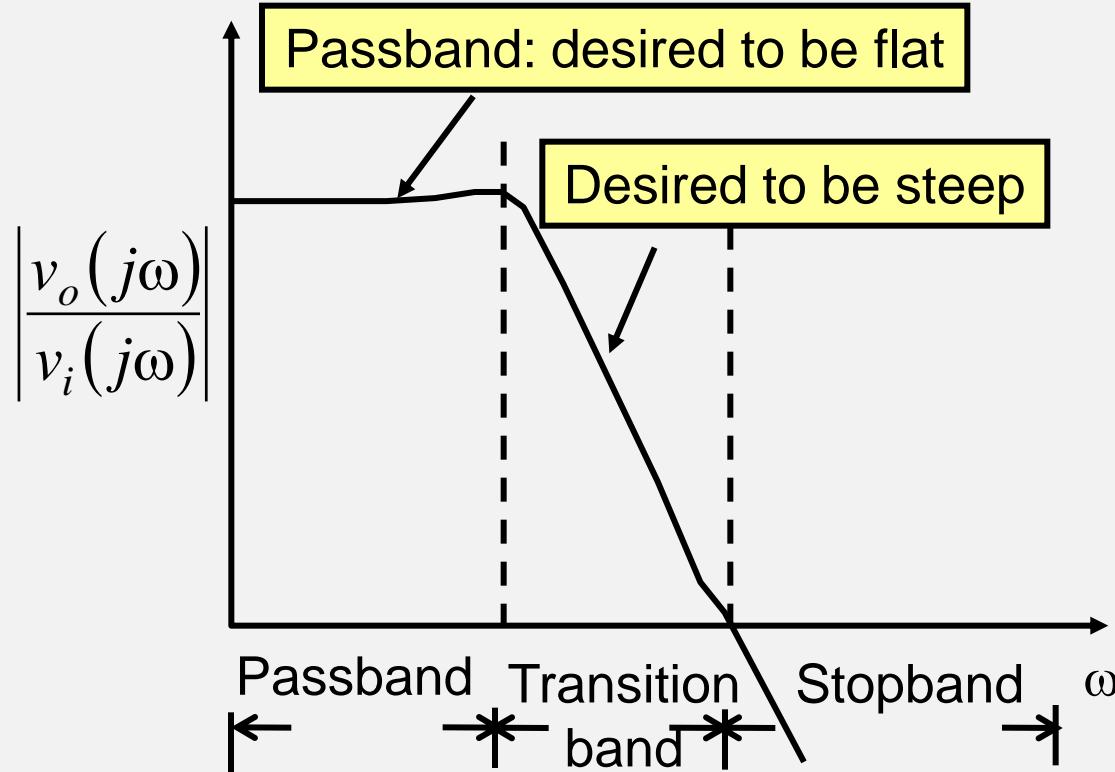
# Filter Design and Specifications

- It is usually desired to achieve a flat passband and a high roll-off rate (depending on the applications) in the transition band





# Types of Active Filters

---

- First-order active filters :
  - Low-pass, high-pass, band-pass, and band-reject filters
- Second-order active filters :
  - Sallen-Key filter
  - Biquad filter
  - State-Variable filter
  - ...etc.
- Higher-order active filters:
  - Butterworth、Chebyshev、Cauer (elliptic)、Bessel filters, etc

# First-Order Circuit: Differentiator

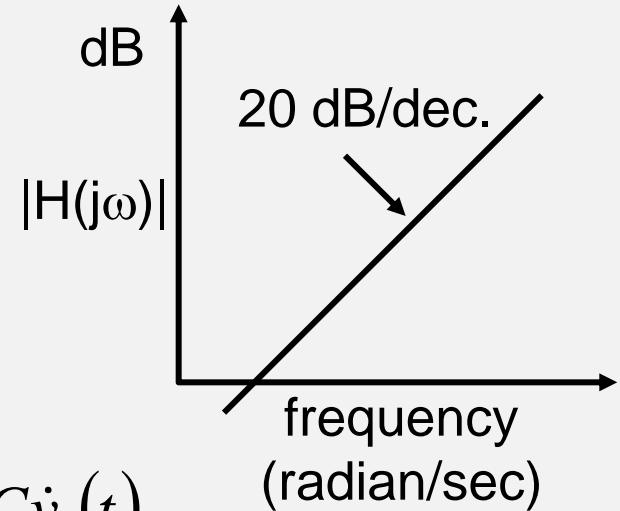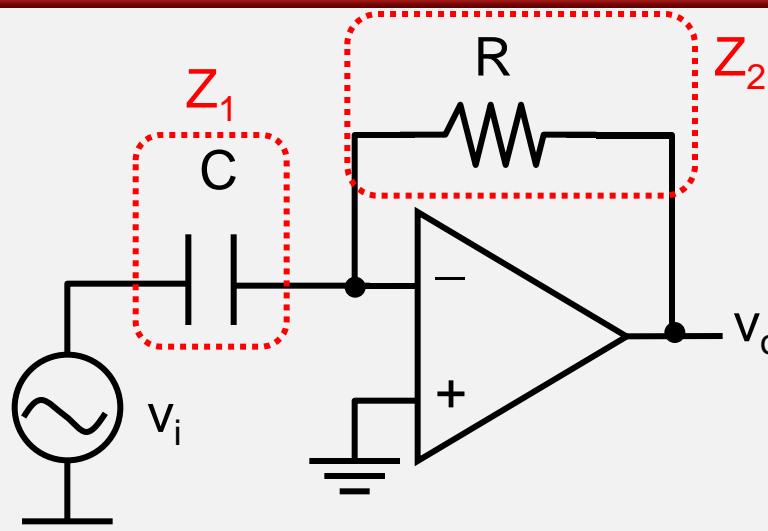


$$H(s) = \frac{v_o(s)}{v_i(s)} = -\frac{Z_2}{Z_1} = -sRC, v_o(t) = -RC\dot{v}_i(t)$$

$$\Rightarrow H(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = -j\omega RC$$


- $\therefore |H(j\omega)| = \omega RC$
1. 頻率每增加十倍，增益也增為十倍（即20 dB/dec）
  2.  $H(j0) = 0 = -\infty \text{ dB}$

# Integrator

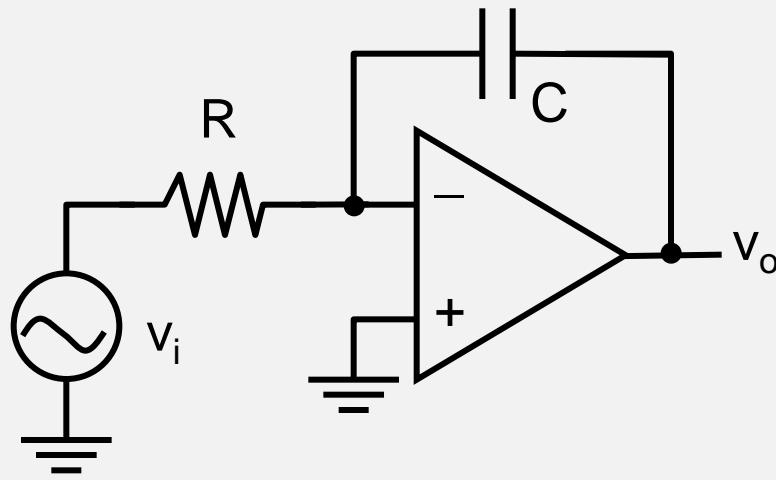


$$H(s) = \frac{v_o(s)}{v_i(s)} = -\frac{1}{sRC}, \quad v_o(t) = -\frac{\int_0^t v_i(t) dt}{RC}$$

$$\therefore |H(j\omega)| = \frac{1}{\omega RC}$$

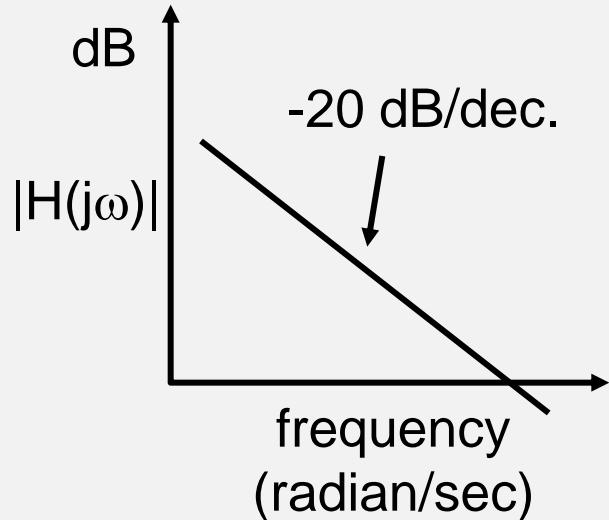

1. 頻率每增加十倍，增益減為十分之一（即-20 dB）
2.  $|H(j0)| = \infty$


# Low-Pass Filter with Gain

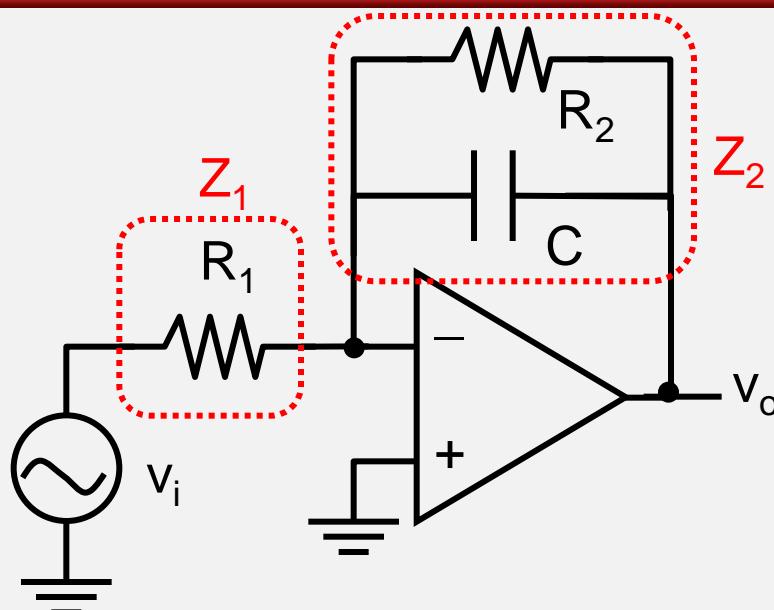

$$H(s) = \frac{v_o(s)}{v_i(s)} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1} \frac{1}{sR_2C + 1}$$

$$\therefore |H(j\omega)| = \frac{R_2}{R_1} \frac{1}{\sqrt{\omega^2 R_2^2 C^2 + 1}}$$

$\frac{1}{R_2C}$  is the -3dB frequency

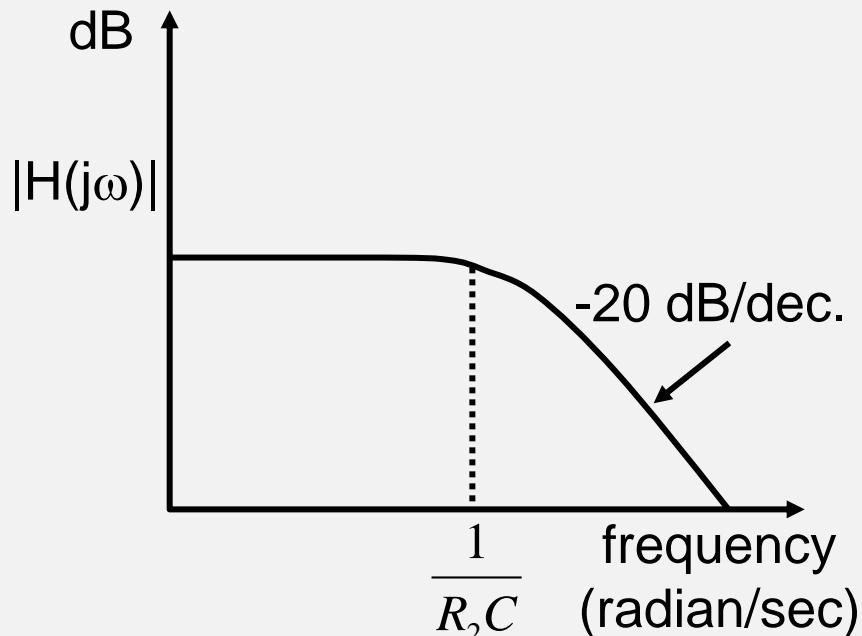


$$|H(j\omega)|_{\omega=0} = \frac{R_2}{R_1}$$

$$|H(j\omega)|_{\omega=\frac{1}{R_2C}} = 0.707 \frac{R_2}{R_1}$$

$$|H(j\omega)|_{\omega=\infty} = 0$$


# High-Pass Filter with Gain

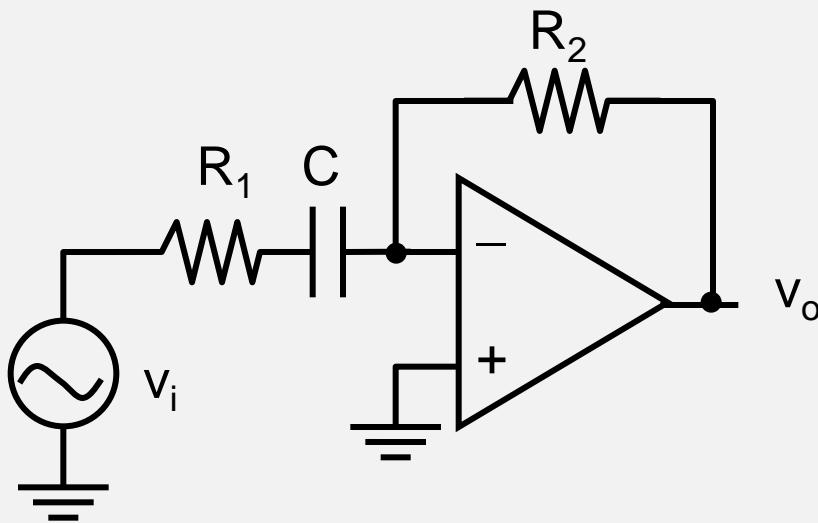

$$H(s) = \frac{v_o(s)}{v_i(s)} = -\frac{R_2}{R_1} \frac{sR_1C}{sR_1C + 1}$$

$$\therefore |H(j\omega)| = \frac{R_2}{R_1} \frac{\omega R_1 C}{\sqrt{\omega^2 R_1^2 C^2 + 1}}$$

$\frac{1}{R_1 C}$  is the -3dB frequency

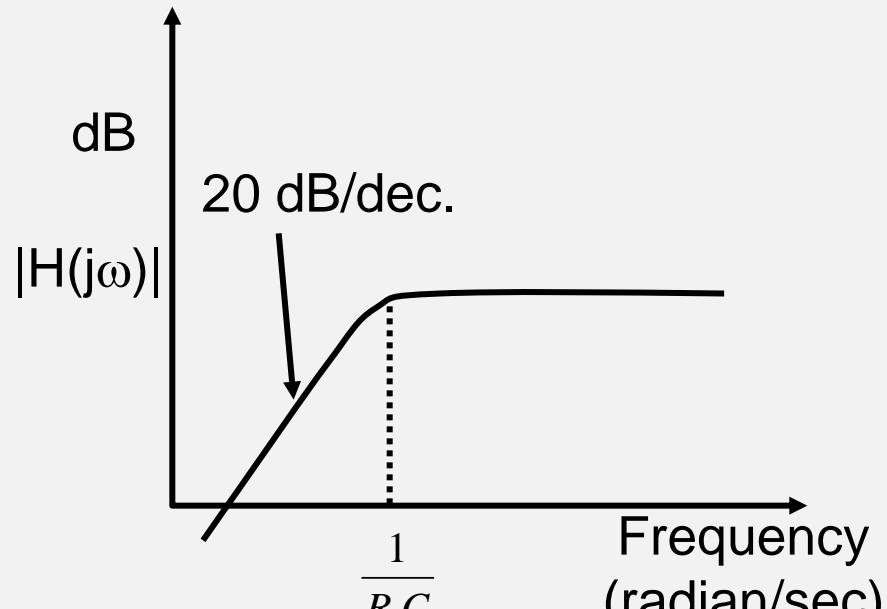


$$|H(j\omega)|_{\omega=0} = 0$$


$$|H(j\omega)|_{\omega=\frac{1}{R_1 C}} = 0.707 \frac{R_2}{R_1}$$

$$|H(j\omega)|_{\omega=\infty} = \frac{R_2}{R_1}$$


# Band-Pass Filter

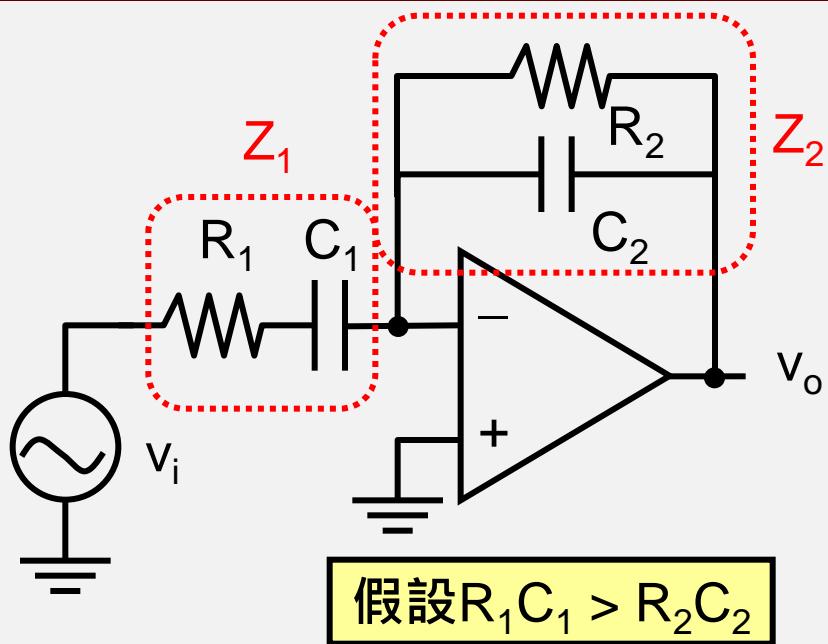

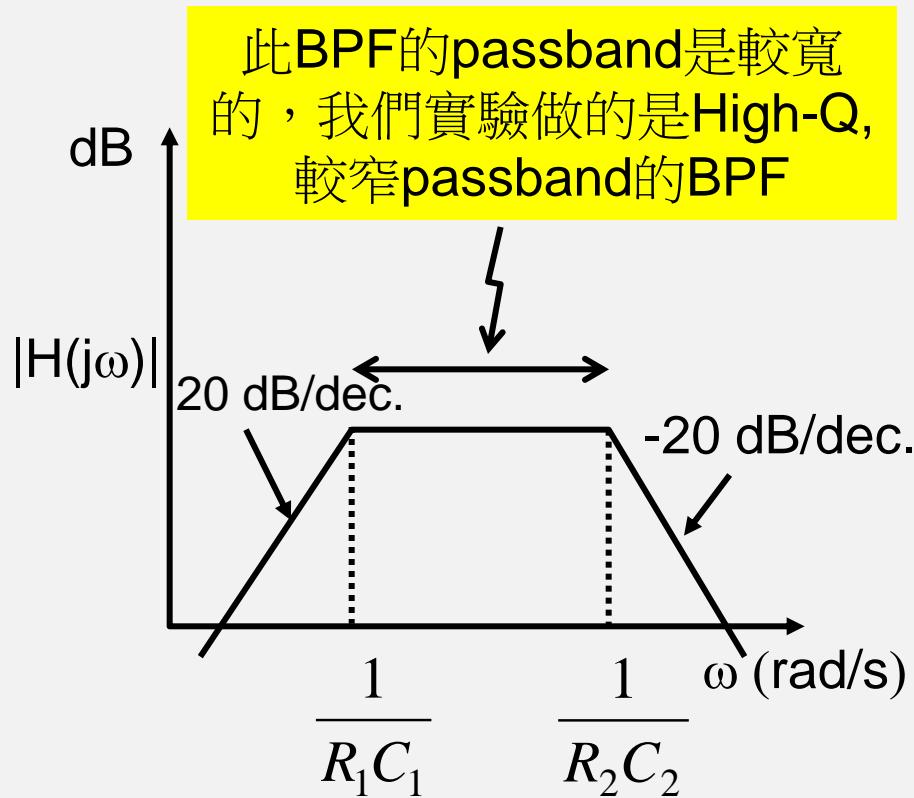
$$\begin{aligned}
 H(s) &= \frac{v_o(s)}{v_i(s)} = -\frac{Z_2}{Z_1} \\
 &= -\frac{R_2}{R_1} \frac{sR_1C_1}{sR_1C_1 + 1} \cdot \frac{1}{sR_2C_2 + 1}
 \end{aligned}$$



# Band-Reject Filter

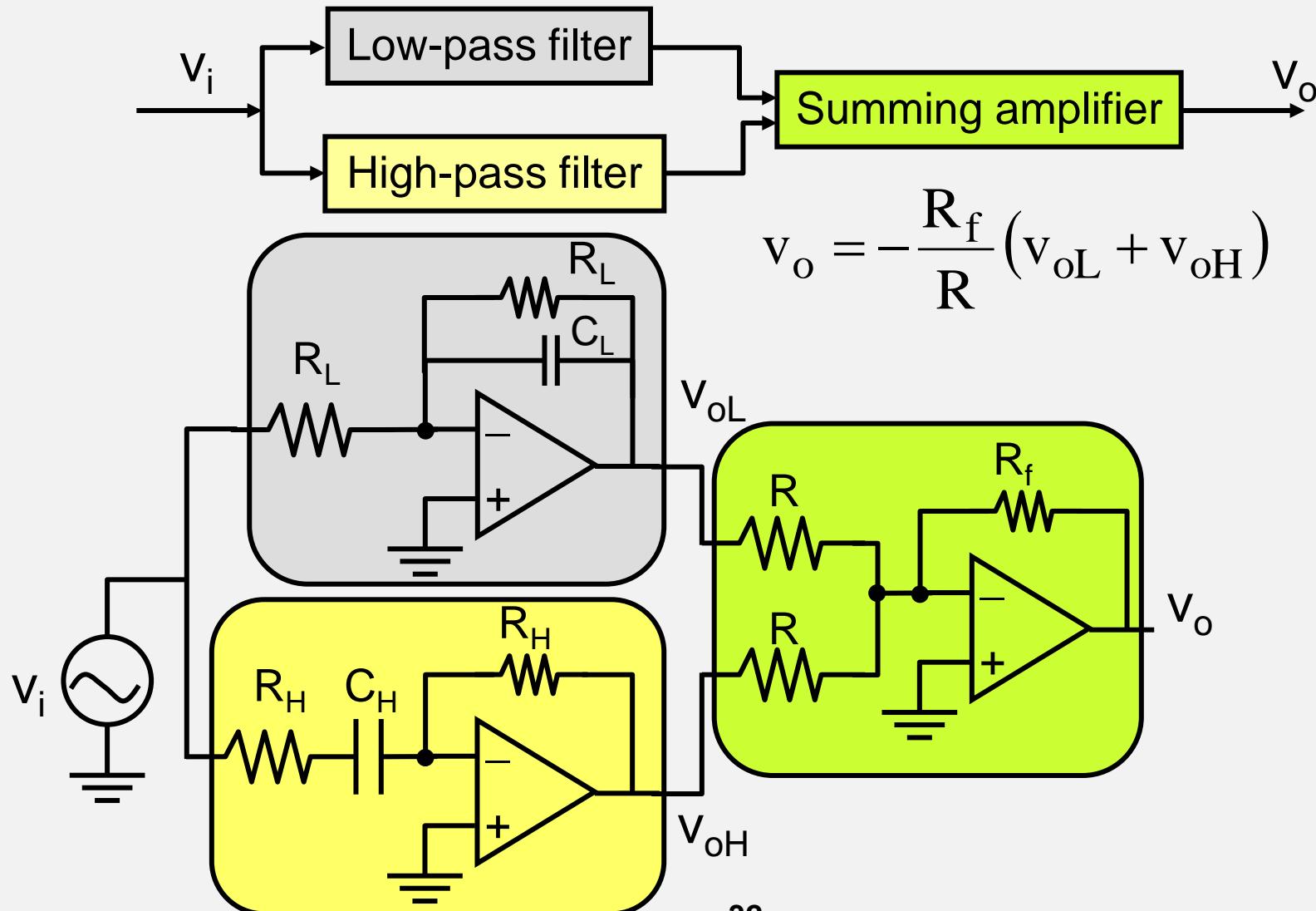

# Cont'd: Frequency Response

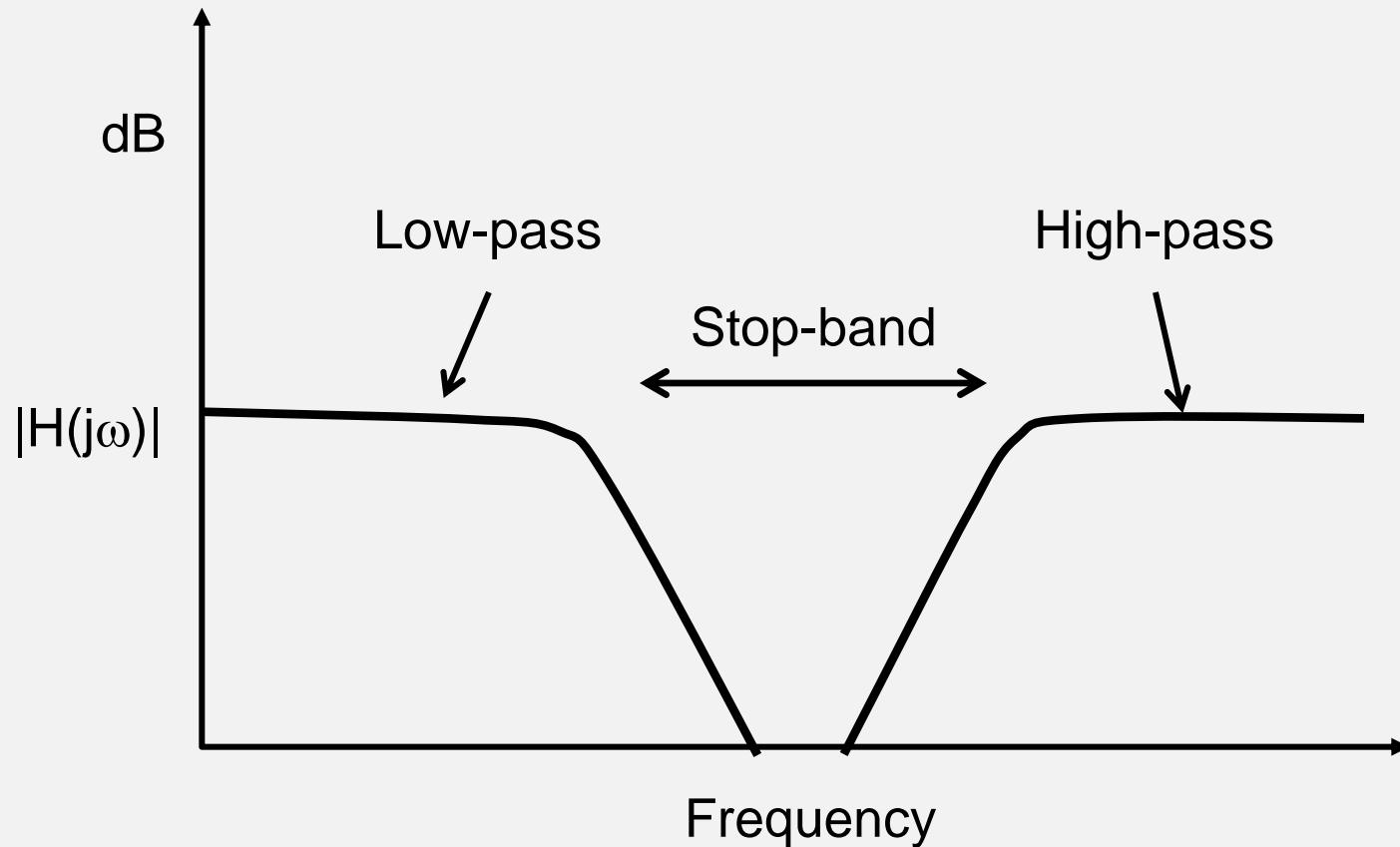

# 2nd-Order Active Filter: Sallen-Key Low-Pass Filter

- Define the non-inverting gain:


$$K = 1 + \frac{R_B}{R_A}$$

- The output  $v_o$ :

$$\begin{aligned} v_o &= Kv_+ \\ &= K \left( \frac{1}{R_2 C_2 s + 1} \cdot v_x \right) \end{aligned}$$

- Summing currents at node  $v_x$ :
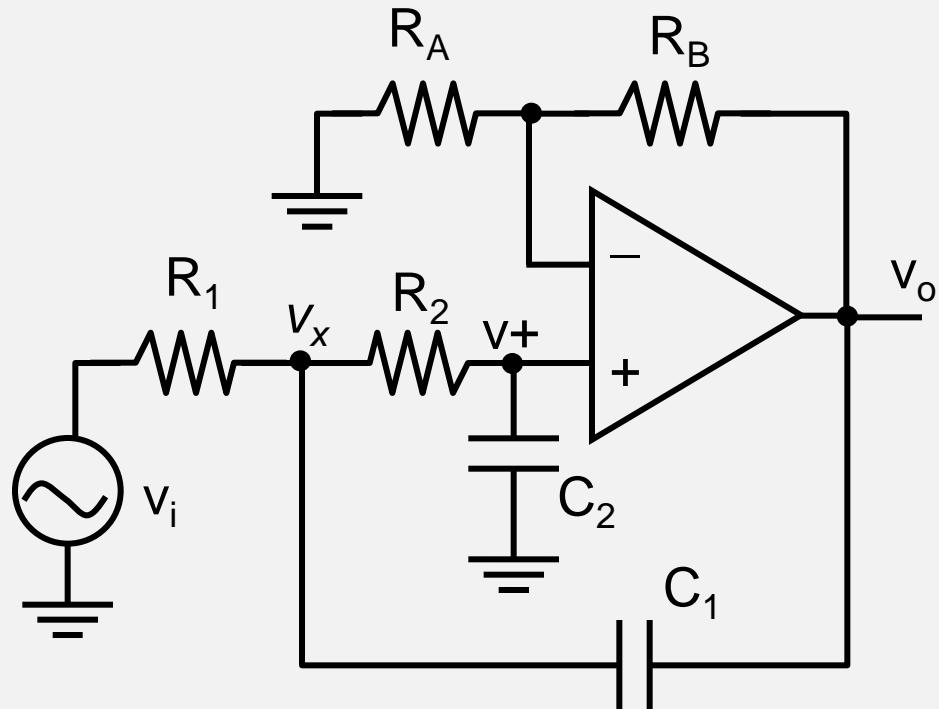
$$\frac{v_i - v_x}{R_1} + \frac{v_+ - v_x}{R_2} + \frac{v_o - v_x}{1/(sC_1)} = 0$$



# Cont'd

## ■ The transfer function:

$$\frac{v_o(s)}{v_i(s)} = \frac{K}{R_1 C_1 R_2 C_2 s^2 + [(1-K)R_1 C_1 + R_1 C_2 + R_2 C_2]s + 1}$$

For solving  $\omega_n$  and  $\xi$  (i.e., Q), remember to use the form:


$$\underline{s^2 + 2\xi\omega_n s + \omega_n^2}$$

## ■ The gain rolls off after the natural frequency:


$$\omega_n = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$Q = \frac{1}{2\xi} = \frac{\sqrt{R_1 C_1 R_2 C_2}}{(1-K)R_1 C_1 + R_1 C_2 + R_2 C_2}$$

# State-Variable Filter (KHN Filter)

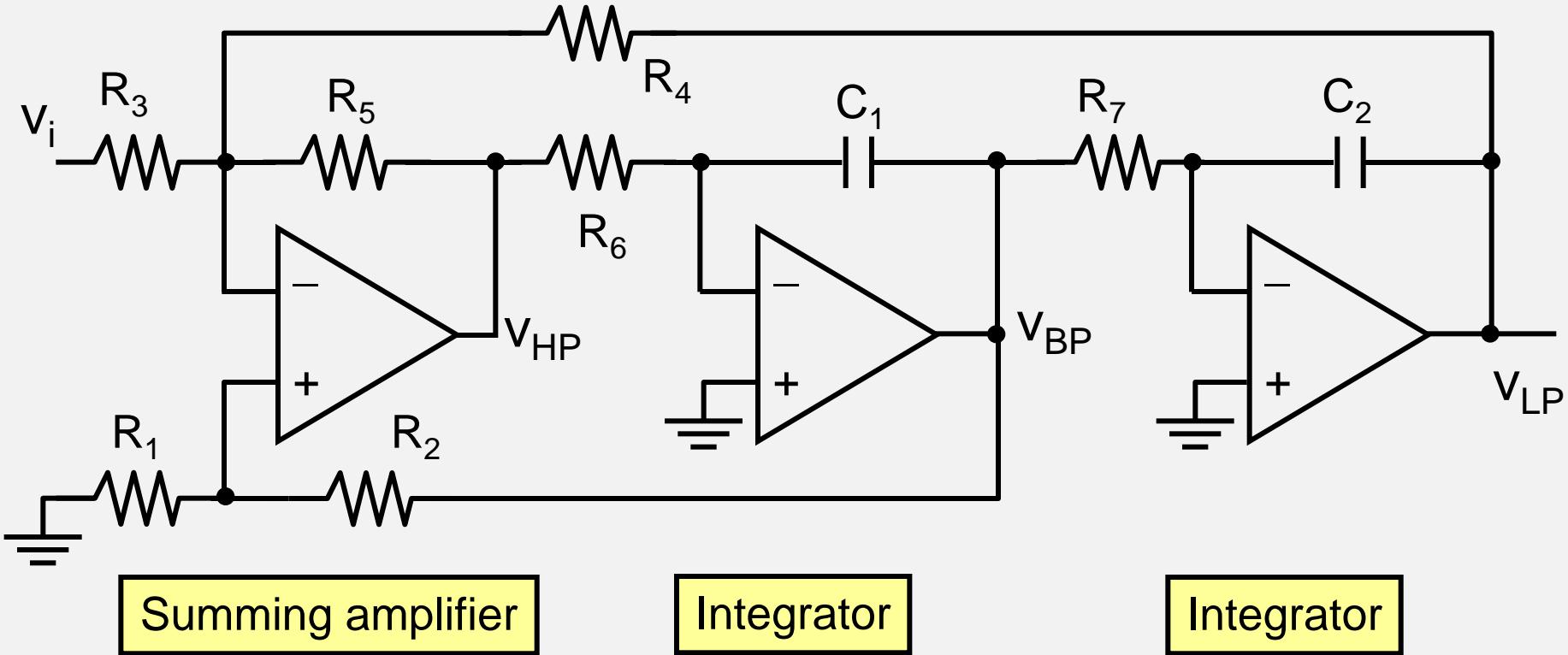

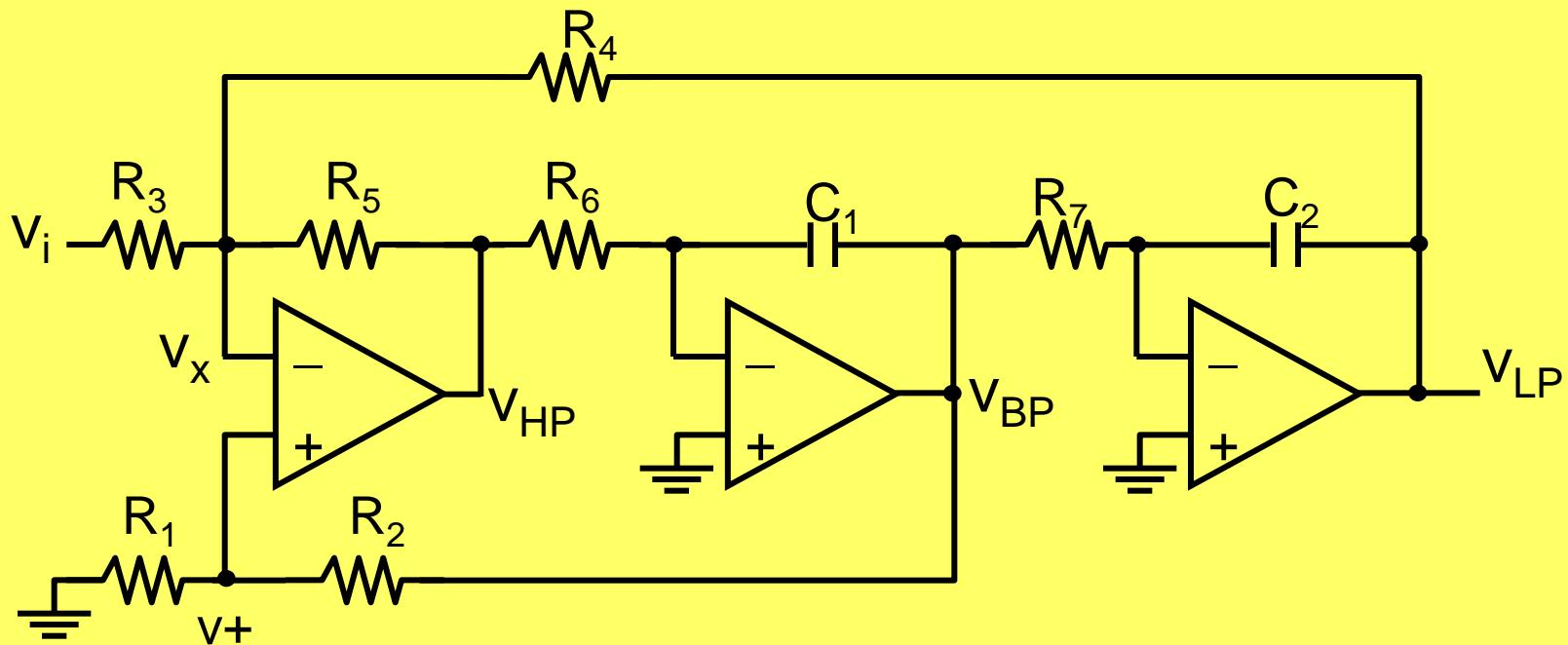- It simultaneously realizes the high-pass ( $v_{HP}$ ), band-pass ( $v_{BP}$ ) and low-pass ( $v_{LP}$ ) frequency responses




By KCL at  $V_x$ :  $\frac{V_i - V_x}{R_3} + \frac{V_{LP} - V_x}{R_4} + \frac{V_{HP} - V_x}{R_5} = 0 \quad (1)$

$$V_x = \frac{R_1}{R_1 + R_2} V_{BP} \quad (2)$$

$$v_{BP} = -\frac{1}{sR_6C_1} v_{HP} \quad (3)$$

$$v_{LP} = -\frac{1}{sR_7C_2} v_{BP} = \frac{1}{s^2 R_6 R_7 C_1 C_2} v_{HP} \quad (4)$$


(3)代入(2)，其結果再與(4)一起代入(1)

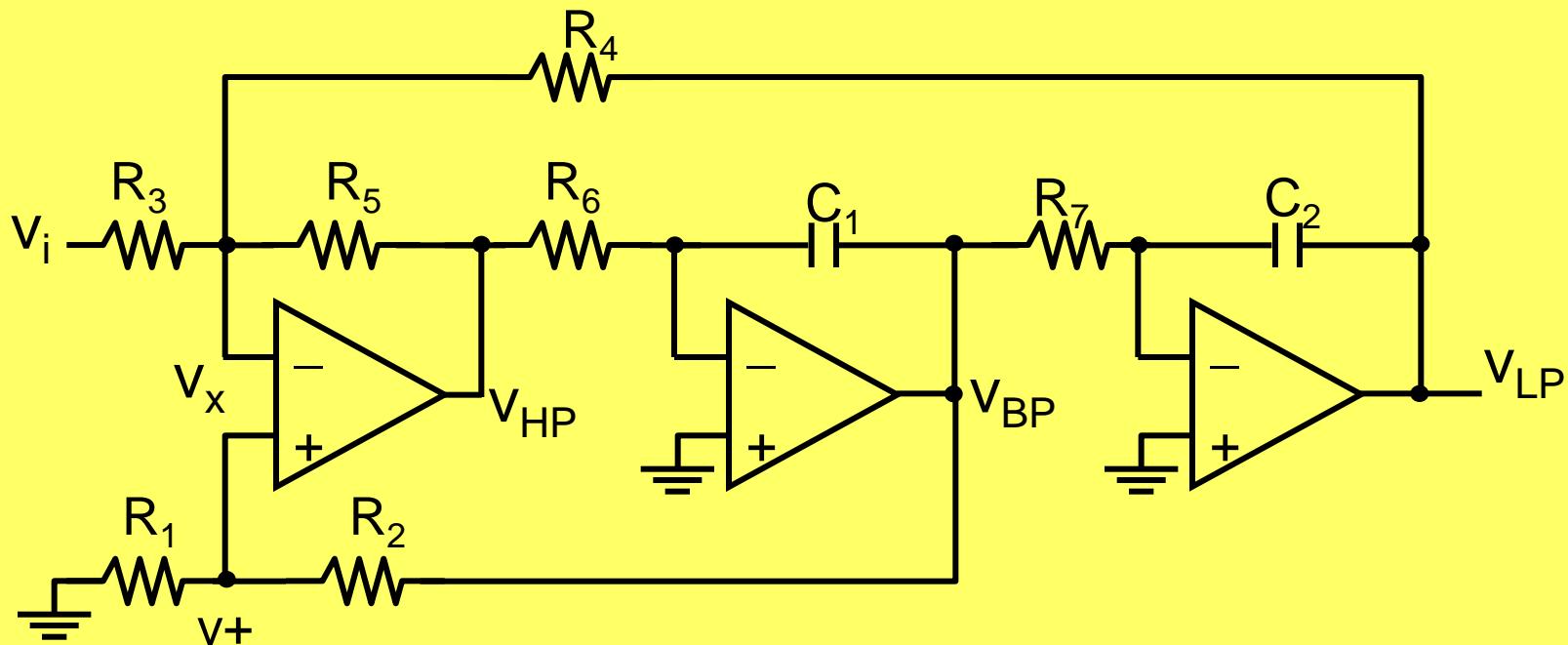

$$\therefore \frac{V_{HP}(s)}{V_i(s)} = -\frac{1}{R_3} \cdot \frac{\frac{R_4 R_6 R_7 C_1 C_2 s^2}{R_5}}{\frac{R_4 R_6 R_7 C_1 C_2}{R_5} s^2 + \frac{R_4 R_7 C_2 (1 + R_5/R_3 + R_5/R_4)}{(1 + R_2/R_1) R_5} s + 1}$$


$$\therefore \omega_n = \frac{\sqrt{R_5/R_4}}{\sqrt{R_6 C_1 R_7 C_2}} \quad Q = \frac{1}{2\xi} = \frac{(1 + R_2/R_1) \sqrt{R_5 R_6 C_1 / R_4 R_7 C_2}}{1 + R_5/R_3 + R_5/R_4}$$

記得如何得到  $\xi$  嗎？

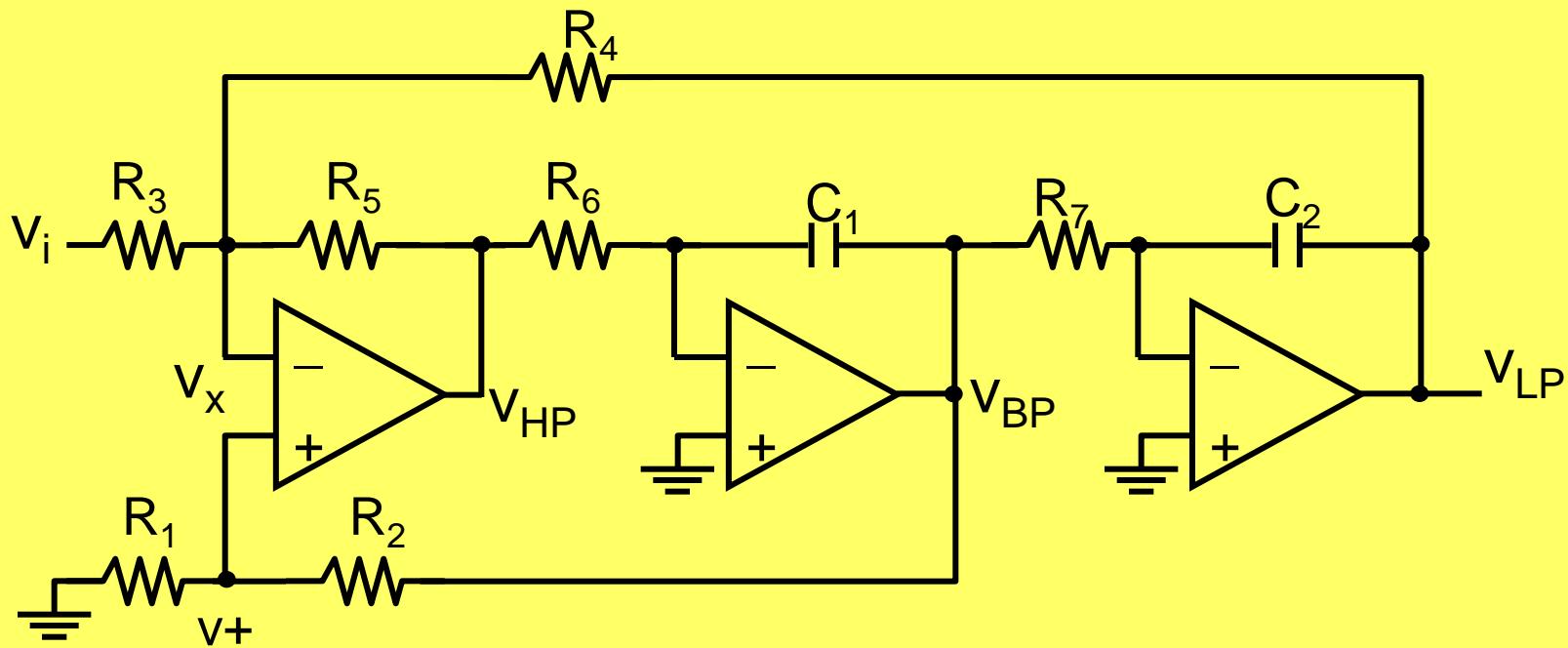

$$\therefore \frac{V_{BP}(s)}{V_i(s)} = -\frac{1}{sR_6C_1} \cdot \frac{V_{HP}(s)}{V_i(s)}$$

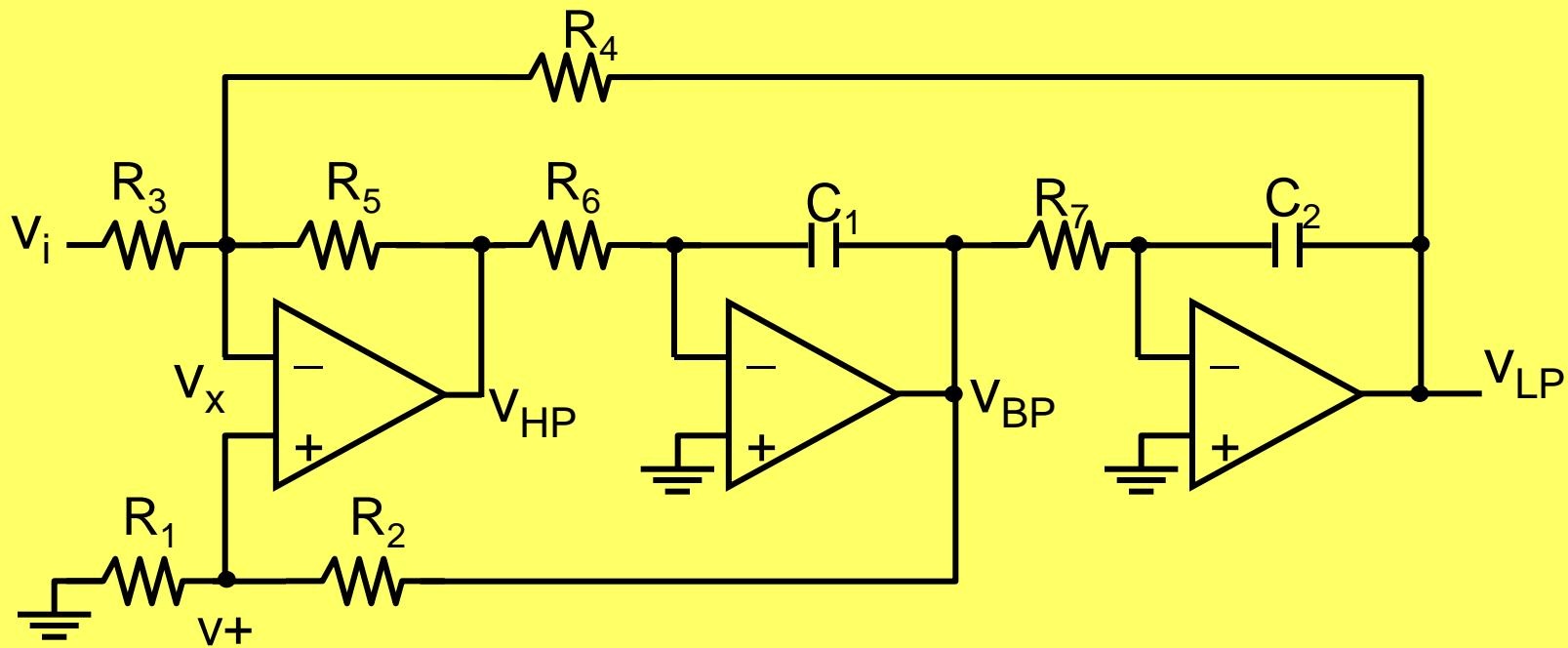
$$= \frac{1}{R_3} \cdot \frac{\frac{R_4R_7C_2s}{R_5}}{\frac{R_4R_6R_7C_1C_2}{R_5}s^2 + \frac{R_4R_7C_2(1+R_5/R_3+R_5/R_4)}{(1+R_2/R_1)R_5}s + 1}$$



$$\therefore \frac{V_{LP}(s)}{V_i(s)} = -\frac{1}{sR_7C_2} \cdot \frac{V_{BP}(s)}{V_i(s)}$$

$$= -\frac{R_4}{R_3} \cdot \frac{\frac{1}{R_4R_6R_7C_1C_2}s^2 + \frac{R_4R_7C_2(1+R_5/R_3+R_5/R_4)}{(1+R_2/R_1)R_5}}{s+1}$$
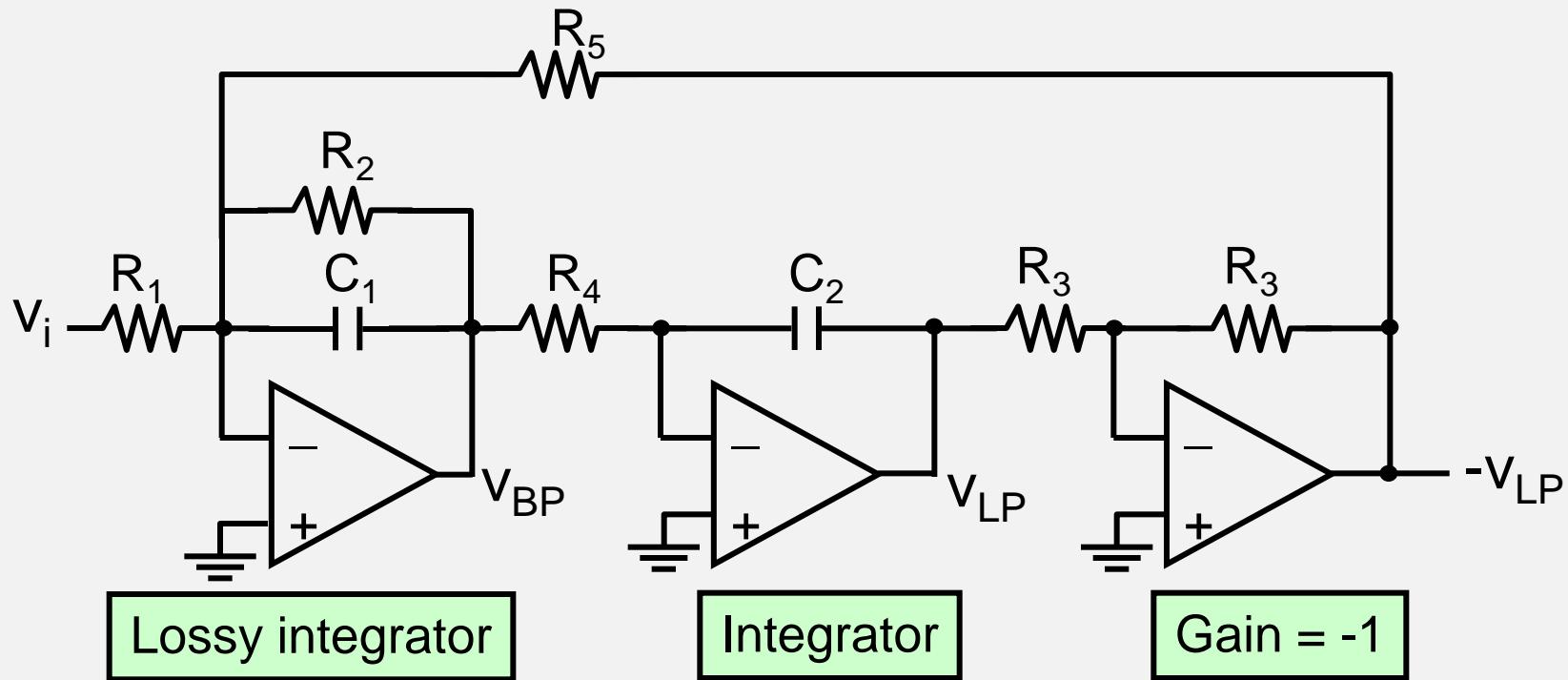
# Biquad Filter (Tow-Thomas Filter) (Design Problem I)



- It simultaneously realizes the band-pass ( $v_{BP}$ ) and low-pass ( $v_{LP}$ ) frequency responses

# Cont'd: Please Derive $\frac{v_{LP}(s)}{v_i(s)}$ on Your Own

At the inverting node of first op amp, by KCL:

$$\frac{V_i}{R_1} - \frac{V_{LP}}{R_5} + \frac{V_{BP}}{R_2} + \frac{V_{BP}}{1/sC_1} = 0 \quad (1)$$


$$\text{and } v_{LP} = -\frac{V_{BP}}{R_4 C_2 s} \quad (2)$$

Solve (1) and (2):

$$\therefore \frac{v_{LP}(s)}{v_i(s)} = \frac{R_5}{R_1} \cdot \frac{1}{R_4 R_5 C_1 C_2 s^2 + \frac{R_4 R_5 C_2}{R_2} s + 1}$$


$$\therefore \omega_n = \frac{1}{\sqrt{R_4 C_1 R_5 C_2}} \quad Q = \frac{R_2 \sqrt{C_1}}{\sqrt{R_4 R_5 C_2}}$$
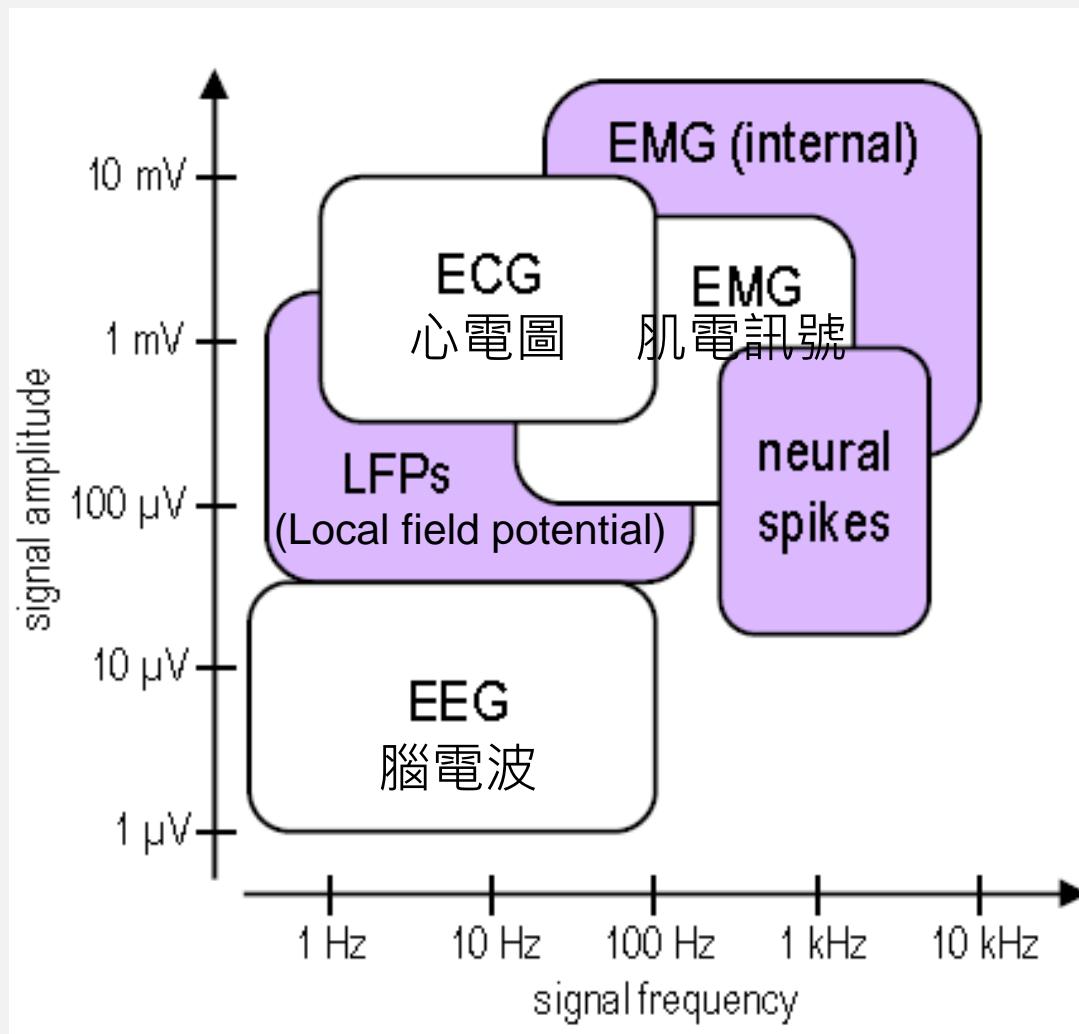
# ECG: Figure Out Your Design for the Specific Application First!



- : measured from skin
- : measured internally

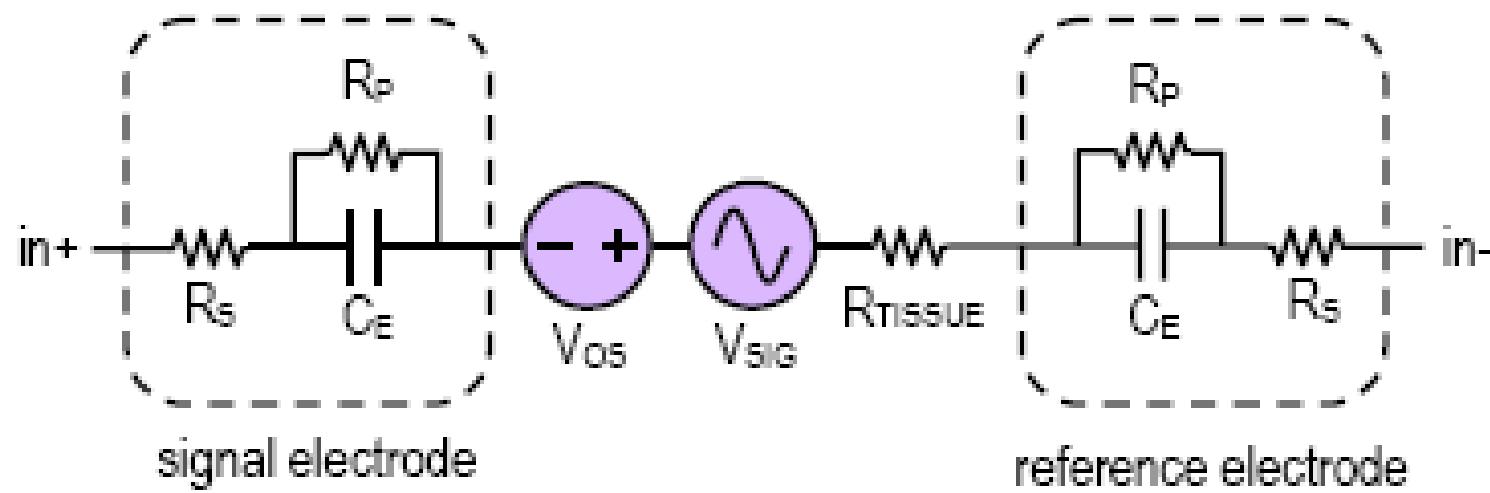
# 訊號與阻抗：Model of Electrode-Electrolyte Interface




來自於身體的生醫訊號會經過身體以及電極的阻抗，再被電路放大
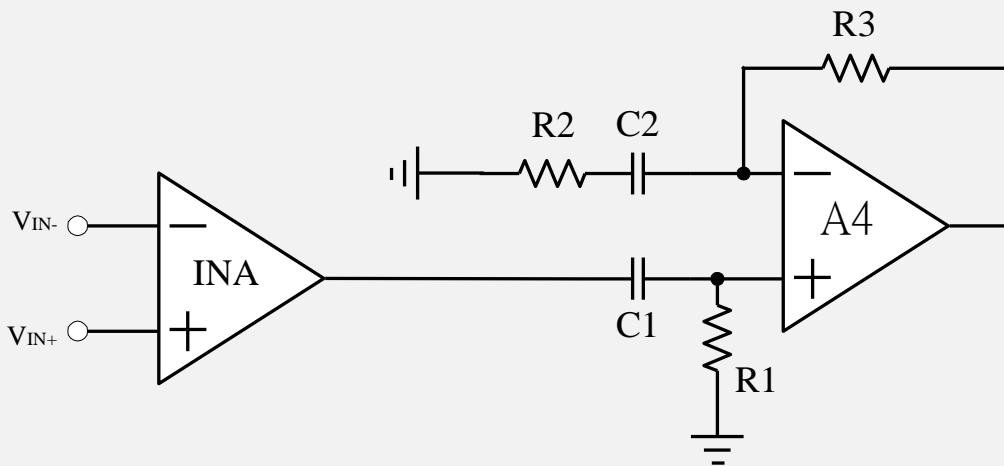
# ECG Measurement (Design Problem II to IV)


- 針對ECG量測，要慎選filter的-3dB frequency,才能濾掉interference signals




Instrumentation  
Amplifier

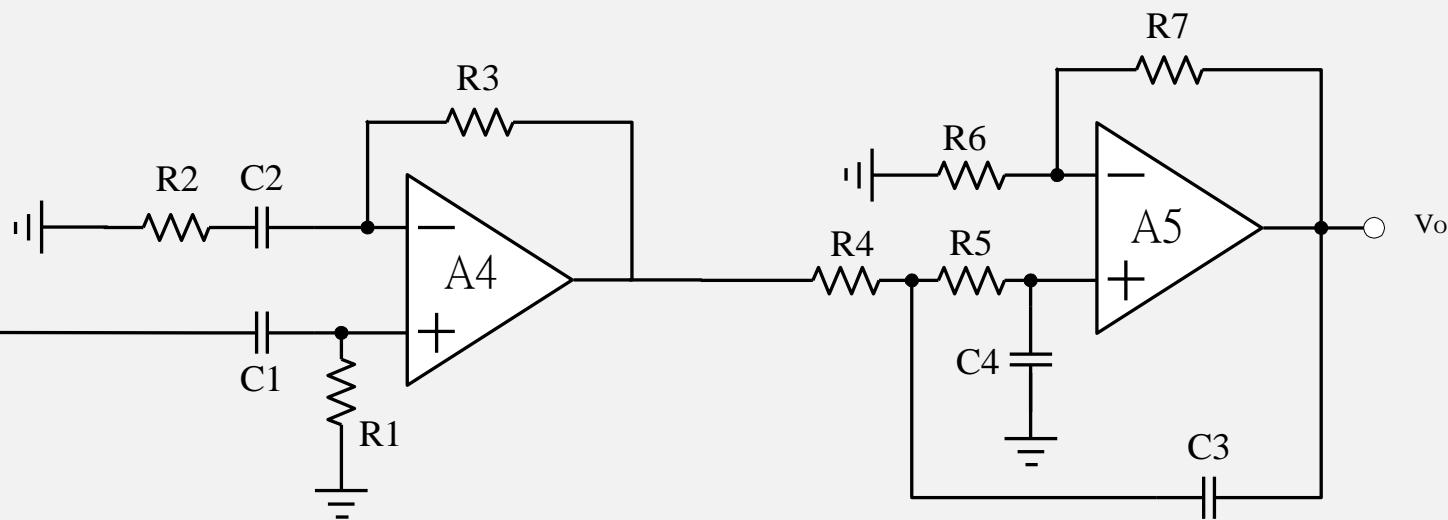

High-Pass Filter

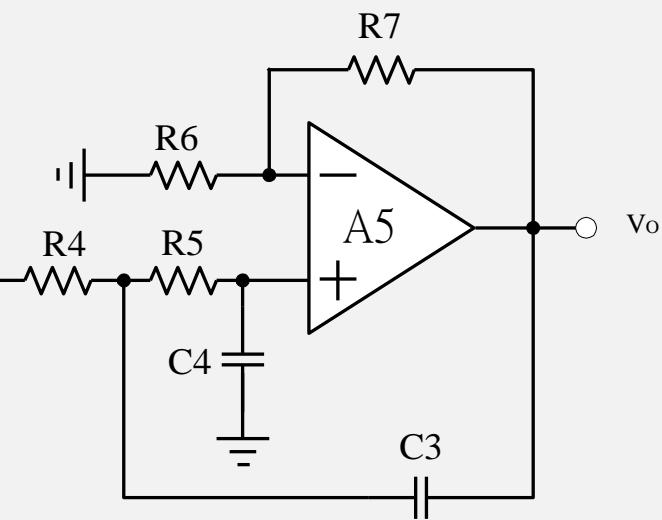


Low-Pass Filter

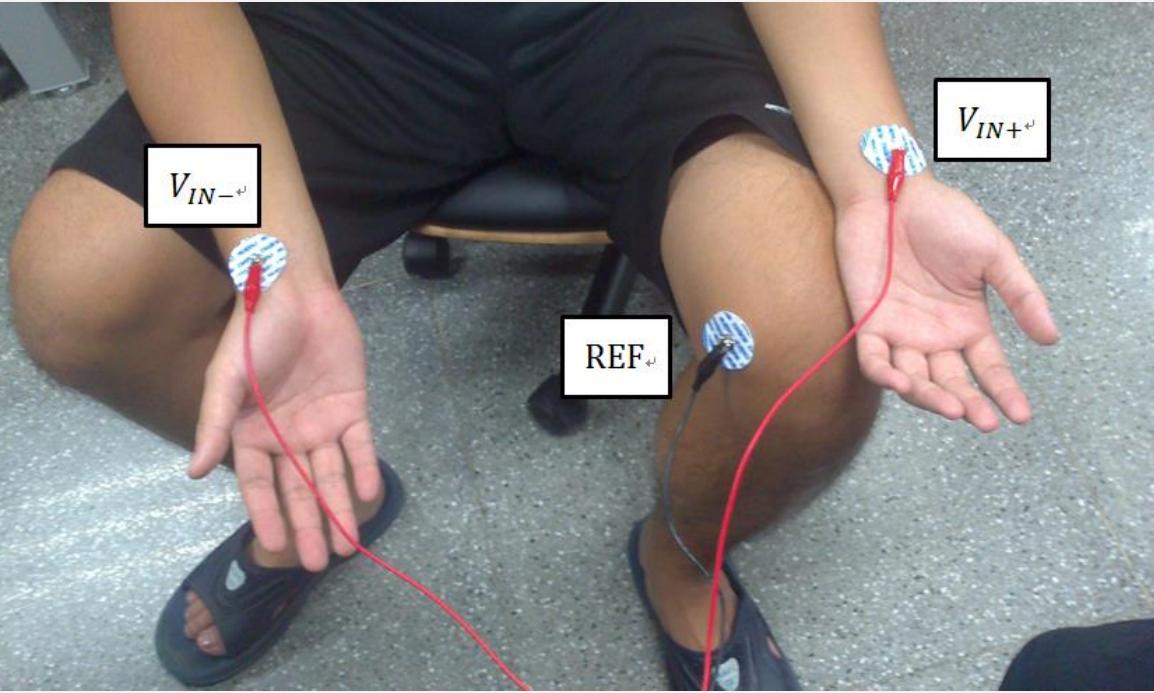
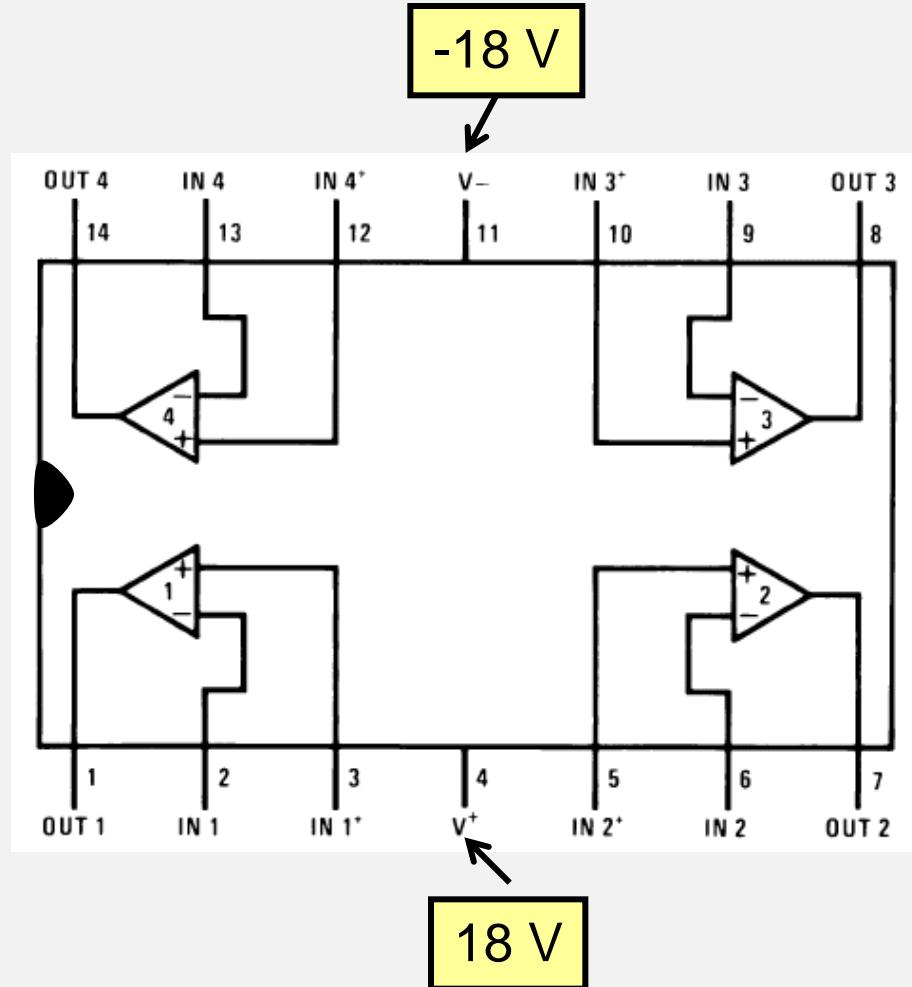
# The LM348 Chip for Design Problem I

- Contains FOUR op amps
- Power supply =  $\pm 18 \text{ V}$
- Caution: avoid touching the metal pins of the chip to reduce damage from electrostatic charges



# The TLC2264 Chip for Design Problems II to IV

Power supply =  $\pm 8$  V

Compared to LM348, TLC 2264 has lower noise and input offset, and higher input impedance, suitable for biomedical signal processing

