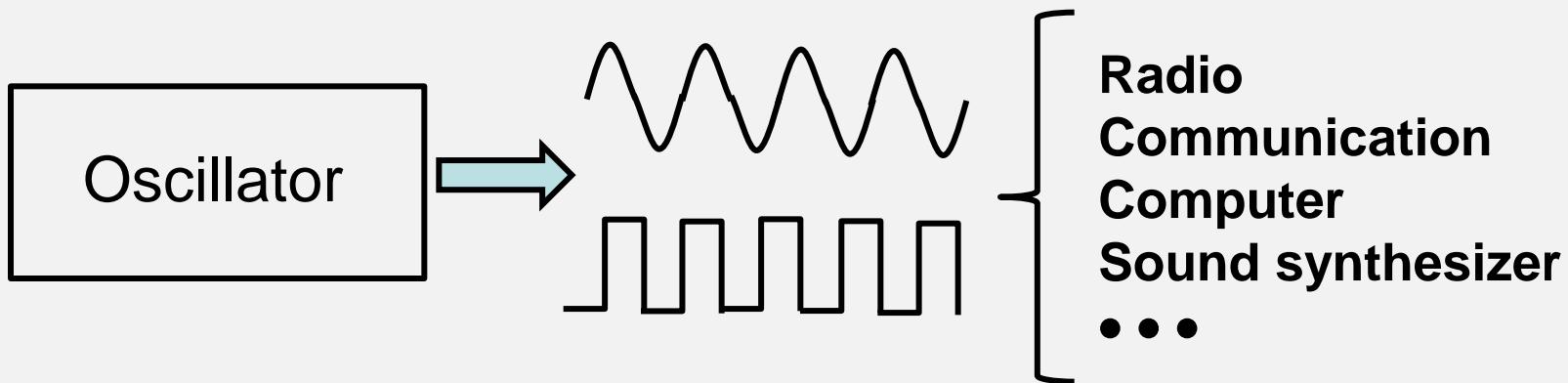

Lab 5: Electronic Oscillator

(振盪器電路)

張孟凡
清華大學電機系

Electronic Oscillator

- An electronic oscillator is a circuit that produces a periodic signal, often a sine wave or a square wave
 - Numerous applications: radio, communication, clock signals for computers, etc
 - 如何能讓振盪器電路插電後便能產生振盪波形?在本次實驗我們將會介紹三種常用的振盪器電路




Types of Oscillators

- Feedback oscillators
 - Operated based on feedback (迴授) ; we need to properly design the loop gain and phase to produce oscillation
 - » Examples: the Wien-bridge oscillator, the phase-shift oscillator, the twin-tee oscillator, etc
- Relaxation oscillators
 - » Also use feedback; usually use a mechanism to alternately charge and discharge a capacitor through a resistor in order to sustain oscillation
- Triangular, square-wave oscillator using Schmitt trigger
 - An integrator is used in the feedback loop


Type I: Feedback Oscillators

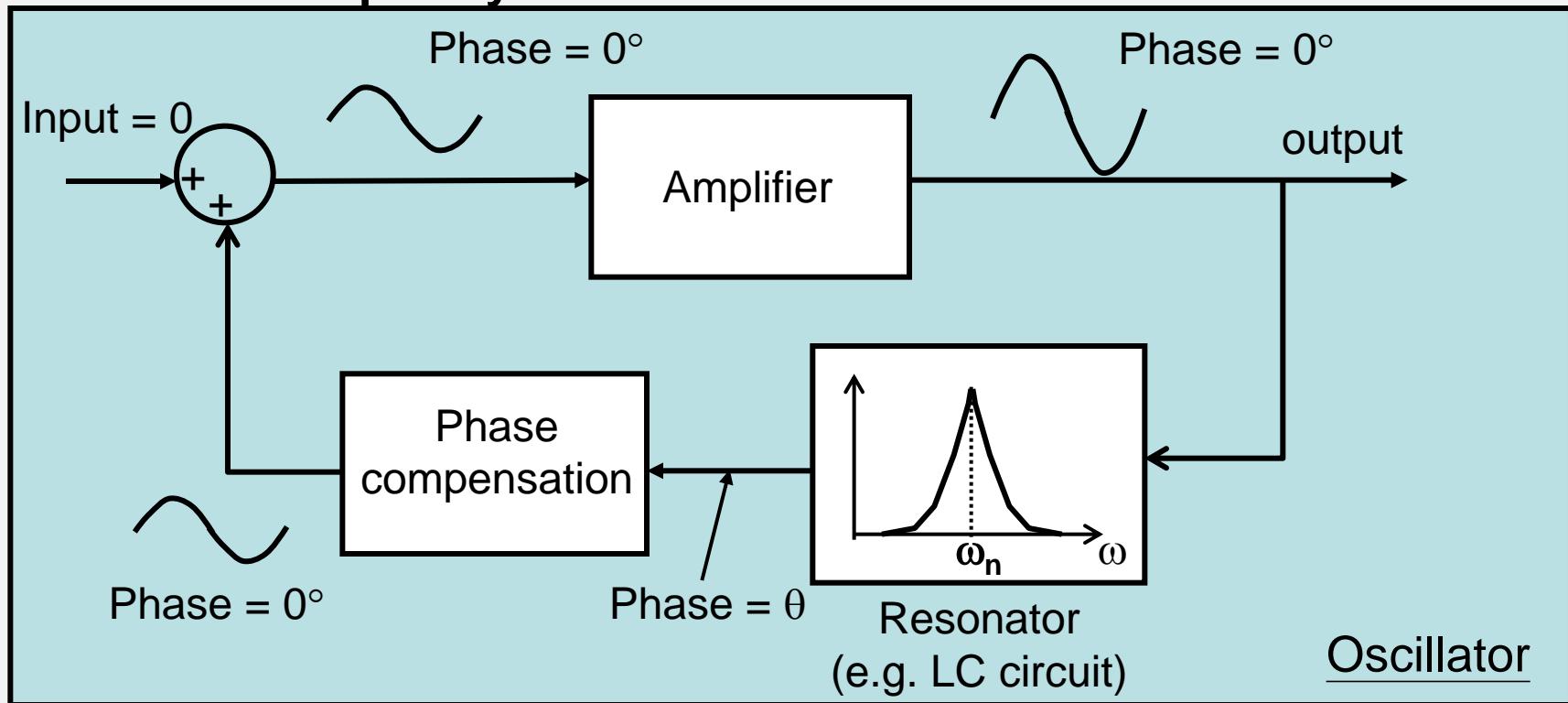- 經由“迴授”，當整個loop有適當的gain以及phase(滿足Barkhausen criterion)，在不需輸入訊號下，電路本身的噪聲(noise)得以被持續放大，形成週期性的振盪訊號
- Key: need a frequency selective device (i.e. resonator) to define the oscillation frequency




Cont'd

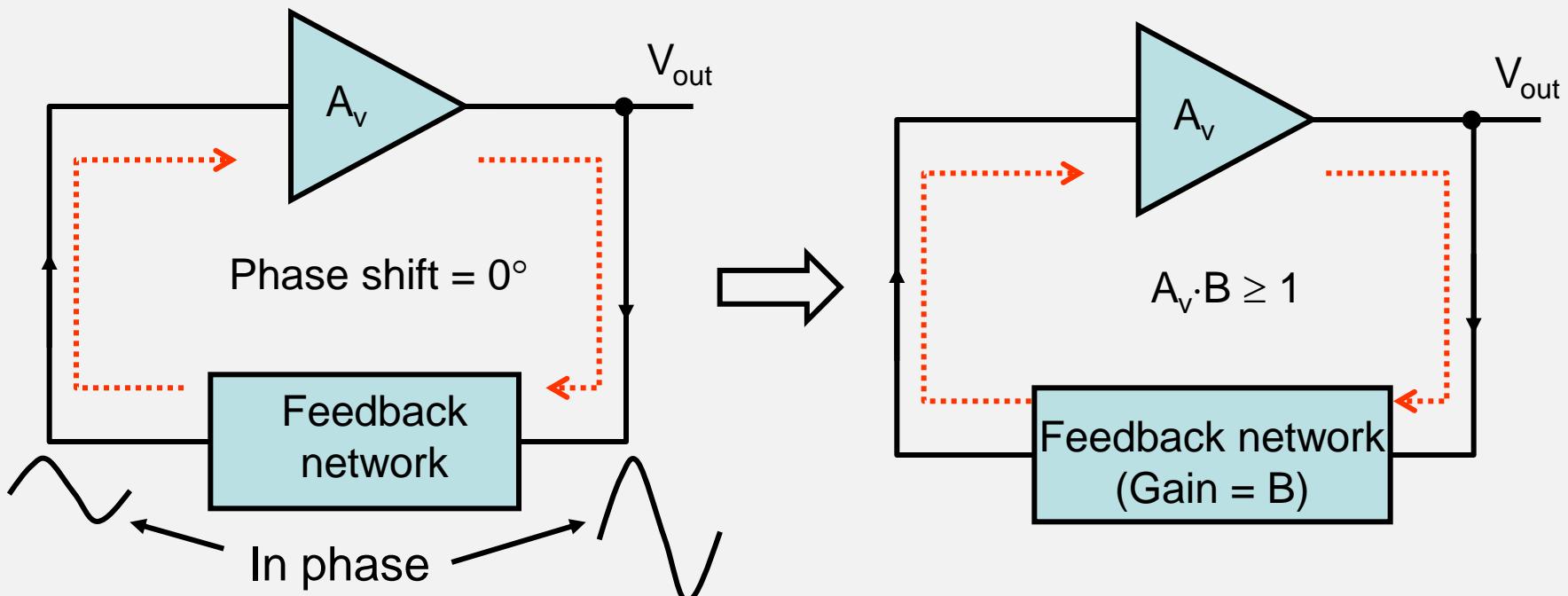
- Conditions (Barkhausen criterion) for producing oscillations (重要!) :
 - The phase shift around the feedback loop must be 0° (or 360°)
 - The loop gain (voltage gain) around the feedback loop must be at least 1



Start-Up Conditions (起振條件)

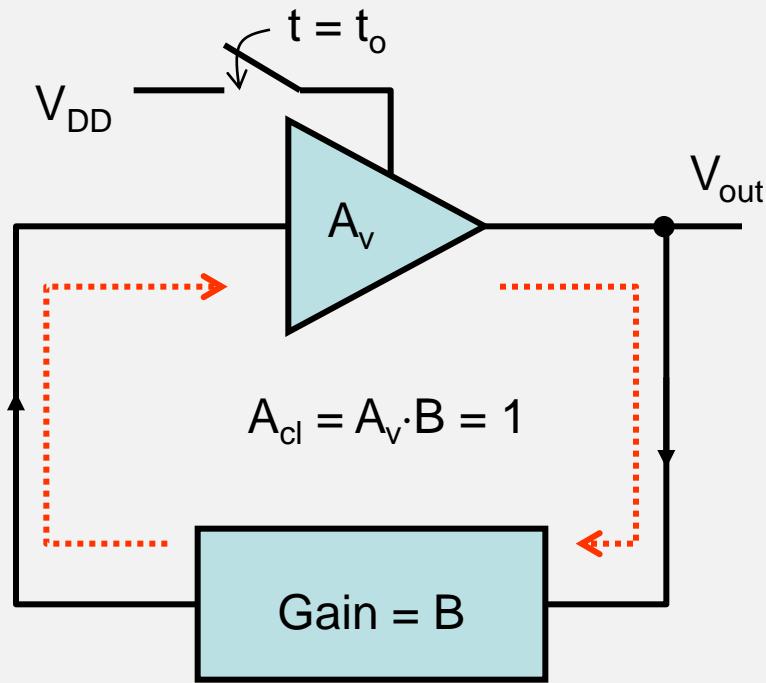


- Oscillation can be produced by electronics noise or initial transient during power-on
- Operation: initial gain can be greater than one to build up the waveform, then decreases to one to maintain the amplitude at the same level

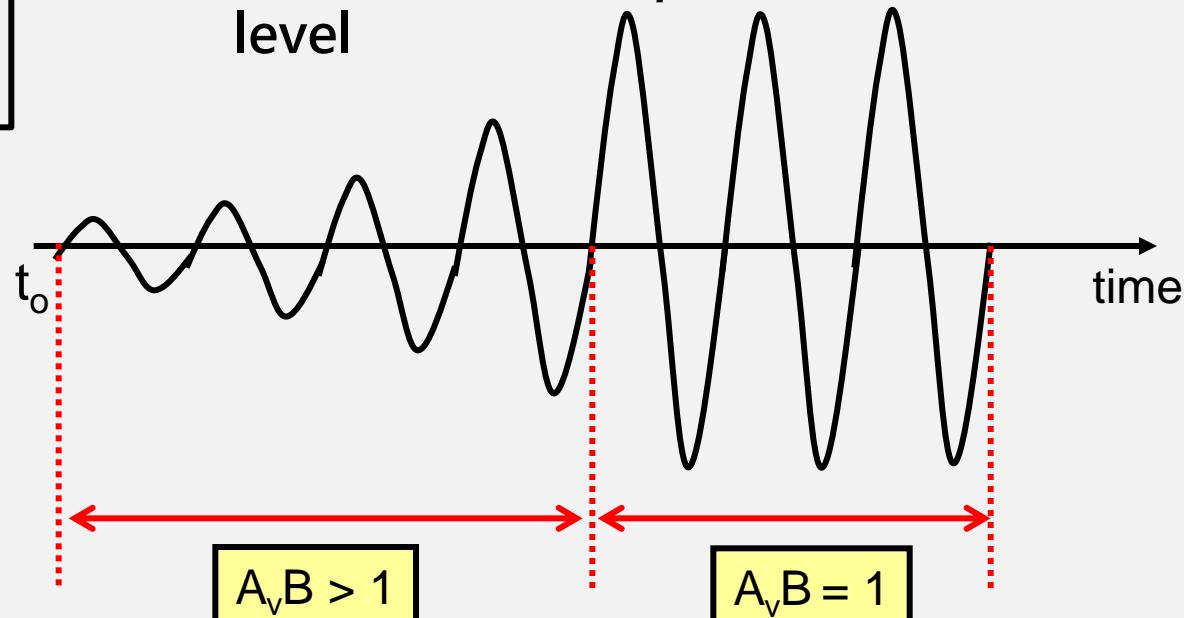

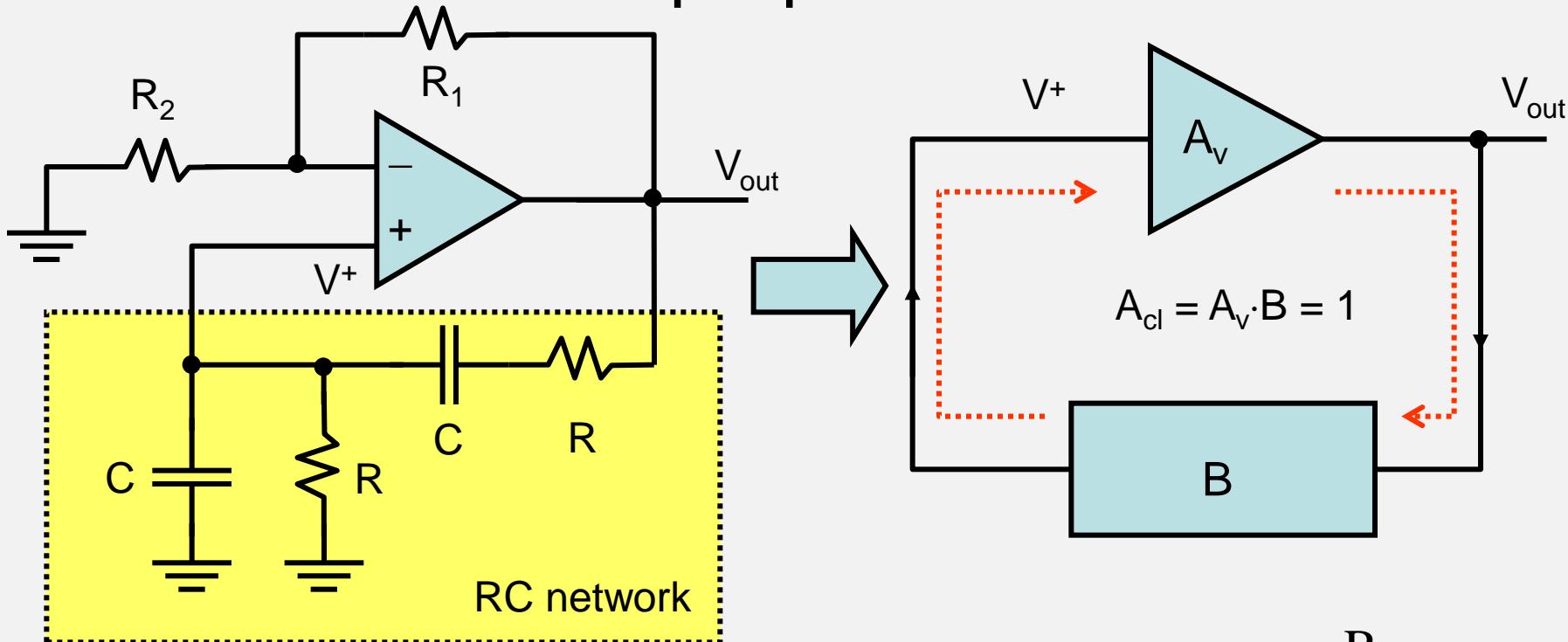Example I: The Wien-Bridge Oscillator


- 分析：電阻與電容要如何設計才能起振？另外，振盪頻率是多少？
- Need to satisfy Barkhausen criterion
- Virtual short exists for the op-amp



What are A_v and B ?


$$A_v = 1 + \frac{R_1}{R_2}$$

Cont'd:

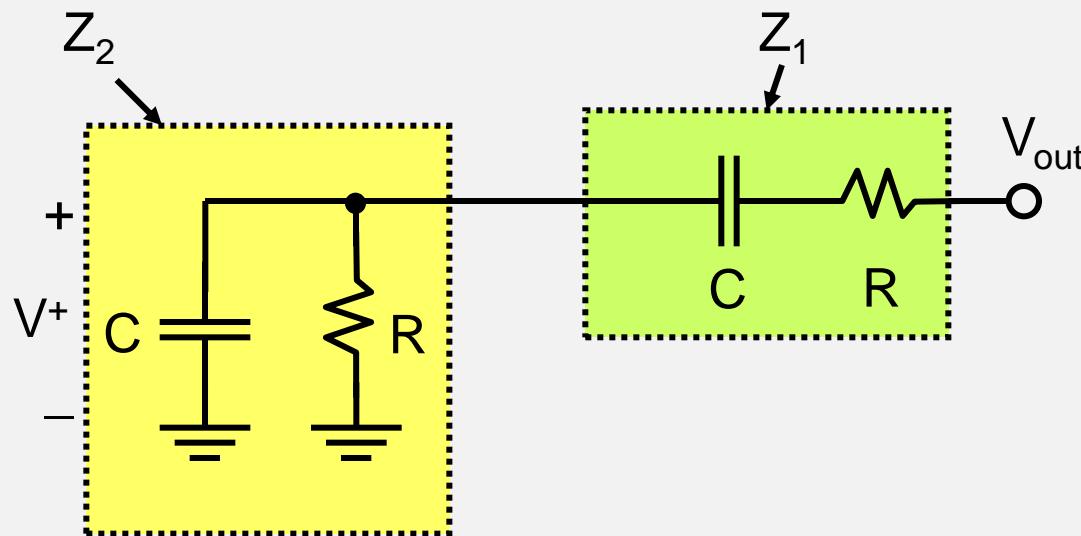

$$\begin{aligned}\frac{V^+(s)}{V_{out}(s)} &= \frac{Z_2}{Z_1 + Z_2} = \frac{R // \frac{1}{sC}}{\left(R + \frac{1}{sC}\right) + R // \frac{1}{sC}} \\ &= \frac{sRC}{R^2C^2s^2 + 3RCs + 1}\end{aligned}$$

Cont'd:

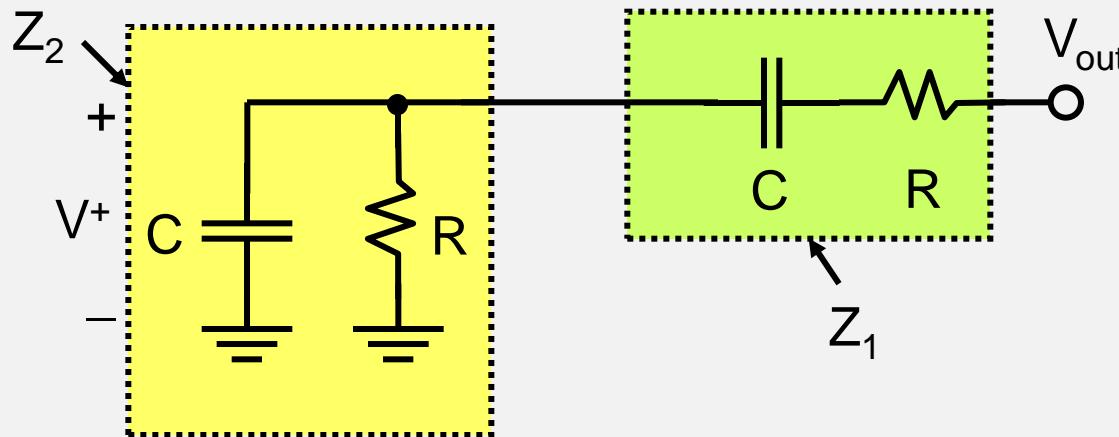

Replacing $s = j\omega$:

$$\frac{V^+(j\omega)}{V_{\text{out}}(j\omega)} = \frac{j\omega RC}{(1 - \omega^2 R^2 C^2) + j\omega 3RC}$$


For now (believe me), the phase shift between V^+ and V_{out} must be zero才能產生振盪 (因為Av是一個單純的gain，相角為零)，therefore:

$$1 - \omega^2 R^2 C^2 = 0 \Rightarrow \omega = \frac{1}{RC} \text{ rad/sec} \therefore \frac{V^+(j\omega)}{V_{\text{out}}(j\omega)} = \frac{j\omega \cdot RC}{j\omega \cdot 3RC} = \frac{1}{3}$$

↑
resonant frequency


Cont'd: 起振條件 -- Determine the Ratio of R_1/R_2

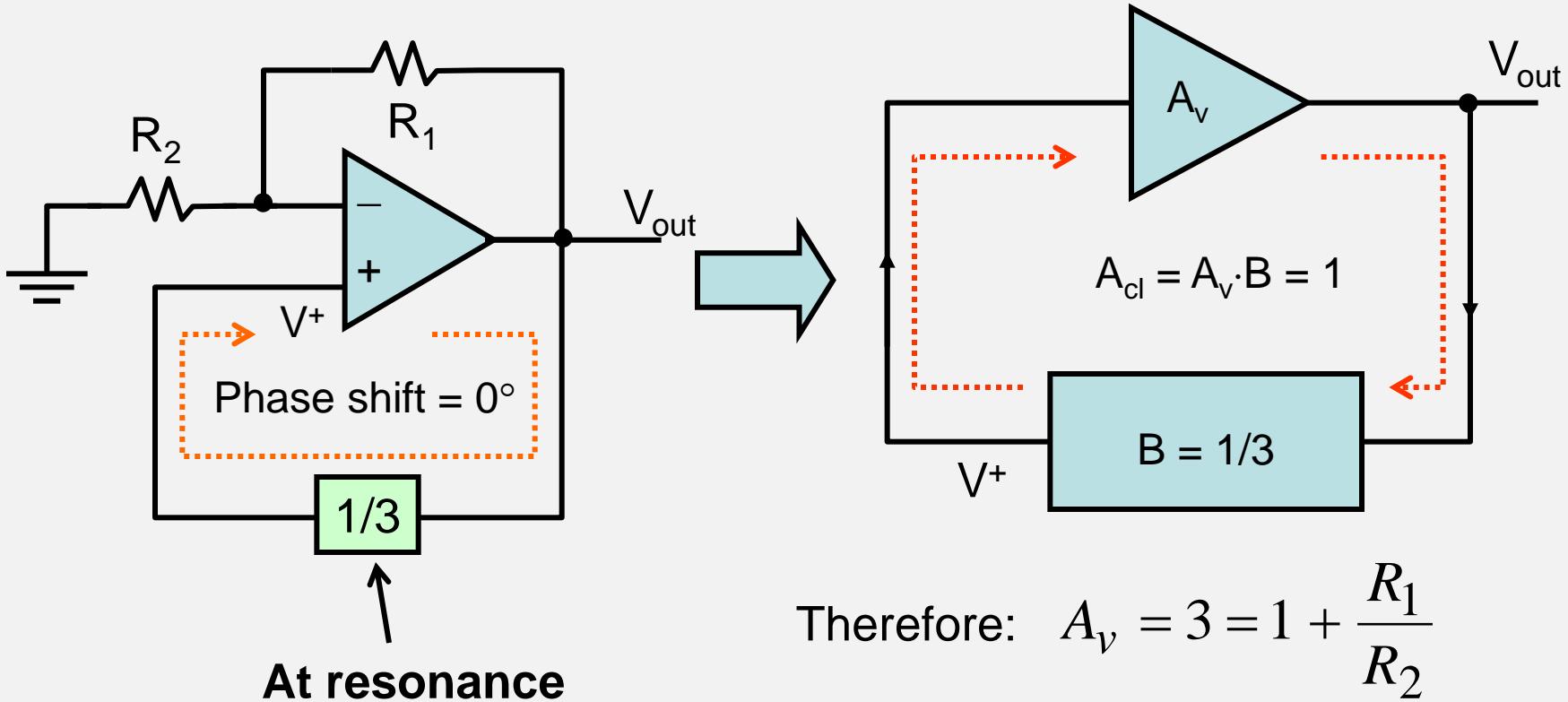- The resonant frequency in Hertz: $f_r = 1/(2\pi RC)$



Start-Up of Oscillations: Implementation


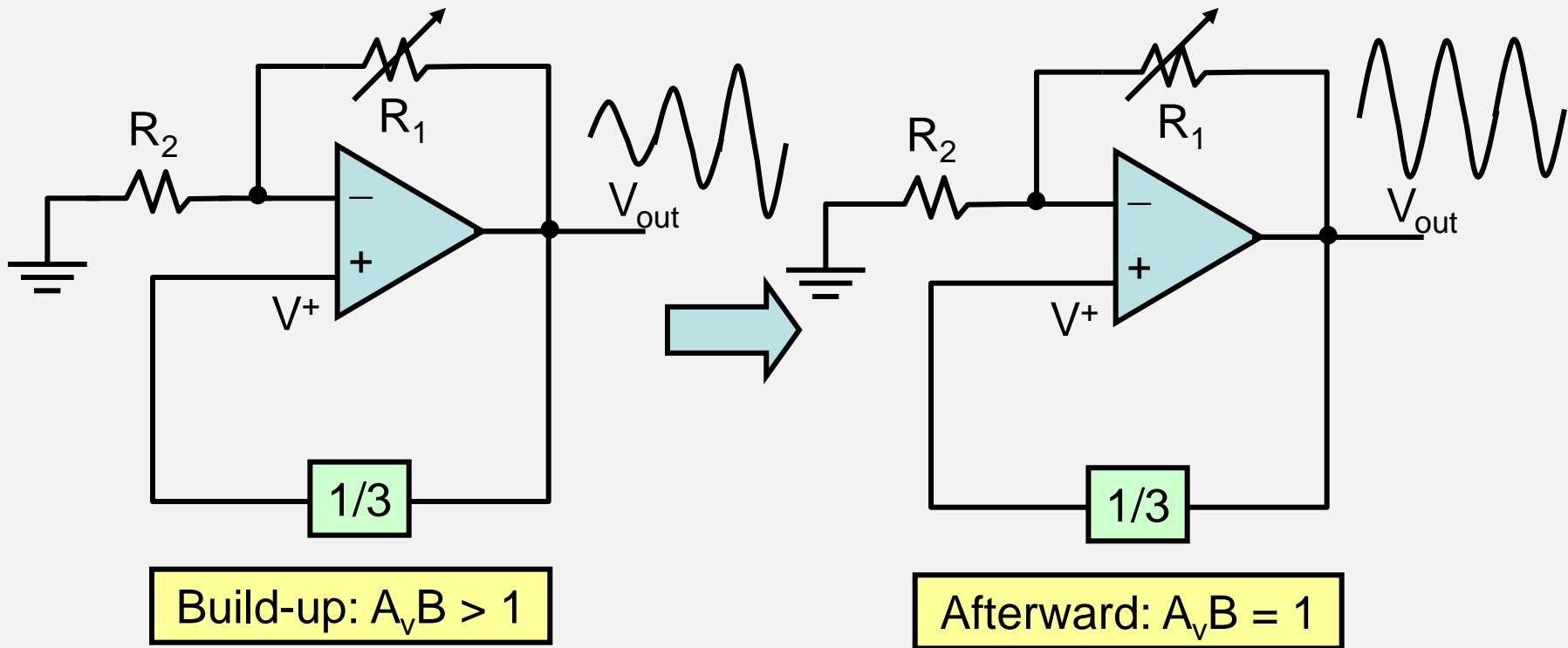
- It is desired to have a loop gain $A_v \cdot B > 1$ to start up the oscillation, then reduce the loop gain to one to sustain the oscillation
 - 如何製作一個可以調整增益的電阻？



Implementation of the Adjustable Gain Using Zener Diodes

■ 想想看：back-to-back connected zener diodes的作用


1. 當還沒起振時（back-to-back連接zener diodes電阻值較大）
2. 當已經產生較大的振盪訊號 V_{out} 之後（back-to-back連接zener diodes電阻值較小，短路）

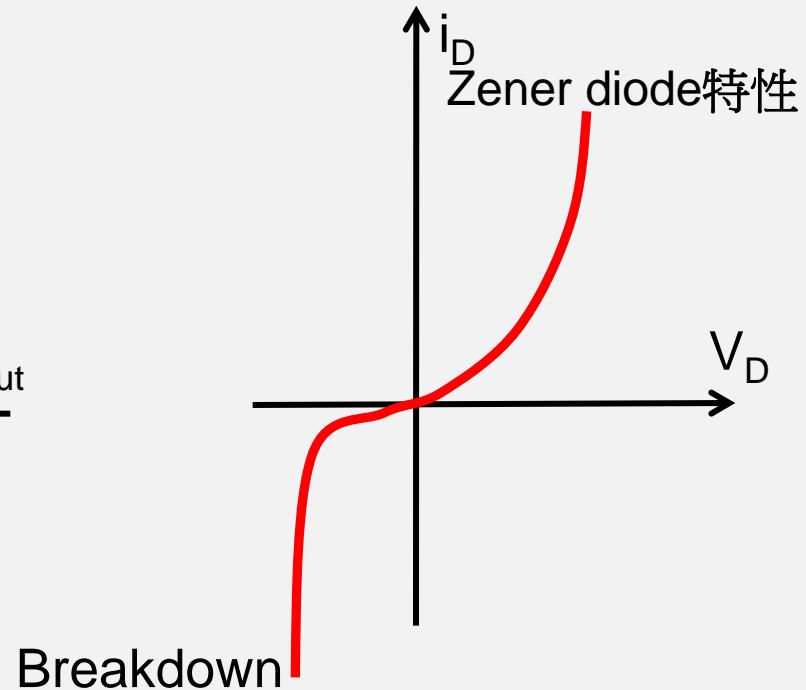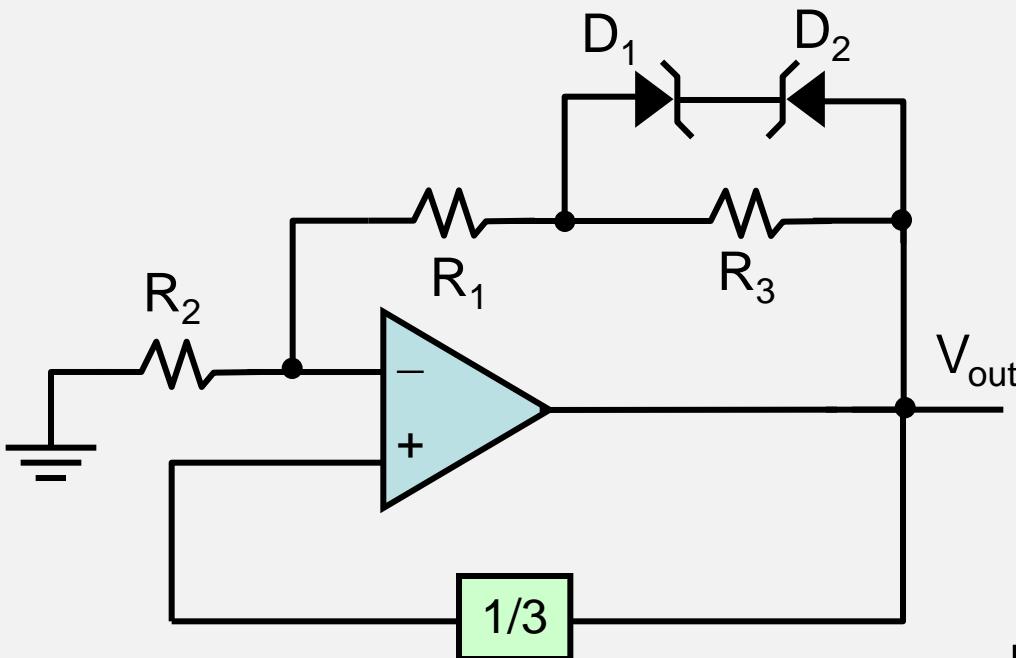

Type II: Relaxation Oscillator


■ Note : the op-amp here works like a comparator (比較器) , no virtual short exists between V^+ and V_C ; the output is a square wave

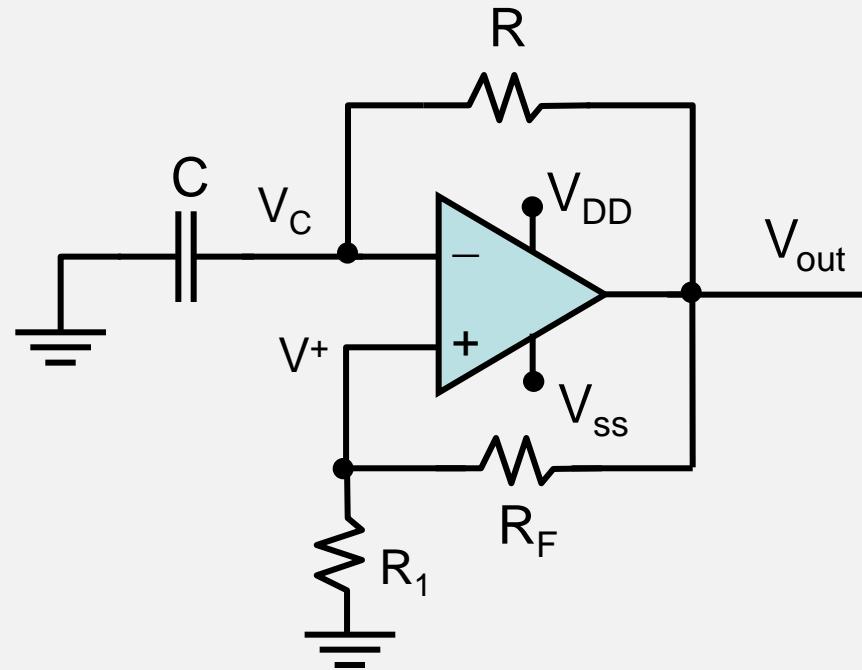1. When $V^+ > V_C$: V_{out} is close to V_{DD}
2. When $V^+ < V_C$: V_{out} is close to V_{ss}




Analysis

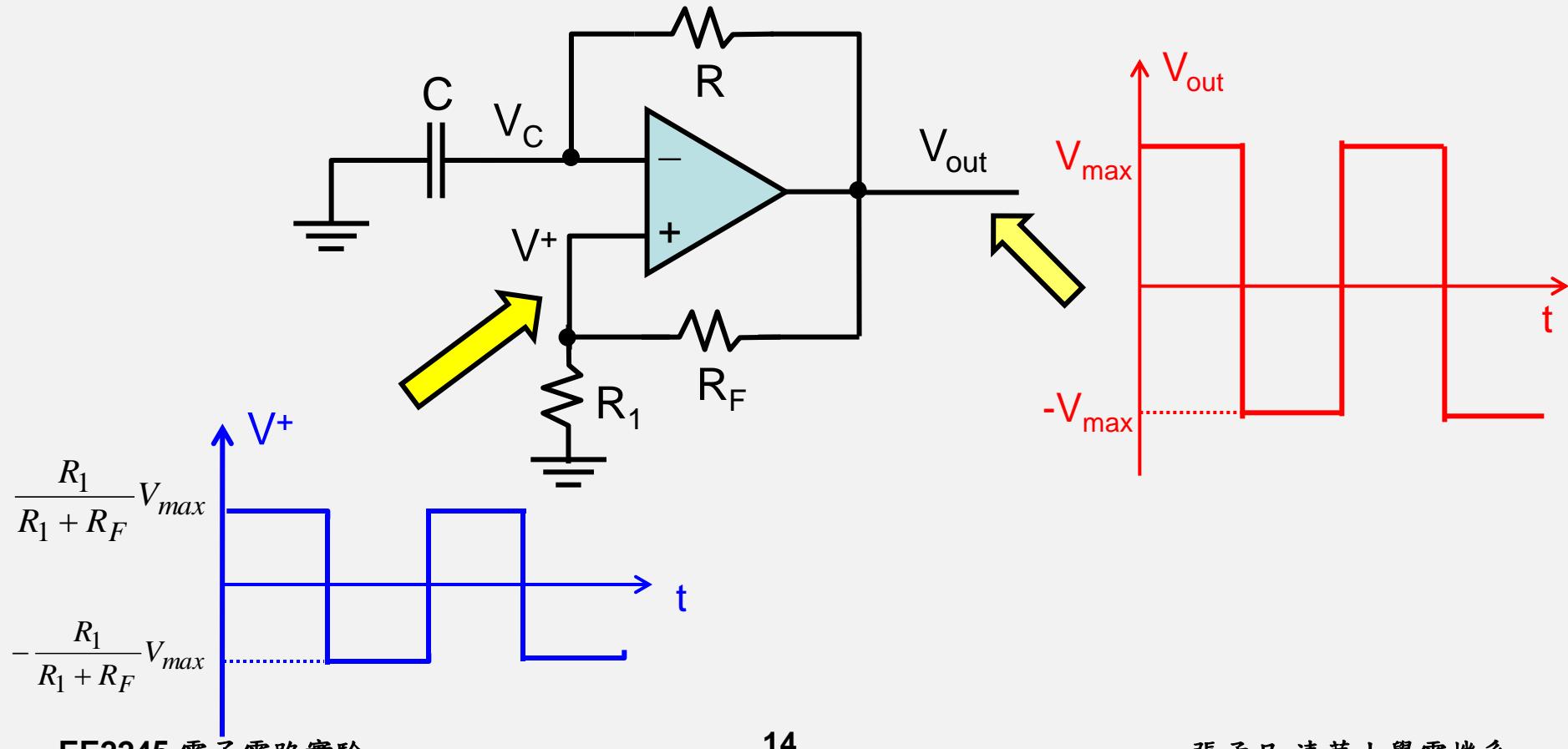- Waveform of V^+ : R_F and R_1 determine the value of V^+ , which sets the level to compare with V_C



Cont'd

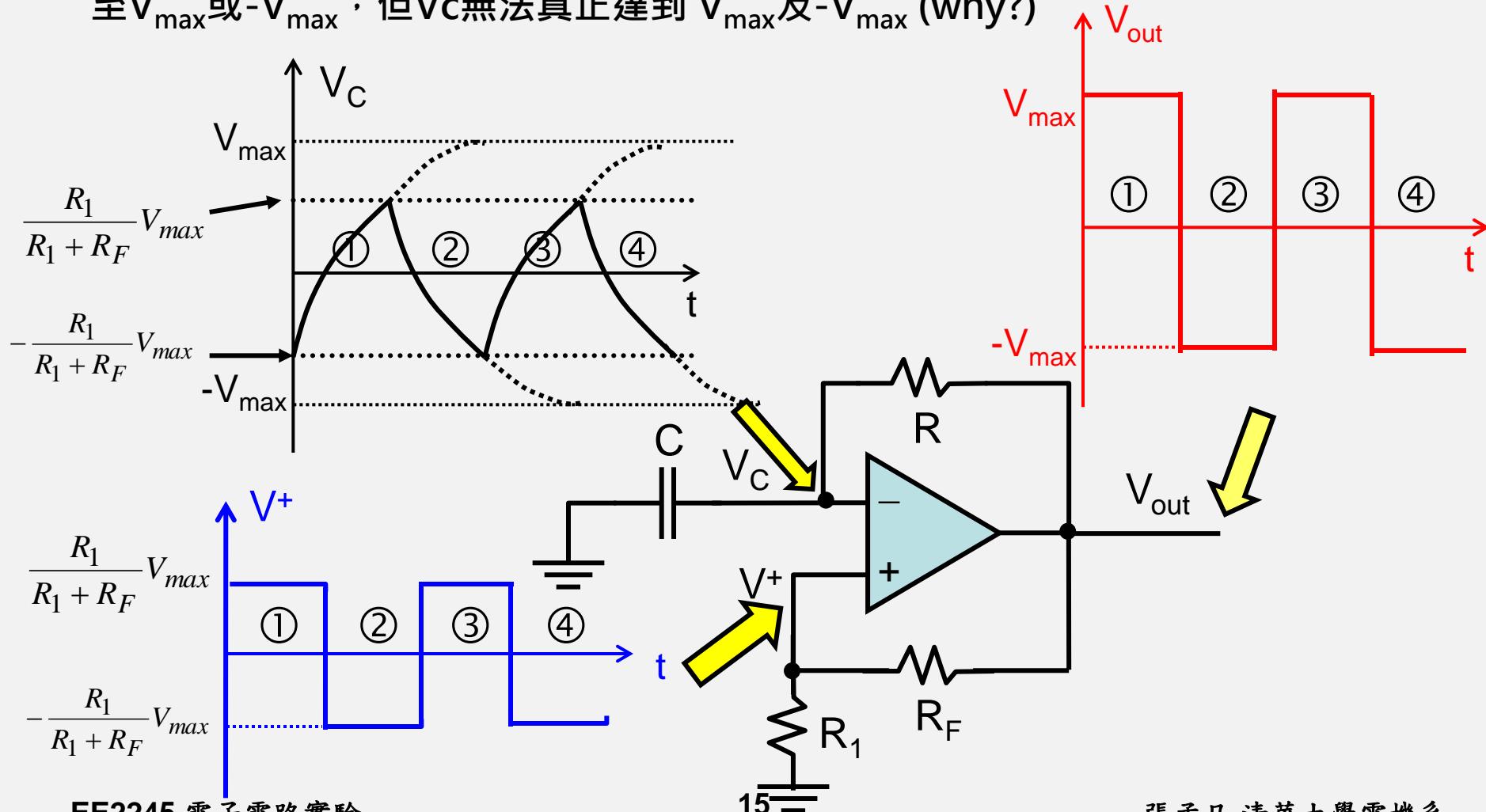
- 當 V_{out} 是 V_{max} 或 $-V_{max}$ 時，會沿著RC路徑(time constant $\tau = RC$)對C充電及放電至 V_{max} 或 $-V_{max}$ ，但 V_C 無法真正達到 V_{max} 及 $-V_{max}$ (why?)





Oscillation Frequency

- Please analyze the frequency based on the waveforms, and show the result to a TA before your implementation
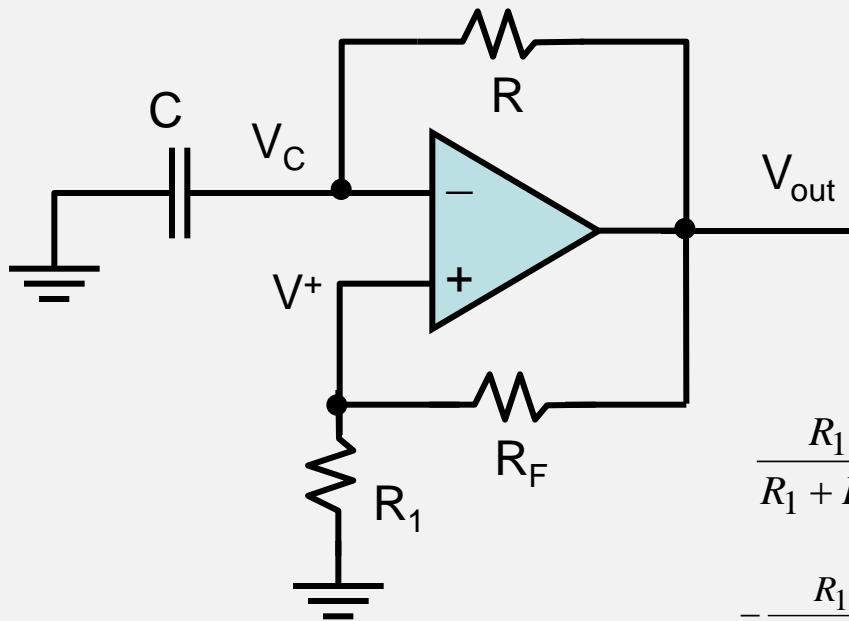
$$f_0 = \frac{1}{T} = \frac{1}{2RC \cdot \ln\left(1 + 2\frac{R_1}{R_F}\right)}$$



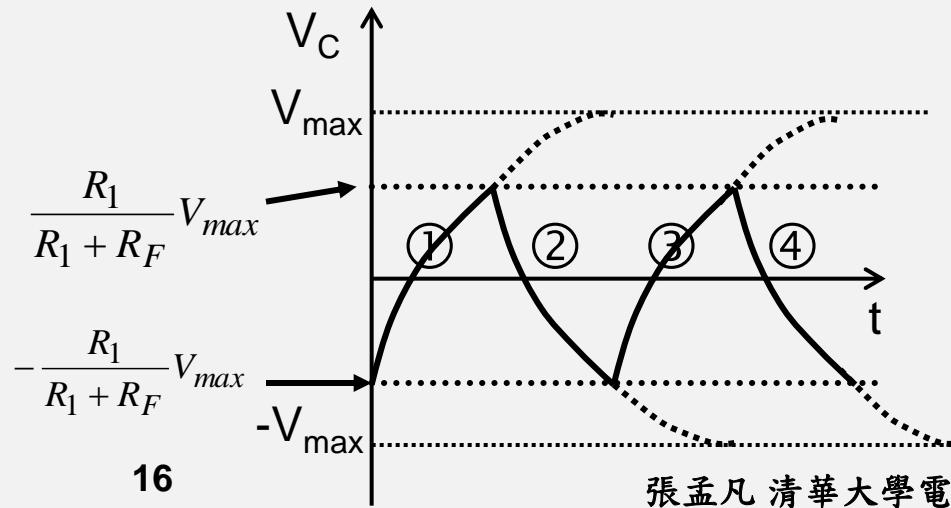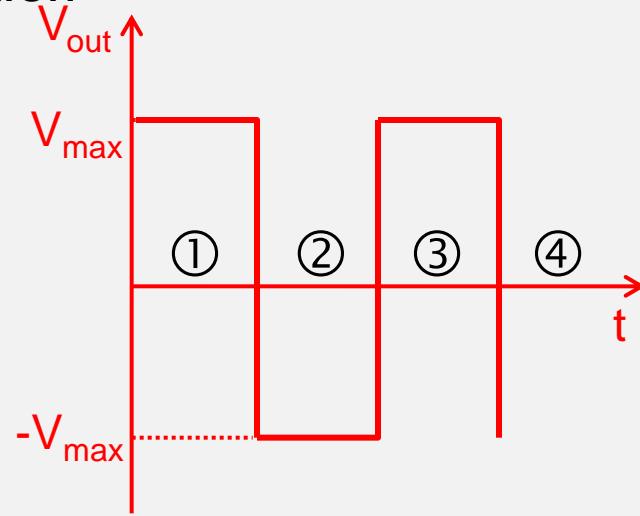
$$\frac{R_1}{R_1 + R_F} V_{max}$$
$$-\frac{R_1}{R_1 + R_F} V_{max}$$



Triangular, Square-Wave Oscillator

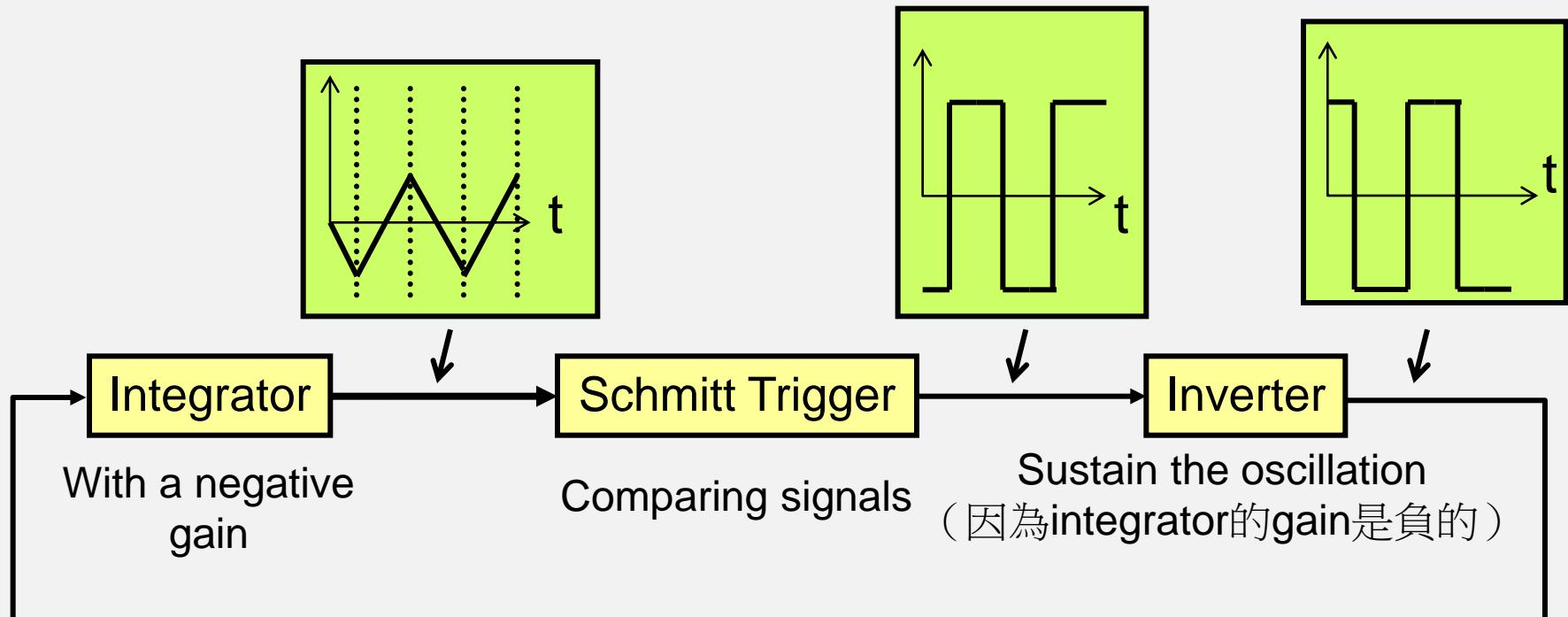- Can be used to make a function generator
- Three important parts:
 - Integrator : 將方波積分、使成為三角波
 - Schmitt trigger : 將三角波與參考電壓比較後，形成方波輸出
 - Inverter (將正訊號變負、負變正)。在整個電路的角色是維持振盪



Integrator with a Negative Gain


- The integrator is:

$$\frac{v_o(s)}{v_i(s)} = -\frac{1}{sRC}$$

Assume v_i is constant:

$$\begin{aligned} \Rightarrow v_o(t) &= \int_0^t -\frac{1}{RC} v_i dt \\ &= -\underbrace{\frac{1}{RC} v_i}_{\text{Slope}} \cdot t \end{aligned}$$

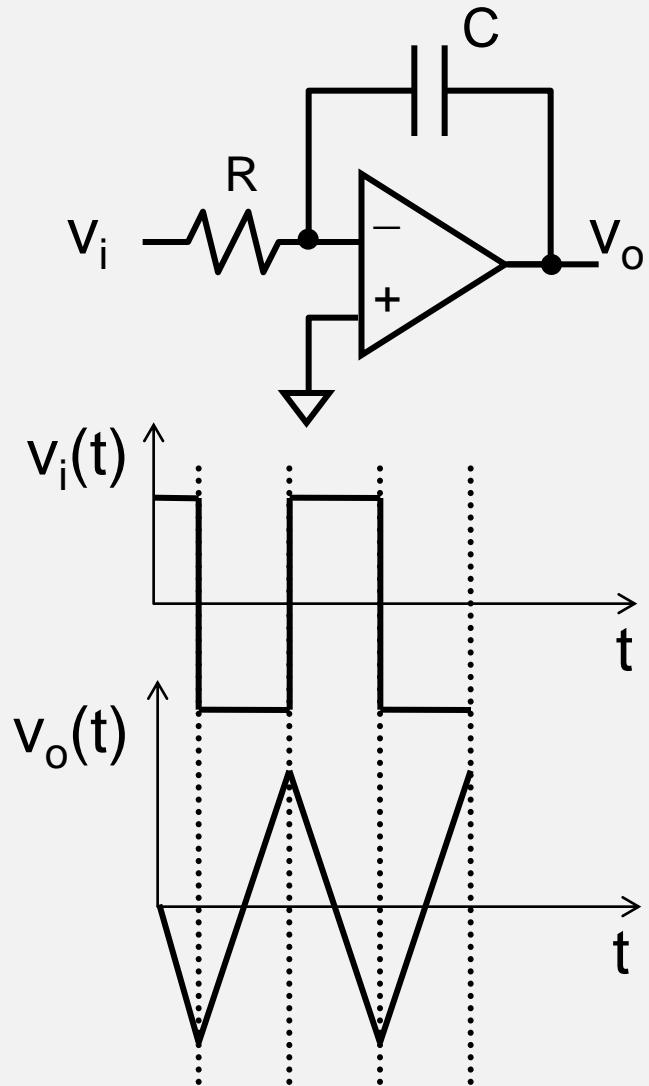
- Given a square waveform, an integrator produces a triangular waveform



Schmitt Trigger


- 注意: V_o 的訊號是拉回到op-amp的正端 (不會有virtual short) · 產生參考電壓 V^+ · 來與輸入訊號 V^- 比較
- V_o is either HIGH or LOW · with values close to V_s 或 $-V_s$
- Example: assume $R_1 = R_2$, $V_s = 10$ V.
Then
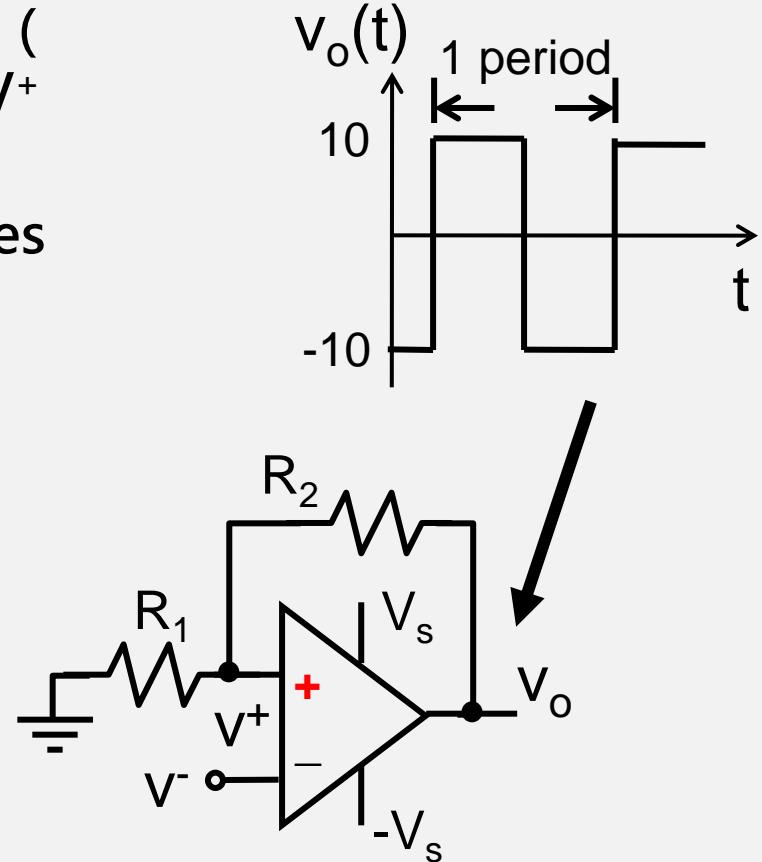
$$v_o \cong \pm 10 \text{ V}, v^+ = \frac{R_1}{R_1 + R_2} v_o = \pm 5 \text{ V}$$




Cont'd

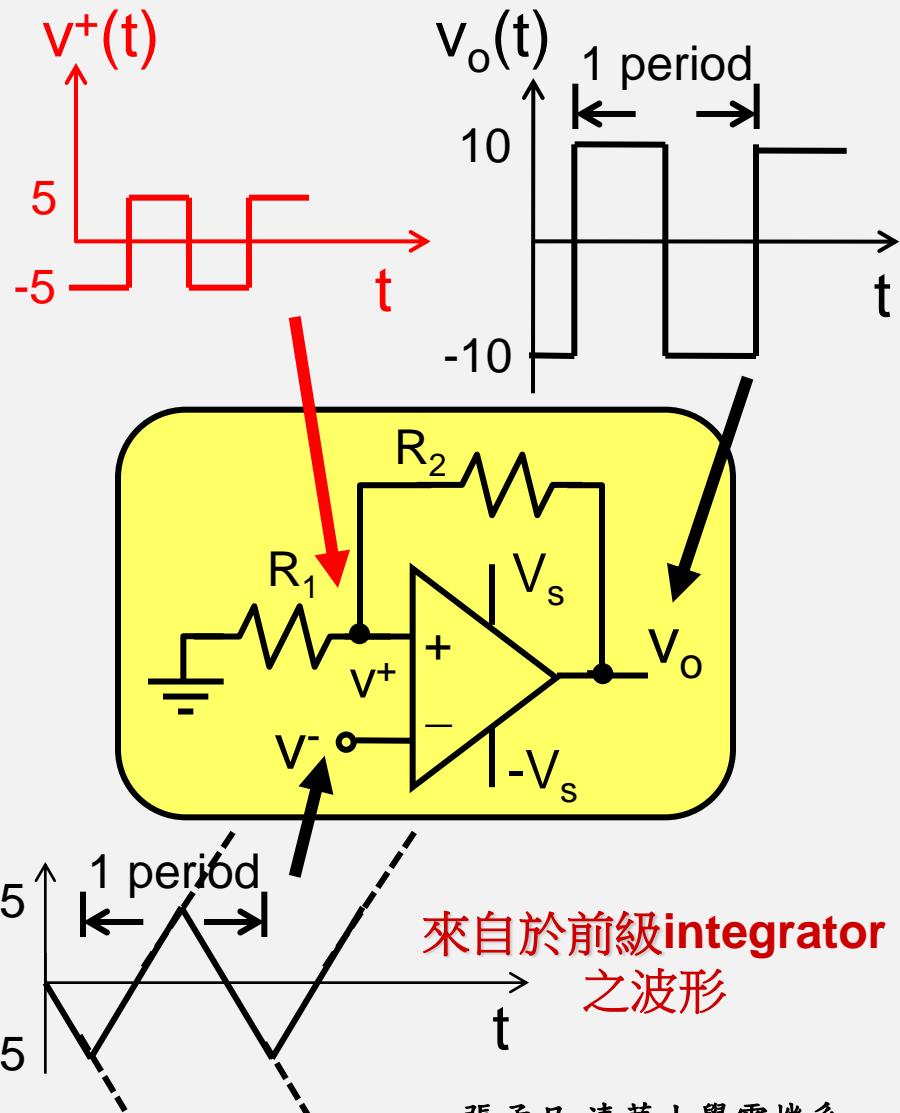- 輸入端 (v^-) 的輸入是 triangular wave，來自於前一級的integrator
- 積分器原本持續積分（如虛線所示），經與 v^+ 比較後，會使 v_o 變號（例如由 LOW 變 HIGH）； v_o 的訊號再經 inverter 變號後（下一張），會使得積分器往相反方向積分
- Schmitt trigger 的輸出及 v^+ 的波形皆是方波 (Here $R_1 = R_2$)
- 設計重點：方波的週期與 v^- 的斜率、 R_1/R_2 ratio 皆有關




Inverter

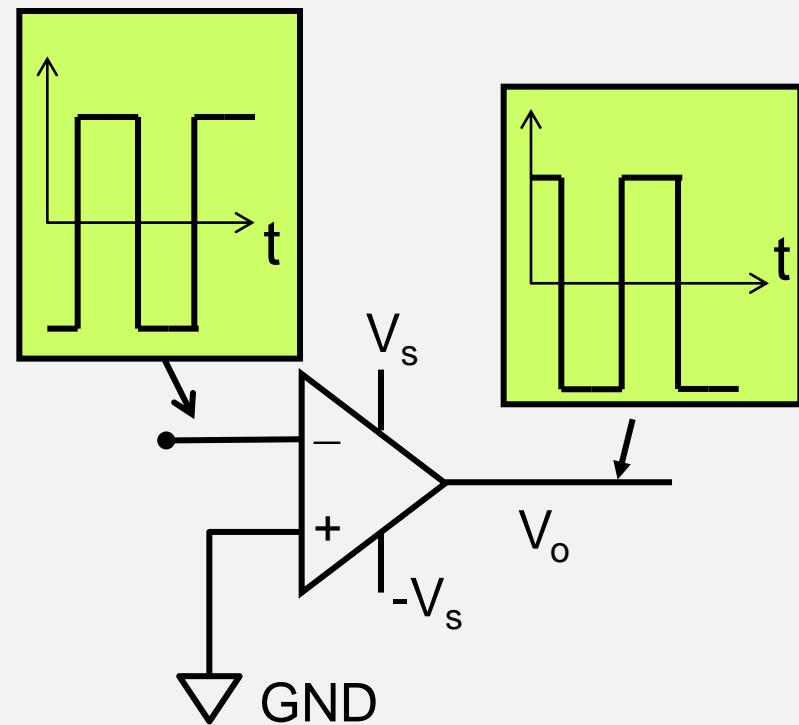- Here, the op-amp is used as a comparator to compare input waveform with 0 V (GND)
- Oscillation can not be sustained without the inverter



Complete Schematic

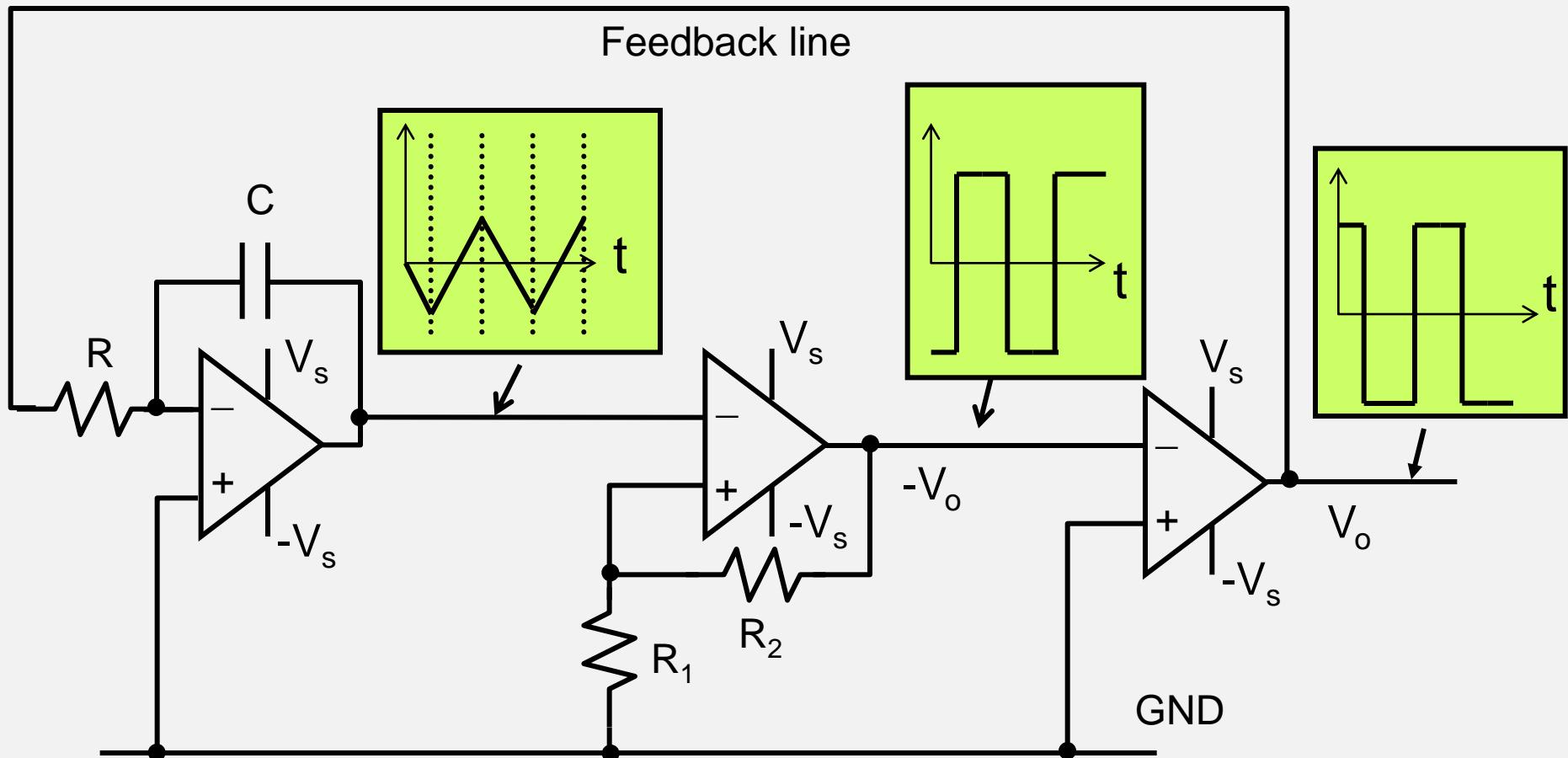

The LM348 Chip

- You will use it to implement oscillators
- FOUR op amps are included in one chip
- Power supply = $\pm 18 \text{ V}$
- Caution: Try not to touch the metal pins of the chip in order to avoid damage due to electrostatic charges

