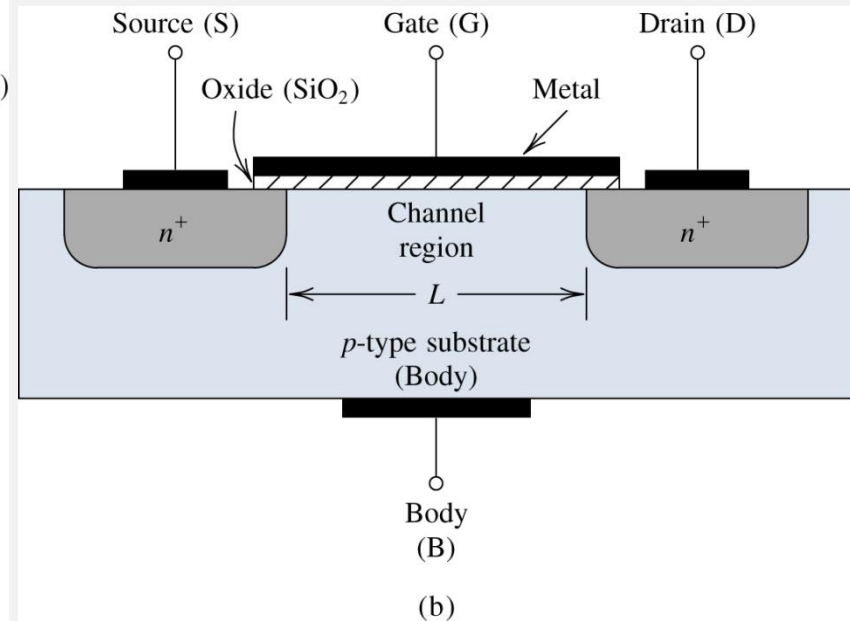
 
 

Lab 6: Parameter Extraction in SPICE MOSFET Model

張孟凡

清華大學電機系


Metal-Oxide-Semiconductor Field-Effect Transistors (MOSFETs)

A voltage-controlled current source




Example: Operation of a N-type MOS Transistor


- 步驟一：增加gate電壓，吸引drain及source端電子累積在矽基板表面

 

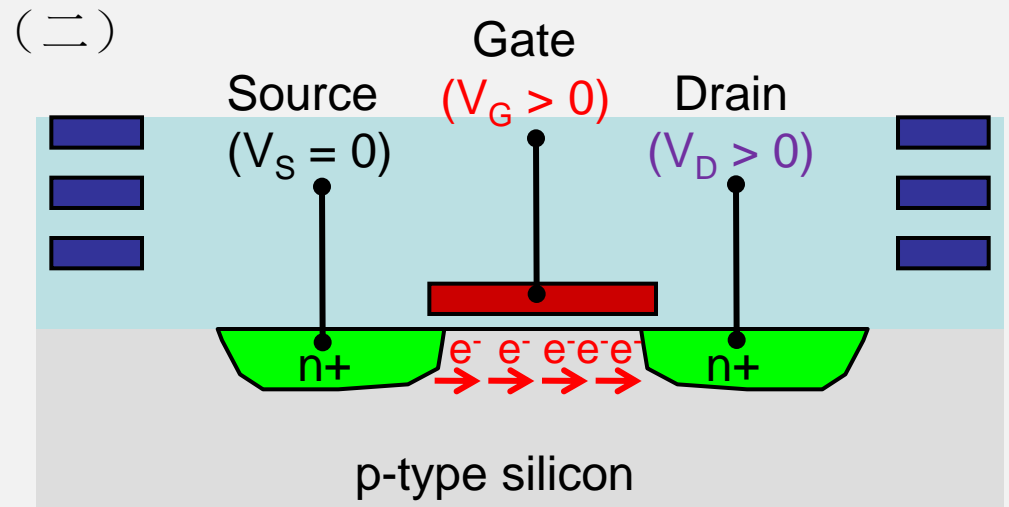- 步驟二：增加drain電壓，將所累積之電子吸引過去，便形成電流（由drain流到source）




Cont'd: Threshold Voltage

 

- $V_{GS} > V_t$ (V_t : threshold voltage) , 則在silicon表面形成n channel (可稱之為channel inversion)
- $V_{GS} < V_t$, 則電晶體可能不導通、或導通微量的sub-threshold current

 $V_{GS} > V_t$: Triode and Active (Saturation) Regions




- Given that $V_{GS} > V_t$:
 1. $V_{DS} < V_{GS} - V_t$ (即 $V_{GD} > V_t$) : the transistor operates in the triode region
 2. $V_{DS} = V_{GS} - V_t$ ($V_{GD} = V_t$, 此為 n channel 在 drain 端成立的最小 V_{GD} 值): the channel becomes pinched off
 3. $V_{DS} > V_{GS} - V_t$ ($V_{GD} < V_t$) : the transistor operates in the active (or saturation) region

MOSFET I-V Relationship


In saturation region:

$$i_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (v_{GS} - V_t)^2$$
$$= \frac{1}{2} k_n \frac{W}{L} (v_{GS} - V_t)^2$$

 μ_n : mobility ($\text{m}^2/(\text{V}\cdot\text{sec})$)
 C_{ox} : gate capacitance per unit area (F/m^2)
 V_t : threshold voltage




Threshold Voltage Measurement

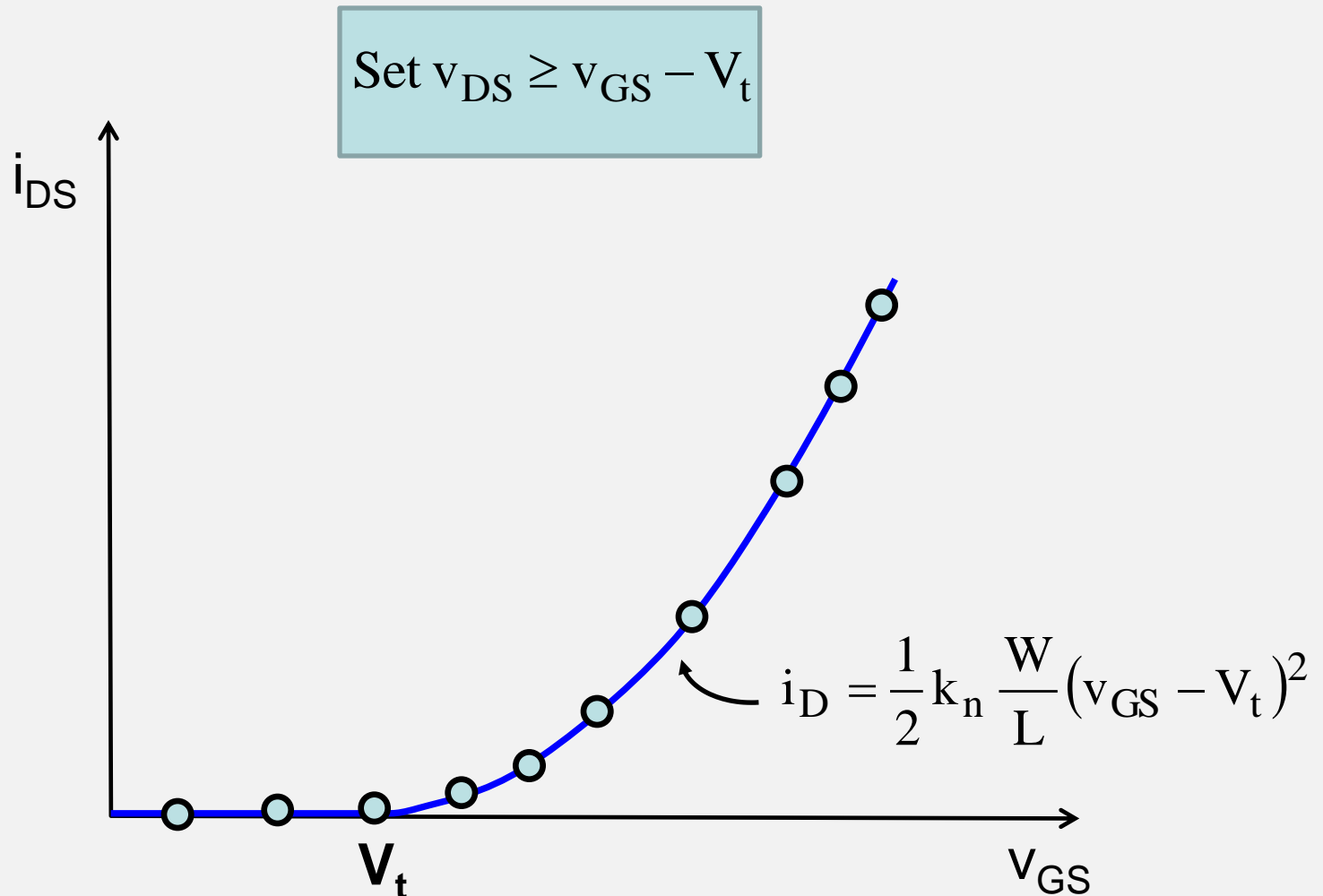

Large-Signal vs. Small-Signal Models

 - Under a fixed DC bias → By linearization to get the small-signal model




- Definition of g_m (transconductance)

$$g_m = \frac{\partial I_D}{\partial V_{gs}} = \mu_n \cdot C_{ox} \cdot \frac{W}{L} (V_{gs} - V_t)$$

$$\text{or } g_m = \frac{2I_D}{V_{gs} - V_t}$$

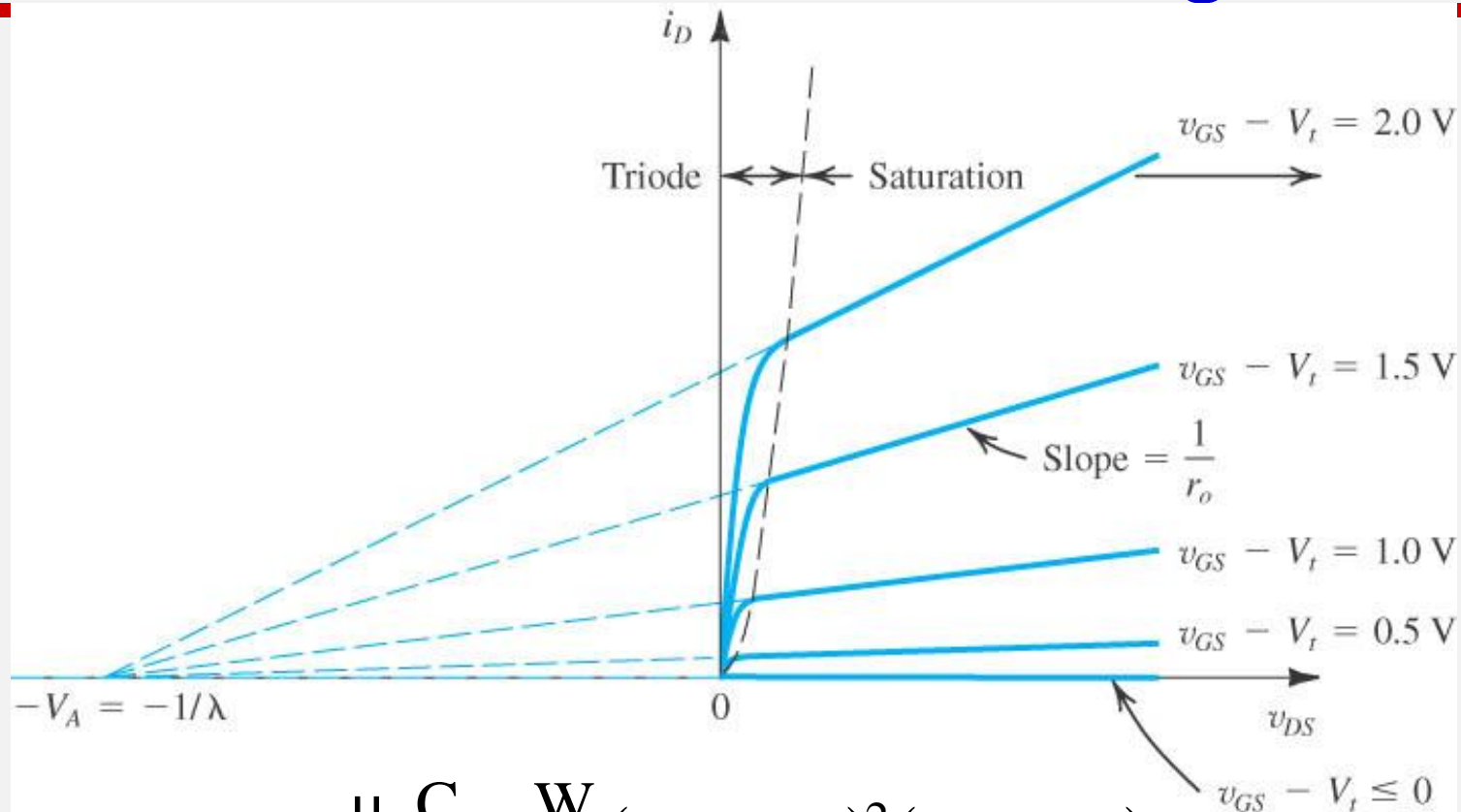Non-Ideal Effect: Finite Output Resistance in Saturation Region






$$i_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

$$\frac{1}{r_o} = \frac{\partial I_D}{\partial V_{DS}} = \lambda I_D = \frac{I_D}{V_A}, \quad I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot (V_{GS} - V_t)^2$$

Important for the Lab: Use Two Power Supplies for PMOS I-V Measurement

   - For example: $V_{sd} = 2.5\text{ V}$, $V_{sg} = 2\text{ V}$: use the connection as shown on the right-hand side



MOSFET Level 1 SPICE Model Parameters

Note: threshold voltage is positive for a NMOS, negative for a PMOS

Parameter	Name	Default value
Vto	Zero-bias threshold voltage	1.0 V
KP	Transconductance parameter	$2 \times 10^{-5} \text{ A/V}^2$
LAMBDA	Channel-length modulation	0.0 V^{-1}
TOX	Thin oxide thickness	$1 \times 10^{-7} \text{ m}$
GAMMA	Body-effect parameter	$0.0 \text{ V}^{0.5}$
PB	Bulk junction potential	0.80 V
CBD	Zero-bias body-drain capacitance	0.0 F/m^2
CBS	Zero-bias body-source capacitance	0.0 F/m^2
CGBO	Gate-body overlap capacitance	0.0 F/m
CGDO	Drain-body overlap capacitance	0.0 F/m

A More Complete MOSFET Model for Advanced Technology

- BSIM (Berkeley Short-channel IGFET Model) CMOS model (the major MOS model used in industry)
 - semi-empirical model



- BSIM model ~ 250 parameters

BSIM4_Model

BSIM4M1

NMOS=yes	Igbmod=	Xf=	Vbx=	Dvt0=	U0=	Rdswmin=	Pdits=	Pbswgs=	Mjswgd=	Voffcv=	Llc=	Wln=	Cle=	Cige=	Pigcd=	Rbpd=
PMOS=no	Paramchk=	Vsat=	Vbm=	Dvt1=	Eu=	Rsw=	Pditsf=	Mjswgs=	Cjd=	Dmcg=	Lln=	Ww=	Cle=	Aigsd=	Poxedge=	Noia=
Capmod=	Binunit=	At=	Xt=	Dvt2=	Ute=	Rdw=	Pditsd=	Cjs=	Cjswd=	Dmci=	Lw=	Wwc=	Dwc=	Bigsd=	Ijthd fwd=	Noib=
Diomod=	Version=	A0=	K1=	Dvt0w=	Voff=	Rdswmin=	Pscbe1=	Cjsws=	Cjswgd=	Dmdg=	Lwc=	Wwn=	Dlc=	Cigsd=	Ijths fwd=	Noic=
Rdsmod=	Toxe=	Ags=	Kt1=	Dvt1w=	Minv=	Rswmin=	Pscbe2=	Cjswgs=	Vfbcv=	Dmctg=	Lwn=	Wwf=	Dlcig=	Aigbacc=	Ijthdrev=	Tnoia=
Tmqsmod=	Toxp=	A1=	Kt1f=	Dvt2w=	Vofff=	Prwg=	Pvag=	Jsd=	Vfb=	Xgw=	Lwl=	Wwc=	Dwj=	Bigbacc=	Ijthsrev=	Tnoib=
Acnqsmod=	Toxm=	A2=	Kt2=	Drout=	Tnom=	Prwb=	Jss=	Jswd=	Tpb=	Xgl=	Lwc=	Wmin=	Alpha0=	Cigbacc=	Xjv d=	Ntnoi=
Mobmod=	Toxref=	Keta=	K2=	Dsub=	Trise=	Prt=	Jsws=	Jswgd=	Tcj=	Rshg=	Lmin=	Wmax=	Alpha1=	Aigbinv=	Xjv s=	Em=
Rbodymod=	Dtox=	Nsub=	K3=	Vth0=	Cgso=	Eta0=	Jswgs=	Pbd=	Tpbsw=	Ngcon=	Lmax=	B0=	Beta0=	Bigbinv=	Bv d=	Ef=
Rgatemod=	Epsrox=	Ndep=	K3b=	Ua=	Cgdo=	Etab=	Pbs=	Njd=	Tcjsw=	Xrcrg1=	Wr=	B1=	Agidl=	Cigbinv=	Bv s=	Af=
Permod=	Cdsc=	Nsd=	W0=	Ua1=	Cgbo=	Pclm=	Njs=	Xtid=	Tpbswg=	Xrcrg2=	Wint=	Cgsl=	Bgidf=	Nige=	Gbmin=	Kf=
Geomod=	Cdscb=	Phin=	Dvtp0=	Ub=	Xpart=	Pdiblc1=	Xtis=	Mjd=	Tcjswg=	Xw=	Dwg=	Cgdl=	Cgidf=	Nigbinv=	Rbdb=	Imelt=
Fnoimod=	Cdscd=	Ngate=	Dvtp1=	Ub1=	Delta=	Pdiblc2=	Mjs=	Pbswd=	Acde=	Xl=	Dwb=	Ckappas=	Egidf=	Nigbacc=	Rbpb=	AllParams=
Tnoimod=	Cit=	Gamma1=	Lpe0=	Uc=	Rsh=	Pdiblc b=	Pbsws=	Mjswd=	Moin=	Lint=	Wf=	Ckappad=	Aigc=	Ntox=	Rbsb=	
Igcmmod=	Nfactor=	Gamma2=	Lpeb=	Uc1=	Rdsw=	Fprout=	Mjsws=	Pbswg d=	Noff=	Lf=	Wlc=	Cf=	Bigc=	Eigbinv=	Rbps=	

CD4007 MOSFET Array

- To avoid damaging the transistors, make sure that you always turn the power off before making any circuit changes

