


EE2245 Microelectronics Labs

Final Exam

Date: January 15, 2016

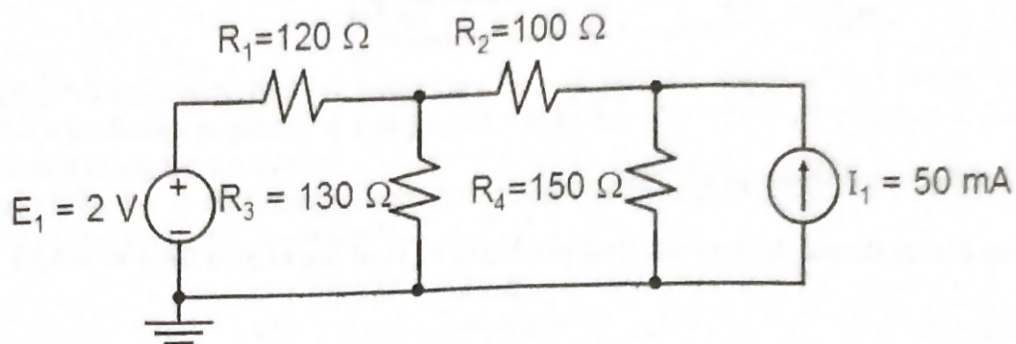1. DC Circuit (10%)

Please calculate the voltage V_i and the current I_i across and through R_1 and R_2 .



2. Time-domain Responses (8%)

Consider the circuit shown in Fig. 1. If the waveform of v_o contains ripples, which action(s) below help to suppress or even remove the ripples? (i) increase R (ii) increase L (iii) increase C? Please explain your answers clearly.

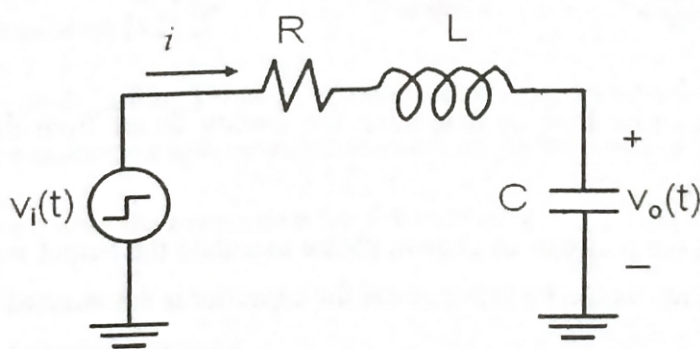


Fig.1

3. Passive filters (18%)

Consider the circuit shown in Fig. 2.

- (a) (6%) Please **derive** the transfer function (in terms of s) for $v_o(s)/v_i(s)$.
- (b) (4%) According to the answer in (a), is it a low-pass, or band-pass, or high-pass filter? Please **explain** your answers clearly.
- (c) (8%) If we would like to increase the quality factor of the filter, how could **the**

individual components (i)R (ii)C (iii)L be adjusted? Please explain your answers clearly.


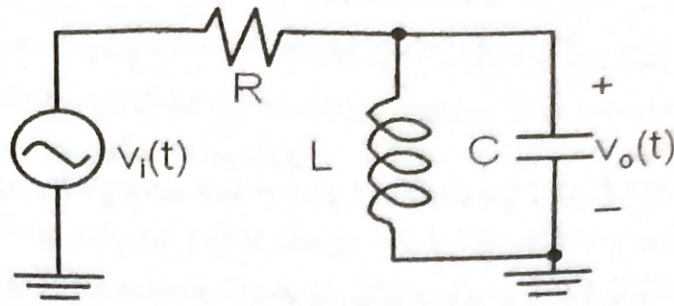


Fig.2

$\frac{1}{sL} + sC$
 $\frac{1 + s^2 LC}{sL}$


4. Active filters and Opamps (20%)

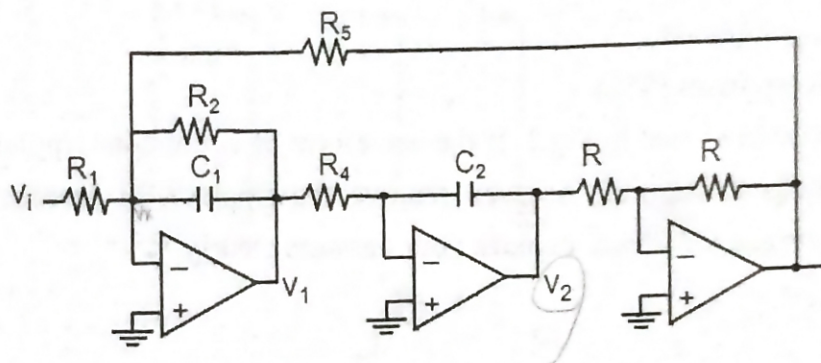(a) (10%) Please derive the transfer function $V_2(s)/V_i(s)$ of the biquad filter as shown below.




(b) (5%) Please describe how to determine the quality factor from the measured frequency response.

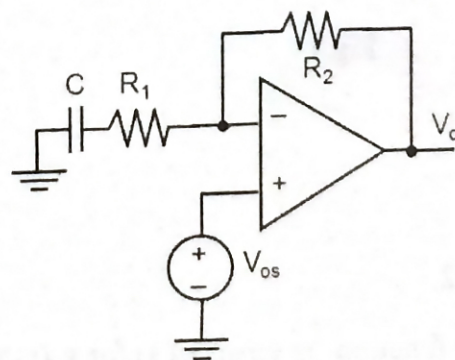(c) (5%) For the op-amp circuit as shown, please calculate the output voltage due to the dc offset V_{os} . What would be the output if the capacitor is not inserted?




5. Oscillators (20%)

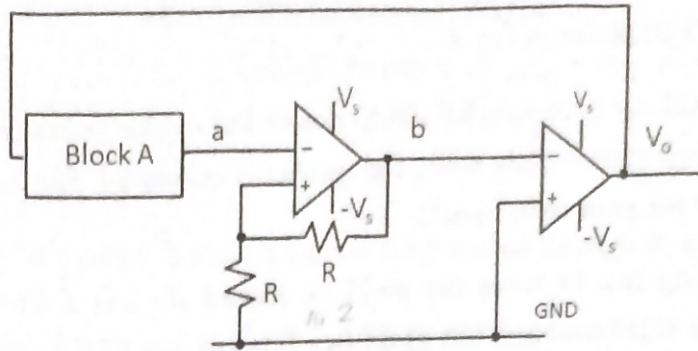(a) (5%) Below is an incomplete schematic of the triangular, square-wave oscillator circuit used in our lab. Please draw the circuit diagram represented by Block A.



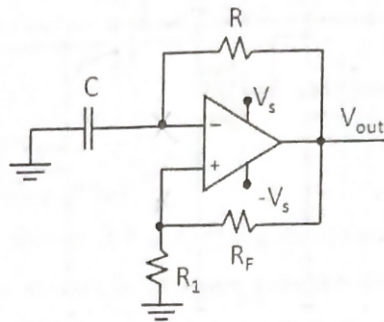- (b) (5%) Following part (a), given that $V_s = 10\text{ V}$, please draw at least one period for the waveforms at points a and b , and make sure the relationship between them is correct along the time axis.
- (c) (10%) For the relaxation oscillator as shown below, please derive the frequency of the output oscillating between V_{\max} and $-V_{\max}$.



6. MOS Transistors (12%)

Consider the circuit in Fig. 3. Let g_m represent the transconductance of the transistor and assume the channel-length modulation effect of the transistor is negligible.

- (a) (4%) Please derive **the expression for the voltage gain v_o/v_i** .
- (b) (8%) If we increase V_G but find the voltage gain v_o/v_i reduces, **what is the likely reason** for this phenomenon?

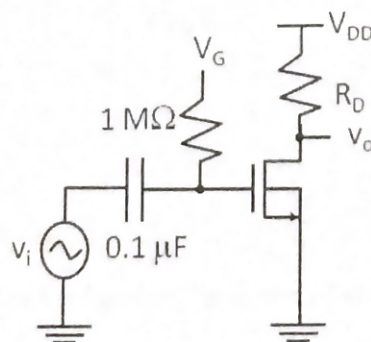


Fig.3

7. MOS Amplifiers (12%)

Consider the MOS amplifier in Fig. 4.

- (a) (4%) Let the voltage gain v_o/v_i be 100dB before the speaker is connected. But the voltage gain drop significantly when the speaker is connected. Would you **explain the reason for the gain reduction**?
- (b) (8%) Following (a), to solve the problem, should we add a **(i)common-gate amplifier** or a **(ii)common-drain amplifier** between v_o and the speaker? Please **explain your answer** clearly.

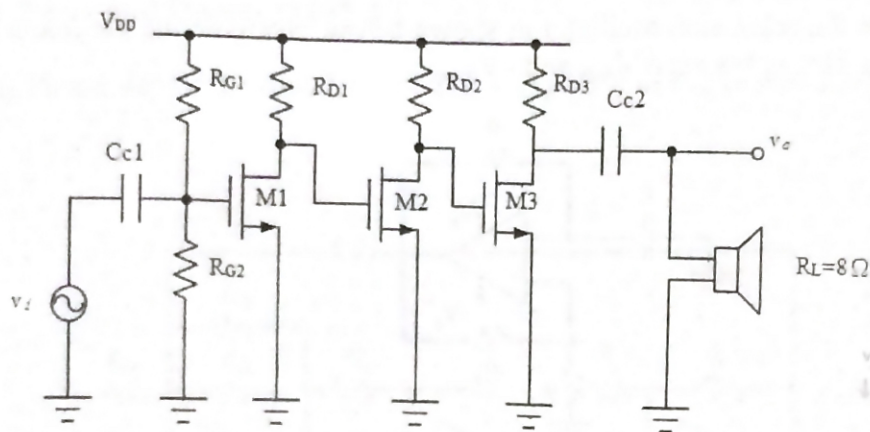


Fig.4