



## EE 2240 Basic Circuit Laboratory

### Final Examination, 6/12/2007

1. (20%)

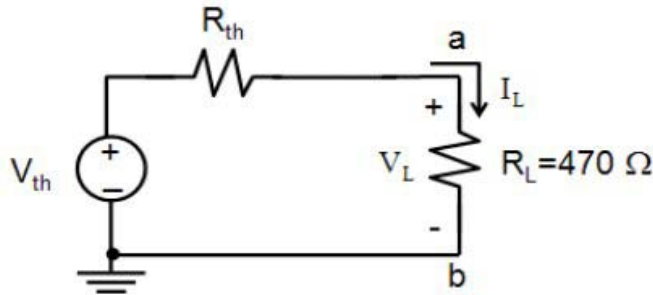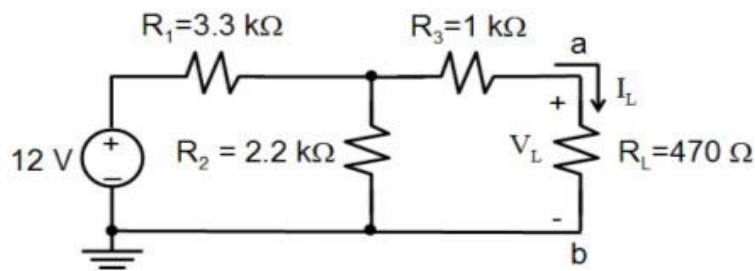(1) (8%) Please calculate the Thévenin voltage  $V_{th}$  and resistance  $R_{th}$  of the circuit.

**Ans:**  $V_{th} = 12 * 2.2k / (2.2k + 3.3k) = 4.8$ .  $R_{th} = 1k + (2.2k \parallel 3.3k) = 2.32k\Omega$ .



(2) (12%) For the circuit below:

(2-1) (3%) Can we measure the voltage  $V_R$  of the resistance directly using the oscilloscope? Please explain.

**Ans:** No.  $V_c$  would be shorted by doing so.

(2-2) (4%) Will the peak-to-peak voltage values satisfy the equation  $V_{C(p-p)} + V_{R(p-p)} = E_{(p-p)}$ ? Please give your reasoning to the answer.

**Ans:** No. It should be:  $V_{C(p-p)}^2 + V_{R(p-p)}^2 = E_{p-p}^2$ .

(2-3) (5%) How would you obtain/judge the phase difference, including the sign (+ or -) and value, between the sinusoidal signals  $V_c$  and  $E_s$  of the period  $T$  on the oscilloscope?

**Ans:** (1) Find the time difference  $\Delta T$  of the input and output signals.

(2) For  $V_c$  is lagging behind the input signal of period  $T$ ,  $V_c$  will appear on the right of the input. Then


$$\theta = -\frac{\Delta T}{T} \times 360^\circ$$

2. (25%)

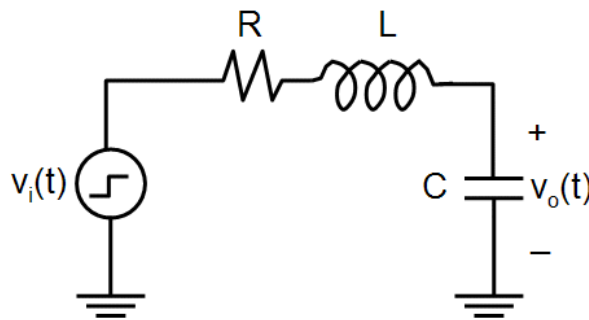(1) (15%) For the R-L-C circuit as shown,  $v_i(t)$  is a unit-step input, and the value of  $R$ ,  $L$ , and  $C$  are  $50 \Omega$ ,  $10 \text{ mH}$ , and  $1 \mu\text{F}$ , respectively. Please calculate the damping ratio, the quality factor, and the natural frequency of the circuit. Also, please compute the rise time and overshoot in the output.


Ans:  $\frac{v_o(s)}{v_i(s)} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$ . Damping ratio = 0.25,  $Q = 2$ ,  $\omega_n = 10000 \text{ rad/s}$ ,

rise time =  $\tan^{-1}\left(-\sqrt{1-\xi^2}/\xi\right)/\left(\omega_n \sqrt{1-\xi^2}\right) = 1.883 \times 10^{-4}$ , overshoot =  $\exp\left(-\xi\pi/\sqrt{1-\xi^2}\right) = 0.4443 = 44.43\%$




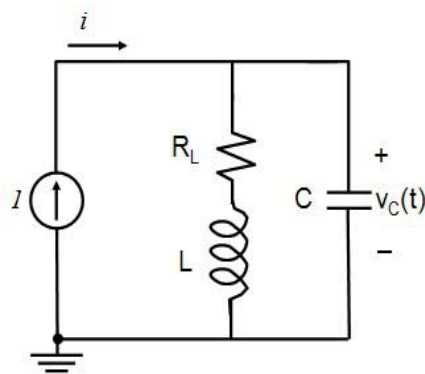(2) (5%) For the circuit as shown below, determine whether the resistance  $R_L$  should be large or small to produce a high quality factor. Give your reasoning.

Ans:  $Q = \omega_r L/R_L$ . So a small  $R_L$  is desired for a large  $Q$ .



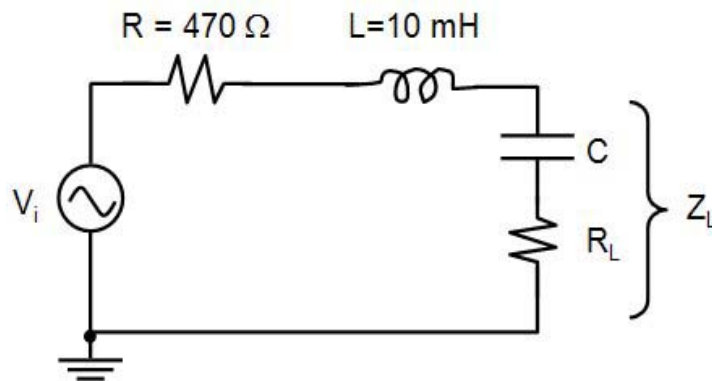
(3) (5%) For the circuit as shown, determine the values of C and  $R_L$  for maximum power transfer to the load  $Z_L$  at 40 kHz.



Ans:  $R_L = 470 \Omega$ .  $\omega L = 1/(\omega C)$ ,  $2\pi(40 \cdot 10^3) \cdot (10 \cdot 10^{-3}) = \frac{1}{2\pi(40 \cdot 10^3)C}$ ,  $C = 1.583 \text{ nF}$

3. (25%)

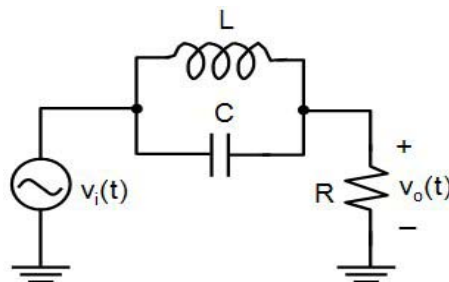
(1) (7%) Find the transfer function  $v_o(s)/v_i(s)$  of the filter as shown, and explain what type of filter it is with your reasoning.



Ans:  $\frac{v_o(s)}{v_i(s)} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$

At  $\omega = 0$ ,  $\left| \frac{v_o(j\omega)}{v_i(j\omega)} \right| = 1$ . At  $\omega = \infty$ ,  $\left| \frac{v_o(j\omega)}{v_i(j\omega)} \right| = 1$ . At  $\omega = 1/\sqrt{LC}$ ,  $\left| \frac{v_o(j\omega)}{v_i(j\omega)} \right| = 0$ . A band-reject filter.

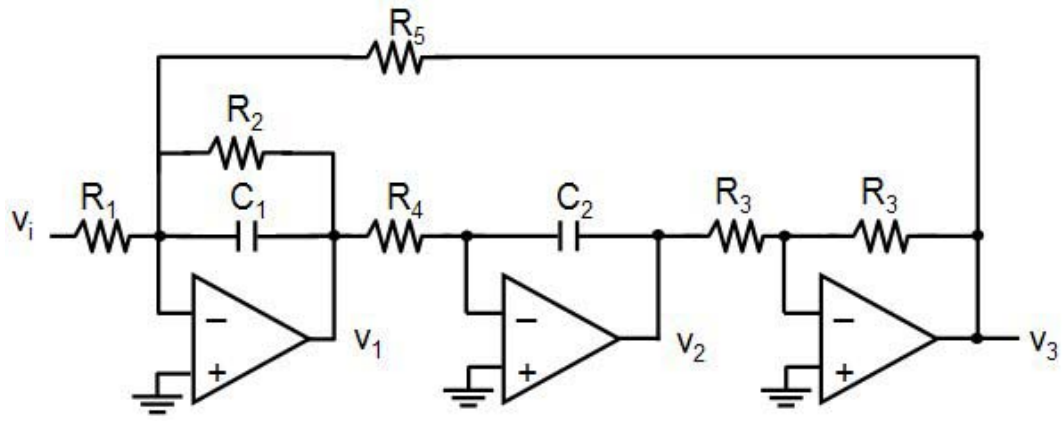
(2) (10%) Find the transfer function  $v_2(s)/v_1(s)$  of the filter as shown.




Ans:  $\frac{v_i}{R_1} + \frac{v_3}{R_5} + \frac{v_1}{R_2} + \frac{v_1}{\frac{1}{sC_1}} = 0, \quad v_2 = -\frac{1}{sR_4C_2}v_1, \quad v_3 = -v_2$

so,  $\frac{v_2(s)}{v_i(s)} = \frac{1}{C_1C_2R_1R_4} \frac{1}{s^2 + \frac{1}{R_2C_1}s + \frac{1}{C_1C_2R_4R_5}}$

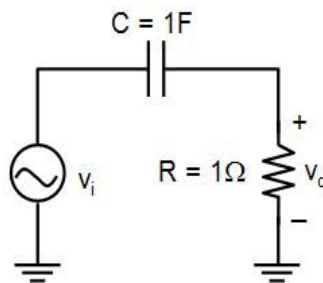(3) (8%) Please draw the frequency response (magnitude and phase) of the R-C circuit as shown. Especially you should provide the values at  $\omega = 0, \infty$ , and the 3dB frequency.



Ans:

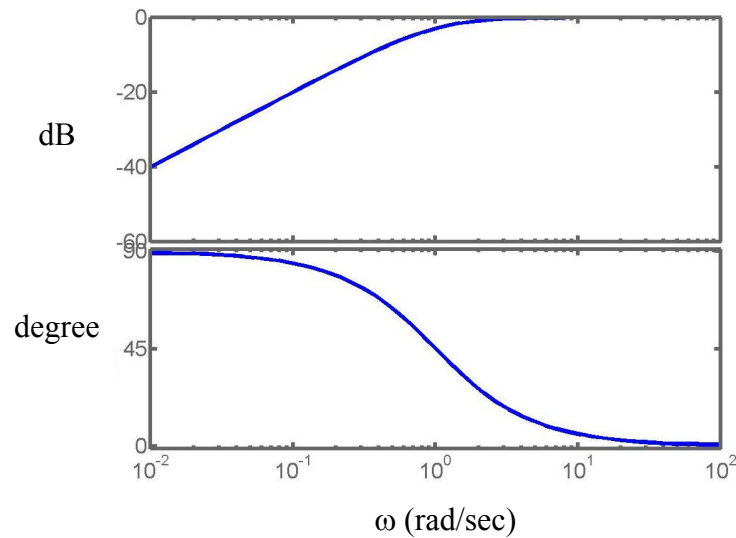


4. (10%) Determine the order of a low-pass Butterworth filter that has a dc gain of 1, a cut-off frequency of 10 kHz, and a gain of no more than -60 dB at 50 kHz.

**Ans:**  $n = \log_{10} \frac{\sqrt{10^{-0.1 \cdot (-60)} - 1}}{\sqrt{10^{-0.1 \cdot (-3)} - 1}} / \log_{10} \left( \frac{50 \text{ kHz}}{10 \text{ kHz}} \right) = 4.2935$ . So  $n = 5$ .

5. (20%)

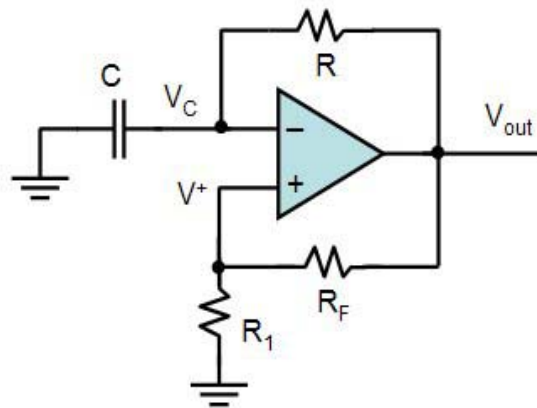(1) (10%) Derive the oscillation frequency of the circuit below.



**Ans:**


**When charging the capacitor:**

$$V_{max} = -\frac{R_1}{R_1 + R_F} V_{max} + \left( V_{max} - \left( -\frac{R_1}{R_1 + R_F} V_{max} \right) \right) \cdot \left( 1 - e^{-\frac{t}{RC}} \right)$$

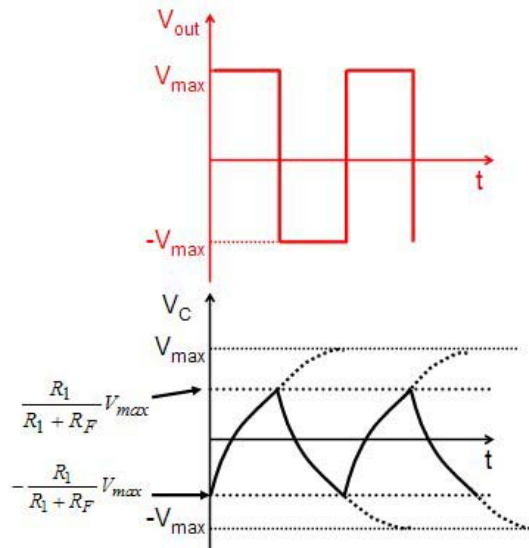
**At  $t = T/2$ :**

$$\frac{R_1}{R_1 + R_F} V_{max} = -\frac{R_1}{R_1 + R_F} V_{max} + \left( V_{max} - \left( -\frac{R_1}{R_1 + R_F} V_{max} \right) \right) \cdot \left( 1 - e^{-\frac{T/2}{RC}} \right)$$

Then  $T = 2RC \ln \frac{R_F + 2R_1}{R_F}$ ,  $f = 1/T$ .



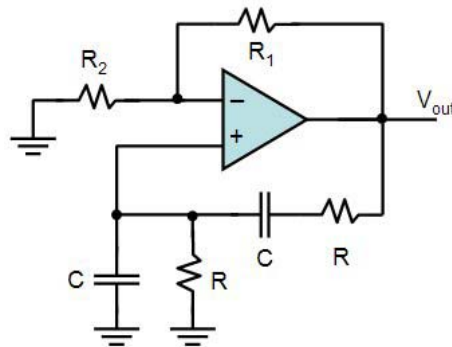(2) (10%) Derive the oscillation frequency of the circuit below, and determine the value of  $R_1/R_2$  to start the oscillation.



Ans:  $\frac{v^+(s)}{v_{out}(s)} = \frac{sRC}{R^2C^2s^2 + 3RCs + 1}$

$$\frac{v^+(j\omega)}{v_{out}(j\omega)} = \frac{j\omega RC}{(1 - \omega^2 R^2 C^2) + j\omega 3RC}$$

when at resonant frequency =  $1/(RC)$

$$\left| \frac{v^+(j\omega)}{v_{out}(j\omega)} \right| = \frac{1}{3}, \text{ Then } (1 + R_1/R_2) = 3 \text{ to start the oscillation. } R_1/R_2 = 2.$$