

**Lab 2: Time-Domain Responses of 1<sup>st</sup>- and 2<sup>nd</sup>-Order Circuits (2 Weeks)**

實驗室: 218 組別: \_\_\_\_\_ Names and ID Numbers: 吳俊毅 106061125

**Objectives :**

- (1) Validate conclusions regarding the behavior of capacitors in a steady-state dc network.
- (2) Validate the behaviors of the 1<sup>st</sup>-order RC circuits.
- (3) Design and implement a RLC circuit with the desired specifications.


**Equipment Required :**

Resistors: 1 kΩ, 5.1 kΩ, 20 kΩ

Capacitors: 1 μF, 2.2 μF, 100 μF

Instruments: Multimeter, Oscilloscope, function generator, and dc power supply.

注意：填寫實驗數據時如有『單位』請記得填入。

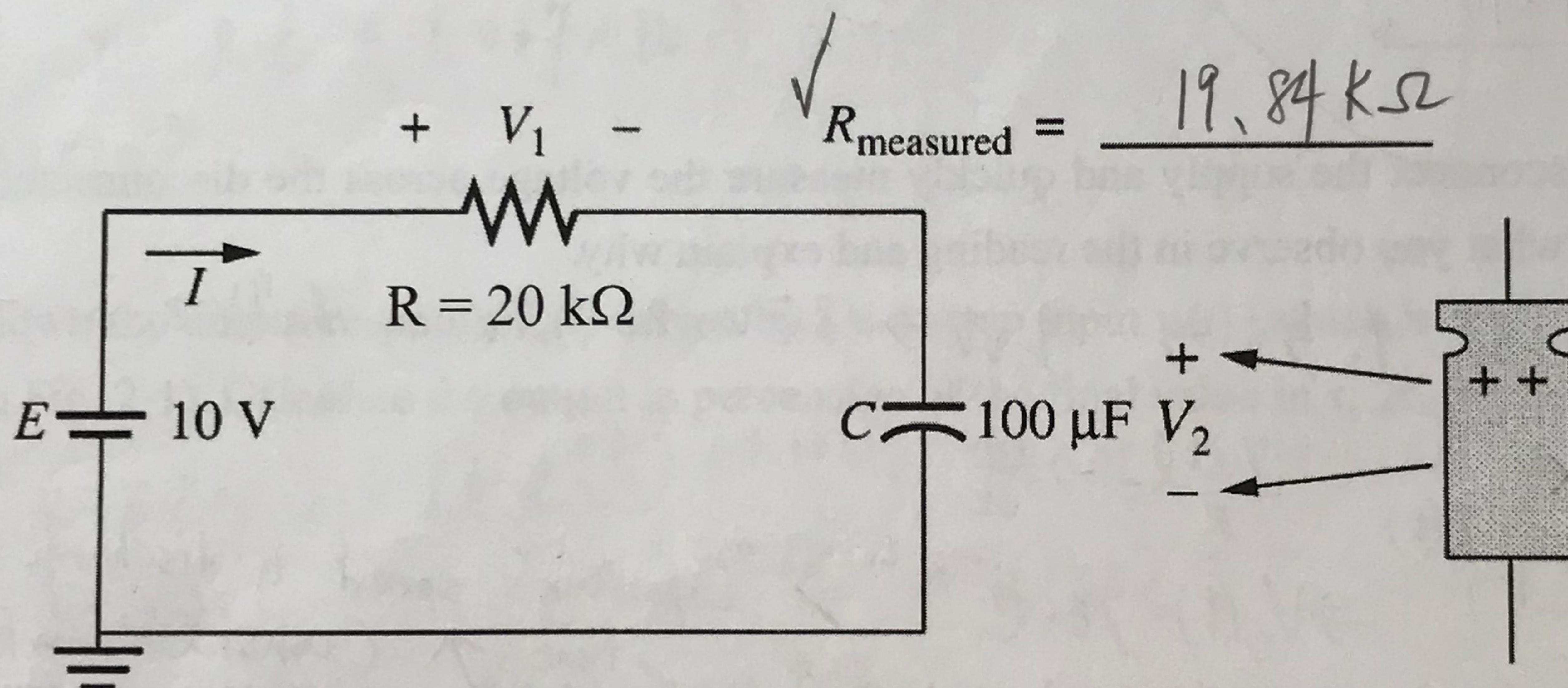**Procedure :****Part 1: Basic Series R-C Circuit****Figure 1-1**

- (a) Construct the network as shown in Fig. 1-1. Insert the measured resistance value. Be sure to note polarity on electrolytic capacitor as shown in the figure.

- (b) Show your calculation of the steady-state value (defined by a period of time greater than five time constants) of the current  $I$  and the voltages  $V_1$  and  $V_2$ .

Calculation:  $V_1 = V_0 e^{-\frac{t}{RC}} = 10e^{-\frac{t}{5T}} = 0.0674 \text{ V}$

$$V_2 = V_0 (1 - e^{-\frac{t}{RC}}) = 9.9326$$

$$I = \frac{V_1}{R} = \frac{0.0674}{19840} = 3.397 \mu\text{A}$$

$$I = 3.397 \mu A, V_1 = 0.0674 V, \text{ and } V_2 = 9.9326 V.$$

(c) Measure the steady-state voltages  $V_1$  and  $V_2$  and calculate the current from Ohm's law. Compare with results from part 1(b).

$$\checkmark V_1 = 0.0628, V_2 = 9.988, \text{ and } I = 0.141 \mu A$$

Comment:

$$I = \frac{0.0628}{19840} = 0.141 \mu A < I_{\text{calculated}} (3.397 \mu A) \quad (\text{過太久才去觀測} \quad (t \gg 5T))$$

實電流值小於電流變得不小 ( $I_c = e^{-\frac{t}{RC}}$ )

(d) Calculate the energy stored in the capacitor.

Calculation:

$$W = \frac{1}{2} C V_2^2 = \frac{1}{2} \times 93 \times 10^{-6} \times (9.988)^2 = 4.638 \times 10^{-3} J$$

$$W = 4.638 \times 10^{-3} J$$

(e) Carefully disconnect the supply and quickly measure the voltage across the disconnected capacitor.

Please describe what you observe in the reading and explain why.

Comment:  $9.9V \rightarrow 9.3V \rightarrow 9.0V \rightarrow 8.5V \rightarrow 7.9V \rightarrow 6.7V \dots \rightarrow 0V$

$$\frac{dV_C(t)}{dt} + \frac{1}{RC} V_C(t) = 0 \quad \frac{V_C(t)}{R} = -C \frac{dV_C(t)}{dt}$$

$$\Rightarrow V_C(t) = 10 \cdot e^{-\frac{1}{RC} t}$$

$\Rightarrow$  Capacitor's speed to discharge got faster as time  $\uparrow$  (consistent with observation)

(f) Short the capacitor by connecting a wire to both terminals and then measure  $V_C$  again. What happens after this step?

Comment:

$V_C = 0$ , and  $Q = CV_C \Rightarrow Q = 0$ . Capacitor is discharged due to short circuit

## Part 2: Time-Domain Response of the Basic R-C Circuit

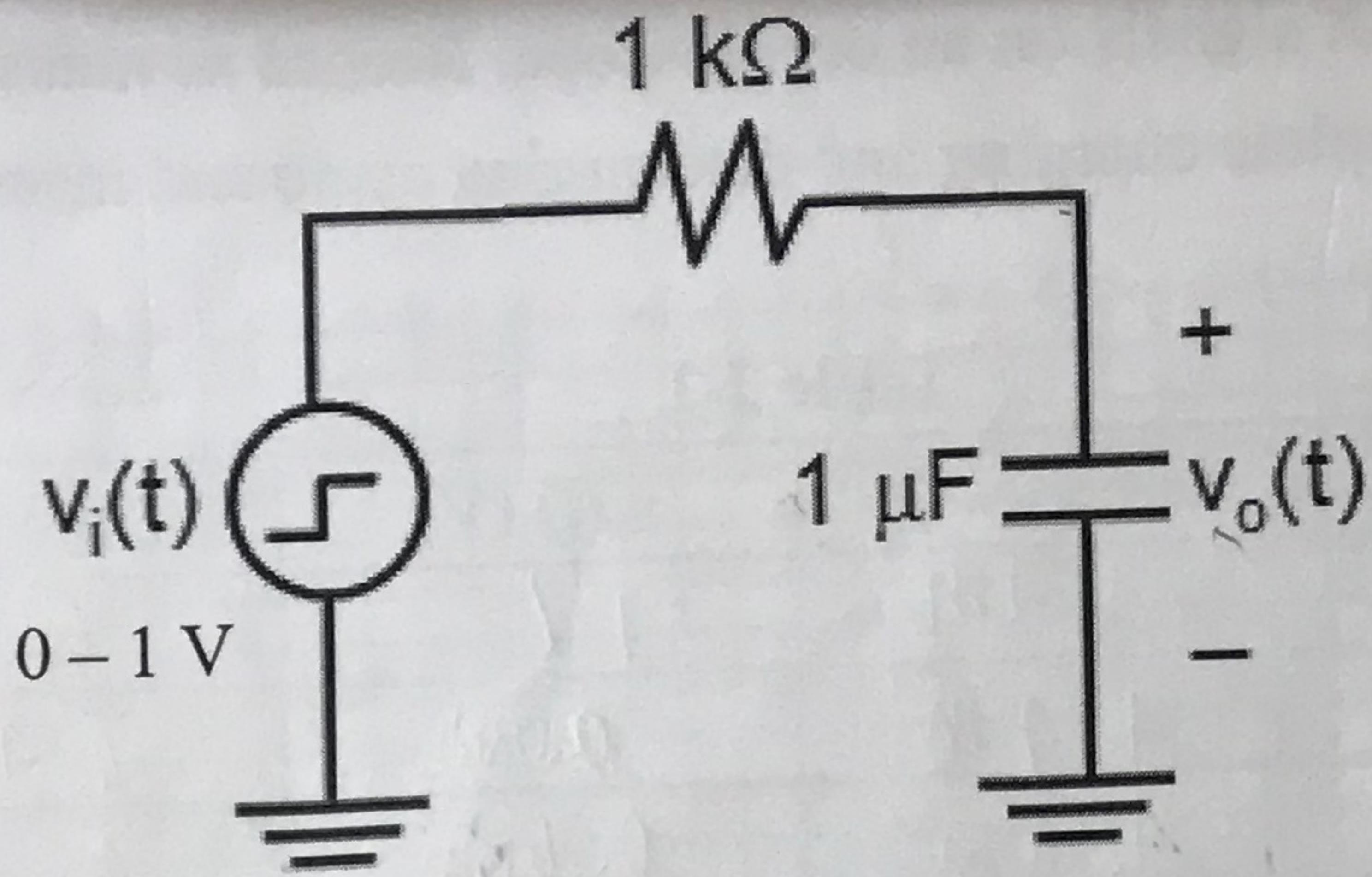


Figure 2-1

- ✓ (a) Construct the  $RC$  circuit of Fig. 2-1. Measure the resistance and capacitance values. Use the function generator to produce the input square waveform  $v_i(t)$  with a minimum value at 0 V and a maximum value at 1 V. Check the input waveform on a oscilloscope before you connect it to the circuit.

$$R = 1.031 \text{ k}\Omega, C = 1.034 \mu\text{F}$$

- (b) Calculate the  $RC$  time constant  $\tau$  using the measured resistance.

Calculation:  $\tau = R \cdot C = 1.037 \times 10^{-3}$

$$\tau = 1.037 \times 10^{-3} \text{ s}$$

✓

- (c) Write down the output response  $v_o(t)$  driven by a unit-step input  $v_i(t)$  (which is replaced by a square waveform in Fig. 2-1). Calculate the output in percentage of the final value in  $\tau, 2\tau, 3\tau, 4\tau$ , and  $5\tau$ .

Calculation:  $v_o(\tau) = v_i(t) (1 - e^{-1}) = 0.6321$        $v_o(4\tau) = v_i(t) (1 - e^{-4}) = 0.9817$   
 $v_o(2\tau) = v_i(t) (1 - e^{-2}) = 0.8647$        $v_o(5\tau) = v_i(t) (1 - e^{-5}) = 0.9933$   
 $v_o(3\tau) = v_i(t) (1 - e^{-3}) = 0.9502$

$$v_o(\tau) = 63.21 \% v_i(t), v_o(2\tau) = 86.47 \% v_i(t), v_o(3\tau) = 95.02 \% v_i(t), v_o(4\tau) = 98.17 \% v_i(t), \\ v_o(5\tau) = 99.33 \% v_i(t)$$

- ✗ (d) Based on the time constant, determine a proper input frequency  $f_i$  that would allow you to clearly observe the transient and steady-state responses of the output waveform. Comment on how you pick the frequency.

$$f_i = \frac{1}{5\tau} = \frac{1}{5RC}$$

Comment:

$$f_i \leq \frac{1}{5\tau} = \frac{1}{5RC}$$


$$\text{choose } T = 10\tau \Rightarrow f_i = \frac{1}{10\tau} = 96.41 \text{ Hz}$$

- ✓ (e) Display the input and output signals on an oscilloscope. Record as many data points as possible of the output waveform in one complete charging and discharging cycle and insert them in Table 2-1.

Table 2-1

| Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) |
|------------|--------------|------------|--------------|------------|--------------|
| -950 $\mu$ | 0.04         | 3.4 m      | 1.12         | 6 ms       | 0.22         |
| -400 $\mu$ | 0.52         | 4.4 m      | 0.81         | 6.4 m      | 0.18         |
| 200 $\mu$  | 0.14         | 4.6 m      | 0.68         | 6.6 m      | 0.14         |
| 1.2 m      | 0.9          | 5 m        | 0.5          | 7 m        | 0.1          |
| 2 m        | 0.98         | 5.2 m      | 0.42         | 7.2 m      | 0.01         |
| 2.6 m 5    | 0.99         | 5.6 m      | 0.32         | 7.8 m      | 0.06         |

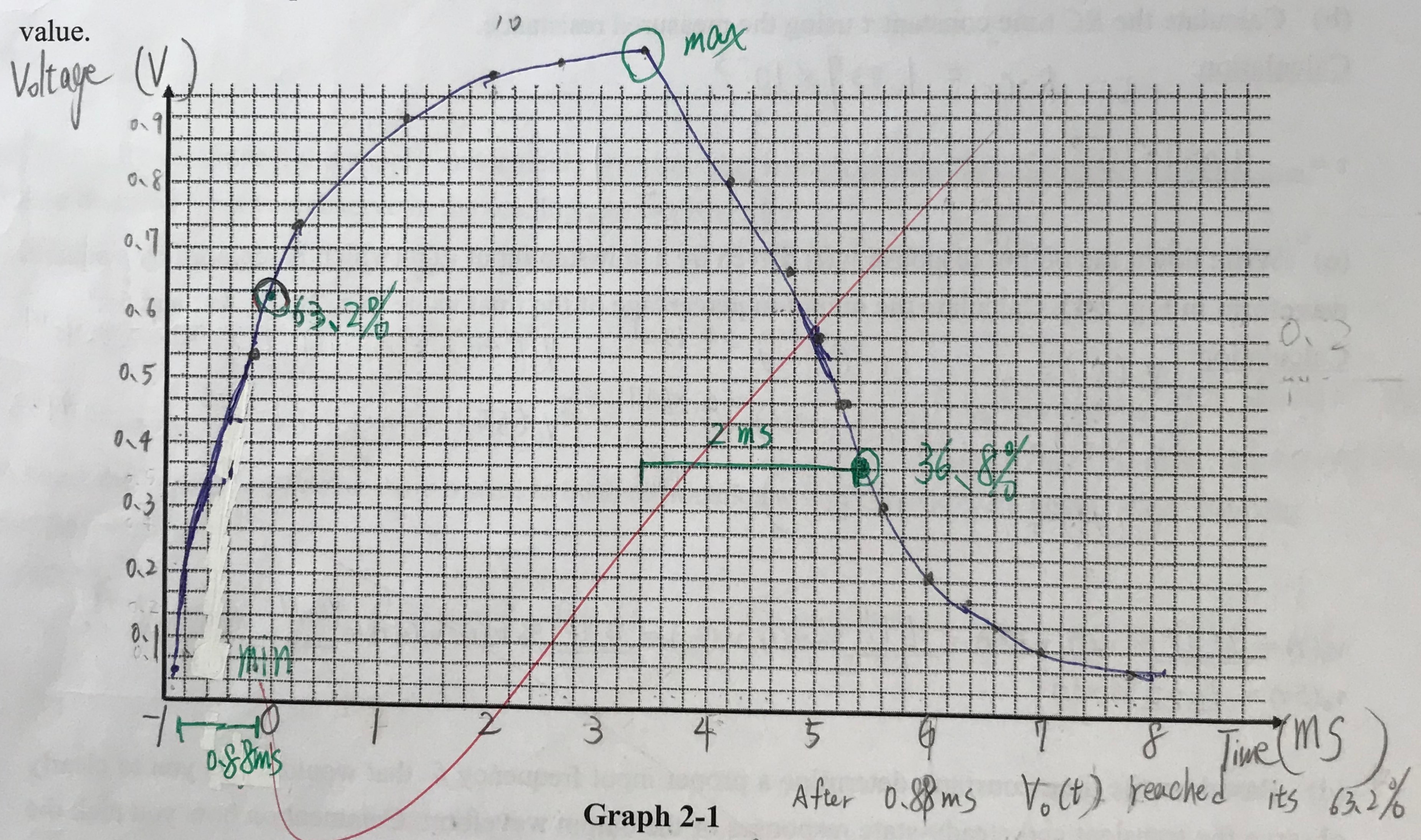- (f) Plot one period of the output response (charging and discharging) on Graph 2-1. Label the voltage and time at 63.2% of the steady-state value when charging the capacitor, and the voltage and the time at 36.8% of the steady-state value when discharging the capacitor. You must label the unit of time on the x axis. Calculate the capacitance value based on the measured time constant and the measured resistor value.




$$C_{measured} = 0.877 \mu F$$

$$t = 0.88 \text{ ms} = 1.003 \text{ } K \cdot C \Rightarrow 0.877 \mu F$$

- (g) Repeat part (f) by using an input square waveform with a period of only two  $RC$  time constants ( $T = 2RC$ ). The output would look like a sawtooth waveform. Plot one period of the steady-state output

$$f = 48.16 \text{ Hz}$$

waveform on Graph 2-2, and label the maximum and minimum voltage values. Comment on if the voltage levels are reasonable based on your analysis.

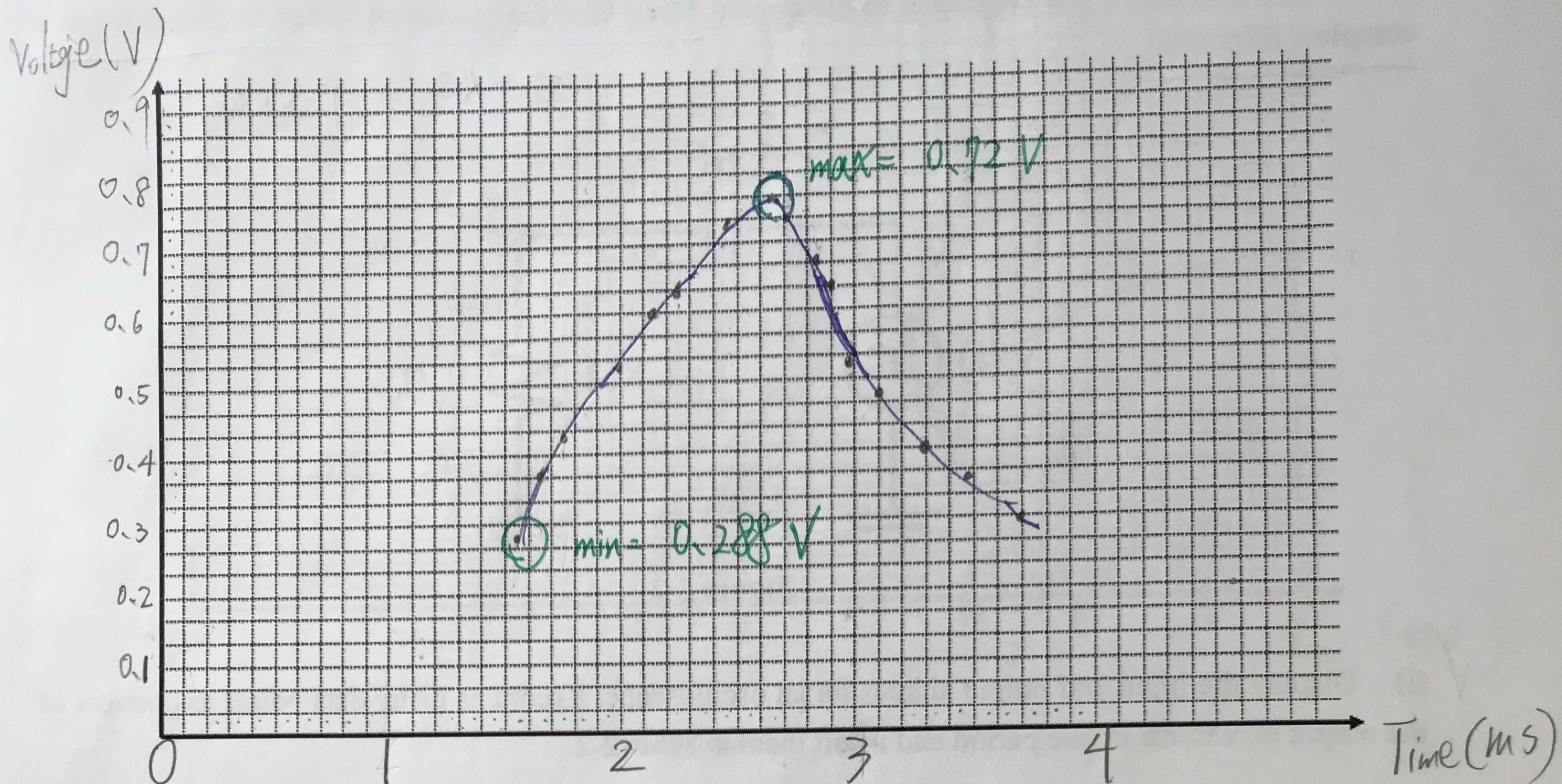

Graph 2-2

Analysis & Comment:

| Time (sec) | $V_o(t) (v)$ |
|------------|--------------|
| 1.56 m     | 288 m        |
| 1.68 m     | 368 m        |
| 1.76 m     | 416 m        |
| 1.8 m      | 432 m        |
| 1.84 m     | 456 m        |
| 2 m        | 528 m        |
| 2.08 m     | 568 m        |
| 2.16 m     | 600 m        |
| 2.24 m     | 6.24         |
| 2.44 m     | 688 m        |
| 2.56 m     | 720 m        |
| 2.72 m     | 648 m        |
| 2.8 m      | 608 m        |
| 2.96 m     | 520 m        |
| 3.12 m     | 456 m        |
| 3.28 m     | 392 m        |
| 3.4 m      | 360 m        |
| 3.6 m      | 296 m        |

- 1. max value is 0.72 V. In theory,  $V_c(2T)$  because = 0.86. It's probably due to internal resistor inside voltmeter, so there is error
- 2. Voltage across capacitor didn't reach its original maximum, minimum (0, 0 V). Because period of square wave is too short to charge and discharge capacitor completely
- 3. min value ≠ 0, reasonable! Capacitor was not discharged completely

- (h) Construct the  $RC$  circuit of Fig. 2-2. Use the function generator to produce the input square waveform  $v_i(t)$  with a minimum value at 0 V and a maximum value at 1 V. Check the input waveform on an oscilloscope before you connect it to the circuit. Make sure the waveform period is proper to get a complete response.

$$\tau = RC \Rightarrow T > 5\tau$$

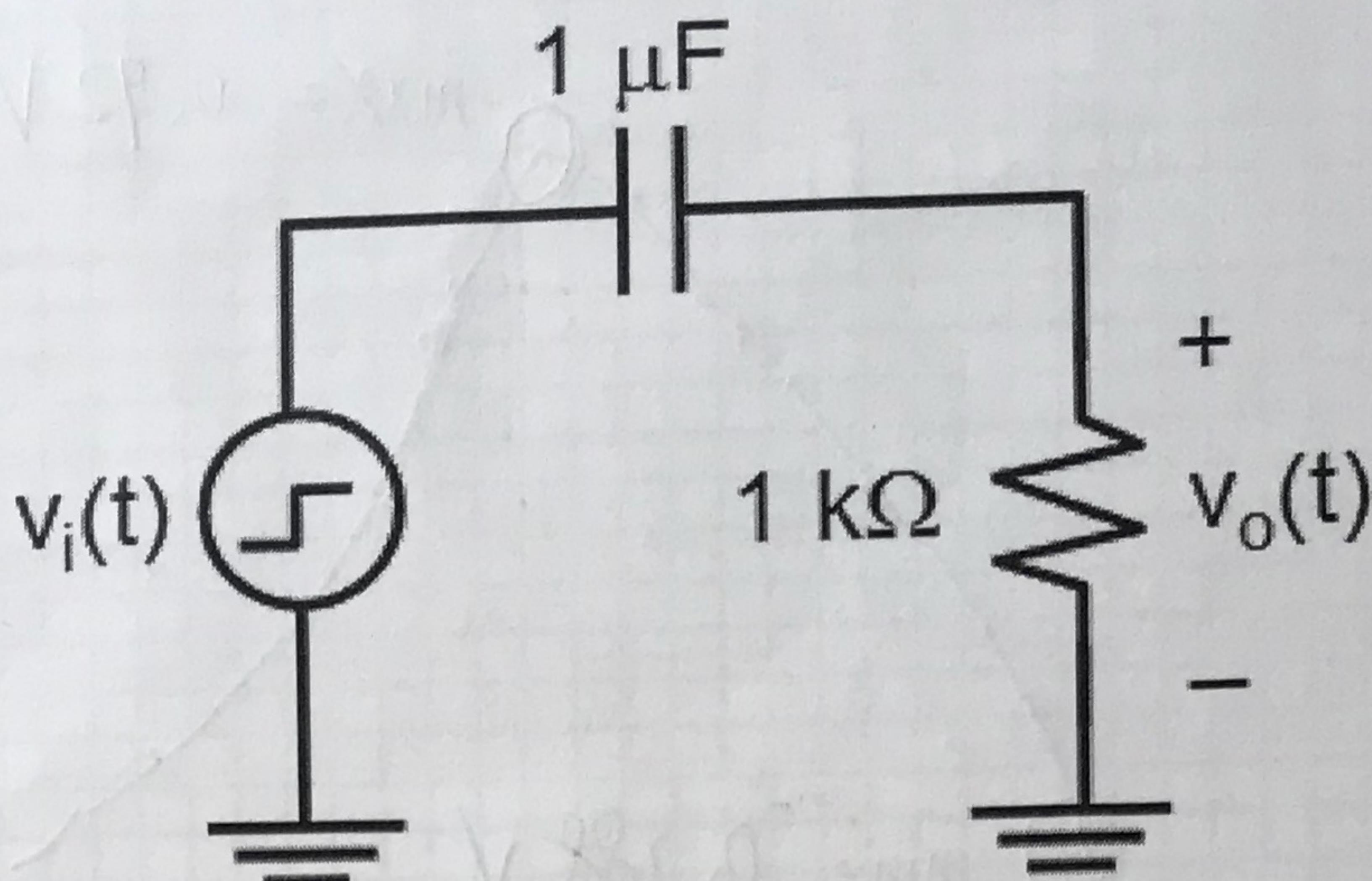


Figure 2-2

- ✓ (i) Display the input and output signals on an oscilloscope. Record as many data points as possible of the output waveform in one period and insert them in Table 2-2.

Table 2-2

| Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) |
|------------|--------------|------------|--------------|------------|--------------|
| 10 ms      | 0            | 13.6 ms    | 0.08         | 16.4 ms    | -0.4         |
| 10.4 ms    | 0.86         | 13.8       | 0.06         | 16.6 ms    | -0.34        |
| 10.6 ms    | 0.72         | 14.2       | 0.06         | 16.8 ms    | -0.28        |
| 10.8 ms    | 0.6          | 14.4       | 0.06         | 17.2 ms    | -0.18        |
| 11.2 ms    | 0.42         | 15.2       | 0.04         | 17.6 ms    | -0.14        |
| 12 ms      | 0.22         | 15.6       | -0.8         | 18 ms      | -0.08        |
| 13.2 ms    | 0.1          | 16         | -0.58        | 19.8 ms    | 0            |


- (j) Plot one period of the output response on Graph 2-3 and label the curve. Label the voltage and time at 36.8% of the maximum input value. You must label the unit of time on the x axis. Do you think the measured waveform is correct? Is it accurate based on the measured resistance and capacitance values? Comment accordingly.

Comment:  $\tau = RC = 1003.1 \times 1.034 \times 10^{-6} = 1.037$  ms

$$v_o(t) = e^{-\frac{t}{\tau}} = 0.368 \Rightarrow t_{calculated} = 1.036 \text{ ms}$$

by graph 2.3,  $t_{measured} \approx 1.1 \text{ ms}$  與  $t_{calculated}$  幾乎相同

$$\text{Error is } \frac{1.1 - 1.036}{1.036} = 6.18\%$$

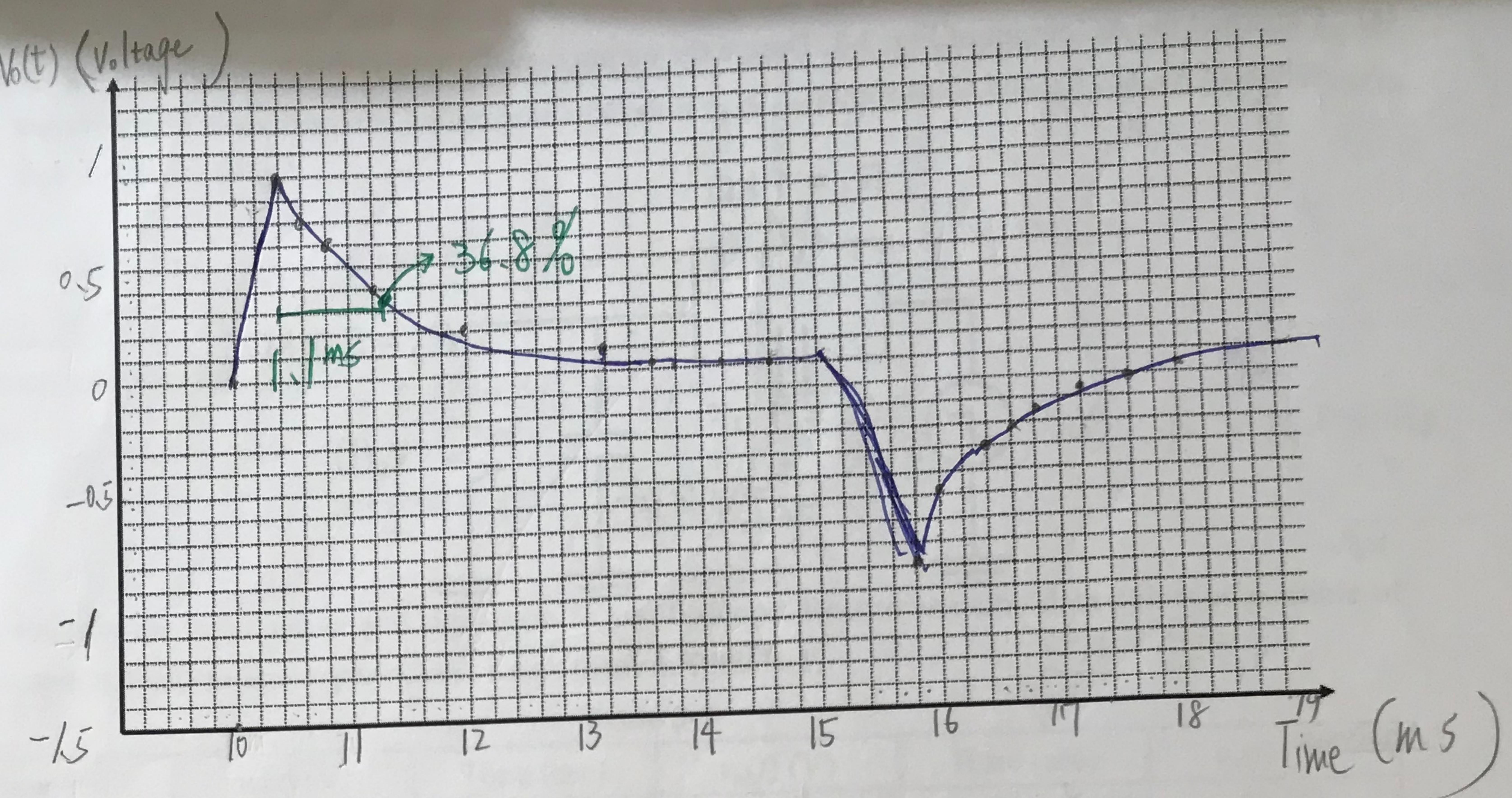

Graph 2-3

**Question:** Please derive the analytic expression of the step response for the RC circuit in Fig. 2-3.

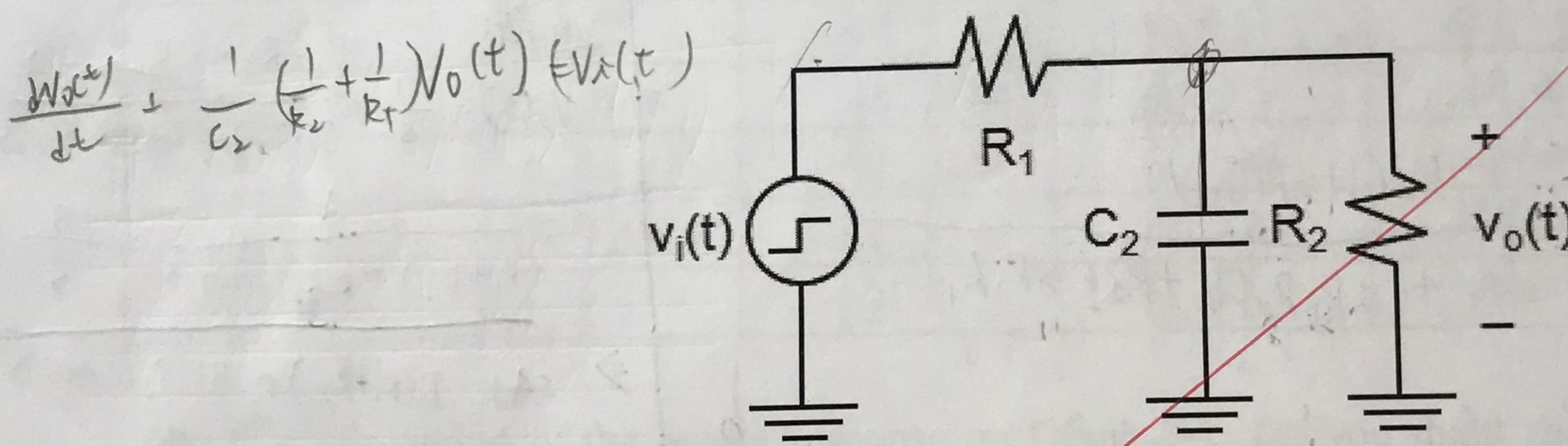


Figure 2-3

Analysis:  $\frac{V_i(t) - V_o(t)}{R_1} = C_2 \frac{dV_o(t)}{dt} + \frac{V_o(t)}{R_2}$

$$\Rightarrow R_1 C_2 \frac{dV_o(t)}{dt} + \frac{1}{C_2} \left( \frac{R_1}{R_2} + 1 \right) V_o(t) = V_i(t)$$

$$\Rightarrow \frac{dV_o(t)}{dt} + \frac{1}{C_2} \left( \frac{1}{R_2} + \frac{1}{R_1} \right) V_o(t) = \frac{V_i(t)}{C_2}$$

$$D + \frac{1}{C_2} \left( \frac{1}{R_2} + \frac{1}{R_1} \right) = 0 \Rightarrow D = -\frac{1}{C_2} \left( \frac{1}{R_2} + \frac{1}{R_1} \right)$$

$$\therefore V_{oh}(t) = A \cdot e^{-\frac{1}{C_2} \left( \frac{1}{R_2} + \frac{1}{R_1} \right) t} \quad (\text{homogeneous})$$

$V_{op}(t) = \frac{R_2}{R_1 + R_2}$  if  $V_i(t)$  is a "unit step function"

$$V_o(t) = A \cdot e^{-\frac{1}{C_2} \left( \frac{1}{R_2} + \frac{1}{R_1} \right) t} + \frac{R_2}{R_1 + R_2} =$$

$$\text{at } t=0, V_o(t)=0 \Rightarrow A = -\frac{R_2}{R_1 + R_2} \quad \therefore V_o(t) = \frac{R_2}{R_1 + R_2} \left( 1 - e^{-\frac{1}{C_2} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) t} \right) u(t)$$

### Part 3: Step Response of a RC network

- (a) Construct the  $RC$  circuit of Fig. 3-1. Derive the output waveform  $v_o(t)$  due to a unit-step input using values of  $R_1$ ,  $C_1$ ,  $R_2$ , and  $C_2$  as shown.

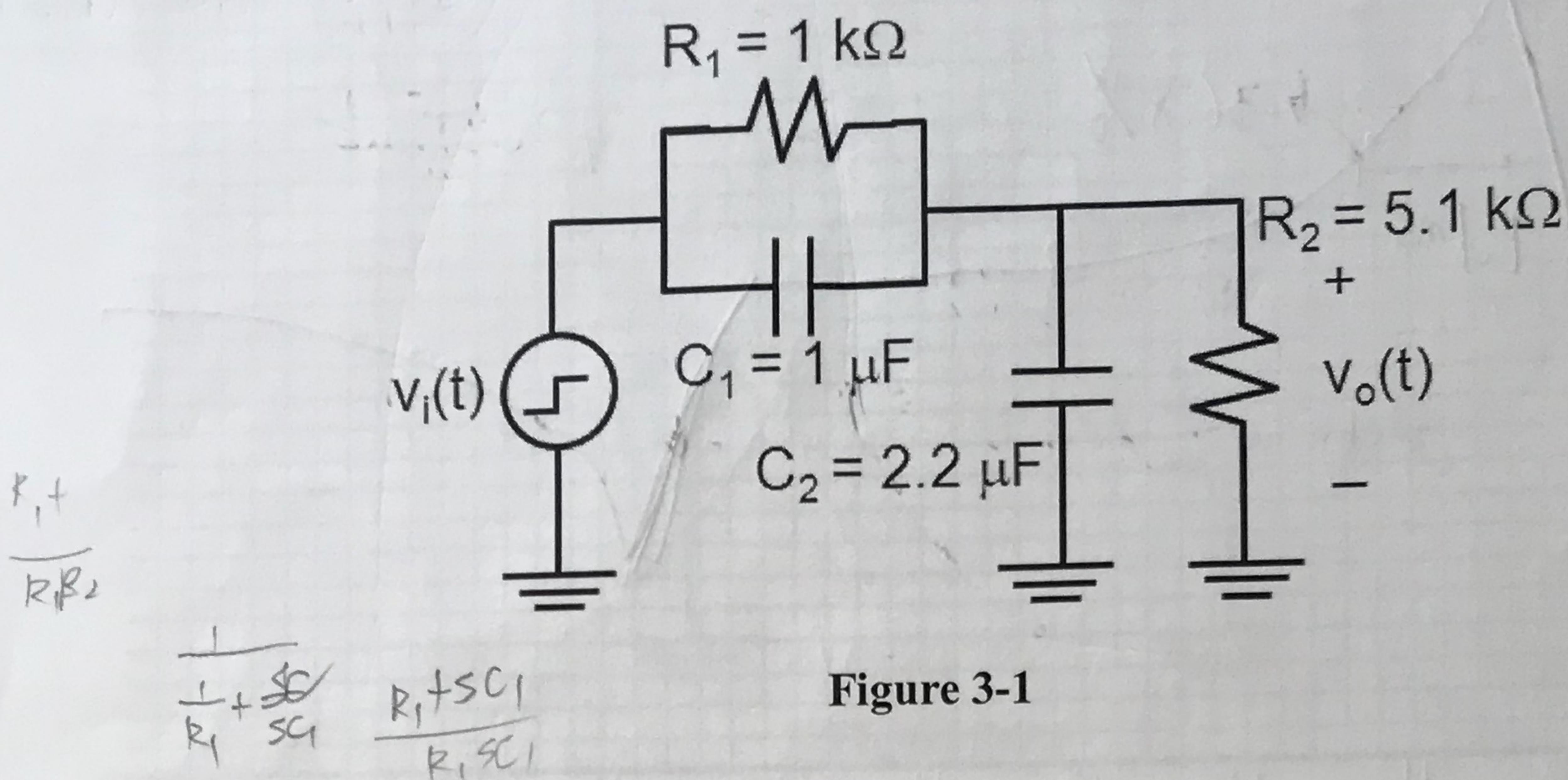


Figure 3-1

Analysis:

$$R_1 \text{ in parallel with } C_1 \Rightarrow \frac{R_1}{1 + sR_1 C_1} \quad (\text{effective resistance})$$

$$R_2 \text{ in parallel with } C_2 \Rightarrow \frac{R_2}{1 + sR_2 C_2} \quad (\text{effective resistance})$$

$$\mathcal{L}\{V_i(t)\} = \frac{1}{s}$$

$$\Rightarrow V_o(s) = \frac{1}{s} \times \frac{R_2(1 + sR_1 C_1)}{1R_1 + sR_1 R_2 C_2 + R_2 + sR_2 R_1 C_1}$$

$$= \frac{5100 + 5.1s}{6100 + 16.32s} \times \frac{1}{s} = \frac{a}{6100 + 16.32s} + \frac{b}{s}$$

$$\therefore a = -0.545, \quad b = 0.836$$

$$\therefore V_o(s) = \frac{-0.524}{s + 3.74} + \frac{0.836}{s}$$

$$V_o(t) = \mathcal{L}^{-1}\{V_o(s)\} = \frac{51}{61}u(t) - 0.524e^{-3.74t}u(t)$$

unit step function

$$= (0.836 - 0.524e^{-3.74t})u(t)$$

通解:

$$V_o(s) = \frac{1}{s} \times \frac{R_2 + R_2 R_1 C_1 s}{(R_1 + R_2) + R_1 R_2 (C_1 + C_2)s}$$

$$= \frac{A}{(R_1 + R_2) + R_1 R_2 (C_1 + C_2)s} + \frac{B}{s}$$

$$\Rightarrow sA + B(R_1 + R_2) + BR_1 R_2 (C_1 + C_2)s$$

$$= R_2 + R_2 R_1 C_1 s$$

$$\Rightarrow s(A + BR_1 R_2 (C_1 + C_2)) + BR_1 R_2$$

$$= sR_2 R_1 C_1 + R_2$$

$$\therefore B = \boxed{\frac{R_2}{R_1 + R_2}}$$

$$A = R_2 R_1 C_1 - \frac{R_2}{R_1 + R_2} \cdot R_1 R_2 (C_1 + C_2)$$

$$= \boxed{\frac{R_1^2 R_2 C_1 - R_2^2 R_1 C_2}{R_1 + R_2}}$$

$$= \boxed{\frac{R_1 R_2 (R_1 C_1 - R_2 C_2)}{R_1 + R_2}}$$

(b) Measure the resistance and capacitance values. Use the measured values to calculate the time constant  $\tau$ . Use the measured time constant to calculate the input frequency  $f_i$  of the square waveform  $v_i(t)$  with a minimum value at 0 V and a maximum value at 1 V. Check the input waveform on a oscilloscope before you connect it to the circuit. What the input frequency  $f_i$  of  $v_i(t)$  that you pick? Why?

$$R_1 = \frac{1.0031 \text{ k}\Omega}{36.825 \text{ Hz}}, C_1 = 1.034 \mu\text{F}, R_2 = 5.108 \text{ k}\Omega, C_2 = 2.2047 \mu\text{F}$$

Comment on the choice of  $f_i$ :

$$T = \frac{R_1 R_2 (C_1 + C_2)}{R_1 + R_2} = 2.715 \text{ ms}$$

$\Rightarrow$  choose  $T \geq 5\tau$  (enough time to charge capacitor)  $\Rightarrow T = 27.15 \text{ ms} \Rightarrow f = 36.825 \text{ Hz}$

- ✓ (c) Display the input and output signals on an oscilloscope. Record as many data points as possible of the output waveform in one period and insert them in Table 3-1.

Table 3-1

| Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) |
|------------|--------------|------------|--------------|------------|--------------|
| 24.8 m     | 0.02         | 34 m       | 0.84         | 42.8 m     | 0.14         |
| 25.6 m     | 0.08         | 37.6 m     | 0.86 max     | 43.6 m     | 0.12         |
| 26 m       | 0.42         | 38.8 m     | 0.86         | 44 m       | 0.1          |
| 27.2 m     | 0.58         | 39.2 m     | 0.5          | 45.6 m     | 0.06         |
| 27.6 m     | 0.62         | 39.6 m     | 0.42         | 46.8 m     | 0.04         |
| 28.8 m     | 0.7 m        | 40.8 m     | 0.28         | 47.6 m     | 0.04         |
| 29.6 m     | 0.74         | 41.2 m     | 0.24         | 48 m       | 0.04         |
| 30.8 m     | 0.78         | 41.6 m     | 0.22         | 49.2 m     | 0.02         |
| 32 m       | 0.82         | 42.4 m     | 0.16         | 50.8 m     | 0.02         |

- (d) Plot one period of the output response on Graph 3-1. Do you think the measured waveform is accurate based on the measured resistance and capacitance values? Comment accordingly.

Comment: Use measured R.C 1st order transient

$$A = -8.572, B = 0.836$$

$$\Rightarrow V_o(s) = \frac{-0.517}{s+368.5} + \frac{0.836}{s} e^{-368.5t} u(t)$$

$$\Rightarrow V_o(t)_{\max} = 0.836 \text{ V}$$

$$V_o(t)_{\text{measured, max}} = 0.86 \text{ V}$$


$$\Rightarrow \text{Error} = \frac{0.86 - 0.836}{0.86} \approx 2.79\%$$

$$\textcircled{2} \text{ When } t = T = 2.715 \times 10^{-3} \text{ s}$$

$$V_o(\tau) = 0.645 \text{ V} \Rightarrow \text{Error} = \frac{0.645 - 0.62}{0.645} \approx 3.015\%$$

$$\text{Measured value} = 0.62 \text{ V}$$

In general, no error is pretty small. The results are very consistent!

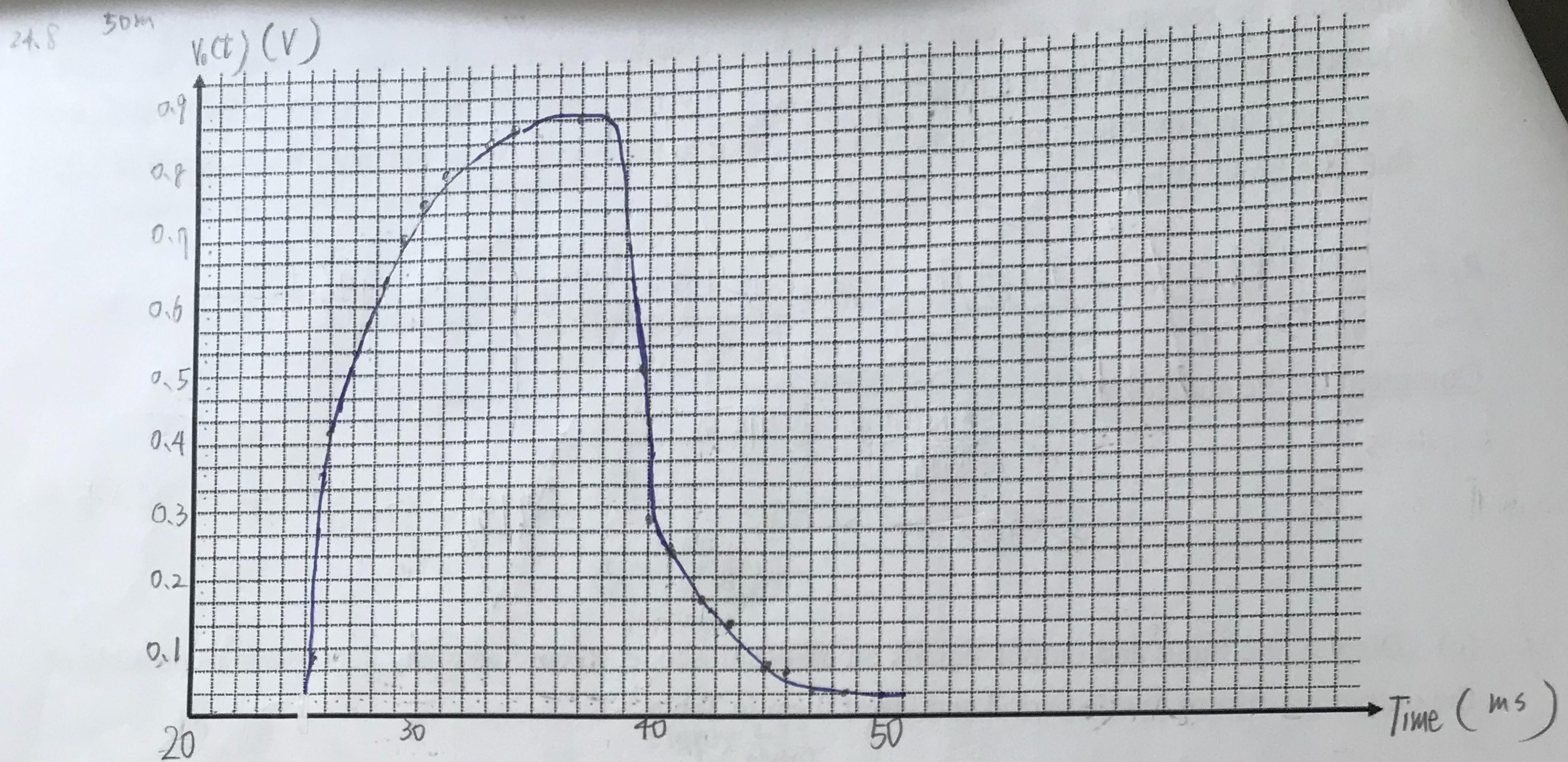

Graph 3-1

**Part 4: Design Problem: Under-Damped Response of the 2<sup>nd</sup>-Order Series RLC Circuit**

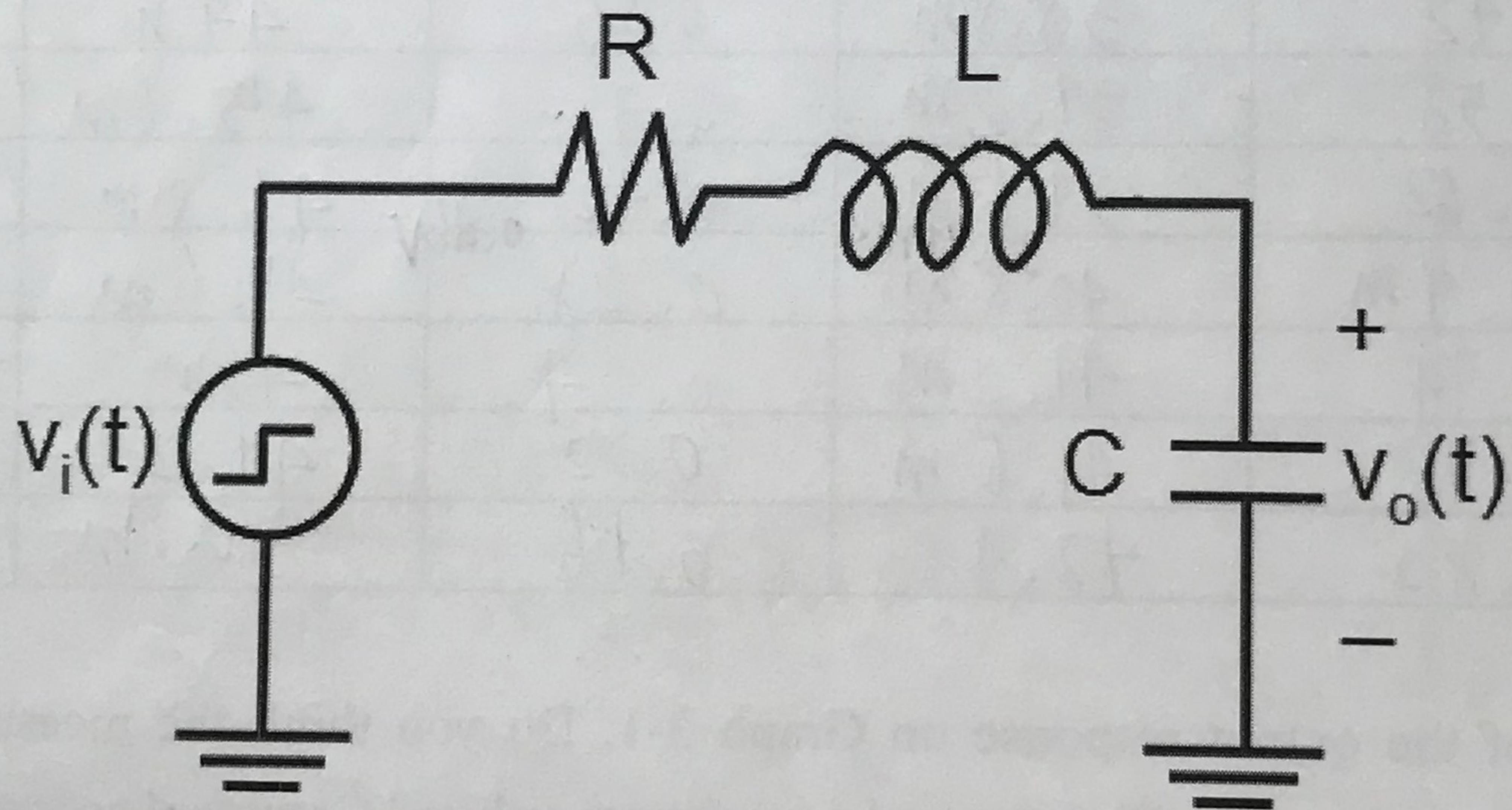


Figure 4-1

- (a) A 2<sup>nd</sup>-order series RLC circuit is shown in Fig. 4-1. You are required to select the proper  $R$ ,  $L$ , and  $C$  in the circuit to achieve the following design specifications for the output response under a step input (use square waveform with the minimum and maximum values of 0 V and 1 V, respectively).

(1) Rise time = 100 to 110  $\mu$ s;  $t_r$

(2) Overshoot = 30 to 40%  $M_p$

Show your calculation for the design, and report values of the passive elements. Report the passive elements that you actually use in experiment.

$$R_{cal} = \frac{1265 \Omega}{1053 \Omega}, L_{cal} = \frac{100 \text{ mH}}{100.11 \text{ mH}}, \text{ and } C_{cal} = \frac{25 \text{ nF}}{26.5 \text{ nF}}$$

Calculation:

$$M_p = e^{-\left(\frac{\gamma}{\sqrt{1-\gamma^2}}\right) \pi t}$$

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$\text{Let } M_p = 0.35$$

$$\Rightarrow -\frac{\gamma}{\sqrt{1-\gamma^2}} \pi t = \ln(0.35)$$

$$\gamma_d = \omega_n \sqrt{1-\gamma^2} \Rightarrow \gamma = \frac{|\ln(0.35)|}{\sqrt{|\ln(0.35)|^2 + \pi^2 t^2}} = 0.317$$

$$f = \frac{R}{2\pi} = 6280 \text{ Hz}$$

$$\Rightarrow \text{choose } f = 628 \text{ Hz}$$

square wave frequency

Objective:  
 $t_r = 100 \mu\text{s}$   
 $M_p = 35\%$

$$t_r = \frac{\tan^{-1}\left(\frac{-\sqrt{1-\gamma^2}}{\gamma}\right)}{\omega_d}$$

$$\text{Let } t_r = 100 \mu\text{s} \text{ rad}$$

$$\omega_d = \frac{\tan^{-1}\left(\frac{-\sqrt{1-\gamma^2}}{\gamma}\right)}{t_r}$$

$$= 18932 = \omega_n \sqrt{1-\gamma^2}$$

$$\Rightarrow \omega_n = 19961.5$$

$$\Rightarrow LC = 2.5 \times 10^{-9}$$

$$\text{choose } L = 100 \text{ mH}, C = 25 \text{ nF}$$

$$R = 1265 \Omega$$

- ✓ (b) Display the input and output signals on an oscilloscope. Be aware, the function generator has a source impedance of  $50 \Omega$  which will affect the total resistance. Record the data points of the output waveform when the capacitor is charged in Table 4-1. You must show TA your waveform with the correct rise time and overshoot.

Table 4-1

| Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) | Time (sec) | $v_o(t)$ (V) |
|------------|--------------|------------|--------------|------------|--------------|
| 0          | 0.68         | 240 $\mu$  | 1            | 960 $\mu$  | -0.12        |
| 10 $\mu$   | 0.8          | 730 $\mu$  | 1            | 1060 $\mu$ | 0.06         |
| 40 $\mu$   | 1.04         | 750 $\mu$  | 0.88         | 1180       | 0.02         |
| 60 $\mu$   | 1.16         | 790 $\mu$  | 0.46         | 1500       | 0.20         |
| 90 $\mu$   | 1.24         | 820 $\mu$  | 0.14         | 1540       | 0.2          |
| 150 $\mu$  | 1.18         | 850 $\mu$  | -0.06        | 1560       | 0.4          |
| 170 $\mu$  | 1.14         | 920 $\mu$  | -0.18        | 1580       | 0.64         |
| 200 $\mu$  | 1.06         | 950 $\mu$  | -0.14        | 1600       | 0.84         |

Measured rise time = 101  $\mu$ s, measured overshoot = 31 %


- ✓ (c) Change the resistor in the circuit with another value, and record the values of rise time and overshoot.

You must make sure the output is underdamped.  $\gamma < 1$

$R_{exp} = 1.800 \text{ k}\Omega$ , rise time = 67  $\mu$ s, overshoot = 18 %

Please analyze whether the values of rise time and overshoot are reasonable based on  $R_{exp}$ .

$$\frac{0.18}{1}$$

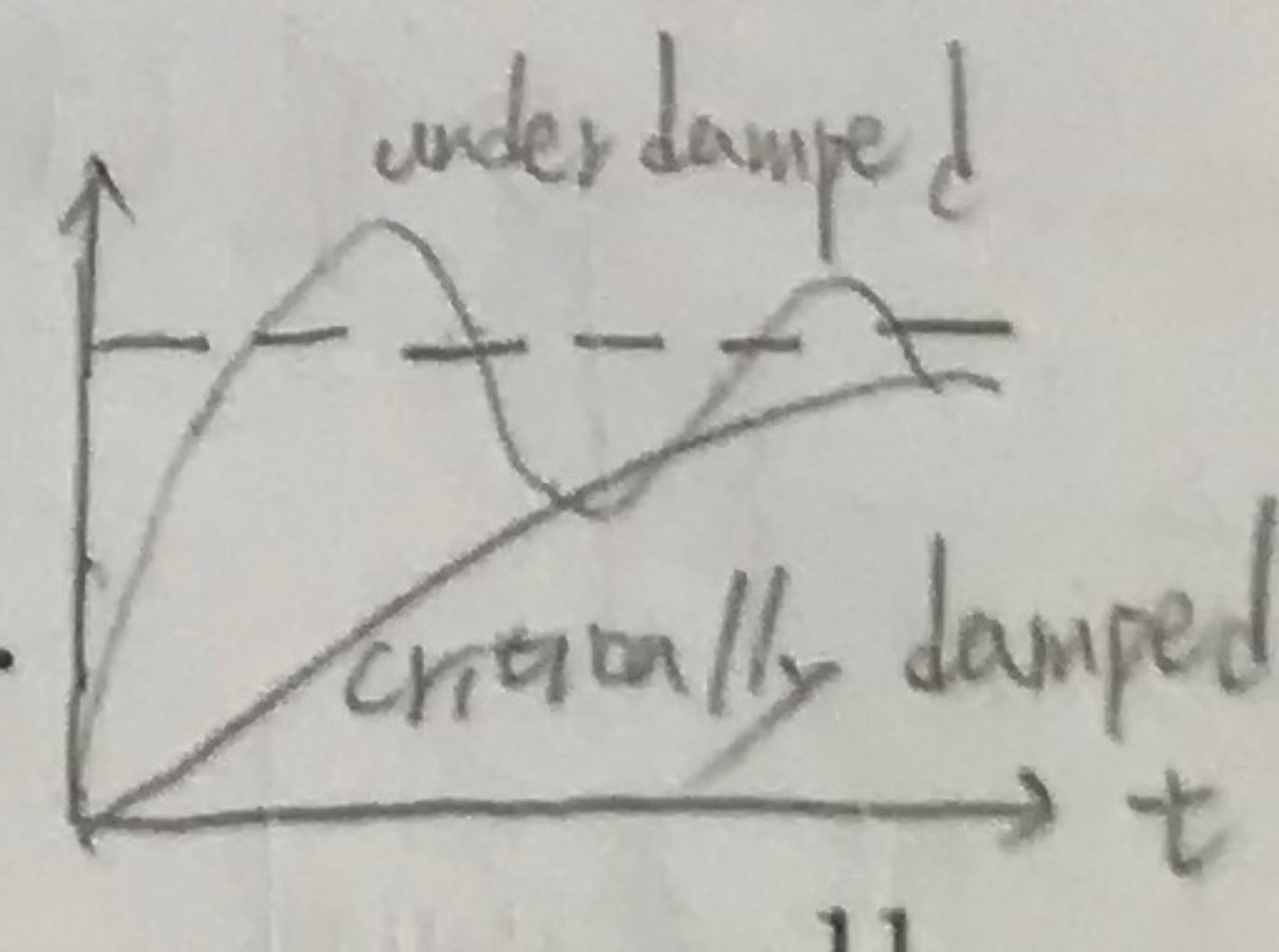

Analysis:

$$\gamma = \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{1800}{2} \times \sqrt{\frac{26.5 \times 10^{-9}}{100 \times 10^{-3}}} = 0.463$$

$$M_p = \exp\left(\frac{-\gamma}{\sqrt{1-\gamma^2}} T\right) = 19.37\%, \text{ Error is } \frac{19.37 - 18}{18} = 7.61\% \quad \left. \begin{array}{l} \text{Error is pretty,} \\ \text{small. The results} \end{array} \right\}$$

$$\omega_n = \frac{1}{\sqrt{LC}} = 19416 \text{ rad/s}, \quad \omega_d = \omega_n \sqrt{1-\gamma^2} = 17209.5$$

$$t_r = \frac{\tan^{-1}\left(\frac{\sqrt{1-\gamma^2}}{\gamma}\right)}{\omega_d} = 63.3 \text{ ns}, \text{ Error is } \frac{63.3 - 64}{64} = -1.09\% \quad \left. \begin{array}{l} \gamma=1 \\ \text{are precise!} \end{array} \right\}$$

- ✓ (d) Change the resistor in the circuit until you get a critically damped response (overshoot = 0). Record the resistor value and analyze whether resistor value is reasonable.

$$R_{exp} = 3.95 \Omega$$

Analysis:

$$\gamma = \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{R_{cal}}{2} \cdot \sqrt{\frac{26.5 \times 10^{-9}}{100 \times 10^{-3}}} = 1 \Rightarrow R_{cal} = 3882 \Omega$$

$$\text{Error} = \frac{3950 - 3882}{3882} = 1.75\%$$

**Question:** Please derive the step response of the RLC circuit in Fig. 4-2.

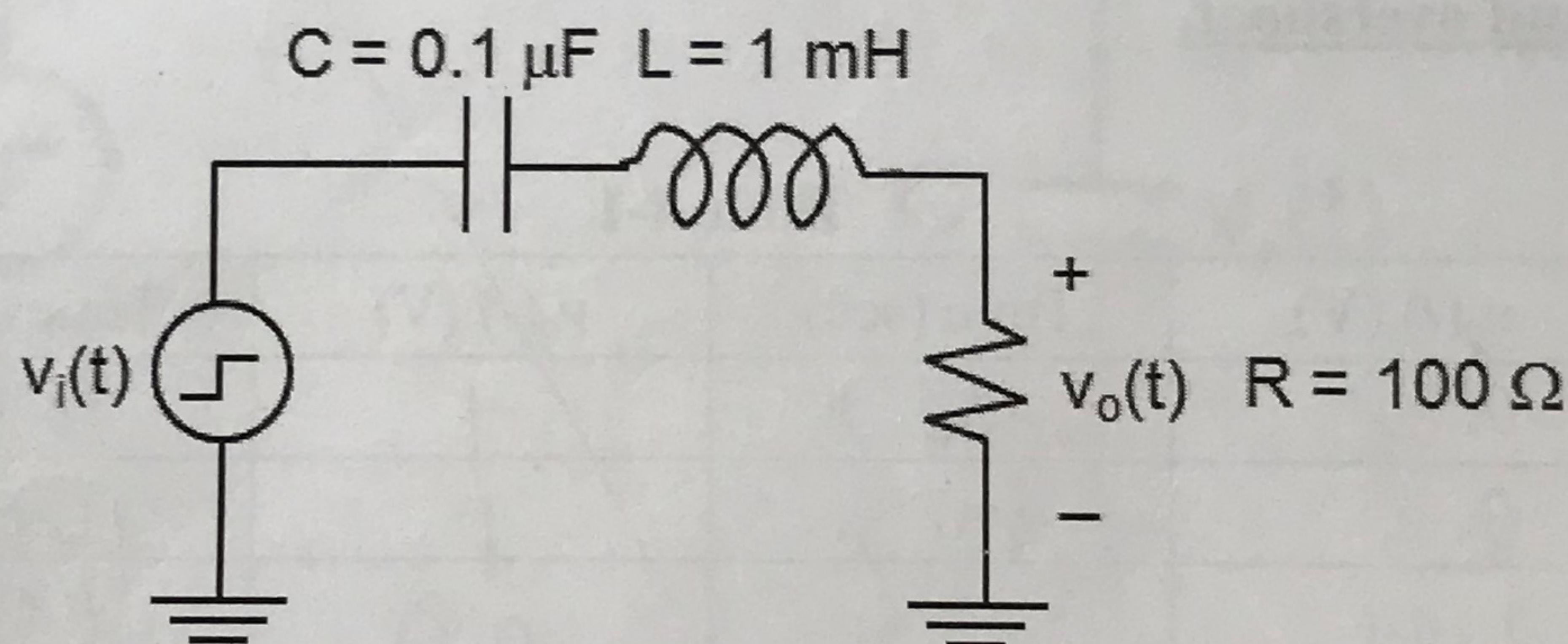


Figure 4-2

$$\text{Analysis: } V_o(s) = \frac{1}{s} \times \frac{R}{R + \frac{1}{sC} + sL} = \frac{R}{s^2L + sR + \frac{1}{C}} = \frac{R}{L} \cdot \frac{1}{s^2 + \frac{sR}{L} + \frac{1}{LC}}$$

$$= 10^5 \cdot \frac{1}{(s + \frac{50}{L})^2 + \frac{1}{LC} - (\frac{50}{L})^2} = 10^5 \cdot \frac{1}{\frac{1}{LC} - (\frac{50}{L})^2} \cdot \frac{\frac{1}{\frac{1}{LC} - (\frac{50}{L})^2}}{(s + \frac{50}{L})^2 + (\frac{1}{LC} - \frac{50}{L})^2}$$

$$\begin{aligned} & \Rightarrow V_o(t) = 10^5 \cdot \frac{1}{\frac{1}{LC} - (\frac{50}{L})^2} e^{-\frac{50}{L}t} \sin\left(\sqrt{\frac{1}{LC} - \left(\frac{50}{L}\right)^2} t\right) u(t) \\ & = \frac{1}{b} e^{at} \sin(bt) \cdot u(t) \\ & = 1.15 \times e^{-50000t} \cdot \sin(86602.5t) u(t) \end{aligned}$$