

EE 2245 Microelectronics Labs

Lab 3: Passive Filters

實驗室: 218 組別 _____ Names and ID Numbers: 吳俊毅 106061125

Objectives :

- (1) Become familiar with the characteristics of passive low-pass and high-pass filters.
- (2) Plot the phase response for low-pass and high-pass filters.
- (3) Analyze the frequency response of tuned band-pass and band-stop filters.
- (4) Become adept in the use of semilog graph paper.

Equipment Required :

Resistors: 300 Ω , 1 k Ω

Capacitors: 0.1 μF

Inductors: 10 mH

Instruments: Digital multimeter (DMM), digital oscilloscope, function generator.

注意：填寫實驗數據時如有『單位』請記得填入。在這個實驗你必須 demo low-pass filter 及 band-stop filter 的設計。

Procedure :

Part 1: Low-Pass R-C Filter Design

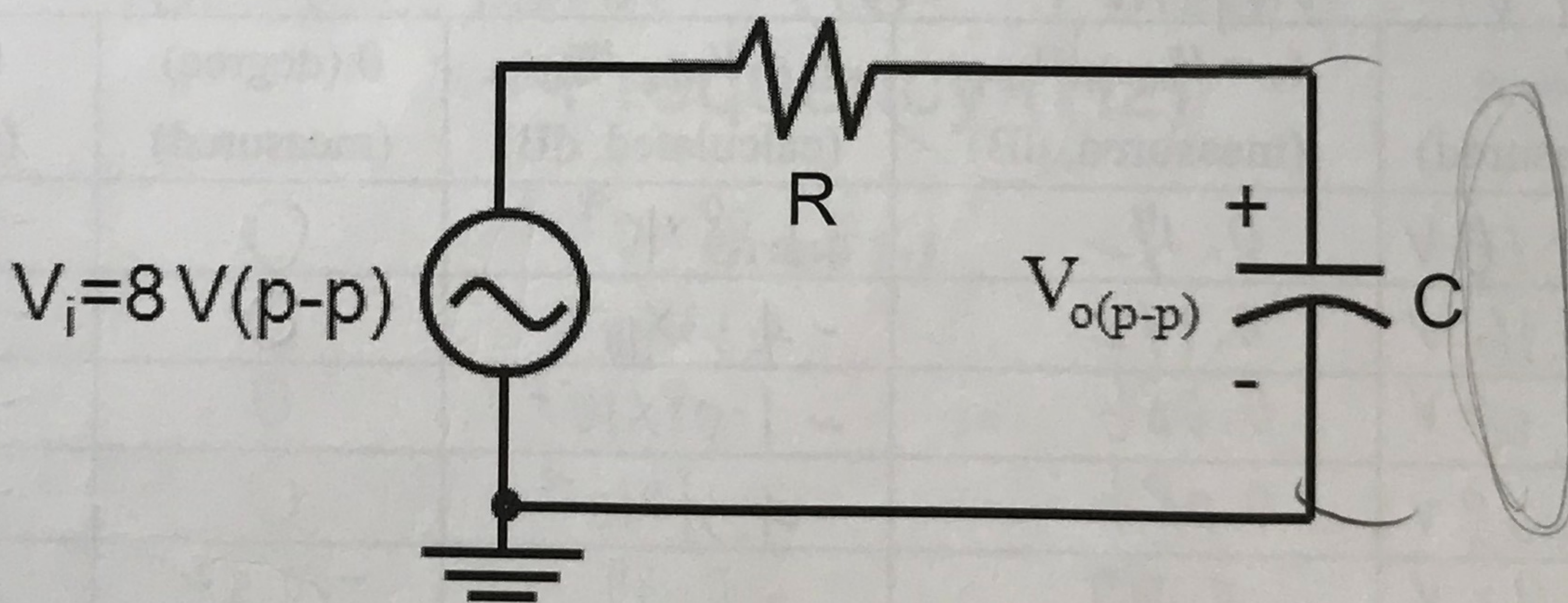


Figure 1-1

You are required to design a low-pass filter, as shown in Fig. 1-1, with a -3-dB frequency at 10 kHz (with tolerance of $\pm 2\%$, i.e. 9.8 – 10.2 kHz). Please demonstrate your result to a teaching assistant or the teacher.

- (a) Please show your analysis, and write down the resistor and capacitor values of your choice. Please also record the measured values.

Analysis:

(背面)

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sRC}$$

choose $R = 1.59k$
 $C = 10nF$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}} \text{ (-3 dB)} \therefore \omega RC = 1 \Rightarrow \omega = \frac{1}{RC}$$

$$\omega = \frac{1}{RC} = 2\pi f \Rightarrow RC = 1.59 \times 10^{-5}$$

$$R = 1.59k\Omega; C = 10nF$$

$$R_{measured} = 1.596k\Omega; C_{measured} = 9.98nF$$

(b) Write down the magnitude and phase of $V_o(j\omega)/V_i(j\omega)$ in terms of R and C.

Analysis: $s = j\omega$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sRC} = \frac{1}{1 + j\omega RC}$$

$$|V_o(j\omega)/V_i(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}; \angle(V_o(j\omega)/V_i(j\omega)) = -\tan^{-1}(\omega RC)$$

Note: For those of you who use a small resistor or a small capacitor in the circuit, you may not successfully get the desired gain or observe some undesired phenomena in the input.


(c) Please complete Table 1-1. The angle θ is the angle by which V_o leads the input voltage V_i . The sign of θ is minus when V_o lags the input voltage V_i . Please use the measured and calculated gains and phases in Table 1-1 to complete Graph 1-1 and 1-2.

Table 1-1 $20 \log |A_v|$ $\theta = \Delta t \cdot f \cdot 360^\circ$


Frequency (kHz)	$V_{o(p-p)}$ (measured)	$A_v = V_{o(p-p)}/V_{i(p-p)}$ (measured, dB)	$A_v = V_{o(p-p)}/V_{i(p-p)}$ (calculated, dB)	θ (degree) (measured)	θ (degree) (calculated)
0.05	8.16V	0.172	-1.08×10^4	0	-0.2862°
0.1	8.16V	0.172	-4.33×10^4	0	-0.572°
0.5	8.08V	0.086	-1.08×10^2	0	-2.859°
1.0	8.08V	0.086	-4.31×10^2	0	-5.705°
3.0	7.92V	-0.087	-0.37	-20.52°	-16.6839°
5.0	7.28V	-0.820	-0.96	-27°	-26.5427°
8.0	6.16V	-2.270	-2.145	-39.32°	-38.63°
8.5	6.04V	-2.441	-2.358	-42.13°	-40.33°
9	5.88V	-2.674	-2.573	-43.32°	-41.96°
9.5	5.76V	-2.853	-2.789	-43.6°	-43.50°
10	5.6V	-3.098	-3.006	-46.1°	-44.97°
10.5	5.48V	-3.286	-3.223	-47.3°	-46.37°
11	5.36V	-3.478	-3.439	-49.3°	-47.69°
20	3.64V	-6.839	-6.983	-60.48°	-63.41°

1.4 = X-95

40	2.16V	-11.37	-12.297	-72.6°	-75.95°
70	1.40V	-15.14	-16.981	-80.4°	-81.86°
100	1.04V	-17.72	-20.034	-86.5°	-84.283°
500	0.16V	-33.98	-33.97	-84.31°	-88.531°
1000	0.09V	-38.98	-39.99	-89.5°	-89.4265°

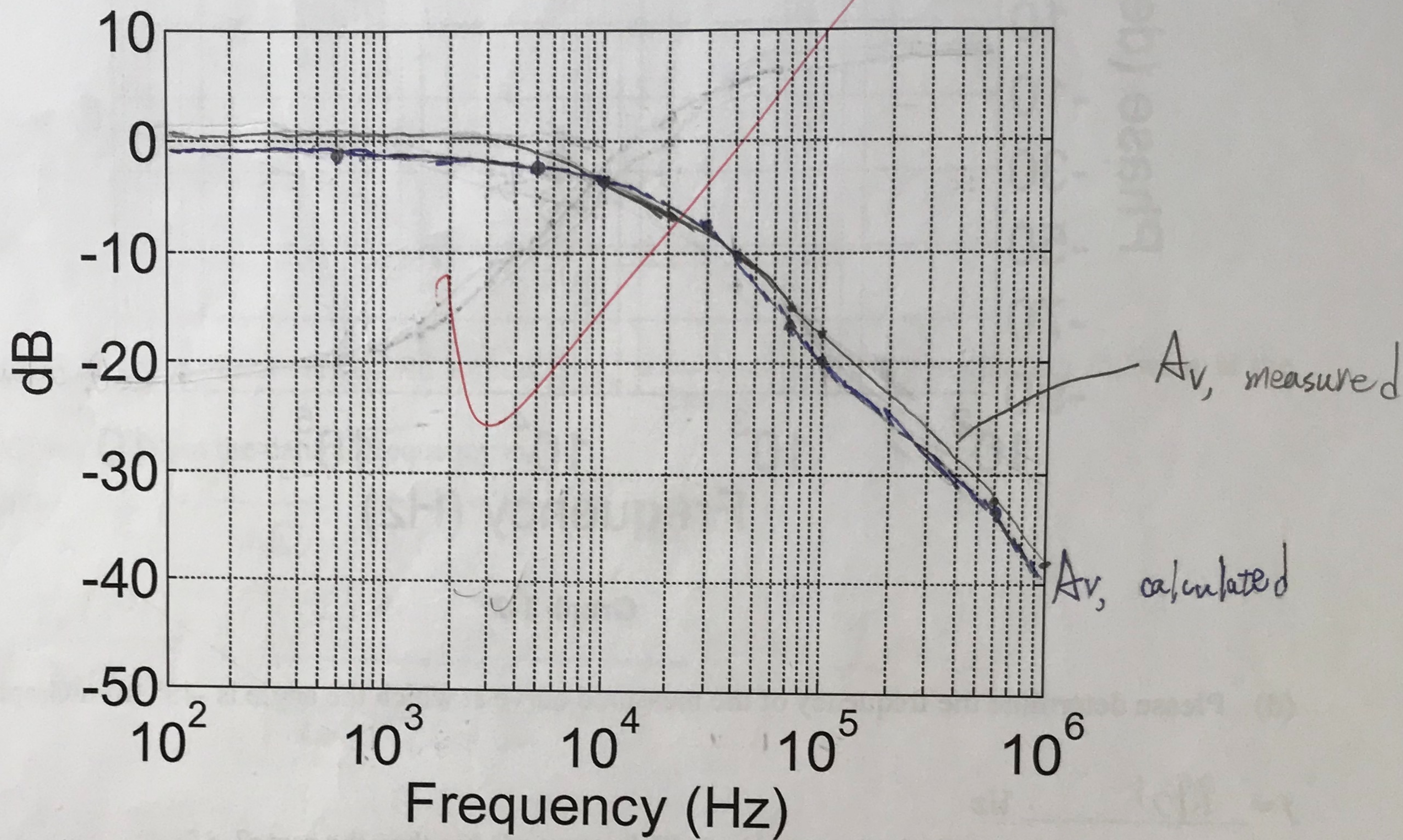

Graph 1-1

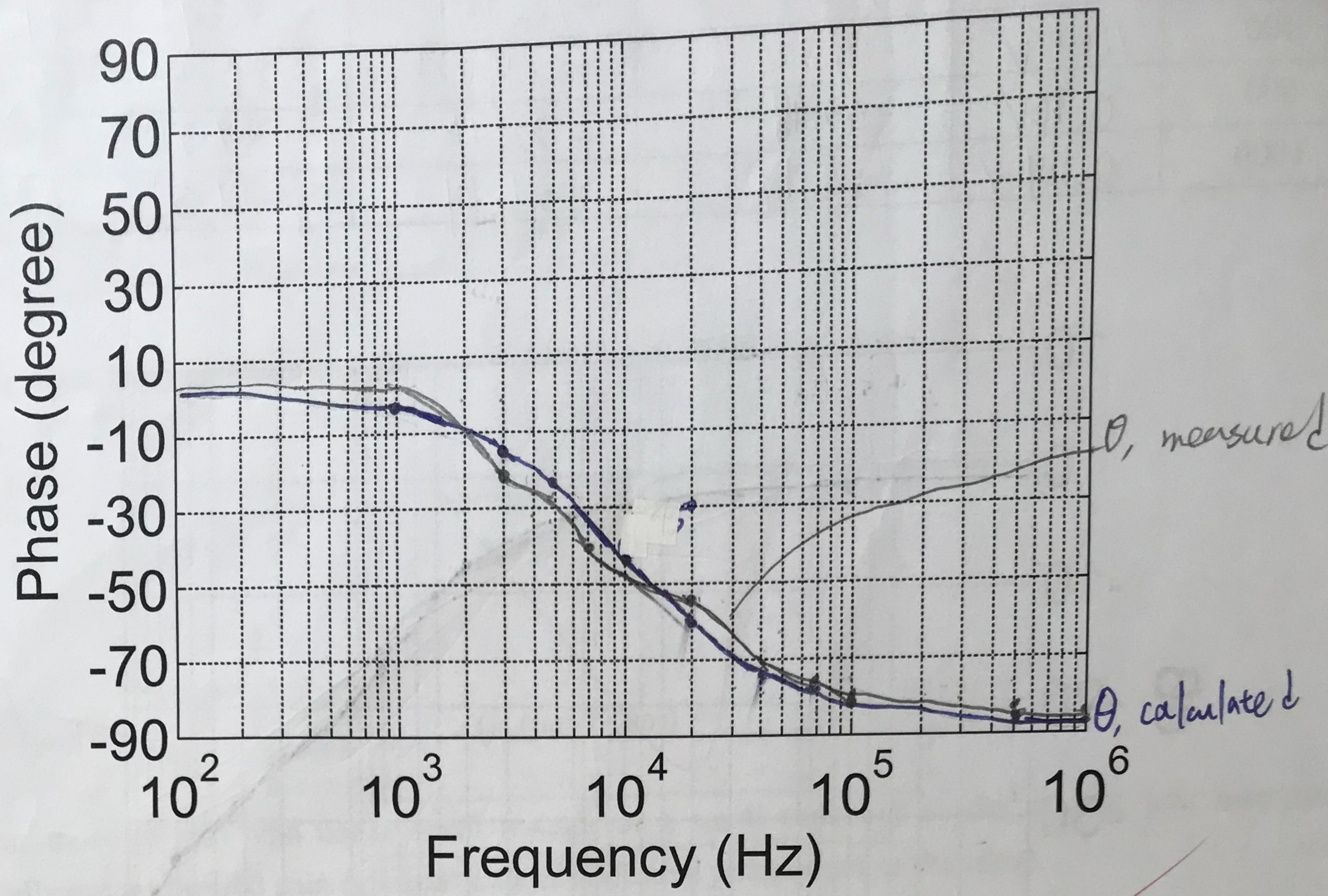

Graph 1-2

(d) Please determine the frequency of the measured curve at which the angle is -45° from Graph 1-2.

$f = \underline{9.73k}$ Hz

How does it compare with the measured -3-dB frequency? Are they the same?

Comment: $\text{Error} = \frac{9.73 - 10}{10} = 2.66\%$, They are pretty close!

Part 2: Band-Pass Filter

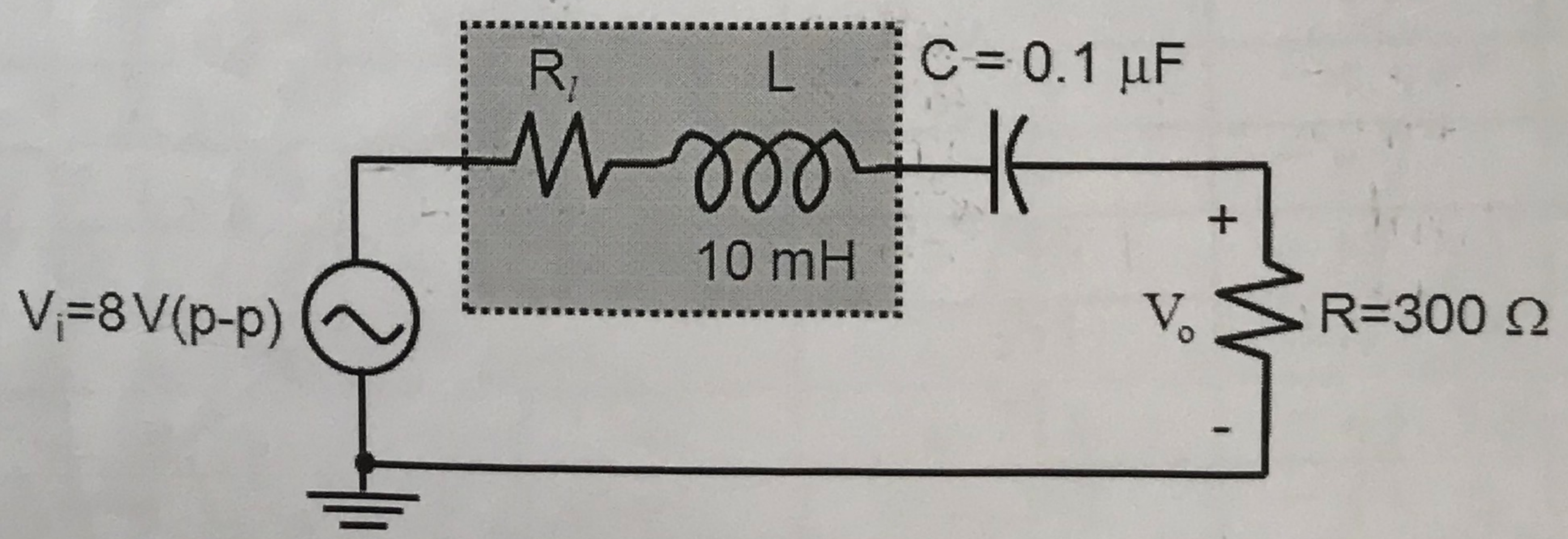


Figure 2-1

✓ (a) Construct the network of Fig. 2-1. Fill in the measured resistor value and R_i for the inductor.

$$R_{\text{measured}} = \underline{296 \Omega}, R_{l \text{ measured}} = \underline{85 \Omega}, L_{\text{measured}} = \underline{9.97 \text{ mH}}, C_{\text{measured}} = \underline{98.72 \text{ nF}}$$

(b) Write down the transfer function of $V_o(s)/V_i(s)$ without considering R_l . By replacing $s = j\omega$ into $V_o(s)/V_i(s)$, what is the dc gain (at $\omega = 0$) of $|V_o(j\omega)/V_i(j\omega)|$?

Calculation: $\frac{V_o(s)}{V_i(s)} = \frac{R}{R + sL + \frac{1}{sC}} = \frac{R}{s^2LC + sRC + R}$. $\omega \rightarrow 0, \frac{V_o(j\omega)}{V_i(j\omega)} \rightarrow 0$

$$V_o(s)/V_i(s) = \frac{sRC}{s^2LC + sRC + R}, |V_o(j\omega)/V_i(j\omega)|_{\omega=0} = \underline{0}$$

The natural frequency of the series LRC circuit is $f_n = \frac{1}{2\pi\sqrt{LC}}$ (Hz). By neglecting R_l , what is the gain of $|V_o(j\omega)/V_i(j\omega)|$ at the natural frequency ω_n ?

Calculation: $f_n = \frac{1}{2\pi\sqrt{LC}} \Rightarrow \omega_n = 2\pi f_n = \frac{1}{\sqrt{LC}}$

$$\frac{V_o(j\omega_n)}{V_i(j\omega_n)} = \left| \frac{j \frac{1}{\sqrt{LC}} RC}{-\frac{1}{LC} LC + j \frac{1}{\sqrt{LC}} RC + 1} \right| = \underline{1}$$

$$\sqrt{f_n} = \frac{1}{2\pi\sqrt{LC}} = \underline{5073.06} \text{ Hz}, |V_o(j\omega_n)/V_i(j\omega_n)| = \underline{1}$$

(c) Please calculate the ratio of V_o/V_i at the natural frequency using the measured resistor values (including that of the inductor). Please also calculate the gain at other frequencies listed in Table 2-1 and fill in the values.

Calculation: $H(j\omega) = \frac{R}{R + R_l + j\omega L + \frac{1}{j\omega C}} = \frac{j\omega RC}{j\omega RC + j\omega R_l C - \omega^2 LC + 1}$

$$\Rightarrow |H(j\omega)|_{\omega = \frac{1}{\sqrt{LC}}} = \left| \frac{RC}{RC + R_l C} \right| = \frac{R}{R + R_l} = \underline{0.776}$$

$$|V_o(j\omega_n)/V_i(j\omega_n)| = \underline{0.776}$$

(d) Energize the network of Fig. 2-1 and set the function generator to each of the frequencies appearing in Table 2-1. Make sure $V_i = 8 \text{ V}_{(p-p)}$ on the scope before you apply to the circuit. You may observe the loading effect of the $300\text{-}\Omega$ resistor at some frequencies such that V_i will not be $8 \text{ V}_{(p-p)}$, since the function generator has an impedance of $50 \text{ }\Omega$. Please complete Table 2-1.

(e) Plot the measured and calculated A_v vs. frequency on Graph 2-1. Find the maximum value of A_v and compare to the calculated value in part (c). Please comment accordingly.


$A_{v, \text{max}} = 0.719$ (✓)
 In theory, A_v is 0.776
 Comment: A_v has the maximum at $f = 5 \text{ kHz}$, A_v (measured) = 0.719 , A_v (calculated) = 0.781
 Errors are $\frac{0.719 - 0.776}{0.776} \approx -7\%$ and $\frac{0.781 - 0.776}{0.776} \approx 0.644\%$ respectively!

Table 2-1

Frequency (kHz)	$V_{o(p-p)}$ (measured)	$A_v = V_{o(p-p)} / V_{i(p-p)}$ (measured)	$A_v = V_{o(p-p)} / V_{i(p-p)}$ (calculated)	$V_{i(p-p)}$ (measured)
✓ 0.1	0.158 V	0.019	0.017	8.16
✓ 0.2	0.308 V	0.037	0.035	8.16
✓ 0.4	0.6 V	0.073	0.070	8.16
✓ 0.6	0.896 V	0.111	0.106	8.08
✓ 0.8	1.17 V	0.143	0.142	8.16
✓ 1.0	1.45 V	0.179	0.178	8.08
✓ 1.2	1.76 V	0.218	0.215	8.08
✓ 1.4	2.00 V	0.248	0.252	8.08
✓ 1.6	2.26 V	0.283	0.290	8
✓ 1.8	2.50 V	0.313	0.328	8
✓ 2.0	2.72 V	0.343	0.366	7.92
✓ 3.0	4.14 V	0.539	0.558	7.68
✓ 4.0	4.99 V	0.672	0.714	7.44
✓ 5.0	5.29 V	0.719	0.781	7.36
✓ 6.0	5.44 V	0.708	0.758	7.68
✓ 8.0	4.64 V	0.598	0.620	7.76
✓ 10.0	3.88 V	0.490	0.498	7.92
✓ 12.0	3.32 V	0.411	0.411	8.08
✓ 14.0	2.88 V	0.353	0.350	8.16
✓ 16.0	2.56 V	0.314	0.304	8.16
✓ 18.0	2.28 V	0.277	0.269	8.24
✓ 20.0	2.08 V	0.252	0.241	8.24
40.0	1 V	0.120	0.119	8.32

60.0	0.64 V	0.077	0.079
100.0	0.38 V	0.046	0.047

8.32
8.32

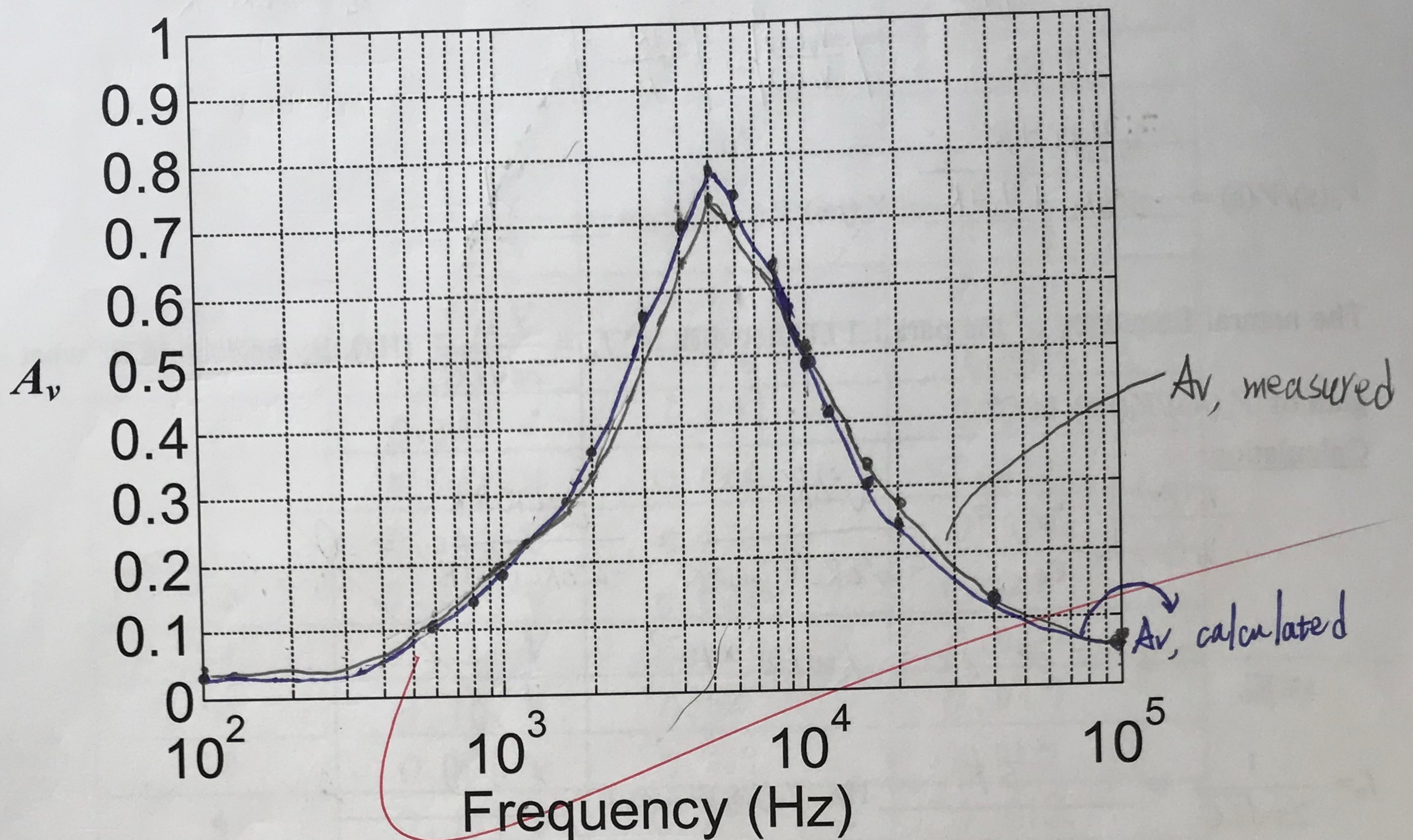

Graph 2-1

Part 3: Band-Stop Filter Design

You are required to design a band-stop filter, as shown in Fig. 3-1, with a band-stop frequency (with the lowest gain) at 5 kHz (with a tolerance of $\pm 10\%$; i.e. 4.5 – 5.5 kHz) and a corresponding gain less than -15 dB (i.e. 0.178) at that frequency. Please demonstrate your result to a teaching assistant or the teacher.

$\frac{0.05}{8}$

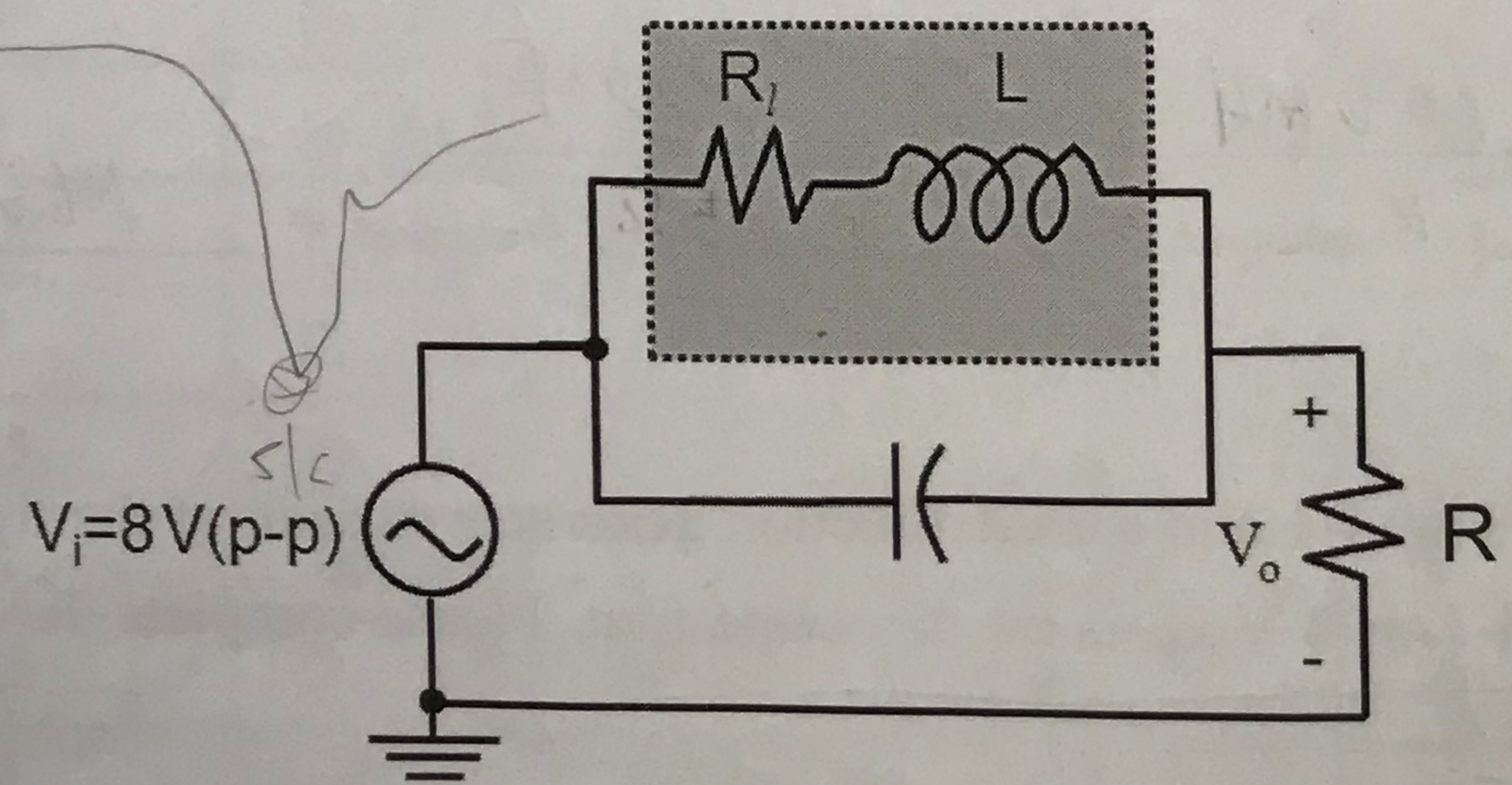


Figure 3-1

(a) Write down the transfer function of $V_o(s)/V_i(s)$ without considering R_l . By replacing $s = j\omega$ into $V_o(s)/V_i(s)$, what is the dc gain (at $\omega = 0$) of $|V_o(j\omega)/V_i(j\omega)|$?

Calculation:
$$\frac{V_o(s)}{V_i(s)} = \frac{R}{\frac{1}{sL} + R} = \frac{R}{\frac{1}{sL} + \frac{R}{1}} = \frac{sLR + R}{sL + s^2LR + R}$$

$$\left| \frac{V_o(s)}{V_i(s)} \right| = \left| \frac{R}{R} \right| = 1$$

$$V_o(s)/V_i(s) = \frac{s^2LR + R}{sL + s^2LR + R}, |V_o(j\omega)/V_i(j\omega)|_{\omega=0} = 1$$

The natural frequency of the parallel LC network is $f_n = \frac{1}{2\pi\sqrt{LC}}$ (Hz). By neglecting R_l , what is the gain of $|V_o(j\omega)/V_i(j\omega)|$ at f_n ?

Calculation:
$$\left. \frac{V_o(j\omega)}{V_i(j\omega)} \right|_{\omega = \frac{1}{\sqrt{LC}}} = \frac{-\omega^2LR + R}{-\omega^2LRC + j\omega L + R} = \frac{-\frac{1}{LC} \cdot LRC + R}{-\omega^2LRC + j\omega L + R} = 0$$

$$f = \frac{1}{2\pi\sqrt{LC}} = 5000 \Rightarrow LC = 1.013 \times 10^{-9}$$

$$f_n = \frac{1}{2\pi\sqrt{LC}} = 3k \text{ Hz}, |V_o(j\omega_n)/V_i(j\omega_n)| = 0$$

(b) By considering R_l , please determine the ratio $|V_o(j\omega_n)/V_i(j\omega_n)|$.

Calculation:
$$\frac{V_o(j\omega_n)}{V_i(j\omega_n)} = \frac{R}{(sL + R_l) \left(\frac{1}{sC} + R \right)} = \frac{R}{\frac{1}{sC} (sL + R_l) + R(sL + R_l) + R} = \frac{R(s^2LC + sR_lC + 1)}{(sL + R_l) + R(s^2LC + sR_lC + 1)}$$

$$\left| \frac{V_o(j\omega_n)}{V_i(j\omega_n)} \right| = \left(\frac{R^2 R_l^2 C^2}{R_l^2 + \frac{L}{C} + \frac{R^2 R_l^2 C}{L} + 2R R_l} \right)^{1/2}$$

$$\left| \frac{V_o(j\omega_n)}{V_i(j\omega_n)} \right| = \frac{L}{2C} (L^2 + 2R R_l C L + R^2 R_l^2 C^2)$$

(c) Please write down the inductor, capacitor, and resistor values of your choice, and the measured values.

$R = 100 \Omega, L = 100 \text{ mH}, C = 10.13 \text{ nF}$


$R_{\text{measured}} = 99 \Omega, R_l \text{ measured} = 304 \Omega, L_{\text{measured}} = 106.5 \text{ mH}, C_{\text{measured}} = 9.98 \text{ nF}$

(d) Energize the network of Fig. 3-1 and set the function generator to each of the frequencies appearing in Table 3-1. Make sure that $V_i = 8 \text{ V}_{(p-p)}$ is on the scope first. Please complete Table 3-1. R_l should be considered when calculating A_v .

(e) Plot the measured and calculated A_v vs. frequency on Graph 3-1.

✓ Table 3-1 ✓

Frequency (kHz)	$V_{o(p-p)}$ (measured)	$A_v = V_{o(p-p)}/V_{i(p-p)}$ (measured)	$A_v = V_{o(p-p)}/V_{i(p-p)}$ (calculated)
0.1	1.8 V	0.225	0.242
0.5	1.39 V	0.174	0.187
1.0	0.944 V	0.118	0.122
1.5	0.664 V	0.083	0.083
2	0.48 V	0.06	0.059
2.2	0.42 V	0.053	0.052
2.4	0.37 V	0.046	0.045
2.6	0.328 V	0.041	0.040
2.8	0.288 V	0.036	0.035
3	0.256 V	0.032	0.030
3.2	0.224 V	0.028	0.026
3.4	0.192 V	0.024	0.022
3.6	0.16 V	0.02	0.019
3.8	0.136 V	0.017	0.015
4	0.109 V	0.014	0.012
4.2	0.088 V	0.011	0.009
4.4	0.067 V	0.008	0.006
4.6	0.0528 V	0.007	0.005
4.8	0.046 V	0.006	0.003
5	0.052 V	0.006	0.003
5.2	0.062 V	0.008	0.005
5.4	0.078 V	0.01	0.008
5.6	0.090 V	0.011	0.009
5.8	0.104 V	0.013	0.011
6	0.119 V	0.015	0.013
6.5	0.16 V	0.02	0.018
7	0.196 V	0.025	0.022
7.5	0.232 V	0.029	0.027
8	0.268 V	0.034	0.031
8.5	0.298 V	0.037	0.035
9	0.33 V	0.041	0.039
10	0.404 V	0.051	0.047

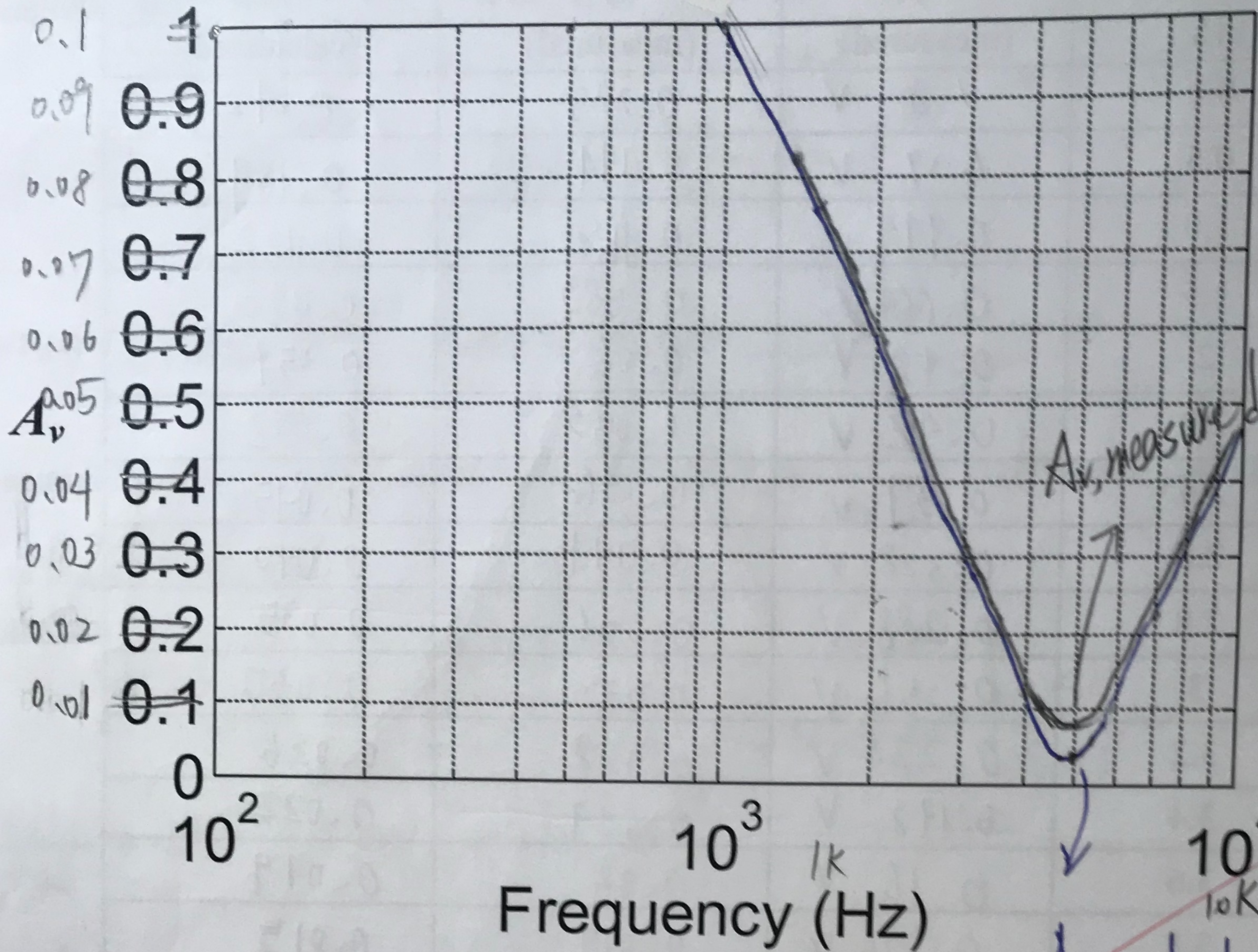

Graph 3-1

