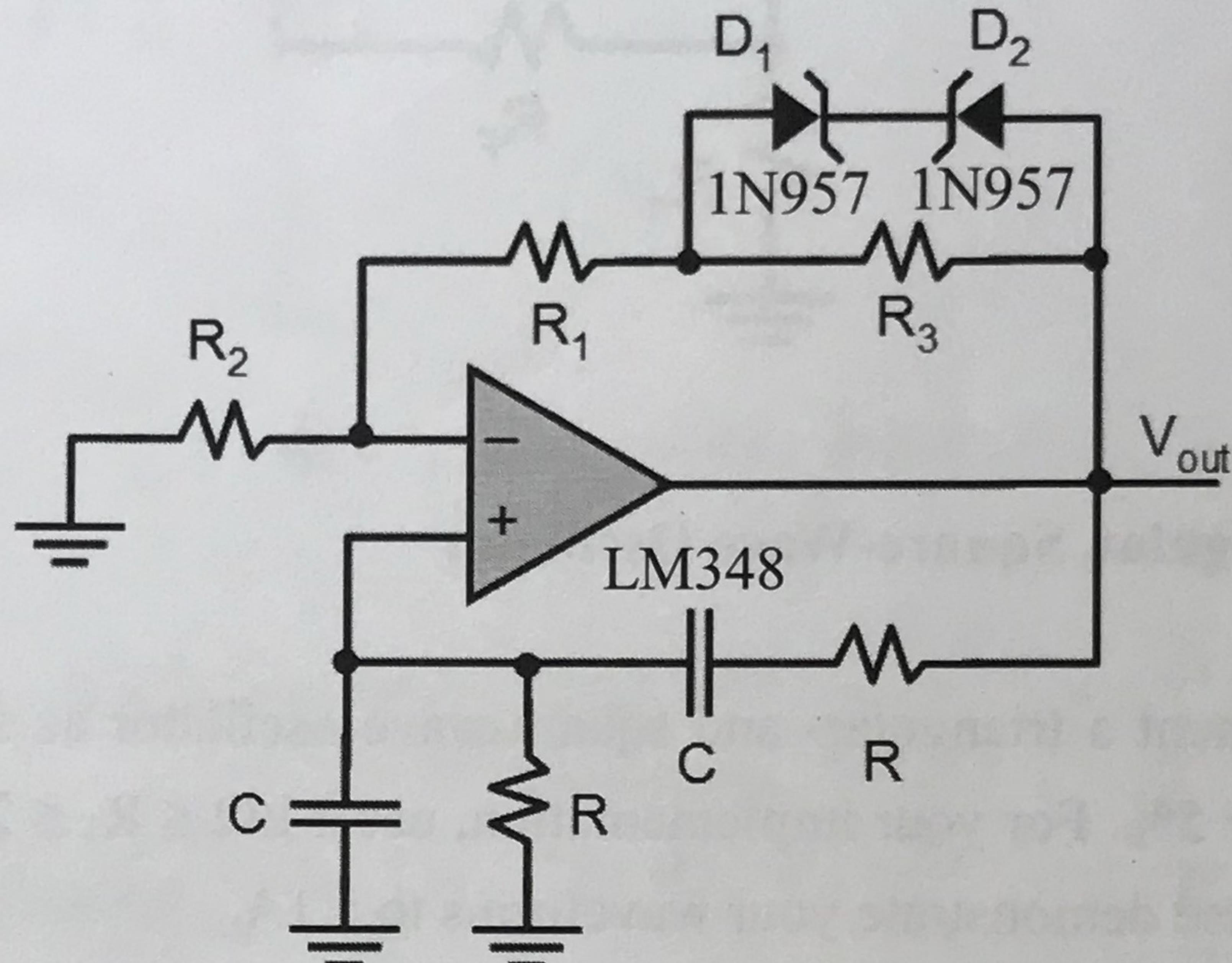


Lab 5: Oscillator Design

實驗室: 218 組別: _____ Names and ID Numbers: 106061125 吳俊毅

Design Problem I: The Wien-Bridge Oscillator

You are required to implement a Wien-bridge oscillator as shown with an oscillation frequency of 4 kHz and a tolerance of $\pm 5\%$. For your implementation, you can only use resistors with values from $1 \text{ k}\Omega$ to $40 \text{ k}\Omega$. Please show your waveform to a TA.



In the report, you need to provide:

- (1) Design procedure.
- (2) Values of passive elements used in the experiment.
- (3) The measured output waveform with some data points indicating the values.
- (4) Comments on the experimental result with respect to your calculation.


Design Problem II: The Relaxation Oscillator

You are required to implement a relaxation oscillator as shown with an oscillation frequency of 1 kHz and a tolerance of $\pm 5\%$. Before you implement the circuit, please show your calculation of the oscillation frequency to a TA (or me). For your implementation, you can only use resistors with values from $1 \text{ k}\Omega$ to $10 \text{ k}\Omega$. Please show your waveform to a TA.

In the report, you need to provide:

- (1) Design procedure.

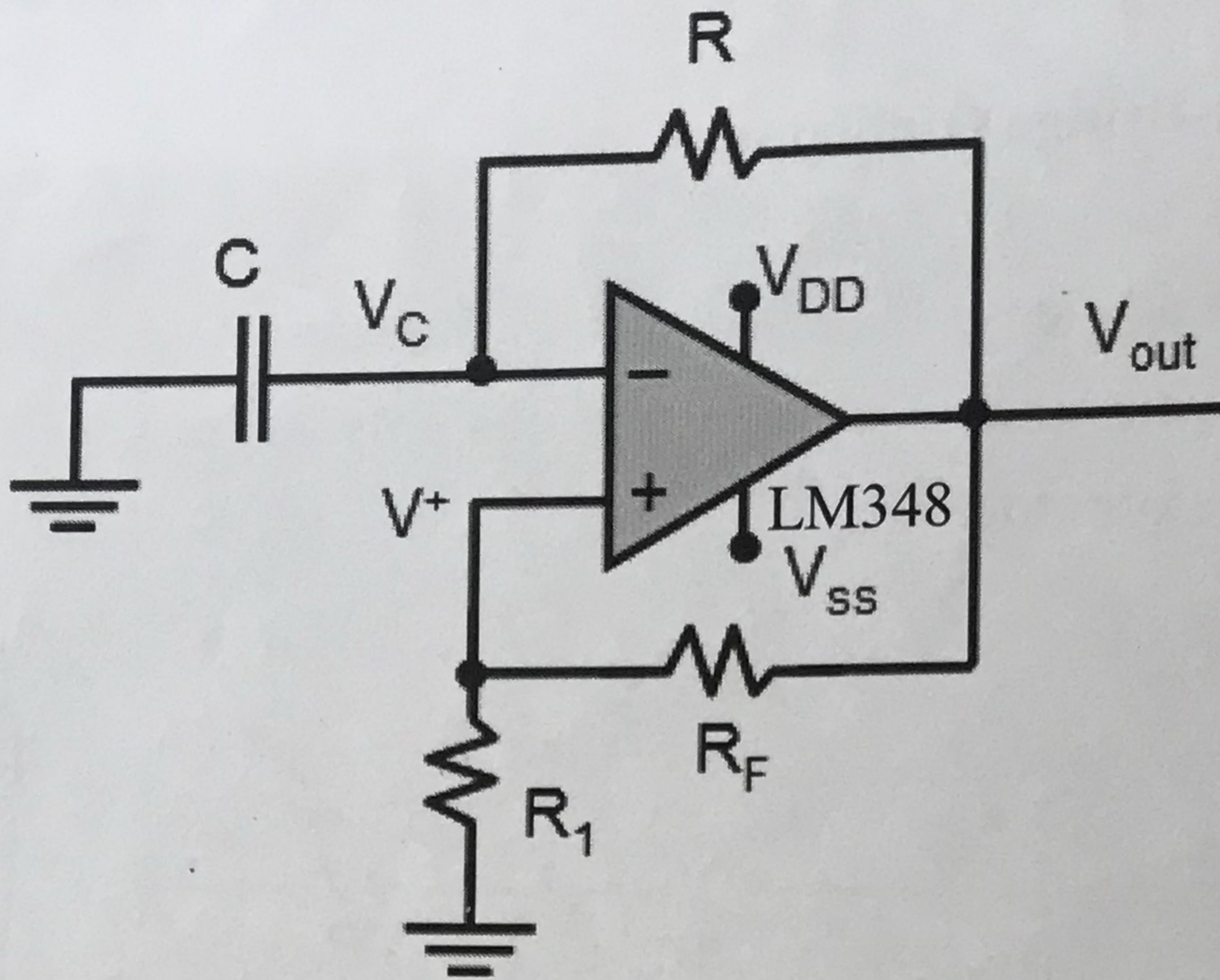- (2) Values of passive elements used in the experiment.
 (3) The measured waveforms of V_{out} and V_c with some data points indicating the values.
 (4) Comments on the experimental result with respect to your calculation.




Design Problem III: Triangular, Square-Wave Oscillator

You are required to implement a triangular- and square-wave oscillator as shown with a frequency of 800 Hz and a tolerance of $\pm 5\%$. For your implementation, use $1 \text{ k}\Omega \leq R_1 \leq 20 \text{ k}\Omega$, $1 \text{ k}\Omega \leq R_2 \leq 20 \text{ k}\Omega$, and $1 \text{ k}\Omega \leq R \leq 30 \text{ k}\Omega$. Please demonstrate your waveforms to a TA.


In the report, you need to provide:

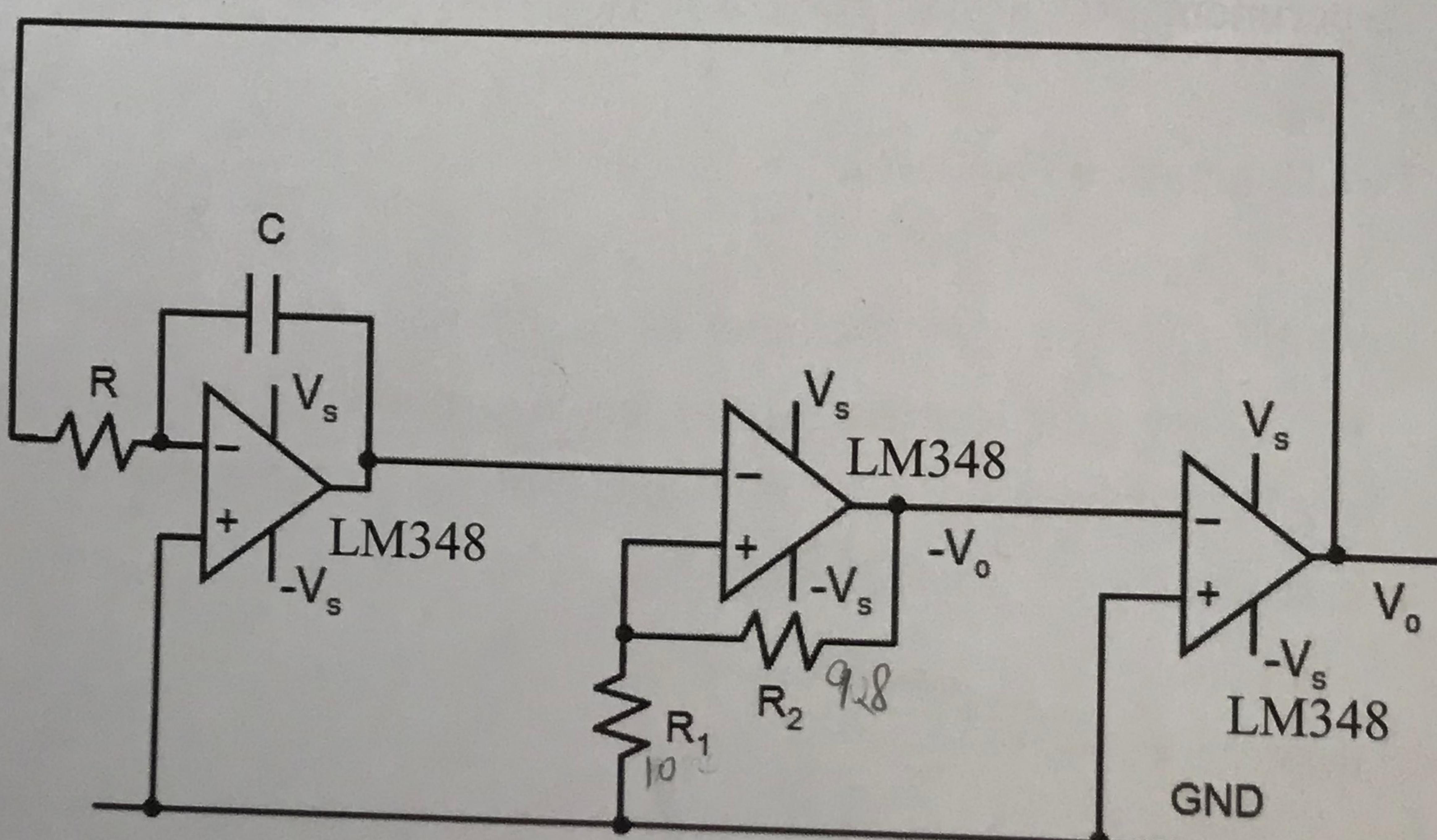- (1) Design procedure.
 (2) Values of passive elements used in the experiment.
 (3) The measured square and triangular waveforms with some data points indicating the values.
 (4) Comments on the experimental result with respect to your calculation.



Design Problem I

大设计

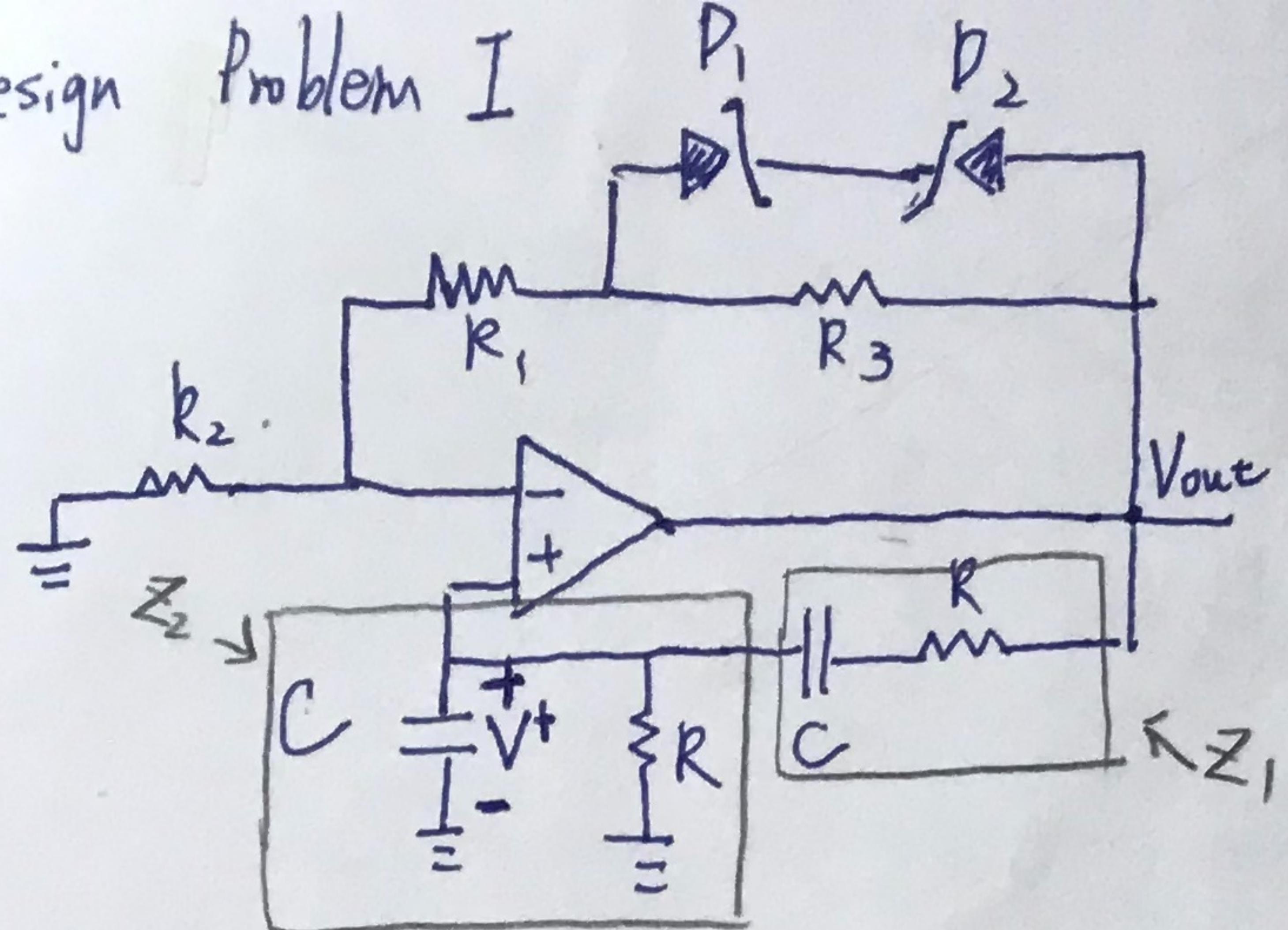


$$\frac{V^+(s)}{V_{\text{out}}(s)} = \frac{Z_2}{Z_1 + Z_2} = \frac{R'' \frac{1}{sC}}{(R + \frac{1}{sC}) + R'' \frac{1}{sC}}$$

$$= \frac{sRC}{RCs^2 + 3RCs + 1}$$

$$s = j\omega + j\lambda$$

$\frac{V^+(j\omega)}{V_{\text{out}}(j\omega)} = \frac{j\omega RC}{(1 - \omega^2 R^2 C^2) + j\omega 3RC}$, and the phase shift between V^+ & V_{out} must be zero to

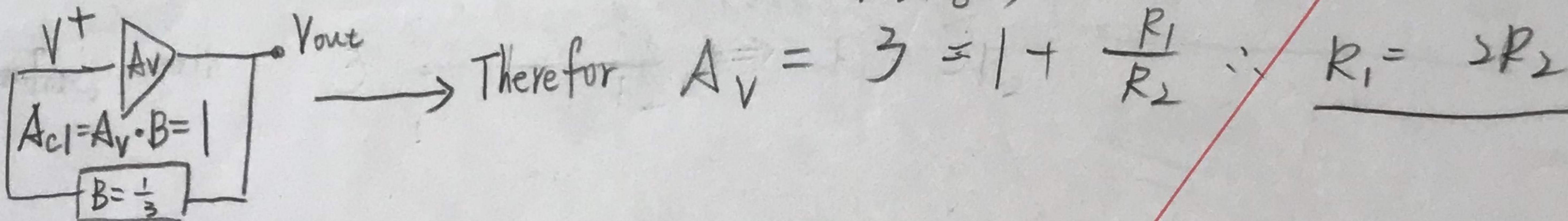produce oscillation. $\therefore 1 - \omega^2 R^2 C^2 = 0 \Rightarrow \omega = \frac{1}{RC}$ $\Rightarrow \frac{V^+(j\omega)}{V_{\text{out}}(j\omega)} = \frac{j\omega RC}{j\omega 3RC} = \frac{1}{3}$



(2) To get $f = 4 \text{ kHz} = \frac{1}{2\pi RC}$, and $R_1 = R_2$

	R_1	R_2	R_3	R	C	C
calculated value	$20k\Omega$	$10k\Omega$	$1k\Omega$	$20k\Omega$	$20k\Omega$	$2nF$
measured value	$20.074k\Omega$	$9.91k\Omega$	$1.002k\Omega$	$20.85k\Omega$	$19.96k\Omega$	$1.96nF$

(4)



由於 R 取的比理論值大一點，
 $\because A_v$ 太大造成 V_{out} 大過於 V_{DD}
 造成波峰會有平的部分
 measured frequency = 3.925 kHz

$$\text{Error rate} = \frac{3.925 - 4}{4} = -1.875\%$$

The error rate is pretty small!

3) waveform 附在最後一頁

Design Problem II:

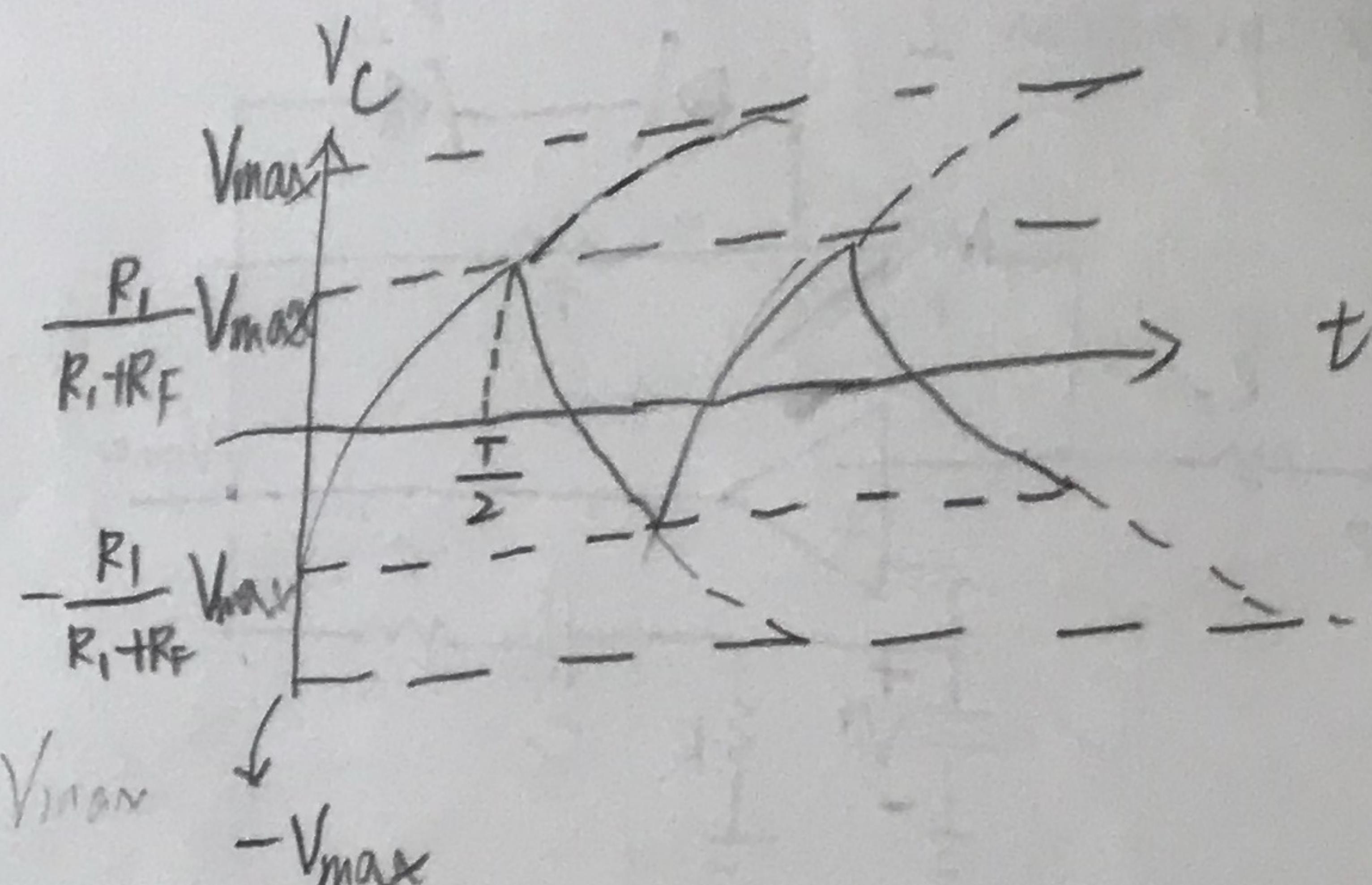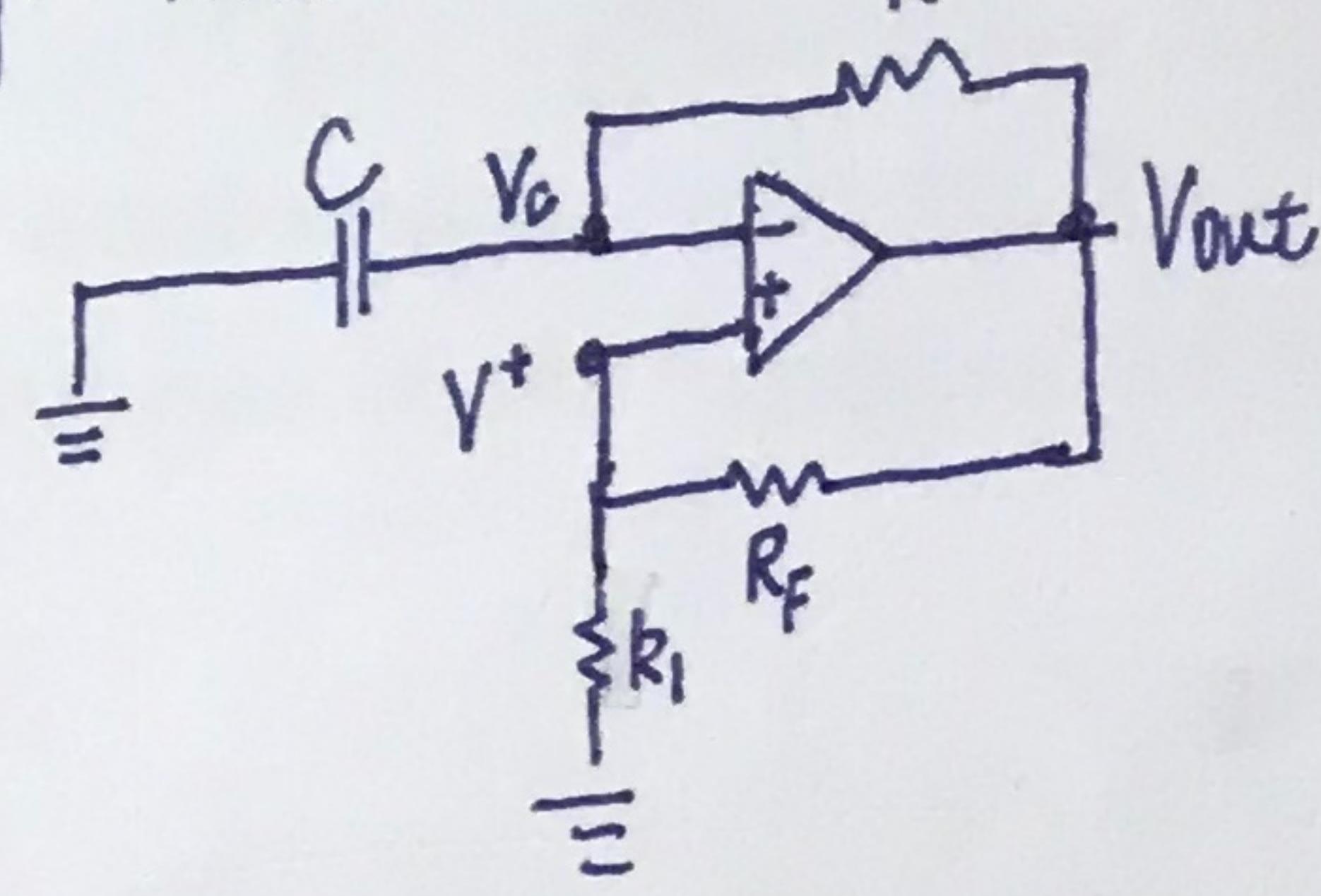

* (1)

$$\frac{V_{out} - V_c}{R} = C \frac{dV_c}{dt}$$

$$\Rightarrow \frac{dt}{RC} = \frac{dV_c}{V_{out} - V_c}$$

$$\Rightarrow \frac{-t}{RC} \Big|_{t=0}^t = -\ln(V_{out} - V_c) \quad \left| \begin{array}{l} V_c(t) \\ V_c(0) \end{array} \right.$$

$$\Rightarrow \frac{-t}{RC} = \ln \left(\frac{V_{out} - V_c(t)}{V_{out} - V_c(0)} \right)$$

$$\Rightarrow e^{-\frac{t}{RC}} = \frac{V_{out} - V_c(t)}{V_{out} + \frac{R_1}{R_1 + R_F} V_{out}}$$

$$V_c(\frac{T}{2}) = \frac{R_1}{R_1 + R_F} V_{max} = V_{out}$$

$$\Rightarrow e^{-\frac{T}{2RC}} = \frac{\frac{R_1}{R_1 + R_F} V_{out}}{V_{out} + \frac{R_1}{R_1 + R_F} V_{out}} = \frac{\frac{R_1}{R_1 + R_F} V_{out}}{2V_{out} + \frac{R_1}{R_1 + R_F} V_{out}}$$

$$\Rightarrow \frac{-T}{2RC} = \ln \left(\frac{\frac{R_1}{R_1 + R_F} V_{out}}{2V_{out} + \frac{R_1}{R_1 + R_F} V_{out}} \right) \Rightarrow T = -2RC \cdot \ln \left(\frac{\frac{R_1}{R_1 + R_F} V_{out}}{2V_{out} + \frac{R_1}{R_1 + R_F} V_{out}} \right)$$

$$\Rightarrow f_o = \frac{1}{T} = \frac{1}{2RC \ln \left(1 + \frac{2R_1}{R_1 + R_F} \right)} = 1 \text{ kHz}$$

Assume $R_1 = R_F = 2 \text{ k}\Omega$

$$\Rightarrow f_o = \frac{1}{2RC \ln(3)} = 1 \text{ kHz} \Rightarrow RC = 9.5512 \times 10^{-4}$$

(2)

	R	C	R_1	R_F
selected value	4551.252	100nF	2kΩ	2kΩ
measured value	4.67kΩ	102.5nF	1.98kΩ	1.99kΩ

(3) Waveform 在最後一頁

$$(4) V_c / \text{measured frequency} = 988.1 \text{ Hz} \quad (V_c)$$



$$\text{Error rate} = \frac{988.1 - 1000}{1000} = -1.19\%$$

$$V_{out} : \text{measured frequency} = 989.4 \text{ Hz}$$

$$\text{Error rate} = \frac{989.4 - 1000}{1000} = -1.06\%$$

誤差可能來自導線、儀器微量的寄生電阻

Design Problem III

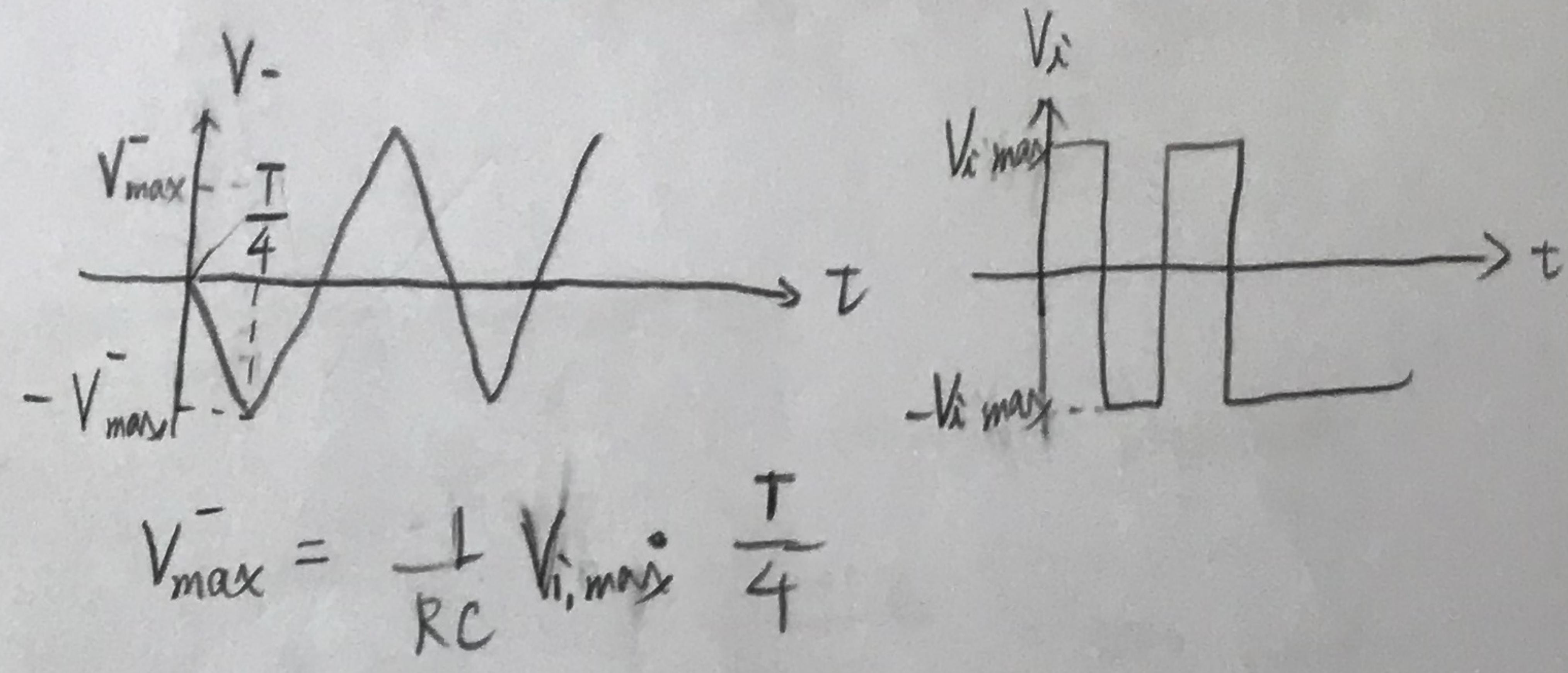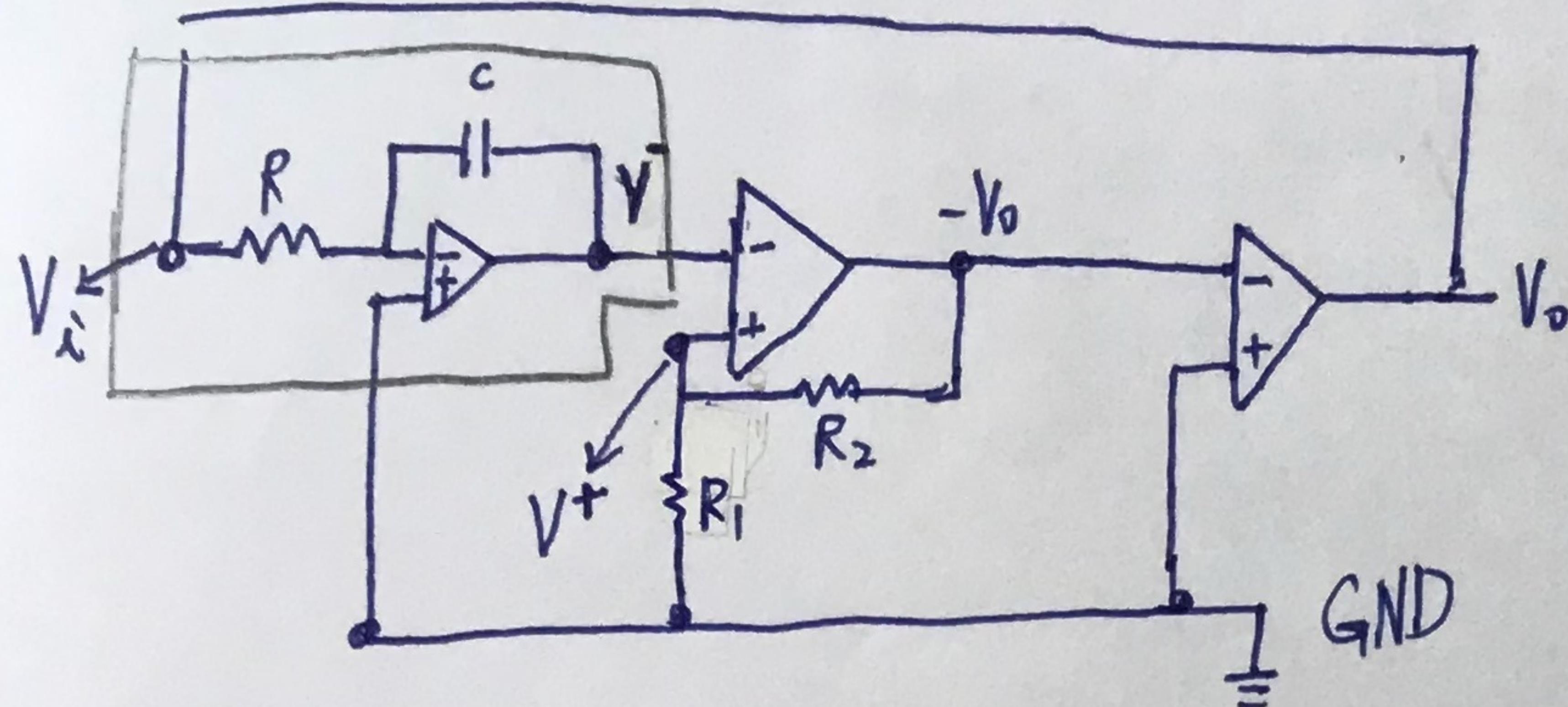

1)

$$\frac{\bar{V}(s)}{V_i(s)} = -\frac{1}{sRC}$$

$$\Rightarrow \bar{V}(t) = \int_0^t \frac{-1}{RC} V_i(dt)$$

$$= \frac{-1}{RC} V_i t$$

$$\text{振幅} = \left| \frac{1}{2} V_{i,max} \right| \text{才能比較}$$

Schmitt Trigger: $\because R_1 = R_2 \Rightarrow V^+ = \frac{-1}{2} V_o \Rightarrow V^- \text{ 振幅} = \left| \frac{1}{2} V_{i,max} \right|$

$$\therefore \frac{T}{4} \times \frac{1}{RC} V_{i,max} = \frac{1}{2} V_{i,max} \Rightarrow RC = \frac{T}{2} \Rightarrow T = 2RC = \frac{1}{800} \Rightarrow RC = 6.25 \times 10^{-4}$$

2)

	Selected	Measured
R ₁	10kΩ	9.84kΩ
R ₂	10kΩ	10.05kΩ
R	6.25kΩ	6.26kΩ
C	0.1μF	60nF

(3)

waveform 附在最後一頁

(4)

Measured frequency = 821 Hz


$$\text{Error rate} = \frac{821 - 800}{800} = 2.625\%$$

Note that the value of measured C
is much less than its calculated value.

I think it's because the value of
measured R is larger than its calculate value,
 $RC = \text{constant}$ and there is some parasitic
resistance in wire.


Also, parasitic resistance may cause error on
measured frequency.

Design Problem 1

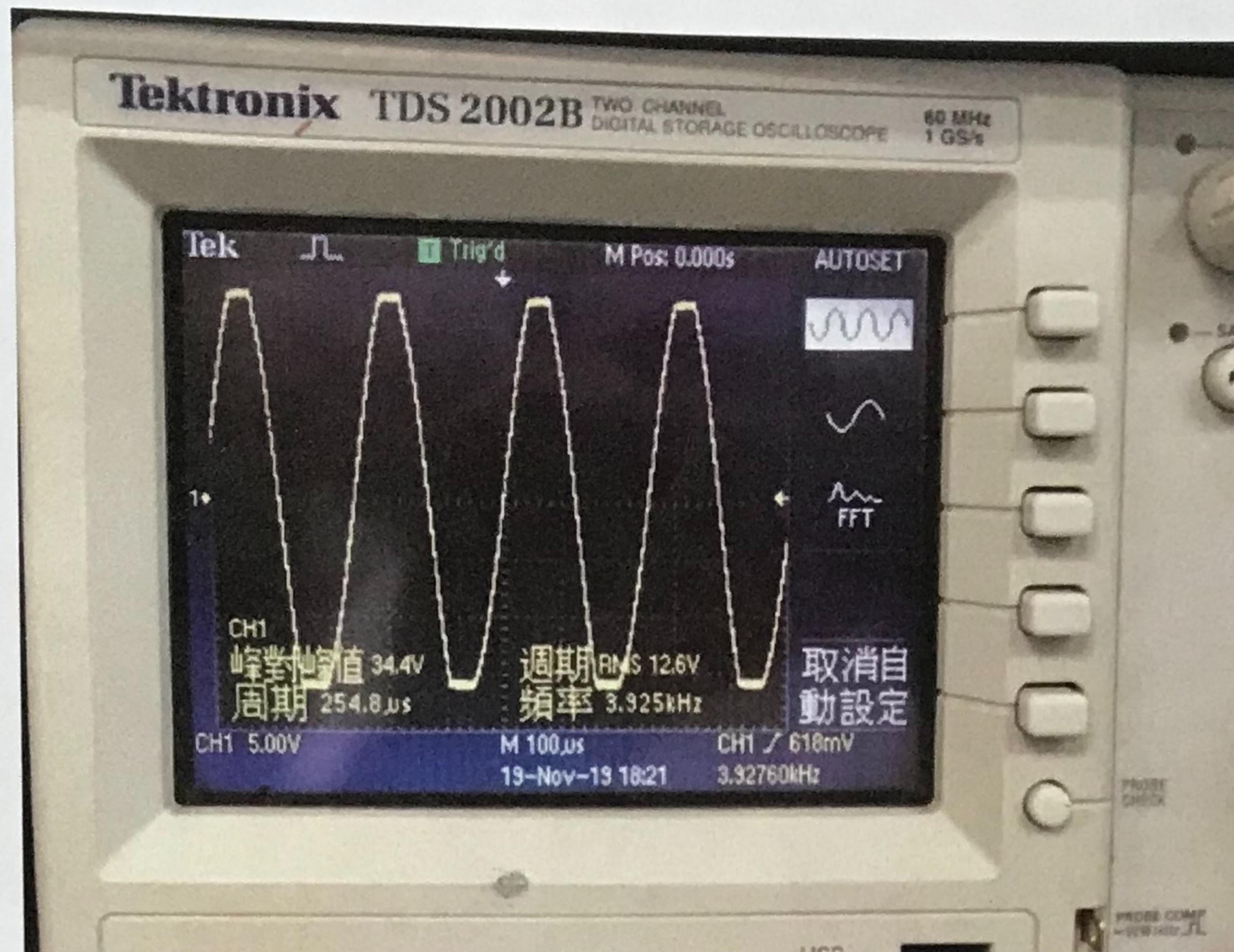


Design Problem 2

V_{out}

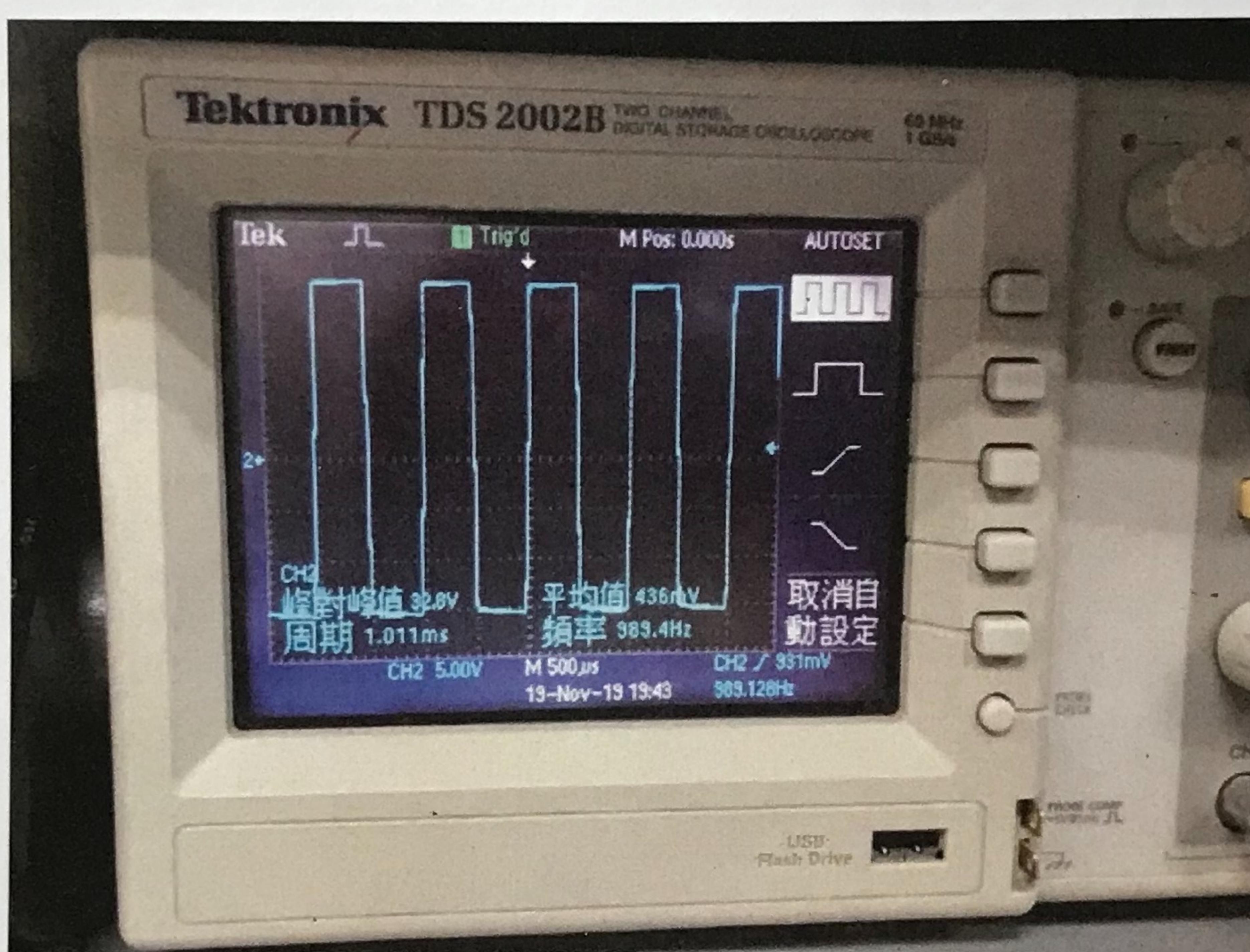


V_C

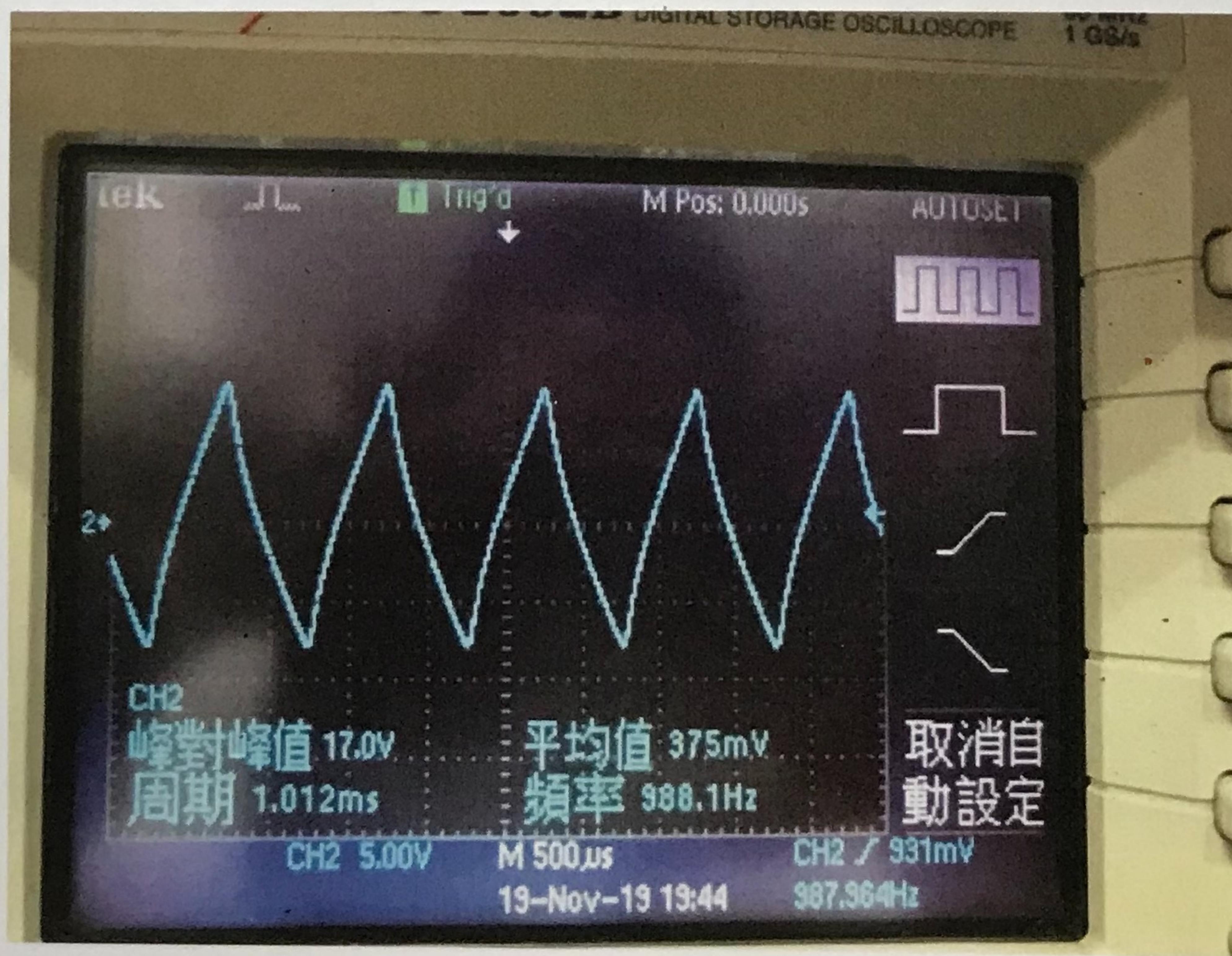

Design Problem 3

Integrator output

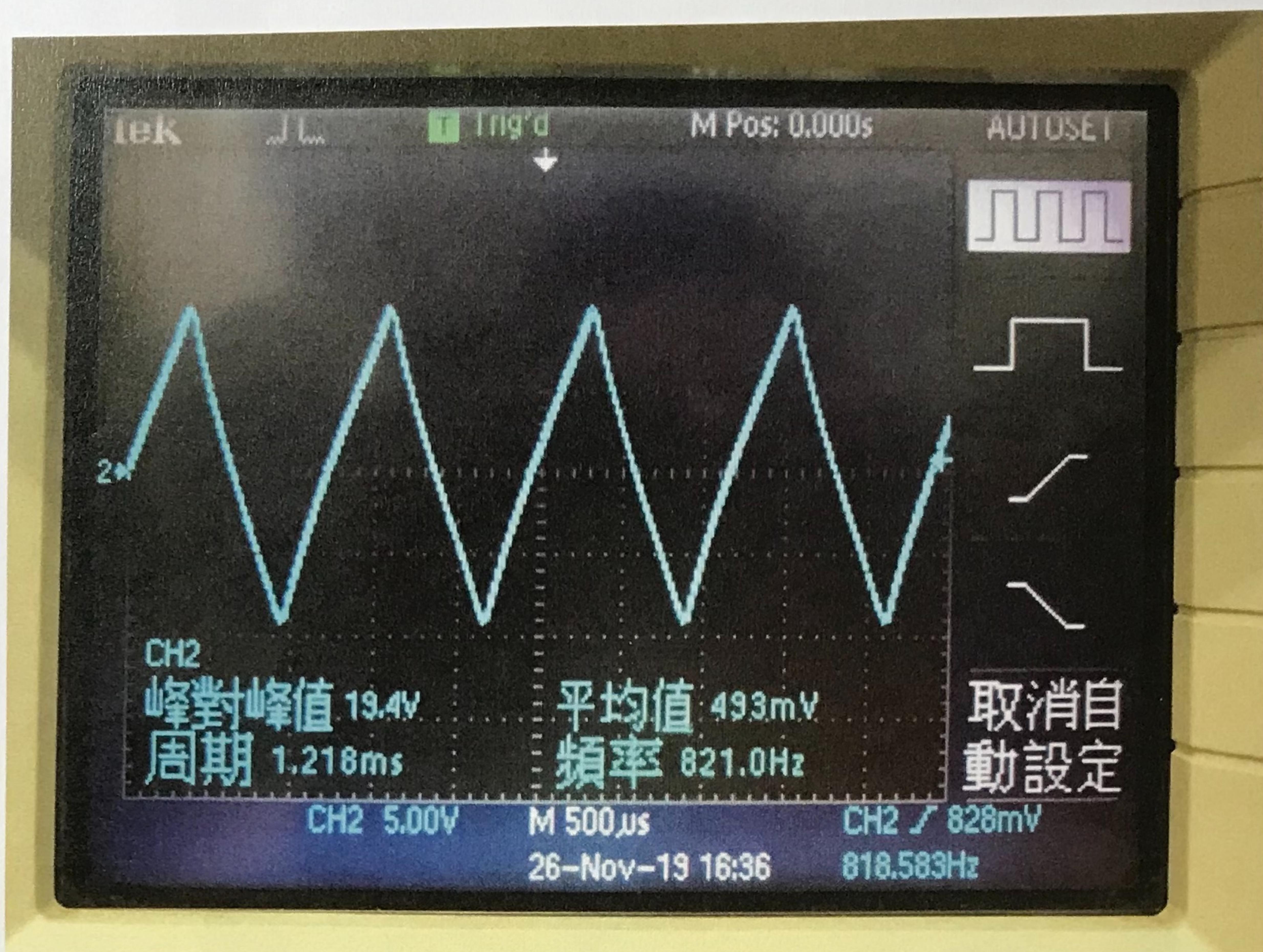

Blue curve is V_0 and yellow line is $-V_0$

