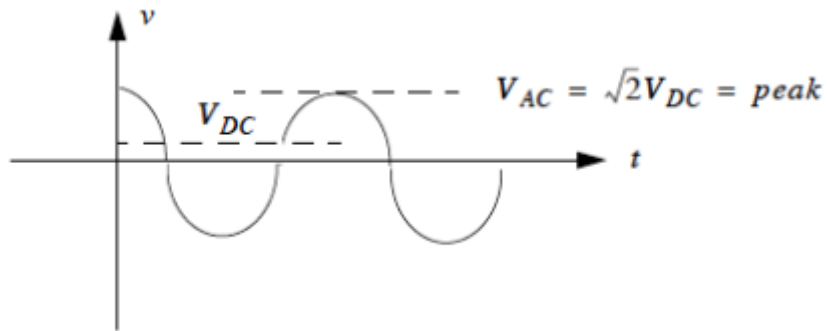


EE2210 Electric Circuits, Spring 2017
Practice Problems Solutions (Lecture1-Lecture3)

1.

Solution:



a) If peak voltage is V_{AC} , then

b)

$$V_{AC} = \sqrt{2}V_{DC}$$

Where V_{DC} is the average amplitude of the voltage signal.

$$\text{Average Power} = \frac{(V_{\text{average}})^2}{R} = \frac{V_{DC}^2}{R} = \frac{(V_{AC}/\sqrt{2})^2}{R} = \frac{V_{AC}^2}{2R}$$


c) If peak voltage is V_{AC} , then

$$V_{AC} = \sqrt{2}V_{DC}$$

Where V_{DC} is the average amplitude of the voltage signal.

ANS: (a) $V_{AC}^2/2R$ (b) $V_{AC} = \sqrt{2}V_{DC}$

2.

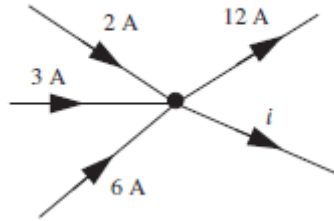

Solution:

KCL:

$$2\text{A} + 3\text{A} + 6\text{A} = 12\text{A} + i$$

$$i = -1\text{A}$$

ANS:

$$i = -1\text{A}$$

3.

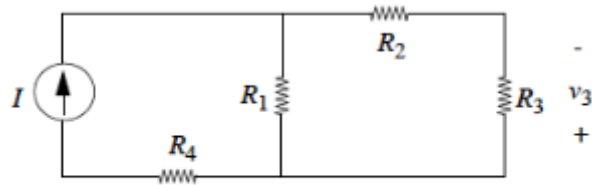


Figure 2.30:

Solution:

$$R_T = R_4 + \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3}$$

Voltage across current source is not zero. $V_T = I \times \left(R_4 + \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3} \right)$

Using voltage divider, $-v_3 = IR_T \times \frac{\frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3}}{R_T} \times \frac{R_3}{R_2 + R_3}$

$$v_3 = -I \times \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3} \times \frac{R_3}{R_2 + R_3}$$

ANS: $v_3 = -I \times \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3} \times \frac{R_3}{R_2 + R_3}$

4.

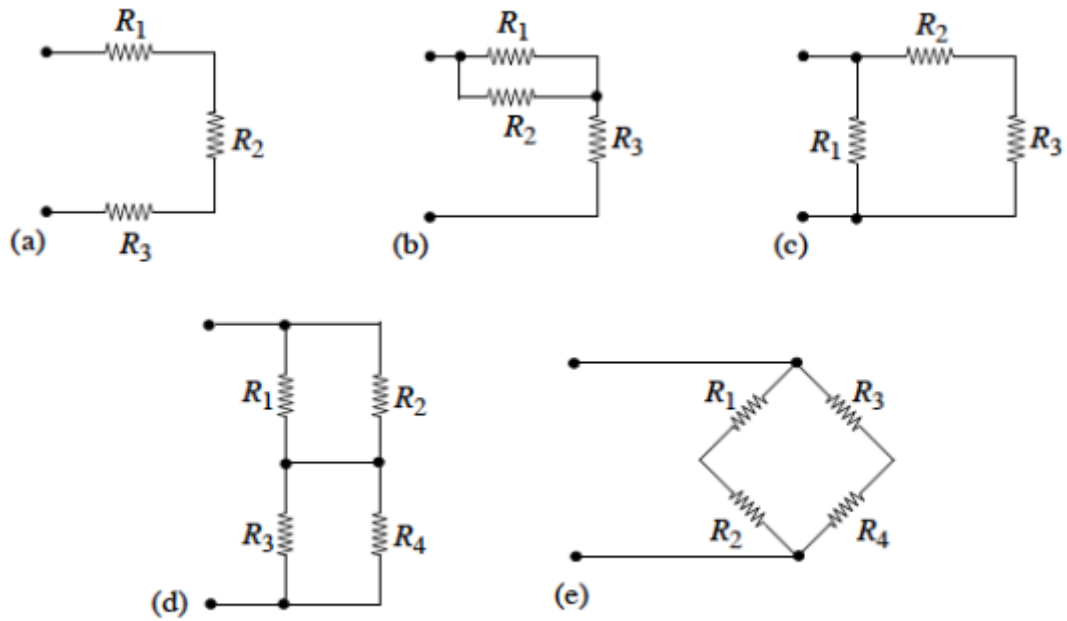


Figure 2.8:

Solution:

a)

$$R_{EQ} = R_1 + R_2 + R_3$$

b)

$$R_{EQ} = R_1 \parallel R_2 + R_3 = \frac{R_1 R_2 + R_3(R_1 + R_2)}{R_1 + R_2}$$

c)

$$R_{EQ} = R_1 \parallel R_2 + R_3 = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

d)

$$R_{EQ} = R_1 \parallel R_2 + R_3 \parallel R_4 = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4}$$

e)

$$R_{EQ} = (R_1 + R_2) \parallel (R_3 + R_4) = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$

5.

Solution:

The equivalent circuit resistance is 2Ω , so $\frac{3}{2}A$ of current is split between the 2Ω and 4Ω resistors. Therefore, $1A$ current goes through R .


Power = $2W$

ANS: Power = $2W$

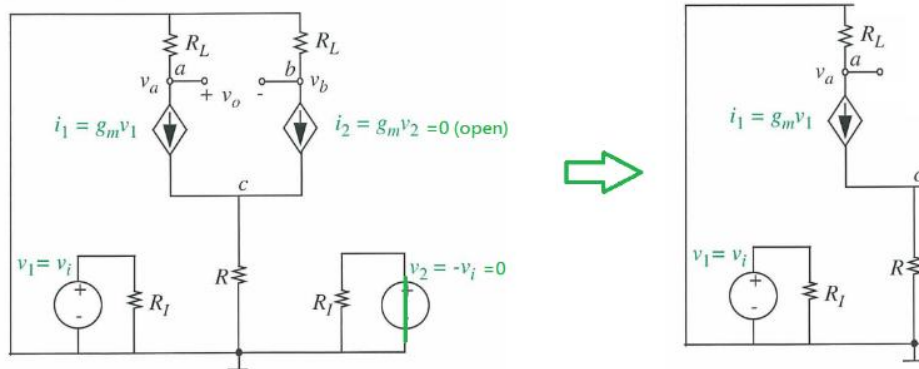6.

Solution:


By using superposition method, we can turn off V_2 first, which is given by



KCL at V_a node, we have

$$g_m V_i + \frac{V_a}{R_L} = 0 \rightarrow V_a = -g_m V_i R_L$$

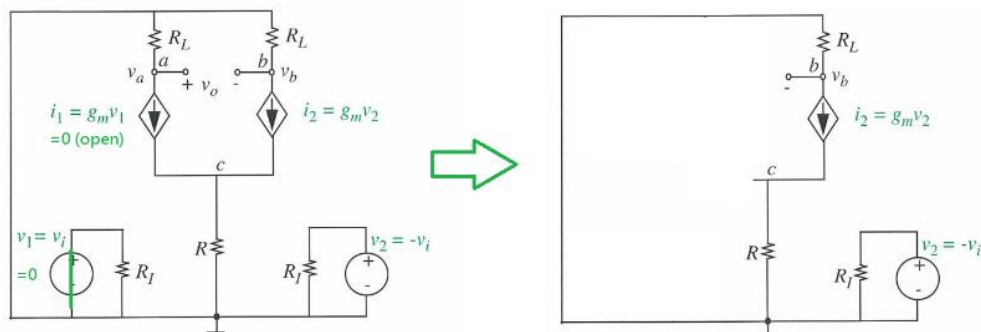Then we can turn off V_1 , which is given by



KCL at V_b node, we have


$$-g_m V_i + \frac{V_b}{R_L} = 0 \rightarrow V_b = g_m V_i R_L$$

Thus,

$$V_o = V_a - V_b = -2g_m V_i R_L$$

7.

Solution:

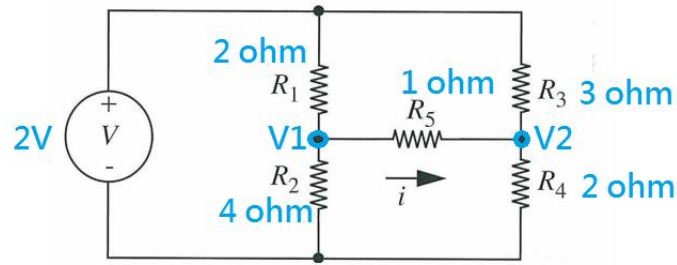

KCL at V1 node, we have

$$\frac{V_1 - 2}{2} + \frac{V_1 - V_2}{1} + \frac{V_1 - 0}{4} = 0$$

KCL at V2 node, we have

$$\frac{V_1 - 2}{3} + \frac{V_2 - V_1}{1} + \frac{V_2 - 0}{2} = 0$$


$$\rightarrow \begin{cases} V_1 = 1.13207 \text{ V} \\ V_2 = 0.9813 \text{ V} \end{cases}$$

Thus,

$$i = \frac{V_1 - V_2}{1} = 1.13207 - 0.9813 = 0.15094 \text{ A}$$

8.

Solution:

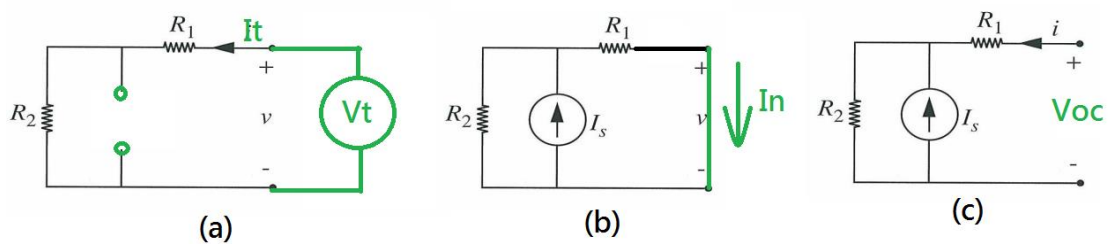

To find R_n & R_{Th} ($R_n = R_{Th}$), we need to turn off all the independent source and add a test voltage on the output node. $R_n = R_{Th} = \frac{V_t}{I_t}$. Please refer to figure (a).


$$R_n = R_{Th} = R_1 + R_2$$

We need to find out the short circuit current (I_n) for Norton equivalent. Please refer to figure (b).

$$I_N = I_S \frac{R_2}{R_1 + R_2}$$

And open circuit voltage for Thevenin equivalent. Please refer to figure (c).

$$V_{OC} = I_S R_2$$

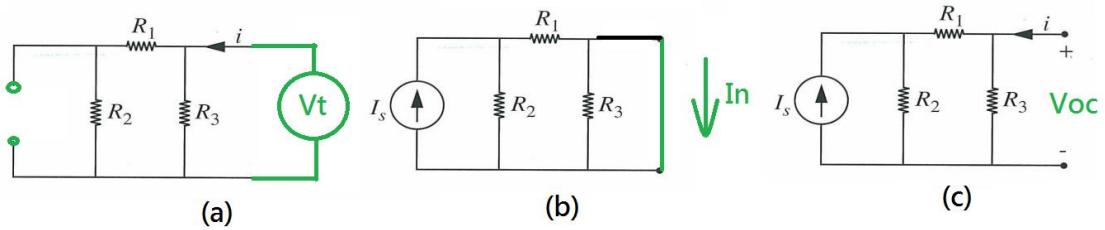

To find R_n & R_{Th} ($R_n = R_{Th}$), we need to turn off all the independent source and add a test voltage on the output node. $R_n = R_{Th} = \frac{V_t}{I_t}$. Please refer to figure (a).

$$R_n = R_{Th} = (R_1 + R_2) \parallel R_3$$

We need to find out the short circuit current (I_n) for Norton equivalent. Please refer to figure (b).


$$I_N = I_s \frac{R_2}{R_1 + R_2}$$

And open circuit voltage for Thevenin equivalent. Please refer to figure (c).


$$V_{OC} = I_s \left(\frac{R_2}{R_1 + R_2 + R_3} \right) R_3$$

10.

Solution:

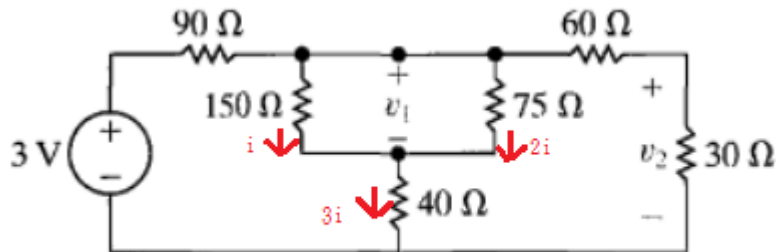

圖一

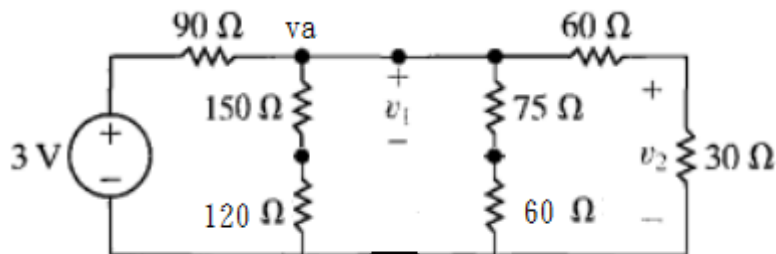

圖二

由圖一

$$\begin{aligned} 3i * 40\Omega &= i * 120\Omega \\ &= 2i * 60\Omega \end{aligned}$$

等效圖二

$$\begin{aligned}v_a &= 3V * \frac{(150 + 120) \parallel (75 + 60) \parallel (60 + 30)}{90 + (150 + 120) \parallel (75 + 60) \parallel (60 + 30)} \\&= 3V * \frac{45\Omega}{90\Omega + 45\Omega} \\&= 1V\end{aligned}$$

先求 v1

$$\begin{aligned}v_1 &= 1V * \frac{150\Omega}{150\Omega + 120\Omega} \\&= 1V * \frac{15\Omega}{27\Omega} \\&= \frac{5}{9}V\end{aligned}$$

再求 v2

$$\begin{aligned}v_2 &= 1V * \frac{30\Omega}{90\Omega} \\&= \frac{1}{3}V\end{aligned}$$