

EE2210 Electric Circuits, Spring 2017  
Practice problems (Lecture11-Lecture14)

1.  
Find the magnitude and phase of each of the following expression:

$$(8 + j7)(5e^{j30^\circ})(e^{-j39^\circ})(0.3 - j0.1)$$

2.  
Find the real and imaginary parts of the following expressions:


a)

$$(3 + j5)(4e^{j50^\circ})(7e^{-j20^\circ})$$

b)


$$(10e^{j50^\circ})(e^{j20^\circ})$$

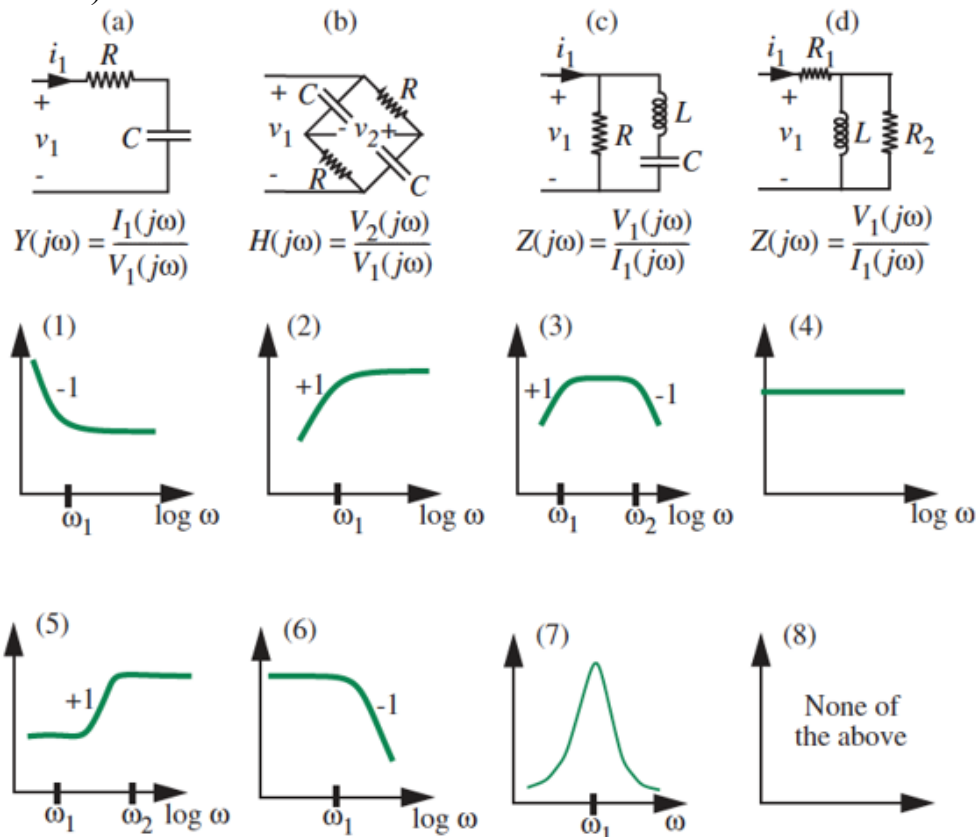3.  
For each of the circuits shown in the following figures, select the magnitude of the frequency response for the system function (that is, impedance, admittance )




4.

Write expressions for  $H(j\omega) = V_o/V_i$ , its magnitude  $|H(j\omega)|$ , and its phase angle  $\angle H(j\omega)$ , as a function of  $\omega$  in the following figure.

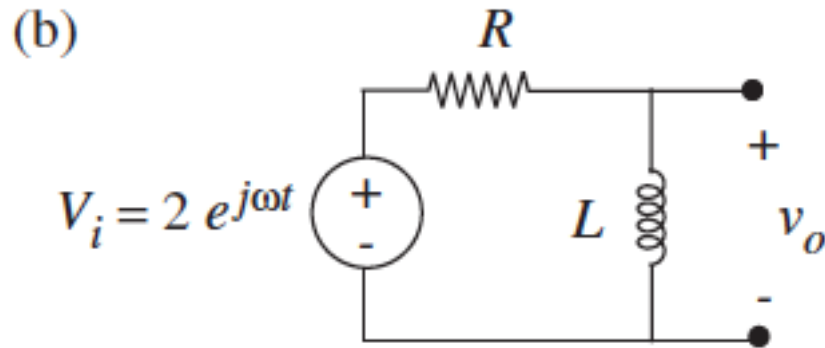

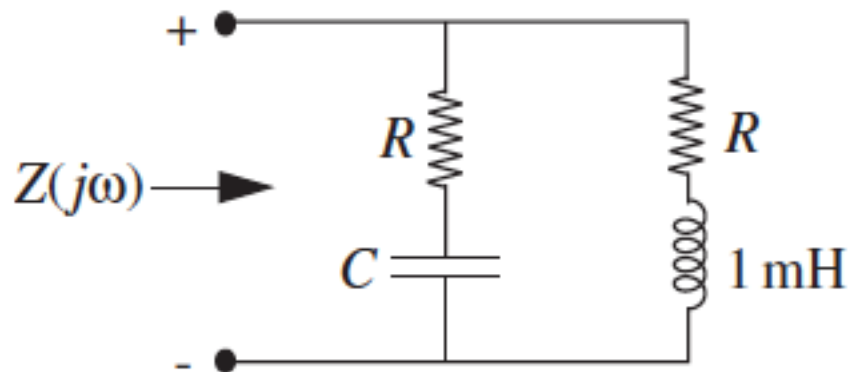5.


The impedance of the network shown in Figure is found to be  $2 \text{ k}\Omega$  and is purely real all frequencies. The value of the inductor is one  $\text{mH}$  as shown. What are the values of  $R$  and  $C$ ?



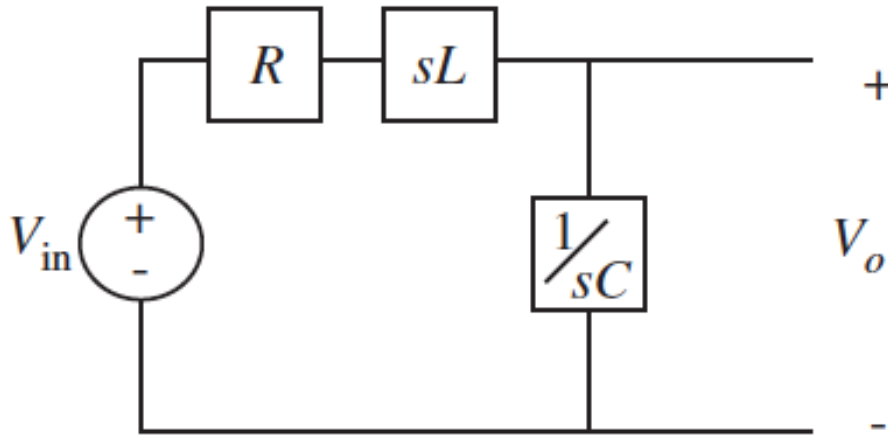6.


The circuit shown in Figure has an input voltage  $v_{inl}(t) = V_1 \cos(120\pi t)$ , and  $L = 500 \text{ mH}$ ,  $C = 80 \mu\text{F}$ , and  $R = 50 \Omega$ .

Compute the transfer function  $H(s) = V_o(s)/V_{inl}(s)$ .



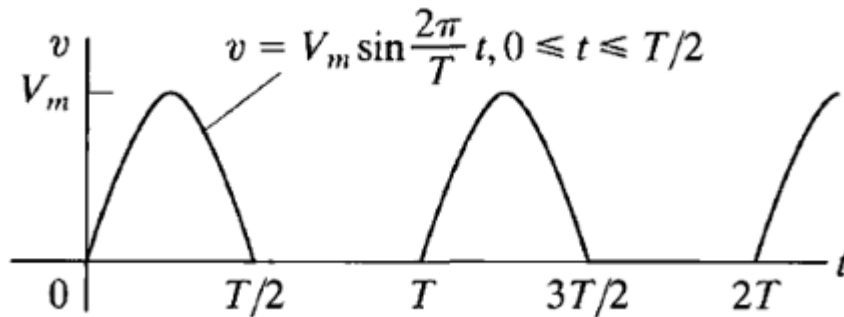
7.

Find the rms value of the half-wave rectified sinusoidal voltage shown.



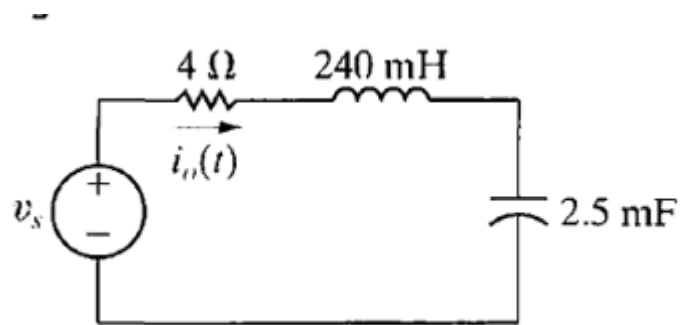
8.

Find the steady-state expression for  $i_o(t)$  in the circuit in the following figure if  $v_s = 100\sin 50t$  mV.



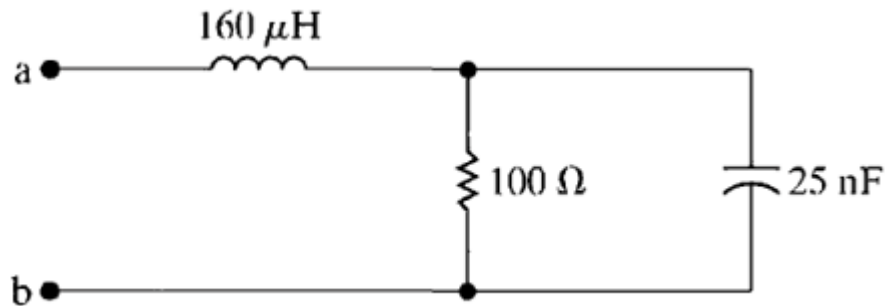9.

- For the circuit shown in the figure below, find the frequency (in radians per second) at which the impedance  $Z_{ab}$  is purely resistive.
- Find the value of  $Z_{ab}$  at the frequency of (a).




10.

A resistor denoted as  $R_L$  is connected in parallel with the capacitor in the circuit in the following Figure 14.7. The loaded low-pass filter circuit is shown in the following Figure 14.7.

- Derive the expression for the voltage transfer function  $\frac{V_o}{V_i}$ .
- At what frequency will the magnitude of  $H(j\omega)$  be maximum?
- What is the maximum value of the magnitude of  $H(j\omega)$ ?
- At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by  $\sqrt{2}$ ?
- Assume a resistance of  $10\text{ k}\Omega$  is added in parallel with the  $100\text{ nF}$  capacitor in the circuit in Fig 14.4.  
Find  $\omega_c$ ,  $H(j0)$ ,  $H(j\omega_c)$ ,  $H(j0.1\omega_c)$ , and  $H(j10\omega_c)$ .

**Figure P14.7**

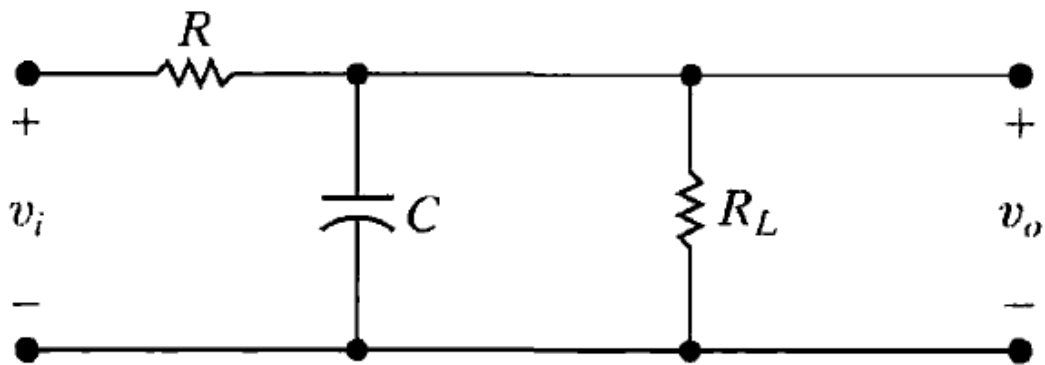

**Figure P14.4**

