
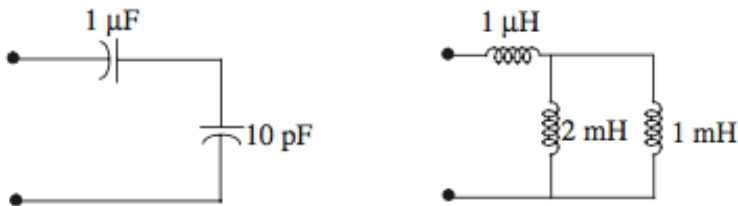


EE2210 Electric Circuits, Spring 2017  
Practice problems (Lecture4-Lecture7)

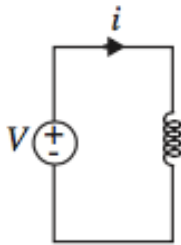
1. Find the equivalent capacitance or inductance of the following circuits.




2. Find the current  $i$  in the following figure when the voltage source is an impulse function  $\delta(t)$ .



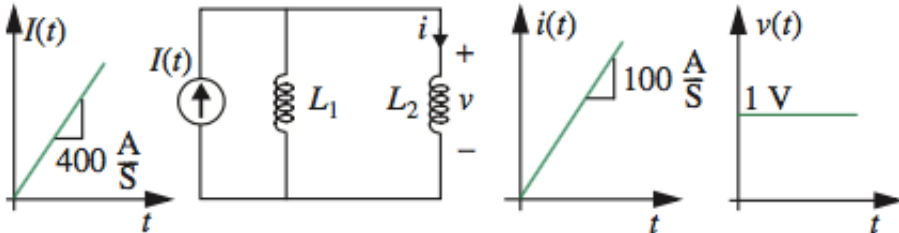
3. Consider the following circuit with two parallel inductors and one current source. The current source  $I(t)$ , the current flows through  $L_2$ ,  $i(t)$ , and the voltage across  $L_2$ ,  $v(t)$  are shown as follows. What are  $L_1$  and  $L_2$ ?





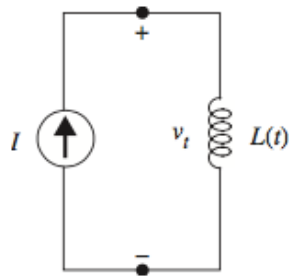
4. A constant current source having value  $I$  drives a time-varying inductor shown in the following figure. The inductance is  $L(t) = L_0 + L_1 \sin(\omega t)$ . Determine the inductor voltage  $v(t)$ .



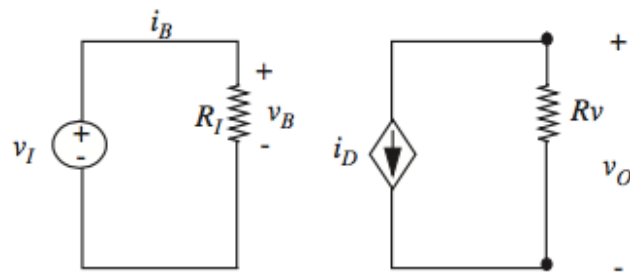
5. Consider the circuit in the following figure. (a) Determine  $v_o$  if  $i_D = K_1 v_B$ . (b) Determine  $v_o$  if  $i_D = K_2 i_B$ .



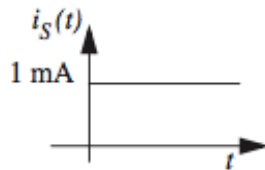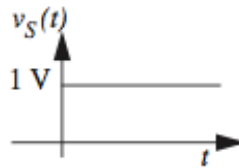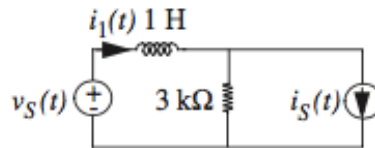
6. Determine  $i_1(t)$  in the following circuit.



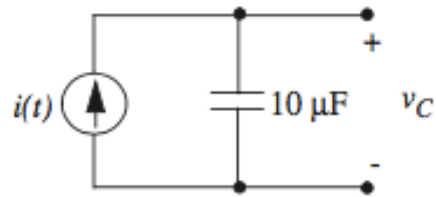7. In the following circuit,  $i(t) = 100 \mu\text{A}$  between  $0 < t < 1 \text{ s}$ , and  $i(t) = 0 \text{ A}$  otherwise. At  $t = 2 \text{ s}$ , the voltage  $v_C = 5 \text{ V}$ . What is  $v_C$  at  $t = -1 \text{ s}$ ?



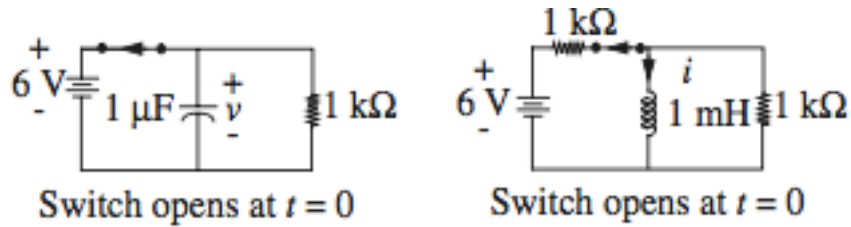8. Find the response of the following circuits for  $t > 0$ . Assume the input is shown for  $t > 0$ , and initial zero state.



9. The switch has been closed for a long time before opening at  $t = 0$ . (a) Find the value of  $L$  such that  $v_o(t = 1 \text{ ms})$  equals  $0.5 \cdot v_o(t = 0)$ . (b) Find the energy dissipated by the  $10\text{-}\Omega$  resistor at  $t = 1 \text{ ms}$ .

