
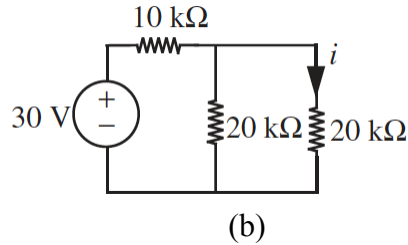


Quiz 1 (Total 120 points) **Solutions**

It is a closed-book, closed-note quiz. Calculator is allowed. Please show the process of thinking/calculation. Indicate your final answers clearly. Unit is needed if applicable.

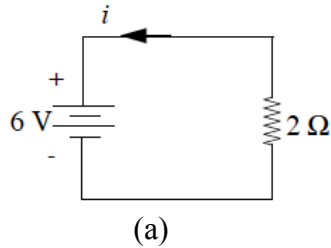- (i) Find the current i indicated in the network in the following figures. (14%)
 (ii) What is the power dissipated by the 2- Ω resistor in figure (a)? (5%)



Solution:

(1)



(a) $i = -\frac{6}{2} = -3A$ (7%)

(b) $i = \frac{30V}{10K + (20K || 20K)} * \frac{1}{2} = 0.75mA$ (7%)

(2)

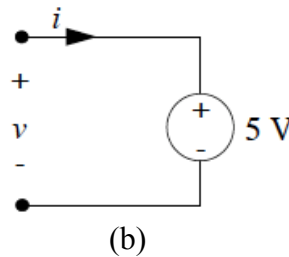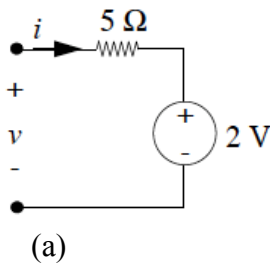(a) $P = v_R * i_R = 6 * 3 = 18W$ (5%)



- Sketch the $i - v$ characteristics for the networks in the following figures. (16%)




Solution:

(a). (8%)

(b). (8%)

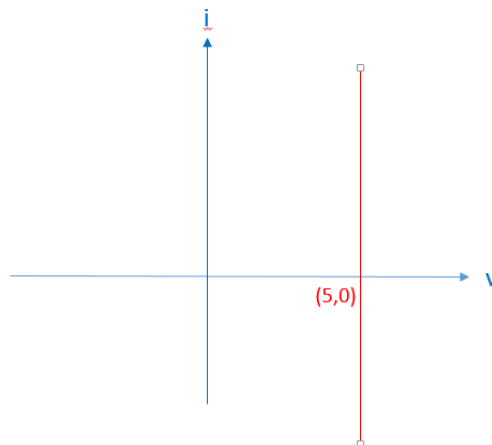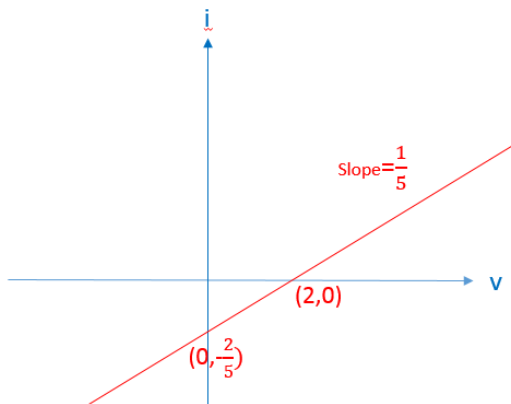


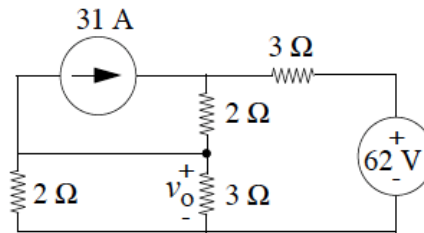3. Find the voltage v_0 in the network in the following figure using superposition.
(15%)




Solution:

Turn off the voltage source(short)

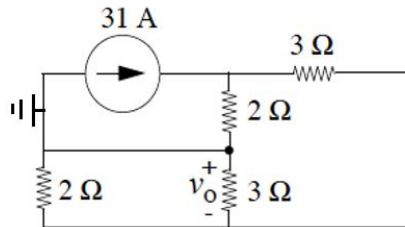

$$v_{o,cs} = -31A * \frac{2\Omega}{2\Omega + (3\Omega + 3\Omega \parallel 2\Omega)} * \frac{2\Omega}{3\Omega + 2\Omega} * 3\Omega = -12V$$


Turn off the current source(open)

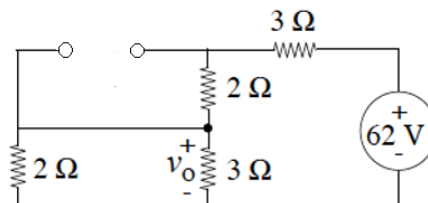


$$v_{o,vs} = 62V * \frac{3\Omega \parallel 2\Omega}{3\Omega + 2\Omega + 3\Omega \parallel 2\Omega} = 12V$$

$$v_o = v_{o1} + v_{o2} = -12V + 12V = 0V$$

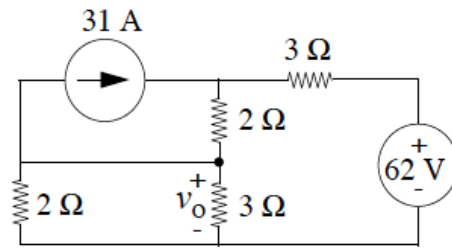4. Find the voltage v_o in the network in the following figure using node method. (15%)



Solution:

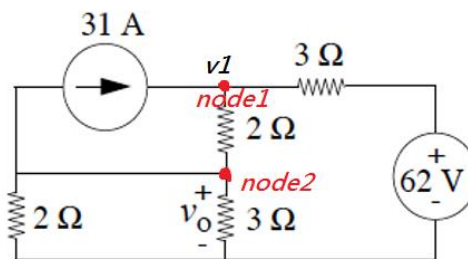

$$\text{node1: } 31A + \frac{62V - v_1}{3\Omega} - \frac{v_1 - v_o}{2\Omega} \text{----- (1)}$$

$$\text{node2: } \frac{v_1 - v_o}{2\Omega} = \frac{v_o}{3} + \frac{v_o}{2} + 31A \text{----- (2)}$$


From (2) we know

$$v_1 = \frac{8v_o + 186}{3} \text{----- (3)}$$

and from (1) and (3), we get


$$v_o = 0V$$

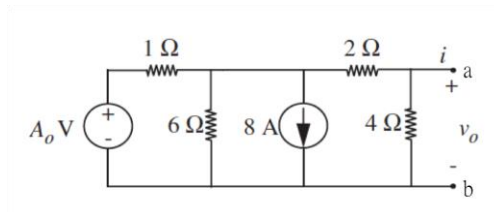5. Find the Thevenin equivalent of the circuit at terminal ab in the following figure.
Assume $A_0 = 4$. (20%)




Solution:

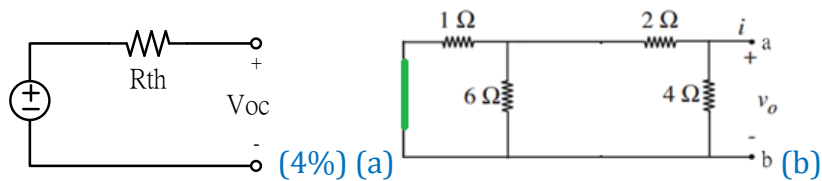To find Thevenin equivalent, we have to find out the open circuit voltage (V_{oc}) and equivalent impedance (R_{th}), which is indicated on the following figure (a). To find R_{Th} , we need to turn off all the independent source and the circuit becomes figure (b).



$$R_{Th} = \frac{5}{3} \Omega$$

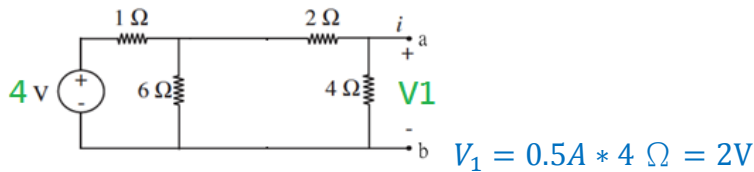For finding V_{oc} , we use superposition method. Turn off the current source.



Turn off the Voltage source.




$$i_2 = -8A * \frac{\frac{6}{7} \Omega}{\frac{6}{7} \Omega + 6 \Omega} = -1A$$

$$V_2 = i_2 * 4 \Omega = -4V$$


$$\rightarrow V_{oc} = V_1 + V_2 = -2V \text{ (16\%)}$$

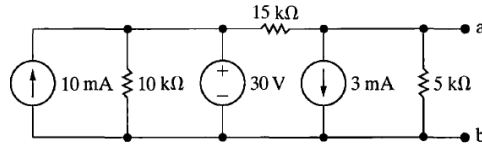6. Find the Norton equivalent of the circuit at terminal ab in the following figure. (20%)




Solution:

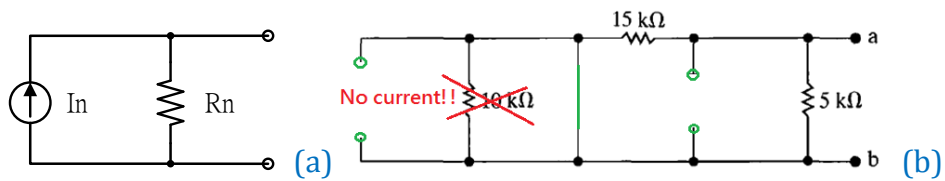To find Norton equivalent, we have to find out the short circuit current (I_s) and equivalent impedance (R_N), which is indicated on the following figure (a). To find R_N , we need to turn off all the independent source and the circuit becomes figure (b).




$$R_N = \frac{15}{4} \text{ k}\Omega$$

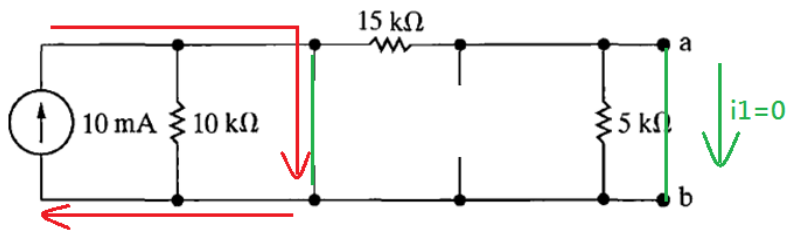For finding I_n , we use superposition method. Turn off the 30V voltage source and 3mA current source.




$$i_1 = 0 \text{ A}$$

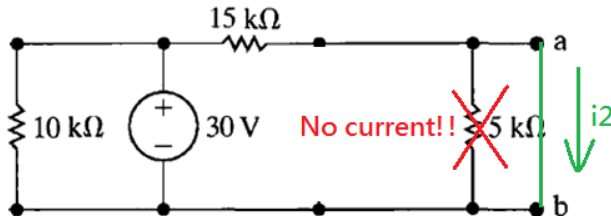Turn off the 10mA current source and 3mA current source.



$$i_2 = \frac{30\text{V}}{15\text{k}\Omega} = 2 \text{ mA}$$

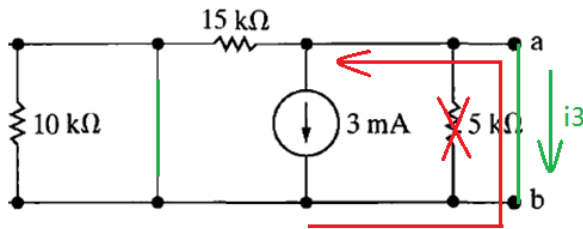
Turn off the 10mA current source and 30V voltage source.




$$i_3 = -3 \text{ mA}$$

$$I_N = i_1 + i_2 + i_3 = -1 \text{ mA} \quad (16\%)$$

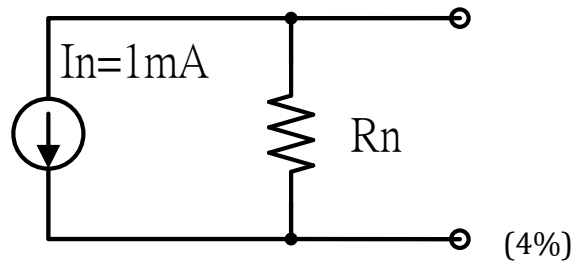The answer is acceptable with $I_N = 1 \text{ mA}$, but the current direction is converse, please refer to the following figure.



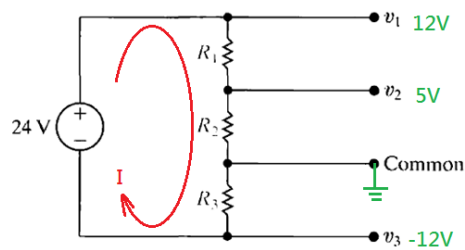7. Determine the values of the resistors R_1 , R_2 , and R_3 such that $v_1 = 12 \text{ V}$, $v_2 = 5 \text{ V}$, $v_3 = -12 \text{ V}$, and the total power dissipated by the circuit by the 24 V source is 80W in the following figure. (15%)



Solution:

$$80\text{W} = 24 \text{ V} * I \rightarrow I = \frac{10}{3} \text{ A}$$

$$R_1 = (12\text{V} - 5\text{V}) / I = 2.1 \Omega (5\%)$$

$$R_2 = (5\text{V} - 0\text{V}) / I = 1.5 \Omega (5\%)$$

$$R_3 = 12\text{V} / I = 3.6 \Omega (5\%)$$