

Quiz2(沒寫單位一律扣 1 分!!!!沒寫算式，答案又錯者，該題一律 0 分!!)

1.

The power dissipated in the 10-Ohm resistor :

After $t = 0$,

$$R_{eq} = 2 + (40 || 10) = 10\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{10} = 0.2$$

$$i_L(t) = 20e^{-\frac{1}{0.2}t} A = 20e^{-5t} A, t \geq 0 \text{ (5\%)}$$


$$i_{10\Omega}(t) = -i_L \frac{40}{10+40} = -16e^{-5t} A, t \geq 0 \text{ (5\%)}$$

$$p_{10\Omega}(t) = i_{10\Omega}^2 * 10 = 2560e^{-10t} W, t \geq 0 \text{ (5\%) (寫 2560 : -2)}$$

Initial energy stored in the 2-H inductor at $t = 0$: (5%)


$$w_L(0) = \frac{1}{2} L * i_L(0)^2 = 0.5 * 2 * 20^2 = 400J$$

2.

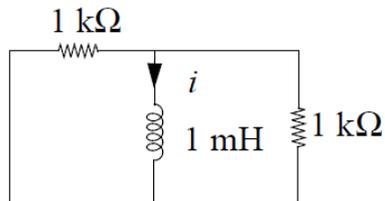

$$i(0) = 6 \text{ mA}$$
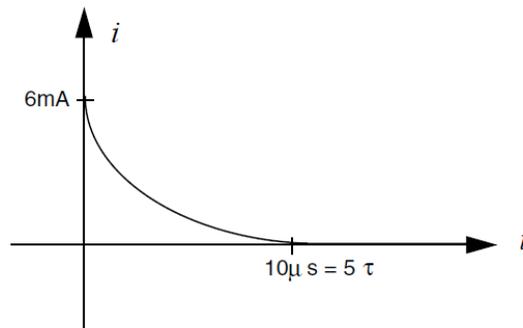
$$i = (6 \times 10^{-3}) e^{-t/\tau}, \tau = 2\mu s \text{ (15\%)}$$



(15%)

圖或是算式其中一項對，就給滿分

4.

(a)

$$\frac{d^2 v_c(t)}{dt^2} + \frac{1}{LC} v_c(t) = 0$$

(正負號寫錯給一半分數)

(b)

$$\omega_o = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/s}$$

(少寫單位扣一分，式子列錯一半分數)

(c)

$$v_c(t) = v_c(0) \cos(\omega_o t) = \cos(10^5 t)$$

(式子列對但沒求出 ω_o 扣一分；有寫算式但錯的不離譜只給一半分數)