

Quiz 3 solutions

1.

At time $t > 0$, the circuit becomes an LC oscillator.

The natural frequency ω_o is equal to $\sqrt{\frac{1}{LC}}$. Since the capacitor starts out charged, initially, the voltage across the capacitor is a cosine function with maximum amplitude of 2 V. The current through the inductor is the same as the current through the capacitor, and it is characterized by the capacitor I-V relation : $i_c = C \frac{dv_c}{dt}$. Taking the derivative, we get a negative sinusoidal relation.


$$v_c(t) = v_c(0)\cos(\omega_o t)$$


$$i_L(t) = -\sqrt{\frac{C}{L}}v_c(0)\sin(\omega_o t)$$

ANS :

$$v_c = 2 \cos\left(\sqrt{\frac{1}{LC}} t\right) = 2\cos(10t)$$

$$i_L(t) = -0.2\sin(10t)$$

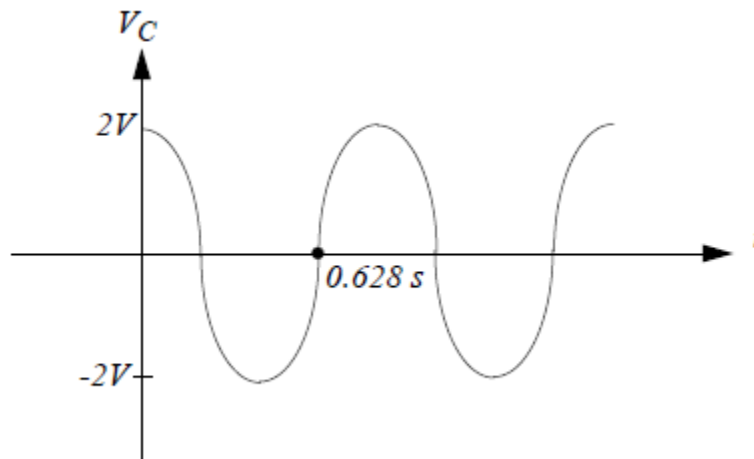

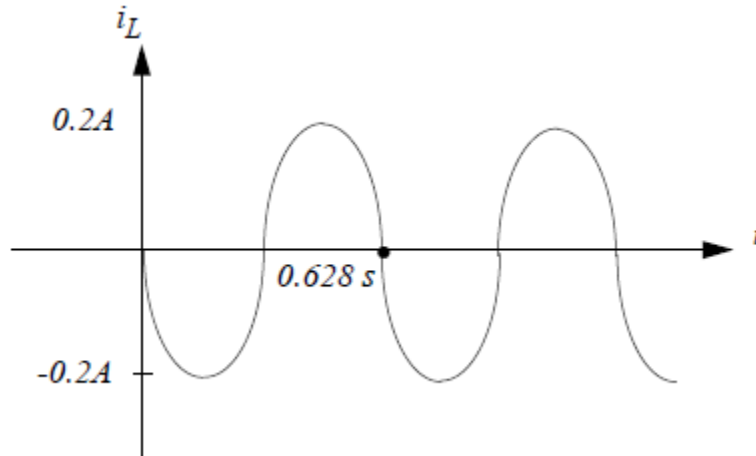

2.

$$\frac{v_2}{v_i} = \frac{L_s || R_2}{R_1 + L_s || R_2} = |H(j\omega)|e^{j\phi}$$

where

$$|H(j\omega)| = \frac{\omega R_2 L}{\sqrt{\omega^2 L^2 (R_1 + R_2)^2 + R_1^2 R_2^2}}$$

And

$$\phi = \frac{\pi}{2} - \tan^{-1}\left[\frac{\omega L(R_1 + R_2)}{R_1 R_2}\right]$$

For $\omega = 4$, $\phi = \frac{\pi}{4}$, and $|H(j\omega)| = \frac{1}{3\sqrt{2}}$,

$$v_2(t) = \frac{1}{\sqrt{2}} \cos\left(4t + \frac{\pi}{4}\right)$$


ANS :

$$v_2(t) = \frac{1}{\sqrt{2}} \cos\left(4t + \frac{\pi}{4}\right)$$

3.

ANS:

$$Z = \frac{R}{1 + j\omega RC}$$

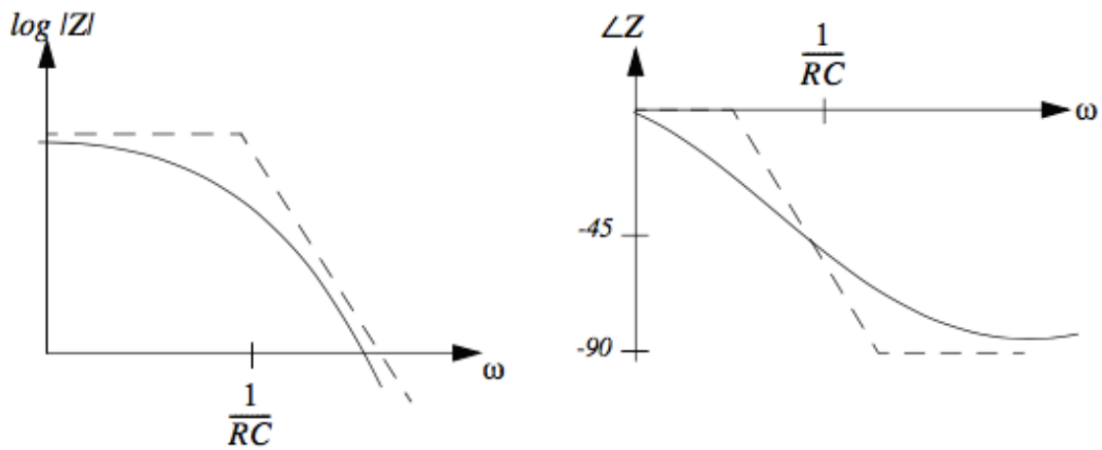

4.

$$i_L + i_R + i_C = 0$$

$$\frac{1}{sL} + \frac{1}{R} + sC = 0$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \quad (s^2 + 2\alpha s + \omega_0^2 = 0)$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 * \frac{25}{3} * 0.001} = 60$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 100$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 80$$

$\alpha < \omega_0$, underdamped

$$\text{Assume } v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

For underdamped, $v(t)$ can be expressed as

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$= e^{-60t}(B_1 \cos 80t + B_2 \sin 80t)$$

The initial condition $v(t=0) = 10 \text{ V}$,

$$B_1 = 10$$

$$i_L = \frac{1}{L} \int v(t) dt$$

$$= \frac{1}{L} \left\{ \left(-\frac{1}{500} e^{-60t} \right) [(3B_1 + 4B_2) \cos 80t + (-4B_1 + 3B_2) \sin 80t] + C \right\}$$

The initial condition $i_L(t=0) = -0.6 \text{ A}$,

$$\frac{1}{0.1} \left(-\frac{1}{500} \right) (3B_1 + 4B_2 + C) = -0.6$$

Because

$$\frac{1}{0.1} \left(-\frac{1}{500} \right) 3B_1 = \frac{1}{0.1} \left(-\frac{1}{500} \right) 30 = -0.6$$

$$4B_2 + C = 0$$

Assume $C = 0$, then $B_2 = 0$

From above equation,

$$v(t) = 10e^{-60t} \cos 80t \text{ (V)}$$

the number of cycles $v(t)$ takes to settle = Q,


$$Q = \frac{\omega_0}{2\alpha} = \frac{100}{2 * 60} = \frac{5}{6}$$

$$\text{the period of } v(t) = \frac{2\pi}{\omega_d} = \frac{2\pi}{80}$$

Ans:


a. $v(t) = 10e^{-60t} \cos 80t \text{ (V)}$

b.

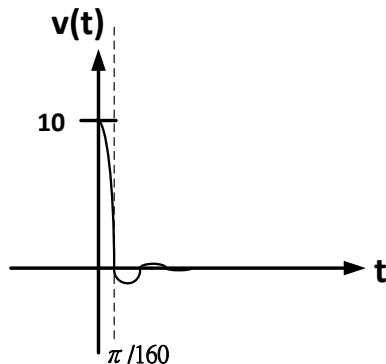

- c. the period of $v(t) = \frac{2\pi}{80}$
 d. the number of cycles $v(t)$ takes to settle = $\frac{5}{6}$

5.

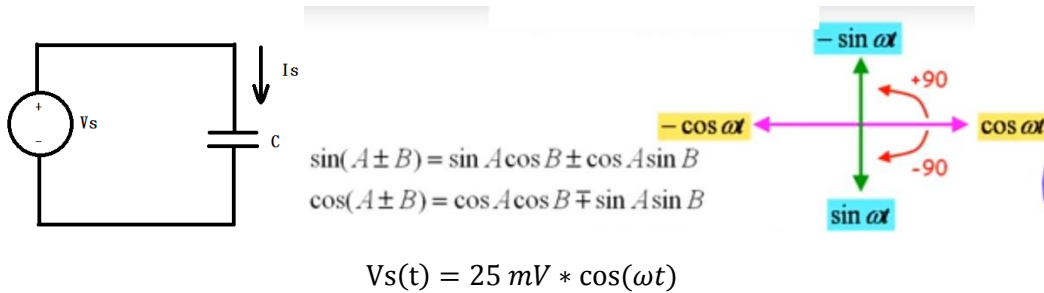

$$I_s(t) = C * \frac{dV_s}{dt} = C * (25 \text{ mV})(-\sin(\omega t)) * \omega = C * (25 \text{ mV})(\cos(\omega t + 90^\circ)) * \omega$$

Steady state current: $C * (25 \text{ mV}) * \omega = 628.32 \mu\text{A}$

$$\rightarrow C = \frac{628.32 \mu\text{A}}{(25 \text{ mV}) * \omega} = \frac{628.32 \mu\text{A}}{(25 \text{ mV}) * (2\pi * 80 \text{ kHz})} = 5 * 10^{-8} \text{ F} = 50 \text{ nF}$$

Impedance:

$$Z_c = \frac{1}{j\omega C} = -j * \frac{1}{(2\pi * 80 \text{ kHz})(5 * 10^{-8} \text{ F})} = -j39.79 \Omega$$

Ans:

- a. $f=80 \text{ kHz}$
 b. $+90^\circ$
 c. $C=5 * 10^8 \text{ F} = 50 \text{ nF}$
 d. $Z_c = -j39.79 \Omega$