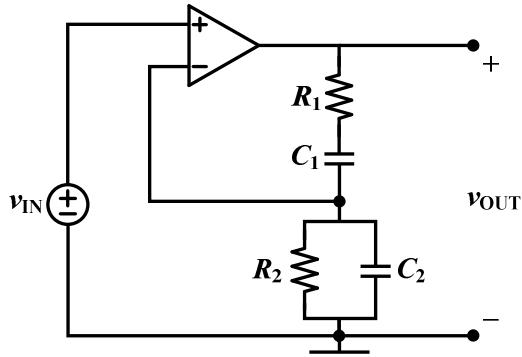


學號：_____

姓名：_____

For the circuit as shown,

- Determine the transfer function $\mathbf{H}(j\omega) = \mathbf{V}_{\text{out}}(j\omega)/\mathbf{V}_{\text{in}}(j\omega)$ in terms of R_1, R_2, C_1 , and C_2 .
- Find $\mathbf{H}(j\omega)$ at low frequency ($\omega \rightarrow 0$).
- Find $\mathbf{H}(j\omega)$ at high frequency ($\omega \rightarrow \infty$).
- For a special case with $R_1 = R_2 = R$ and $C_1 = C_2 = C$, Find $\mathbf{H}(j\omega)$ when $\omega = 1/RC$.



Solution:

(a)

$$\begin{aligned} \mathbf{V}_{\text{out}} &= \mathbf{V}_{\text{in}} + \left[\left(\frac{\mathbf{V}_{\text{in}}}{R_2 \parallel \frac{1}{j\omega C_2}} \right) \times \left(R_1 + \frac{1}{j\omega C_1} \right) \right] \\ \Rightarrow \mathbf{H}(j\omega) &= \frac{\mathbf{V}_{\text{out}}}{\mathbf{V}_{\text{in}}} (j\omega) = 1 + \left(\frac{R_1 + \frac{1}{j\omega C_1}}{R_2 \parallel \frac{1}{j\omega C_2}} \right) = 1 + \left[\frac{\left(R_1 + \frac{1}{j\omega C_1} \right) \left(R_2 + \frac{1}{j\omega C_2} \right)}{R_2 \frac{1}{j\omega C_2}} \right] = \frac{R_1}{R_2} + \frac{C_2}{C_1} + 1 + j\omega C_2 R_1 + \frac{1}{j\omega C_1 R_2} \end{aligned}$$

$$\Rightarrow \mathbf{H}(j\omega) = \left(\frac{R_1}{R_2} + \frac{C_2}{C_1} + 1 \right) + j \left(\omega C_2 R_1 - \frac{1}{\omega C_1 R_2} \right)$$

(b)

$$\boxed{\mathbf{H}(j\omega)|_{\omega \rightarrow 0} = -j \frac{1}{\omega C_1 R_2}}$$

(c)

$$\boxed{\mathbf{H}(j\omega)|_{\omega \rightarrow \infty} = j\omega C_2 R_1}$$

(d)

When $R_1 = R_2 = R, C_1 = C_2 = C$,

$$\Rightarrow \mathbf{H}(j\omega) = (1+1+1) + j\left(\omega CR - \frac{1}{\omega CR}\right)$$

$$\therefore \mathbf{H}(j\omega)\Big|_{\omega=\frac{1}{RC}} = 3$$

(a) $\mathbf{H}(j\omega) = \underline{\hspace{10cm}},$

(b) $\mathbf{H}(j\omega)\Big|_{\omega \rightarrow 0} = \underline{\hspace{10cm}},$

(c) $\mathbf{H}(j\omega)\Big|_{\omega \rightarrow \infty} = \underline{\hspace{10cm}},$

(d) $\mathbf{H}(j\omega)\Big|_{\omega=\frac{1}{RC}} = \underline{\hspace{10cm}}.$