

電路學(EE2210)第六次隨堂考

2013年11月6日


時間：10 分鐘

Close Book

學號： _____


姓名： _____

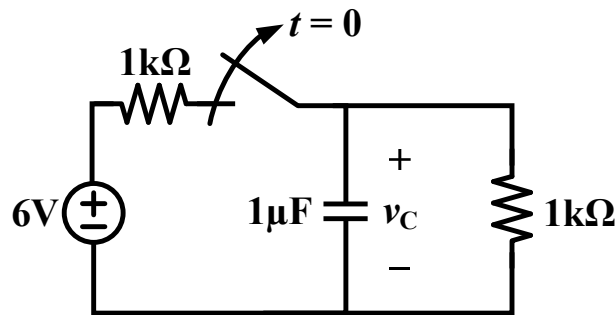For the circuit as shown in the following figure, the switch has been closed for a long time before opening at $t = 0$. Find the voltage across the capacitor $v_C(0^+)$ and its first derivative $\frac{dv_C(0^+)}{dt}$, i.e. right after the switch opens.



Solution:

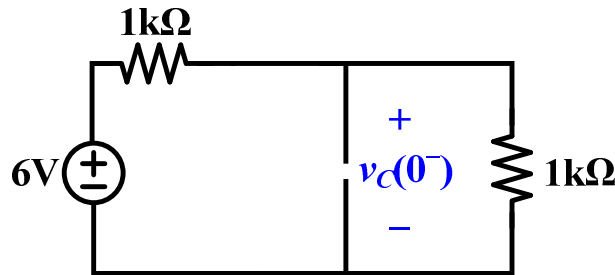
Because the switch has been closed for a long time before $t = 0$, the capacitor can be regarded as open, as shown in the following circuit.



The voltage drop across the capacitor can be found from the voltage divider circuit.

$$v_C(0^+) = v_C(0^-) = 6 \times \frac{1k}{1k + 1k} = 3V$$

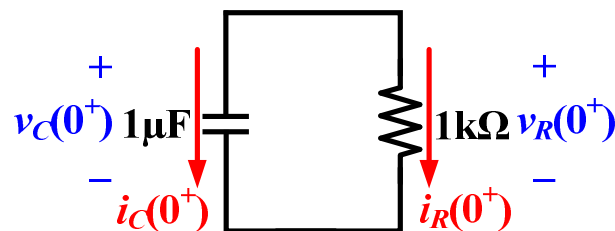Immediately after the switch is opened at $t = 0$, the equivalent circuit become



The voltage drop across the resistor is $v_C(0^+) = v_C(0^-) = 3V$, thus the current go through the resistor is



$$i_R(0^+) = \frac{v_R(0^+)}{1\text{ k}\Omega} = \frac{v_C(0^+)}{1\text{ k}\Omega} = \frac{3\text{ V}}{1\text{ k}\Omega} = 3\text{ mA}$$


and

$$i_C(0^+) = -i_R(0^+) = -3\text{ mA}$$

From element relation for capacitor, $i_C = C \frac{dv_C}{dt}$, we have


$$\frac{dv_C(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-3\text{ mA}}{1\text{ }\mu\text{F}} = -3000\text{ V/sec.}$$

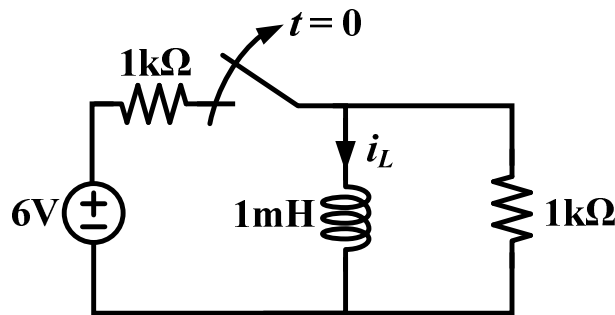For the circuit as shown in the following figure, the switch has been closed for a long time before opening at $t = 0$. Find the current pass through the inductor $i_L(0^+)$ and its first derivative $\frac{di_L(0^+)}{dt}$, i.e. right after the switch opens.



Solution:

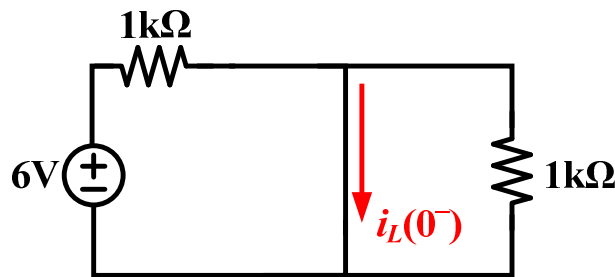
The switch has been closed for a long time before $t = 0$, the inductor can be regarded as short circuit for the terminal, as shown as the following circuit.



The current pass through the inductor is simply the current through the left-hand side 1 kΩ resistor.

$$i_L(0^+) = i_L(0^-) = \frac{6\text{ V}}{1\text{ k}\Omega} = 6\text{ mA}$$

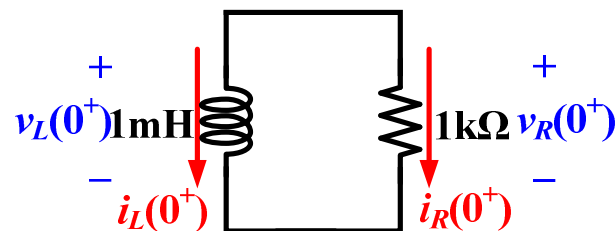After the switch is opened at $t = 0$, the circuit become



The current pass through the resistor is $i_L(0^+) = i_L(0^-) = 6 \text{ mA}$ and the voltage drop across the resistor is $v_R(0^+) = -i_L(0^+) \times 1 \text{ k}\Omega = -6 \text{ mA} \times 1 \text{ k}\Omega = -6 \text{ V}$

and

$$v_L(0^+) = v_R(0^+) = -6 \text{ V}$$

From element relation for inductor, $v_L = L \frac{di_L}{dt}$, we have

$$\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{-i_L(0^+) \times 1\text{k}}{1\text{m}} = \frac{-6\text{m} \times 1\text{k}}{1\mu} = -6000 \text{ A/sec}$$

$$v_C(0^+) = \underline{\hspace{2cm} 3\text{V} \hspace{2cm}}, \quad \frac{dv_C(0^+)}{dt} = \underline{\hspace{2cm} -3000\text{V/sec} \hspace{2cm}},$$

$$i_L(0^+) = \underline{\hspace{2cm} 6\text{mA} \hspace{2cm}}, \quad \frac{di_L(0^+)}{dt} = \underline{\hspace{2cm} -6000\text{A/sec} \hspace{2cm}}.$$