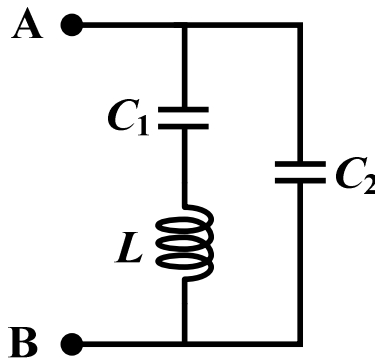


學號： _____

姓名： _____

For the following circuit as shown, answer that following questions.



- (1) Find the impedance between terminal A and B at frequency ω . (30%)
- (2) Find the frequency ω_0 at which the impedance between terminal A and B is zero. (10%)
- (3) Find the frequency range at which the impedance between terminal A and B behave like an inductor. (30%)
- (4) Find the frequency range at which the impedance between terminal A and B behave like a capacitor. (30%)

Solution:

(a)

$$Z(j\omega) = \frac{\left(\frac{1}{j\omega C_1} + j\omega L\right) \frac{1}{j\omega C_2}}{\left(\frac{1}{j\omega C_1} + j\omega L\right) + \frac{1}{j\omega C_2}} = \frac{1 - \omega^2 C_1 L}{j[\omega(C_1 + C_2) - \omega^3 C_1 C_2 L]} = -j \frac{1 - \omega^2 C_1 L}{[\omega(C_1 + C_2) - \omega^3 C_1 C_2 L]}$$

$$= j \frac{\omega^2 L C_1 - 1}{\omega[(C_1 + C_2) - \omega^2 C_1 C_2 L]} = j \frac{\omega L C_1 - \frac{1}{\omega}}{[(C_1 + C_2) - \omega^2 C_1 C_2 L]}$$

(b)

$$\text{If } Z(j\omega_0) = j \frac{\omega_0 L C_1 - \frac{1}{\omega_0}}{[(C_1 + C_2) - \omega_0^2 C_1 C_2 L]} = 0$$

$$\Rightarrow \omega_0 L C_1 - \frac{1}{\omega_0} = 0$$

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{L C_1}}$$

(c)

If the impedance $Z(j\omega)$ is like an inductor $j\omega L'$,

Case (1):

The conditions of $\omega LC_1 - \frac{1}{\omega} > 0$ and $[(C_1 + C_2) - \omega^2 C_1 C_2 L] > 0$ are must satisfied simultaneously,

$$\Rightarrow \omega > \sqrt{\frac{1}{LC_1}} \text{ and } 0 < \omega < \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}$$

Because $\frac{C_1 C_2}{C_1 + C_2} < C_1$, thus $\sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}} > \sqrt{\frac{1}{LC_1}}$,

Thus in this case, the completed region is $\sqrt{\frac{1}{LC_1}} < \omega < \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}$

Case (2):

The conditions of $\omega LC_1 - \frac{1}{\omega} < 0$ and $[(C_1 + C_2) - \omega^2 C_1 C_2 L] < 0$ are must satisfied simultaneously,

$$\Rightarrow 0 < \omega < \sqrt{\frac{1}{LC_1}} \text{ and } \omega > \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}$$

Thus in this case, the completed region is none.

By case (1) and (2), the total region is $\boxed{\sqrt{\frac{1}{LC_1}} < \omega < \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}}$.

(d)

If the impedance $Z(j\omega)$ is like a capacitor $-j\frac{1}{\omega C'}$,

Case (3):

The conditions of $\omega LC_1 - \frac{1}{\omega} > 0$ and $[(C_1 + C_2) - \omega^2 C_1 C_2 L] < 0$ are must satisfied simultaneously,

$$\Rightarrow \omega > \sqrt{\frac{1}{LC_1}} \text{ and } \omega > \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}$$

In this case, the completed region is $\omega > \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}$.

Case (4):

The conditions of $\omega LC_1 - \frac{1}{\omega} < 0$ and $[(C_1 + C_2) - \omega^2 C_1 C_2 L] > 0$ are must satisfied simultaneously,

$$\Rightarrow 0 < \omega < \sqrt{\frac{1}{LC_1}} \text{ and } 0 < \omega < \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}$$

In this case, the completed region is $0 < \omega < \sqrt{\frac{1}{LC_1}}$.

By case (3) and (4), the total regions are $0 < \omega < \sqrt{\frac{1}{LC_1}}$ and $\omega > \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}}}$.

(1) $Z_{AB} =$ _____, (2) $\omega_0 =$ _____,

(3) _____, (4) _____.