


學號：_____

姓名：_____

Find the sinusoidal steady state $v_o(t)$ for the following circuit by

- convert the $v_i(t)$ in time domain into the phasor expression $\mathbf{V}_i(j\omega)$ in the frequency domain,
- find the transfer function $\mathbf{H}(j\omega)$ in the frequency domain,
- find the numerical value of the $\mathbf{H}(j\omega)$ for $\omega = 5 \text{ rad/s}$ and $\omega = 50000 \text{ rad/s}$,
- find the $\mathbf{V}_o(j\omega)$ in the frequency domain from (a) and (c),
- convert the $\mathbf{V}_o(j\omega)$ in the frequency domain into $v_o(t)$ in time domain.

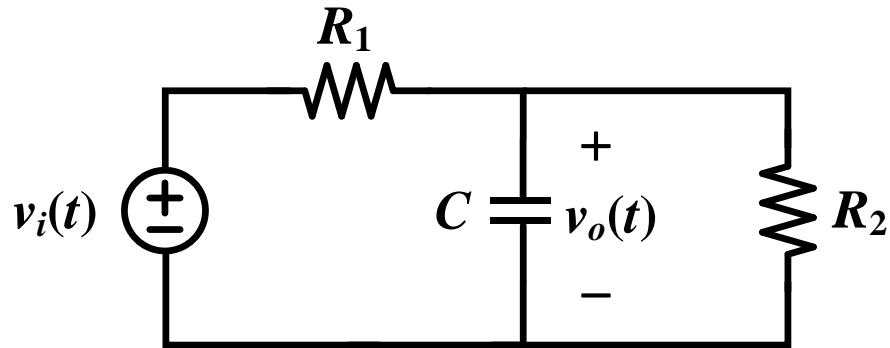(Assuming $R_1 = 6 \text{ k}\Omega$, $R_2 = 3 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$, and $v_i(t) = 6\cos(5t) + 12\cos(50000t) \text{ V.}$)



Solution:

(a)

$$v_i(t) = \operatorname{Re}\{\mathbf{V}_i e^{j\omega t}\} = \operatorname{Re}\{6e^{j0}e^{j5t} + 12e^{j0}e^{j50000t}\}$$

$$\therefore \boxed{\mathbf{V}_i|_{\omega=5} = 6\text{V}} \text{ and } \boxed{\mathbf{V}_i|_{\omega=50000} = 12\text{V}}$$

(b)

$$\begin{aligned} \mathbf{H}(j\omega) &= \frac{\mathbf{V}_o}{\mathbf{V}_i}(j\omega) = \frac{R_2 // \frac{1}{j\omega C}}{R_1 + R_2 // \frac{1}{j\omega C}} = \frac{\frac{1}{j\omega C} R_2}{\frac{1}{j\omega C} + R_2} = \frac{\frac{1}{j\omega C} R_2}{\frac{1}{j\omega C} + R_2} \\ &= \frac{\frac{R_2}{j\omega C}}{\left(\frac{1}{j\omega C} + R_2\right)R_1 + \frac{1}{j\omega C} R_2} = \frac{\frac{R_2}{j\omega C}}{R_1 R_2 + \frac{R_1 + R_2}{j\omega C}} = \frac{R_2}{(R_1 + R_2) + j\omega C R_1 R_2} = \frac{1}{\left(\frac{R_1 + R_2}{R_2}\right) + j\omega C R_1} \\ &= \frac{\frac{R_2}{R_1 + R_2}}{1 + \frac{j\omega C R_1}{\left(\frac{R_1 + R_2}{R_2}\right)}} = \frac{\frac{R_2}{R_1 + R_2}}{1 + \frac{j\omega C R_1}{\left(\frac{R_1 + R_2}{R_2}\right)}} = \frac{\frac{R_2}{R_1 + R_2}}{1 + j\omega C \frac{R_1 R_2}{R_1 + R_2}} \\ &= \frac{\frac{3000}{6000 + 3000}}{1 + j\left(\omega \frac{1}{1000000} \frac{3000 \times 6000}{3000 + 60000}\right)} = \frac{\frac{1}{3}}{1 + j\left(\frac{\omega}{500}\right)} \end{aligned}$$

(c)

$$\mathbf{H}(j\omega) = |\mathbf{H}| \angle \phi$$

$$\therefore |\mathbf{H}(j\omega)| = \frac{\frac{1}{3}}{\sqrt{1^2 + \left(\frac{\omega}{500}\right)^2}} \quad \text{and} \quad \phi = \angle \mathbf{H}(j\omega) = -\tan^{-1}\left(\frac{\omega}{500}\right)$$

$$\boxed{|\mathbf{H}(j\omega)|_{\omega=5} = \frac{\frac{1}{3}}{\sqrt{1^2 + \left(\frac{\omega}{500}\right)^2}} = \frac{\frac{1}{3}}{\sqrt{1^2 + \left(\frac{5}{500}\right)^2}} = 0.33 \cong \frac{1}{3}}$$

$$|\mathbf{H}(j\omega)|_{\omega=50000} = \frac{\sqrt[3]{3}}{\sqrt{1^2 + \left(\frac{\omega}{500}\right)^2}} = \frac{\sqrt[3]{3}}{\sqrt{1^2 + \left(\frac{50000}{500}\right)^2}} = 3.33 \times 10^{-3}$$

$$\angle \mathbf{H}(j\omega)_{\omega=5} = -\tan^{-1}\left(\frac{5}{500}\right) = -0.57^\circ \cong 0^\circ$$

$$\angle \mathbf{H}(j\omega)_{\omega=50000} = -\tan^{-1}\left(\frac{50000}{500}\right) = -89.43^\circ \cong -90^\circ$$

(d)

$$\mathbf{V}_o(j\omega) = \mathbf{V}_i(j\omega) \times \mathbf{H}(j\omega)$$

$$\mathbf{V}_o(j\omega)_{\omega=5} = \mathbf{V}_i(j5) \times \mathbf{H}(j5) = 6e^{j(0^\circ)} \times \sqrt[3]{3} e^{j(-0.57^\circ)} = 2e^{j(-0.57^\circ)} \cong 2e^{j(0^\circ)} \mathbf{V}$$

$$\mathbf{V}_o(j\omega)_{\omega=50000} = \mathbf{V}_i(j50000) \times \mathbf{H}(j50000) = 12e^{j(0^\circ)} \times 3.33 \times 10^{-3} e^{j(-89.43^\circ)} = 0.03996 e^{j(-89.43^\circ)} \cong 0.04 e^{j(-90^\circ)} \mathbf{V}$$

(e)

$$\begin{aligned} v_o(t) &= v_o(t)_{\omega=100} + v_o(t)_{\omega=50000} \\ &= 2\cos(5t - 0.57^\circ) + 0.04\cos(50000t - 89.43^\circ) \\ &\cong 2\cos(5t) + 0.04\cos(50000t - 90^\circ) \end{aligned}$$

(a) $\mathbf{V}_i(j\omega)$ (at $\omega = 5$ rad/s) = _____,

$\mathbf{V}_i(j\omega)$ (at $\omega = 50000$ rad/s) = _____,

(b) $\mathbf{H}(j\omega) =$ _____,

(c) $\mathbf{H}(j\omega) = |\mathbf{H}| \angle \phi$

where $|\mathbf{H}|$ (at $\omega = 5$ rad/s) = _____,

$|\mathbf{H}|$ (at $\omega = 50000$ rad/s) = _____,

and ϕ (at $\omega = 5$ rad/s) = _____,

ϕ (at $\omega = 50000$ rad/s) = _____,

(d) $\mathbf{V}_o(j\omega)$ (at $\omega = 5$ rad/s) = _____,

$\mathbf{V}_o(j\omega)$ (at $\omega = 50000$ rad/s) = _____,

(e) $v_o(t) =$ _____.