

電路學(EE2210)第三次隨堂考

2015年10月7日


時間：10 分鐘

Close Book

學號： _____

姓名： _____

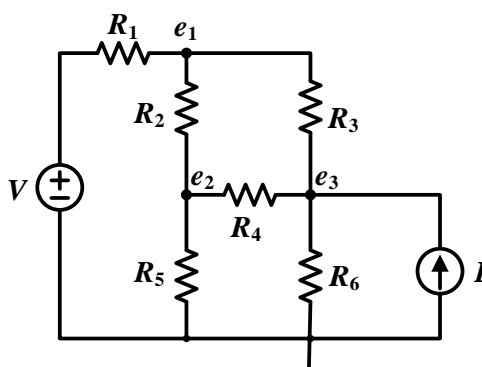The network shown below has three nodes with unknown node voltages e_1 , e_2 and e_3 . Use conductance instead of resistance to write the node equations. Simplify the equations by collecting terms and arranging them in the “standard” form for n linear equations in n unknowns. (*Do not solve the equations.*)



Matrix Form:
$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} S_1 \\ S_2 \\ S_3 \end{bmatrix}$$

$G_{11} = \underline{G_1 + G_2 + G_3}$, $G_{12} = \underline{-G_2}$, $G_{13} = \underline{-G_3}$,

$G_{21} = \underline{-G_2}$, $G_{22} = \underline{G_2 + G_4 + G_5}$, $G_{23} = \underline{-G_4}$,

$G_{31} = \underline{-G_3}$, $G_{32} = \underline{-G_4}$, $G_{33} = \underline{G_3 + G_4 + G_6}$,

$S_1 = \underline{G_1 V}$, $S_2 = \underline{0}$, $S_3 = \underline{I}$,

(i) KCL equations:

$$\text{node } e_1: G_1(e_1 - V) + G_2(e_1 - e_2) + G_3(e_1 - e_3) = 0$$

$$\text{node } e_2: G_2(e_2 - e_1) + G_5(e_2 - 0) + G_4(e_2 - e_3) = 0$$

$$\text{node } e_3: G_3(e_3 - e_1) + G_4(e_3 - e_2) - I + G_6(e_3 - 0) = 0$$

(ii) n linear equations:

$$\begin{cases} (G_1 + G_2 + G_3)e_1 + (-G_2)e_2 + (-G_3)e_3 = G_1V \\ (-G_2)e_1 + (G_2 + G_4 + G_5)e_2 + (-G_4)e_3 = 0 \\ (-G_3)e_1 + (-G_4)e_2 + (G_3 + G_4 + G_6)e_3 = I \end{cases}$$

(iii) Matrix form:

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} S_1 \\ S_2 \\ S_3 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} (G_1 + G_2 + G_3) & (-G_2) & (-G_3) \\ (-G_2) & (G_2 + G_4 + G_5) & (-G_4) \\ (-G_3) & (-G_4) & (G_3 + G_4 + G_6) \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} G_1V \\ 0 \\ I \end{bmatrix}$$