

學號： _____


姓名： _____

An inverter circuit using a MOSFET and a resistor is shown in the figure below. The MOSFET has a threshold voltage $V_T = 2$ V. Assume that $V_S = 5$ V and $R_L = 9$ k Ω . For this program, model the MOSFET using its switch-resistor model. Assume that the on-state resistance of the MOSFET is $R_{ON} = 1$ k Ω

(a) Draw the voltage transfer characteristics for the inverter. (20%)

(b) Does the inverter satisfy the static discipline, which has voltage thresholds given by $V_{IL} = 0.3$ V, $V_{OL} = 0.2$ V, $V_{IH} = 1.7$ V, and $V_{OH} = 4.8$ V ? (40%)

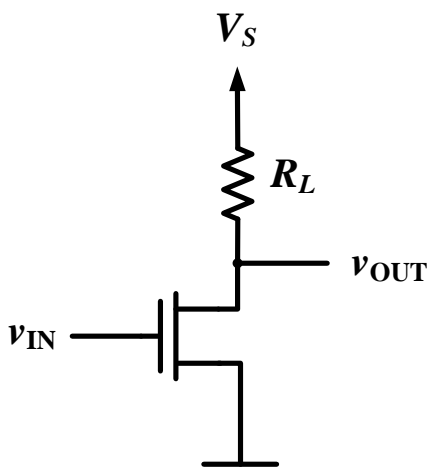(c) Does the inverter satisfy the static discipline, which has voltage thresholds given by $V_{IL} = 2.5$ V, $V_{OL} = 1$ V, $V_{IH} = 3.5$ V, and $V_{OH} = 4$ V ? (40%)




(a) The output high voltage V_{OH} for the inverter is 5 V.


The output low voltage V_{OL} for the inverter is

$$V_S \times \left(\frac{R_{ON}}{R_L + R_{ON}} \right) = 5 \times \frac{1}{9 + 1} \Rightarrow V_{OUT} = 0.5 \text{ V}$$

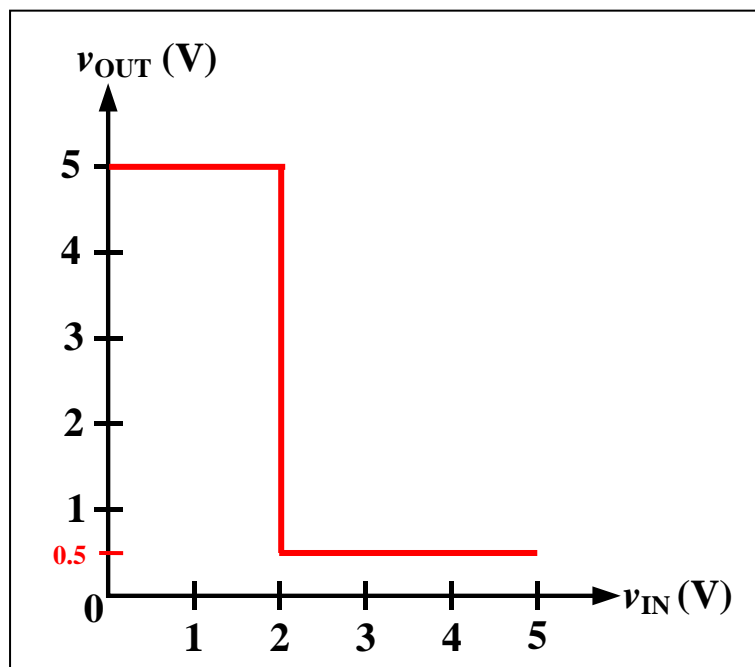The lowest input voltage recognized as a logical 1 is $V_T = 2$ V




(b)

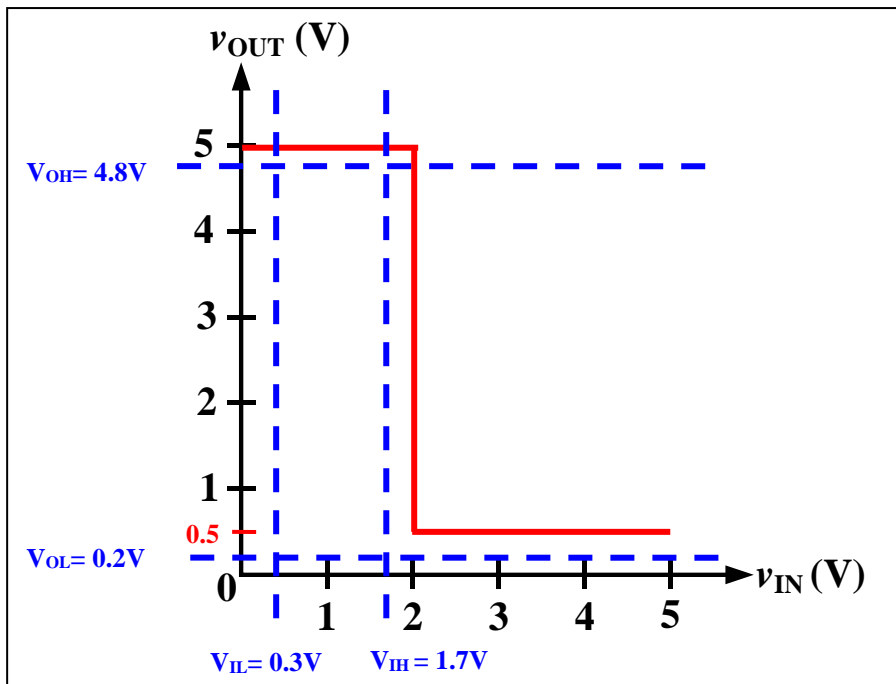

- (i) V_{IL} : satisfy
- (ii) V_{OL} : not satisfy
- (iii) V_{IH} : not satisfy
- (iv) V_{OH} : satisfy

(c)

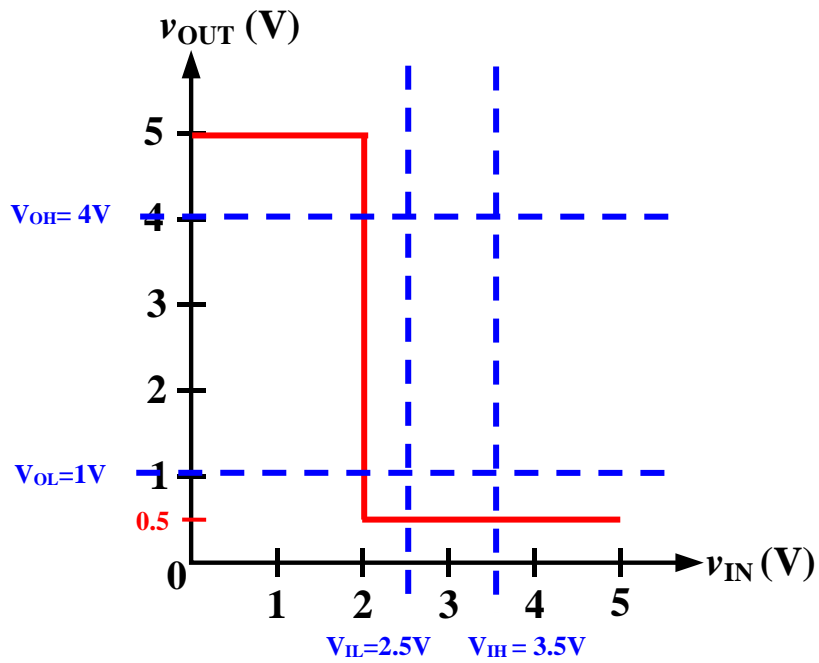

- (i) V_{IL} : not satisfy
- (ii) V_{OL} : satisfy
- (iii) V_{IH} : satisfy
- (iv) V_{OH} : satisfy

(O : satisfy, X : not satisfy)

(b)

(i) V_{IL} : O , (ii) V_{OL} : X , (iii) V_{IH} : X , (iv) V_{OH} : O .

(c)

(i) V_{IL} : X , (ii) V_{OL} : O , (iii) V_{IH} : O , (iv) V_{OH} : O .