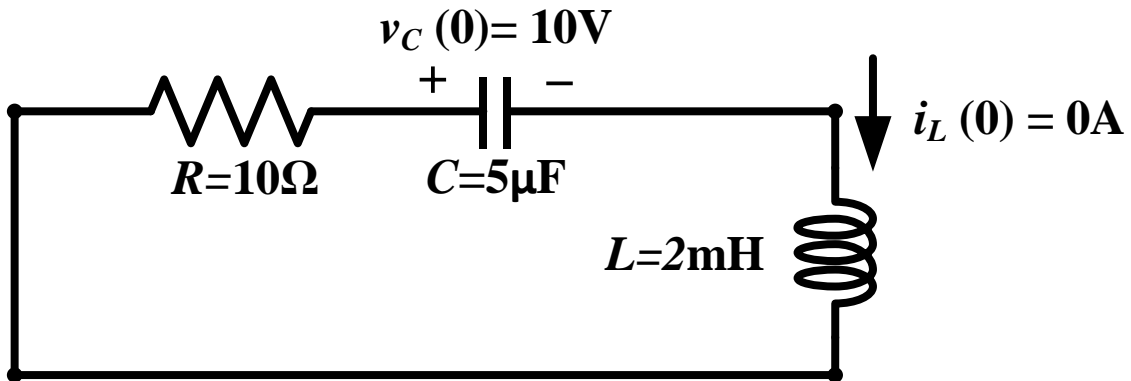



學號： _____

姓名： _____

For the circuit as shown in the following figure, assume the initial state of the capacitor $v_C(0)$ is 10V and that of inductor $i_L(0) = 0$ A, answer that following questions.



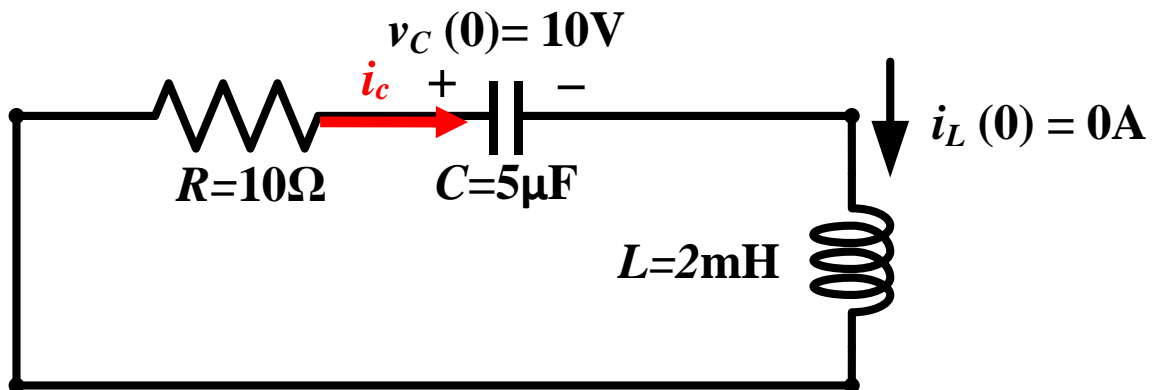- (1) Find the differential equation with constant coefficients for i_L (10%)
- (2) Find $i_L(0^+)$. (10%)
- (3) Find $\frac{di_L(0^+)}{dt}$. (10%)
- (4) Find the undamped natural frequency, ω_0 . (10%)
- (5) Find the damping factor, α . (10%)
- (6) Find the approximate damped-natural frequency, ω_d . (10%)
- (7) Find the approximate period of the ringing, T . (10%)
- (8) Find the quality factor, Q . (10%)
- (9) Sketch the zero-input response $i_L(t)$ for $t \geq 0$. (Label the key values in your sketch.) (20%)



To analysis the response for the undriven RLC circuit, we apply KVL to the loop first.

$$\text{KVL: } v_R + v_L + v_C = 0$$

$$v_R = i_L R, v_L = L \frac{di_L}{dt}, v_C = \frac{1}{C} \int i_C dt \Rightarrow i_C = C \frac{dv_C}{dt} \Rightarrow \frac{i_C}{C} = \frac{dv_C}{dt}$$

$$\Rightarrow i_L R + L \frac{di_L}{dt} + v_C = 0$$

By differentiating above equation with t , we have

$$\Rightarrow R \frac{di_L}{dt} + L \frac{d^2 i_L}{dt^2} + \frac{dv_C}{dt} = 0$$

$$\Rightarrow R \frac{di_L}{dt} + L \frac{d^2 i_L}{dt^2} + \frac{i_C}{C} = 0$$

where $i_L = i_C$ from KCL.

Let us rearrange terms to find the differential equation for i_L

$$\Rightarrow \frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{i_L}{LC} = 0$$

(1) Differential equation for i_L ,

$$\boxed{\frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{i_L}{LC} = 0}$$

(2) $i_L(0^+)$.

$$\boxed{i_L(0^+) = i_L(0^-) = 0\text{A}}$$

(3) $\frac{di_L(0^+)}{dt}$,

$$\boxed{\frac{di_L(0^+)}{dt} = \frac{-v_C(0^+)}{L} = \frac{v_L(0^+)}{L} = \frac{-10\text{V}}{2\text{mH}} = \frac{-10}{2 \times 10^{-3}} = -5000 \text{ rad/sec}}$$

The characteristic equation can be found from the following steps.

$$\frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{i_L}{LC} = s^2 A e^{st} + \frac{R}{L} s A e^{st} + \frac{1}{LC} A e^{st} = 0$$

$$\Rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = s^2 + 2\alpha s + \omega_0^2 = 0$$

$$(4) \omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2\text{mH} \times 5\mu\text{F}}} = \frac{1}{\sqrt{2 \times 10^{-3} \times 5 \times 10^{-6}}} = 10^4 \text{ rad/sec}$$

$$(5) 2\alpha = \frac{R}{L} \Rightarrow \alpha = \frac{R}{2L}$$

$$\alpha = \frac{R}{2L} = \frac{10\Omega}{2 \times 2\text{mH}} = \frac{10\Omega}{4 \times 10^{-3}} = 2500 \text{ rad/sec}$$

$\alpha < \omega_0 \Rightarrow$ under-damped

(6)


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9682.45 \text{ rad/sec. Note that } \omega_d \text{ is approximate equal to } \omega_0.$$

(7) The period $T \approx \frac{2\pi}{\omega_0} = 0.628\text{ms}$ approximately, or $T = \frac{2\pi}{\omega_d} = 0.648\text{ms}$ exactly.

(8) Finally, the quality factor Q is

$$Q = \frac{\omega_0}{2\alpha} = \frac{10000}{2 \times 2500} = 2.$$

(9)

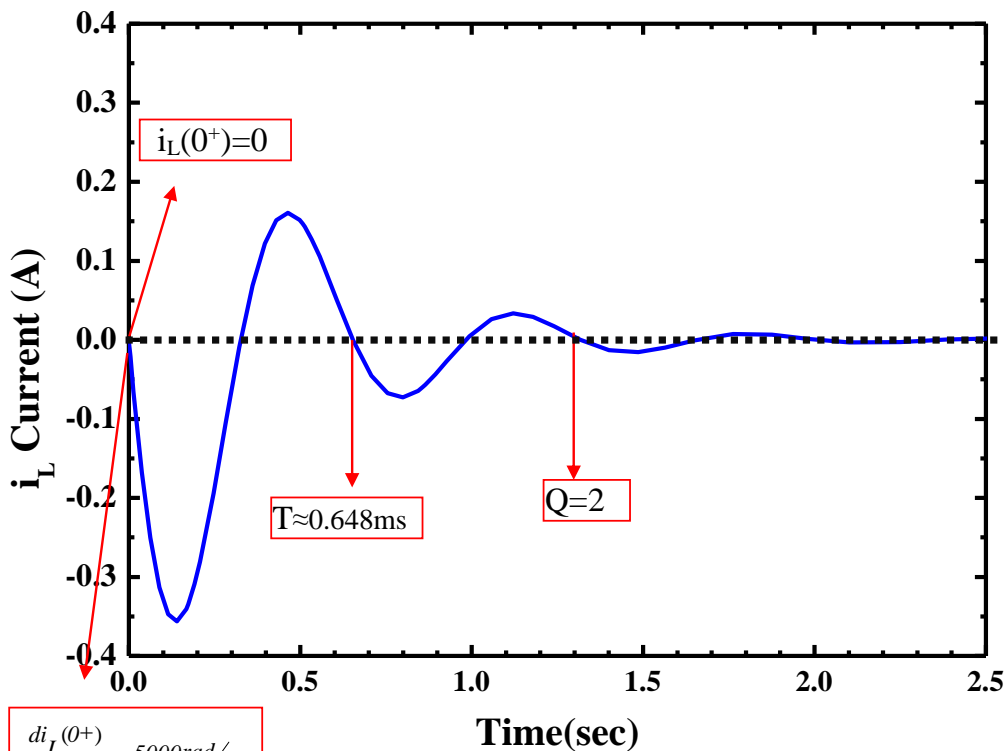

$$\frac{di_L(0^+)}{dt} = -5000 \text{ rad/sec}$$

Differential equation for i_L : $\frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{i_L}{LC} = 0,$

$i_L(0^+) = \underline{0 \text{ A}}, \frac{di_L(0^+)}{dt} = \underline{-5000 \text{ rad/sec}}, \omega_0 = \underline{10^4 \text{ rad/sec}},$

$\alpha = \underline{2500 \text{ rad/sec}}, \omega_d \approx \underline{9682.45 \text{ rad/sec}}, T \approx \underline{0.648\text{ms}}, Q = \underline{2}$