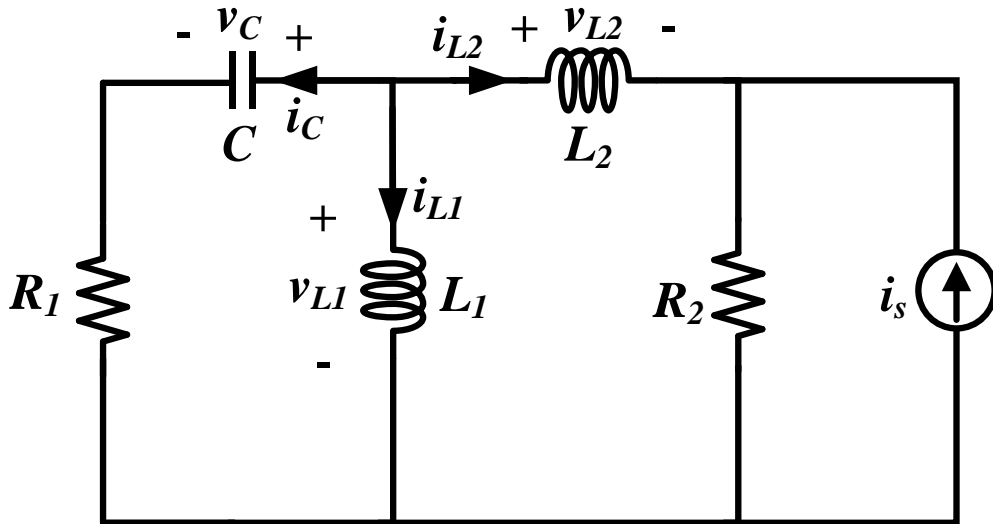


學號： \_\_\_\_\_


姓名： \_\_\_\_\_

By using superposition, find the state equation of inductance  $L_2$  for the circuit as shown.




This circuit we replace the capacitor by a voltage source and inductor by a current source.

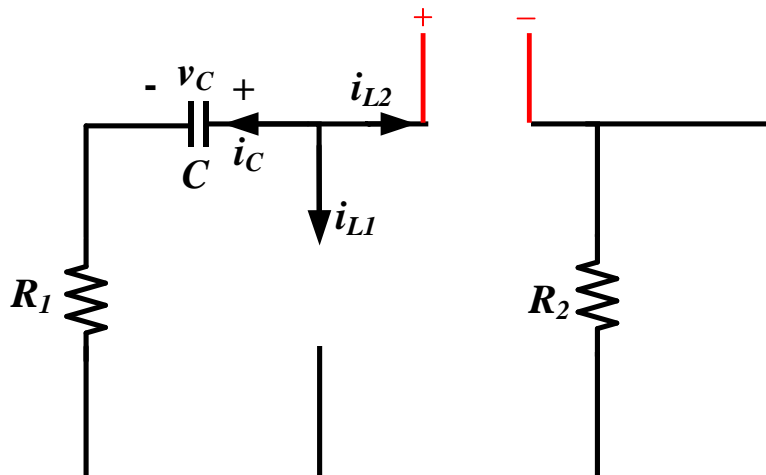(i) Using superposition for capacitance  $C$  :



$$v_{L2} = v_C$$

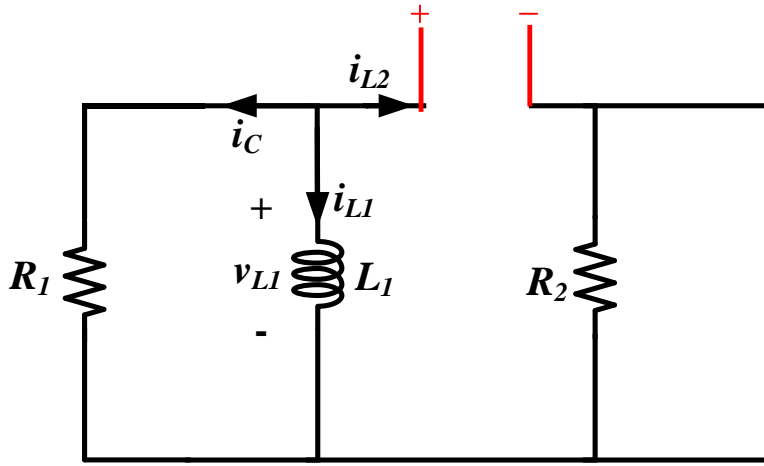
(ii) Using superposition for inductance  $L_1$  :



$$i_C = -i_{L1}$$

$$v_{L2} = -i_{L1}R_1$$

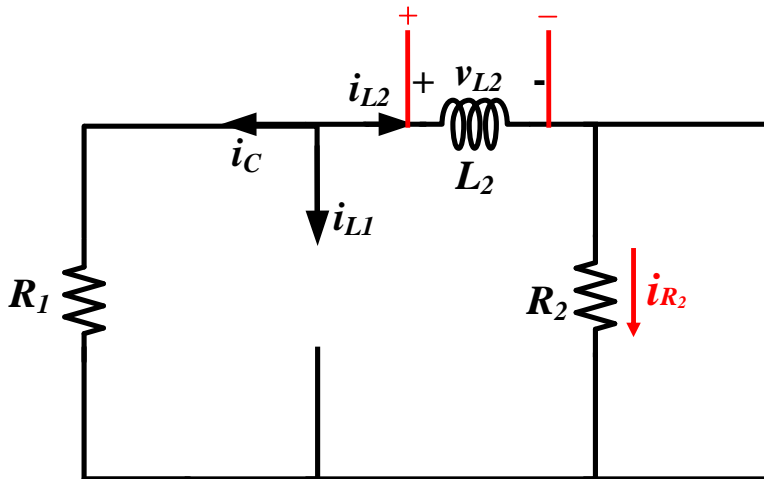
(iii) Using superposition for inductance  $L_2$  :



$$i_{R_2} = i_{L2}$$

$$v_{L2} = -i_{L2}(R_1 + R_2)$$

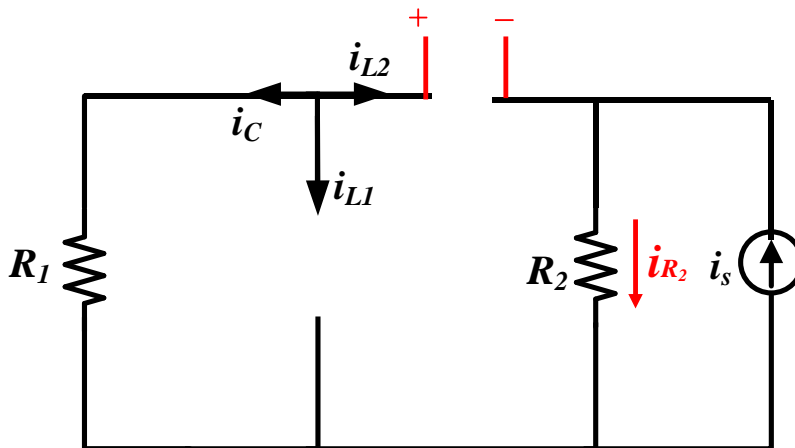(iv) Using superposition for inductance  $i_s$  :



$$i_{R_2} = i_s$$

$$v_{L2} = -i_s R_2$$

$$(v) \quad v_{L2} = L_2 \frac{di_{L2}}{dt} = v_c - i_{L1}R_1 - i_{L2}(R_1 + R_2) - i_s R_2$$

	$v_c$	$i_{L1}$	$i_{L2}$	$i_s$
$v_{L2} = L_2 \frac{di_{L2}}{dt}$	1	$-R_1$	$-(R_1 + R_2)$	$-R_2$

$$v_{L2} = L_2 \frac{di_{L2}}{dt} = v_c - i_{L1}R_1 - i_{L2}(R_1 + R_2) - i_s R_2$$