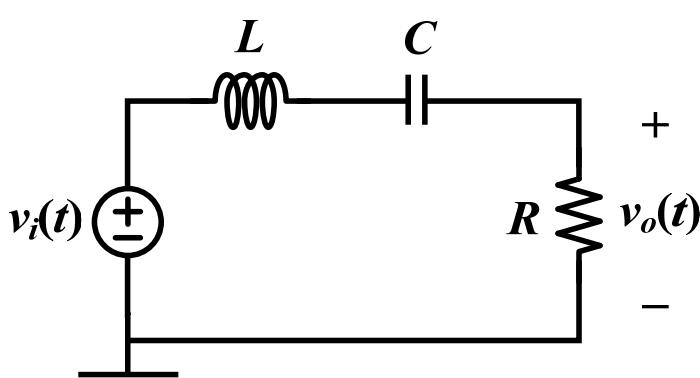


學號：_____

姓名：_____

Find the sinusoidal steady state $v_o(t)$ for the following circuit by

- convert the $v_i(t)$ in time domain into the frequency domain \mathbf{V}_i ,
- find the transfer function $\mathbf{H}(j\omega)$ in the frequency domain,
- find the numerical value of the $\mathbf{H}(j\omega)$ by plugging the frequency ω given in the figure,
- find the \mathbf{V}_o in the frequency domain from (a) and (c),
- convert the \mathbf{V}_o in the frequency domain into $v_o(t)$ in time domain.

(Assuming $L = 2 \text{ mH}$, $R = 2 \text{ k}\Omega$, $C = 0.2 \mu\text{F}$, and $v_i(t) = 5\cos(100t) + 1\cos(50000t) \text{ V.}$)

Solution:

(a)

$$v_i(t) = \operatorname{Re}\{\mathbf{V}_i e^{j\omega t}\} = \operatorname{Re}\{5e^{j0} e^{j100t} + 1e^{j0} e^{j50000t}\}$$

$$\therefore \mathbf{V}_i|_{\omega=100} = 5\text{V} \text{ and } \mathbf{V}_i|_{\omega=50000} = 1\text{V}$$

(b)

$$\mathbf{H}(j\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i}(j\omega) = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{1 + j\left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)} = \frac{1}{1 + j\left(\frac{\omega}{1 \times 10^6} - \frac{2500}{\omega}\right)}$$

$$\therefore |\mathbf{H}(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{1 \times 10^6} - \frac{2500}{\omega}\right)^2}}, \text{ and } \angle \mathbf{H}(j\omega) = -\tan^{-1}\left(\frac{\omega}{1 \times 10^6} - \frac{2500}{\omega}\right)$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = 50000 \text{ rads/sec}$$

(c)

For $\omega = 100$,

$$\mathbf{H}(j100) = 0.039e^{j(87.7^\circ)} \cong 0.04e^{j(90^\circ)}$$

For $\omega = 50000$,

$$\mathbf{H}(j50000) = 1e^{j(0^\circ)}$$

(d)

$$\mathbf{V}_o(j\omega)|_{\omega=100} = \mathbf{V}_i(j100) \times \mathbf{H}(j100) = 5e^{j(0^\circ)} \times 0.04e^{j(90^\circ)} = 0.2e^{j(90^\circ)}$$

$$\mathbf{V}_o(j\omega)|_{\omega=50000} = \mathbf{V}_i(j50000) \times \mathbf{H}(j50000) = 1e^{j(0^\circ)} \times 1e^{j(0^\circ)} = 1e^{j(0^\circ)}$$

(e)

$$v_o(t) = v_o(t)|_{\omega=100} + v_o(t)|_{\omega=50000} = 0.2 \cos(100t + 90^\circ) + 1 \cos(50000t + 0^\circ)$$

(a) \mathbf{V}_i (at $\omega = 100$ rads/sec) = _____,

\mathbf{V}_i (at $\omega = 50000$ rads/sec) = _____,

(b) $\mathbf{H}(j\omega) =$ _____,

(c) $\mathbf{H}(j\omega) = |\mathbf{H}| \angle \phi$

where $|\mathbf{H}|$ (at $\omega = 100$ rads/sec) = _____,

$|\mathbf{H}|$ (at $\omega = 50000$ rads/sec) = _____,

and ϕ (at $\omega = 100$ rads/sec) = _____,

ϕ (at $\omega = 50000$ rads/sec) = _____,

(d) \mathbf{V}_o (at $\omega = 100$ rads/sec) = _____,

\mathbf{V}_o (at $\omega = 50000$ rads/sec) = _____,

(e) $v_o(t) =$ _____.