

電路學(EE2210)第六次隨堂考

2015年4月29日


時間：10 分鐘

Close Book

學號： _____


姓名： _____

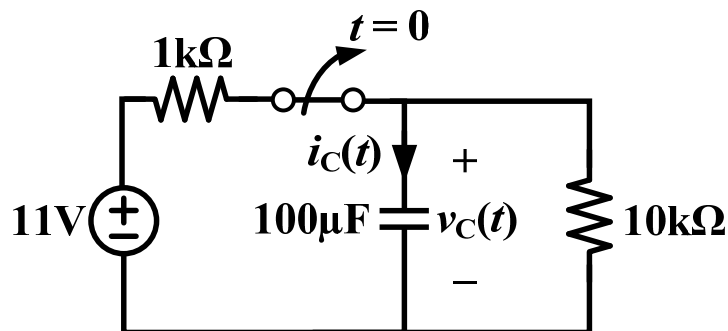For the circuit as shown in the following figure, the switch has been closed for a long time before it is opened at $t = 0$. Find $v_C(0^+)$ and $i_C(0^+)$, i.e. right after the switch is opened.




Solutions:

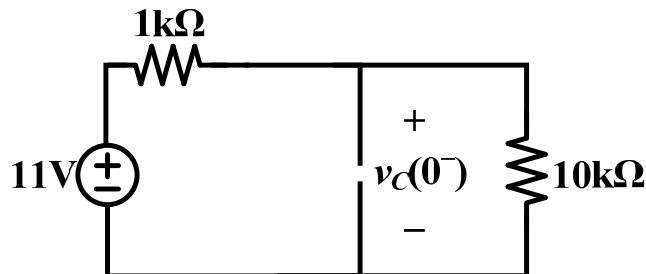Because the switch has been closed for a long time before $t = 0$, the capacitor can be regarded as open circuit, as shown as the following circuit.



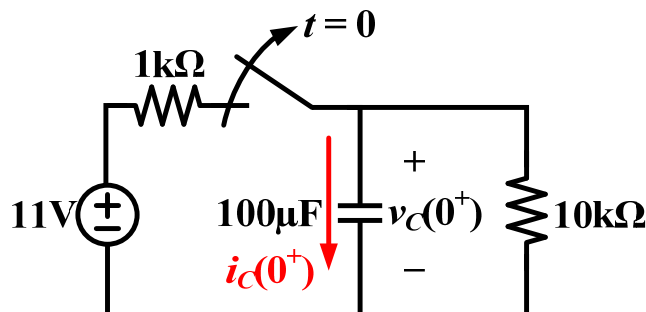After the switch is opened at $t = 0$, the circuit become



Since the voltage across the capacitor must be the same as the switch is opened, i.e. $v_C(0^+) = v_C(0^-)$, thus $v_C(0^+)$ and $i_C(0^+)$ can be found from the above two circuits.

$$v_C(0^+) = v_C(0^-) = 11 \times \frac{10\text{k}}{1\text{k} + 10\text{k}} = 10\text{V}$$

$$i_C(0^+) = -\frac{v_C(0^+)}{10\text{k}\Omega} = -1\text{mA}$$

$v_C(0^+) = \underline{\hspace{2cm} 10\text{V} \hspace{2cm}}, i_C(0^+) = \underline{\hspace{2cm} -1\text{mA} \hspace{2cm}}.$
--