


學號： \_\_\_\_\_

姓名： \_\_\_\_\_

For  $v_I(t)$  being sinusoidal input, please answer the following questions according to the circuit given below :

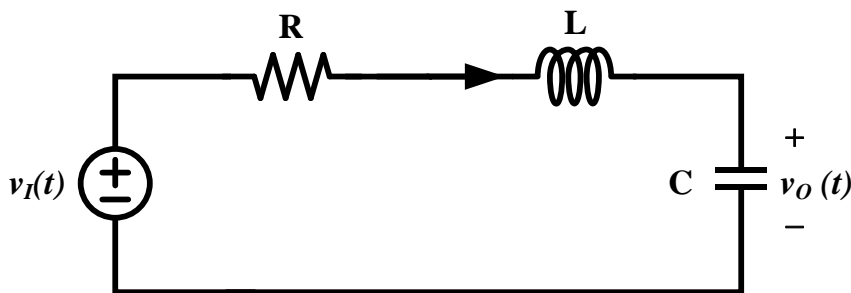- (a) Find the transfer function  $\mathbf{H}(j\omega) = \mathbf{V}_O(j\omega) / \mathbf{V}_I(j\omega)$ . (20%)
- (b) Find the resonant frequency  $\omega_0$ . (20%)
- (c) Find the quality factor  $Q$ . (20%)
- (d) Sketch the Bode plot of log magnitude versus log frequency (Please point out  $Q$ ,  $\omega_0$ , and slope in the plot). (40%)

(Assuming  $R = 5\Omega$ ,  $L = 250\text{mH}$  and  $C = 1\mu\text{F}$ )



Solution:

(a)

$$v_o = \frac{1}{j\omega C} \frac{1}{R + j\omega L + \frac{1}{j\omega C}} v_I$$

$$\mathbf{H}(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

(b)

To analysis the response for the undriven RLC circuit, we write KVL equation for its loop.

KVL:  $v_R + v_L + v_C = 0$

$$\Rightarrow i_C R + L \frac{di_L}{dt} + v_C = 0, \text{ where } i_L = i_C = C \frac{dv_C}{dt}$$

$$\Rightarrow RC \frac{dv_C}{dt} + LC \frac{d^2 v_C}{dt^2} + v_C = 0$$

$$\Rightarrow \frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0$$

Thus, the characteristic equation can be written as

$$s^2 + 2\alpha s + \omega_0^2 = s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Where

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{250\text{mH} \times 1\mu\text{F}}} = 2000\text{rad/sec}$$


$$\alpha = \frac{R}{2L} = \frac{5}{2 \times 250\text{mH}} = 10\text{rad/sec}$$

(c)

The quality factor is

$$Q = \frac{\omega_0}{2\alpha} = \frac{2000}{20} = 100$$

(d)

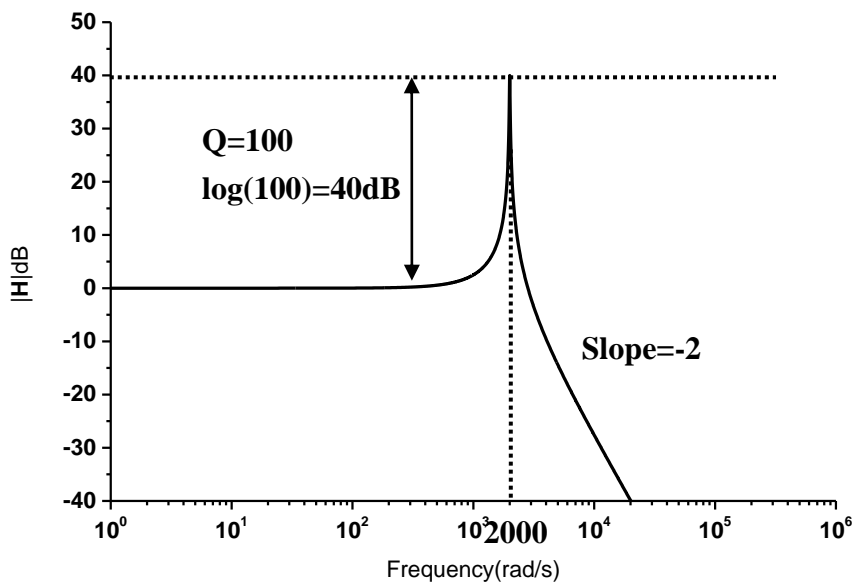

(a)  $\mathbf{H}(j\omega) =$  \_\_\_\_\_,

(b)  $\omega_0 =$  \_\_\_\_\_, (c)  $Q =$  \_\_\_\_\_,

(d)

