

電路學(EE2210)第一次隨堂考

2016年9月26日

時間：10 分鐘


Close Book

學號： _____

姓名： _____

For the circuit as shown below, there are six elements which observe the *Associated Variables Convention*. Among the eight elements, the voltages for four elements are given on the figure. The current for element a is $i_a = -3\text{A}$, for element e is $i_e = -6\text{A}$, for element d is $i_d = 2\text{A}$, and for element f is $i_f = 4\text{A}$. By using the KVL and KCL, please find

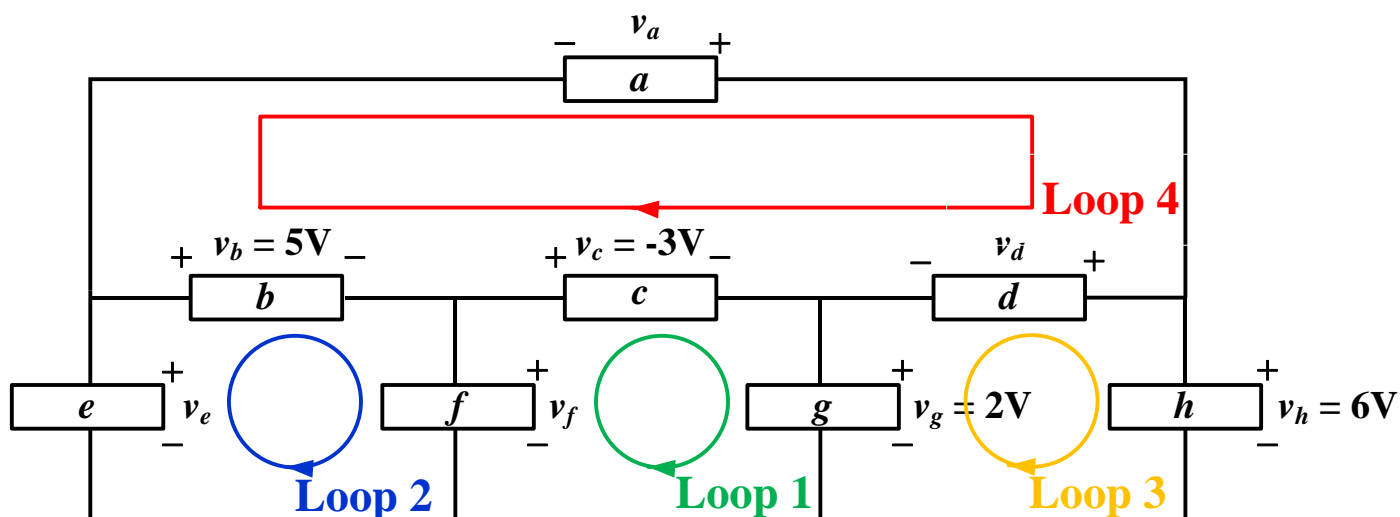- (i) the voltages of element a and e (v_a and v_e),
- (ii) the currents of element c and g (i_c and i_g),
- (iii) the power of element e (p_e).



Solutions:

(i)

Applying KVL to the two loops:

$$\begin{aligned} \text{Loop 1: } v_c + v_g - v_f &= 0 \\ \Rightarrow -3\text{V} + 2\text{V} - v_f &= 0 \\ \Rightarrow v_f &= -1\text{V} \end{aligned}$$

$$\begin{aligned} \text{Loop 2: } v_b + v_f - v_e &= 0 \\ \Rightarrow 5\text{V} - 1\text{V} - v_e &= 0 \\ \Rightarrow v_e &= 4\text{V} \end{aligned}$$

Loop 3: $-v_d + v_h - v_g = 0$


$\Rightarrow -v_d + 6V - 2V = 0$

$\Rightarrow v_d = 4V$

Loop 4: $-v_a + v_d - v_c - v_b = 0$

$\Rightarrow -v_a + 4V + 3V - 5V = 0$

$\Rightarrow v_a = 2V$

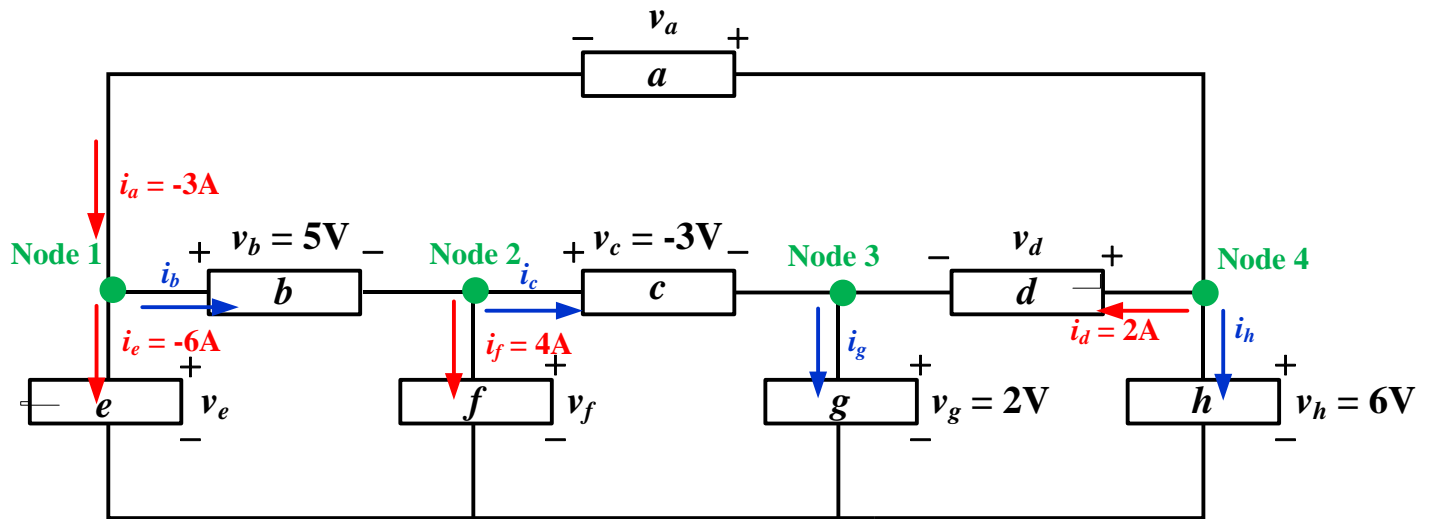

(ii)

Applying KCL to the two nodes:

Node 1: $i_a - i_e - i_b = 0$

$\Rightarrow -3A - (-6A) - i_b = 0$

$\Rightarrow i_b = 3A$

Node 2: $i_b - i_c - i_f = 0$

$\Rightarrow 3A - i_c - 4A = 0$

$\Rightarrow i_c = -1A$

Node 3: $i_c + i_d - i_g = 0$

$\Rightarrow -1A + 2A - i_g = 0$

$\Rightarrow i_g = 1A$

Node 4: $-i_d - i_a - i_h = 0$

$\Rightarrow -2A - (-3A) - i_h = 0$

$\Rightarrow i_h = 1A$

(iii)

$$p_e = v_e \times i_e = 4 \times (-6) = -24\text{W}$$

$$p = v \times i$$

$$p_a = 2 \times (-3) = -6\text{W}$$

$$p_b = 5 \times 3 = 15\text{W}$$

$$p_c = (-3) \times (-1) = 3\text{W}$$

$$p_d = 4 \times 2 = 8\text{W}$$

$$p_e = 4 \times (-6) = -24\text{W}$$

$$p_f = (-1) \times 4 = -4\text{W}$$

$$p_g = 2 \times 1 = 2\text{W}$$

$$p_h = 6 \times 1 = 6\text{W}$$

$$p_a + p_b + p_c + p_d + p_e + p_f + p_g + p_h = 0\text{W} \text{ (Power conservation in this circuit.)}$$

(i) $v_a =$ _____ 2V _____, $v_e =$ _____ 4V _____,

(ii) $i_c =$ _____ -1A _____, $i_g =$ _____ 1A _____,

(iii) $p_e =$ _____ -24W _____.
--