

電路學(EE2210)第二次隨堂考

2016年10月5日


時間：10 分鐘

Close Book

學號： _____

姓名： _____

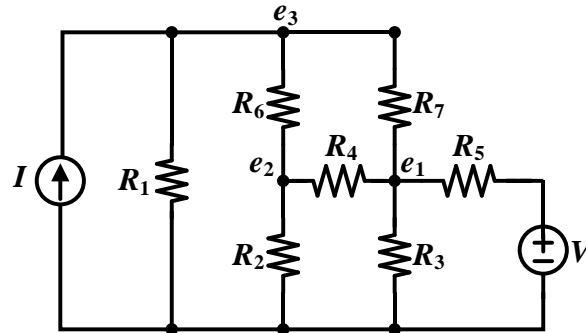The network shown below has three nodes with unknown node voltages e_1 , e_2 and e_3 . Use conductance instead of resistance to write the node equations. Simplify the equations by collecting terms and arranging them in the “standard” form for n linear equations in n unknowns. (*Do not solve the equations.*)




Matrix Form:
$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} S_1 \\ S_2 \\ S_3 \end{bmatrix}$$

$G_{11} =$ _____, $G_{12} =$ _____, $G_{13} =$ _____,

$G_{21} =$ _____, $G_{22} =$ _____, $G_{23} =$ _____,

$G_{31} =$ _____, $G_{32} =$ _____, $G_{33} =$ _____,

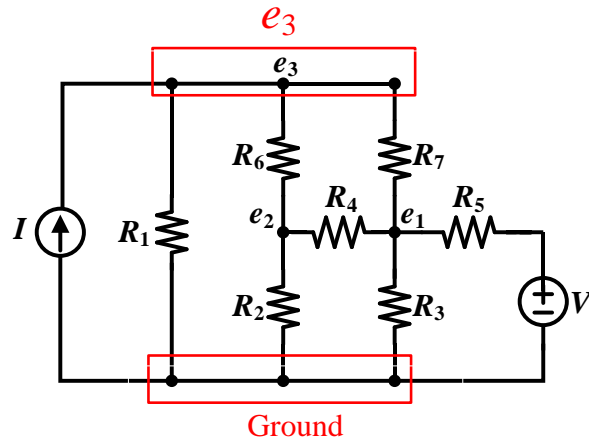$S_1 =$ _____, $S_2 =$ _____, $S_3 =$ _____,



Solutions:

(i) KCL equations:

$$\text{node } e_1: G_5(V - e_1) + G_3(0 - e_1) + G_4(e_2 - e_1) + G_7(e_3 - e_1) = 0$$

$$\text{node } e_2: G_4(e_1 - e_2) + G_2(0 - e_2) + G_6(e_3 - e_2) = 0$$

$$\text{node } e_3: G_6(e_2 - e_3) + G_7(e_1 - e_3) + I + G_1(0 - e_3) = 0$$

(ii) n linear equations:

$$\begin{cases} (G_3 + G_4 + G_5 + G_7)e_1 + (-G_4)e_2 + (-G_7)e_3 = G_5V \\ (-G_4)e_1 + (G_2 + G_4 + G_6)e_2 + (-G_6)e_3 = 0 \\ (-G_7)e_1 + (-G_6)e_2 + (G_1 + G_6 + G_7)e_3 = I \end{cases}$$

(iii) Matrix form:

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} S_1 \\ S_2 \\ S_3 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} (G_3 + G_4 + G_5 + G_7) & (-G_4) & (-G_7) \\ (-G_4) & (G_2 + G_4 + G_6) & (-G_6) \\ (-G_7) & (-G_6) & (G_1 + G_6 + G_7) \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} G_5V \\ 0 \\ I \end{bmatrix}$$

or

$$\Rightarrow \begin{bmatrix} -(G_3 + G_4 + G_5 + G_7) & (G_4) & (G_7) \\ (G_4) & -(G_2 + G_4 + G_6) & (G_6) \\ (G_7) & (G_6) & -(G_1 + G_6 + G_7) \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} -G_5V \\ 0 \\ -I \end{bmatrix}$$