

電路學(EE2210)第五次隨堂考

2016年11月02日


時間：10 分鐘

Close Book

學號： \_\_\_\_\_


姓名： \_\_\_\_\_

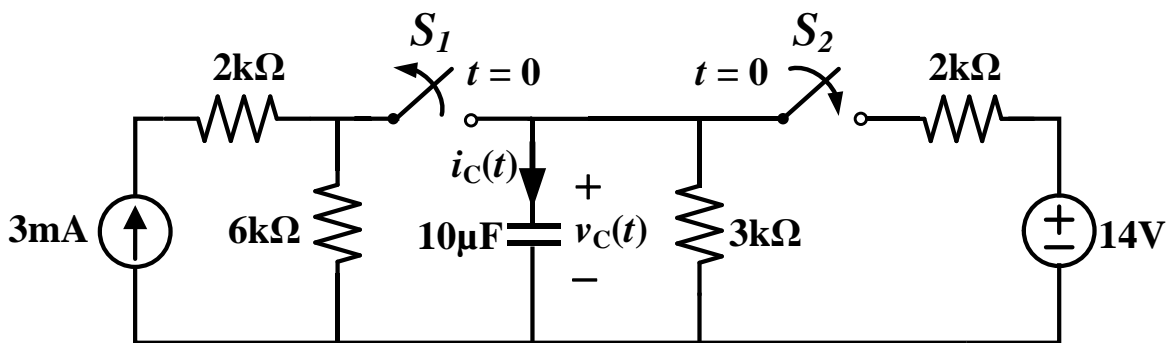For the circuit as shown in the following figure, the switch  $S_1$  has been closed for a long time before it is opened at  $t = 0$  and the switch  $S_2$  has been opened for a long time before it is closed at  $t = 0$ . Find  $v_C(0^+)$  and  $i_C(0^+)$ .




Solutions:

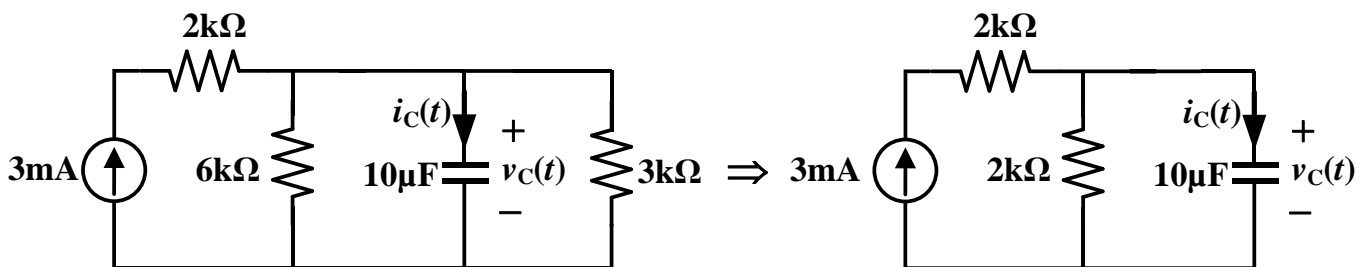Because the switch  $S_2$  has been closed for a long time before  $t = 0$ , the capacitor can be regarded as opened terminal, the equivalent circuit is



$$v_C(0^+) = v_C(0^-) = 3mA \times 2k\Omega = 6V$$

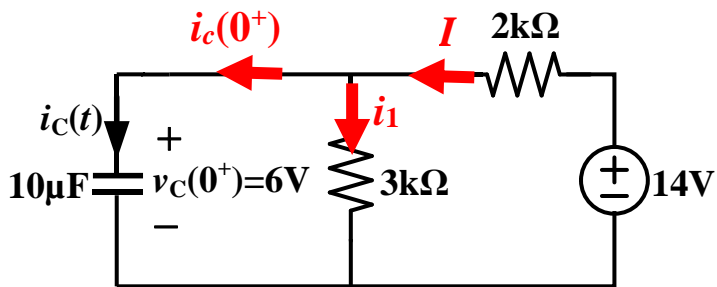After the switch  $S_2$  is closed at  $t = 0$ , and switch  $S_1$  is opened, the equivalent circuit is



$$i_1 = \frac{6\text{V}}{3\text{k}\Omega} = 2\text{mA}$$

$$I = \frac{14\text{V} - 6\text{V}}{2\text{k}\Omega} = 4\text{mA}$$

$$i_C(0^+) = 4 - 2 = 2\text{mA}$$

$v_C(0^+) = \underline{\hspace{2cm}} 6\text{V} \underline{\hspace{2cm}}, i_C(0^+) = \underline{\hspace{2cm}} 2\text{mA} \underline{\hspace{2cm}}.$