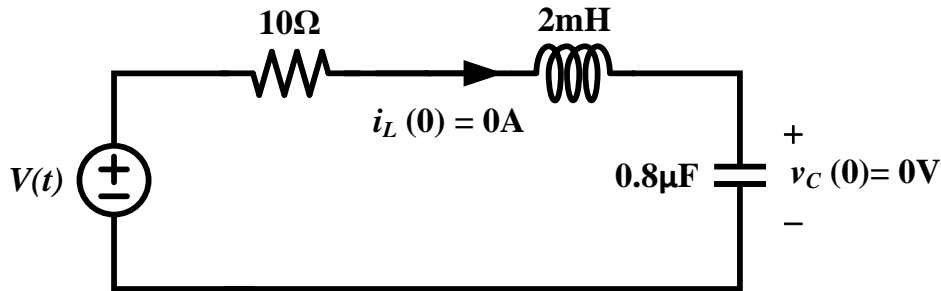


學號： _____

姓名： _____

For the following circuit as shown, assume $V(t) = V_I u(t)$, $V_I = 5V$, the initial state of the capacitor $v_C(0)$ is $0V$ and that of inductor $i_L(0) = 0A$, answer that following questions.



- (1) Find the undamped natural frequency, ω_0 . (15%)
- (2) Find the damping factor, α . (15%)
- (3) Find the approximate damped-natural frequency, ω_d . (15%)
- (4) Find the approximate period of the ringing, T . (15%)
- (5) Find the quality factor, Q . (15%)
- (6) Sketch $v_C(t)$ for $t \geq 0$. (25%)

To analysis the response for the undriven RLC circuit, we write KVL equation for its loop.

KVL: $v_R + v_L + v_C = 0$

$$\Rightarrow i_C R + L \frac{di_L}{dt} + v_C = 0, \text{ where } i_L = i_C = C \frac{dv_C}{dt}$$

$$\Rightarrow RC \frac{dv_C}{dt} + LC \frac{d^2 v_C}{dt^2} + v_C = 0$$

$$\Rightarrow \frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0$$

Thus, the characteristic equation can be written as

$$s^2 + 2\alpha s + \omega_0^2 = s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Where

$$(1) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2mH \times 0.8\mu F}} = 25000 \text{ rads/sec}$$


$$(2) \alpha = \frac{R}{2L} = \frac{10}{2 \times 2m} = 2500 \text{ rads/sec}$$

$\therefore \alpha < \omega_0 \Rightarrow$ under-damped dynamics

$$(3) \omega_d \text{ is approximate equal to } \omega_0, \text{ or the accurate value is } \omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx 24874.69 \text{ rads/sec}.$$

$$(4) \text{ Thus, the period is } T = \frac{2\pi}{\omega_0} = 0.251 \text{ msec}, \text{ or the accurate value is } T = \frac{2\pi}{\omega_d} = 0.252 \text{ msec}$$

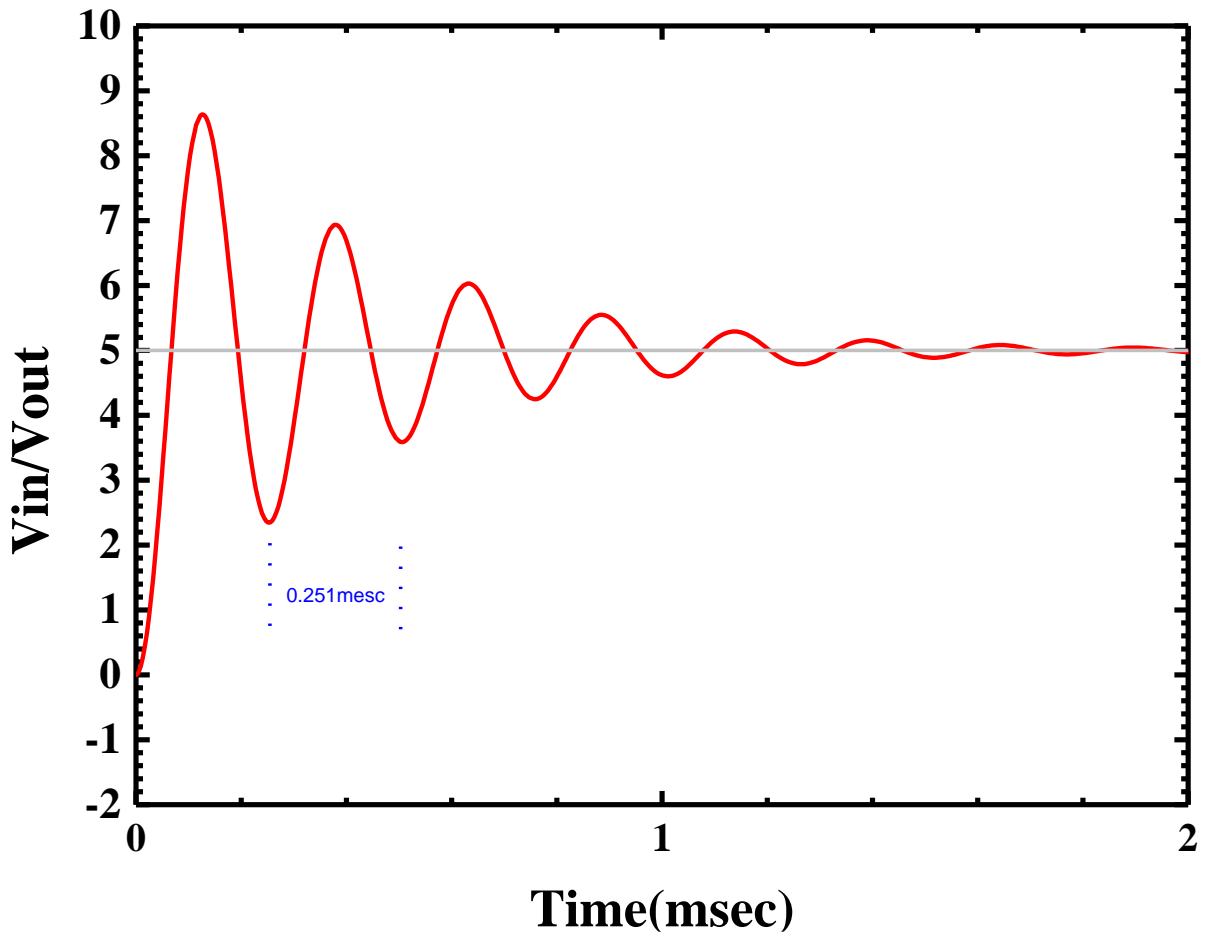(5) The quality factor is $Q = \frac{\omega_0}{2\alpha} = 5$.



$\omega_0 =$ 25000rad/sec, $\alpha =$ 2500 rad/sec, $\omega_d \approx$ 24874.69rad/sec,
 $T \approx$ 0.251msec, $Q =$ 5,

