

學號： _____

姓名： _____

Find the sinusoidal steady state $v_o(t)$ for the following circuit by


(a) find the transfer function $\mathbf{H}(j\omega)$.

(b) find the numerical complex value of the $\mathbf{H}(j\omega)$ for $\omega=4$ rad/s and $\omega=4000$ rad/s.

(c) find $v_o(t)$ for $\omega=4$ rad/s and $v_o(t)$ $\omega=4000$ rad/s.

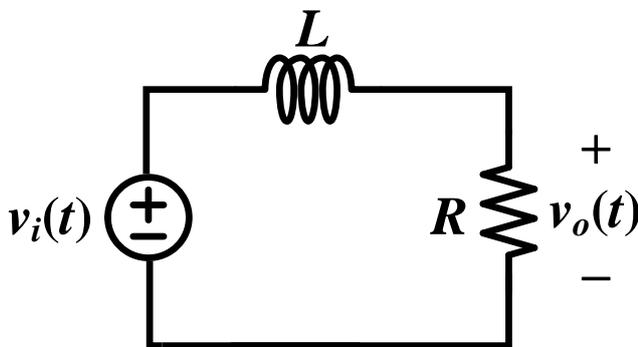(d) find $v_o(t)$.

(Assuming $R=4\Omega$, $L=1\text{H}$, and $v_i(t)=10\cos(4t)+10\cos(4000t)$ V.)



Solution:

(a)

$$\mathbf{H}(j\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i}(j\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}}$$

(b)

$$\mathbf{H}(j\omega) = |\mathbf{H}| \angle \phi$$

$$|\mathbf{H}(j\omega)| = \frac{1}{\sqrt{1^2 + (\frac{\omega}{4})^2}} \quad \text{and} \quad \phi = \angle \mathbf{H}(j\omega) = -\tan^{-1}(\frac{\omega}{4})$$

$$|\mathbf{H}(j\omega)|_{\omega=4} = \frac{1}{\sqrt{1^2 + (\frac{4}{4})^2}} = \frac{1}{\sqrt{2}} \approx 0.707$$

$$|\mathbf{H}(j\omega)|_{\omega=4000} = \frac{1}{\sqrt{1^2 + (\frac{4000}{4})^2}} = \frac{1}{\sqrt{1000001}} \approx 0.001$$

$$\angle \mathbf{H}(j\omega)_{\omega=4} = -\tan^{-1}\left(\frac{4}{4}\right) = -45^\circ$$

$$\angle \mathbf{H}(j\omega)_{\omega=4000} = -\tan^{-1}\left(\frac{4000}{4}\right) = -89.94^\circ \approx -90^\circ$$

(c)

$$v_o(t)|_{\omega=4} = 5\sqrt{2} \cos(4t - 45^\circ) \text{ V}$$

$$v_o(t)|_{\omega=4000} = 0.01 \cos(4000t - 90^\circ) \text{ V}$$

(d)

$$\begin{aligned} v_o(t) &= v_o(t)|_{\omega=4} + v_o(t)|_{\omega=4000} \\ &= 5\sqrt{2} \cos(4t - 45^\circ) + 0.01 \cos(4000t - 90^\circ) \text{ V} \end{aligned}$$

(a) $\mathbf{H}(j\omega) =$ _____,

(b) $\mathbf{H}(j\omega) = |\mathbf{H}| \angle \phi$

where $|\mathbf{H}|$ (at $\omega = 4$ rad/s) = _____,

$|\mathbf{H}|$ (at $\omega = 4000$ rad/s) = _____,

and ϕ (at $\omega = 4$ rad/s) = _____,

ϕ (at $\omega = 4000$ rad/s) = _____,

(c) $v_o(t)$ (for $\omega = 4$ rad/s) = _____,

$v_o(t)$ (for $\omega = 4000$ rad/s) = _____,

(d) $v_o(t) =$ _____.