

# Energy and Power

Chenhsin Lien and Po-Tai Cheng

CENTER FOR ADVANCED POWER TECHNOLOGIES

Dept. of Electrical Engineering

National Tsing Hua University

Hsinchu, TAIWAN





# CAPT

Center for Advanced Power Technologies  
National Tsing Hua University, TAIWAN

# Why worry about energy?



## ● Portability

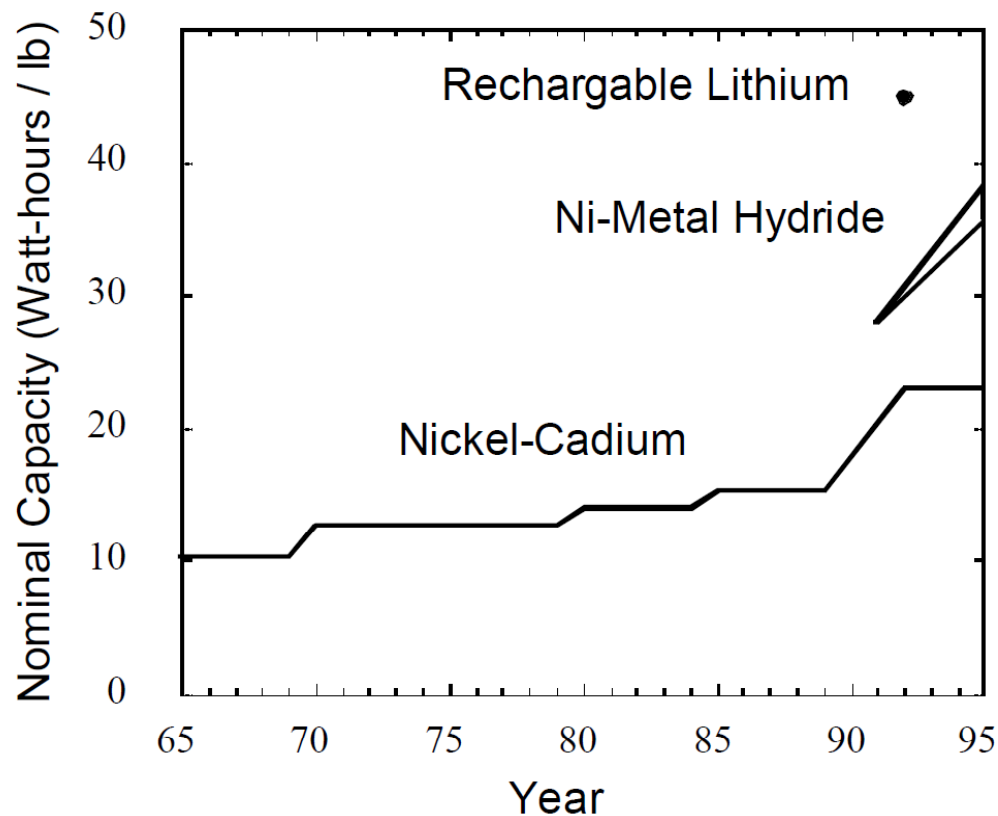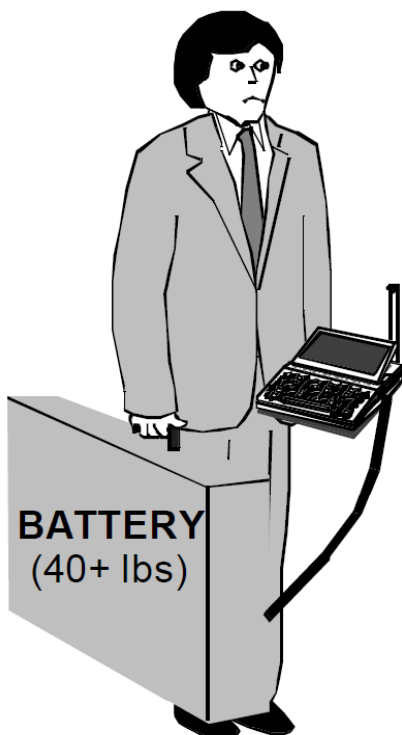


## ● Want to learn about.

- How long will the battery last? (1) in stand-by mode. (2) in active use.
- Will the chip overheat and self-destruct?

# Energy Dissipation in MOSFET Gates



- For the logic gate below:

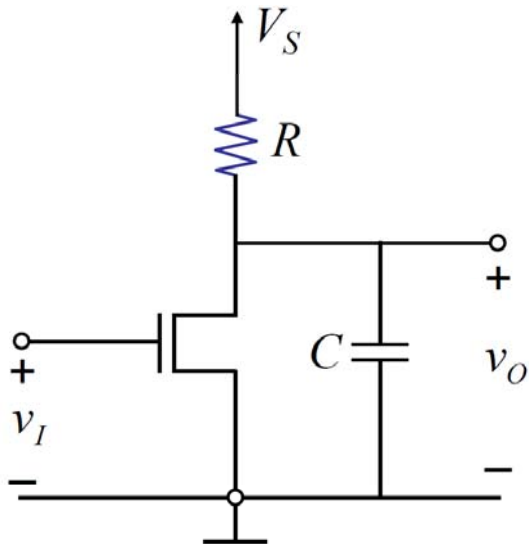


$$C = C_{Wire} + C_{GS}$$

- Let us determine *standby power* and *active use power*.
- Let's work out a few related examples first.

# Example #1



- The Circuit #1

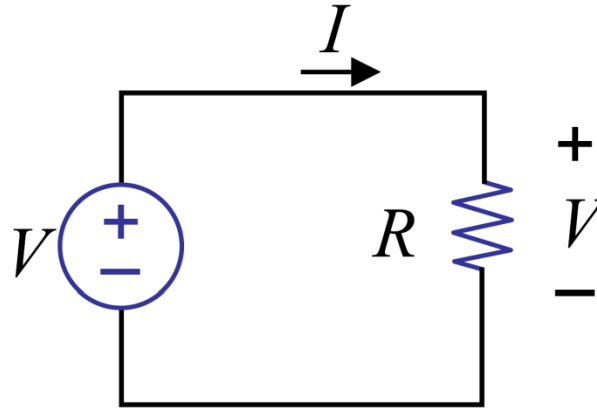

- Power  $P$ .

$$P = VI = \frac{V^2}{R}$$


- Energy dissipated in time  $T$ .

$$E = VIT = \frac{V^2}{R}T$$


# Example #1



- Applying to our gate

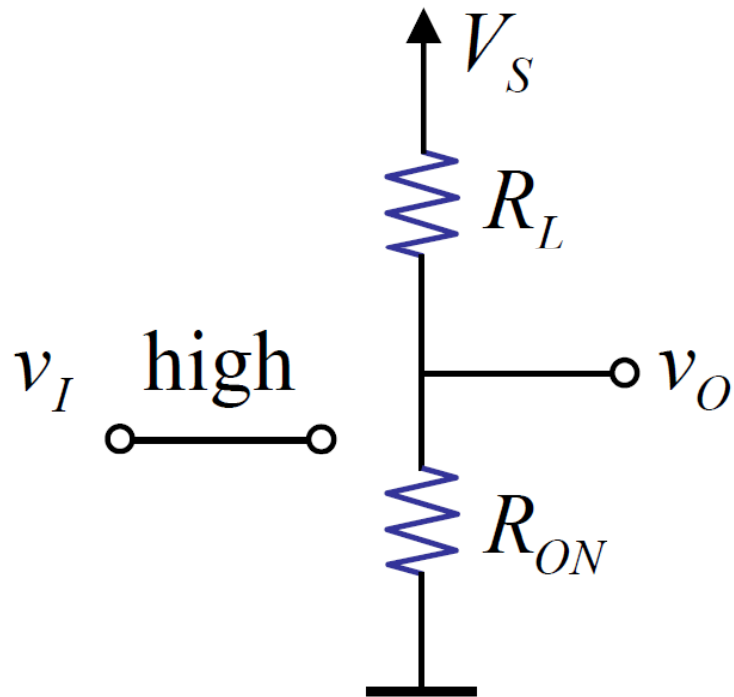

$$P = \frac{V_S^2}{R_L + R_{ON}}$$


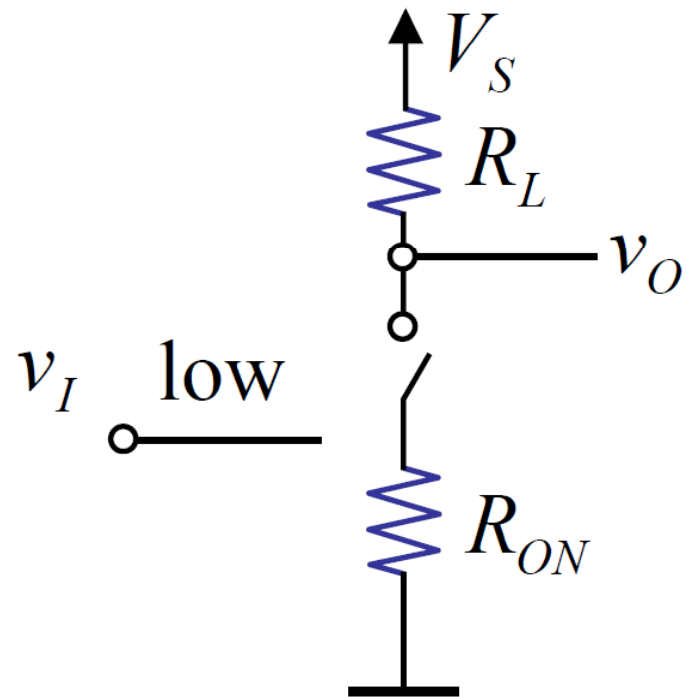


$$P = 0$$

# Example #2



## The Circuit #2

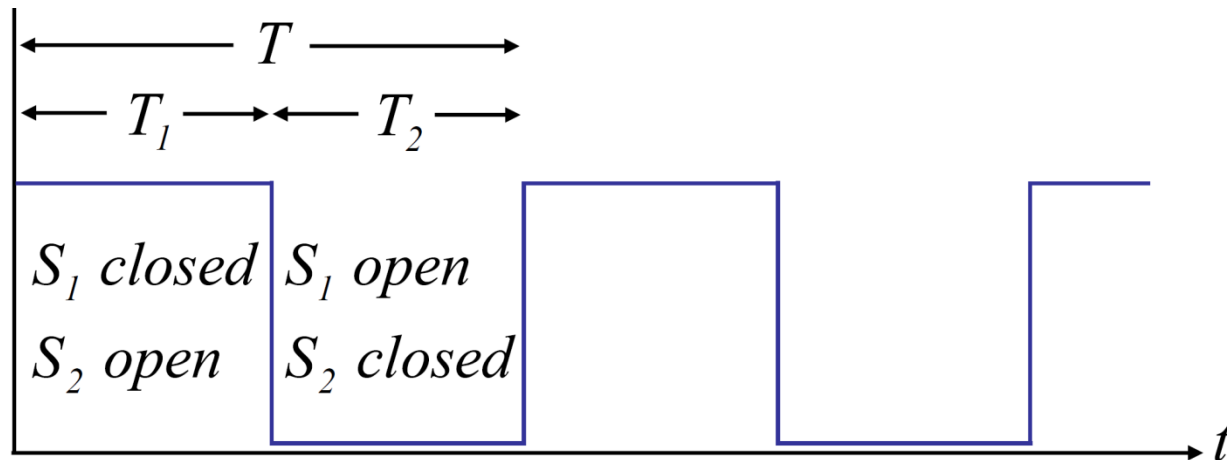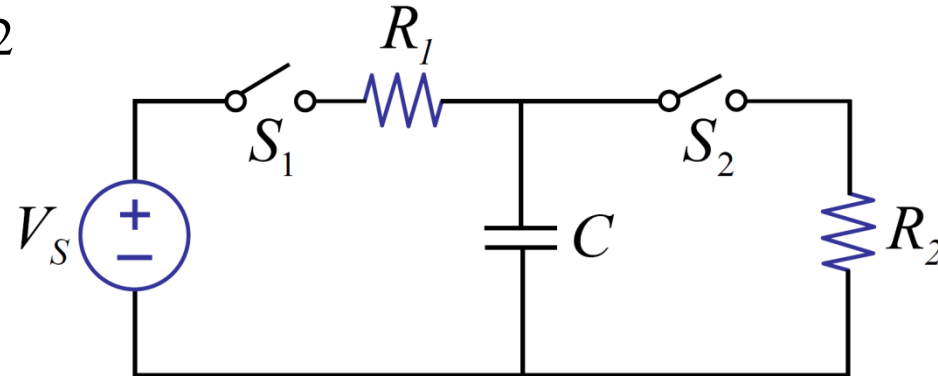


- Find energy dissipated in each cycle.
- Find average power  $\bar{P}$ .


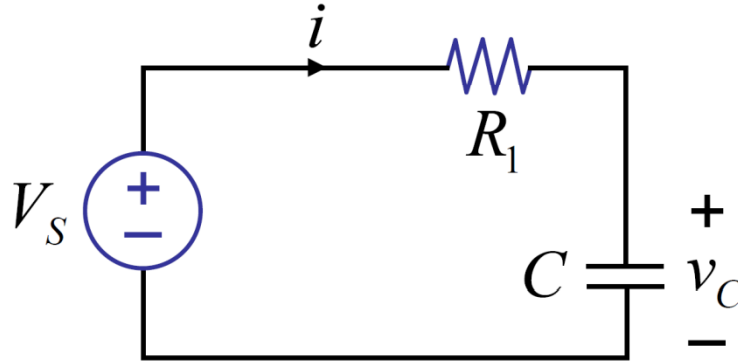
## Example #2



- During  $T_1$ :  $S_1$  closed,  $S_2$  open.



- Assume  $v_C = 0$  at  $t = 0$ .

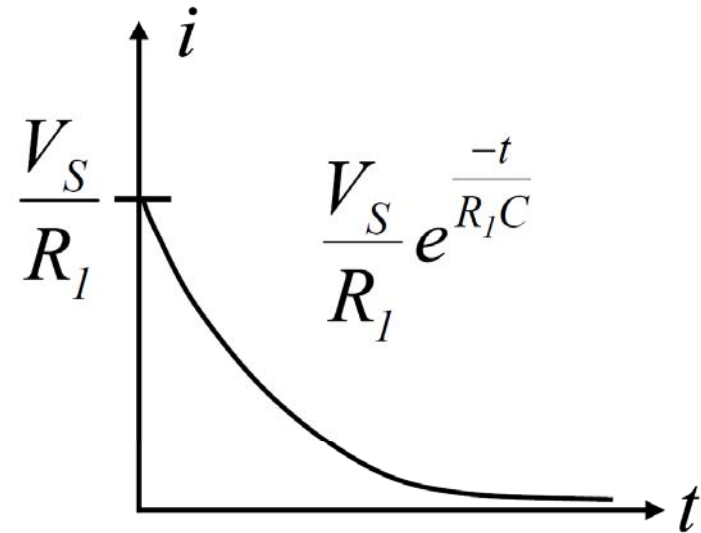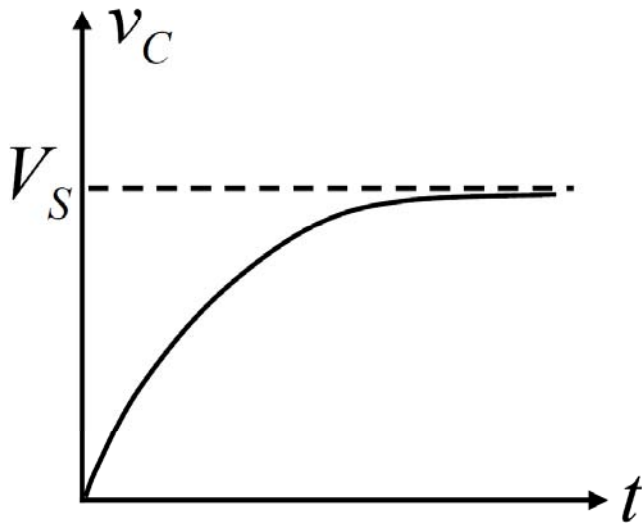

# Total energy



- Total energy provided by source during  $T_1$ :

$$E = \int_0^{T_1} V_S i dt = \int_0^{T_1} \frac{V_S^2}{R_1} e^{-\frac{t}{R_1 C}} dt = -\frac{V_S^2}{R_1} R_1 C e^{-\frac{t}{R_1 C}} \Big|_0^{T_1}$$

$$E = CV_S^2 \left( 1 - e^{-\frac{T_1}{R_1 C}} \right)$$

$$E \approx CV_S^2 \quad \text{if } T_1 \gg R_1 C, \text{ i.e. if we wait long enough}$$

- $\frac{1}{2} CV_S^2$  stored in capacitor.

- $E_1 = CV_S^2 - \frac{1}{2} CV_S^2 = \frac{1}{2} CV_S^2$  dissipated in  $R_1$ .


*Independent of R!!*


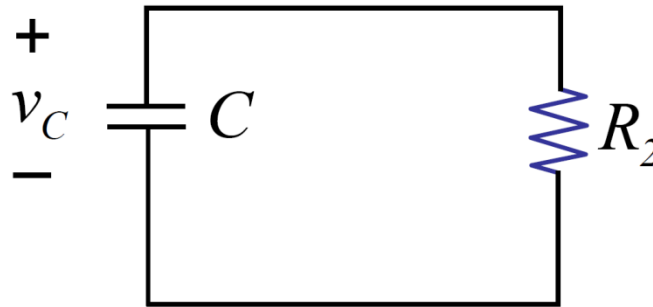
## Example #2



- During  $T_2$ :  $S_2$  closed,  $S_1$  open.



- Initially,  $v_C = V_s$ . (Recall  $T_1 \gg R_1 C$ ).
- So, initially, energy stored in capacitor is  $\frac{1}{2} C V_s^2$ .
- Assume  $T_2 \gg R_1 C$ .
- Thus, capacitor discharges about fully in  $T_2$ .
- Thus, energy dissipated in  $R_2$  during  $T_2$  is  $E_2 = \frac{1}{2} C V_s^2$ .
- Both  $E_1$  and  $E_2$  are independent of  $R_1$  and  $R_2$ !

## Example #2



- Putting the two periods,  $T_1$  and  $T_2$ , together.
- We have energy dissipated in each cycle

$$E = E_1 + E_2 = \frac{1}{2} CV_s^2 + \frac{1}{2} CV_s^2$$

$$E = CV_s^2$$

- $E$  is the energy dissipated in charging and discharging capacitor  $C$ .  
Assumes  $C$  charges and discharges fully.
- The average power is :



$$\bar{P} = \frac{E}{T} = \frac{CV_s^2}{T} = CV_s^2 f$$

- Where  $f = \frac{1}{T}$  is the frequency.

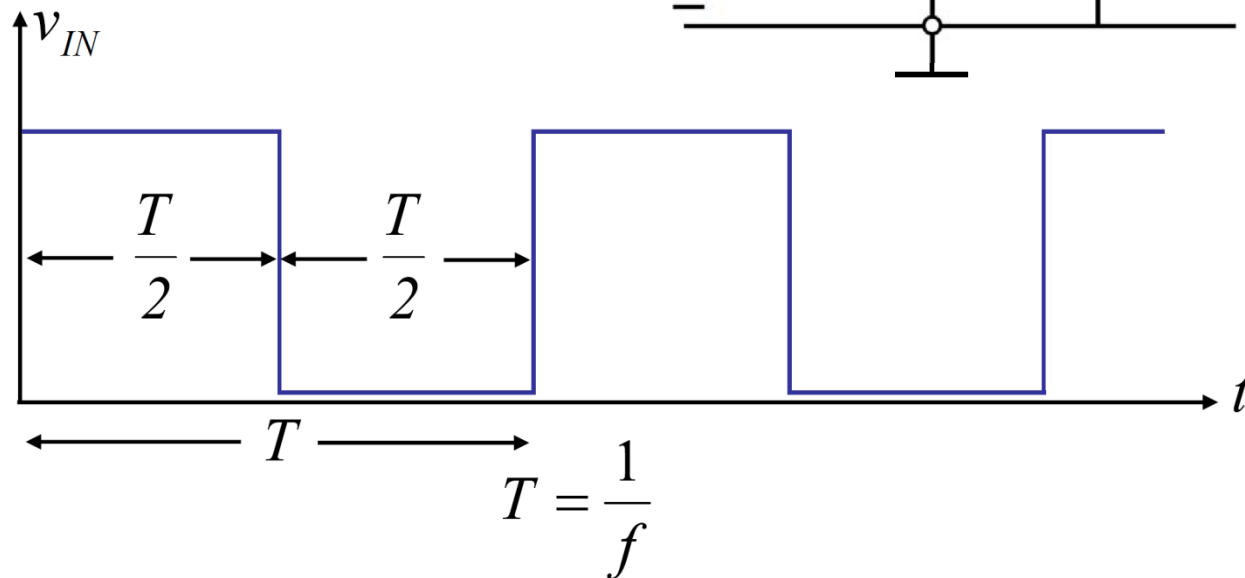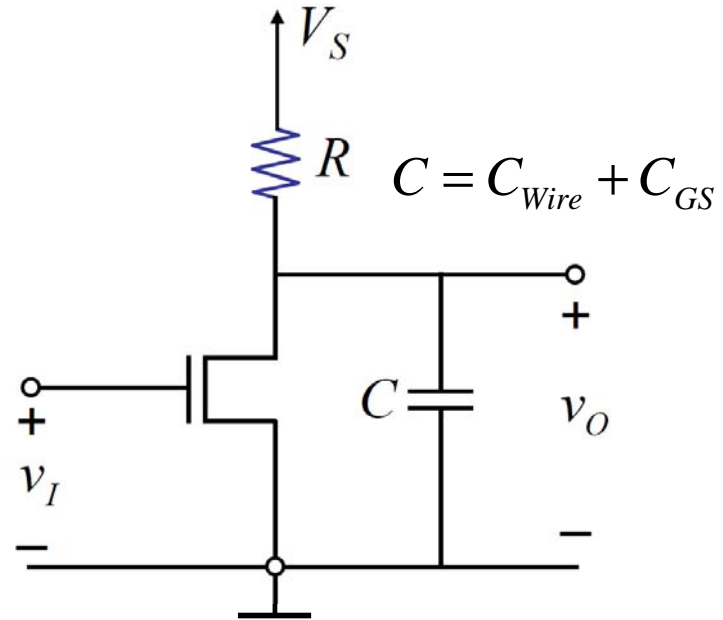
# Back to our inverter




- What is  $\bar{P}$  for the following input?




# Equivalent Circuit

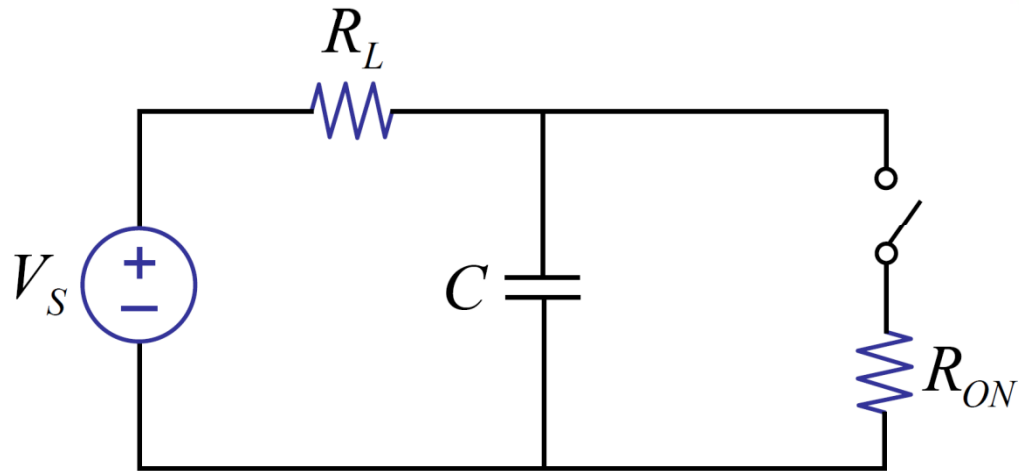

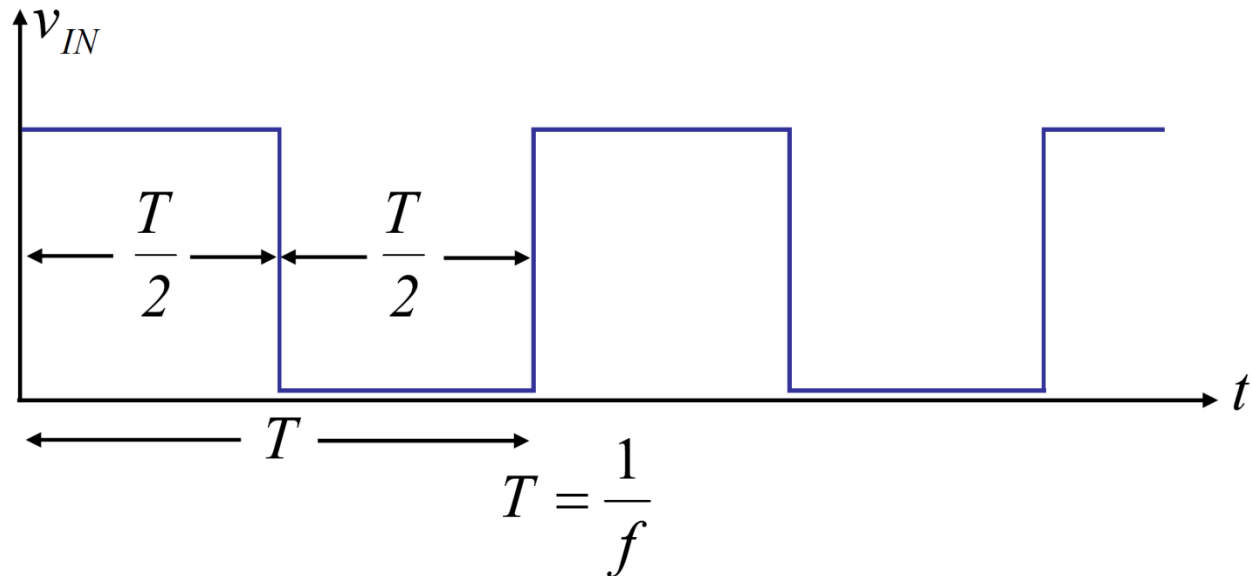• What is  $\bar{P}$  for the following input?



# S Closed

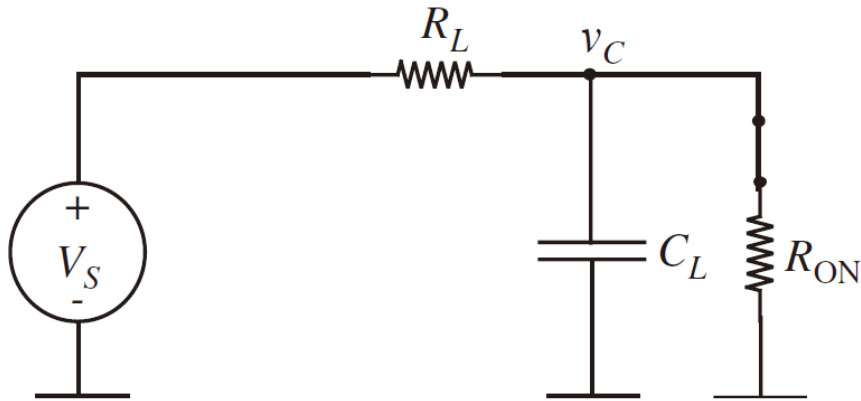


$$p(t) = \frac{(V_S - v_C(t))^2}{R_L} + \frac{v_C^2(t)}{R_{on}}$$

$$w_1 = \int_0^{T_1} p(t) dt$$


• Thévenin equivalent circuit
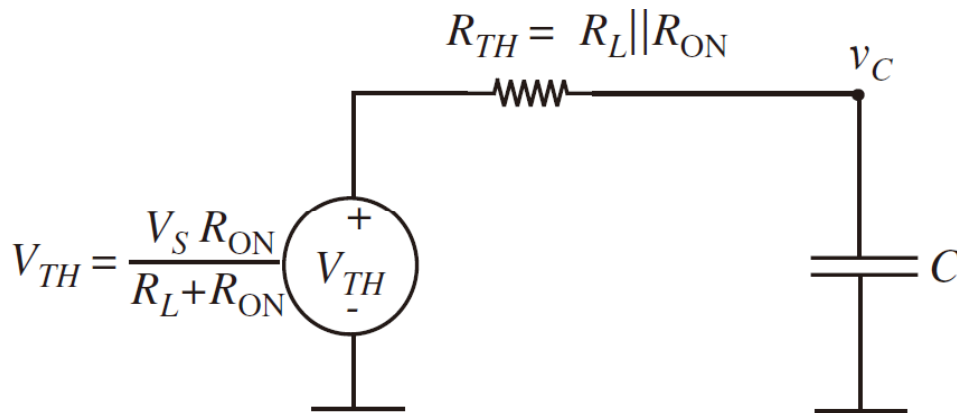
$$w_1 = \frac{V_S^2}{R_L + R_{ON}} T_1 + CV_S^2 \frac{R_L^2}{2(R_L + R_{ON})^2}$$



$$v_C = V_{TH} + (V_S - V_{TH}) e^{-\frac{t}{R_{TH}C}}$$

# S Opened

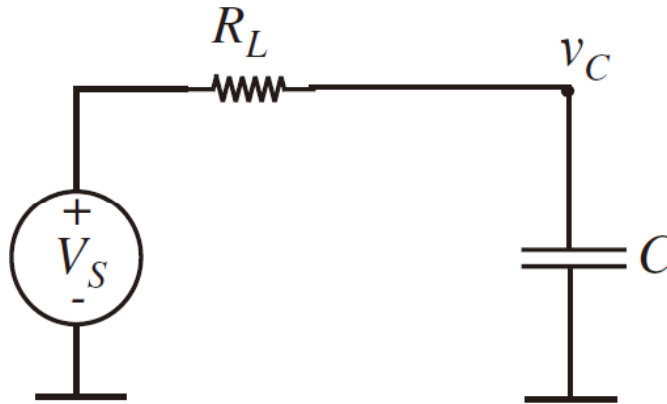

- Energy dissipated in  $R_L$ .

$$v_c = V_{TH} + (V_s - V_{TH})(1 - e^{-\frac{t}{R_L C}}) \quad w_2 = CV_s^2 \frac{R_L^2}{2(R_L + R_{ON})^2}$$

$$p(t) = \frac{(V_s - v_c(t))^2}{R_L}$$

# What is $\bar{P}$ for gate?



- $\bar{P}$  for gate is:

$$\bar{P} = \frac{w_1 + w_2}{T} = \frac{V_S^2}{2(R_L + R_{ON})} + CV_S^2 f \frac{R_L^2}{(R_L + R_{ON})^2}$$

- When  $R_L \gg R_{ON}$

$$\bar{P} = \frac{V_S^2}{2R_L} + CV_S^2 f$$

- The first term  $\bar{P}_{Static} = \frac{V_S^2}{2R_L}$  is called static power dissipation (independent of  $f$ ). The MOSFET is ON half of the time.
- The second term  $\bar{P}_{Dynamic} = CV_S^2 f$  is called dynamic power dissipation (proportional to  $f$  and  $C$ ).

# Standby Mode



- When  $R_L \gg R_{ON}$

$$\bar{P} = \frac{V_S^2}{2R_L} + CV_S^2 f$$

- In standby mode,  $f \rightarrow 0$  and dynamic power is 0.

- Thus,  $\bar{P}_{\text{Standby}} = \frac{V_S^2}{2R_L}$

- From above, in standby mode, half the gates in a chip can be assumed as be on.

- Standby power and active power

$$\bar{P} = \bar{P}_{\text{Standby}} + \bar{P}_{\text{Active}} = \frac{V_S^2}{2R_L} + CV_S^2 f$$



# Some numbers



- A chip with  $10^6$  gates clocking at 100 MHz.
- Assume  $C = 1$  fF,  $R_L = 10$  k $\Omega$ , and  $V_S = 5$  V.

$$\bar{P} = 10^6 \times \left( \frac{V_S^2}{2R_L} + CV_S^2 f \right)$$

$$\bar{P} = 10^6 \times \left( \frac{5^2}{2 \times 10^4} + 10^{-15} \times 5^2 \times 10^8 \right)$$

$$\bar{P} = 10^6 \times (1.25 \text{ mW} + 2.5 \mu\text{W})$$

$$\bar{P} = \bar{P}_{\text{Standby}} + \bar{P}_{\text{Active}} = 1.25 \text{ KW} + 2.5 \text{ W}$$


**Problem**

**Not bad,  
Reducing  $V_S$   
From 5 to 1V  
Become 150 mW**

# How to get rid of static power?




Intuition:

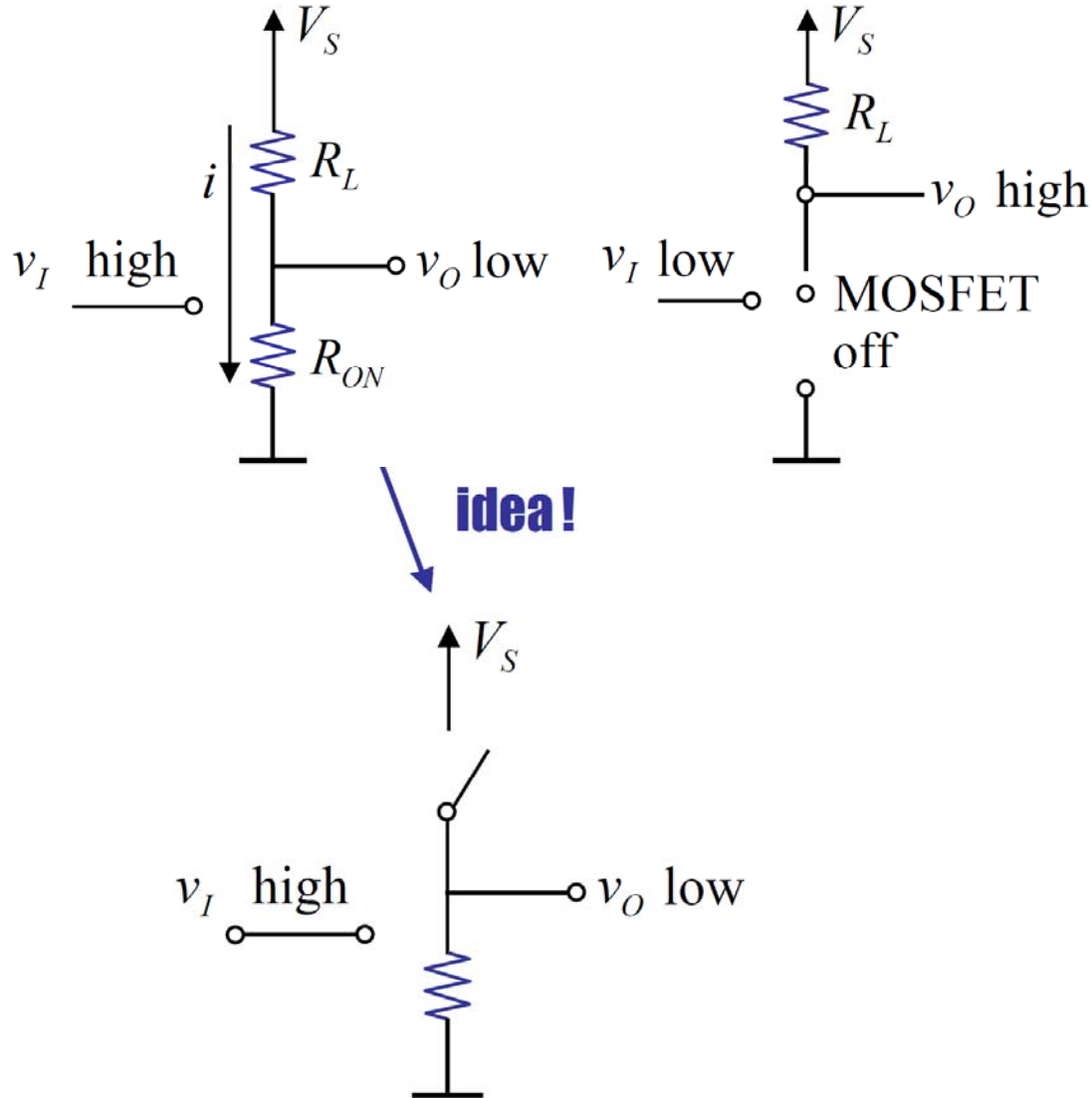


# PMOS



- P-channel MOSFET (PMOS)

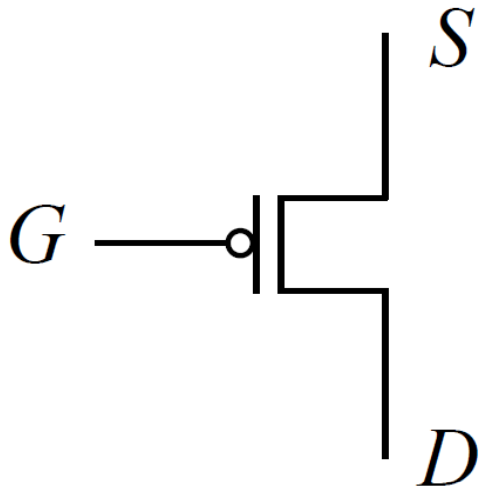

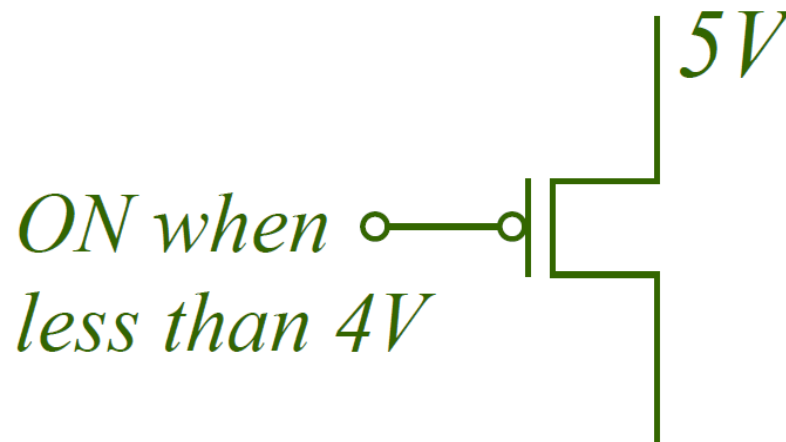
on when  $v_{GS} \leq V_{TP}$   
off when  $v_{GS} > V_{TP}$   
e.g.  $V_{TP} = -1V$




# CMOS



- Consider this circuit:

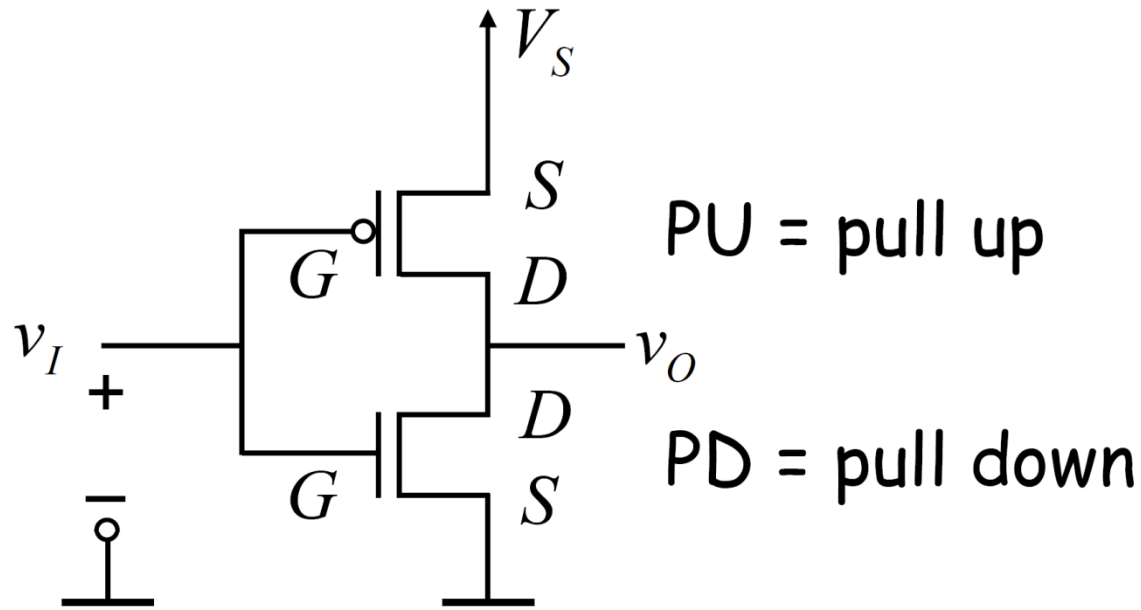


- Works like an inverter!

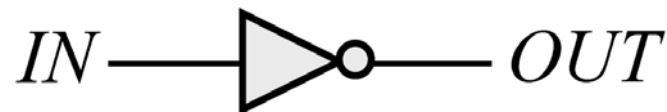

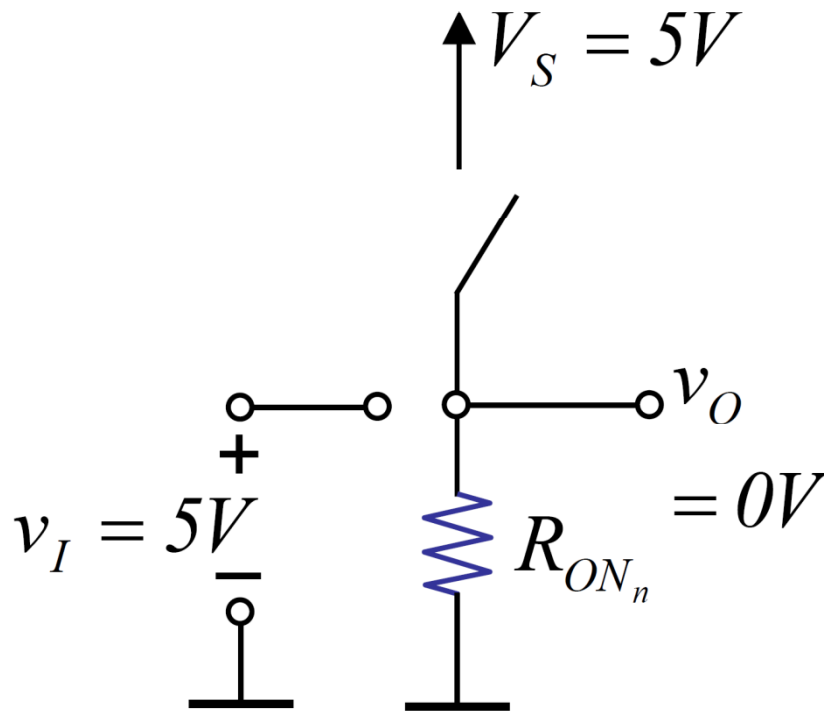
# CMOS



- Called "CMOS logic" or Complementary MOS logic. (Our previous logic was called "NMOS")



$v_I = 5V$  (input high)


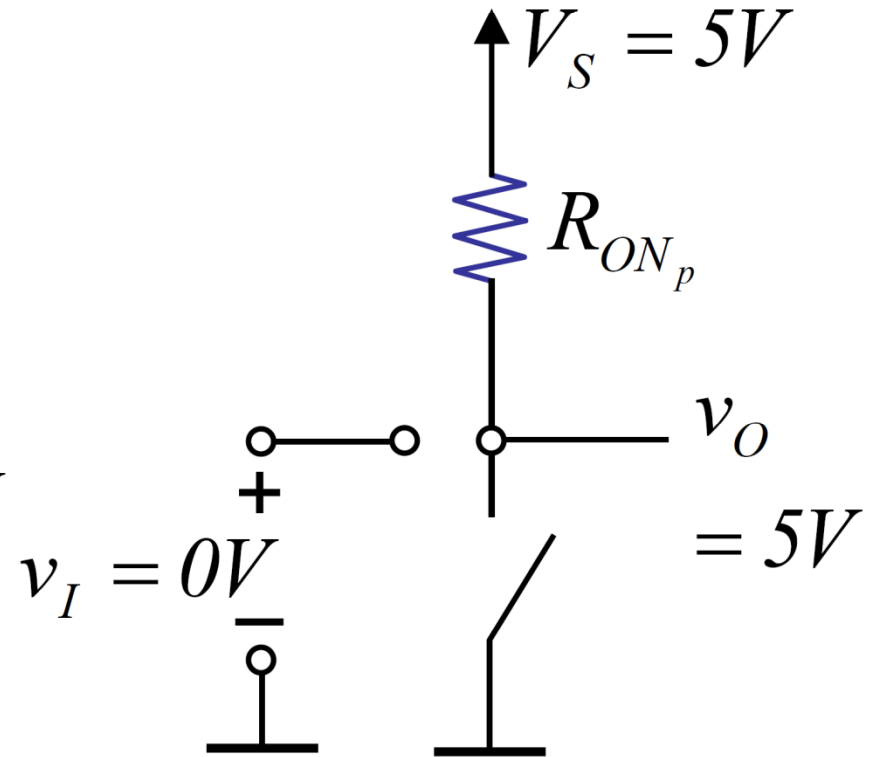


$v_I = 0V$  (input low)

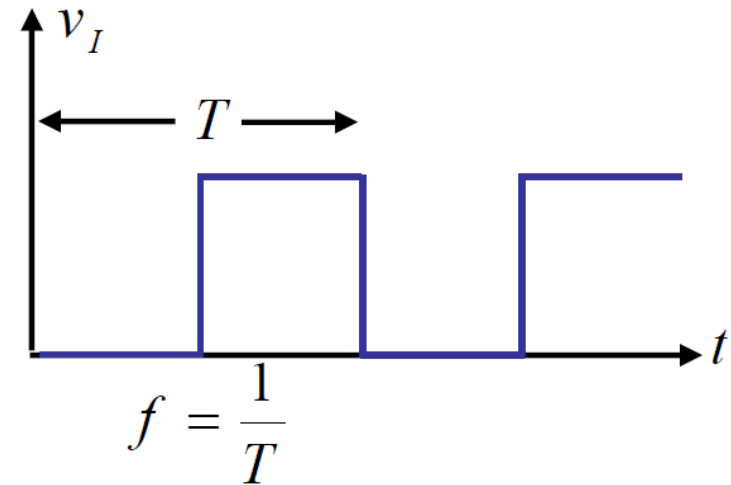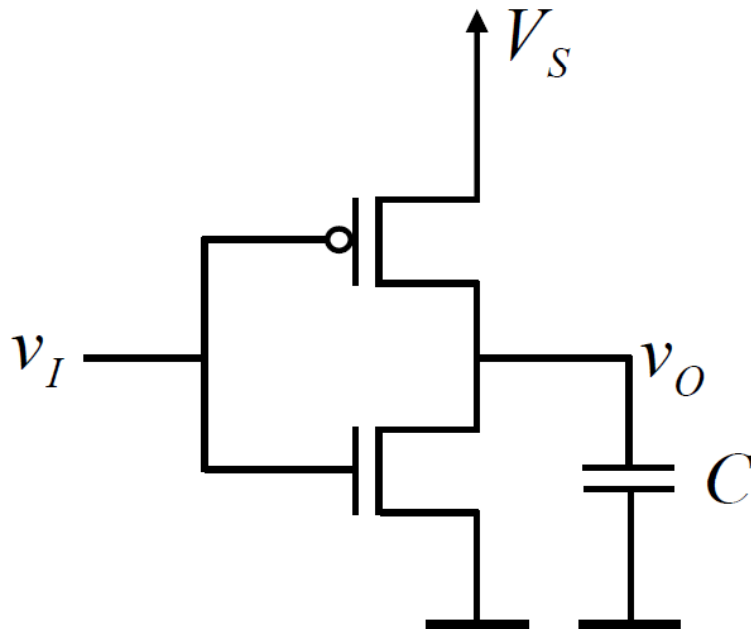
# Power of CMOS Logic



- Since there are no path from VS to GND! Thus, there are no static power dissipation!
- Let's compute  $\bar{P}_{\text{Active}}$  or  $\bar{P}_{\text{Dynamic}}$  .



# Power of CMOS Logic

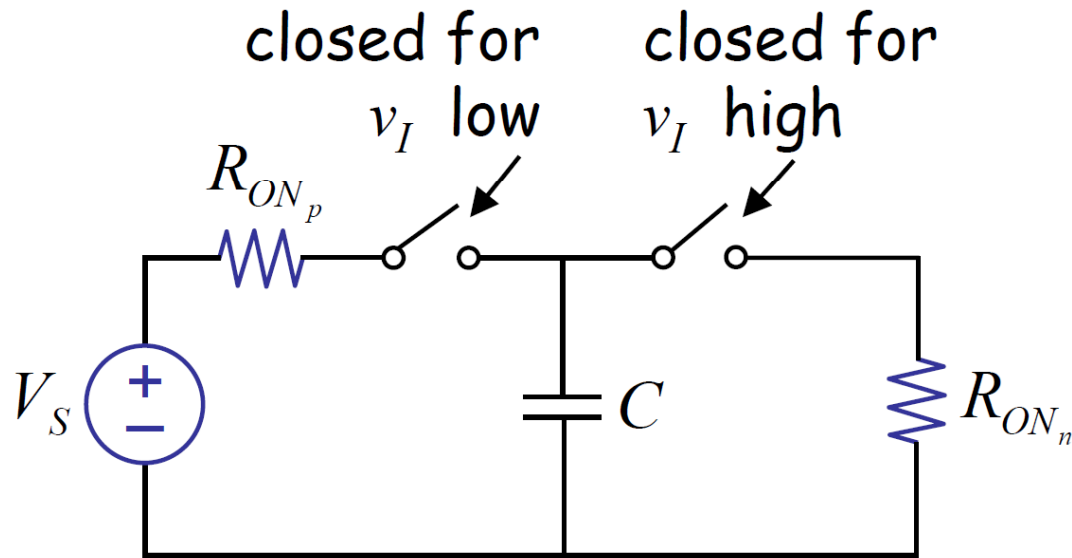

From previous discussion, we have  $\bar{P}_{\text{Dynamic}}$  as:

$$\bar{P}_{\text{Dynamic}} = CV_S^2 f$$

# For our previous example



- A chip with  $10^6$  gates clocking at 100 MHz.
- Assume  $C = 1$  fF,  $R_L = 10$  k $\Omega$ , and  $V_S = 5$  V.

Gates	$f$	$P$
$10^6$	100 MHz	2.5 W
$2 \times 10^6$	300 MHz	15 W
$2 \times 10^6$	600 MHz	30 W
$8 \times 10^6$	1.2 GHz	240 W
$25 \times 10^6$	3 GHz	1875 W



# How to reduce power?



- Reduce  $V_S$ .
- Turn off circuit when not in use (Sleep mode).
- Change  $V_S$  depending on need.
- Use multicore to reduce  $f$  without sacrificing speed of the circuits.

Power Trends in Intel's Microprocessors

