

# Second Order Circuits

Chenhsin Lien and Po-Tai Cheng

CENTER FOR ADVANCED POWER TECHNOLOGIES

Dept. of Electrical Engineering

National Tsing Hua University

Hsinchu, TAIWAN



# CAPT

Center for Advanced Power Technologies  
National Tsing Hua University, TAIWAN

# Overview




- Second order circuits can be characterized by circuit contain two independent energy storage elements.
- Second order circuits can be characterized second order differential equations .
- The LC circuit.
- The series  $R - L - C$  circuit.
  - Over damped.
  - Critically damped.
  - Under damped.
- The Intuitive Analysis
- Parallel  $R - L - C$  circuit.
- The State-variable analysis
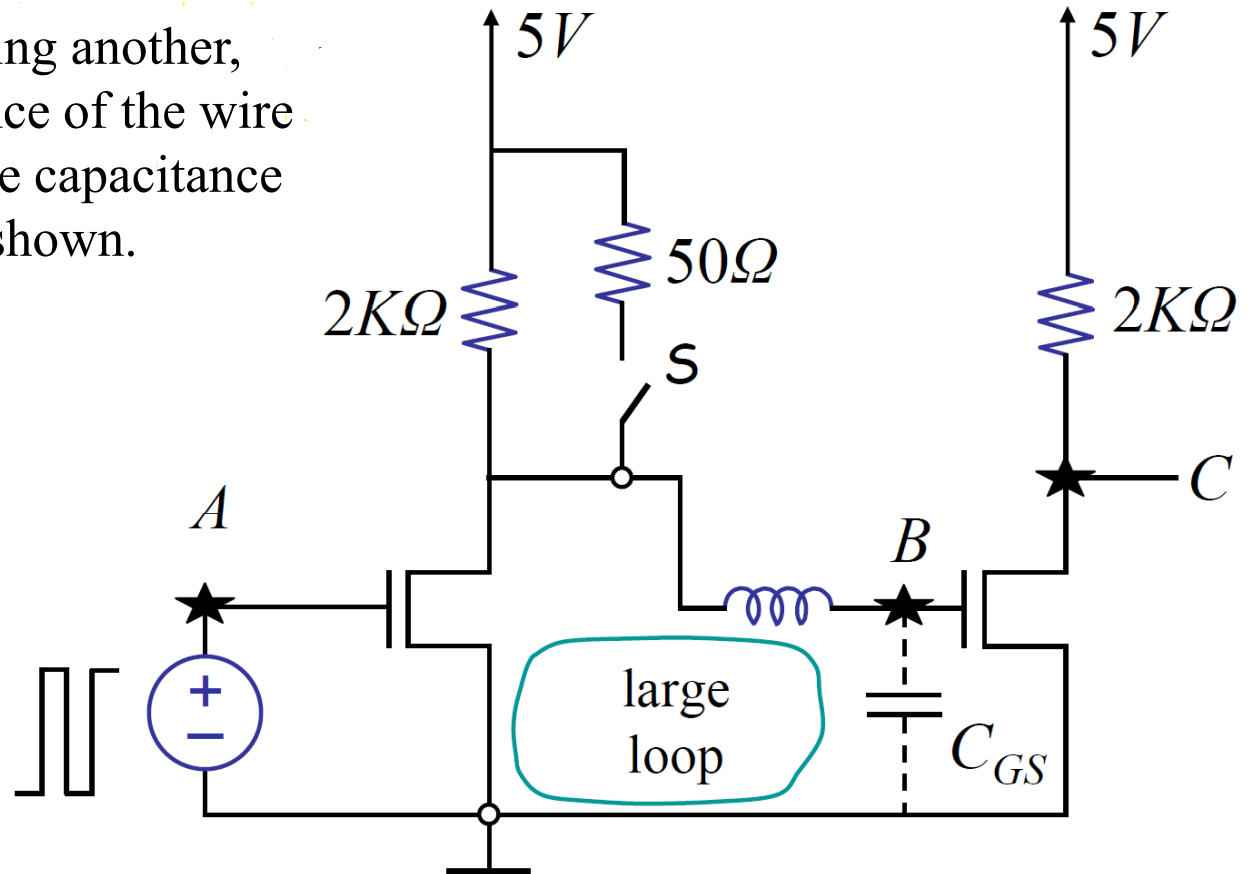
# The Inverter Chain




For this inverter driving another, the parasitic inductance of the wire and the gate-to-source capacitance of the MOSFET are shown.






# With 2 kΩ Load Resistance

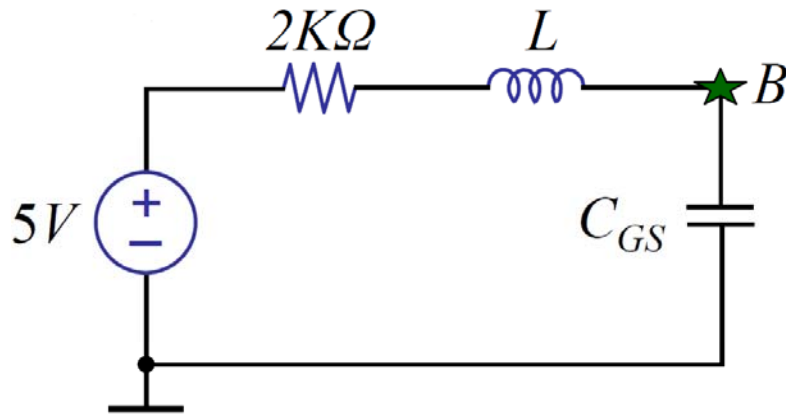

Now, let's try to speed up our inverter by closing the switch  $S$  to lower the effective resistance.


## Observed Output 2kΩ

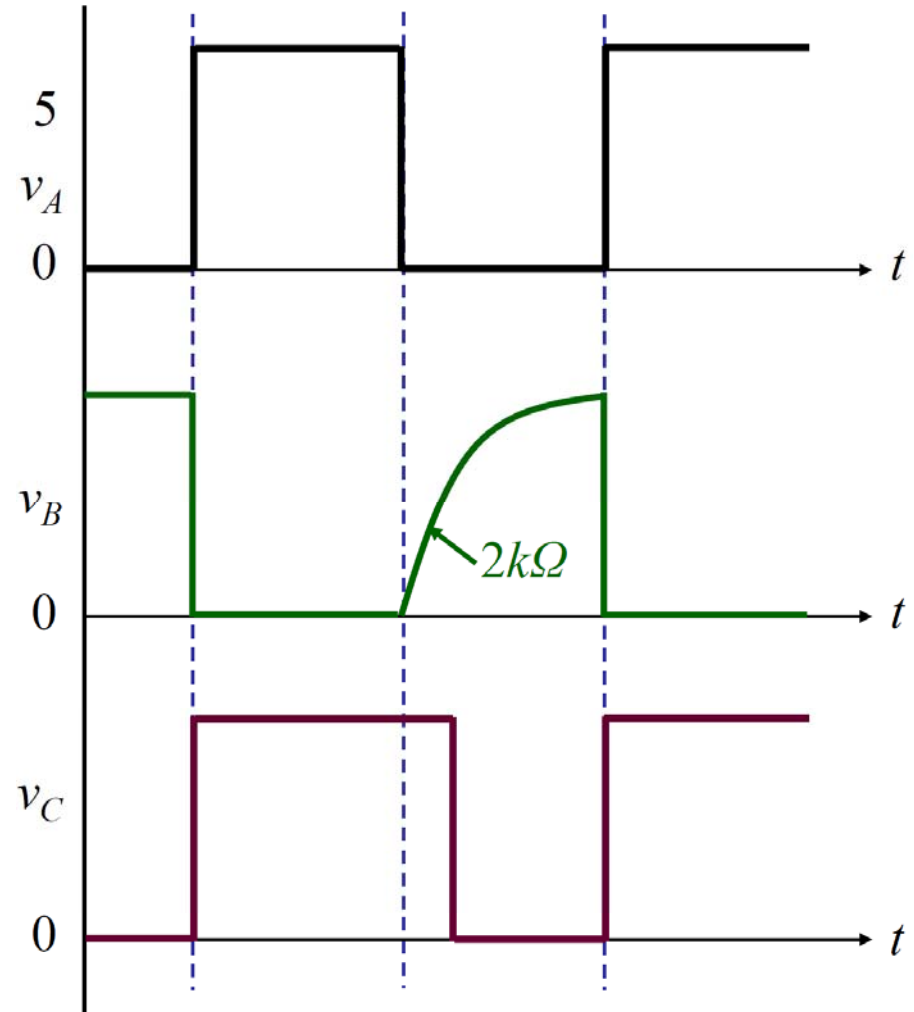




# With $50\ \Omega$ Load Resistance

Observed Output  $\sim 50\ \Omega$

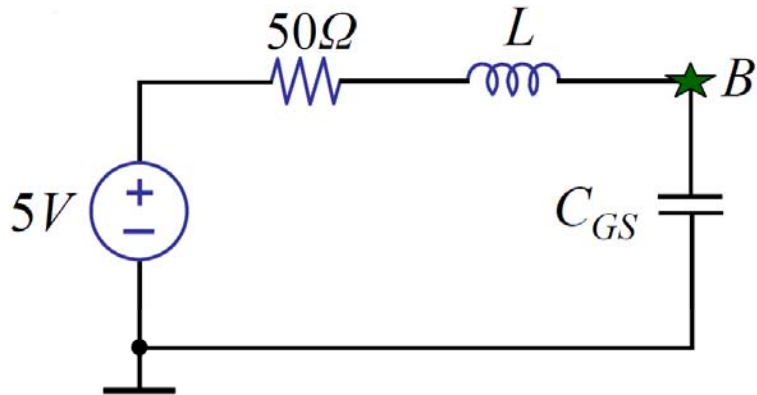

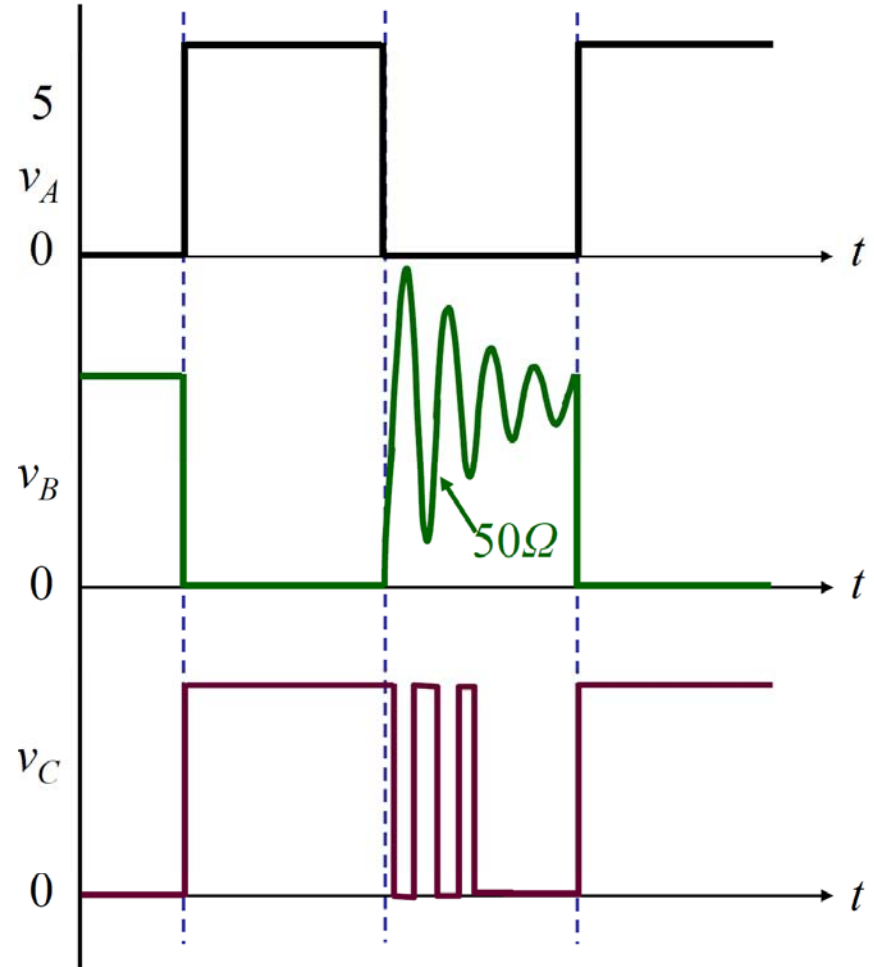
In addition to the speedy rising time. There are additional unexpected ringing.


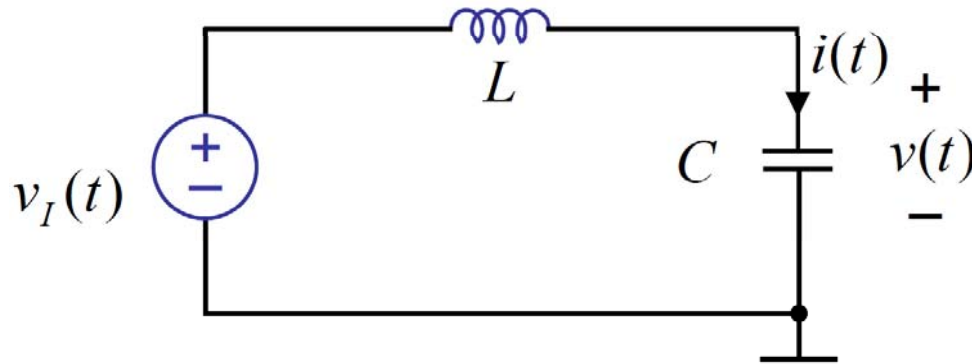
# LC Network



- To understand this, let's analyze the LC network first (instead of RLC).



- Node method:

$$i(t) = C \frac{dv}{dt} \quad v_I - v = L \frac{di}{dt} \Rightarrow i = \frac{1}{L} \int_{-\infty}^t (v_I - v) dt$$


$$\frac{1}{L} \int_{-\infty}^t (v_I - v) dt = C \frac{dv}{dt} \Rightarrow \frac{1}{L} (v_I - v) = C \frac{d^2v}{dt^2}$$

$$LC \frac{d^2v}{dt^2} + v = v_I$$

- $v, i$  are state variables.

Unit of  $LC$  is  $\text{Time}^2$
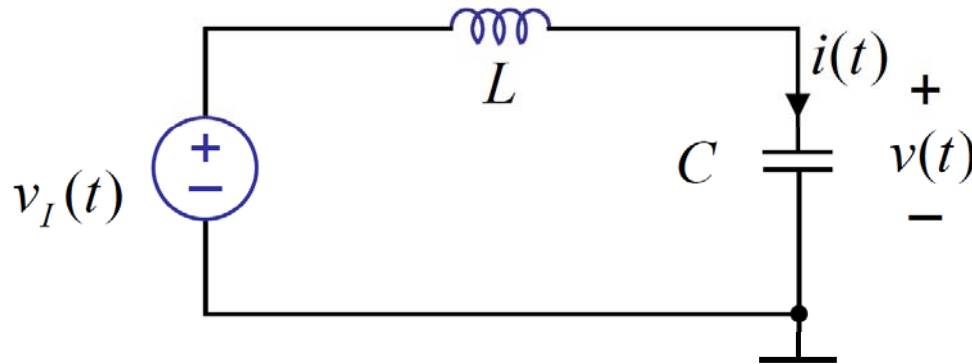
# Method of homogeneous and particular solutions




- Find the particular solution,  $v_P$ .
- Find the homogeneous solution,  $v_H$ .
- The total solution is the sum of the particular and homogeneous solutions,  $v = v_P + v_H$ .
- Use the initial conditions to solve for the remaining constants.

# LC Circuit



- Solve:

$$LC \frac{d^2 v}{dt^2} + v = v_I$$

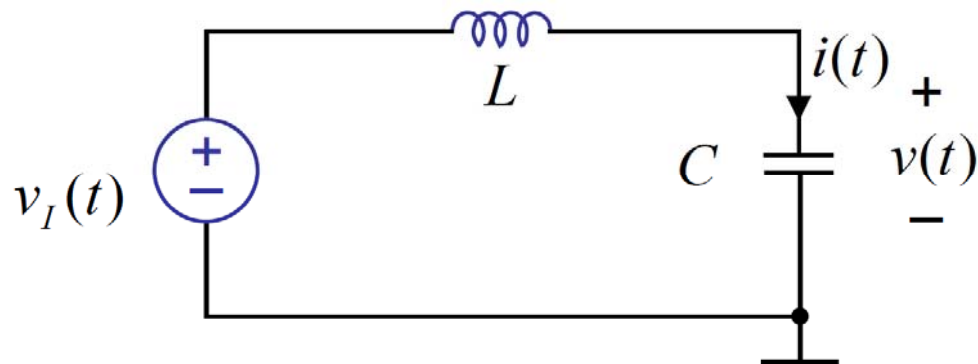


- With input:

$$v_I(t) = V_0 u(t)$$

- And zero initial state:

$$v(0) = 0$$


$$i(0) = 0$$

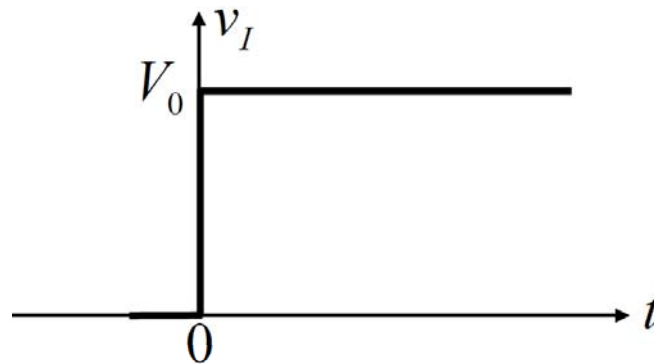

- Zero State Response (ZSR).



# The Particular solution

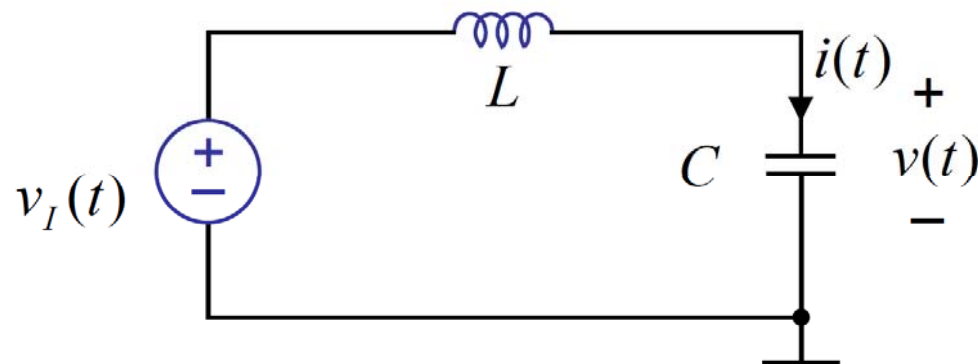

- Find the particular solution for  $LC \frac{d^2 v_P}{dt^2} + v_P = v_I$
- Use trial and error : Try  $v_P = K, .$

$$LC \frac{d^2 K}{dt^2} + K = V_0 \Rightarrow 0 + K = V_0 \Rightarrow K = V_0 \Rightarrow v_P = V_0$$

# The Homogeneous Solution



• Find the homogeneous solution,  $v_H$ , for  $LC \frac{d^2 v_H}{dt^2} + v_H = 0$

• Assume solution is of this form:  $v_H = Ae^{st}$

$$LC \frac{d^2 Ae^{st}}{dt^2} + Ae^{st} = 0 \Rightarrow LCAs^2 e^{st} + Ae^{st} = 0 \Rightarrow LCs^2 + 1 = 0$$

• Characteristic equation:  $LCs^2 + 1 = 0$

• Root:  $\Rightarrow s = \pm j \sqrt{\frac{1}{LC}} = \pm j \omega_0$  where  $\omega_0 = \sqrt{\frac{1}{LC}}$

•  $\omega_0$  is the natural frequency.

• The homogeneous solution,  $v_H$ :  $v_H = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$

# The Total solution



- The total solution is the sum of the particular and homogeneous solutions:

$$v = v_P + v_H = V_0 + A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$$

- Use the initial conditions:  $v(0) = 0$  V and  $i(0) = 0$  A

$$v(0) = 0 = V_0 + A_1 e^{j\omega_0 0} + A_2 e^{-j\omega_0 0} = V_0 + A_1 + A_2$$

$$i(0) = 0 = C \frac{dv}{dt} = CA_1 j\omega_0 e^{j\omega_0 0} - CA_2 j\omega_0 e^{-j\omega_0 0} = CA_1 j\omega_0 - CA_2 j\omega_0$$

$$\Rightarrow A_1 = A_2 = -\frac{V_0}{2}$$

- The total solution  $v$  :

$$v = V_0 - \frac{V_0}{2} (e^{j\omega_0 t} + e^{-j\omega_0 t})$$


# The Total solution




• The total solution  $v$  and  $i$ :  $v = V_0 - V_0 \cos \omega_0 t$

$$i = CV_0 \omega_0 \sin \omega_0 t$$

• The output looks sinusoidal.

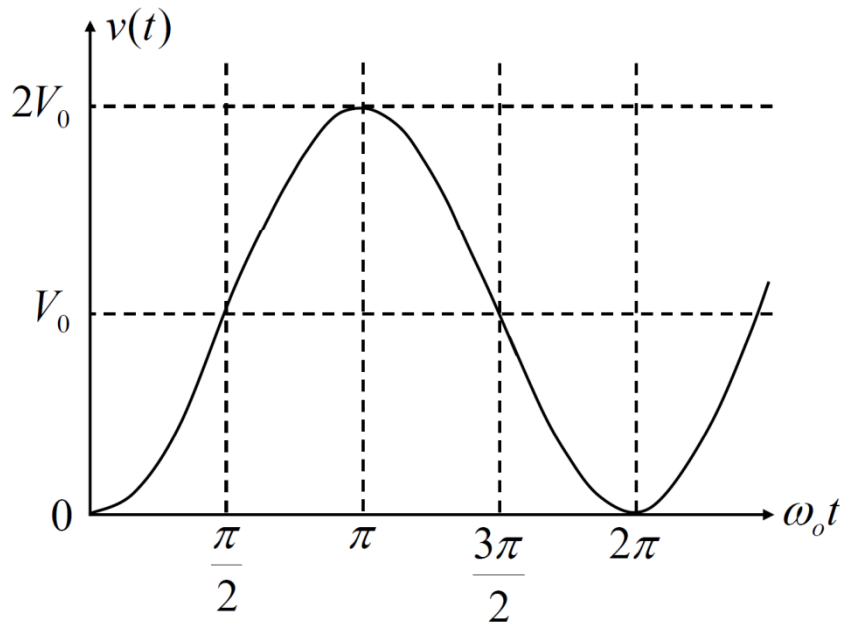

$$v = V_0 - V_0 \cos \omega_0 t$$

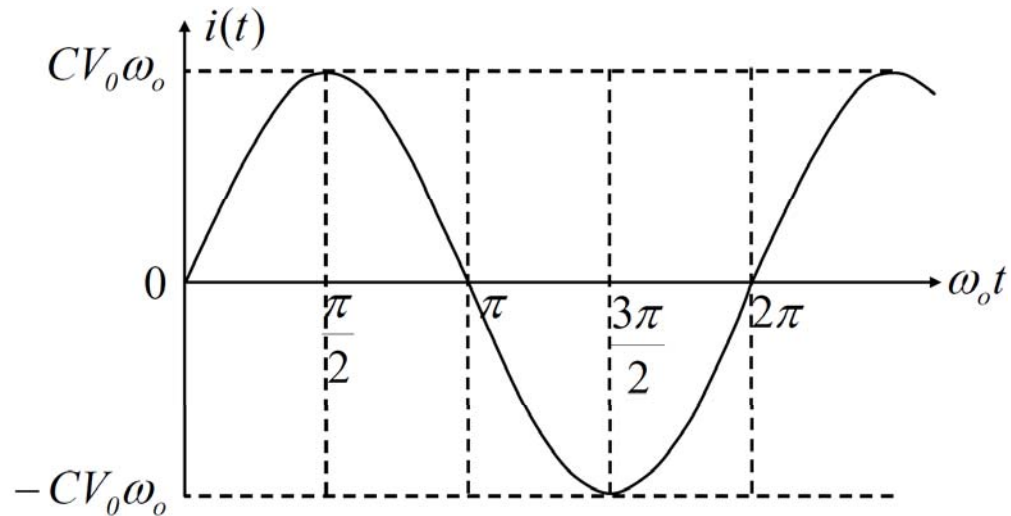

$$i = CV_0 \omega_0 \sin \omega_0 t$$




# Summary of the Method

- ① Write the DE for the circuit by applying the node method.
- ② Find particular solution  $v_P$  by guessing and trial & error.
- ③ Find homogeneous solution  $v_H$  by.
  - Assume the solution of the form  $v_H = Ae^{st}$
  - Obtain the characteristic equation.
  - Solve the characteristic equation for roots  $s_j$ .
  - Form  $v_H$  by summing the  $A_i e^{s_i t}$  terms.
- ④ Total solution is  $v = v_P + v_H$ , and solving for the remaining constants by using the initial conditions.
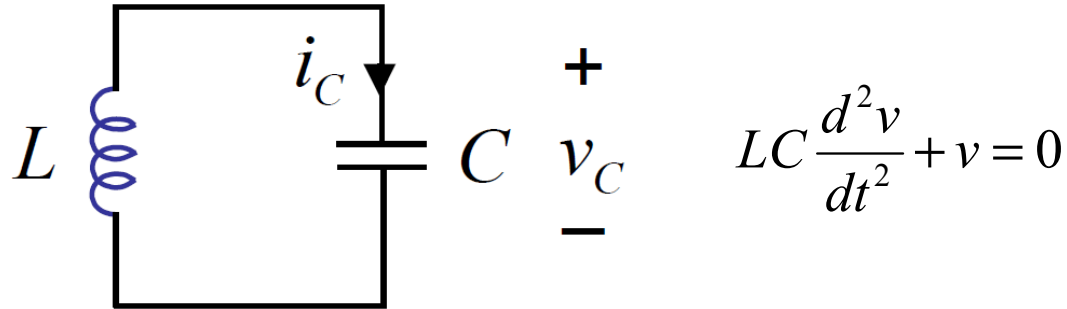
# Undriven LC Network



- The undriven response is also the Zero Input Response (ZIR) of the circuit.



- With zero input  $v_I = 0$ .
- And nonzero initial state

$$\begin{aligned} v_C(0) &= V \\ i_C(0) &= 0 \end{aligned}$$

$$v_C(0) = V = A_1 e^{j\omega_0 0} + A_2 e^{-j\omega_0 0} \Rightarrow V = A_1 + A_2$$

$$i(0) = 0 = CA_1 j\omega_0 - CA_2 j\omega_0 \Rightarrow A_1 = A_2$$


$$A_1 = A_2 = \frac{V}{2}$$

- The Solutions

$$v = V \cos \omega_0 t$$

$$i = -CV\omega_0 \sin \omega_0 t$$


# Undriven LC Network

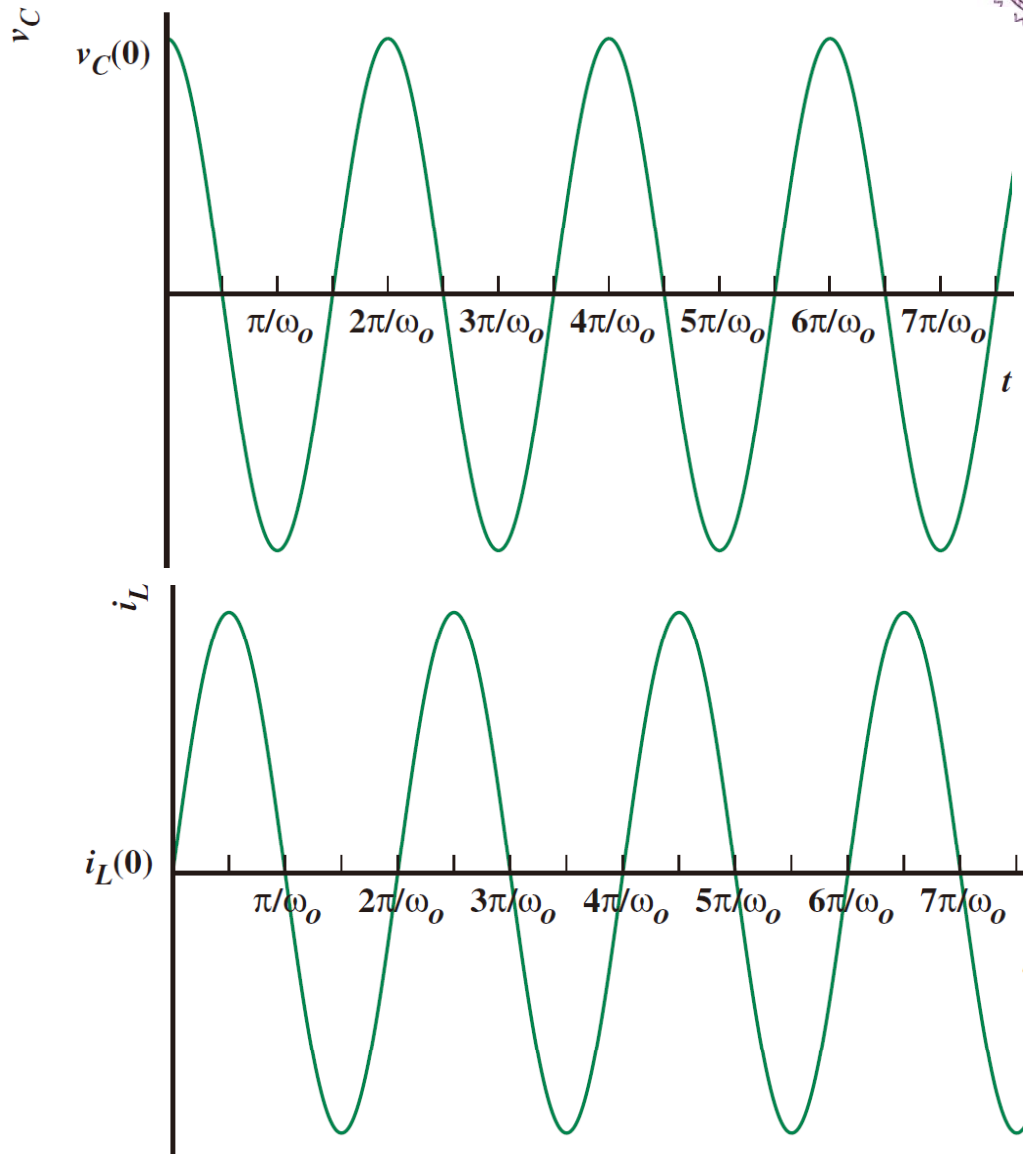
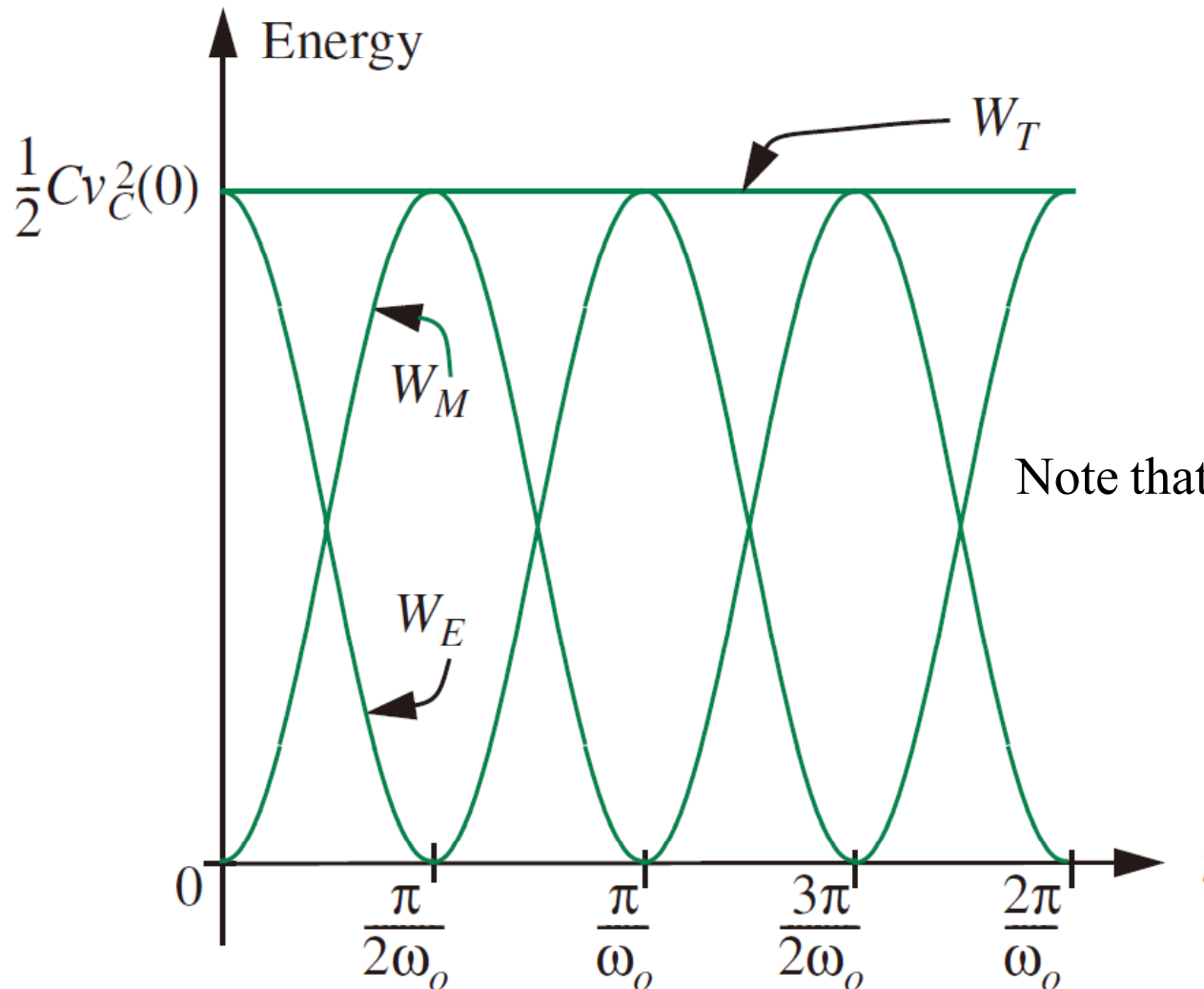
# The Energy



- Total energy in the system is a constant, but it sloshes back and forth between the Capacitor and the inductor.



Note that  $\frac{1}{2}Cv_C^2 + \frac{1}{2}Li_C^2 = \frac{1}{2}CV^2$



# RLC Network (Damped Oscillator)




CAPT

Center for Advanced Power Technologies  
National Tsing Hua University, TAIWAN

- Now, let's add a resistor to the LC network and analyze the RLC network.
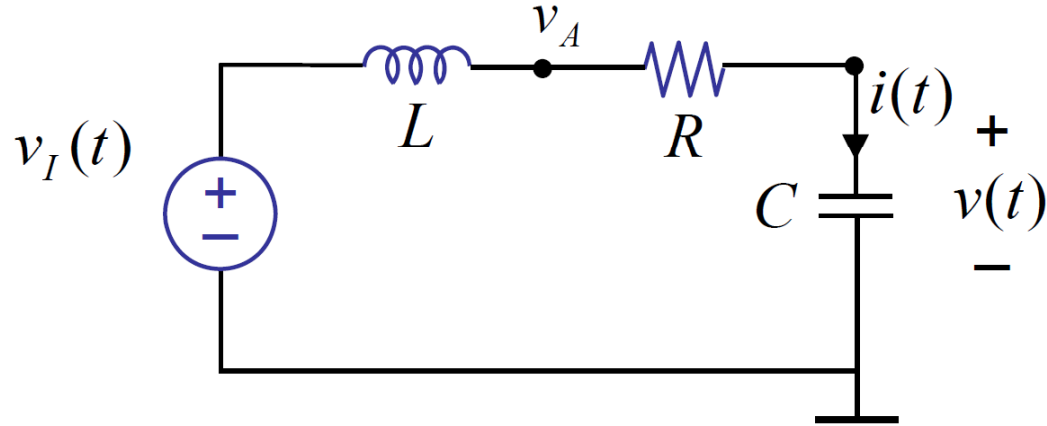
$$LC \frac{d^2 v}{dt^2} + RC \frac{dv}{dt} + v = v_I$$



- Node method:



$$\text{Node } v_A: \frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = i = \frac{v_A - v}{R}$$

$$\text{Node } v: C \frac{dv}{dt} = i = \frac{v_A - v}{R} \Rightarrow RC \frac{dv}{dt} = v_A - v$$

$$C \frac{d^2 v}{dt^2} = \frac{1}{R} \frac{d(v_A - v)}{dt} = \frac{v_I - v_A}{L} \Rightarrow LC \frac{d^2 v}{dt^2} = v_I - v_A$$

$$LC \frac{d^2 v}{dt^2} + RC \frac{dv}{dt} = v_I - v_A + v_A - v \Rightarrow LC \frac{d^2 v}{dt^2} + RC \frac{dv}{dt} + v = v_I$$
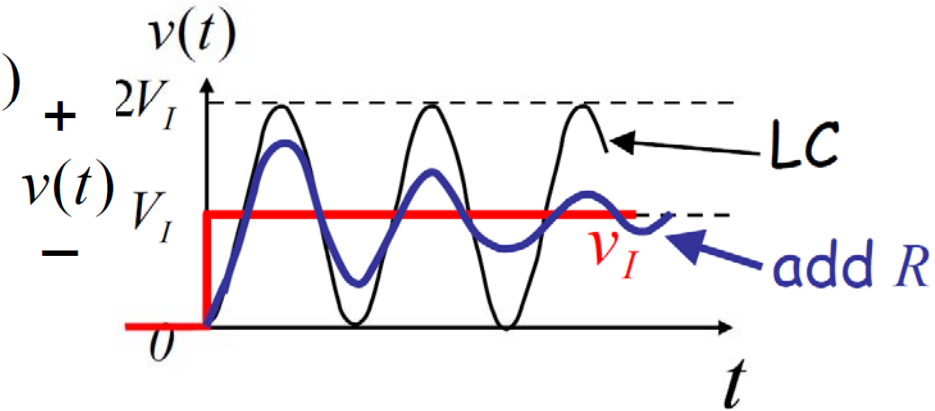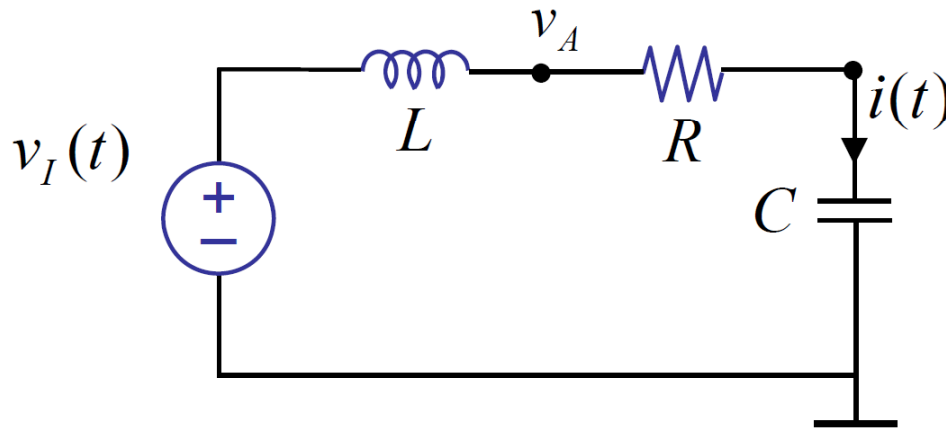
# Method of homogeneous and particular solutions




- Find the particular solution,  $v_P$ .
- Find the homogeneous solution,  $v_H$ .
- The total solution is the sum of the particular and homogeneous solutions,  $v = v_P + v_H$ .
- Use the initial conditions to solve for the remaining constants.
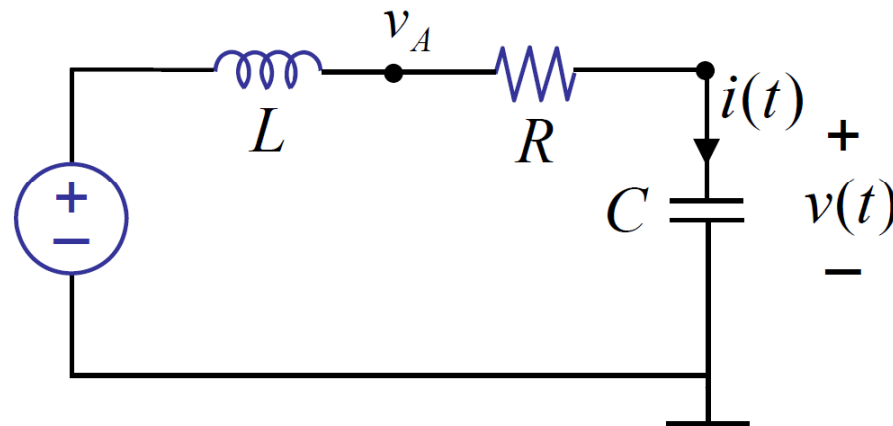
# RLC Circuit



- Solve:

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I(t)$$




- With input:

$$v_I(t) = V_I u(t)$$

- And zero initial state:


$$v(0) = 0$$

$$i(0) = 0$$

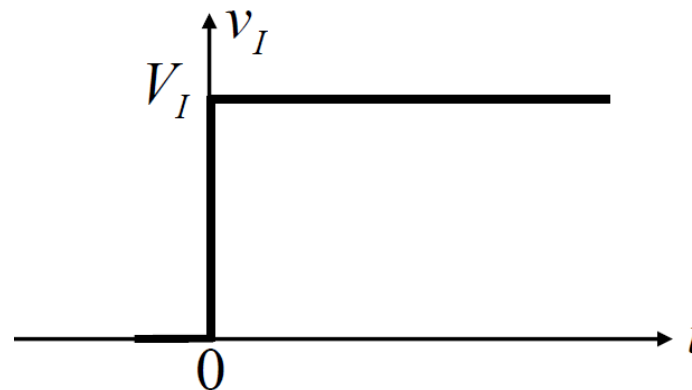

- Zero State Response (ZSR).

# The Particular solution

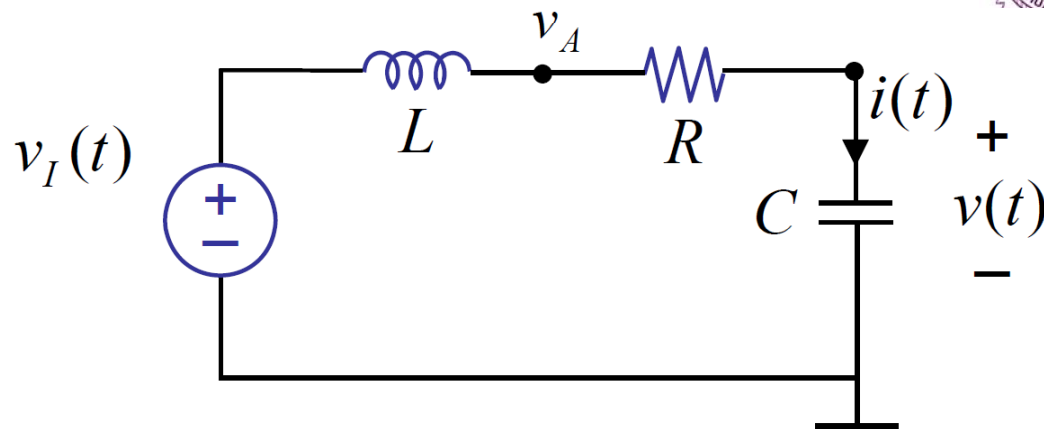

- Find the particular solution for  $\frac{d^2 v_P}{dt^2} + \frac{R}{L} \frac{dv_P}{dt} + \frac{1}{LC} v_P = \frac{1}{LC} V_I$
- Use trial and error : Try  $v_P = K, .$

$$\frac{d^2 K}{dt^2} + \frac{R}{L} \frac{dK}{dt} + \frac{1}{LC} K = \frac{1}{LC} V_I \Rightarrow 0 + 0 + \frac{1}{LC} K = \frac{1}{LC} V_I \Rightarrow K = V_I$$

$$\Rightarrow v_P = V_I$$

# The Homogeneous Solution



• Find the homogeneous solution,  $v_H$ , for  $\frac{d^2 v_H}{dt^2} + \frac{R}{L} \frac{dv_H}{dt} + \frac{1}{LC} v_H = 0$

• Assume solution is of this form:  $v_H = Ae^{st}$

$$\frac{d^2 Ae^{st}}{dt^2} + \frac{R}{L} \frac{dAe^{st}}{dt} + \frac{1}{LC} Ae^{st} = 0 \Rightarrow s^2 Ae^{st} + \frac{R}{L} sAe^{st} + \frac{1}{LC} Ae^{st} = 0$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

• Characteristic equation:

$$s^2 + 2\alpha s + \omega_0^2 = 0 \quad \text{where } \alpha = \frac{R}{2L} \text{ and } \omega_0^2 = \frac{1}{LC}$$

# The Homogeneous Solution



- Characteristic equation:

$$s^2 + 2\alpha s + \omega_0^2 = 0 \quad \text{where } \alpha = \frac{R}{2L} \text{ and } \omega_0^2 = \frac{1}{LC}$$

- Root:  $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

- The homogeneous solution,  $v_H$ :  $v_H = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$v_H = A_1 e^{\left(-\alpha + \sqrt{\alpha^2 - \omega_0^2}\right)t} + A_2 e^{\left(-\alpha - \sqrt{\alpha^2 - \omega_0^2}\right)t}$$

# The Total solution



- The total solution is the sum of the particular and homogeneous solutions:

$$v(t) = v_P + v_H = V_I + A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})t}$$

- Use the initial conditions:  $v(0) = 0$  V and  $i(0) = 0$  A

$$v(0) = V_I + A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})0} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})0} = V_I + A_1 + A_2 = 0$$

$$i(0) = C \frac{dv}{dt} = (-\alpha + \sqrt{\alpha^2 - \omega_0^2})A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})0} + (-\alpha - \sqrt{\alpha^2 - \omega_0^2})A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})0} = 0$$

$$(-\alpha + \sqrt{\alpha^2 - \omega_0^2})A_1 + (-\alpha - \sqrt{\alpha^2 - \omega_0^2})A_2 = 0$$

$$\text{If } \alpha \neq \omega_0 \Rightarrow A_1 = -\frac{\alpha + \sqrt{\alpha^2 - \omega_0^2}}{2\sqrt{\alpha^2 - \omega_0^2}} V_I \quad \text{and} \quad A_2 = -\frac{-\alpha + \sqrt{\alpha^2 - \omega_0^2}}{2\sqrt{\alpha^2 - \omega_0^2}} V_I .$$

# Solutions for Damped 2<sup>nd</sup> Order Circuit



- Let's stare at the total solution for a little bit longer...

$$v(t) = V_I + A_1 e^{-\alpha t} e^{\left(\sqrt{\alpha^2 - \omega_0^2}\right)t} + A_2 e^{-\alpha t} e^{\left(-\sqrt{\alpha^2 - \omega_0^2}\right)t}$$

- There are 3 possible cases:  $\alpha > \omega_0$ ,  $\alpha = \omega_0$ , and  $\alpha < \omega_0$ .

- The case for  $\alpha > \omega_0$  is called *overdamped*.

$$v(t) = V_I + A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t}$$


- The case for  $\alpha = \omega_0$  is called *critically damped*.

$$v(t) = V_I - V_I t e^{-\alpha t}$$

- The case for  $\alpha < \omega_0$  is called *underdamped*.

$$v(t) = V_I + A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$
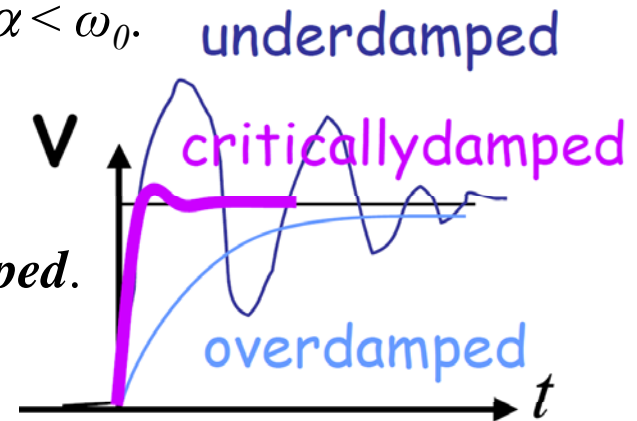
$$v(t) = V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t$$



where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ .



# Damp



Damp:

## Noun

1. moisture in the air; humidity.
2. Lowness of spirits; depression.
3. A restraint or check; a discouragement.

## Transitive verb

1. To make damp or moist; moisten.
2. To restrain or check; discourage.
3. (Music). To slow or stop the vibrations of (the strings of a keyboard instrument) with a damper.
4. (Physics) To decrease the amplitude of (an oscillating system).

# Underdamped



- Let's look at the underdamped case more closely.

- $\alpha < \omega_0$

$$v(t) = V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t$$

- Use the initial conditions:  $v(0) = 0$  V and  $i(0) = 0$  A

$$v(0) = V_I + K_1 = 0 \Rightarrow K_1 = -V_I$$

$$i(0) = C \left( -\alpha K_1 e^{-\alpha \cdot 0} \cos \omega_d \cdot 0 - \omega_d K_1 e^{-\alpha \cdot 0} \sin \omega_d \cdot 0 - \alpha K_2 e^{-\alpha \cdot 0} \sin \omega_d \cdot 0 + \omega_d K_2 e^{-\alpha \cdot 0} \cos \omega_d \cdot 0 \right)$$

$$i(0) = -C\alpha K_1 + C\omega_d K_2 = 0 \Rightarrow K_2 = \frac{\alpha}{\omega_d} K_1 = \frac{\alpha}{\omega_d} V_I$$

- The total solution for underdamped case,  $\alpha < \omega_0$ , is:

$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

# Underdamped




- The total solution for underdamped case,  $\alpha < \omega_0$ , is:

$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

- Since the scaled sum of sines (of the same frequency) are also sines, let's rewrite the total solution as:

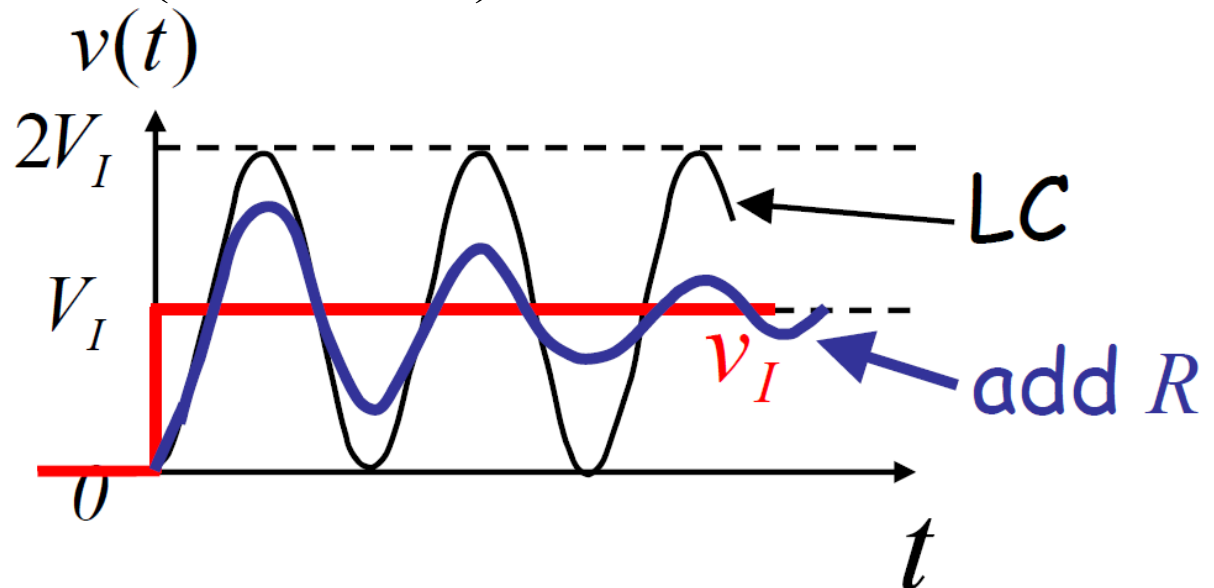
$$v(t) = V_I - V_I \frac{\omega_0}{\omega_d} e^{-\alpha t} \cos \left( \omega_d t - \tan^{-1} \frac{\alpha}{\omega_d} \right)$$






# With 50 Ω Load Resistance

Observed Output ~50Ω

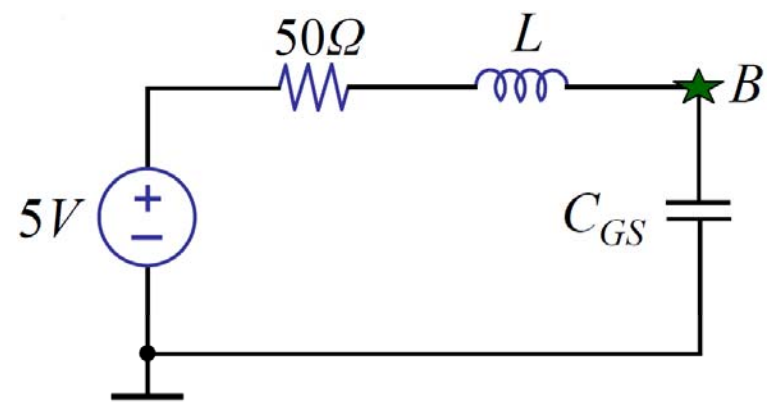

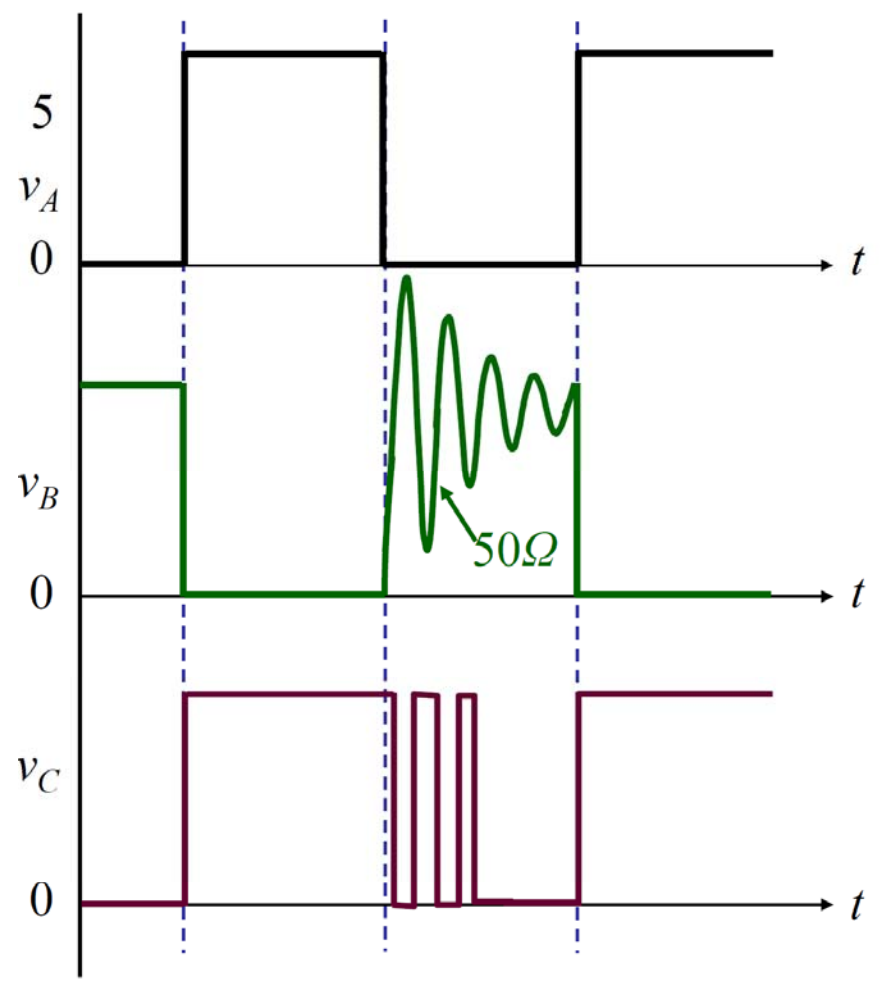Under smaller  $R$  of 50 Ω, the series RLC circuit become *underdamped* and the *ringing* occurs.



# Intuitive Analysis



- The total solution for underdamped case,  $\alpha < \omega_0$ , is:

$$v(t) = V_I - V_I \frac{\omega_0}{\omega_d} e^{-\alpha t} \cos\left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d}\right)$$

- Characteristic equation:  $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$      $s^2 + 2\alpha s + \omega_0^2 = 0$


- $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  is the oscillation frequency.

- $\alpha$  governs the decay rate.

- $V_I$  is the final steady state value.

- $v(0)$  and  $i(0)$  gives the initial value and slope.

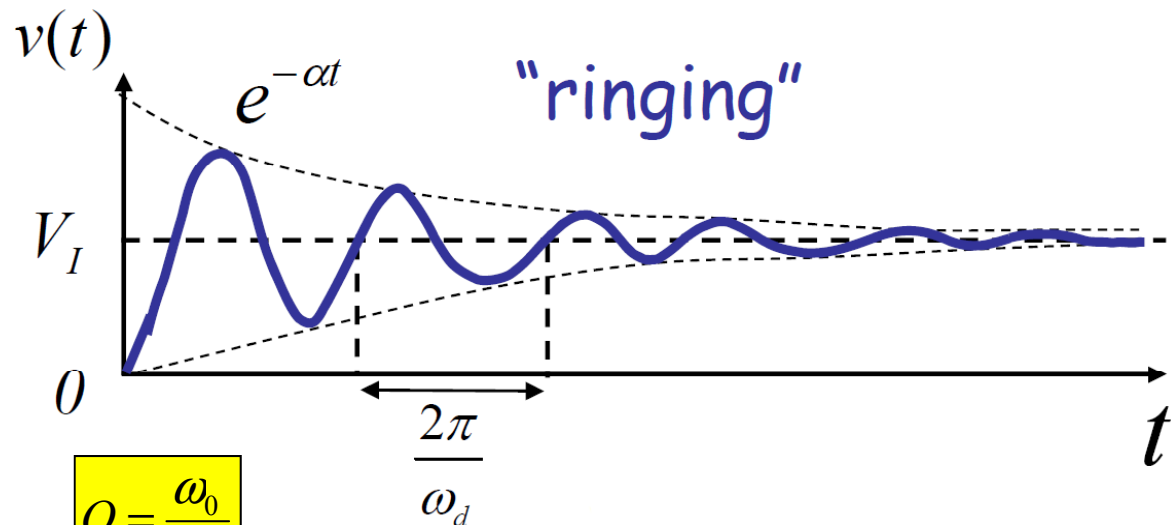- $Q$  is the quality factor (approximately the number of cycles of ringing)



$$Q = \frac{\omega_0}{2\alpha}$$


# Intuitive Analysis RLC Circuit



- The circuit:

$$R = 0.2 \Omega, L = 100 \mu\text{H}, \quad v_I(t)$$

$$C = 100 \mu\text{F}$$

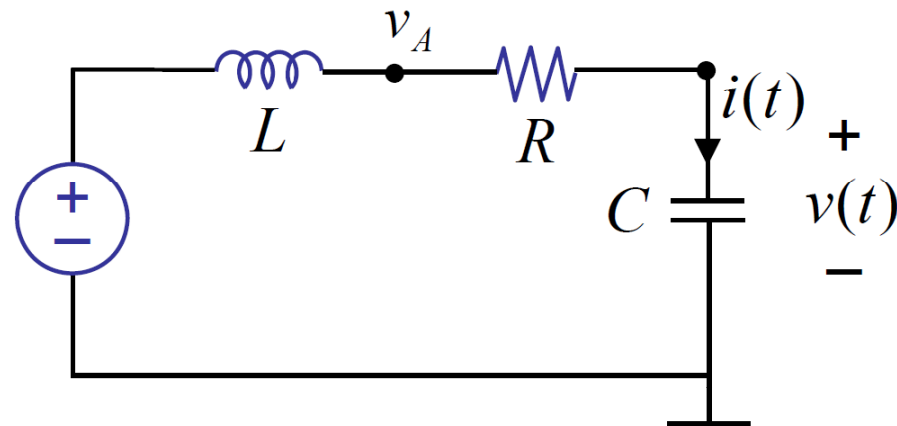


- With input:

$$v_I(t) = V_I u(t) \quad \text{where } V_I = 1 \text{ V}$$

- With initial states:

$$v(0) = 0.5 \text{ V}$$

$$i(0) = -0.5 \text{ A}$$

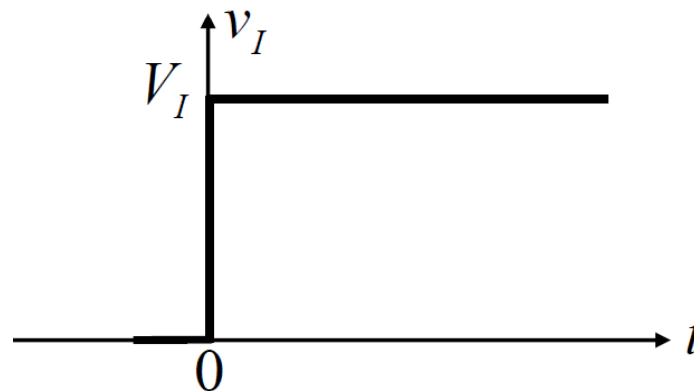

# Intuitive Analysis RLC Circuit




- In the steady state, the capacitor behaves like an open circuit. Therefore, the inductor current vanishes and the input drive appears across the capacitor.

$$v(\infty) = 1 \text{ V}$$

$$i(\infty) = 0 \text{ A}$$

$$v(0) = 0.5 \text{ V}$$

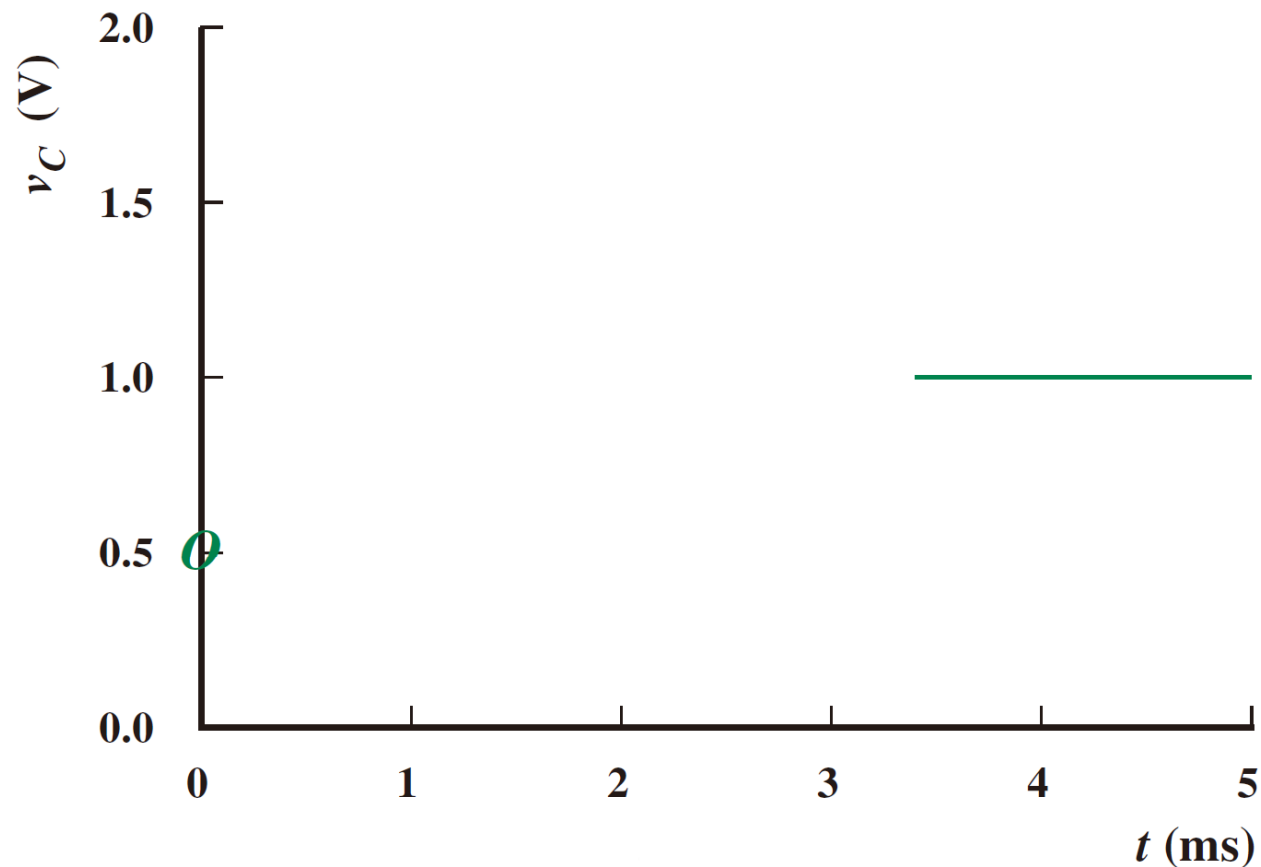

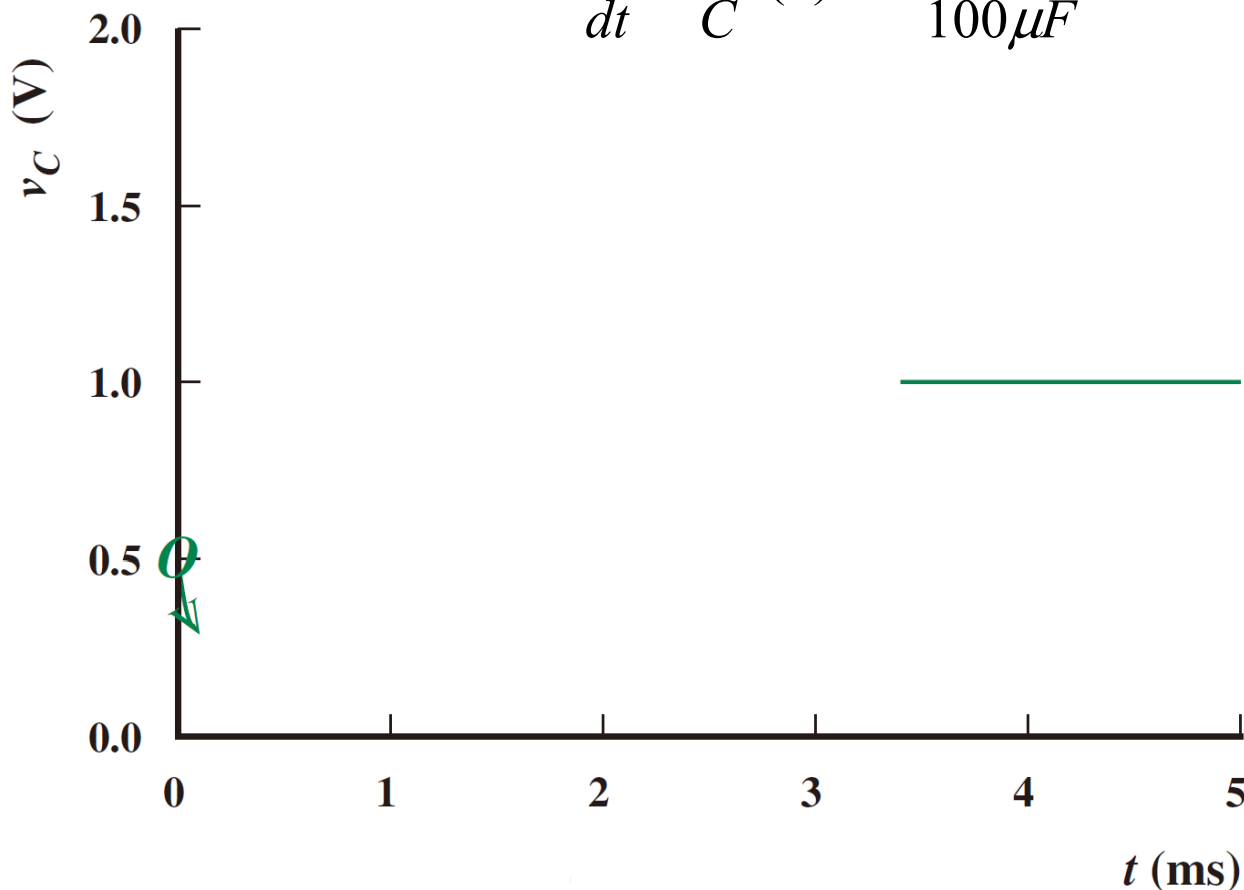
# Intuitive Analysis RLC Circuit



- The initial trajectory of the capacitor voltage (increasing or decreasing) starting from its initial value of 0.5 V is:

$$\frac{dv}{dt} = \frac{1}{C} i(0) = -\frac{0.5 A}{100 \mu F} = 5000 \frac{V}{\text{sec}}$$





# Intuitive Analysis RLC Circuit



- Characteristic equation:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \text{i.e.} \quad s^2 + 2\alpha s + \omega_0^2 = 0$$

$$\alpha = \frac{R}{2L} = 10^3 \text{ rad/sec} \quad \omega_0 = \sqrt{\frac{1}{LC}} = 10^4 \text{ rad/sec}$$

- *Since  $\alpha < \omega_0$ , We conclude that the system is under-damped. The oscillation frequency is given by*


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx 9950 \text{ rad/sec}$$

- Quality factor,  $Q$ :  $Q = \frac{\omega_0}{2\alpha} \approx 5$ , i.e. the system will ring for approximately 5 cycles.
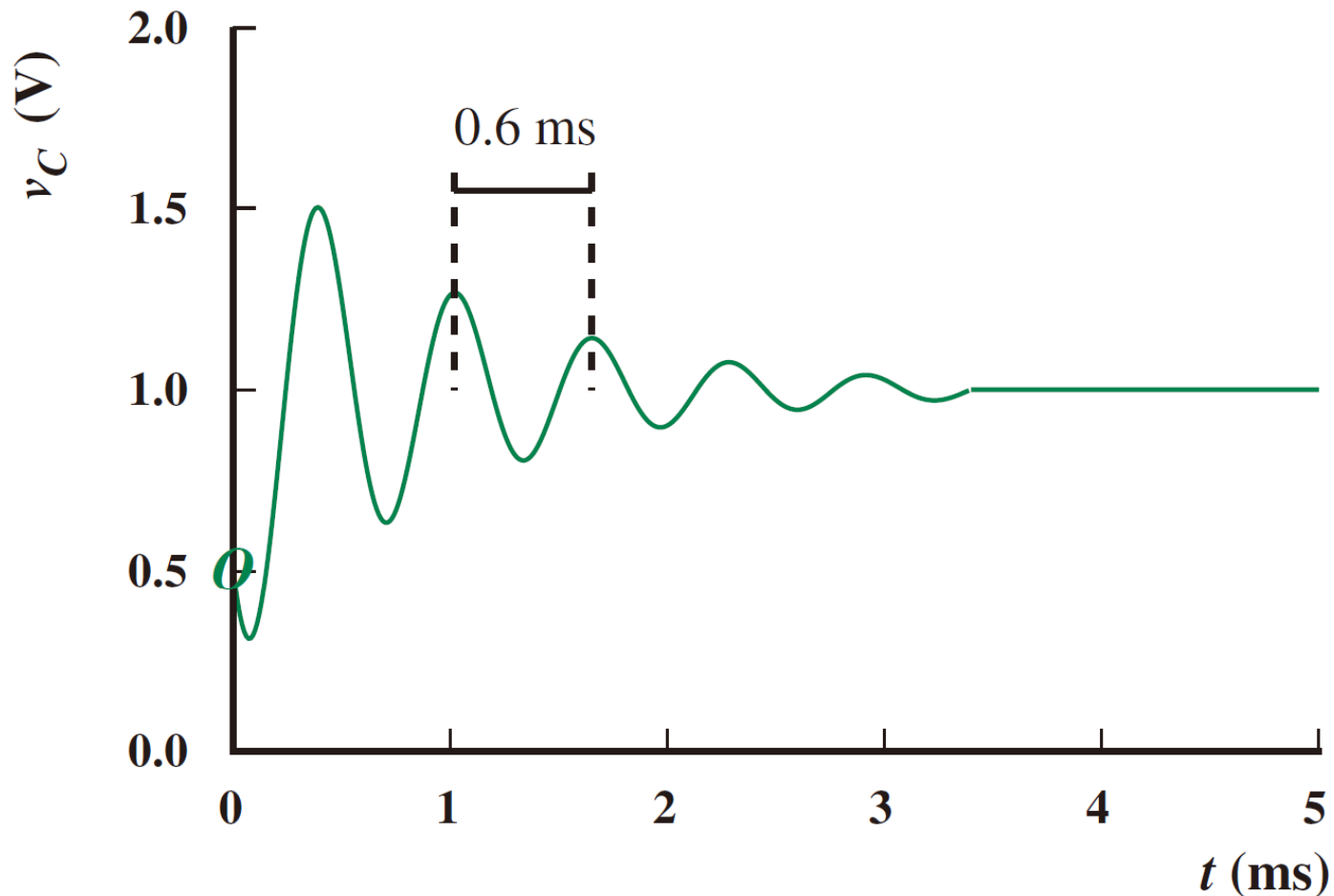
# Intuitive Analysis RLC Circuit




- Knowing the initial trajectory, we can stitch in a sinusoid that decays over about 5 cycles with the correct initial trajectory.


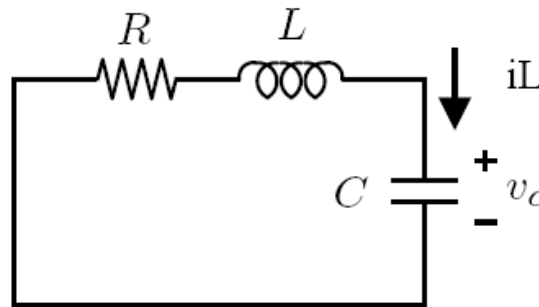
# Undriven RLC Network



- The undriven response is also the Zero Input Response (ZIR) of the circuit. For the following circuit, If  $L = 0.04$  H and  $C = 0.01$  F, find  $v_C(t)$  and  $i_L(t)$  for the following  $R = 5 \Omega$ ,  $4 \Omega$ , and  $1 \Omega$ .



$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0$$

- Nonzero initial state:

$$v_C(0) = 3 \text{ V}$$

$$i_L(0) = 0 \text{ A}$$

- The Equations: 
$$\frac{d^2 v_C}{dt^2} + 25R \frac{dv_C}{dt} + 2500v_C = 0$$


# Undriven RLC Network



- Characteristic equation:

$$s^2 + 25Rs + 2500 = 0$$

$$b^2 - 4ac = 625R^2 - 10000$$

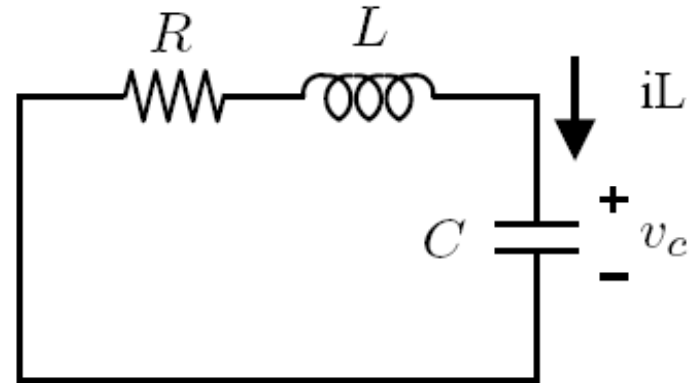

- $R = 5 \Omega$ ,  $625R^2 - 10000 = 5625 > 0$ , *overdamped*

$$s_1 = -25 \text{ and } s_2 = -100 \quad v_C(t) = A_1 e^{-25t} + A_2 e^{-100t}$$

- $R = 4 \Omega$ ,  $625R^2 - 10000 = 0$ , *critically damped*:

$$s_1 = s_2 = -50 \quad v_C(t) = A_1 e^{-50t} + A_2 t e^{-50t}$$

- $R = 1 \Omega$ ,  $625R^2 - 10000 = -9375 < 0$ , *underdamped*:

$$s_{1,2} = -12.5 \pm j48.4 \quad v_C(t) = K e^{-12.5t} \sin(48.4t + \varphi)$$

# Undriven RLC Network



- Determine the coefficient from

Initial conditions:

$$v_C(0) = 3 \text{ V}$$

$$i_L(0) = 0 \quad A = i_L(0) = C \frac{dv_C}{dt}$$

- **$R = 5 \Omega$  , overdamped**

$$A_1 + A_2 = 3 \quad \text{and} \quad -25A_1 - 100A_2 = 0 \Rightarrow A_1 = 4 \quad A_2 = -1$$

$$v_C(t) = 4e^{-25t} - e^{-100t}$$

- **$R = 4 \Omega$  , critically damped:**


$$A_1 = 3 \quad \text{and} \quad -50A_1 + A_2 = 0 \Rightarrow A_1 = 3 \quad A_2 = 150$$

$$v_C(t) = 3e^{-50t} (1 + 50t)$$

- **$R = 1 \Omega$  , underdamped :**

$$K \sin \varphi = 3 \quad \text{and} \quad -12.5 K \sin \varphi + 48.4 K \cos \varphi = 0 \Rightarrow K = 3.1 \quad \varphi = 75.5^\circ$$
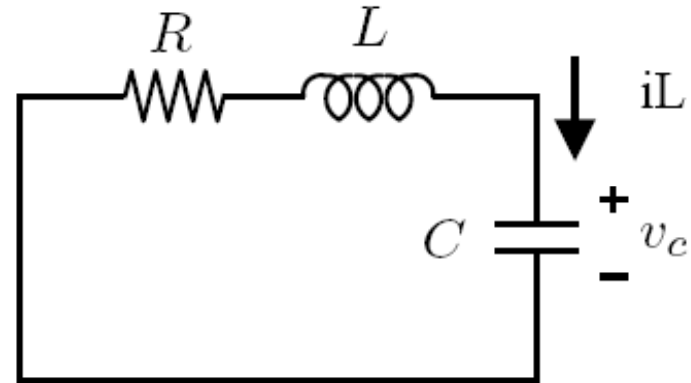
$$v_C(t) = 3.1e^{-12.5t} \sin(48.4t + 75.5^\circ)$$



# Overdamped




•  $R = 5 \Omega$ , overdamped

$$v_C(t) = 4e^{-25t} - e^{-100t} \text{ V}$$

$$i_L(t) = i_C(t) = C \frac{dv_C}{dt}$$
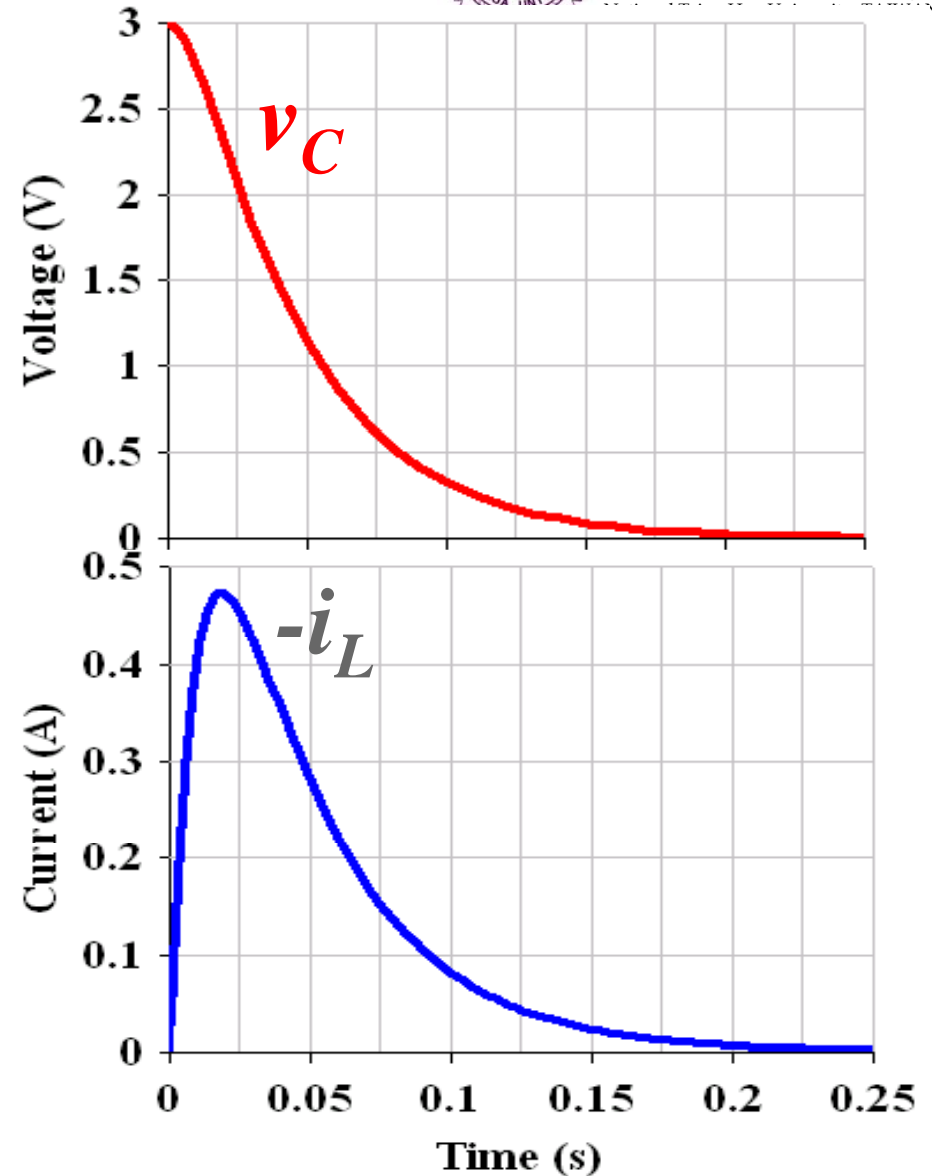
$$i_L(t) = -(e^{-25t} - e^{-100t}) \text{ A}$$





# Critically Damped

- $R = 4 \Omega$ , Critically damped

$$v_C(t) = 3e^{-50t}(1 + 50t) \text{ V}$$

$$i_L(t) = -75te^{-50t} \text{ A}$$

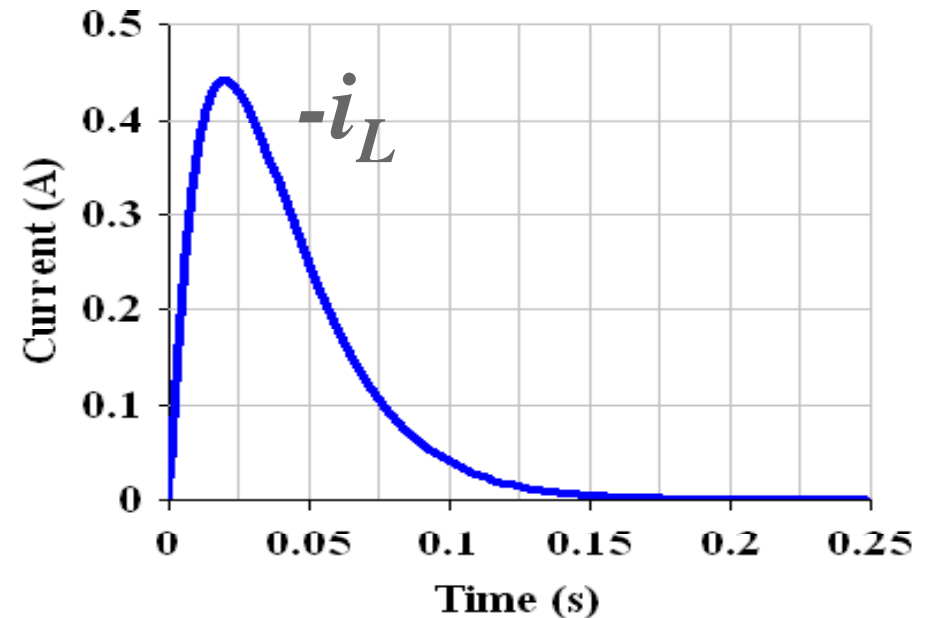
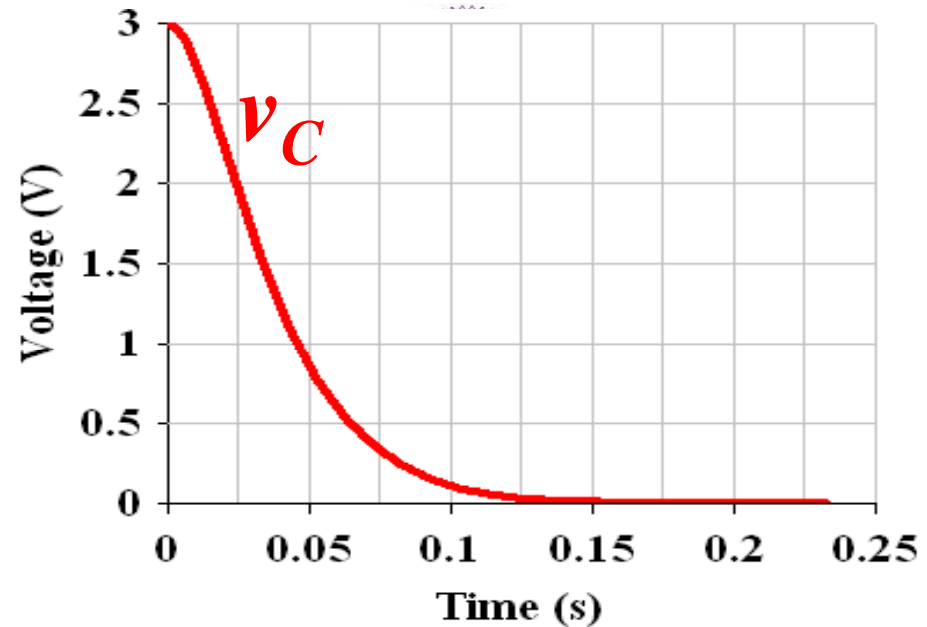


# Under Damped

•  $R = 1 \Omega$ , under damped

$$v_C(t) = 3.1e^{-12.5t} \sin(48.4t + 75.5^\circ) \text{ V}$$
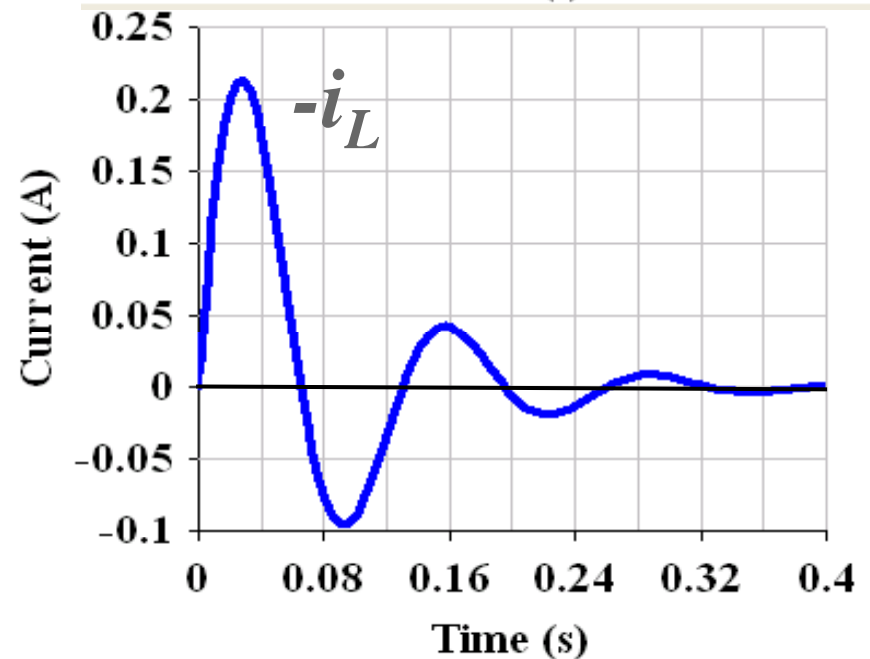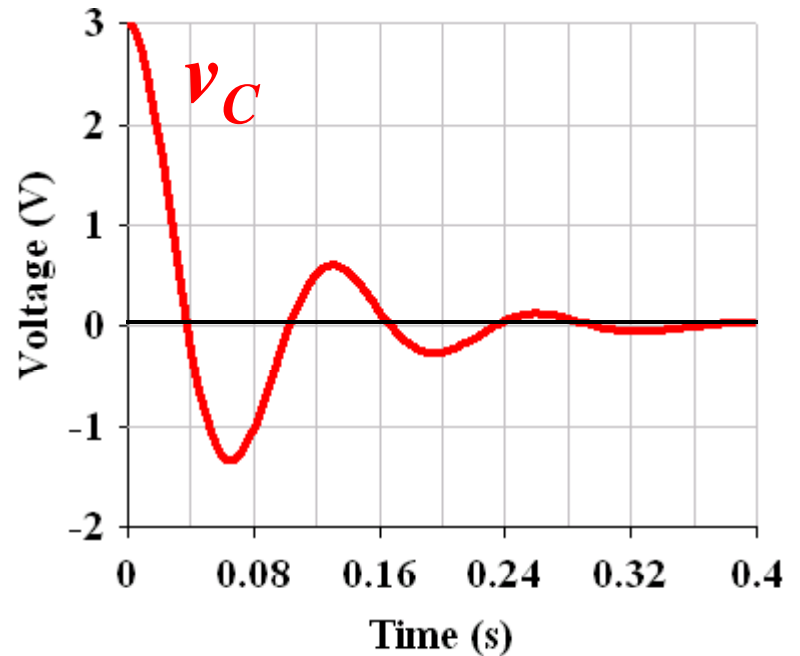
$$i_L(t) = -1.55e^{-12.5t} \sin(48.4t) \text{ A}$$








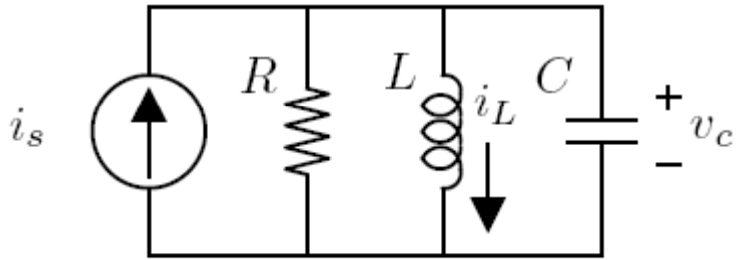
# Natural Response; RLC in parallel

- The RLC circuit can be analyzed by KCL:



$$\begin{aligned} i_s &= \frac{v_c}{R} + i_L + C \frac{dv_c}{dt} \\ &= \frac{L}{R} \frac{di_L}{dt} + i_L + LC \frac{d^2 i_L}{dt^2} \\ \rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L &= \frac{i_s}{LC} \end{aligned}$$

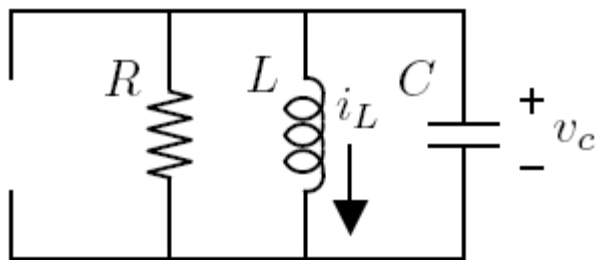- For  $i_s = 0$ , the natural response of the circuit can be derived:



$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

# Natural Response; RLC in parallel



Assume  $i_L = Ae^{st}$ ,

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

$$\rightarrow s^2 Ae^{st} + \frac{1}{RC} s Ae^{st} + \frac{1}{LC} Ae^{st} = 0$$

$$\rightarrow Ae^{st} \left( s^2 + \frac{1}{RC} s + \frac{1}{LC} \right) = 0$$

$$\rightarrow s_1, s_2 = \frac{-\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}}{1}; \frac{-\frac{1}{2RC} \mp \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}}{1}$$
$$= \frac{-\alpha \pm \sqrt{\alpha^2 - \omega_0^2}}{1}; \frac{-\alpha \mp \sqrt{\alpha^2 - \omega_0^2}}{1}$$

$$\text{where } \alpha = \frac{1}{2RC}, \text{ and } \omega_0 = \sqrt{\frac{1}{LC}}$$

The solution can be expressed as follows:

$$i_L = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



# Natural Response; RLC in parallel

Characteristic equation:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0, \quad s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2};$$

- Two distinct real roots:  $\alpha^2 > \omega_0^2 \rightarrow \frac{1}{4R^2C^2} > \frac{1}{LC} \rightarrow L > 4R^2C$ 
  - $s_1$  and  $s_2$  are negative real numbers.
  - $i_L = \underline{A_1 e^{s_1 t} + A_2 e^{s_2 t}}$ .
  - $i_L$  decays exponentially without any oscillations; over-damped.
- Double roots:  $\alpha^2 = \omega_0^2 \rightarrow \frac{1}{4R^2C^2} = \frac{1}{LC} \rightarrow L = 4R^2C$ 
  - $s_1 = s_2 = -\alpha = -\frac{R}{2L}$
  - $i_L = \underline{(A_1 t + A_2) e^{-\alpha t}}$ .
  - $i_L$  decays at a moderate pace, this is referred to as critically-damped



# Natural Response; RLC in parallel






Characteristic equation:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0, \quad s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2};$$

- Two complex roots:  $\alpha^2 - \omega_0^2 < 0 \rightarrow L < 4R^2C$ ;
  - $s_1 = s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\omega_d$ , where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
  - $i_L = \underline{e^{-\alpha t}(A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t))}$ .
  - $i_L$  oscillates within a exponentially-decaying envelope; under-damped.




# Natural Response; RLC in parallel

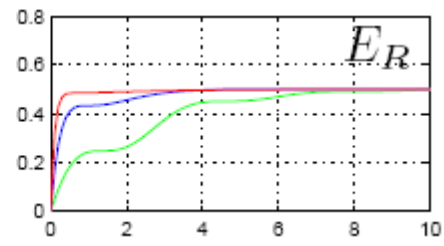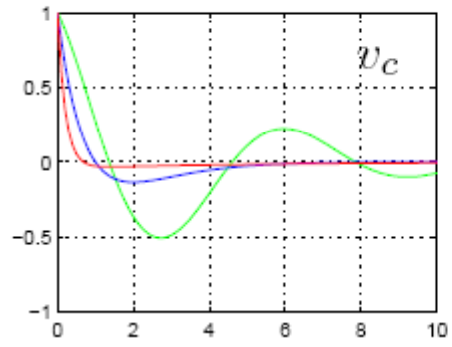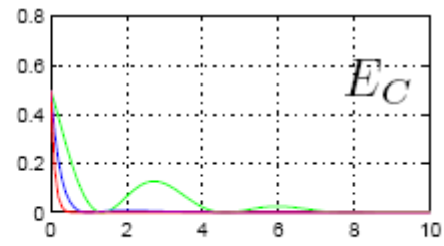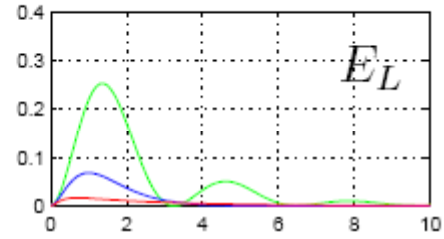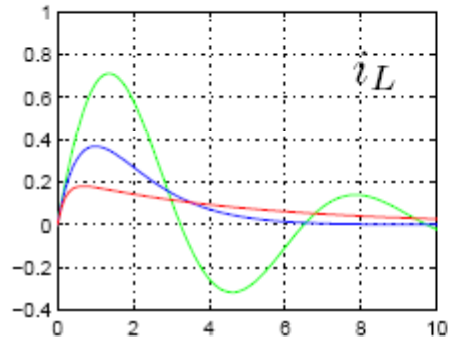


$$L = 1.0 \text{ H}; \quad i_L |_{t=0} = 0$$
$$C = 1.0 \text{ F}; \quad v_C |_{t=0} = 1 \text{ V}$$

$$R = \begin{cases} 2.0 \Omega; & \text{under-damped} \\ 0.5 \Omega; & \text{critically-damped} \\ 0.2 \Omega; & \text{over-damped} \end{cases}$$

# Step Response; RLC in parallel

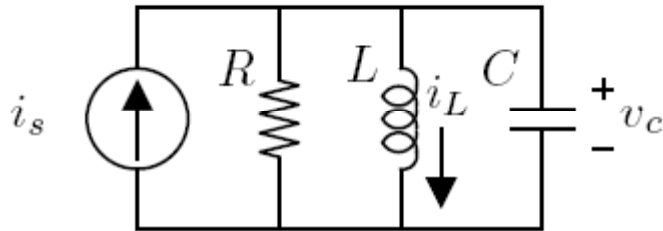

$$i_s = I_s u(t)$$

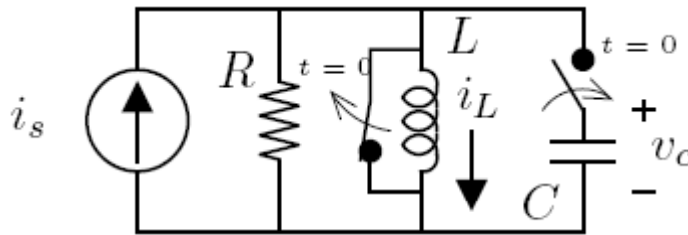

$$v_c |_{t=0} = V_{c0}$$

$$i_L |_{t=0} = I_{L0}$$

By KCL,

$$i_s = \frac{v_c}{R} + i_L + C \frac{dv_c}{dt} = \frac{L}{R} \frac{di_L}{dt} + i_L + LC \frac{d^2 i_L}{dt^2} \rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = \frac{i_s}{LC}$$

Characteristic equation:

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0, \quad s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2};$$



# Step Response; RLC in parallel

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{1}{LC} i_L = \frac{i_s}{LC} = \frac{I_s u(t)}{LC}$$

Step response at steady state:  $i_{Lf} = \underline{I_s}$

• Two distinct real roots:  $\alpha^2 > \omega_0^2 \rightarrow \frac{1}{4R^2 C^2} > \frac{1}{LC} \rightarrow L > 4R^2 C$

•  $s_1$  and  $s_2$  are negative real numbers.

•  $i_L = \underline{A_1 e^{s_1 t} + A_2 e^{s_2 t} + I_s}$

• Double roots:  $\alpha^2 = \omega_0^2 \rightarrow \frac{1}{4R^2 C^2} = \frac{1}{LC} \rightarrow L = 4R^2 C$

•  $s_1 = s_2 = -\alpha = -\frac{R}{2L}$





•  $i_L = \underline{(A_1 t + A_2) e^{-\alpha t} + I_s}$

• Complex roots:  $\alpha^2 - \omega_0^2 < 0 \rightarrow \frac{1}{4R^2 C^2} < \frac{1}{LC} \rightarrow L < 4R^2 C;$

•  $s_1 = s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\omega_d$ , where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ .

•  $i_L = \underline{e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) + I_s}$

# Step Response; RLC in parallel

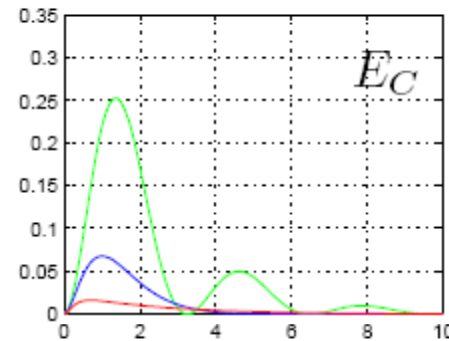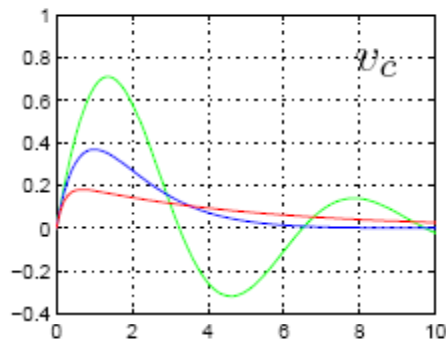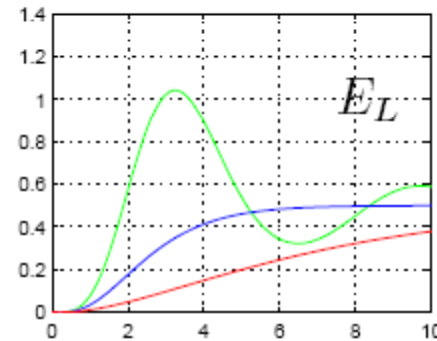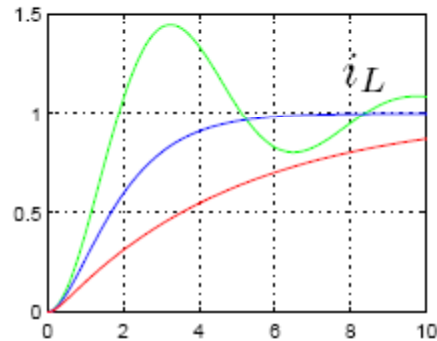

$$L = 1.0 \text{ H}; i_L |_{t=0} = 0$$

$$C = 1.0 \text{ F}; v_C |_{t=0} = 0$$


$$R = \begin{cases} 2.0 \Omega; \text{ under-damped} \\ 0.5 \Omega; \text{ critically-damped} \\ 0.2 \Omega; \text{ over-damped} \end{cases}$$




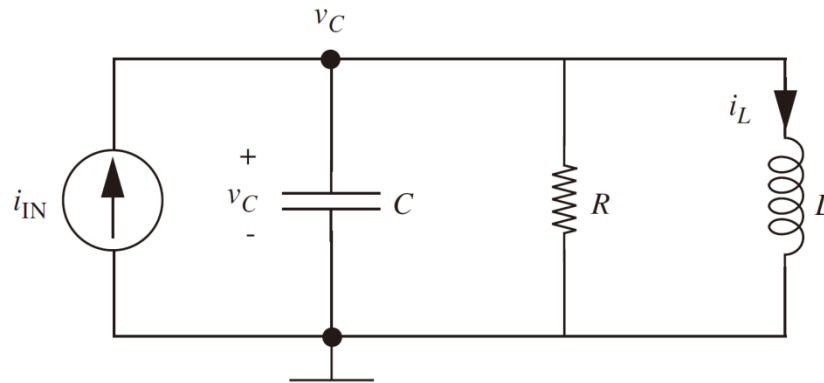
# State-variable Method

- When the circuit states are of primary interest, we can obtain the equations which govern the state evolution, and hence a more direct way to determine the states themselves .




- To find the state equations for the parallel RLC circuit shown above, first, let's chose  $v_C$  and  $i_L$  as State variables.
- To analyze this circuit we replace the capacitor by a voltage source and the inductor by a current source.

# State Equations



- To analyze this circuit, first we replace the capacitor by a voltage source and the inductor by a current source.
- How to find State Equations for  $v_C(t)$  and  $i_L(t)$ ?
- Find the corresponding  $i_C$  and  $v_L$  for state  $v_C(t)$  and  $i_L(t)$  and excitations  $i_{IN}$ .

	$v_C(t)$	$i_L(t)$	$i_{IN}$
$i_C = dv_C/dt$	$-1/R$	$-1$	$1$
$v_L = di_L/dt$	$1$	$0$	$0$

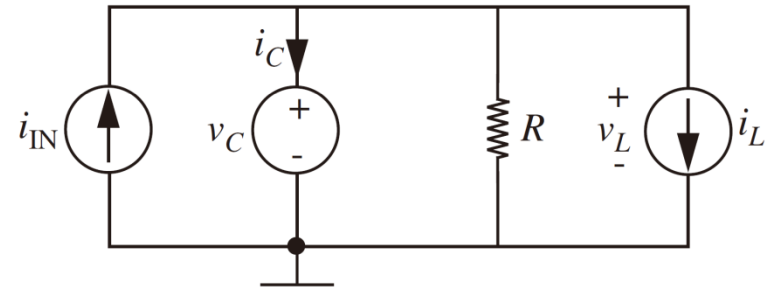

- State Equations for finding  $v_C(t)$  and  $i_L(t)$ .

$$C \frac{dv_C}{dt} = i_C = -\frac{v_C}{R} - i_L + i_{IN}$$

$$L \frac{di_L}{dt} = v_L = v_C - 0i_L + 0i_{IN}$$

$$\begin{bmatrix} \frac{dv_C}{dt} \\ \frac{di_L}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} v_C \\ i_L \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} [i_{IN}]$$

- To analyze this circuit we replace the capacitor by a voltage source and the inductor by a current source

# Summary




- Second Order Circuits have two energy storage elements.
  - Natural frequency  $\omega_0$ .  $\omega_0 = \sqrt{\frac{1}{LC}}$
  - Damping factor  $\alpha$ . SeriesRLC:  $\alpha = \frac{R}{2L}$  and ParalleRLC:  $\alpha = \frac{1}{2RC}$
  - Damped natural frequency.  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
  - Quality factor.  $Q = \frac{\omega_0}{2\alpha}$
- Natural Response depends on circuit parameters and the initial conditions of energy storage elements; There are two energy storage elements.
  - Over damped,  $\alpha > \omega_0$ .
  - Critically damped,  $\alpha = \omega_0$ .
  - Under damped,  $\alpha < \omega_0$ .
- The Intuitive method.
- State-variable method.



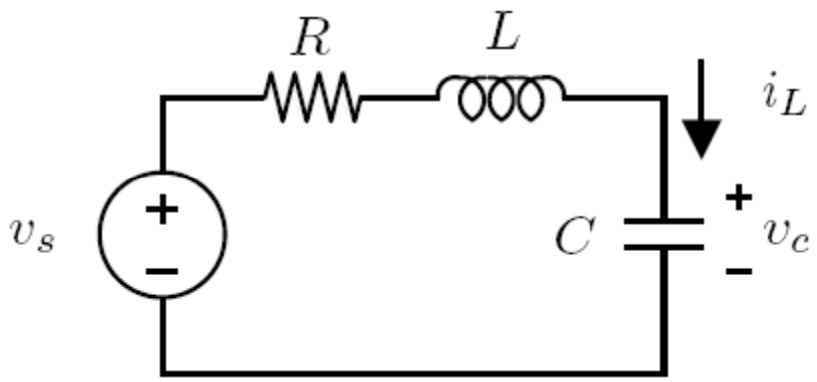
# Natural Response; RLC in series

- The RLC circuit can be analyzed by KVL:



$$\begin{aligned}
 v_s &= Ri_L + v_L + v_c \\
 &= RC \frac{dv_c}{dt} + LC \frac{d^2v_c}{dt^2} + v_c \\
 \rightarrow \frac{d^2v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c &= \frac{v_s}{LC}
 \end{aligned}$$

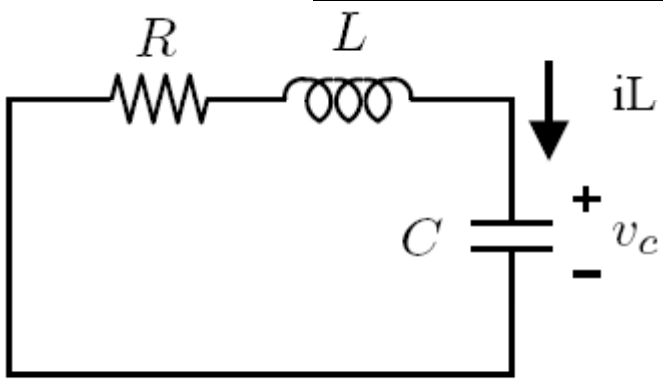- For  $v_s = 0$ , the natural response of the circuit can be derived:



$$\frac{d^2v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = 0$$

# Natural Response; RLC in series



Assume  $v_c = Ae^{st}$ ,

$$\frac{d^2v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = 0$$

$$\rightarrow s^2 Ae^{st} + \frac{R}{L} s Ae^{st} + \frac{1}{LC} Ae^{st} = 0$$

$$\rightarrow Ae^{st} \left( s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0$$

$$\begin{aligned} \rightarrow s_1, s_2 &= \frac{-\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}{1}; \frac{-\frac{R}{2L} \mp \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}{1} \\ &= \frac{-\alpha \pm \sqrt{\alpha^2 - \omega_0^2}}{1}; \frac{-\alpha \mp \sqrt{\alpha^2 - \omega_0^2}}{1} \end{aligned}$$

$$\text{where } \alpha = \frac{R}{2L}, \text{ and } \omega_0 = \sqrt{\frac{1}{LC}}$$

The solution can be expressed as follows:

$$v_c = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



# Natural Response; RLC in series

Characteristic equation:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0, \quad s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2};$$

- Two distinct real roots:  $\alpha^2 > \omega_0^2 \rightarrow \frac{R^2}{4L^2} > \frac{1}{LC} \rightarrow R^2 > \frac{4L}{C}$ 
  - $s_1$  and  $s_2$  are negative real numbers.
  - $v_c = \underline{A_1 e^{s_1 t} + A_2 e^{s_2 t}}$ .
  - $v_c$  decays exponentially without any oscillations; this is referred to as over-damped.
- Double roots:  $\alpha^2 = \omega_0^2 \rightarrow \frac{R^2}{4L^2} = \frac{1}{LC} \rightarrow R^2 = \frac{4L}{C}$ 
  - $s_1 = s_2 = -\alpha = -\frac{R}{2L}$
  - $v_c = \underline{(A_1 t + A_2) e^{-\alpha t}}$ .
  - $v_c$  decays at a moderate pace, this is referred to as critically-damped



# Natural Response; RLC in series

Characteristic equation:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0, \quad s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2};$$

• Two complex roots:  $\alpha^2 - \omega_0^2 < 0 \rightarrow R^2 < \frac{4L}{C}$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\omega_d, \text{ where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}.$$

Let

$$y_1 = e^{(-\alpha + j\omega_d)t} = e^{-\alpha t} (\cos(\omega_d t) + j \sin(\omega_d t))$$

$$y_2 = e^{(-\alpha - j\omega_d)t} = e^{-\alpha t} (\cos(\omega_d t) - j \sin(\omega_d t))$$






Any linear combination of  $y_1$  and  $y_2$  will be a valid solution to the differential equation.

$$v_c = A_1 \left( \frac{1}{2} (y_1 + y_2) \right) + A_2 \left( \frac{1}{j2} (y_1 - y_2) \right) = e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t))$$

$v_c$  oscillates within an exponentially-decaying envelope, this is referred to as under-damped



# Natural Response; RLC in series

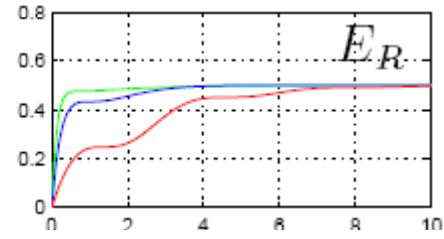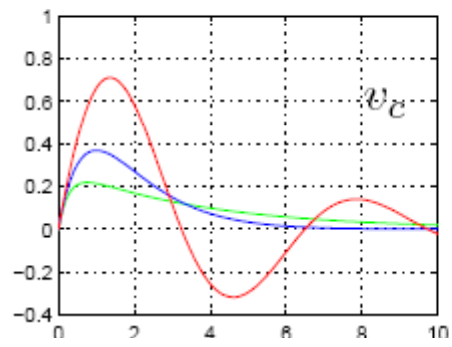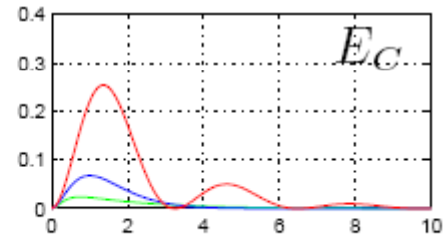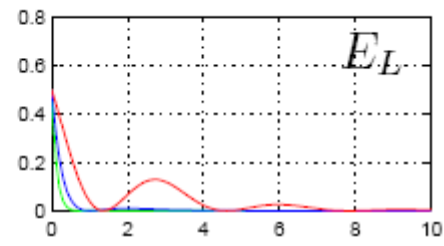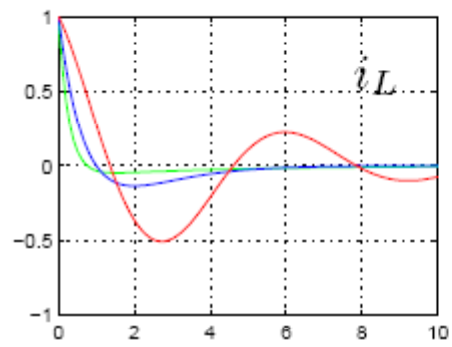



$$L = 1.0 \text{ H}; \quad i_L |_{t=0} = 1 \text{ A}$$
$$C = 1.0 \text{ F}; \quad v_C |_{t=0} = 0$$

$$R = \begin{cases} 0.5 \Omega; & \text{under-damped} \\ 2.0 \Omega; & \text{critically-damped} \\ 4.0 \Omega; & \text{over-damped} \end{cases}$$





# Step Response; RLC in series

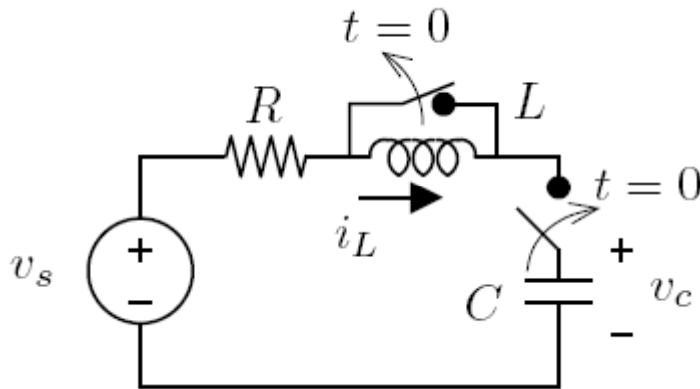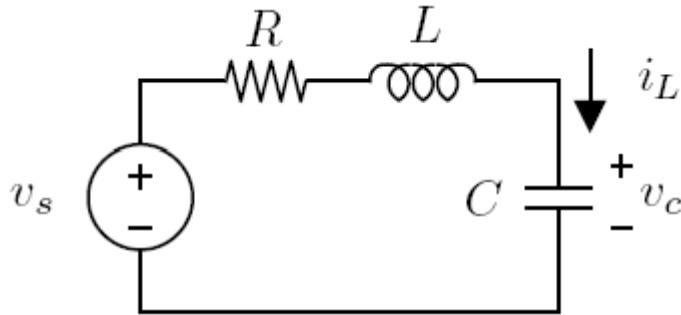

$$v_s = V_s u(t)$$

$$v_c |_{t=0} = V_{c0}$$

$$i_L |_{t=0} = I_{L0}$$

By KVL,

$$v_s = Ri_L + v_L + v_C = RC \frac{dv_c}{dt} + LC \frac{d^2 v_c}{dt^2} + v_c \rightarrow \frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = \frac{v_s}{LC}$$



## Step Response; RLC in series

$$\frac{d^2 v_c}{dt^2} + \frac{R}{L} \frac{dv_c}{dt} + \frac{1}{LC} v_c = \frac{v_s}{LC} = \frac{V_s u(t)}{LC}$$

Step response at steady state:  $v_{cf} = \underline{V_s}$

• Two distinct real roots:  $\alpha^2 > \omega_0^2 \rightarrow \frac{R^2}{4L^2} > \frac{1}{LC} \rightarrow R^2 > \frac{4L}{C}$ ;

•  $s_1$  and  $s_2$  are negative real numbers.

•  $v_c = \underline{A_1 e^{s_1 t} + A_2 e^{s_2 t} + V_s}$

• Double roots:  $\alpha^2 = \omega_0^2 \rightarrow \frac{R^2}{4L^2} = \frac{1}{LC} \rightarrow R^2 = \frac{4L}{C}$ ;

•  $s_1 = s_2 = -\alpha = -\frac{R}{2L}$





•  $v_c = \underline{(A_1 t + A_2) e^{-\alpha t} + V_s}$

• Complex roots:  $\alpha^2 - \omega_0^2 < 0 \rightarrow R^2 < \frac{4L}{C}$ ;

•  $s_1 = s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\omega_d$ , where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ .

•  $v_c = \underline{e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) + V_s}$

# Step Response; RLC in series

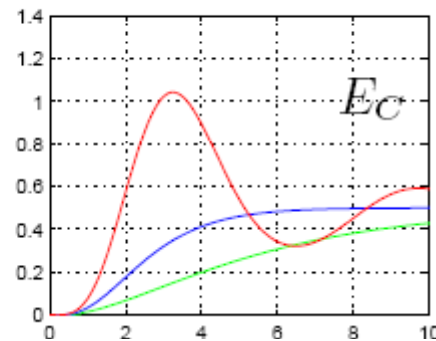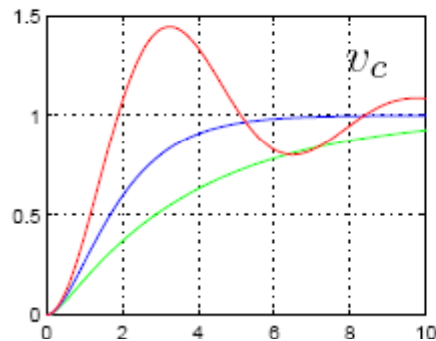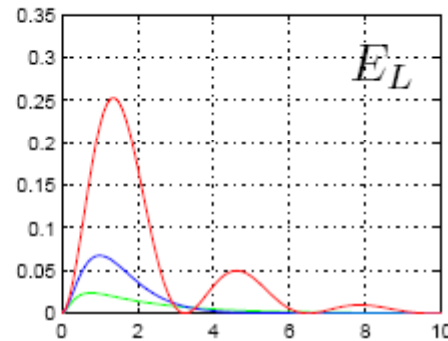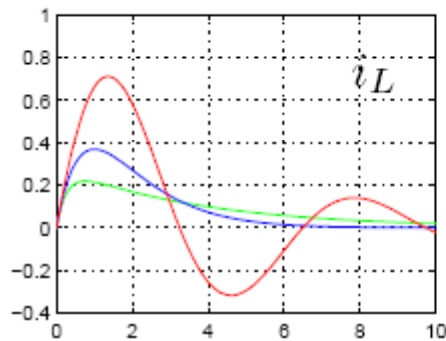

$$\begin{aligned}
 L &= 1.0 \text{ H}; i_L |_{t=0} = 0; \\
 C &= 1.0 \text{ F}; v_C |_{t=0} = 0;
 \end{aligned}
 \quad
 R = \begin{cases} 0.5 \Omega; & \text{under-damped} \\ 2.0 \Omega; & \text{critically-damped} \\ 4.0 \Omega; & \text{over-damped} \end{cases}$$