

Sinusoidal Steady State Impedance and Frequency Response

Chenhsin Lien and Po-Tai Cheng

CENTER FOR ADVANCED POWER TECHNOLOGIES

Dept. of Electrical Engineering

National Tsing Hua University

Hsinchu, TAIWAN




CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

Response to Sinusoidal Drive



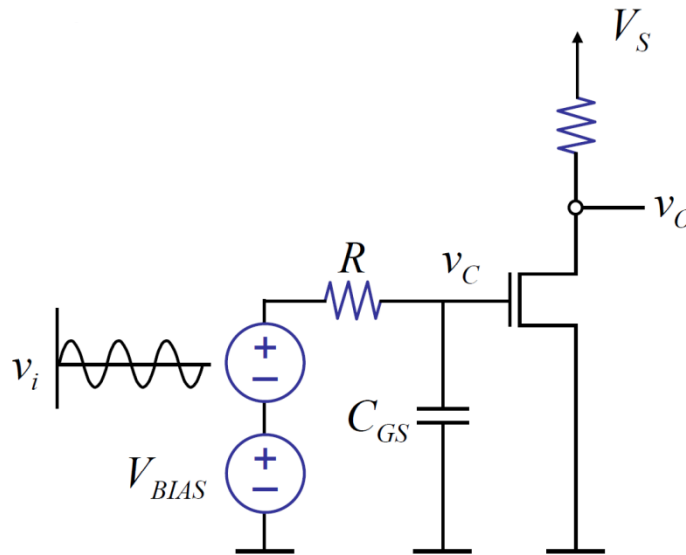- Response of networks to sinusoidal drive.







- Sinusoids is important because signals can be represented as a sum of sinusoids.
- Response to sinusoids of various frequencies –also called as frequency response --tells us a lot about the system.

Sinusoids



- Sinusoids is important because signals can be represented as a sum of sinusoids.

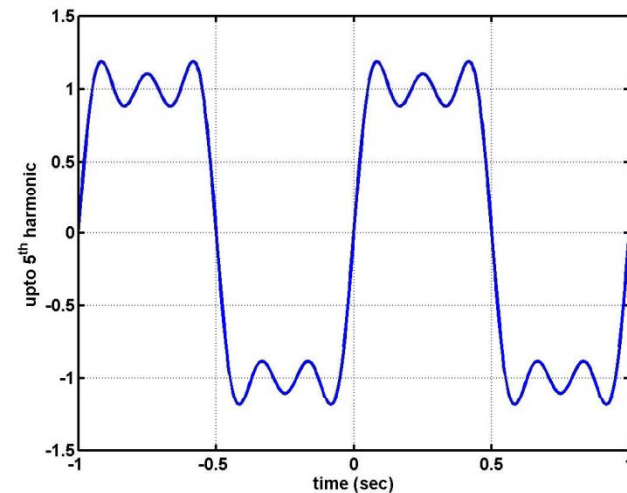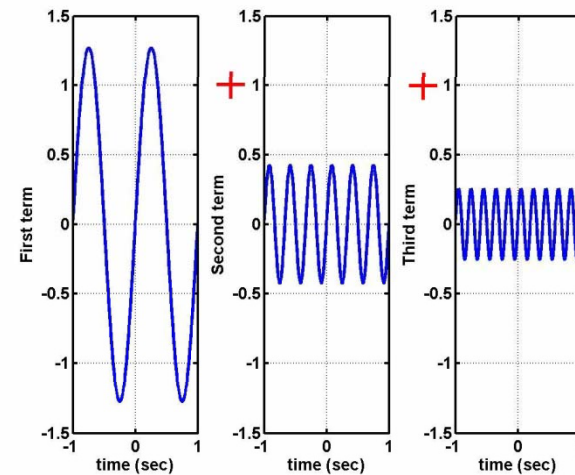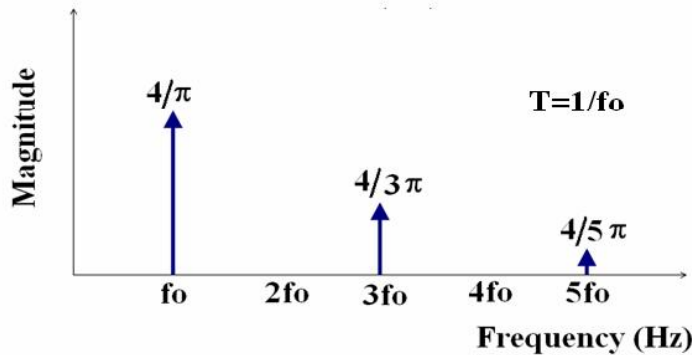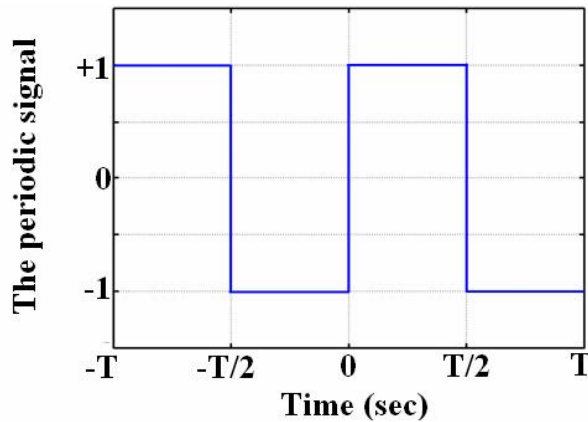
$$x(t) = \sum_{n=1,3,5,\dots}^{\infty} \frac{4}{n\pi} \sin(n\omega_0 t)$$



Response to Sinusoidal Drive



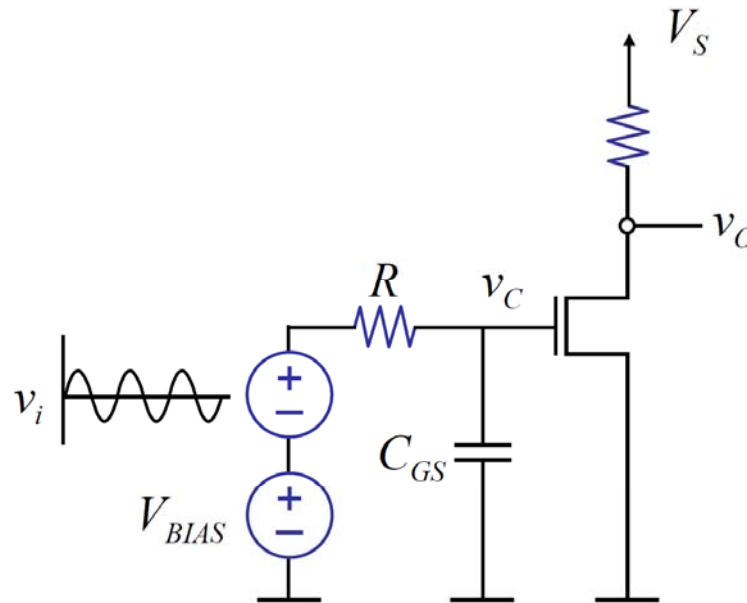- What is the response of the following amplifier to a sinusoidal drive?




- Observing the amplitude of v_o as the frequency of the input v_i changed.
- We found the amplitude of v_o decreased with frequency.
- We also found that v_o shifted as frequency changes (phase).
- Need to study behavior of networks for sinusoidal drive.

Sinusoidal Response of RC Network



- The Circuits:

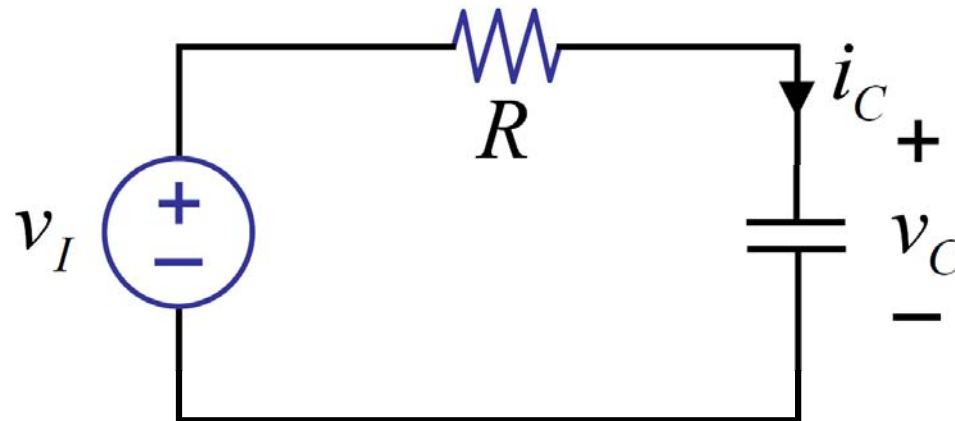


- The input:


$$v_I(t) = V_i \cos(\omega t) \quad \text{for } t \geq 0 \quad V_i \text{ is real.}$$
$$= 0 \quad \text{for } t < 0$$

- Assume zero initial state:

$$v_C(0) = 0 \text{ V}$$

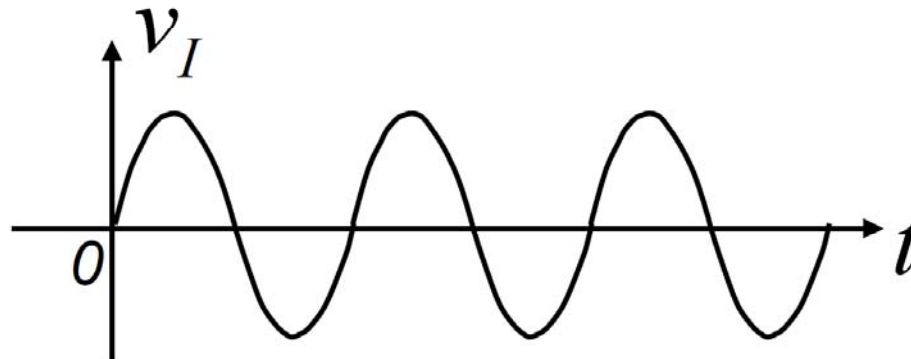


Usual Approach

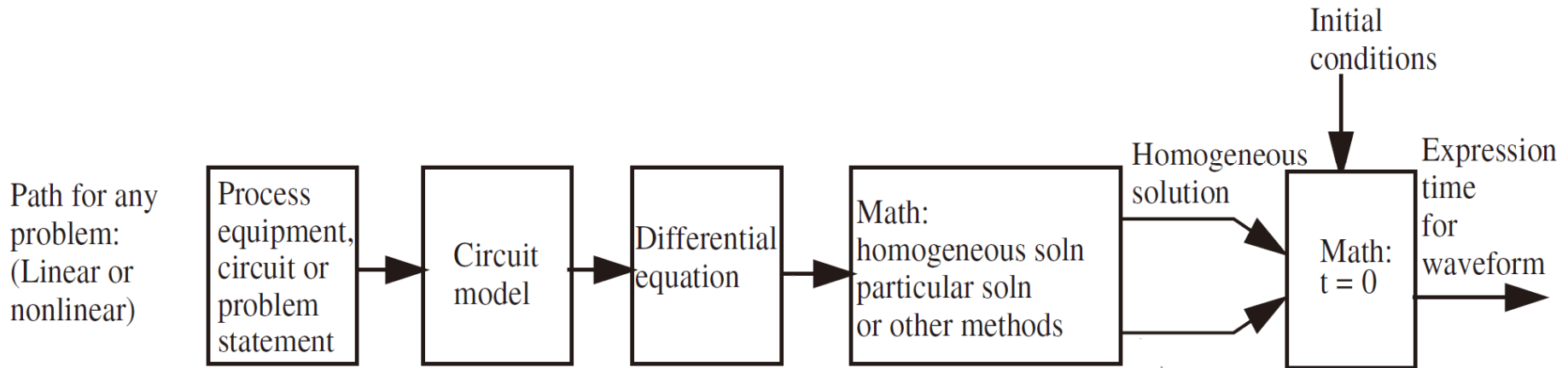

- Set up the differential equation.
- Find the particular solution, v_P .
- Find the homogeneous solution, v_H .
- The total solution is the sum of the particular and homogeneous solutions, $v = v_P + v_H$.
- Use the initial conditions to solve for the remaining constants.

Usual Approach

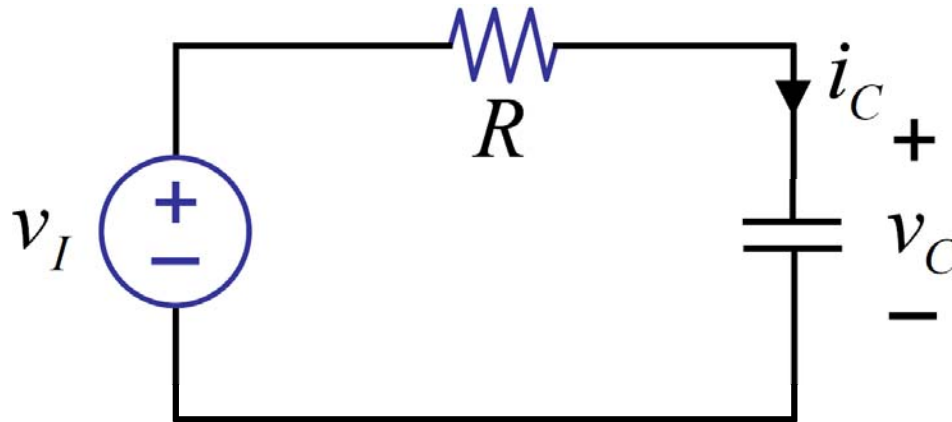

- Set up the differential equation.

$$RC \frac{dv_C}{dt} + v_C = v_I = V_i \cos(\omega t)$$

- That was easy.

Usual Approach



- Find the particular solution, v_P .

$$RC \frac{dv_P}{dt} + v_P = V_i \cos(\omega t)$$

- Try $v_P = K$ $RC \frac{dK}{dt} + K = K \neq V_i \cos(\omega t) \Rightarrow$ Noop

- Try $v_P = A \cos(\omega t)$ $- A \omega RC \sin(\omega t) + A \cos(\omega t) \neq V_i \cos(\omega t) \Rightarrow$ Noop

- Try $v_P = A \cos(\omega t + \phi)$

$$- A \omega RC \sin(\omega t + \phi) + A \cos(\omega t + \phi) = V_i \cos(\omega t)$$

$$- A \omega RC \sin(\omega t) \cos(\phi) - A \omega RC \cos(\omega t) \sin(\phi) +$$

$$A \cos(\omega t) \cos(\phi) - A \sin(\omega t) \sin(\phi) = V_i \cos(\omega t)$$

$$\Rightarrow \sqrt{1 + \omega^2 R^2 C^2} A \cos(\omega t + \phi + \delta) = V_i \cos(\omega t) \quad \text{where } \delta = \tan^{-1}(\omega RC)$$


- Worked but what a trigonometry nightmare.

Sneaky Approach



CAPT

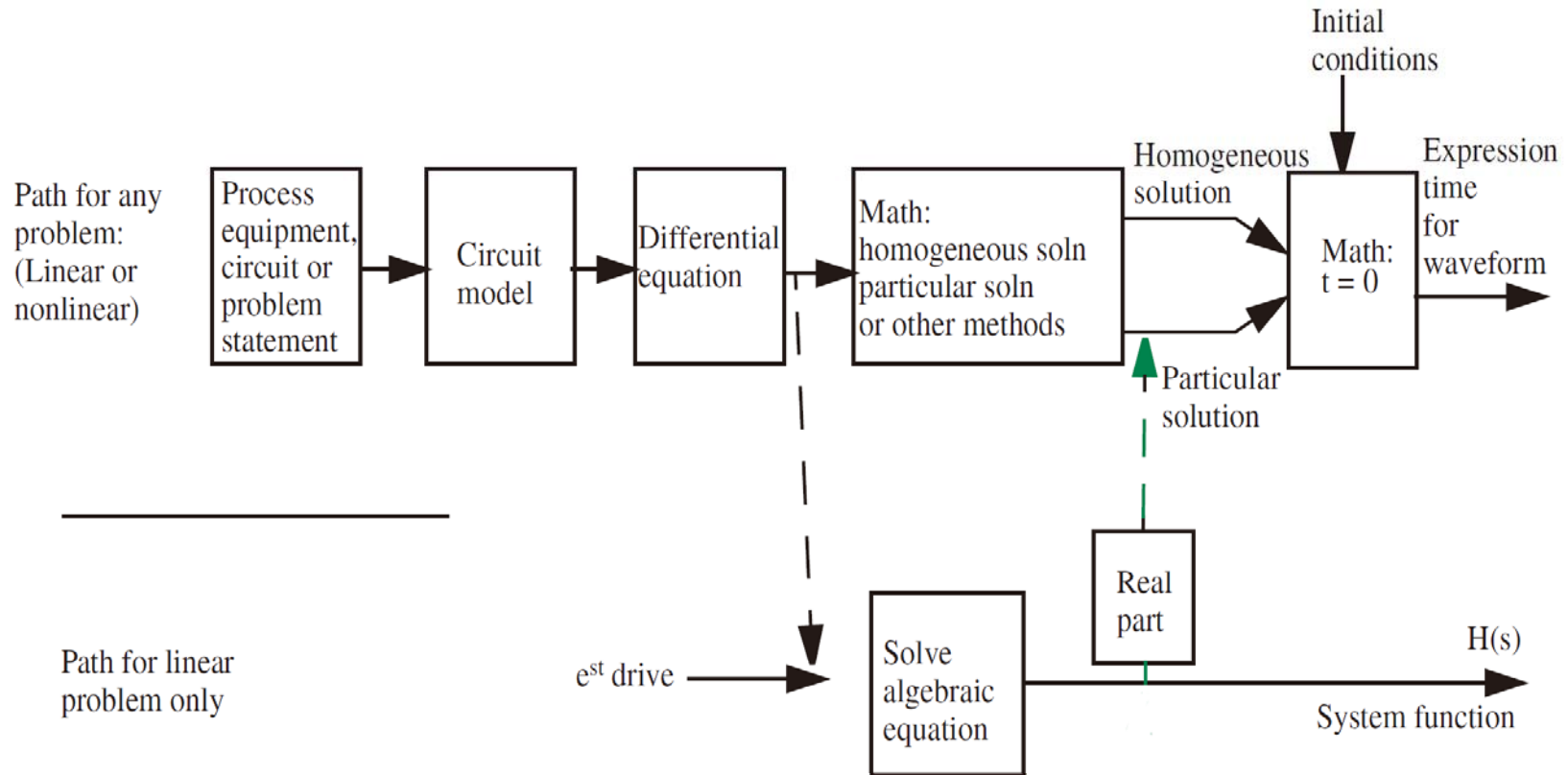
Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN



- Instead of input: $v_I(t) = V_i \cos(\omega t)$
- Find particular solution to another input: $v_I(t) = V_i e^{st}$

$$v_I(t) = V_i e^{st}$$

The Effort of Various Approaches

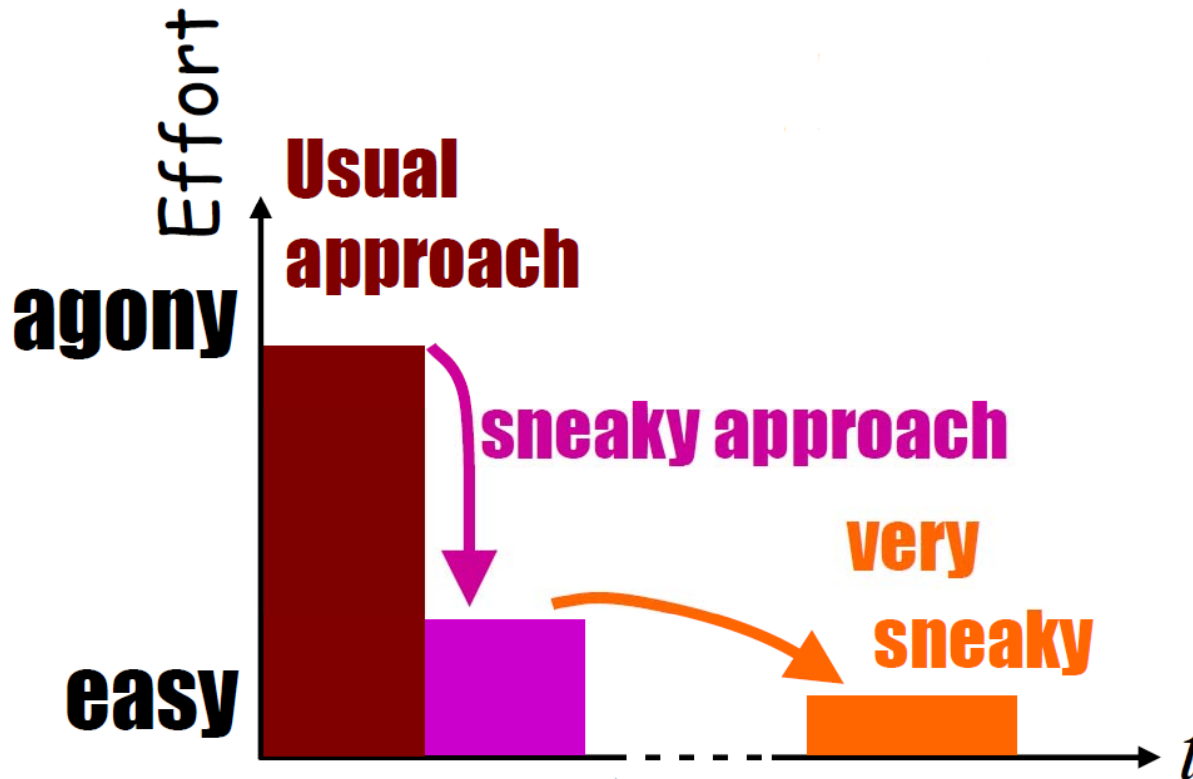

Charles Proteus Steinmetz

German-American mathematician and electrical engineer (1865-1923)

Sneaky Approach



- The new drive: $v_I(t) = V_i e^{st}$
- Find the particular solution, v_{PS} :

$$RC \frac{dv_{PS}}{dt} + v_{PS} = V_i e^{st}$$

- Try solution: $v_{PS} = V_P e^{st}$

$$RC \frac{dV_P e^{st}}{dt} + V_P e^{st} = V_i e^{st} \Rightarrow sRCV_P e^{st} + V_P e^{st} = V_i e^{st}$$

$$\Rightarrow (sRC + 1)V_P = V_i$$

$$\Rightarrow V_P = \frac{V_i}{1 + sRC} \quad \Rightarrow v_{PS} = \frac{V_i}{1 + sRC} e^{st}$$

- $v_{PS} = \frac{V_i}{1 + sRC} e^{st}$ is particular solution for input $v_I(t) = V_i e^{st}$


- Easy!!

Sneaky Approach



- Similarly: $v_{PS} = \frac{V_i}{1 + j\omega RC} e^{j\omega t}$ is particular solution for input $v_I(t) = V_i e^{j\omega t}$
- We have complex amplitude V_P .
- Fact 1: Finding the response to $v_{PS} = V_P e^{j\omega t}$ is easy.
- Fact 2: From Euler relation, $e^{j\omega t} = \cos \omega t + j \sin \omega t$
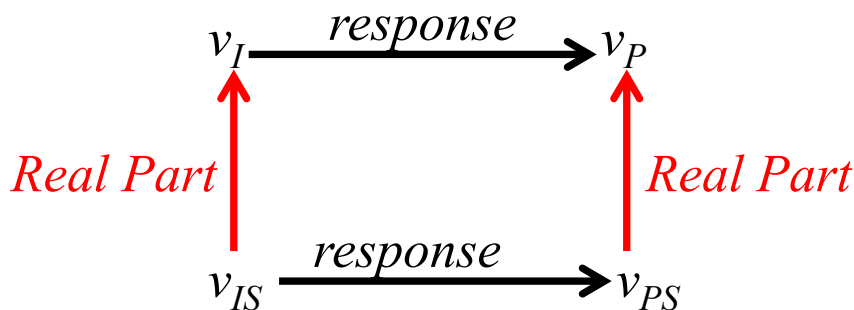
$$v_I(t) = V_i \cos \omega t = \text{Re}[V_i e^{j\omega t}]$$



- An inverse superposition argument, assuming system is real, linear.

Sneaky Approach



- Let's try to find v_P from v_{PS} : $v_I(t) = V_i e^{st}$

$$v_P = \text{Re}[v_{PS}] = \text{Re}[V_p e^{j\omega t}]$$

$$= \text{Re}\left[\frac{V_i}{1 + j\omega RC} e^{j\omega t}\right]$$

$$= \text{Re}\left[\frac{V_i(1 - j\omega RC)}{1 + \omega^2 R^2 C^2} e^{j\omega t}\right]$$

$$= \text{Re}\left[\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j\phi} e^{j\omega t}\right], \quad \tan \phi = -\omega RC$$

$$= \text{Re}\left[\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j(\omega t + \phi)}\right]$$

- The particular solution, v_P for $v_I(t) = V_i \cos(\omega t)$

$$v_P = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi)$$

Sneaky Approach



- Recalled from Chapter 10, the homogeneous solution, v_H :

$$v_H = Ae^{-\frac{t}{RC}}$$

- The total solution is the sum of the particular and homogeneous solutions, $v = v_P + v_H$:

$$v_C = v_P + v_H = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi) + Ae^{-\frac{t}{RC}} \quad \text{where } \tan \phi = -\omega RC$$

- Given: $v_C(0) = 0 \text{ V} \Rightarrow v_C = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega 0 + \phi) + Ae^{-\frac{0}{RC}} = 0$

- So

$$A = -\frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\phi)$$



Sinusoidal Steady State (SSS)



- The total solution :

$$v_C = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \left(\cos(\omega t + \phi) - \cos \phi \cdot e^{-\frac{t}{RC}} \right)$$

$$\text{where } \tan \phi = -\omega RC$$

- We are usually interested only in the particular solution for sinusoids, i.e. after transients have died.
- Notice when $t \rightarrow \infty$, $v_C \rightarrow v_P$ as $e^{-\frac{t}{RC}} \rightarrow 0$

$$v_C = v_P = \frac{V_i}{\sqrt{1 + \omega^2 R^2 C^2}} \cos(\omega t + \phi)$$

- Described as: **Sinusoidal Steady State (SSS)**

Sinusoidal Steady State



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- All information about **Sinusoidal Steady State** is contained in V_P

$$V_P = \frac{V_i}{1 + j\omega RC}$$

- A complex amplitude!
- Steps (1) find the homogeneous solution (2) find the total solution and determine remaining constants from the initial conditions **were a waste of time!**


- Let's rewrite $\frac{V_P}{V_i} = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j\phi}$ where $\tan \phi = -\omega RC$

$$\text{magnitude: } \left| \frac{V_P}{V_i} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$
$$\text{Phase } \phi: \angle \frac{V_P}{V_i} = -\tan^{-1} \omega RC$$

Sinusoidal Steady State



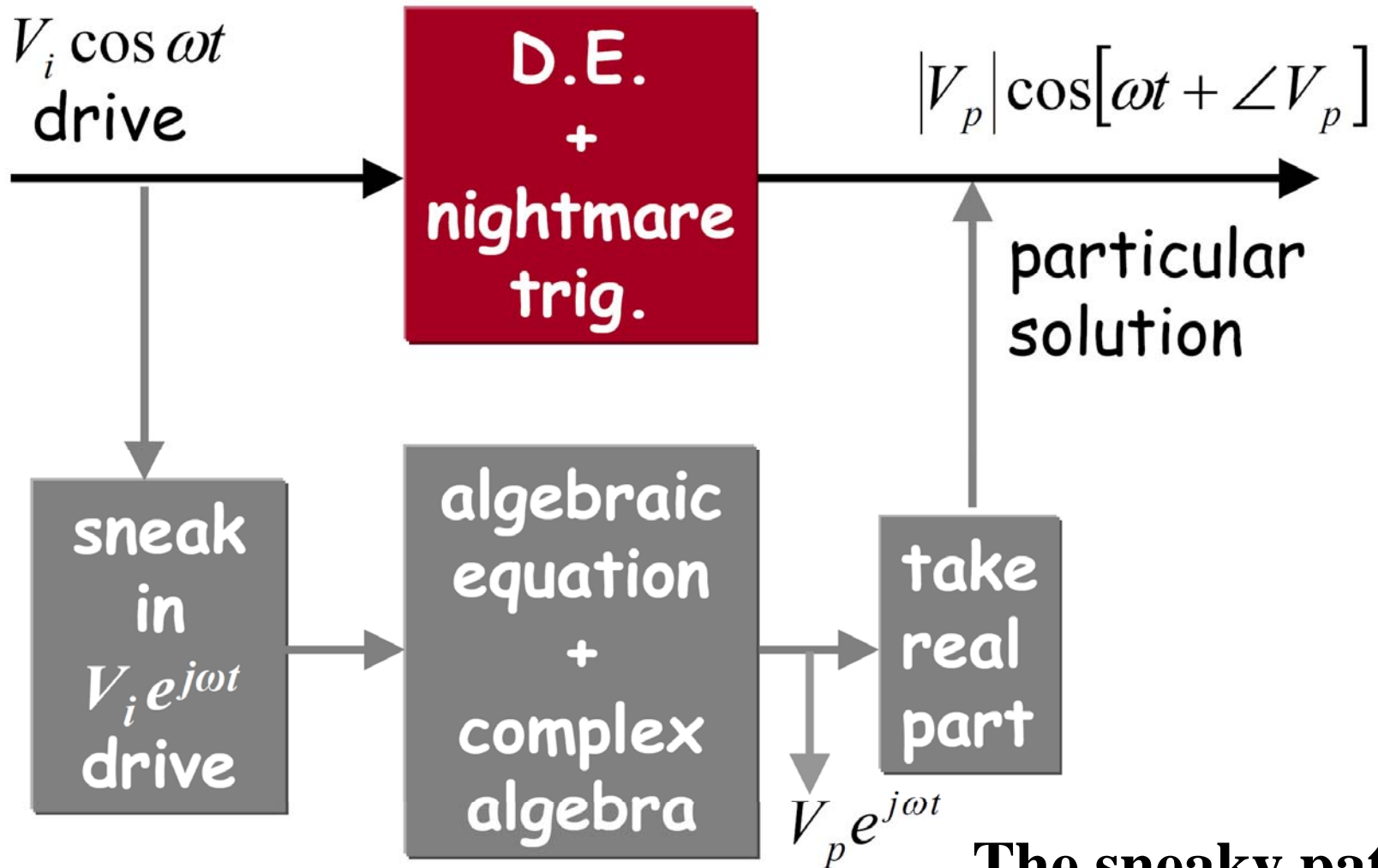- Visualizing the process of finding the particular solution v_P




The sneaky path!

Magnitude Plot



- **Transfer function** $H(j\omega) = \frac{V_P}{V_i}$
- **Transfer function**, also known as a system function, is the ratio of the complex amplitude of the network output to the complex amplitude of the input.

Magnitude: $\left| \frac{V_P}{V_i} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

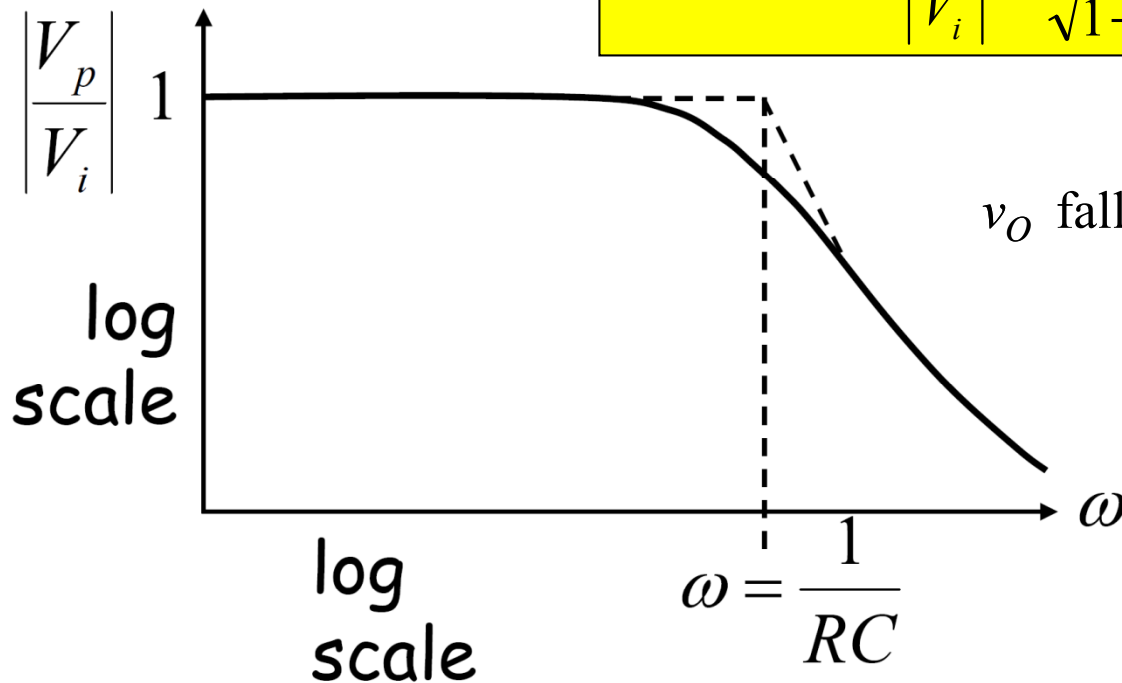

v_O fall off for high frequencies!

Bel and Decibel (dB)



- Curious units called “**decibels**” are used by EEs to measure electric power, voltage, current, the gain or loss of amplifiers, and the insertion loss of filters.
- A **bel** (symbol **B**) is a unit of measure of ratios of power levels, i.e. relative power levels.
 - $1\text{B} = \log_{10}(P_1/P_2)$ where P_1 and P_2 are power levels.
 - The bel is a logarithmic measure
 - 1 bels corresponds to a ratio of 10:1
- The bel is too large for everyday use, so the **decibel (dB)**, equal to 0.1B, is more commonly used.
 - $10\text{dB} = \log_{10}(P_1/P_2)$
 - 10 dB corresponds to a ratio of 10:1
- The word decibel is a reference to powers of ten and to Alexander Graham Bell.

Logarithmic Measure for Power



- To express a power in terms of decibels, one starts by choosing a reference power, $P_{\text{reference}}$, and writing.

$$\text{Power } P \text{ in decibels} = 10 \log_{10}(P/P_{\text{reference}})$$

- Example:
 - Express a power of 50 mW in decibels relative to 1 watt.
 - $P \text{ (dB)} = 10 \log_{10}(50 \times 10^{-3}) = -13 \text{ dB}$
- Use logarithmic scale to express power ratios varying over a large range

$$\text{dB: } 10 \log \left(\frac{P_1}{P_2} \right) \text{ (dB)}$$

Note: dB is not a unit for a physical quantity since power ratio is unitless. It is just a notation to remind us we are in the log scale.

Decibels for Measuring Transfer Function Magnitude?



- Decibels provide a measure of relative power levels.
- They can also be used in transfer functions.
- The key is in realizing that $P \propto V^2 \propto I^2$
- Thus

$$\text{dB} = 10 \log \left(\frac{V_{out}^2}{V_{in}^2} \right) = 20 \log \left(\frac{V_{out}}{V_{in}} \right)$$

- **Transfer function**

$$\left| H(j\omega) \right|_{\text{in dB}} = 20 \log(H(j\omega))$$

Neper



- The "Neper" (after John Napier 1550-1617) is a unit based on Napierian logarithms to the base e .

$$\text{Neper} = \log_e \sqrt{\frac{P_{out}}{P_{in}}} = \frac{1}{2} \log_e \frac{P_{out}}{P_{in}} = \log_e \frac{V_{out}}{V_{in}}$$


- The growth in popularity of the deciBel, since 1929, has been so great that it is now almost a household word throughout all branches of Electrical Engineering and Acoustics.
- The Neper is used in some European countries, but is less commonly encountered than the dB.

Phase Plot



- Transfer function $H(j\omega) = \frac{V_P}{V_i}$
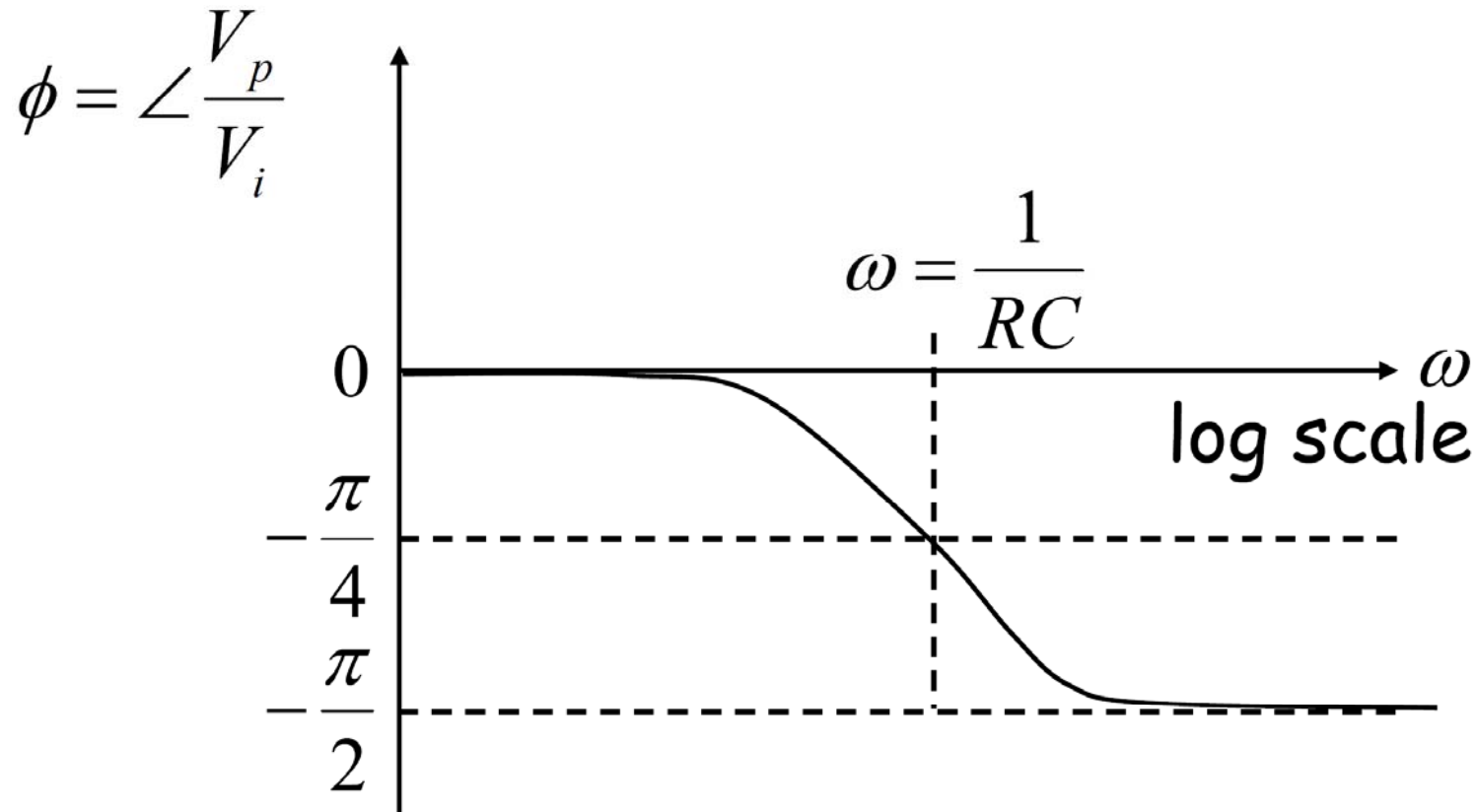
$$\text{Phase } \phi: \quad \phi = \angle \frac{V_P}{V_i} = -\tan^{-1} \omega RC$$



Is there an even simpler way to get V_P ?



- Let us look more closely at V_P

$$V_P = \frac{V_i}{1 + j\omega RC}$$

- Divide numerator and denominator by $j\omega C$.

$$V_P = V_i \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R}$$

- Hmmm...looks like a voltage divider relationship.


$$V_P = V_i \frac{Z_C}{Z_C + R}$$

- Let's explore further...

The Impedance Model



- Consider resistor:

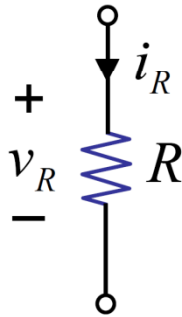


$$i_R = I_r e^{j\omega t} \quad \text{and} \quad v_R = V_r e^{j\omega t}$$
$$v_R = Ri_R \Rightarrow V_r e^{j\omega t} = RI_r e^{j\omega t}$$

- For resistor

$$V_r = RI_r$$

- For capacitor

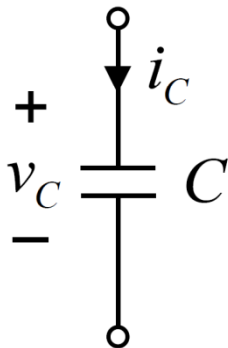


$$i_c = I_c e^{j\omega t} \quad \text{and} \quad v_c = V_c e^{j\omega t}$$
$$i_c = C \frac{dv_c}{dt} \Rightarrow I_c e^{j\omega t} = CV_c j\omega e^{j\omega t}$$

$$V_c = \frac{1}{j\omega C} I_c = Z_C I_c$$

The Impedance Model



• For inductor:

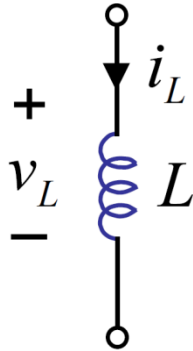

$$i_L = I_l e^{j\omega t} \quad \text{and} \quad v_L = V_l e^{j\omega t}$$

$$v_L = L \frac{di_L}{dt} \Rightarrow V_l e^{j\omega t} = L I_l j \omega e^{j\omega t}$$


$$V_l = j\omega L I_l = Z_L I_l$$

The Impedance Model



• In other words,

• Capacitor

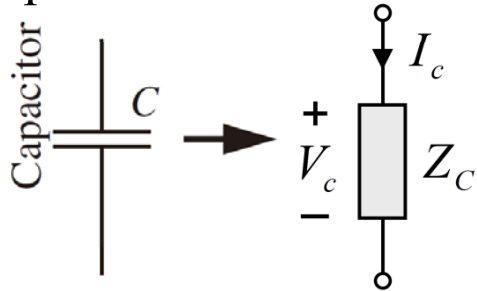


$$V_c = Z_C I_c$$
$$Z_C = \frac{1}{j\omega C}$$

Z_C is called **impedance**


For a drive of the form $V_C e^{j\omega t}$, complex amplitude V_C is related to the complex amplitude I_C algebraically, by a **generalization of Ohm's Law.**

• Inductor

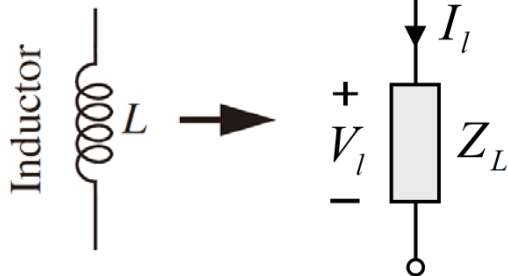

$$V_l = Z_L I_l$$
$$Z_L = j\omega L$$

• Resistor

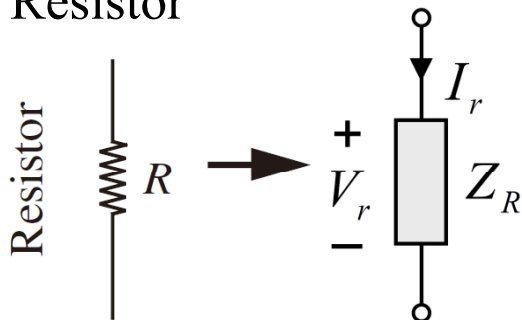

$$V_r = Z_R I_r$$
$$Z_R = R$$

Z_C , Z_L , and Z_R , are called **impedance**




Symbol Conventions

- **DC or operating-point variables:** uppercase symbols with uppercase subscripts (for example, V_A).
- **Total instantaneous variables:** lowercase symbols with uppercase subscripts (for example, v_A).
- **Incremental instantaneous variables:** lowercase symbols with lowercase subscripts (for example, v_a).
- **Complex amplitudes** or complex amplitudes of incremental components, and real amplitudes of sinusoidal input sources: uppercase symbols with lowercase subscripts (for example, V_a).


Back to RC Network



- Circuit:

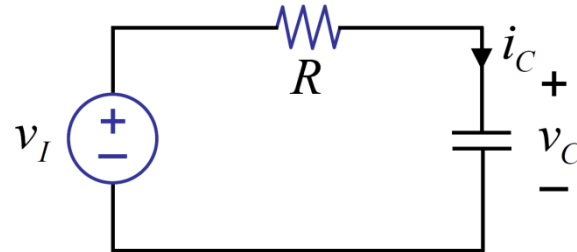

- Impedance model:

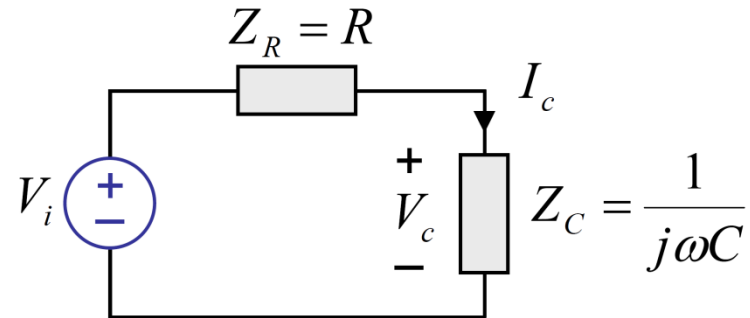

- To find V_P

$$V_P = V_i \frac{Z_C}{Z_C + R} = V_i \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \Rightarrow V_P = \frac{1}{1 + j\omega RC} V_i$$

Done!

- **All our old friends apply! KVL, KCL, superposition...**

The Impedance Method



- **1st Step:** Replace the (sinusoidal) sources by their complex (or real) amplitudes. $v_A = V_a \cos(\omega t)$ is replaced V_a .
- **2nd step:** Replace circuit elements by their impedances. The resulting diagram is called the impedance model of the network..
- **3rd Step:** Determine the complex amplitudes of the voltages and currents in the circuit by any standard linear circuit analysis.
- **4th Step:** Obtain the time variables from the complex amplitudes. For example, the time variable corresponding to node variable V_o is given by $v_o(t) = |V_o| \cos(\omega t + \angle V_o)$. This step is usually not necessary.

Phasor Overview



- Phasor analysis is first developed by Charles Proteus Steinmetz (1865-1923) in 1893 while working for General Electric.
- Phasor is a technique which uses complex number to analyze circuits at sinusoidal steady state;
 - Definition of phasors;
 - Comparison between time domain and phasor domain;
 - Circuit Theories (KCL, KVL, ..) in the phasor domain.


Sinusoidal Excitation



- Sinusoidal Excitation:

$$v(t) = V \cos(\omega t + \phi)$$

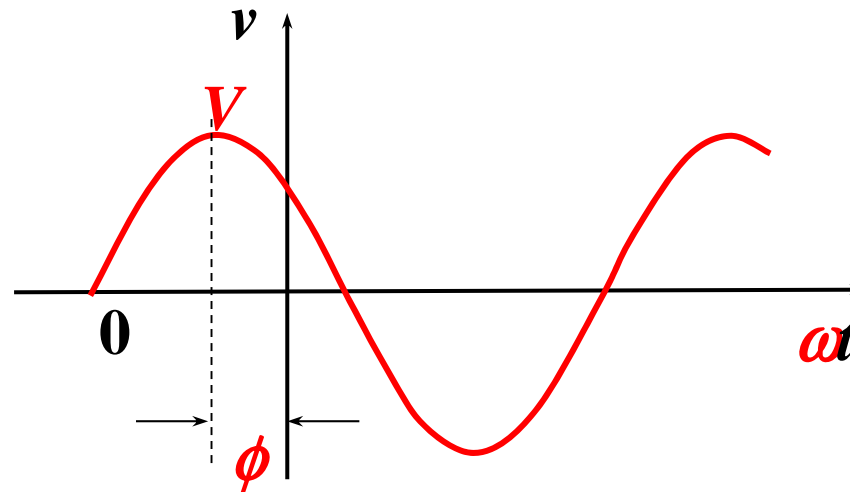- There are 3 parameters: Amplitude V , angular frequency ω , and phase angle ϕ




Lead and lag



- Sinusoidal Excitation:

For $v(t) = V \cos(\omega t + \phi_v)$ and $i(t) = I \cos(\omega t + \phi_i)$

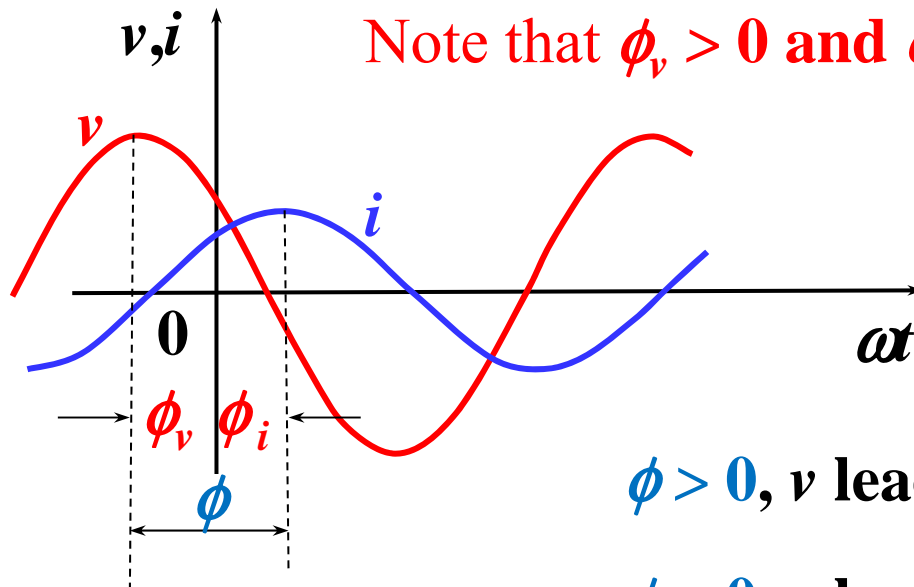- The phase difference $\phi = \omega t + \phi_v - \omega t - \phi_i = \phi_v - \phi_i$



Note that $\phi_v > 0$ and $\phi_i < 0$

$\phi > 0$, v leading i , or i lagging v

$\phi < 0$, v lagging i , or i leading v


Special Phase Relation





CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

Same Phase: $\phi = 0$

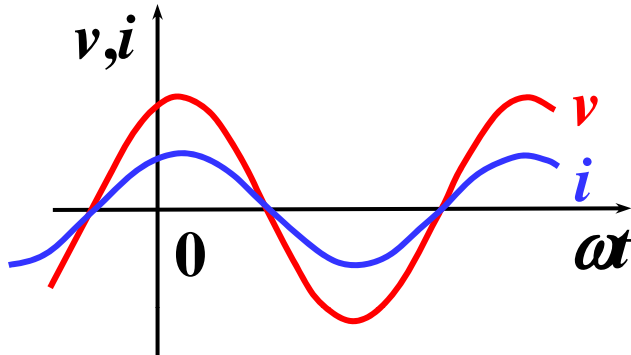

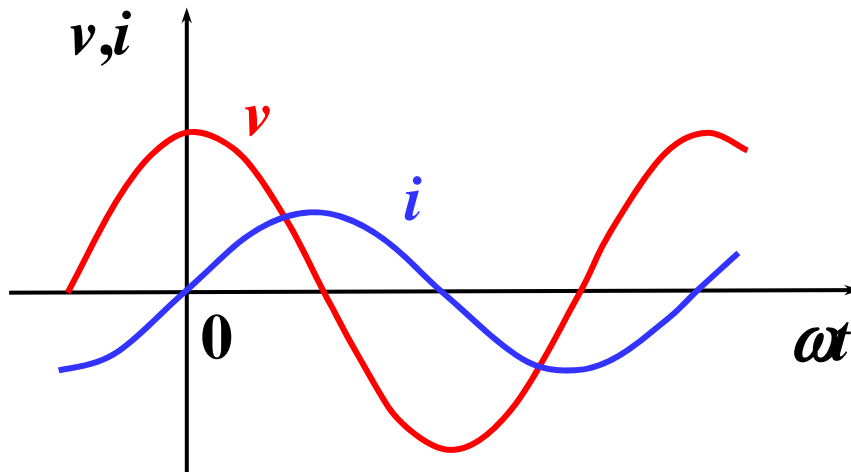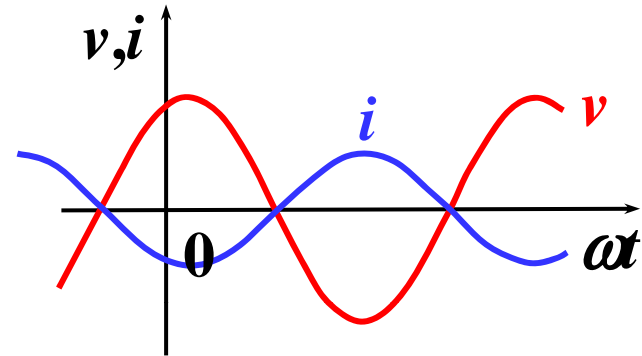Inverting: $\phi = \pm \pi$ ($\pm 180^\circ$)



$\phi = 90^\circ$

*v leading i by 90°
or i lagging v by 90°*

*Not v leading i by 270°
or I lagging v by 270°*

Convention : $|\phi| \leq \pi$ (180°)

Phasor



- Sinusoidal Excitation:

$$v(t) = V \cos(\omega t + \phi)$$

- For sinusoidal excitation with the same frequency ω , there are 2 parameters, amplitude V and phase angle ϕ , left.
- What can be used to represent amplitude V and phase angle ϕ at the same time?
- *Complex number*

Phasor



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- Assuming a source voltage is a sinusoid time-varying function
Sinusoidal Excitation (Time Domain) is a time function :

$$v(t) = V \cos(\omega t + \phi)$$

- We can write

$$v(t) = V_m \cos(\omega t + \phi) = V_m \operatorname{Re} \left[e^{j(\omega t + \phi)} \right] = \operatorname{Re} \left[V_m e^{j\phi} e^{j\omega t} \right] = \operatorname{Re} \left[\mathbf{V} e^{j\omega t} \right]$$

- Define Phasor as

$$\mathbf{V} = V_m e^{j\phi} = V_m \angle \phi$$

- Phasor (Frequency domain) is a complex number:


$$\mathbf{V} = V_m e^{j\phi} \text{ or } V_m \angle \phi = V_m \cos \phi + j V_m \sin \phi$$

$$v(t) = V_m \cos(\omega t + \phi) \leftrightarrow \mathbf{V} = V_m e^{j\phi} \text{ or } V_m \angle \phi$$

Time Domain

Frequency domain

Complex Numbers

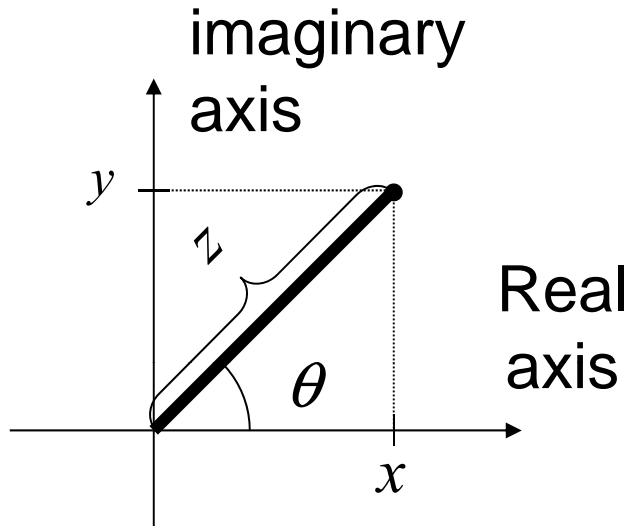

- x is the real part
- y is the imaginary part
- z is the magnitude
- θ is the phase
- Rectangular Coordinates: $\mathbf{Z} = x + jy$
- Polar Coordinates: $\mathbf{Z} = z \angle \theta$

$$x = z \cos \theta \qquad z = \sqrt{x^2 + y^2} \qquad \mathbf{Z} = z(\cos \theta + j \sin \theta)$$
$$y = z \sin \theta \qquad \theta = \tan^{-1} \left(\frac{y}{x} \right) \qquad \mathbf{Z} = z e^{j\theta} = z \angle \theta$$

- Exponential Form: $\mathbf{V} = z e^{j\theta}$
- $$1 = 1e^{j0^\circ} = 1 \angle 0^\circ$$
- $$j = 1e^{j90^\circ} = 1 \angle 90^\circ$$

Addition




- Addition is most easily performed in rectangular coordinates:

$$\mathbf{A} = a + jb$$

$$\mathbf{B} = c + jd$$
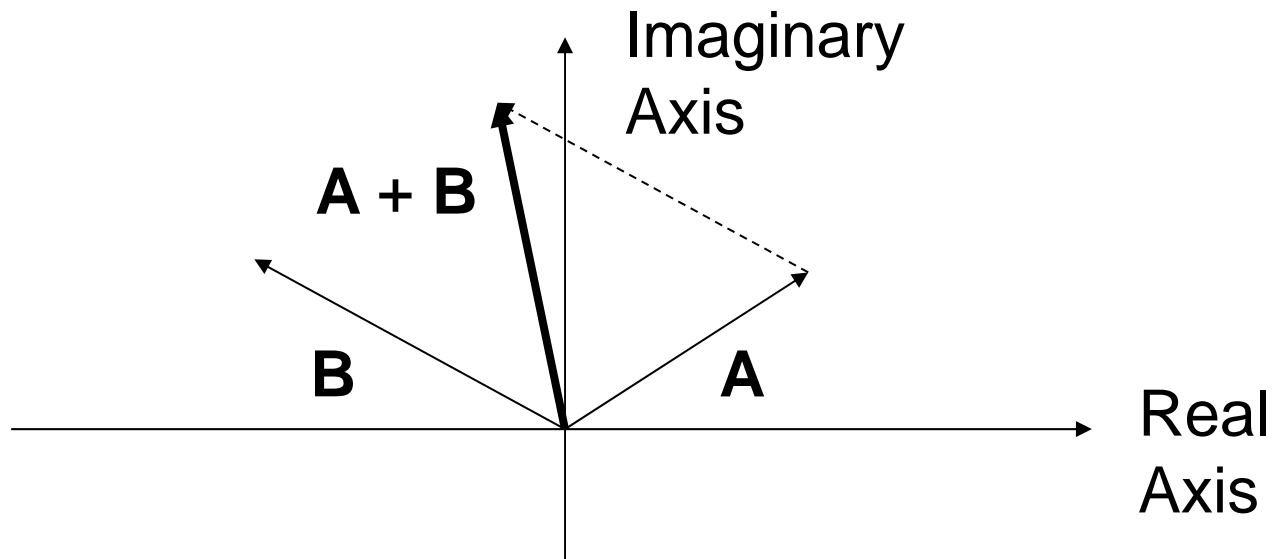
$$\mathbf{A} + \mathbf{B} = (a + b) + j(c + d)$$



Subtraction



CAPT


Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- Subtraction is most easily performed in rectangular coordinates:

$$\mathbf{A} = a + jb$$

$$\mathbf{B} = c + jd$$
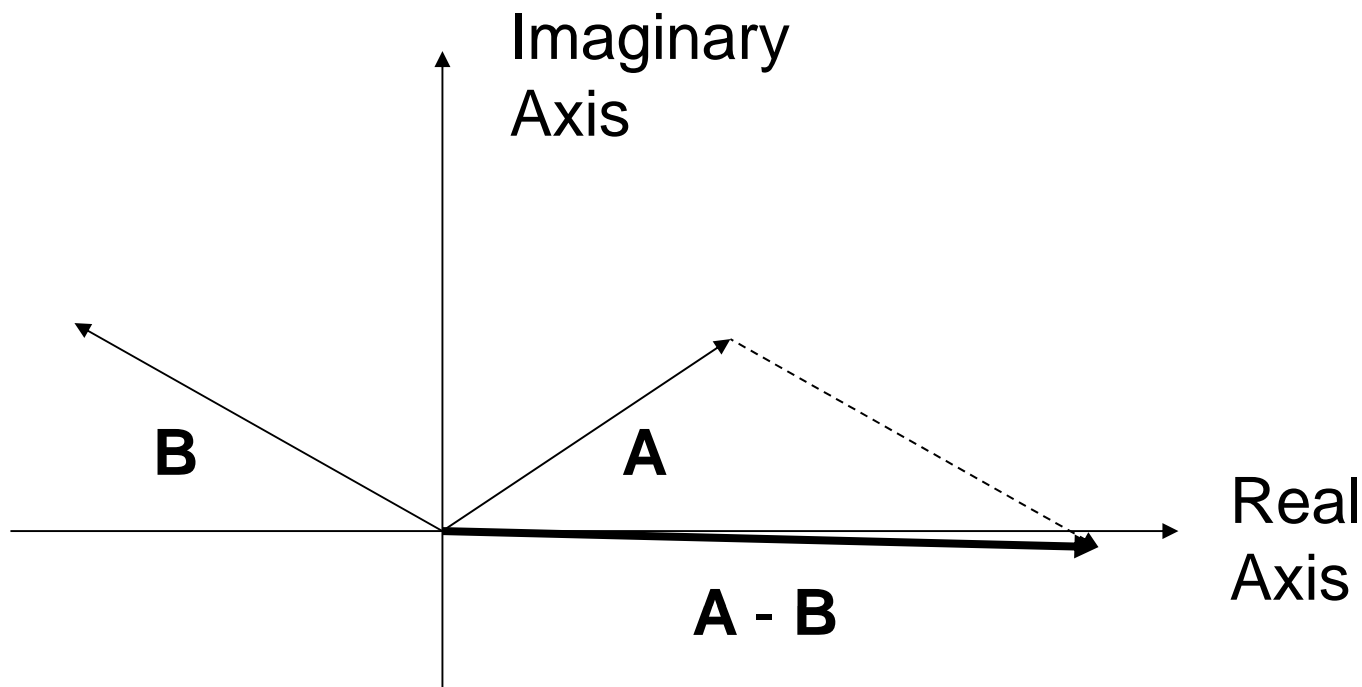
$$\mathbf{A} - \mathbf{B} = (a - b) + j(c - d)$$



Multiplication




- Multiplication is most easily performed in polar coordinates :

$$\mathbf{A} = A_m e^{j\theta} = A_m \angle \theta$$

$$\mathbf{B} = B_m e^{j\phi} = B_m \angle \phi$$
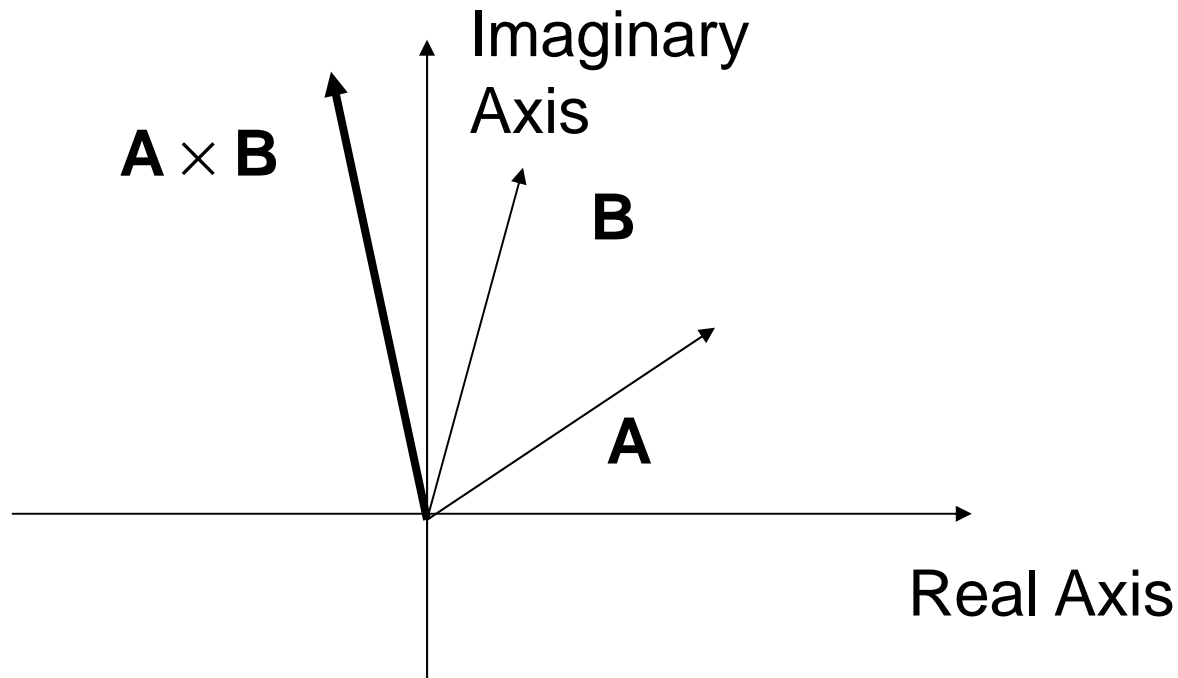
$$\mathbf{A} \times \mathbf{B} = (A_m \times B_m) e^{j(\theta+\phi)} = (A_m \times B_m) \angle (\theta + \phi)$$



Division




- Division is most easily performed in polar coordinates :

$$\mathbf{A} = A_m e^{j\theta} = A_m \angle \theta$$

$$\mathbf{B} = B_m e^{j\phi} = B_m \angle \phi$$
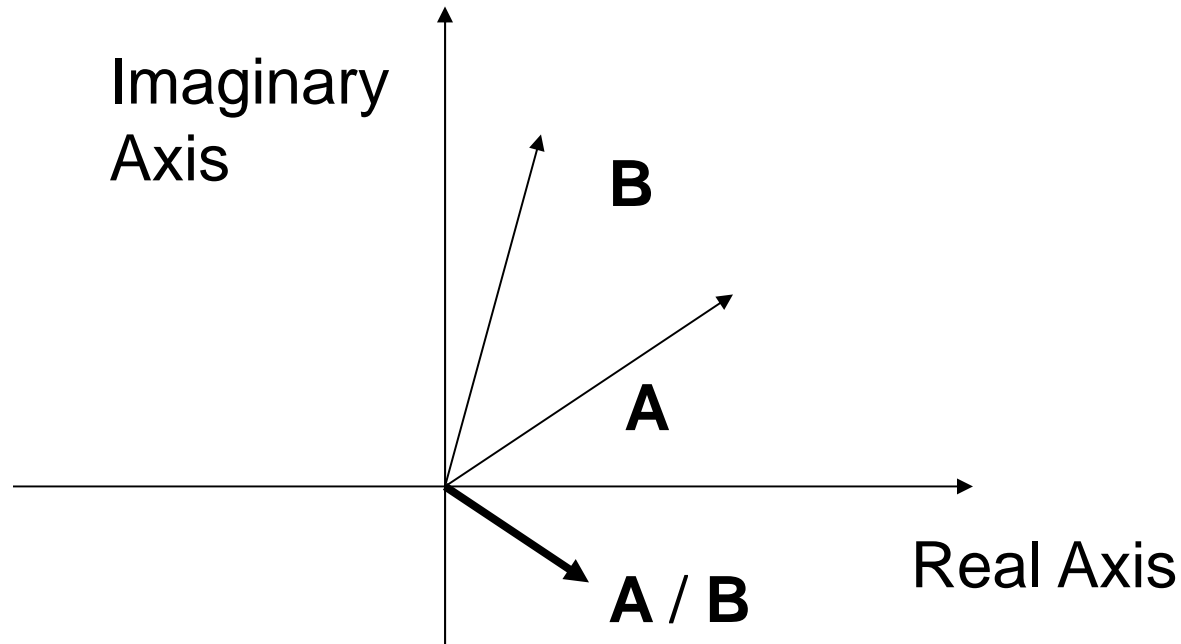
$$\frac{\mathbf{A}}{\mathbf{B}} = \frac{A_m}{B_m} e^{j(\theta-\phi)} = \frac{A_m}{B_m} \angle (\theta - \phi)$$







$$\begin{aligned}
 v_1(t) &= 6\cos(314t + 30^\circ) \text{ V} \\
 v_2(t) &= 4\cos(314t + 60^\circ) \text{ V}
 \end{aligned}
 \Rightarrow
 \begin{cases}
 \mathbf{V}_1 = 6\angle 30^\circ \text{ V} \\
 \mathbf{V}_2 = 4\angle 60^\circ \text{ V}
 \end{cases}$$

$$\begin{aligned}
 \mathbf{V} &= \mathbf{V}_1 + \mathbf{V}_2 = 6\angle 30^\circ + 4\angle 60^\circ = 5.196 + j3 + 2 + j3.464 \\
 &= 7.196 + j6.464 = 9.67\angle 41.9^\circ \text{ V}
 \end{aligned}$$

$$\therefore v(t) = v_1(t) + v_2(t) = 9.67\cos(314t + 41.9^\circ) \text{ V}$$

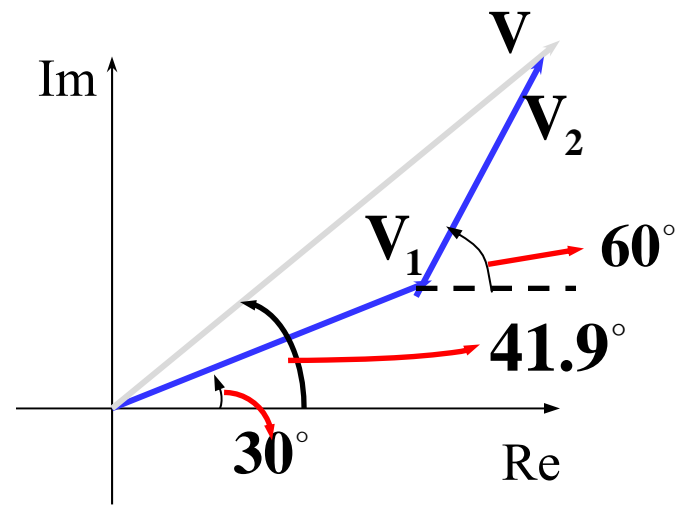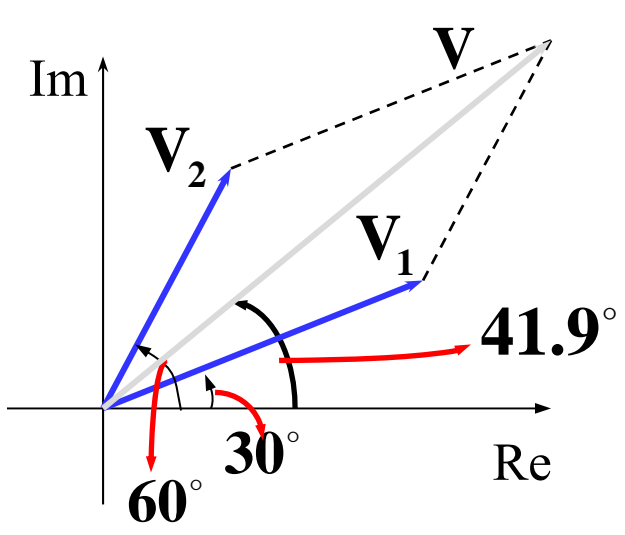The addition of two sinusoidal excitations can be found with the help of the phasor diagram ◦



Algebra With Complex Numbers



- To compute phasor voltages and currents, we need to be able to perform computation with complex numbers.

$$(1) \quad \mathbf{A} + \mathbf{B} = \mathbf{B} + \mathbf{A}$$

$$(3) \quad \mathbf{A} \times \mathbf{B} = \mathbf{B} \times \mathbf{A}$$

$$(5) \quad \mathbf{A} \times (\mathbf{B} + \mathbf{C}) = \mathbf{A} \times \mathbf{B} + \mathbf{A} \times \mathbf{C}$$

$$(7) \quad \mathbf{A}^{\mathbf{B}} \times \mathbf{A}^{\mathbf{C}} = \mathbf{A}^{(\mathbf{B}+\mathbf{C})}$$

$$(9) \quad \mathbf{A} + \mathbf{B} = \mathbf{C}$$

$$(11) \quad \mathbf{A} \times \mathbf{B} = \mathbf{C}$$

$$(13) \quad \mathbf{B}^{\mathbf{A}} = \mathbf{C}$$

$$(15) \quad \mathbf{A}^{\mathbf{B}} = \mathbf{C}$$

$$(2) \quad \mathbf{A} + (\mathbf{B} + \mathbf{C}) = (\mathbf{A} + \mathbf{B}) + \mathbf{C}$$

$$(4) \quad \mathbf{A} \times (\mathbf{B} \times \mathbf{C}) = (\mathbf{A} \times \mathbf{B}) \times \mathbf{C}$$

$$(6) \quad (\mathbf{A} \times \mathbf{B})^{\mathbf{C}} = \mathbf{A}^{\mathbf{C}} \times \mathbf{B}^{\mathbf{C}}$$

$$(8) \quad (\mathbf{A}^{\mathbf{B}})^{\mathbf{C}} = \mathbf{A}^{\mathbf{B} \times \mathbf{C}}$$

$$(10) \quad \mathbf{B} = \mathbf{C} - \mathbf{A}$$

$$(12) \quad \mathbf{B} = \frac{\mathbf{C}}{\mathbf{A}}$$

$$(14) \quad \mathbf{B} = \sqrt[\mathbf{A}]{\mathbf{C}}$$

$$(16) \quad \mathbf{B} = \log_{\mathbf{A}} \mathbf{C}$$

Kirchhoff's Laws for Phasors



- Suitable for AC steady state.

$$\text{KVL: } \underline{v_1 + v_2 + \dots + v_n = 0}$$


$$\rightarrow V_{m1} \cos(\omega t + \phi_1) + V_{m2} \cos(\omega t + \phi_2) + \dots + V_{mn} \cos(\omega t + \phi_n) = 0$$

$$\rightarrow \text{Re} \left[V_{m1} e^{j\phi_1} e^{j\omega t} \right] + \text{Re} \left[V_{m2} e^{j\phi_2} e^{j\omega t} \right] + \dots + \text{Re} \left[V_{mn} e^{j\phi_n} e^{j\omega t} \right] = 0$$


$$\rightarrow \text{Re} \left[(\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n) e^{j\omega t} \right] = 0$$

$$\rightarrow \mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0$$
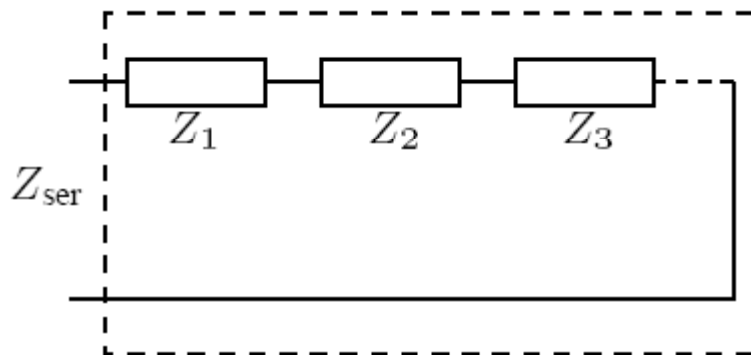
$$\text{KCL: } \underline{i_1 + i_2 + \dots + i_n = 0} \dots \rightarrow \underline{\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0}$$


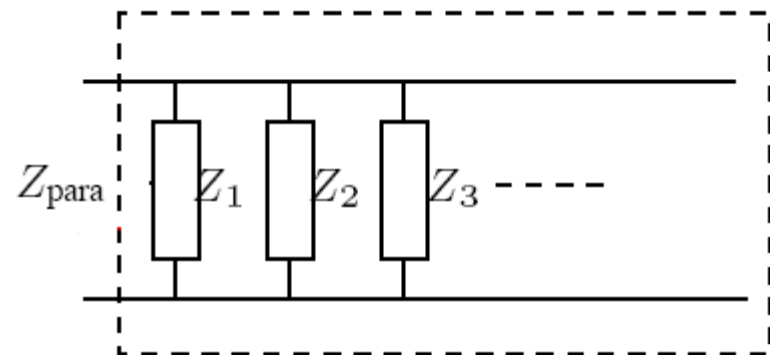
$$Z_{\text{ser}} = Z_1 + Z_2 + Z_3 + \dots$$



$$1/Z_{\text{para}} = 1/Z_1 + 1/Z_2 + \dots$$


Transfer Function




- Map system input to output $\mathbf{V}_o = H(j\omega)\mathbf{V}_i$
- Covert an input $v_i(t) = V_i \cos(\omega t + \phi)$ into phasor \mathbf{V}_i . Plug into above Eq.
- Get an output $\mathbf{V}_o = H(j\omega)\mathbf{V}_i$. Covert back to time domain form.

$$v_o(t) = |H(j\omega)|V_i \cos[\omega t + \phi + \angle H(j\omega)]$$


- Output is scaled by $|H(j\omega)|$

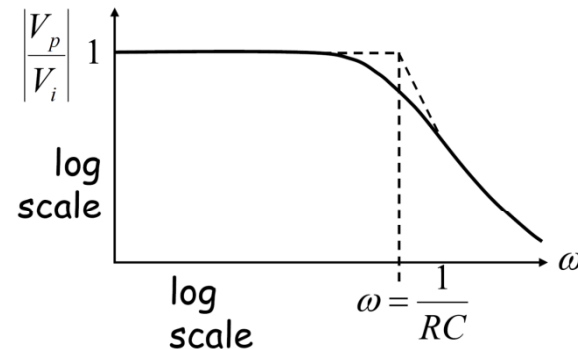

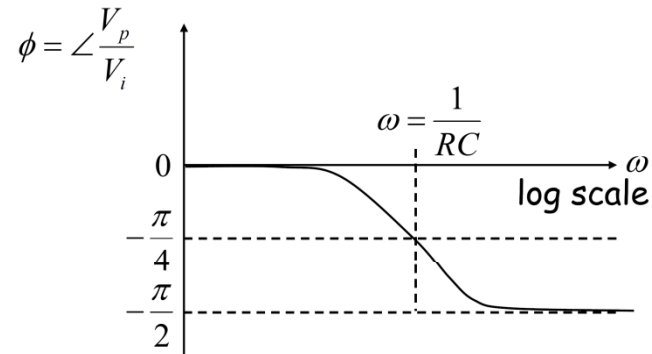
- Shift in time by $\frac{\angle H(j\omega)}{\omega}$




The Effort of Various Approaches

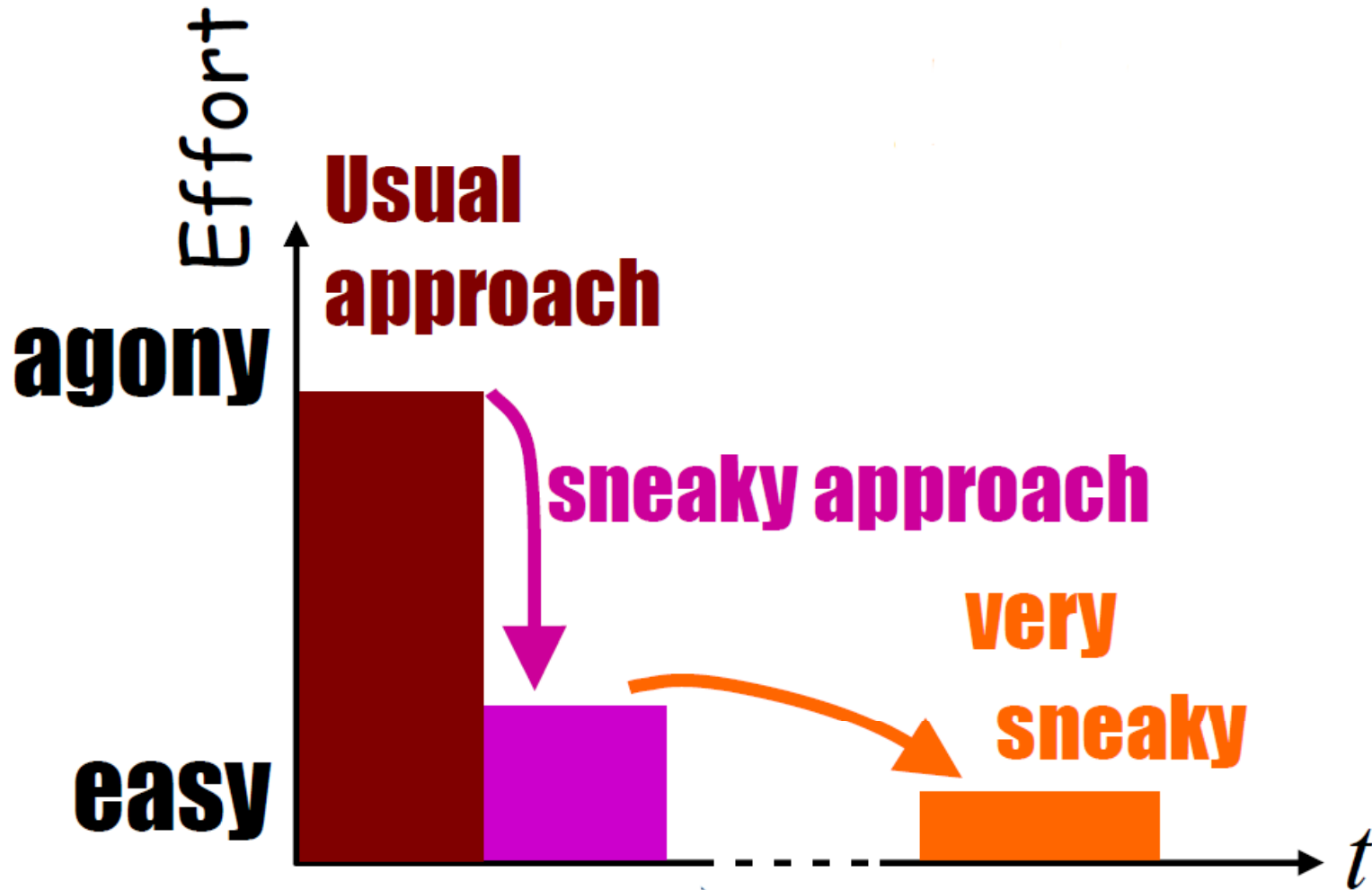


The Big Picture

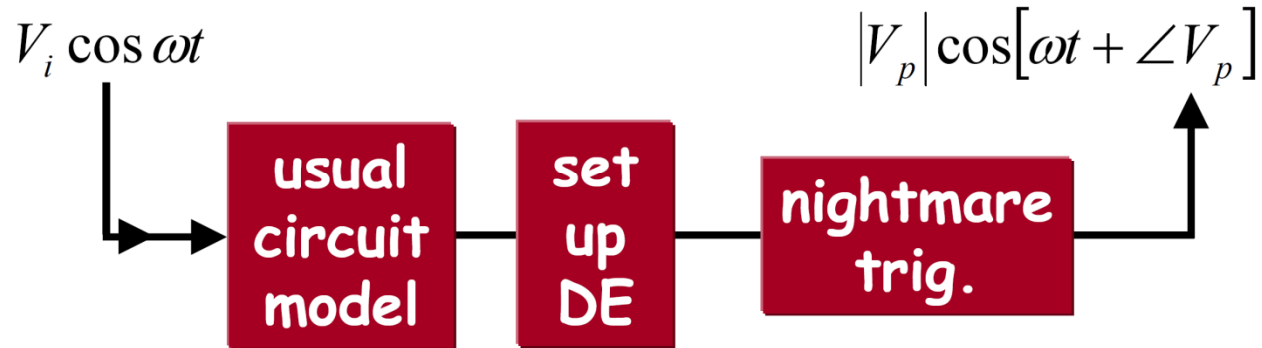


The Big Picture

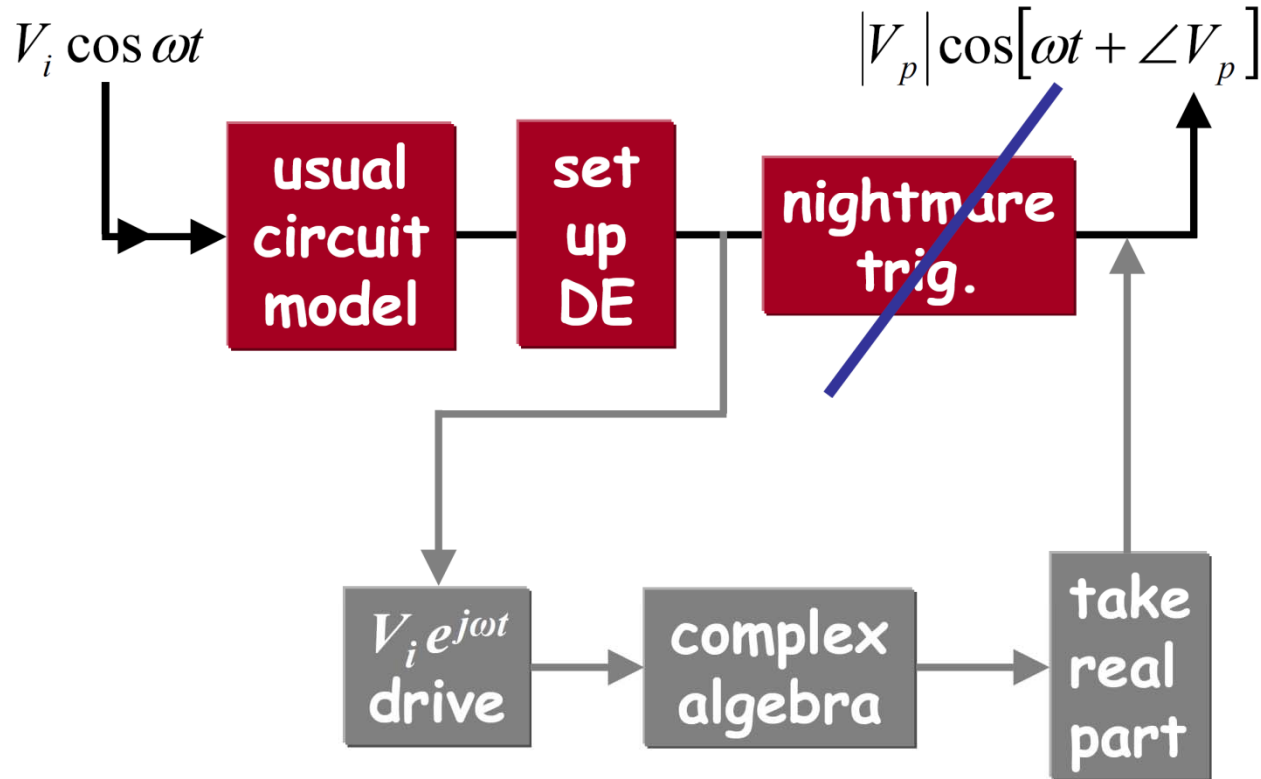

The Big Picture

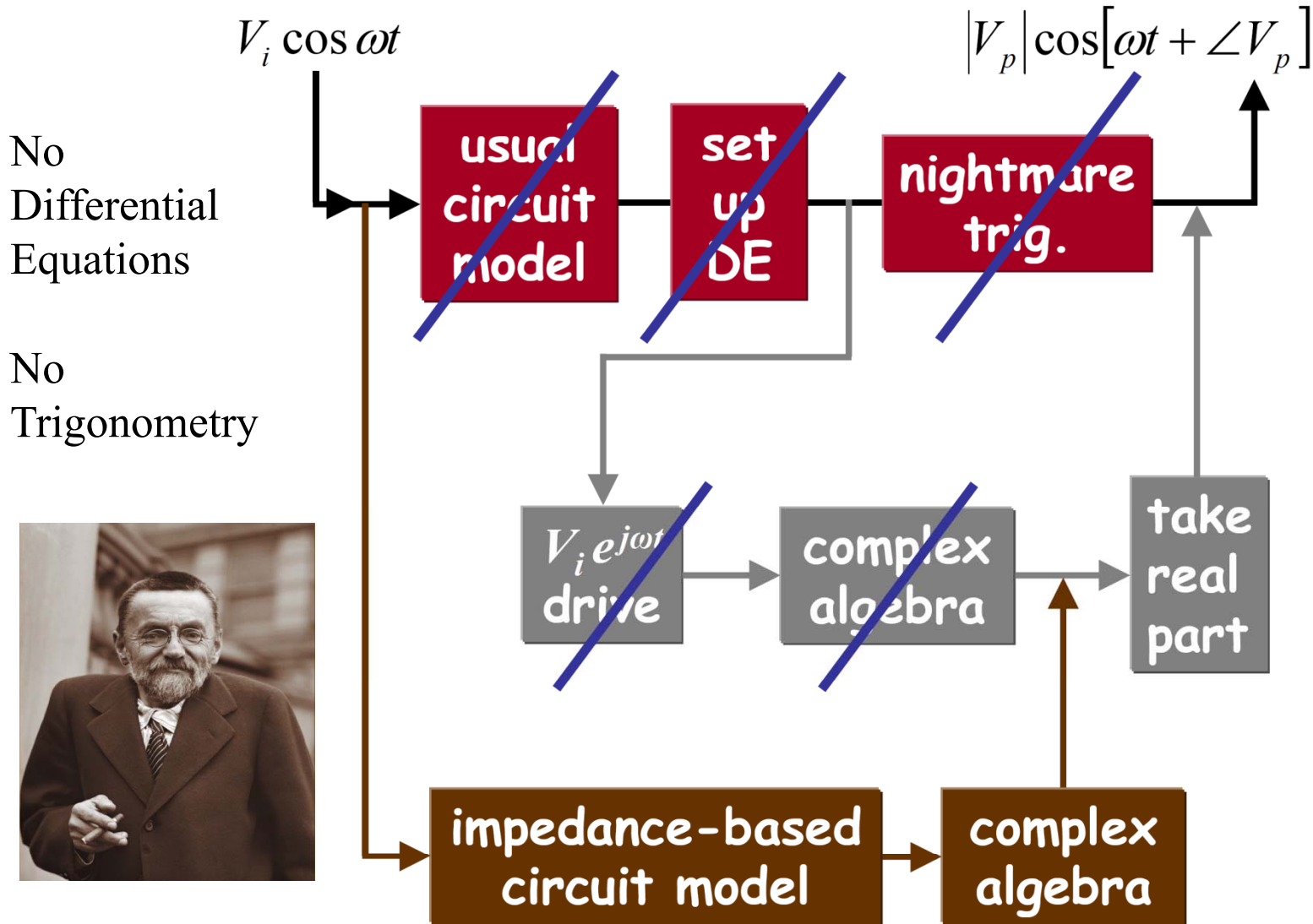

The Big Picture

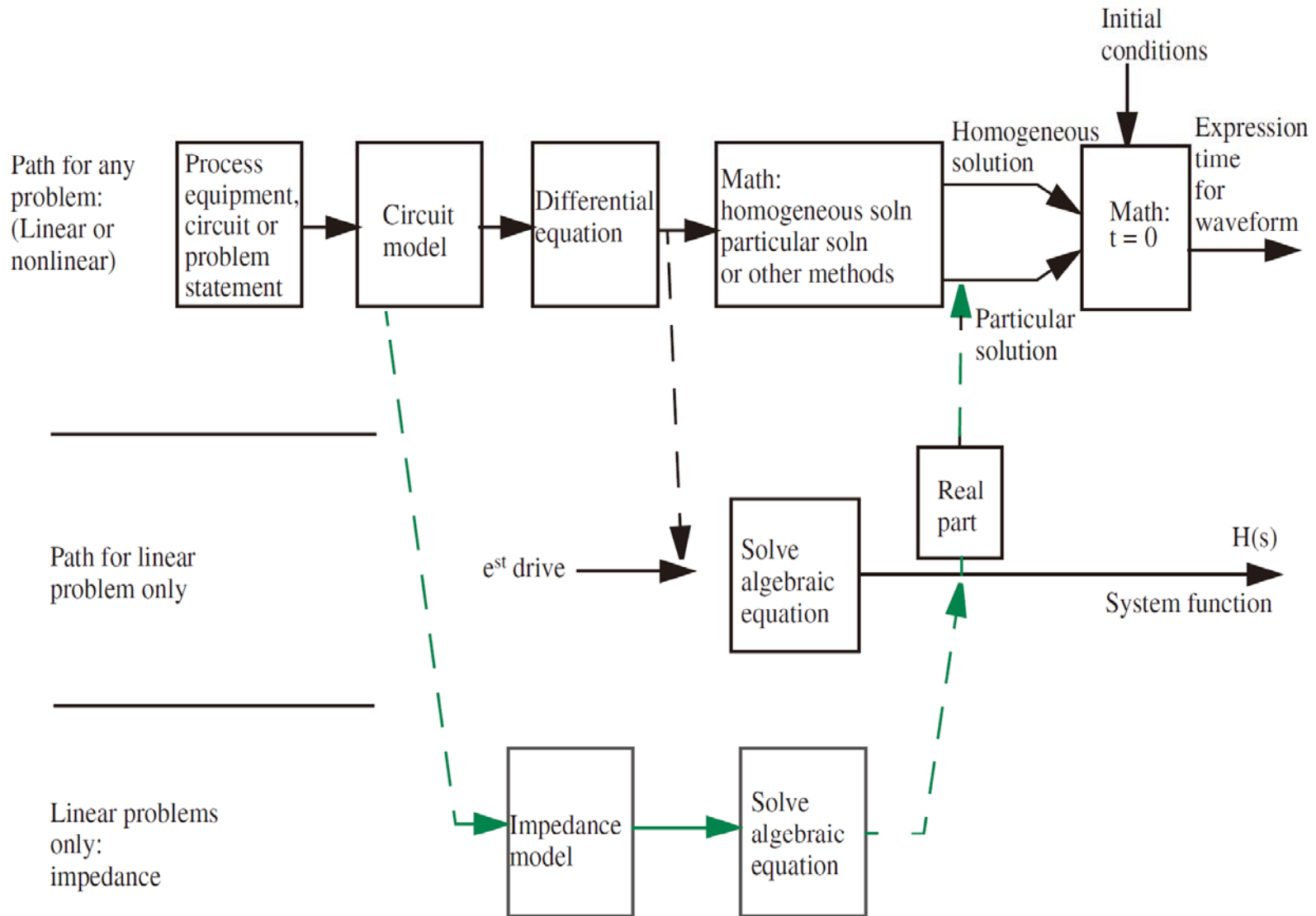

Summary



- Sinusoidal steady state is an important characterization of a linear system. It comprises a frequency response, which includes a gain plot and a phase plot as a function of frequency.
- By assuming complex exponential drives instead of sinusoidal drives for linear time-invariant circuits, the differential equations describing circuit behavior reduce to algebraic equations.
- The impedance method allows us to determine with ease the steady-state response of any linear RLC network for a sinusoidal input.
- The impedance method allows us to determine with ease the steady-state response of any linear RLC network for a sinusoidal input.
- The frequency response characterizes the behavior of a network as a function of frequency. A frequency response plot is a convenient way of summarizing how a network behaves as function of frequency. A frequency response plot has two graphics: the gain plot and the phase plot