

Sinusoidal Steady State Filters and Resonance

Chenhsin Lien and Po-Tai Cheng

CENTER FOR ADVANCED POWER TECHNOLOGIES

Dept. of Electrical Engineering

National Tsing Hua University

Hsinchu, TAIWAN




CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN


Back to RC Network



• Circuit:

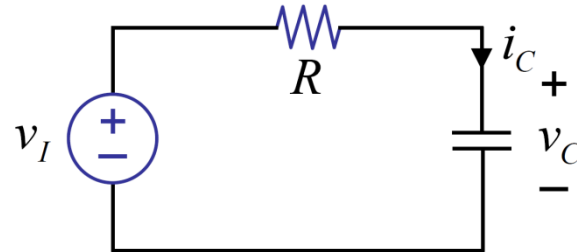

• Impedance model:

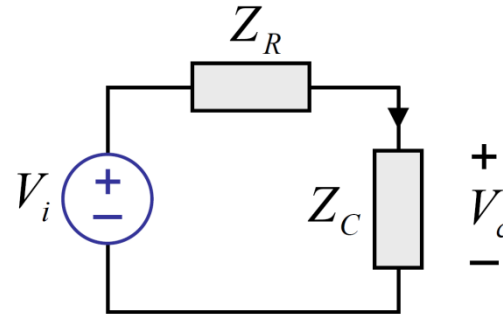



• To find V_P

$$\mathbf{V}_c = \mathbf{V}_i \frac{Z_C}{Z_C + R} = \mathbf{V}_i \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \Rightarrow \mathbf{V}_c = \frac{1}{1 + j\omega RC} \mathbf{V}_i$$

Transfer Function



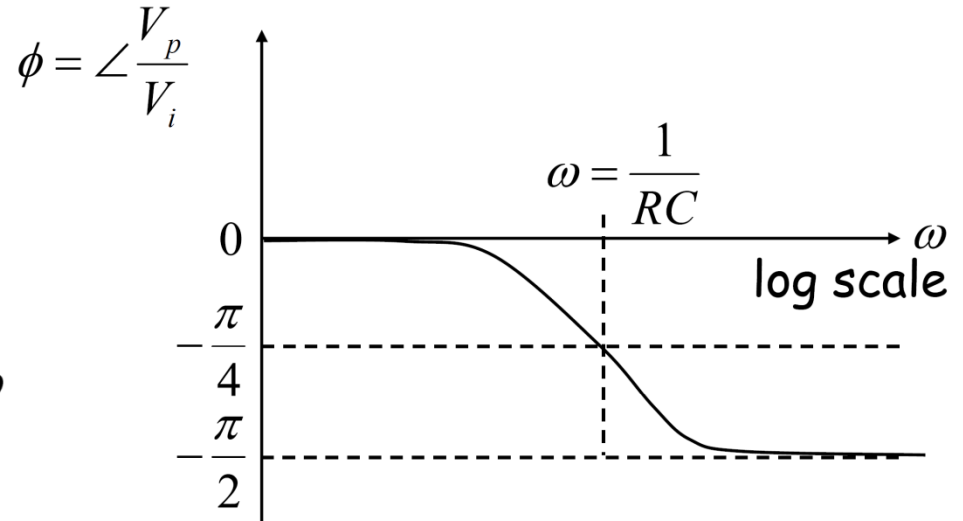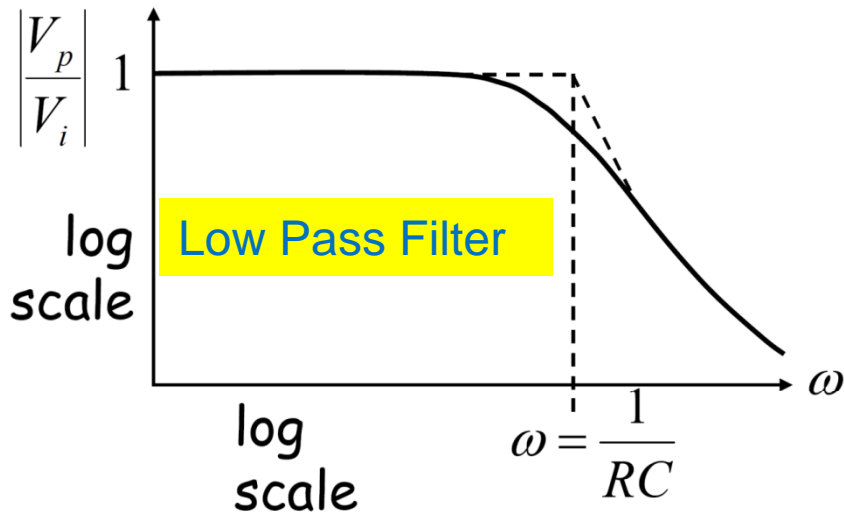- **Transfer function** $H(j\omega) = \frac{V_c}{V_i} = \frac{1}{1 + j\omega RC}$
- **Magnitude and Phase plots, A low pass filter.**




Magnitude: $\left| \frac{V_P}{V_i} \right| = \frac{V_P}{V_i} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

Phase ϕ : $\phi = \angle \frac{V_P}{V_i} = -\tan^{-1} \omega RC$

Bode Plot



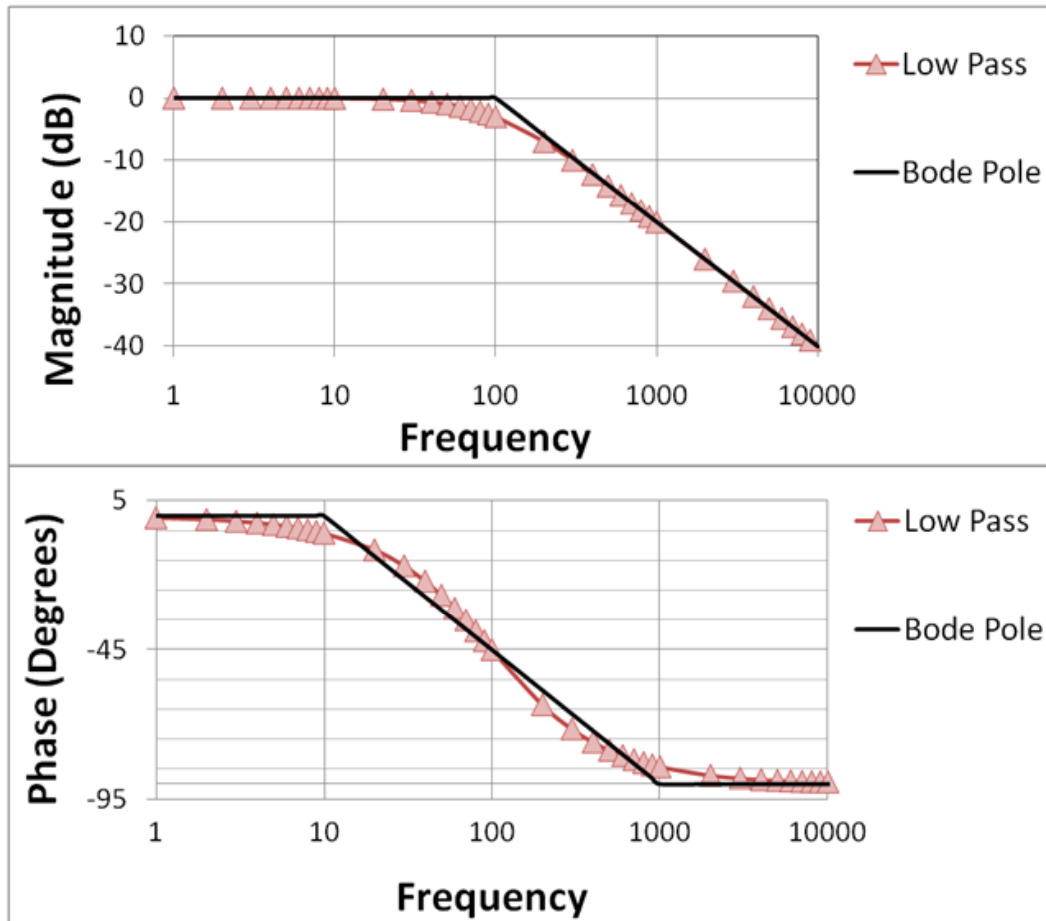
- **Transfer function** $H(j\omega) = \frac{V_c}{V_i} = \frac{1}{1 + j\omega RC}$
- **Bode Plot** for a transfer function assuming $RC = 2\pi \times 100$ rad/sec.



Quick Review of Impedances




● Example1:

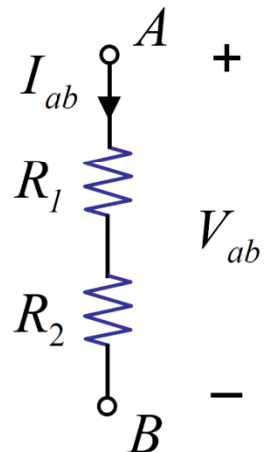

$$R_{ab} = \frac{\mathbf{V}_{ab}}{\mathbf{I}_{ab}} = R_1 + R_2$$

● Example2 :

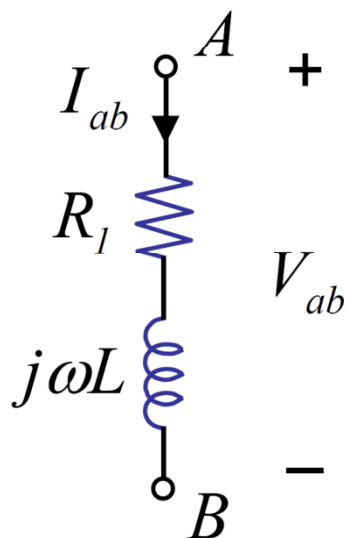


$$Z_{ab} = \frac{\mathbf{V}_{ab}}{\mathbf{I}_{ab}} = R_1 + j\omega L_i$$

Quick Review of Impedances



• Example3:

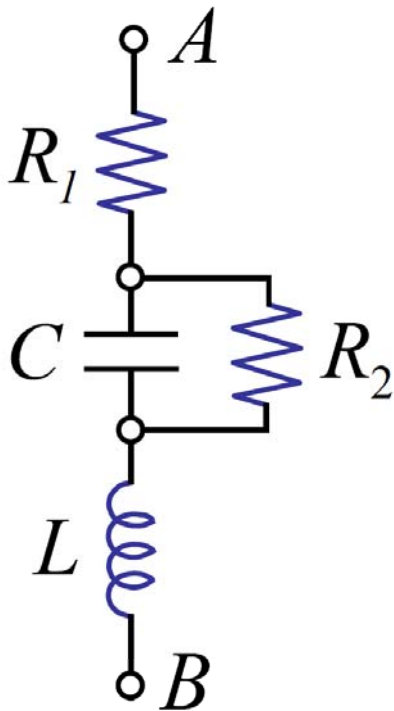


$$\begin{aligned} Z_{ab} &= \frac{V_{ab}}{I_{ab}} = R_1 + Z_C \parallel R_2 + Z_L \\ &= R_1 + \frac{Z_C R_2}{Z_C + R_2} + Z_L \\ &= R_1 + \frac{R_2}{1 + j\omega C R_2} + Z_L \end{aligned}$$

RCL Impedances










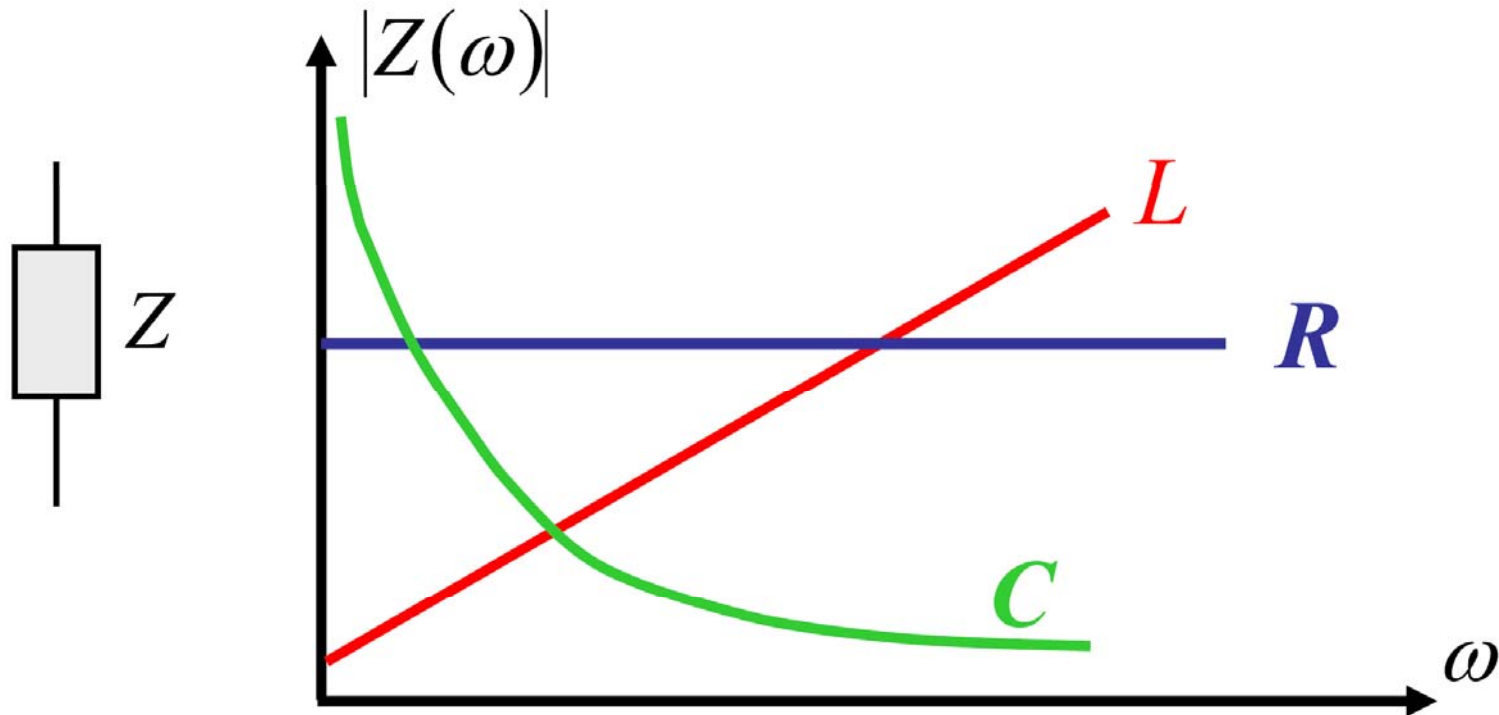
- RLC impedances as a function of frequency:




Filters built by Combining Impedances



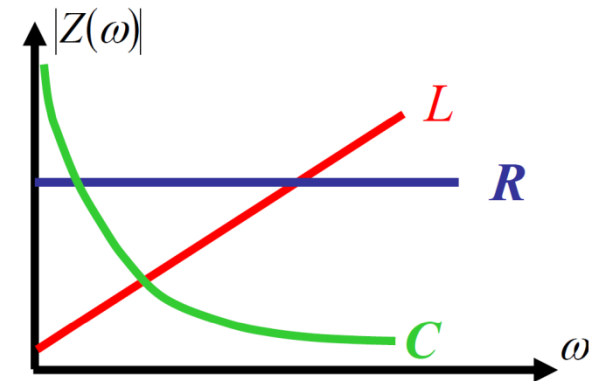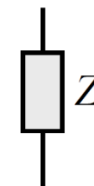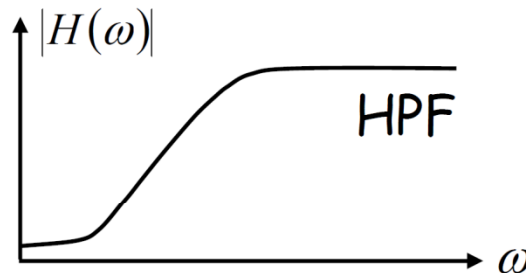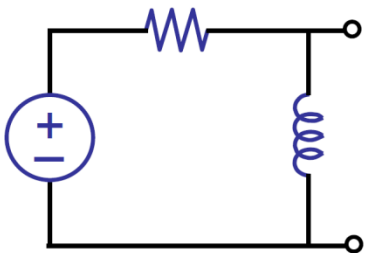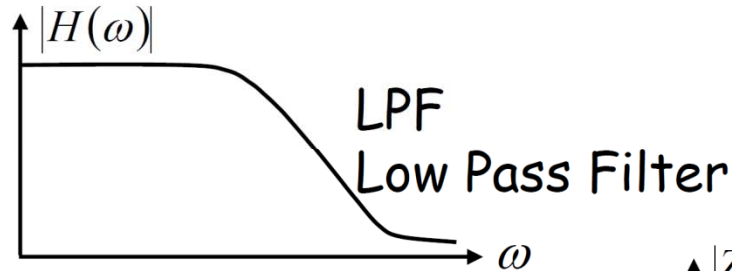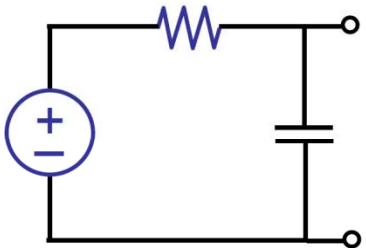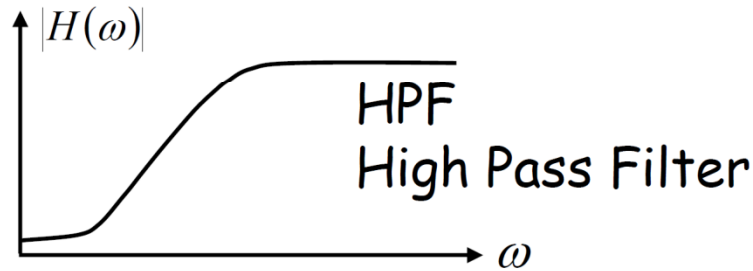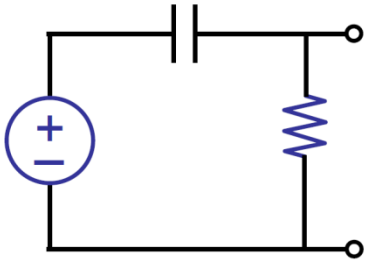• Filters can be built by Combining Impedances :



Series RLC

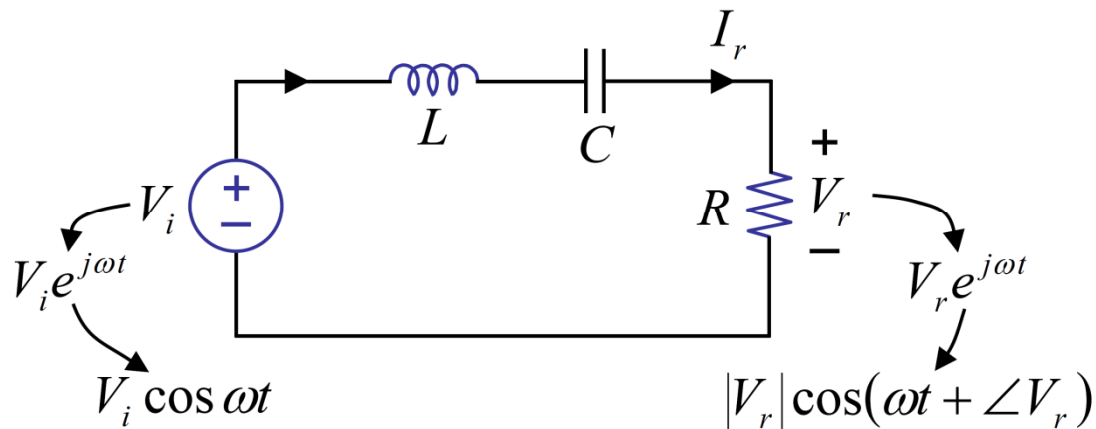

• To find V_r

$$\mathbf{V}_r = \mathbf{V}_i \frac{Z_R}{Z_L + Z_C + Z_R}$$

$$\mathbf{V}_r = \mathbf{V}_i \frac{R}{j\omega L + \frac{1}{j\omega C} + R}$$


$$\mathbf{V}_r = \mathbf{V}_i \frac{j\omega CR}{-\omega^2 LC + 1 + j\omega CR}$$

Transfer Function



- Transfer function
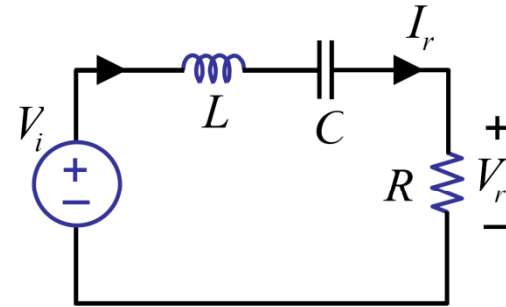
$$\frac{V_r}{V_i} = \frac{j\omega CR}{-\omega^2 LC + 1 + j\omega CR}$$



- Let's study this transfer function

$$\frac{V_r}{V_i} = \frac{j\omega CR}{(1 - \omega^2 LC) + j\omega CR} = \frac{j\omega CR}{(1 - \omega^2 LC) + j\omega CR} \cdot \frac{(1 - \omega^2 LC) - j\omega CR}{(1 - \omega^2 LC) - j\omega CR}$$

$$\left| \frac{V_r}{V_i} \right| = \frac{V_r}{V_i} = \frac{\omega CR}{\sqrt{(1 - \omega^2 LC)^2 + (\omega CR)^2}}$$

Low ω : $\frac{V_r}{V_i} \approx \omega CR$

High ω : $\frac{V_r}{V_i} \approx \frac{R}{\omega L}$

$\omega\sqrt{LC} = 1$: $\frac{V_r}{V_i} = 1$

Graphically




● Transfer function

$$\left| \frac{\mathbf{V}_r}{\mathbf{V}_i} \right| = \frac{V_r}{V_i} = \frac{\omega CR}{\sqrt{(1 - \omega^2 LC)^2 + (\omega CR)^2}}$$

Low ω : $\frac{V_r}{V_i} \approx \omega CR$

High ω : $\frac{V_r}{V_i} \approx \frac{R}{\omega L}$


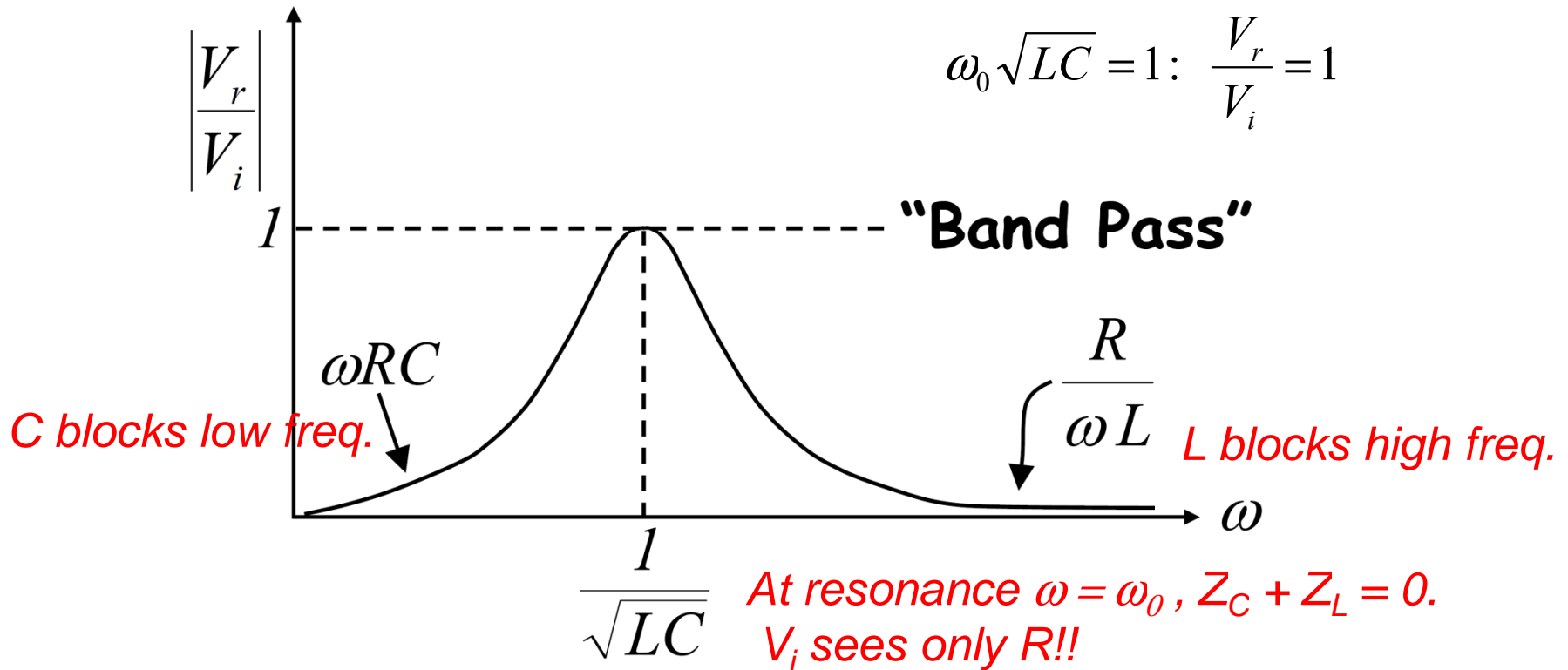
$\omega_0 \sqrt{LC} = 1$: $\frac{V_r}{V_i} = 1$




What about?




- What about taking V_{lc} as output?

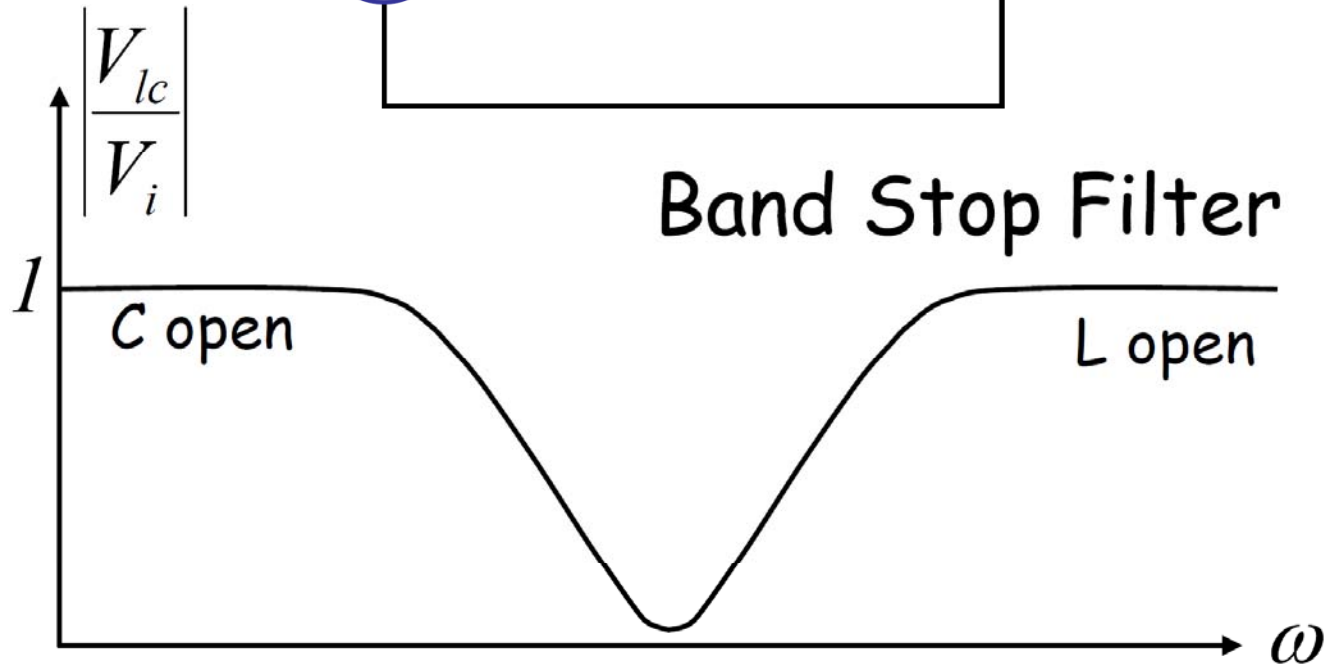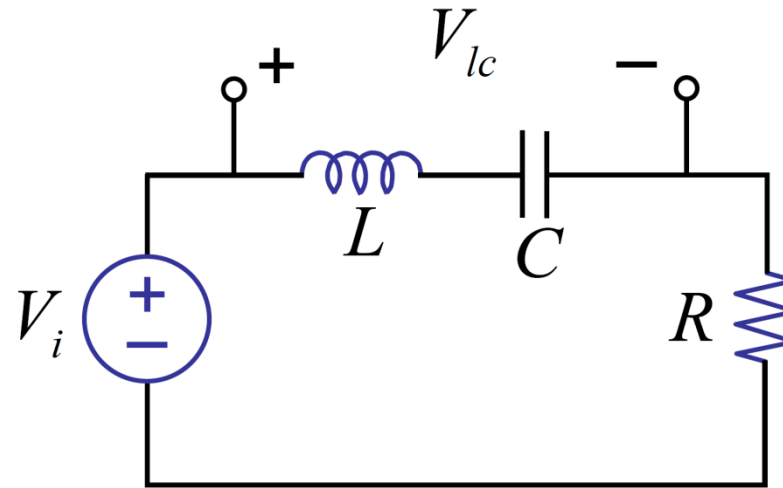


Another example:

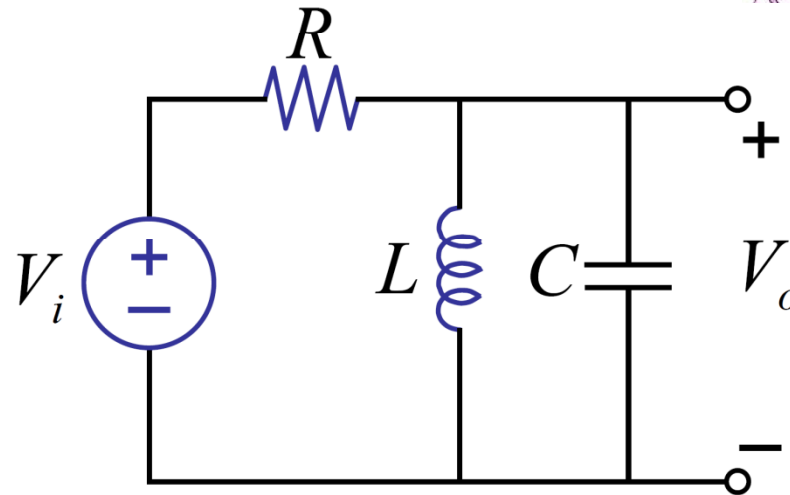

BPF

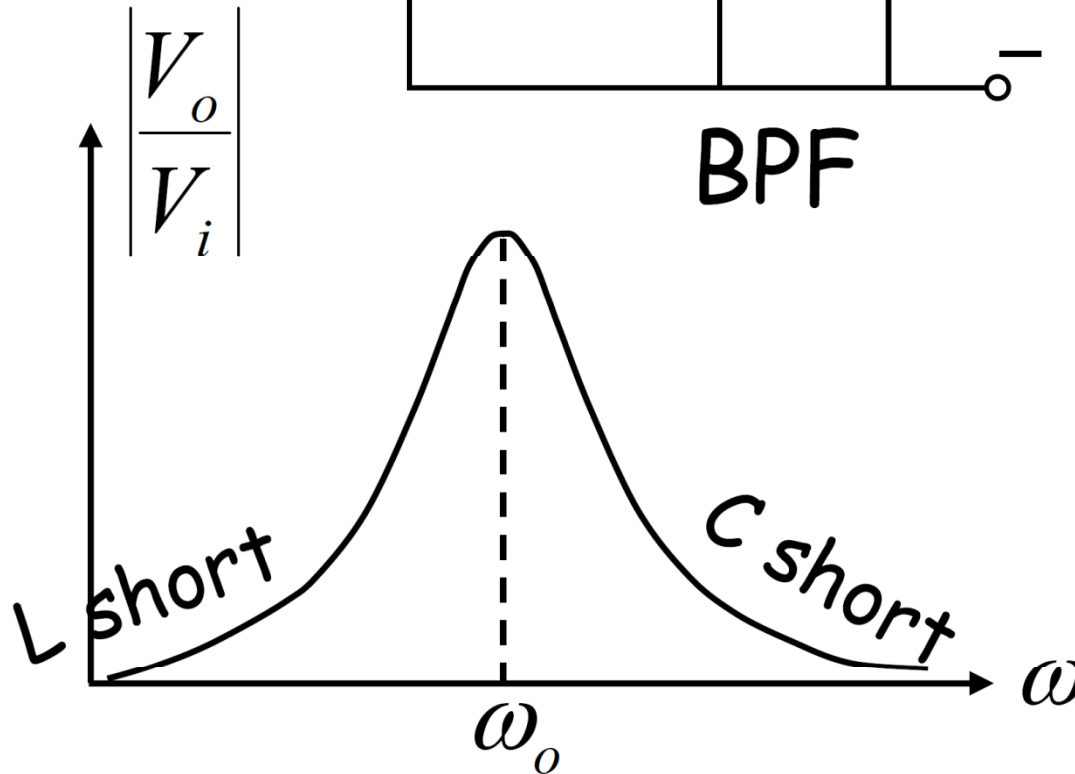



AM Radio Receiver

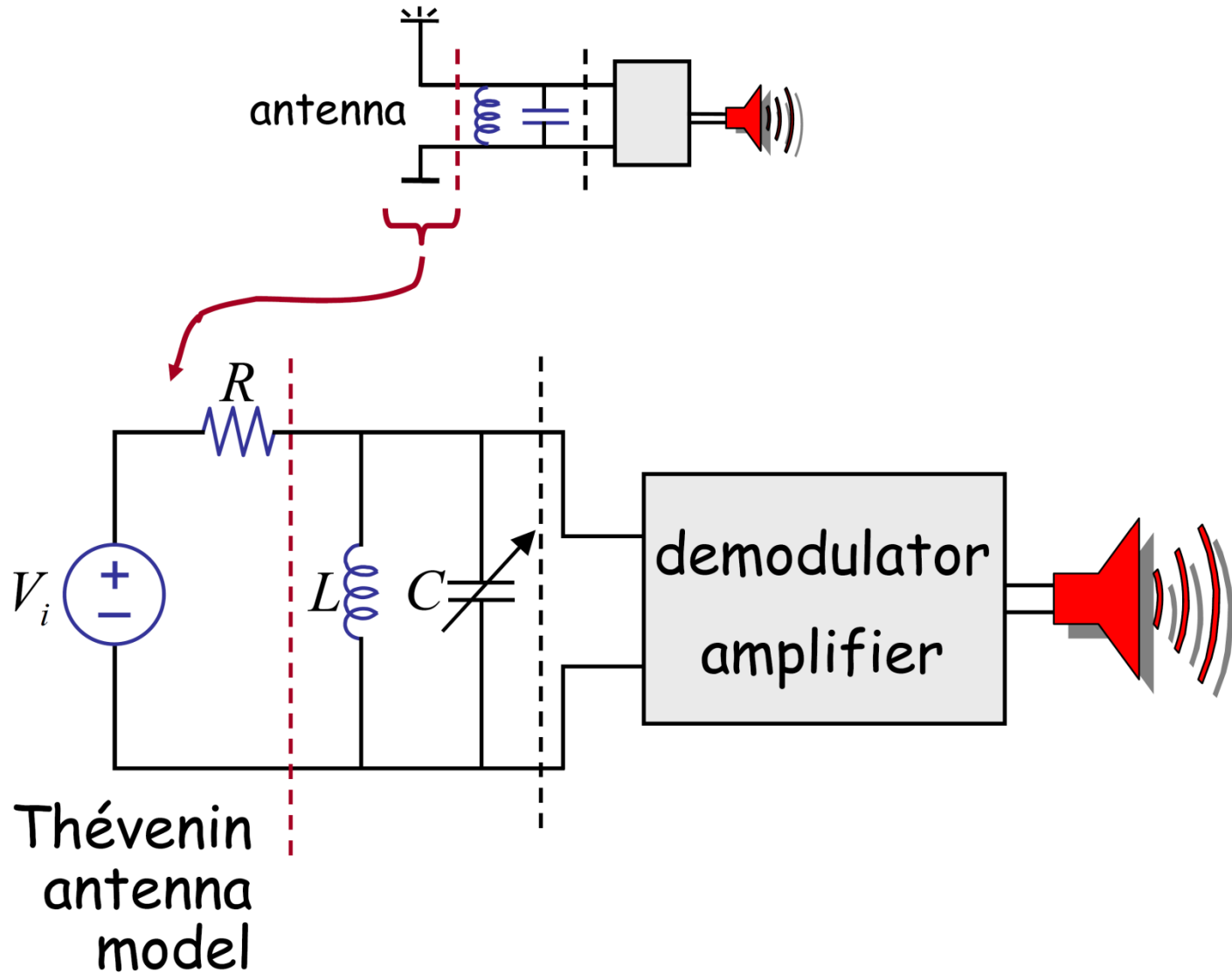


AM Radio Receiver



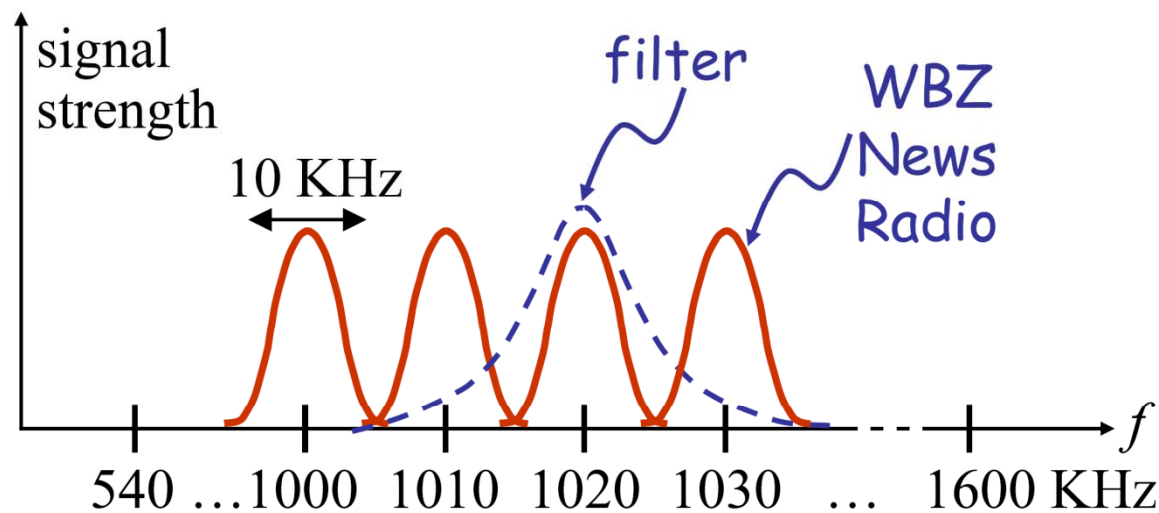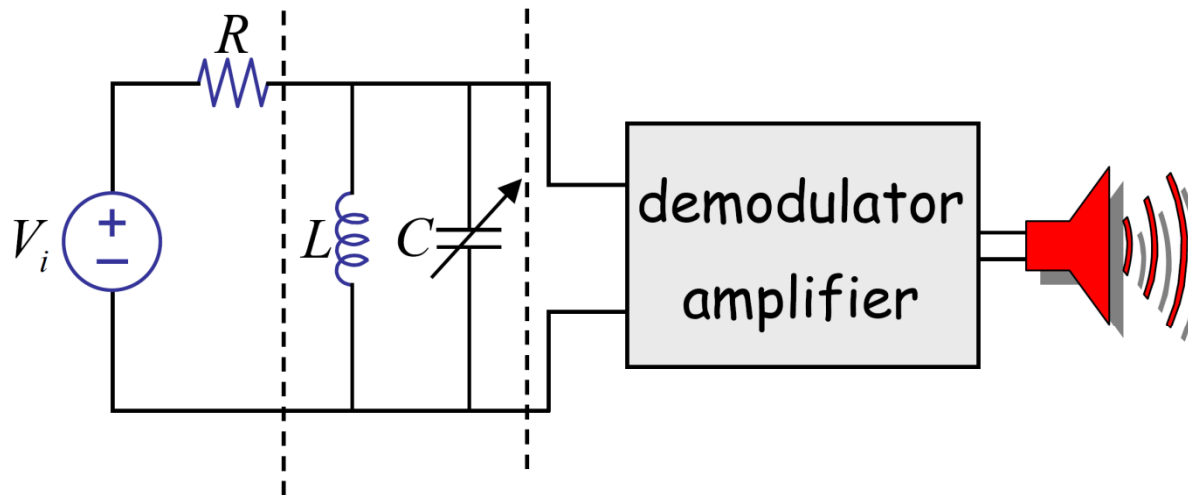- Receiver “Selectivity” is important — relates to a parameter “Q” of the filter.



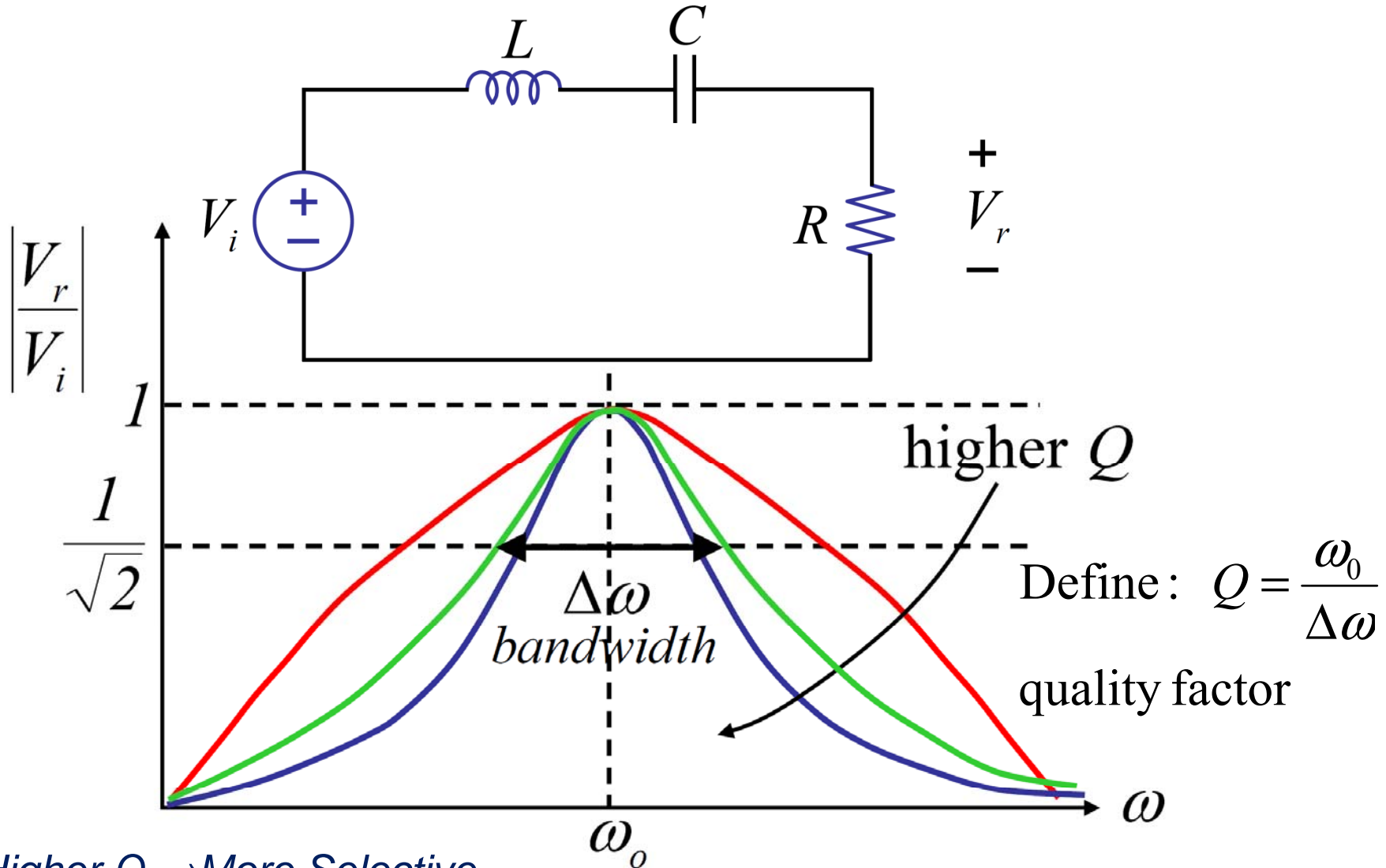Selectivity: Look at series RLC in more detail



Higher $Q \Rightarrow$ More Selective

Quality Factor Q



• To find quality factor $Q = \frac{\omega_0}{\Delta\omega}$

• We need to find ω_0 and $\Delta\omega = ?$

• Recall

$$\frac{V_r}{V_i} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{1 + j\left(\omega \frac{L}{R} - \frac{1}{\omega CR}\right)}$$

• At ω_0 , we have $\omega_0 \frac{L}{R} - \frac{1}{\omega_0 CR} = 0$

• ω_0 is simply : $\omega_0 = \frac{1}{\sqrt{LC}}$

Quality Factor Q



- $\Delta\omega$ is the bandwidth, i.e. ω between magnitude fall to -3dB

- We need to find

$$\left| \frac{\mathbf{V}_r}{\mathbf{V}_i} \right| = \frac{V_r}{V_i} = \frac{1}{\sqrt{2}} = \left| \frac{1}{1 + j \left(\omega \frac{L}{R} - \frac{1}{\omega CR} \right)} \right| = \left| \frac{1}{1 \pm j} \right|$$

- That is $\omega \frac{L}{R} - \frac{1}{\omega CR} = \pm 1$

- Or $\omega^2 \mp \frac{R}{L} \omega - \frac{1}{LC} = 0$

$$\omega_1 = \frac{R}{2L} + \frac{1}{2} \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

- The roots of both equations are

$$\omega_2 = -\frac{R}{2L} + \frac{1}{2} \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

- $\Delta\omega$ is simply : $\Delta\omega = \omega_1 - \omega_2 = \frac{R}{L}$

Quality Factor Q



• The quality factor $Q = \frac{\omega_0}{\Delta\omega}$

• Q is simply : $Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\frac{R}{L}} = \frac{\omega_0 L}{R}$ $\omega_0 = \frac{1}{\sqrt{LC}}$



• Q is simply : $Q = \frac{\omega_0 L}{R}$

• The lower the R (for series RLC), the sharper the peak.

• Another way of looking at Q:

$$Q = 2\pi \frac{\text{Energy Stored}}{\text{Energy lost per cycle}} = 2\pi \frac{\frac{1}{2} L |I_r|^2}{\frac{1}{2} R |I_r|^2 \frac{2\pi}{\omega_0}} = \frac{\omega_0 L}{R}$$

Parallel RLC

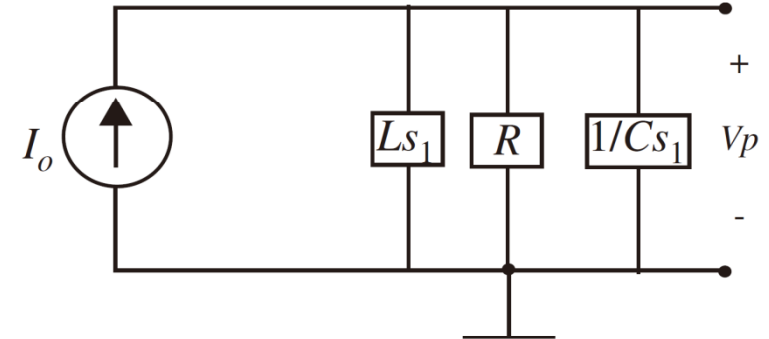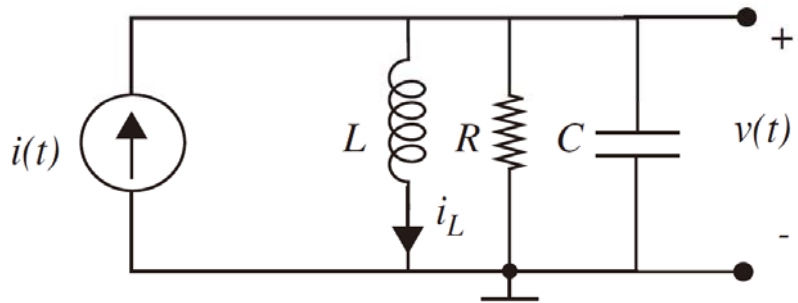

• To find V_p
$$V_p = I_0 \frac{1}{\frac{1}{j\omega L} + \frac{1}{R} + j\omega C} = I_0 \frac{R}{1 + j\left(\omega CR - \frac{R}{\omega L}\right)}$$

$$\frac{V_p}{I_0} = \frac{R}{1 + j\left(\omega CR - \frac{R}{\omega L}\right)} = \frac{1}{G + j\left(\omega C - \frac{1}{\omega L}\right)}$$

Quality Factor Q



• To find quality factor $Q = \frac{\omega_0}{\Delta\omega}$

• We need to find ω_0 and $\Delta\omega = ?$

• Recall

$$\frac{V_p}{I_0} = \frac{R}{1 + j\left(\omega CR - \frac{R}{\omega L}\right)}$$

• At ω_0 , we have $\omega_0 CR - \frac{R}{\omega_0 L} = 0$

• ω_0 is simply : $\omega_0 = \frac{1}{\sqrt{LC}}$

Quality Factor Q



- $\Delta\omega$ is the bandwidth, i.e. ω between magnitude fall to -3dB

- We need to find

$$\left| \frac{\mathbf{V}_i}{\mathbf{I}_0} \right| = \frac{V_i}{I_0} = \frac{R}{\sqrt{2}} = \left| \frac{R}{1 + j\left(\omega CR - \frac{R}{\omega L}\right)} \right| = \left| \frac{1}{1 \pm j} \right|$$

- That is $\omega CR - \frac{R}{\omega L} = \pm 1$

- Or $\omega^2 \mp \frac{1}{RC}\omega - \frac{1}{LC} = 0$

$$\omega_1 = \frac{1}{2RC} + \frac{1}{2} \sqrt{\frac{1}{R^2C^2} + \frac{4}{LC}}$$

- The roots of both equations are

$$\omega_2 = -\frac{1}{2RC} + \frac{1}{2} \sqrt{\frac{1}{R^2C^2} + \frac{4}{LC}}$$

- $\Delta\omega$ is simply: $\Delta\omega = \omega_1 - \omega_2 = \frac{1}{RC}$



Transfer Function



- Transfer function

$$\frac{V_p}{I_0} = \frac{R}{1 + j\left(\omega CR - \frac{R}{\omega L}\right)}$$

- Magnitude and Phase plots.

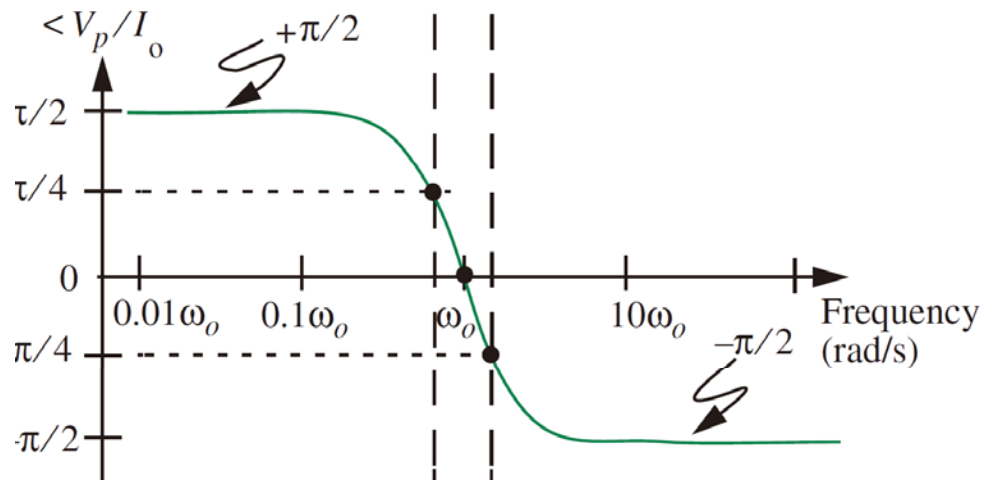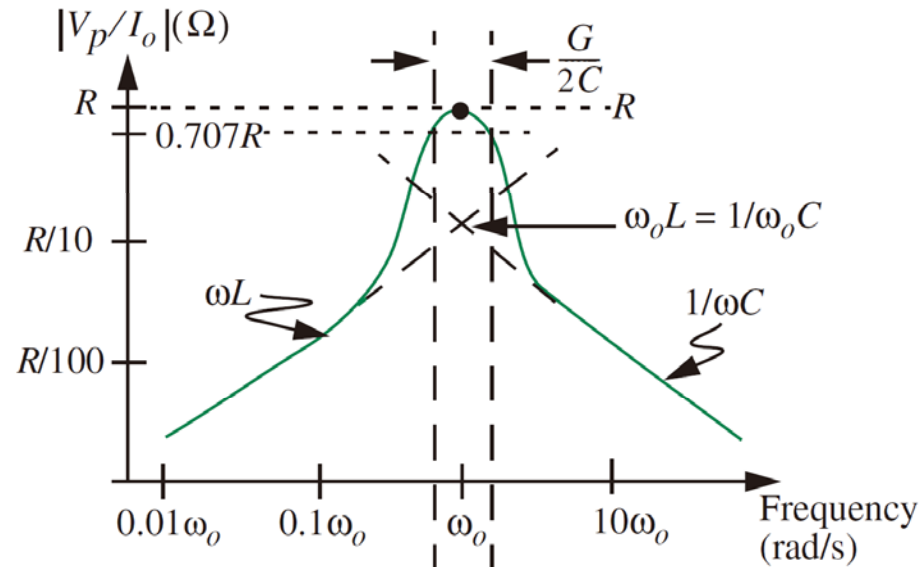

Example




- $L = 0.1 \text{ mH}$, $C = 1 \text{ } \mu\text{F}$ and $R = 10 \text{ } \Omega$
- **Transfer function**

$$\frac{V_c}{I_0} = \frac{R}{1 + j\left(\omega CR - \frac{R}{\omega L}\right)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^5}{2} \text{ rad/s}$$


$$Q = \frac{\omega_0}{2\alpha} = 1$$

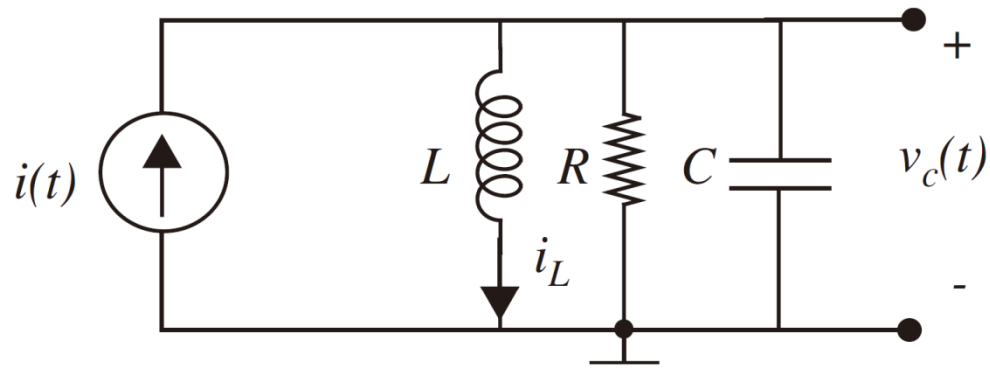

Magnitude and Phase plots



Log scale


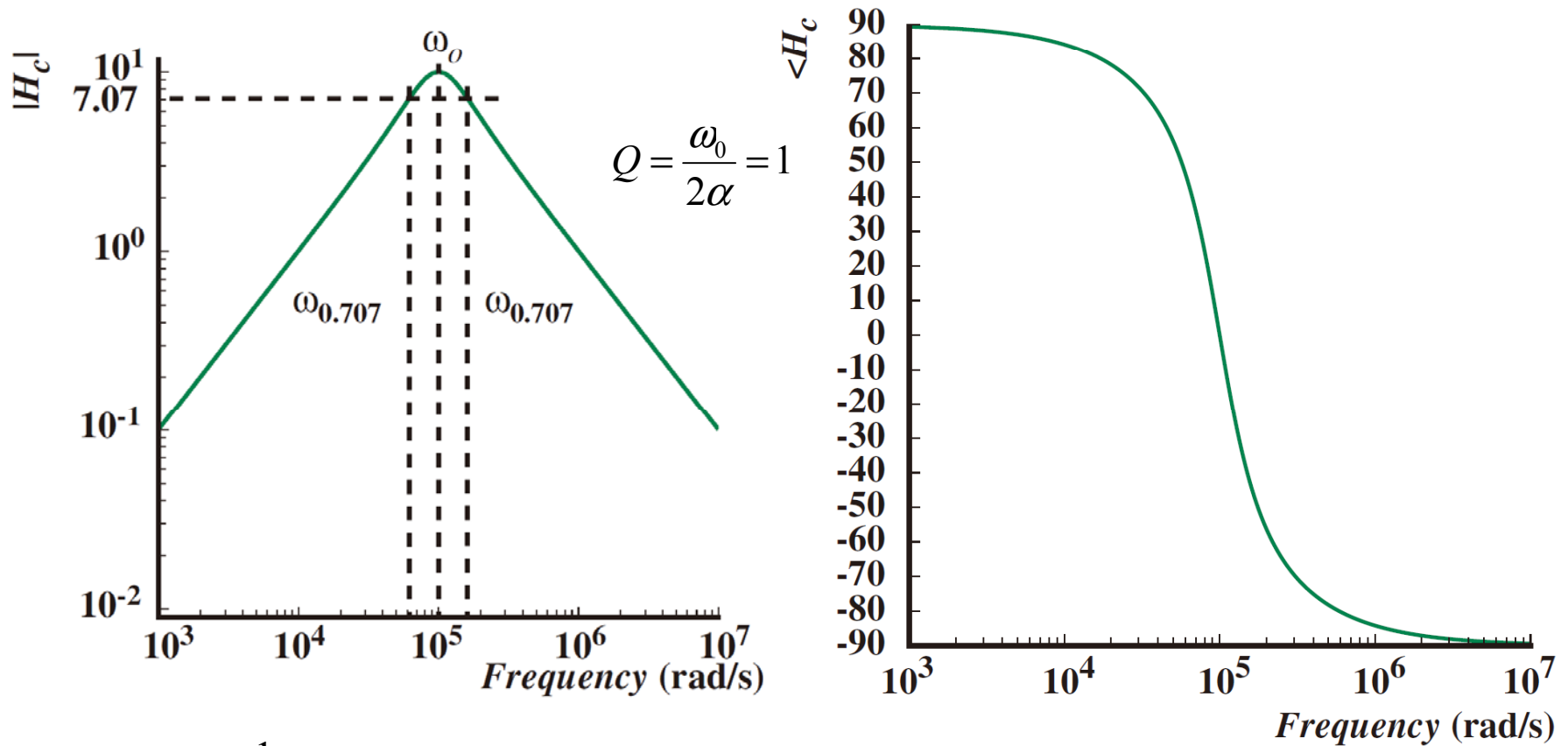


$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/s}$$

Magnitude and Phase plots



Linear scale

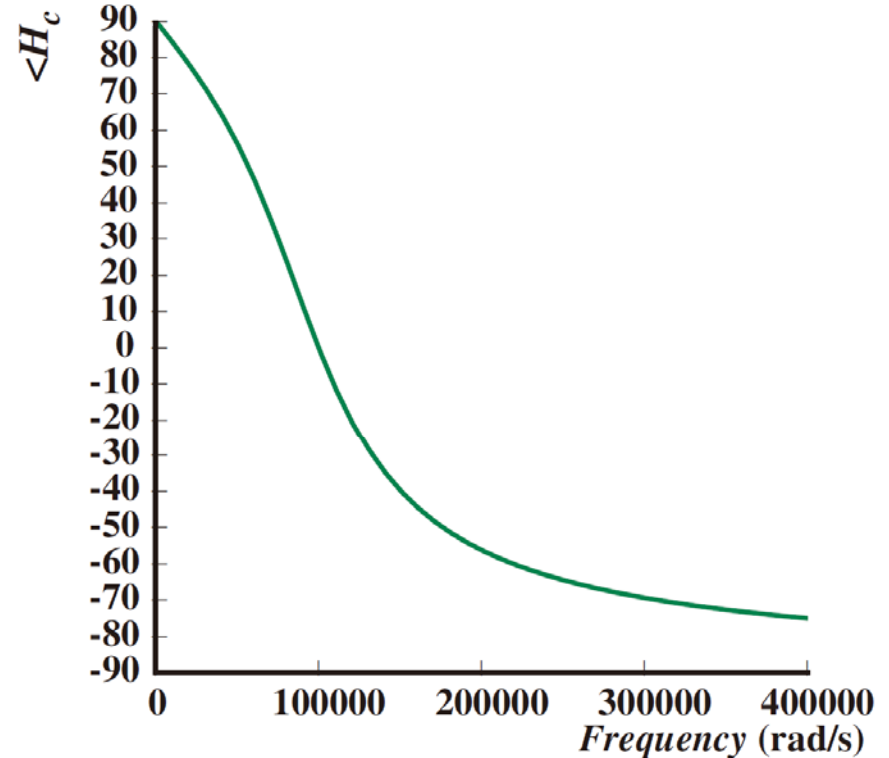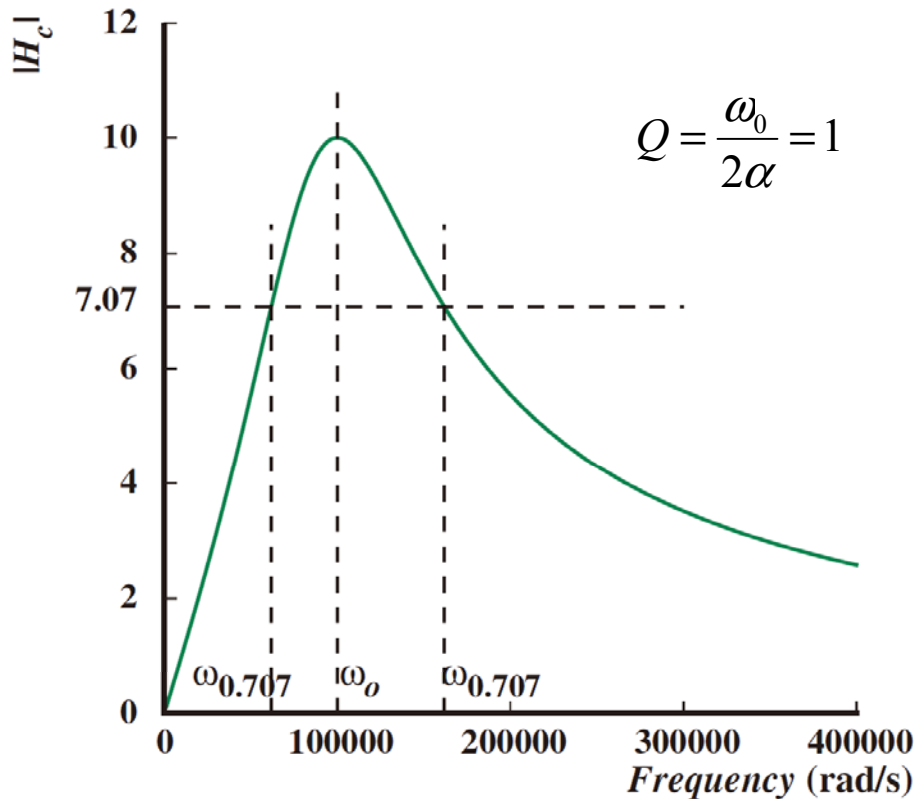



$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^5 \text{ rad/s}$$

Transfer Function and Q



● **Transfer function**
$$\frac{V_p}{I_0} = \frac{R}{1 + j\left(\omega CR - \frac{R}{\omega L}\right)}$$

● **Magnitude and Phase plots.**

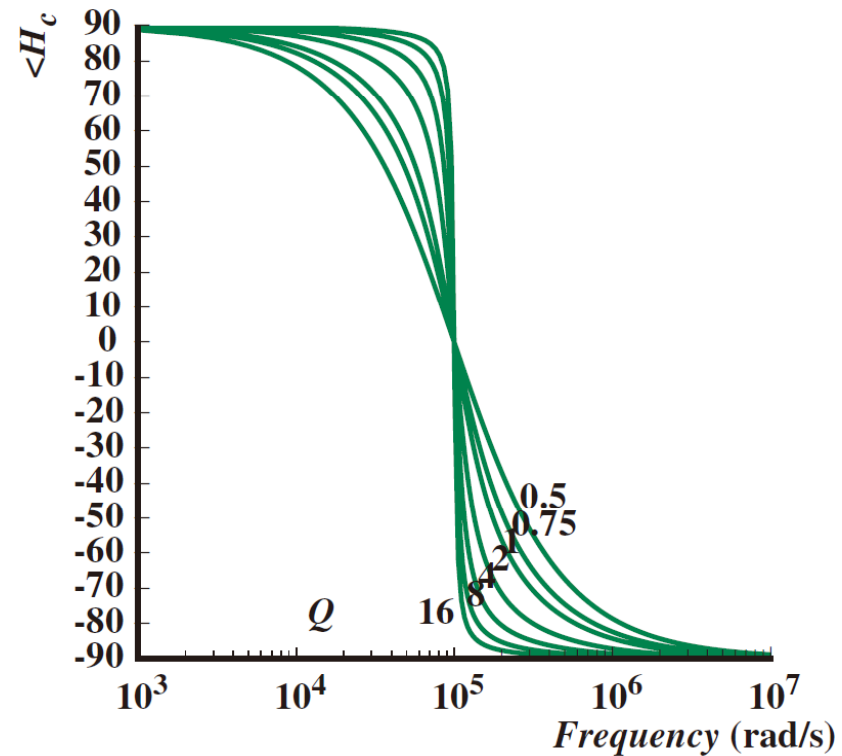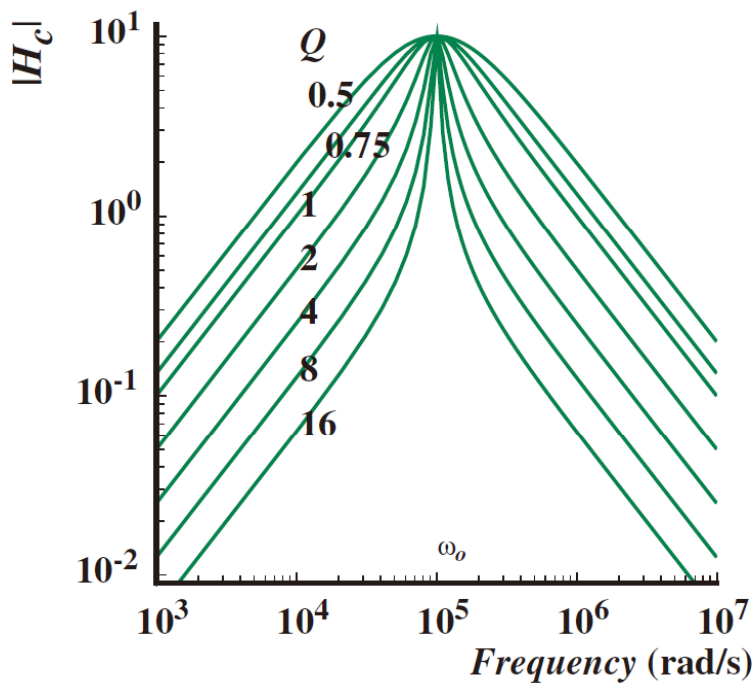

Revisit of the LPF with L




- $L = 20 \text{ mH}$, $C = 13 \text{ nF}$ and $R = 50 \text{ } \Omega$
- **Transfer function**

$$\frac{V_c}{V_i} = \frac{1}{1 + j\left(\omega\frac{L}{R} - \frac{1}{\omega RC}\right)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 6.2 \times 10^4 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = 76.9 \times 10^4 \text{ rad/s} = 12.4\omega_0$$

$$Q = \frac{\omega_0}{2\alpha} = 24.8$$

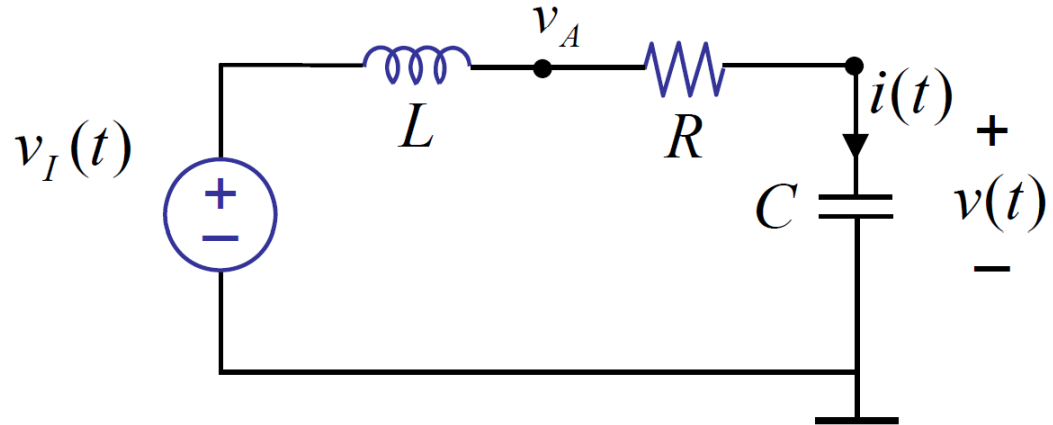


Time-domain Vs Frequency-domain




CAPT

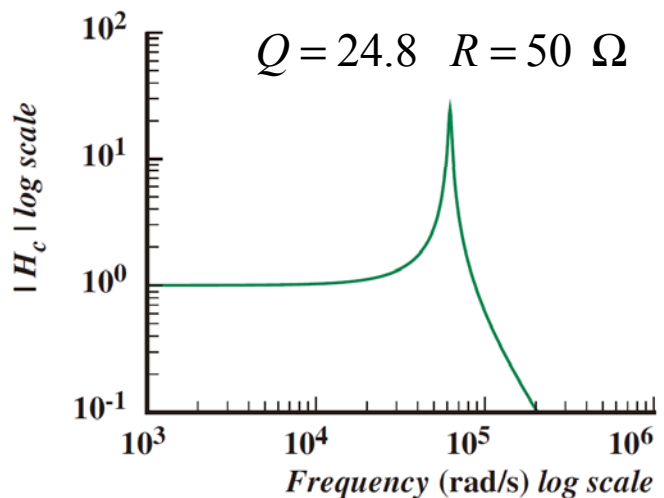
Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN




(a)

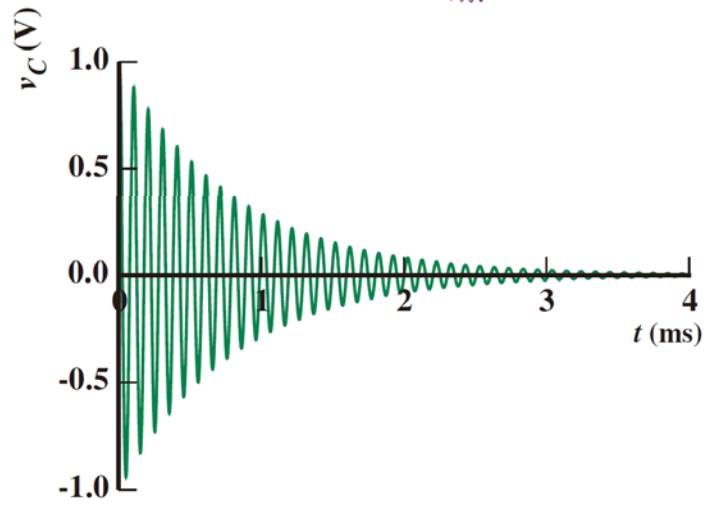

(b)

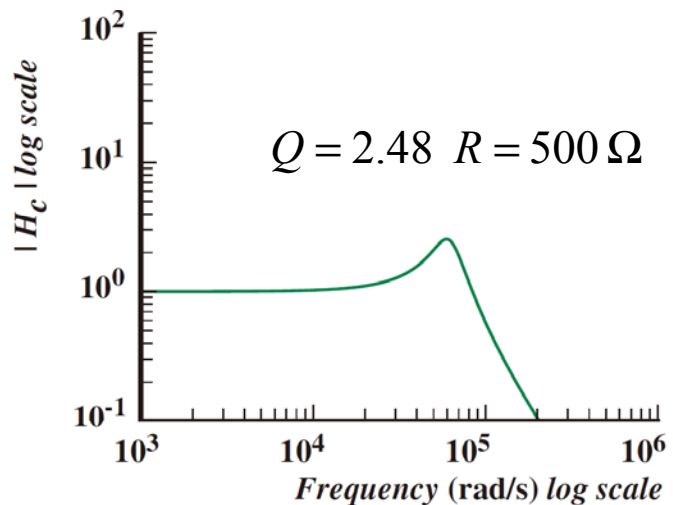

(c)

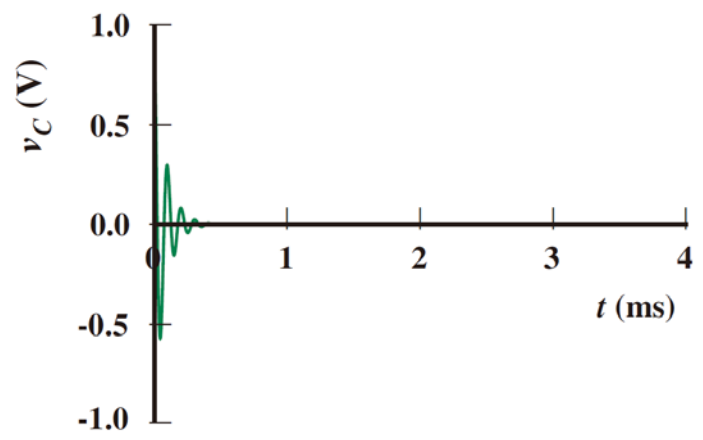

(d)

Power and Energy in an Impedance



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN


- Power and energy are critical issues in the design of circuits.
- The power delivered to some arbitrary impedance $Z = R + jX$ by a sinusoidal source. $v_i(t) = V_i \cos(\omega t + \phi)$

- In Phasor notation $\mathbf{V}_i = V_i e^{j\phi}$

- And

$$\mathbf{I}_i = \frac{\mathbf{V}_i}{Z} = \frac{V_i e^{j\phi}}{R + jX} = \frac{V_i}{\sqrt{R^2 + X^2}} e^{j(\phi - \theta)} = I_i e^{j(\phi - \theta)}$$
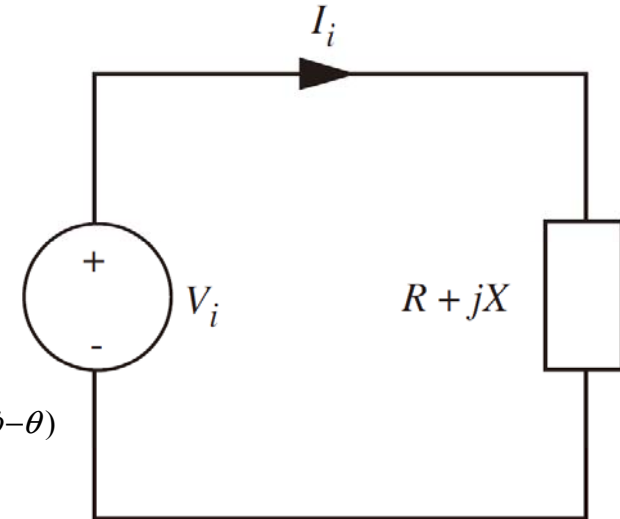
$$\text{Where } \theta = \tan^{-1} \frac{X}{R}$$



- Because power is not a linear function of v and i , we must be cautious about using impedance concepts in power calculations.

Time expressions



- Let's start with time expressions rather than complex amplitudes.
- The current and voltage as a function of time are.

$$i_i(t) = \text{Re}(\mathbf{I}_i e^{j\omega t}) = \frac{V_i}{\sqrt{R^2 + X^2}} \cos(\omega t + \phi - \theta)$$

$$v_i(t) = V_i \cos(\omega t + \phi)$$

- Then, the instantaneous power is given by:

$$\begin{aligned} p(t) = v_i i_i &= \frac{V_i^2}{\sqrt{R^2 + X^2}} \cos(\omega t + \phi) \cos(\omega t + \phi - \theta) \\ &= \frac{1}{2} \frac{V_i^2}{\sqrt{R^2 + X^2}} [\cos(2\omega t + 2\phi - \theta) + \cos \theta] \end{aligned}$$

- The instantaneous power for sinusoidal drive has a sinusoidal component at twice the frequency of the input signal, and the DC component.

Average power



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- Because the average value of $\cos(2\omega t)$ is zero, the average power flowing into an arbitrary impedance is just the DC term of the expression below.

$$p(t) = \frac{1}{2} \frac{V_i^2}{\sqrt{R^2 + X^2}} [\cos(2\omega t + 2\phi - \theta) + \cos \theta]$$

- The average power :

$$\bar{p} = \frac{1}{2} \frac{V_i^2}{\sqrt{R^2 + X^2}} \cos \theta$$

$$\bar{p} = \frac{1}{2} V_i I_i \cos \theta$$

- The average power in terms of complex amplitudes of voltages and currents is one-half the product of the two magnitudes multiplied by the cosine of the angle between them.
- The term $\cos \theta$ is often called **the power factor**.

Average power



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- The average power can also be written directly in terms of complex voltage and complex current.

$$\bar{p} = \frac{1}{2} \operatorname{Re}[\mathbf{V}_i \mathbf{I}_i^*] = \frac{1}{2} \operatorname{Re}[\mathbf{V}_i^* \mathbf{I}_i]$$

Where \mathbf{V}_i^* is the complex conjugate of \mathbf{V}_i .

\mathbf{I}_i^* is the complex conjugate of \mathbf{I}_i .

- Using this notation, $1/2 \mathbf{V} \mathbf{I}^*$ is often called complex power, whence the **real part** of the complex power is the average power, the “**real**” power, and the **imaginary part** is called **reactive power**.

Pure Resistance




- Assume that the impedance is a pure resistance R , that is, $X = 0$ and $\phi = 0$.

$$p(t) = \frac{1}{2} \frac{V_i^2}{\sqrt{R^2}} [\cos(2\omega t) + \cos 0] = \frac{V_i^2}{2R} [1 + \cos(2\omega t)]$$

- The average power dissipated in the resistor is:

$$\bar{p} = \frac{V_i^2}{2R}$$

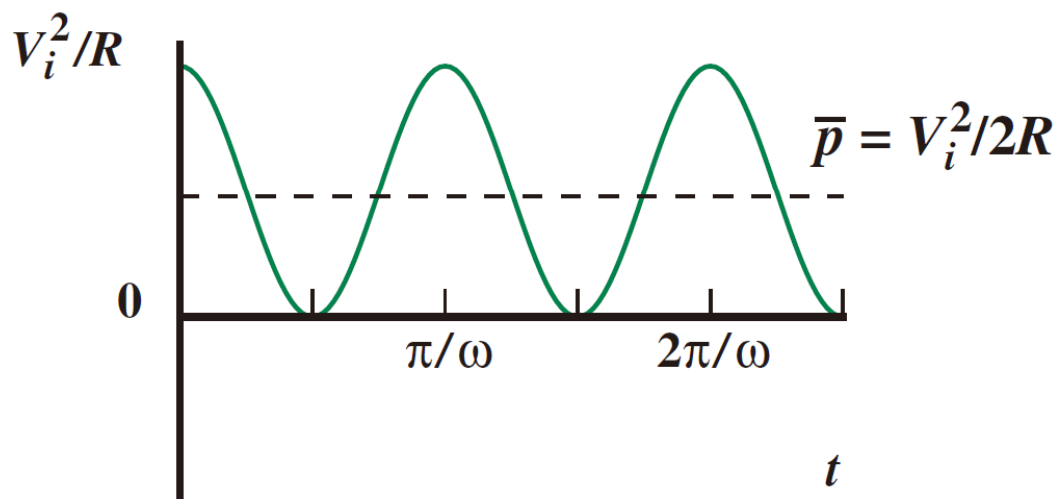- This is exactly one half of the power delivered by the DC voltage of the same amplitude.



Root-Mean-Square (rms) Voltage



- The root-mean-square voltage, abbreviated rms, which is related to the peak amplitude of the sinewave by the square root of two.

$$V_{rms} = \frac{V_i}{\sqrt{2}}$$

- In terms of the rms unit, average power is :

$$\bar{p} = \frac{V_i^2}{2R} = \frac{(V_{rms})^2}{R}$$

- For non-sinusoidal voltages, the general definition of rms voltage is, as the name implies,

$$V_{rms} = \sqrt{\bar{v}^2(t)}$$

- Thus, the 110-V AC power from a wall socket is 110 volts rms,
- Or $110 \times \sqrt{2} = 155.6$ volts peak.

Pure Reactance





- If the impedance consists only of inductor ($\theta = \pi/2$), that is, $R = 0$. Also assume that $\phi = 0$.

$$p(t) = \frac{V_i^2}{2X} \left[\cos\left(2\omega t - \frac{\pi}{2}\right) + \cos\frac{\pi}{2} \right] = \frac{V_i^2}{2X} \cos\left(2\omega t - \frac{\pi}{2}\right) = \frac{V_i^2}{2X} \sin(2\omega t)$$

- If the impedance consists only of capacitor ($\theta = -\pi/2$):

$$p(t) = \frac{V_i^2}{2X} \left[\cos\left(2\omega t + \frac{\pi}{2}\right) + \cos\left(-\frac{\pi}{2}\right) \right] = \frac{V_i^2}{2X} \cos\left(2\omega t + \frac{\pi}{2}\right) = -\frac{V_i^2}{2X} \sin(2\omega t)$$

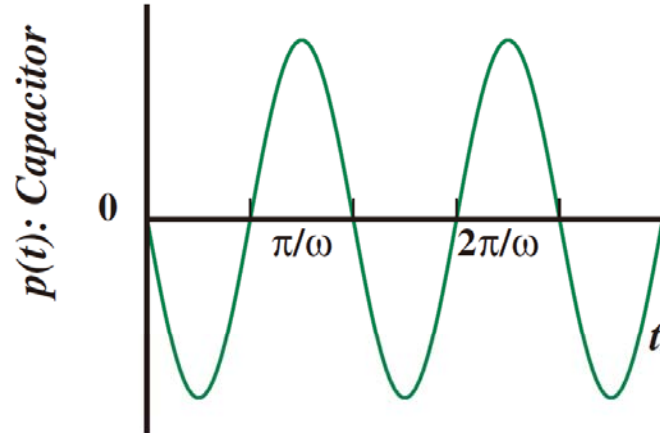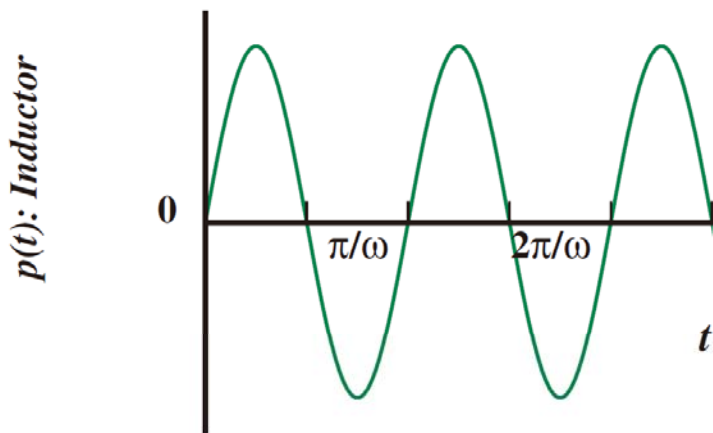- In both cases, the average power is zero.





Pure Reactance



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

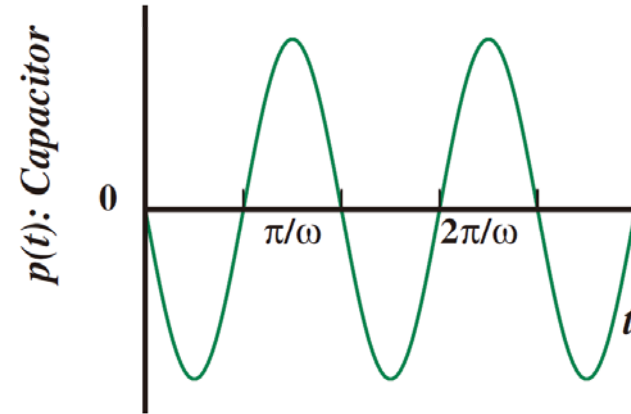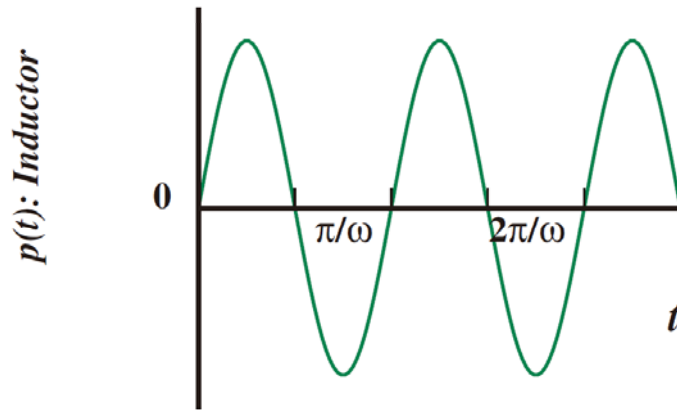- The L's and C's absorb power for two quarters of each cycle, and deliver the power back to the source during the other two quarter cycles.



- Power companies are not happy about this state of affairs, because they still must supply the power and pay for the power losses in the transmission line.
- Although there is no average power supplied to this lossless circuit in the sinusoidal steady state, there is **energy stored** on the average.

Average Stored Energies



- For a capacitor, the stored energy is.

$$W_C = \frac{1}{2} C v^2(t) = \frac{1}{2} C [V_i \cos(\omega t)]^2 = \frac{1}{2} C V_i^2 \left(\frac{1}{2} + \frac{1}{2} \cos(2\omega t) \right)$$

- Again a DC term and a double-frequency term.
- The average stored energy is

$$W_C = \frac{1}{2} C V_i^2 \left(\frac{1}{2} \right) = \frac{1}{4} C V_i^2$$

- A similar derivation for an inductor yields:

$$\overline{W}_L = \frac{1}{4} L I_i^2 \quad \text{where } i_L(t) = I_i \cos(\omega t)$$

Example




- The complex amplitude of the current

$$\mathbf{I}_i = \frac{\mathbf{V}_i}{Z} = \frac{\mathbf{V}_i}{R + \frac{1}{j\omega C}} = \frac{\mathbf{V}_i}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} e^{-j\theta}$$

$$\text{Where } \theta = \tan^{-1} \frac{1}{\omega RC}$$

$$v_i = V_i \cos(\omega t)$$

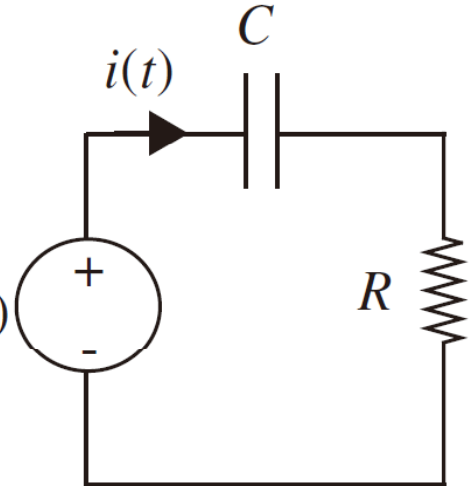


- The average power dissipated in the circuit is

$$\bar{p} = \frac{1}{2} \frac{V_i^2}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \cos \theta = \frac{1}{2} \frac{V_i^2}{|Z|} \cos \theta$$

- At the break frequency or corner frequency
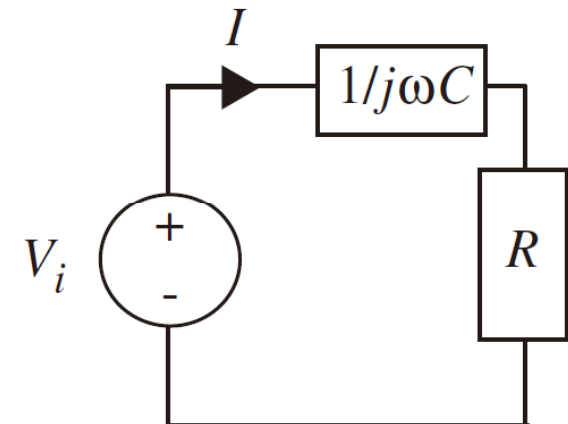
$$\bar{p} = \frac{1}{2} \frac{V_i^2}{R\sqrt{1^2 + 1^2}} \cos \frac{\pi}{4} = \frac{1}{2} \frac{V_i^2}{2R}$$



- Hence the frequency $\omega = 1/RC$ is also called the half-power frequency

Peak Voltage in Resonant Circuit



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN


- Assuming a cosine wave for the voltage source: $v_i(t) = V_i \cos \omega t$
- Assume that the circuit is being driven at its resonant frequency.

$$\mathbf{I} = \frac{\mathbf{V}_i}{1 + j\left(\omega_0 \frac{L}{R} - \frac{1}{\omega_0 RC}\right)} = \frac{\mathbf{V}_i}{R}$$

$$\mathbf{V}_c = \frac{\mathbf{I}}{j\omega_0 C} = \frac{\mathbf{V}_i}{j\omega_0 RC} = -j \frac{\omega_0 L}{R} \mathbf{V}_i$$

$$\Rightarrow V_c = \frac{\omega_0 L}{R} V_i = Q V_i$$
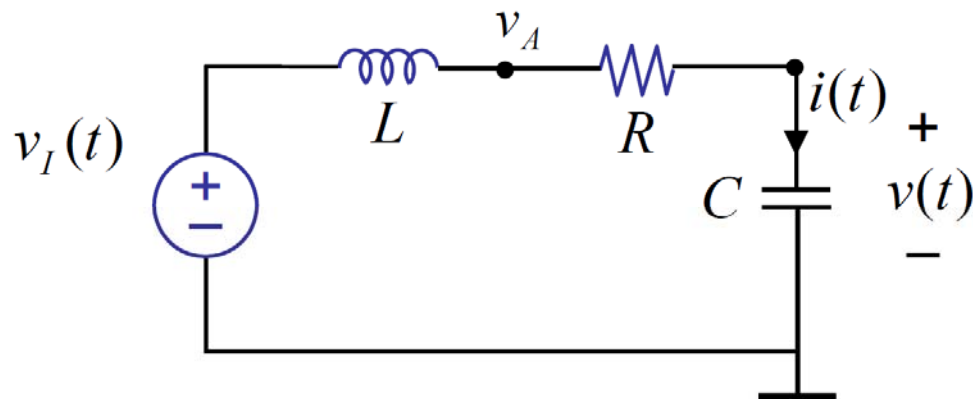
$$\mathbf{V}_l = j\omega_0 L \mathbf{I} = j \frac{\omega_0 L}{R} \mathbf{V}_i \Rightarrow V_l = \frac{\omega_0 L}{R} V_i = Q V_i$$



- The voltage across either the capacitor or the inductor in a series resonant circuit is Q times the input voltage when the circuit is driven at its resonant frequency.

Stored Energy in Resonant Circuit



- Assuming a cosine wave for the voltage source: $v_i(t) = V_i \cos \omega t$
- The voltage across the capacitor is:


$$v_C(t) = \text{Re}[\mathbf{V}_c e^{j\omega_0 t}] = \text{Re}[-jV_i Q e^{j\omega_0 t}] = V_i Q \sin \omega t$$

- The energy stored in the capacitor

$$\begin{aligned} w_C &= \frac{1}{2} C V_i^2 Q^2 \sin^2(\omega_0 t) \\ &= \frac{1}{2} C V_i^2 Q^2 [1 - \cos(2\omega_0 t)] \end{aligned}$$

- The energy stored in the inductor
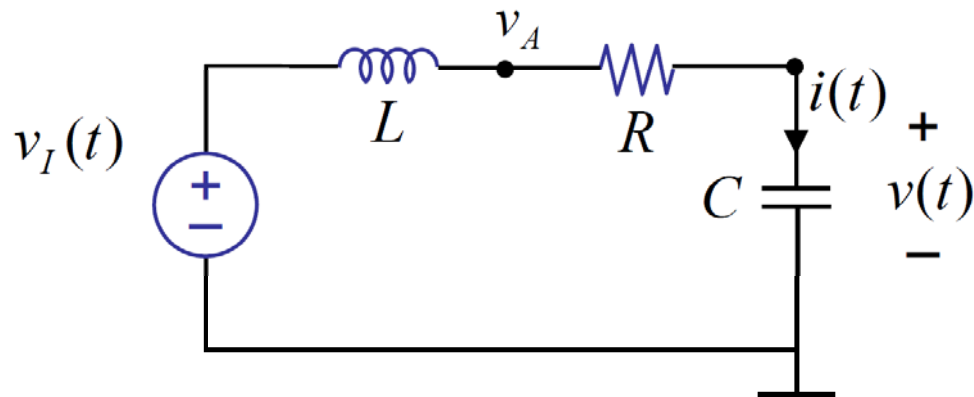
$$i_L(t) = \text{Re}[\mathbf{I} e^{j\omega_0 t}] = \frac{V_i}{R} \cos \omega_0 t$$



$$\begin{aligned} w_L &= \frac{1}{2} L \frac{V_i^2}{R^2} \cos^2(\omega_0 t) \\ &= \frac{1}{2} L \frac{V_i^2}{R^2} [1 + \cos(2\omega_0 t)] \end{aligned}$$

Summary



- The performance of a resonant circuit is summarized by its frequency response. The frequency response comprises plots of magnitude and phase angle versus frequency.
- The magnitude plot is sketched by drawing the low-frequency and the high-frequency asymptotes. The two asymptotes intersect at the break frequency.
- The quality factor Q , the resonant frequency ω_0 , and the damping factor α are three key parameters that characterize the behavior of resonant systems.
- The average power in terms of complex amplitudes of voltages and currents is one-half the product of the two magnitudes multiplied by the cosine of the angle between them.
- The bandwidth is related to the resonant frequency by the quality factor:

$$Q = \frac{\text{Resonant frequency}}{\text{Bandwidth}}$$