

Resistive Networks

Chenhsin Lien and Po-Tai Cheng

CENTER FOR ADVANCED POWER TECHNOLOGIES

Dept. of Electrical Engineering

National Tsing Hua University

Hsinchu, TAIWAN




CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN



Terminology

- A **circuit** is constructed by connecting together a collection of separate elements at their terminals.
- The junction points at which the terminals of two or more elements are connected are referred to as the **nodes** of a circuit.
- The connections between the nodes are referred to as the **edges** or **branches** of a circuit.
- Circuit **loops** are defined to be closed paths through a circuit along its branches.

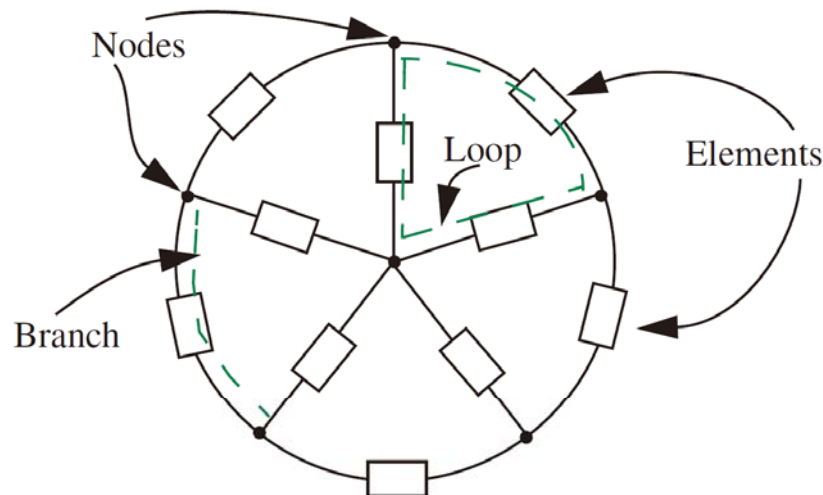


Lumped circuit abstraction



- Capped a set of lumped elements that obey the lumped matter discipline using ideal wires to form an assembly that performs a specific function results in the *lumped circuit abstraction*.

So, what does this buy us?

- For example —

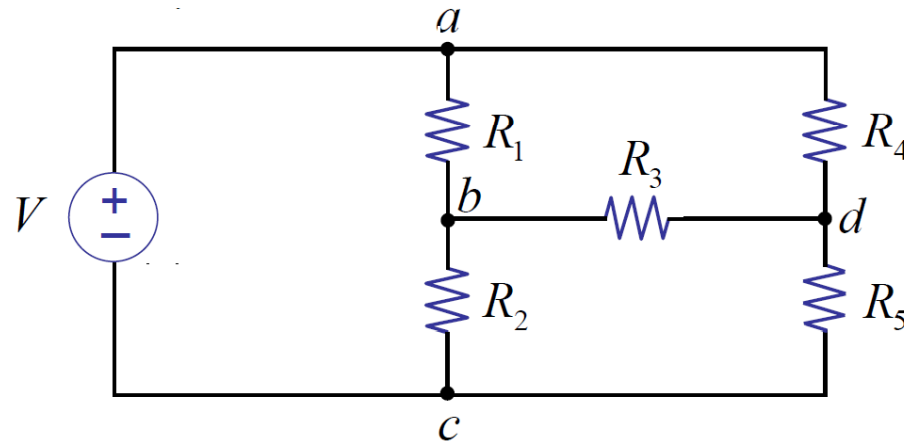


- What can we say about voltages in a loop under the lumped matter discipline?



Kirchhoff's Voltage Law (KVL)

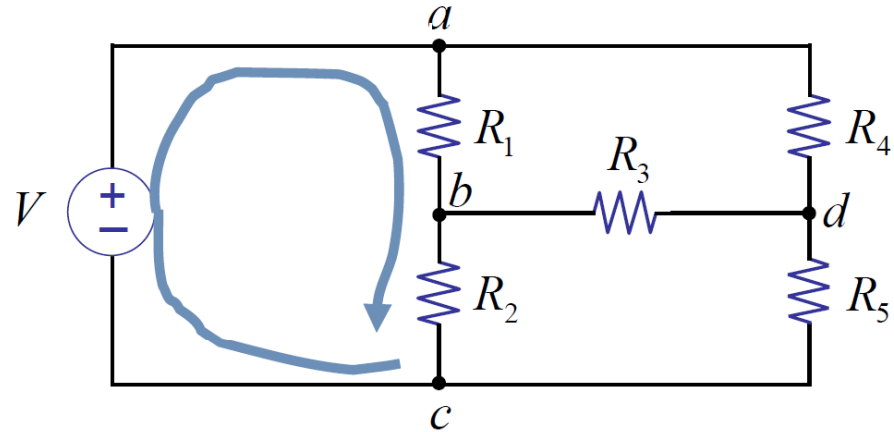- What can we say about voltages in a loop under the lumped matter discipline?



$$\oint_C \mathbf{E} \cdot d\ell = -\frac{\partial \phi_B}{\partial t} = 0$$

$$\int_a^b \mathbf{E} \cdot d\ell + \int_b^c \mathbf{E} \cdot d\ell + \int_c^a \mathbf{E} \cdot d\ell = 0$$


$$V_{ab} + V_{bc} + V_{ca} = 0$$

- Kirchhoff's Voltage Law (KVL):**
The sum of the voltages in a loop is 0.



Kirchhoff's Current Law (KCL)

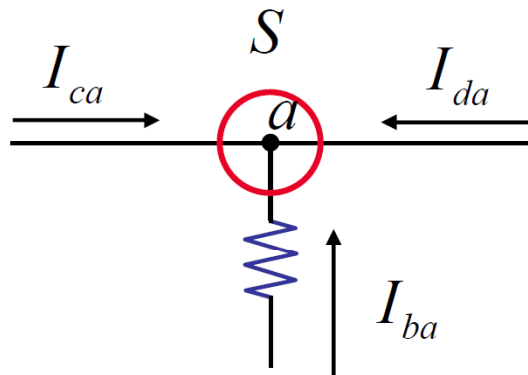- What can we say about currents at a node under the lumped matter discipline?
- Consider —



$$\oint_S \mathbf{J} \cdot d\mathbf{s} = -\frac{\partial q}{\partial t} = 0 \text{ under LMD}$$

$$I_{ba} + I_{ca} + I_{da} = 0$$

- **Kirchhoff's Current Law (KCL):**

The sum of the currents into a node is 0.

- This is simply the conservation of charges.

KVL and KCL Summary



- Maxwell's equations simplify to algebraic KVL and KCL under LMD!

- KVL:

$$\sum_j v_j = 0 \text{ for Loop}$$

- KCL:

$$\sum_j i_j = 0 \text{ for Node}$$

Method 1: Basic KVL, KCL method of Circuit analysis



CAPT
Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN


- Goal: Find all element v 's and i 's.
- Steps
 1. Write element v - i relationships (from lumped circuit abstraction).
 2. Write KCL for all nodes.
 3. Write KVL for all loops.

Lots of unknowns, lots of equations to be solved.


Element v - i relationships




• For resistor R $i = \frac{v}{R}$

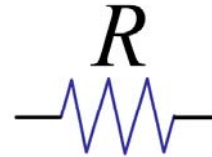

• For voltage source $v = V_0$

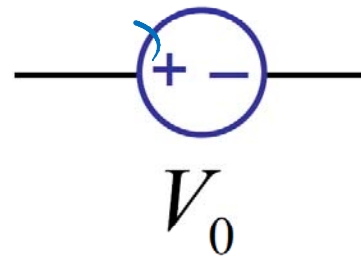


• For current source $i = I_0$

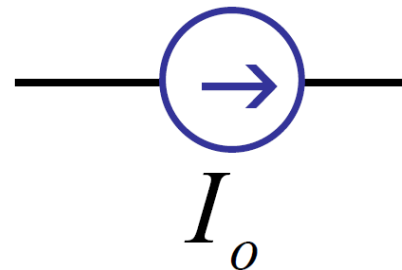



The circuit

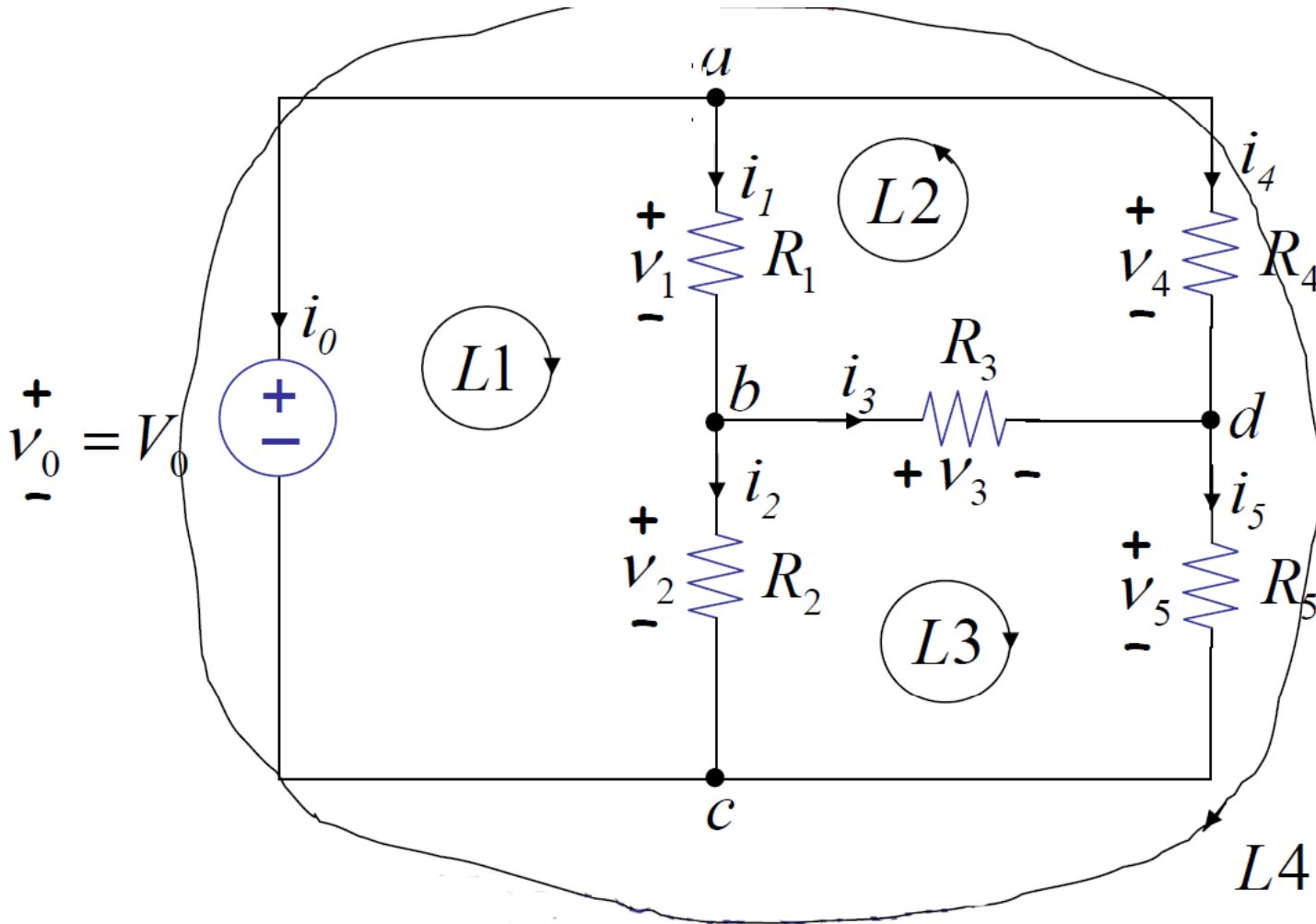

Analysis



• 12 unknowns: $v_0, \dots, v_5, i_0, \dots, i_5$

1. Element relationships: 6 equations.

$$v_0 = V_0 \quad v_3 = i_3 R_3$$

$$v_1 = i_1 R_1 \quad v_4 = i_4 R_4$$

$$v_2 = i_2 R_2 \quad v_5 = i_5 R_5$$

2. KCL at Nodes: 3 equations

$$\mathbf{a} : -i_0 - i_1 - i_4 = 0$$

$$\mathbf{b} : i_1 - i_2 - i_3 = 0$$

$$\mathbf{d} : i_3 + i_4 - i_5 = 0$$

$$\mathbf{c} : i_0 + i_2 + i_5 = 0 \quad \text{redundant}$$

3. KVL for loops: 3 equations

$$\mathbf{L1} : -v_0 + v_1 + v_2 = 0$$

$$\mathbf{L2} : v_1 + v_3 - v_4 = 0$$

$$\mathbf{L3} : v_3 + v_5 - v_2 = 0$$


$$\mathbf{L4} : -v_0 + v_4 + v_5 = 0 \quad \text{redundant}$$

12 unknowns with 12 equations

A very simple example




- The circuit has two branches, one independent source and one resistor, each with a current and a voltage.
- The goal of our circuit analysis is to find these branch variables.
- Two element laws:
 - $i_1 = -I$ and $v_2 = Ri_2$
- The application of KCL at either node yields
 - $i_1 + i_2 = 0$
- The application of KVL at either node yields
 - $-v_1 + v_2 = 0$
- we have assigned a $-$ polarity to v_1 since we first encounter the $-$ sign when traversing the v_1 branch.
- Solve jointly to determine all four branch variables: $-i_1 = i_2 = I$ and $v_1 = v_2 = RI$

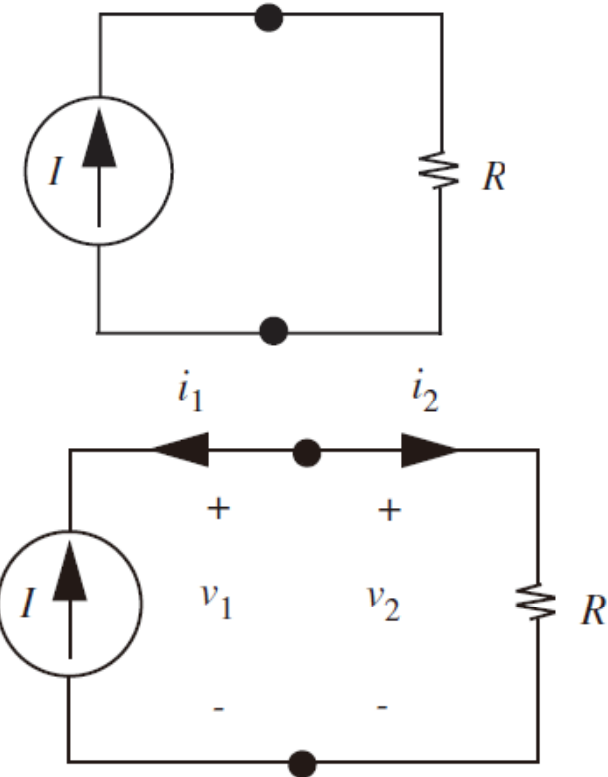

A very simple example




- The circuit has two branches, one independent source and one resistor, each with a current and a voltage.
- The goal of our circuit analysis is to find these branch variables.
- Intuitive approach:
 - $i_2 = I$ and $v_2 = Ri_2$
 - $v_2 = Ri_2 = RI$
- The important message here is that it is not necessary to first assemble all the circuit equations, and then solve them all at once.
- Rather, using a little intuition, it is likely to be much faster to approach the analysis in a different manner.

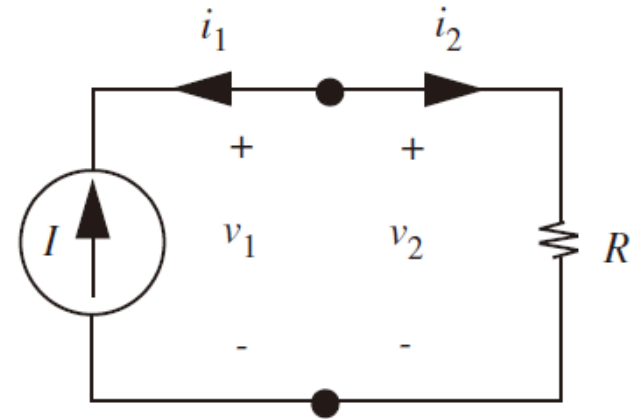

A very simple example



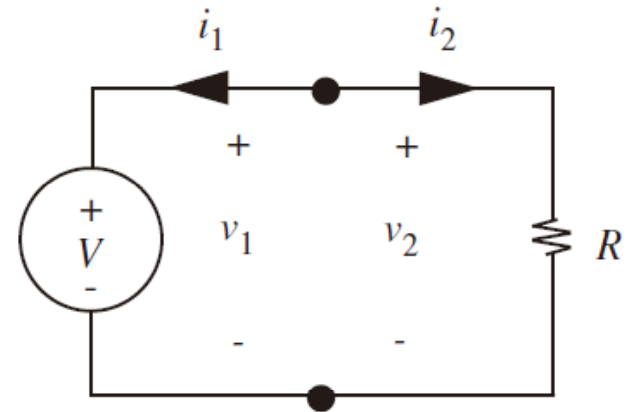- The circuit has two branches, one independent source and one resistor, each with a current and a voltage.
- The goal of our circuit analysis is to find these branch variables.
- Intuitive approach:
 - $v_2 = V$ and $i_2 = v_2/R$
 - $i_2 = V/R$






- It is also important to realize that the physical results of the analysis of the circuit, cannot depend on the polarities of the definitions of the branch variables.

Voltage divider




- A voltage divider is an isolated loop that contains two or more resistors and a voltage source in series.
- Here, we have connected two resistors in series, and connected the pair by some wires to a battery.
- We wish to obtain some arbitrary fraction, say 10%, of the battery voltage at the terminals marked v_2 .
- Want to find the relation between v_2 and the battery voltage V and resistor values, R_1 and R_2 .

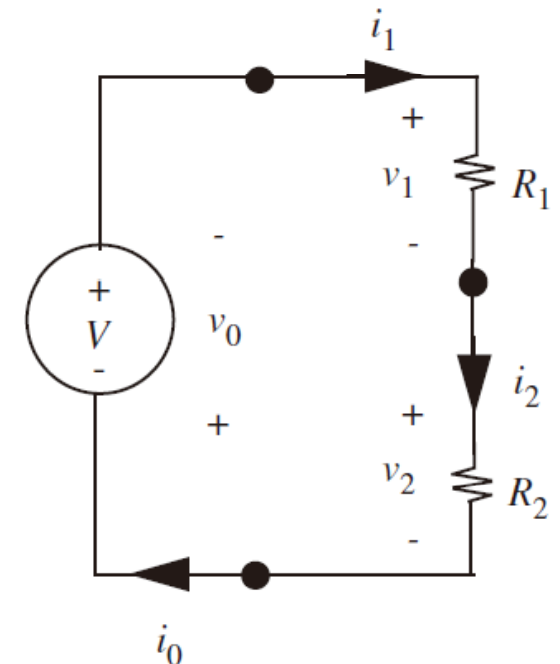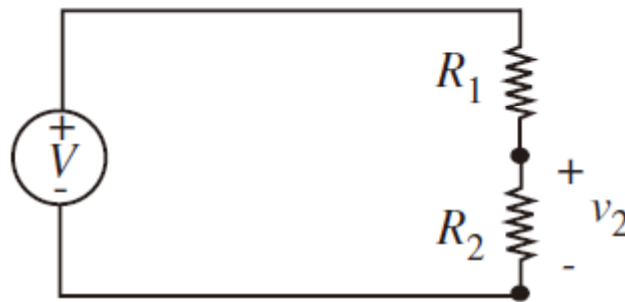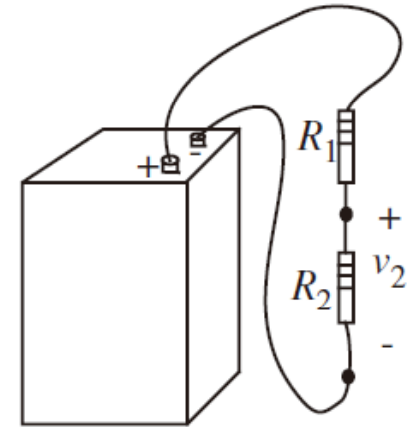

Voltage divider



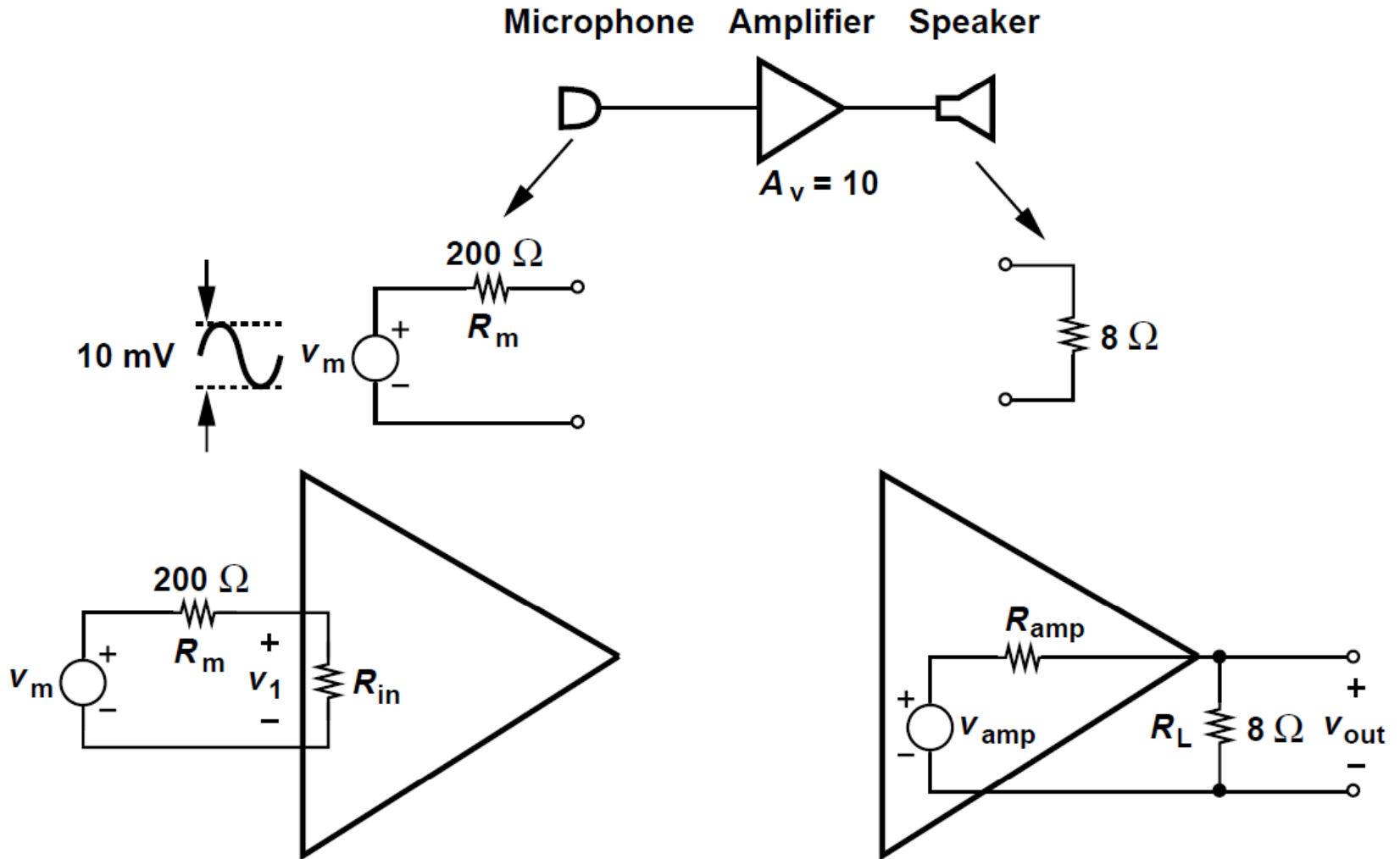- The role of input and output resistance of an amplifier.





Voltage divider

- 6 unknowns: $v_0, v_1, v_2, i_0, i_1, i_2$
- 1. Element relationships: 3 equations.

$$v_0 = -V$$

$$v_1 = i_1 R_1$$

$$v_2 = i_2 R_2$$


- 2. KCL at Nodes: 2 equations

$$i_0 = i_1$$

$$i_1 = i_2$$

- 3. KVL for loops: 1 equation

$$v_0 + v_1 + v_2 = 0$$

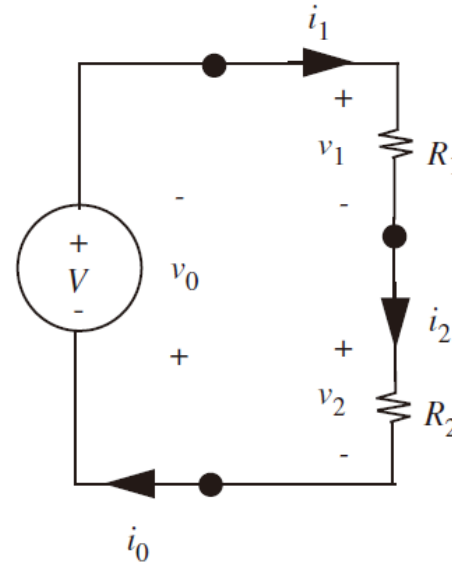

$$i_0 = i_1 = i_2 = \frac{1}{R_1 + R_2} V$$


$$\Rightarrow v_1 = \frac{R_1}{R_1 + R_2} V$$

$$v_2 = \frac{R_2}{R_1 + R_2} V$$

Current divider



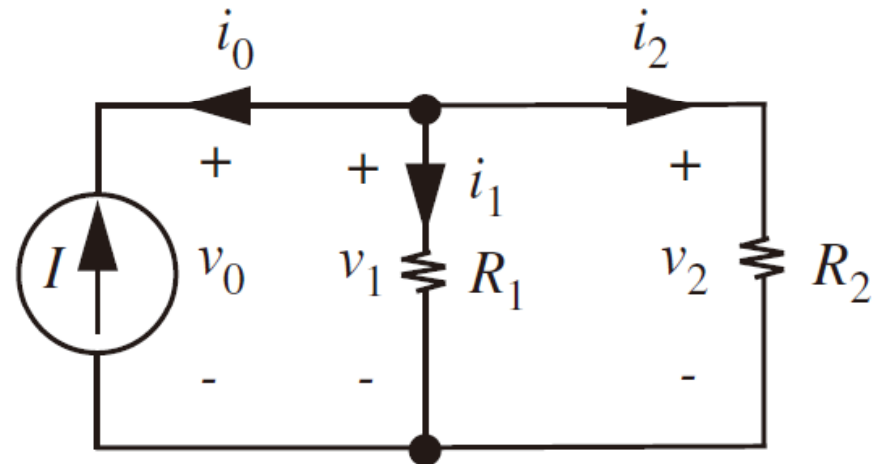- A current divider is a circuit with two nodes joining two or more parallel resistors and a current source.
- Here, a current divider with two resistors is shown.
- In this circuits, the resistors share, or divide, the current from the source in proportion to its conductance.
- Want to find the relation between i_2 (or i_1) and the current I and resistor values, R_1 and R_2 .






Current divider

- 6 unknowns: $v_0, v_1, v_2, i_0, i_1, i_2$
- 1. Element relationships: 3 equations.

$$i_0 = -I$$

$$v_1 = i_1 R_1 \quad \text{or} \quad i_1 = v_1 G_1$$
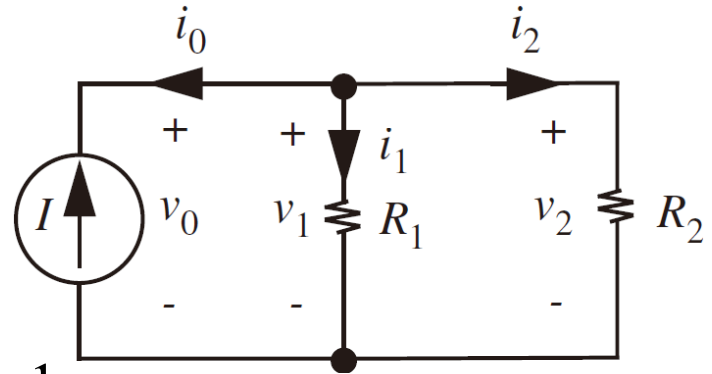
$$v_2 = i_2 R_2 \quad \text{or} \quad i_2 = v_2 G_2 \quad \text{where} \quad G_i = \frac{1}{R_i}$$



- 2. KCL at Nodes: 1 equation

$$i_0 + i_1 + i_2 = 0$$

$$v_0 = v_1 = v_2 = \frac{I}{G_1 + G_2}$$

- 3. KVL for loops: 2 equations

$$v_0 = v_1$$

$$v_1 = v_2$$




$$i_1 = \frac{G_1}{G_1 + G_2} I$$

$$i_2 = \frac{G_2}{G_1 + G_2} I$$



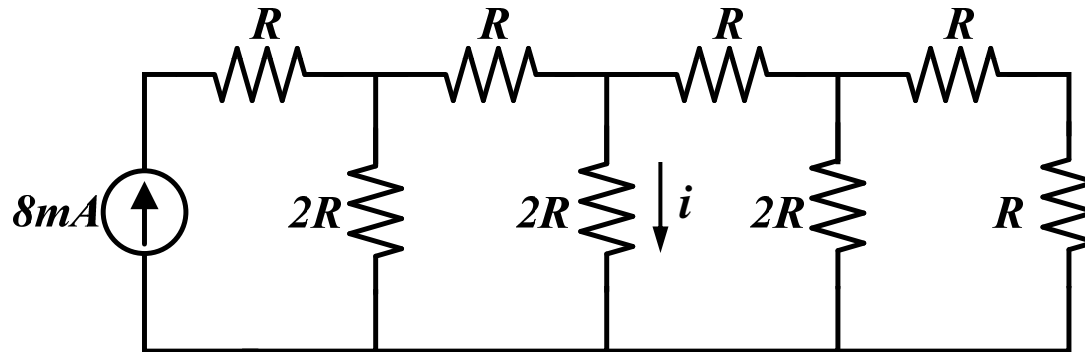Example for Current divider

- Determine the indicated branch current i . i.e. $i = ?$




- This circuit is used in a D/A convertor.

Equivalent Resistances



Series resistors:

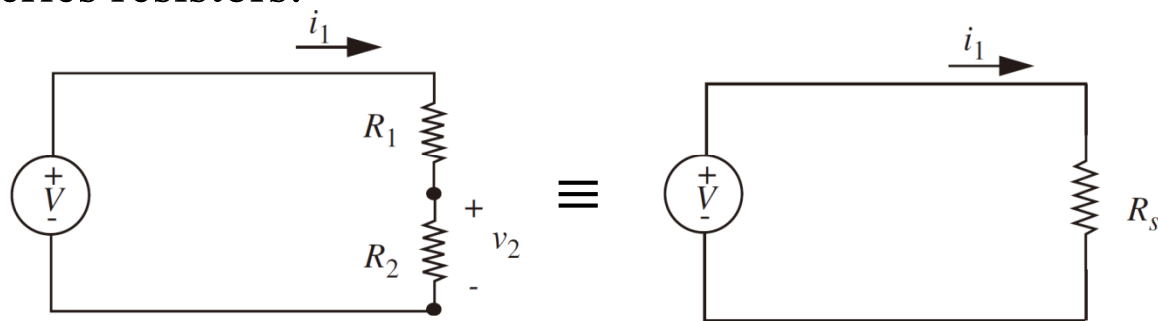


$$i_1 = \frac{V}{R_1 + R_2}$$

$$i_1 = \frac{V}{R_S} \Rightarrow$$


$$R_S = R_1 + R_2$$

Parallel resistors:

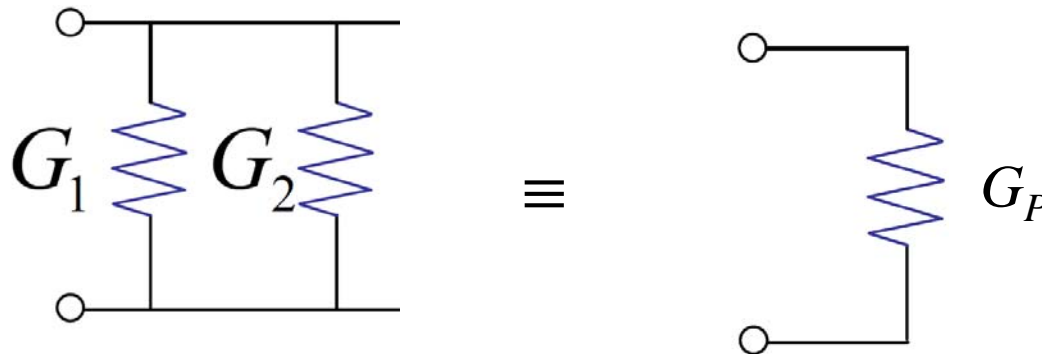

$$G_P = G_1 + G_2$$

A More Complex circuit

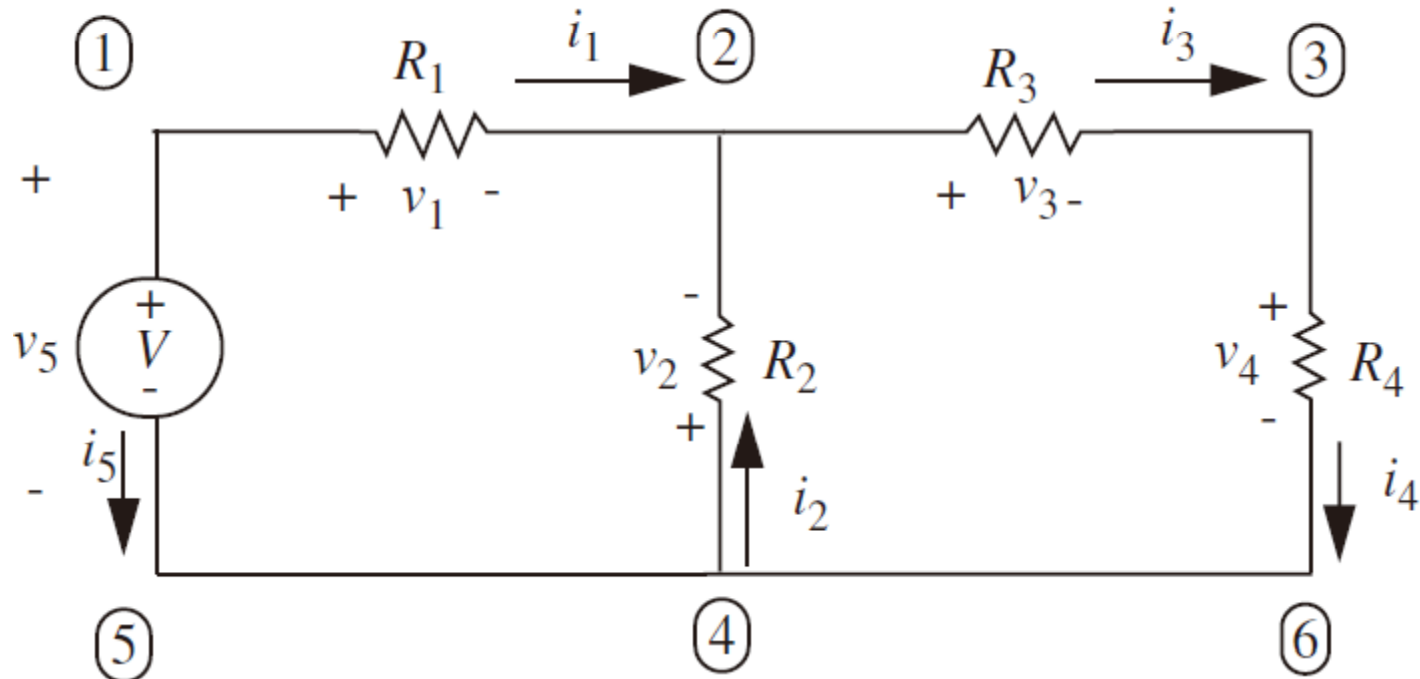

Analysis



10 unknowns: $v_1, \dots, v_5, i_1, \dots, i_5$

1. Element relationships: 5 equations.

$$v_1 = i_1 R_1 \quad v_4 = i_4 R_4$$

$$v_2 = i_2 R_2 \quad v_5 = V$$

$$v_3 = i_3 R_3$$

2. KCL at Nodes: 3 equations

$$1: -i_5 - i_1 = 0$$

$$2: i_1 + i_2 - i_3 = 0$$


$$3: i_3 - i_4 = 0$$

3. KVL for loops: 2 equations

$$\text{L1: } -v_5 + v_1 - v_2 = 0$$

$$\text{L2: } v_2 + v_3 + v_4 = 0$$

10 unknowns with 10 equations

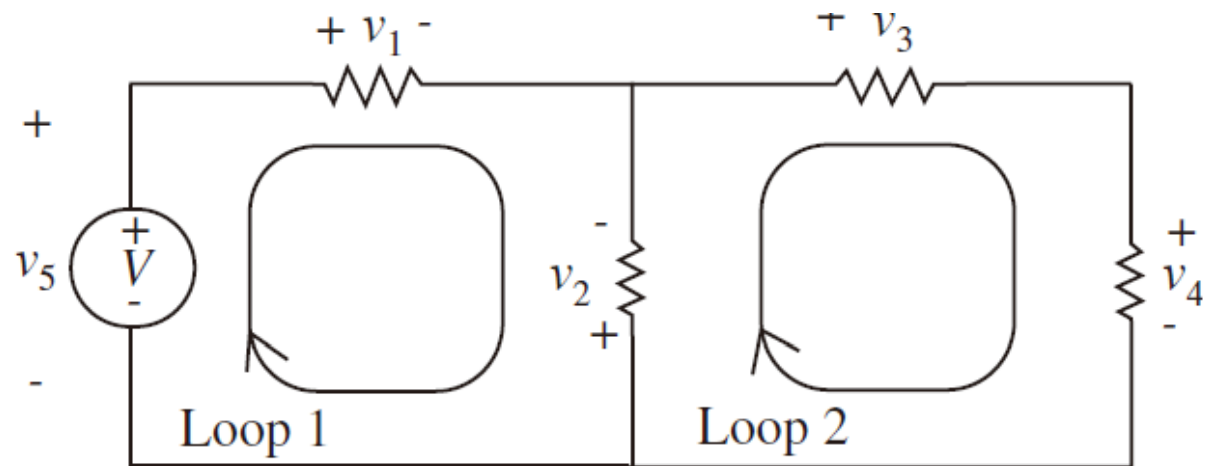

Solutions



$$-i_5 = i_1 = \frac{R_2 + R_3 + R_4}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V$$

$$i_2 = -\frac{R_3 + R_4}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V$$

$$i_3 = i_4 = \frac{R_2}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V$$

Solutions



$$v_1 = \frac{R_1(R_2 + R_3 + R_4)}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V$$

$$v_2 = -\frac{R_2(R_3 + R_4)}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V$$

$$v_3 = \frac{R_2 R_3}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V$$


$$v_4 = \frac{R_2 R_4}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V.$$

$$v_5 = V$$




Method 2: Intuitive method of circuit analysis: Element combination rules

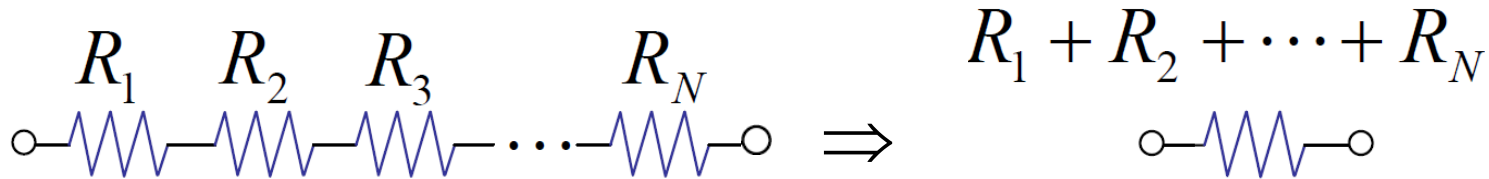- By applying KCL and KVL, we have
- Series resistors




- Parallel resistors

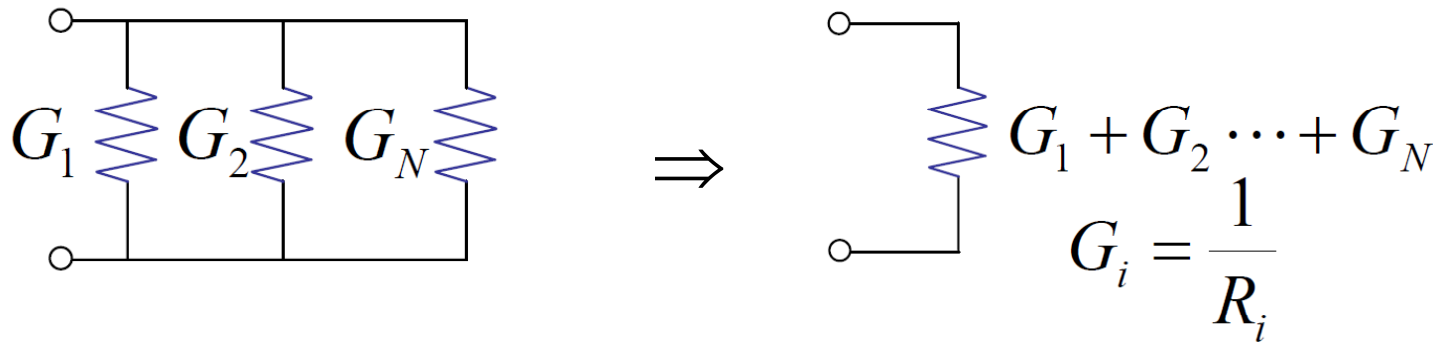


Element combination rules



- Voltage sources

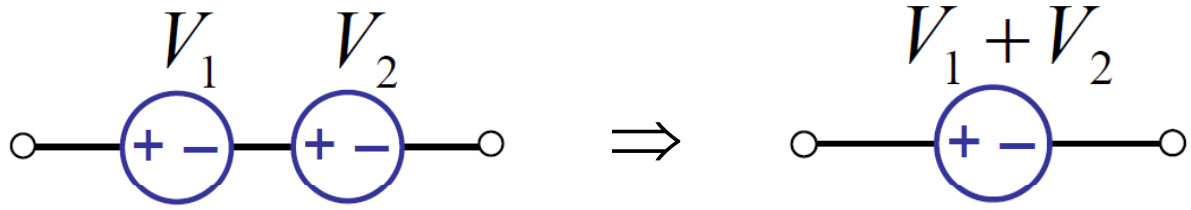

- Current sources

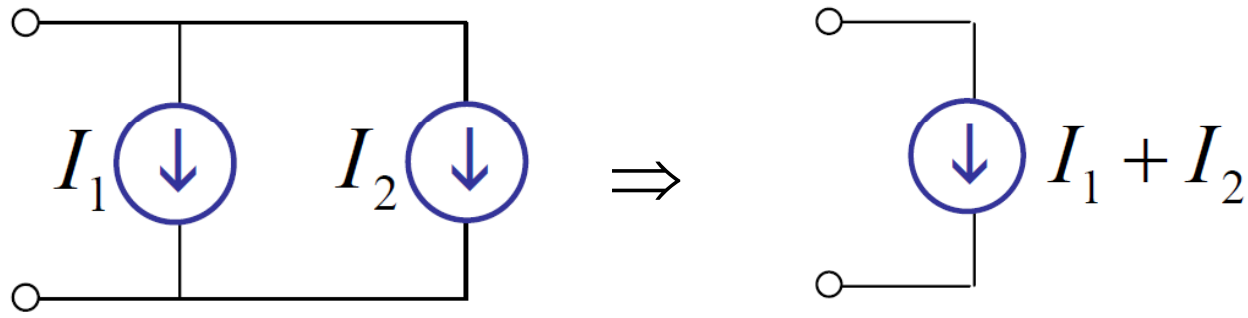


Collapse then Expand Method





CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN


● Collapse (簡化)

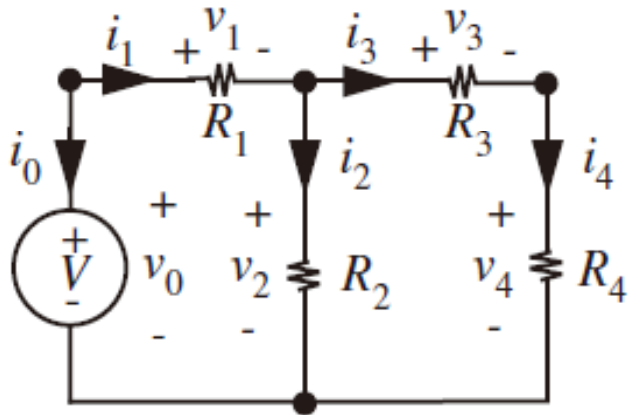

\Rightarrow

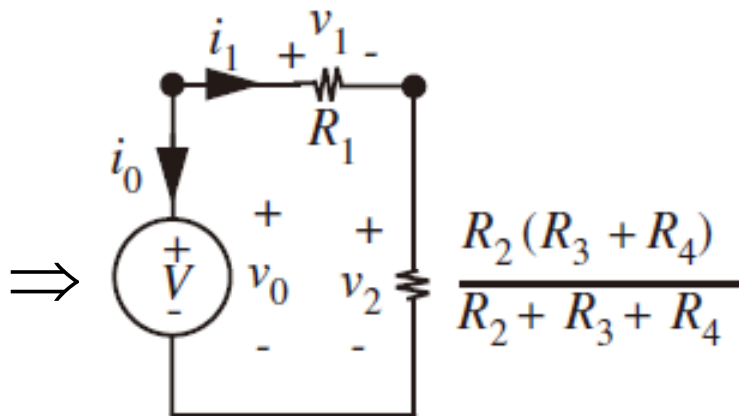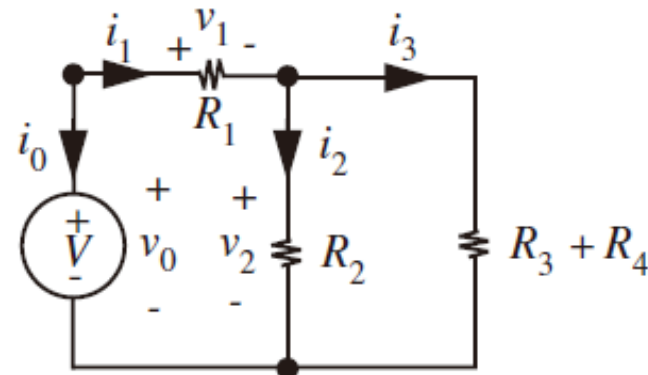

\Rightarrow

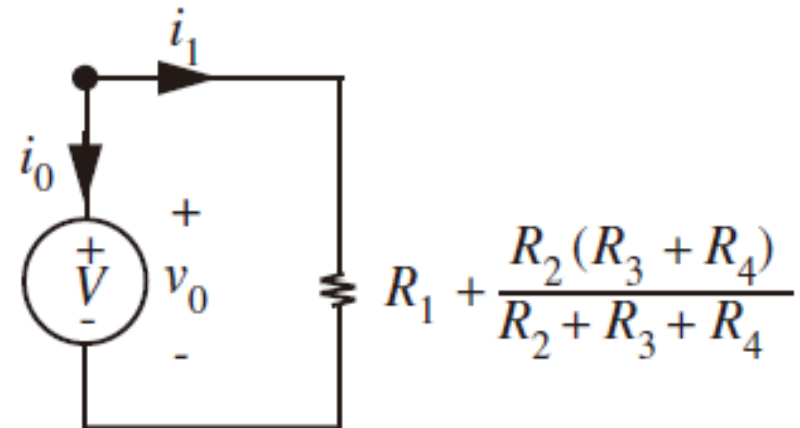


Collapse then Expand Method



CAPT


Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- Expand (展開)
- Find i_1 .

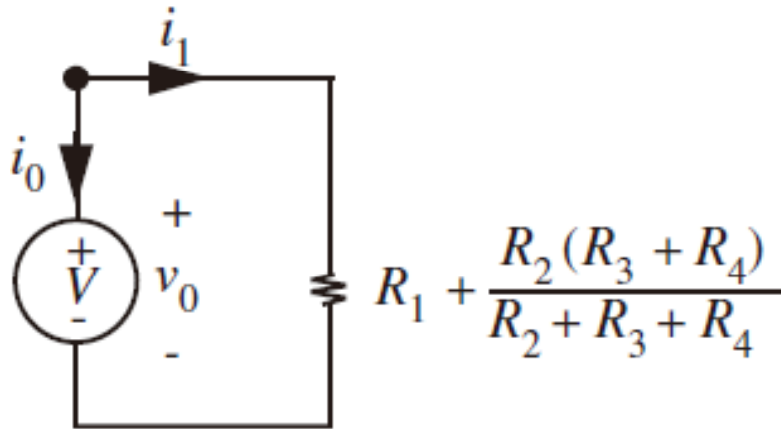

$$i_1 = \frac{V}{R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}}$$

- Find v_2 .

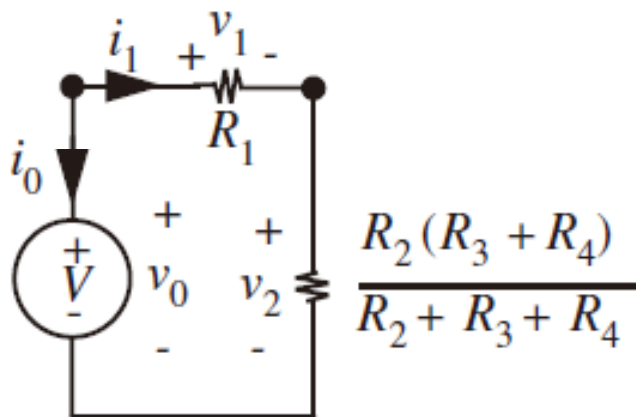


$$v_2 = \frac{\frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}}{R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}} V$$

Collapse then Expand Method




- Expand (展開)
- Find i_2 and i_3 .

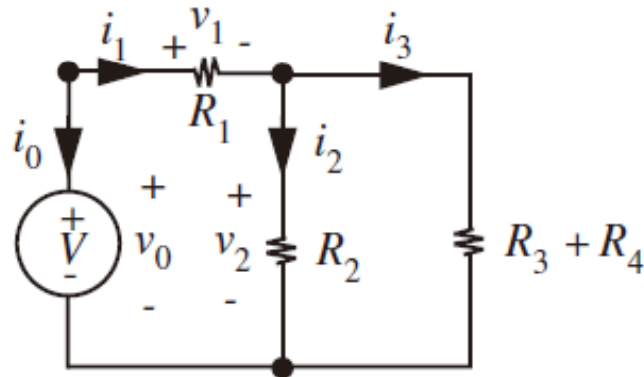

$$i_2 = \frac{v_2}{R_2}$$

$$i_3 = \frac{v_2}{R_3 + R_4}$$

- Find v_3 and v_4 .

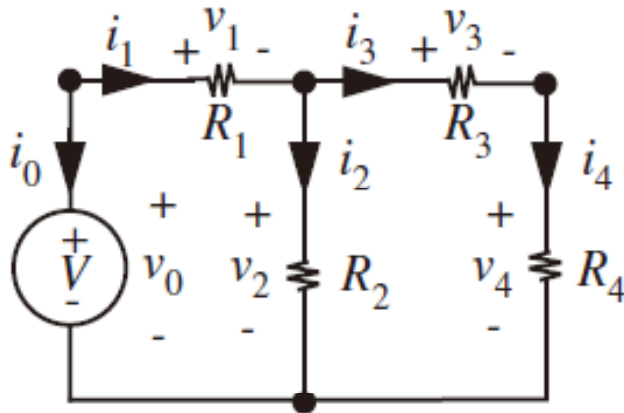




$$v_3 = i_3 R_3$$

$$v_4 = i_3 R_4$$



Example

$$I = ?$$

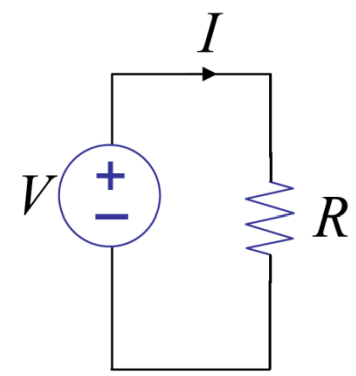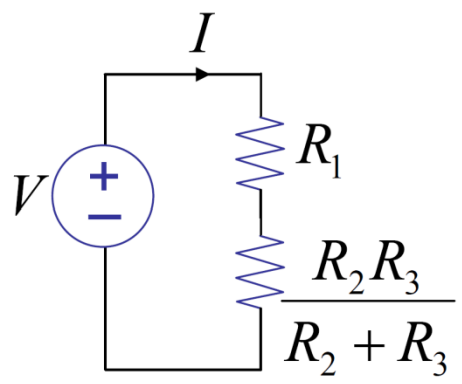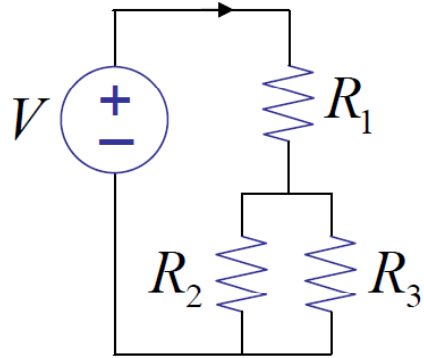



$$I = \frac{V}{R}$$

$$R = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

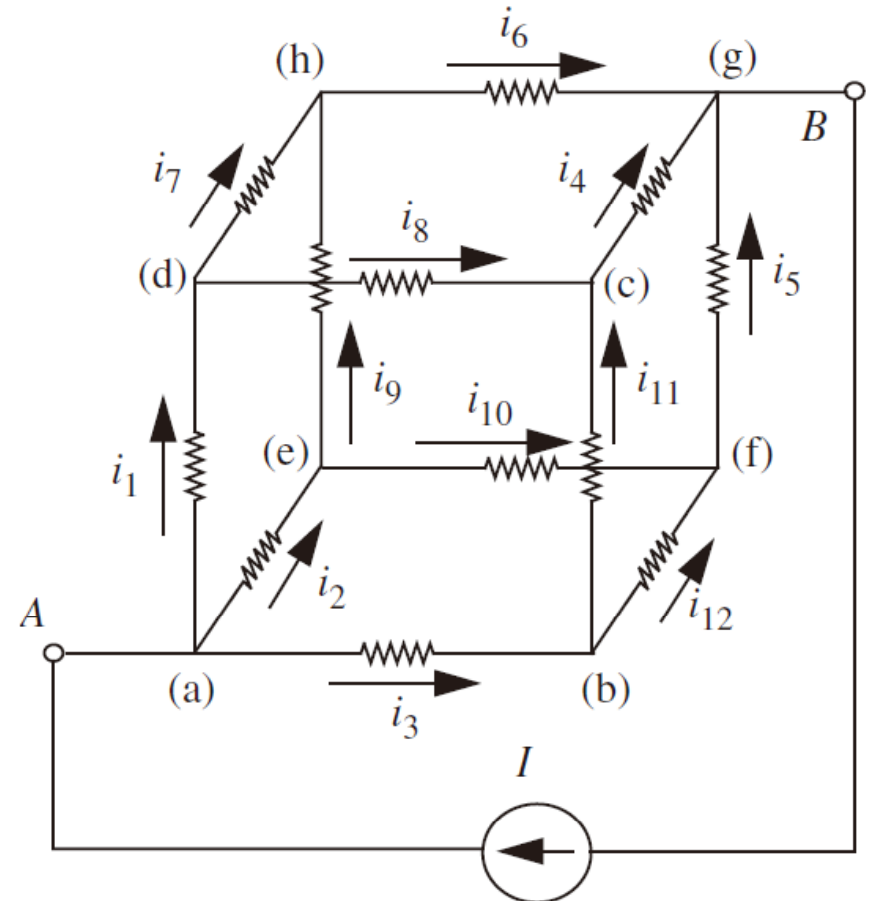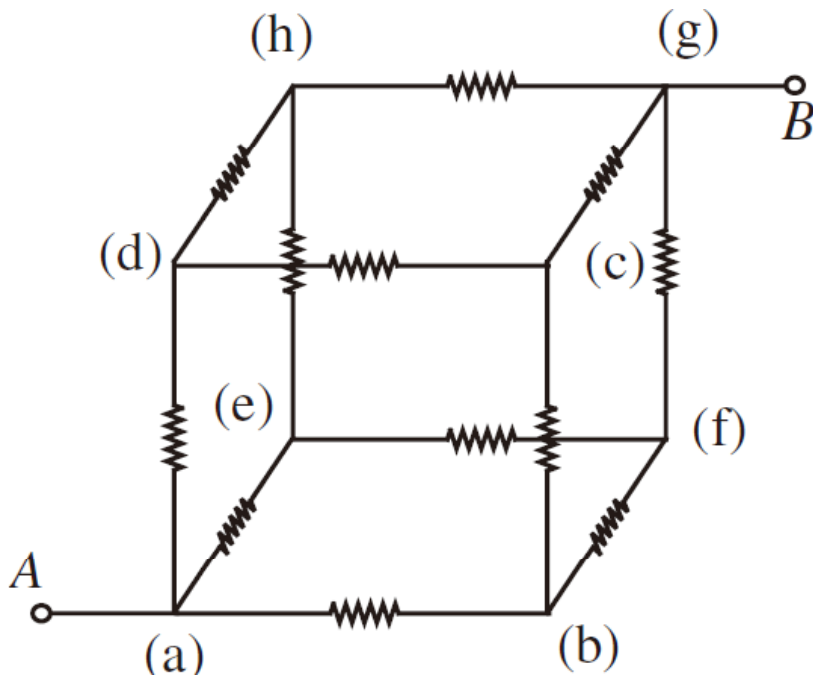Example





- Determine the network equivalent resistance between terminal A and B.
- We can inject a current I into the network and find (or measure) the voltage between A and B.



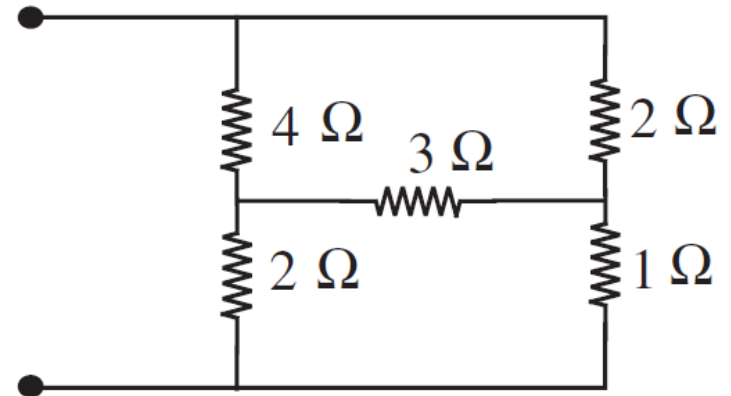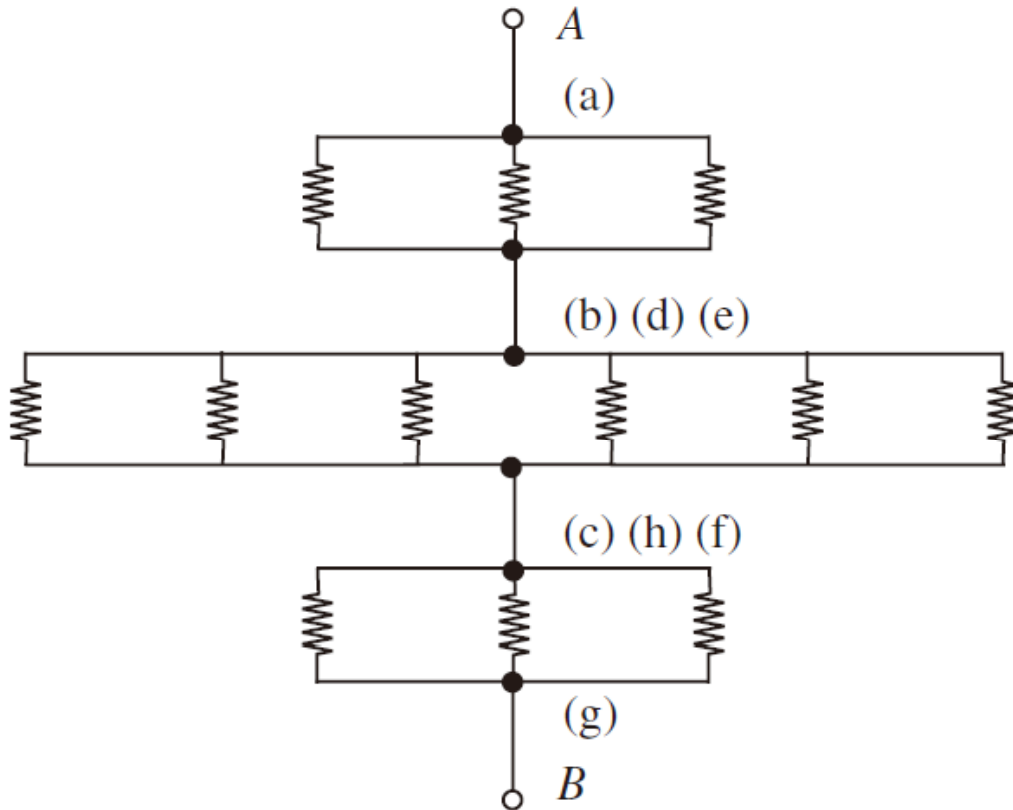Example




- Determine the network equivalent resistance between terminal A and B.



Δ -Y conversion



Delta-Wye Conversion

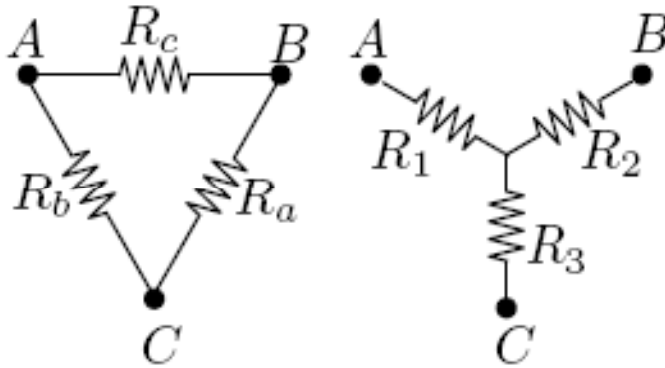

$$R_{AB} = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2$$

$$R_{BC} = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3$$

$$R_{CA} = \frac{R_b (R_c + R_a)}{R_a + R_b + R_c} = R_3 + R_1$$

$$R_1 = \frac{R_c R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Determine the i - v relationship for the two-terminal device

- The two-terminal devices under test

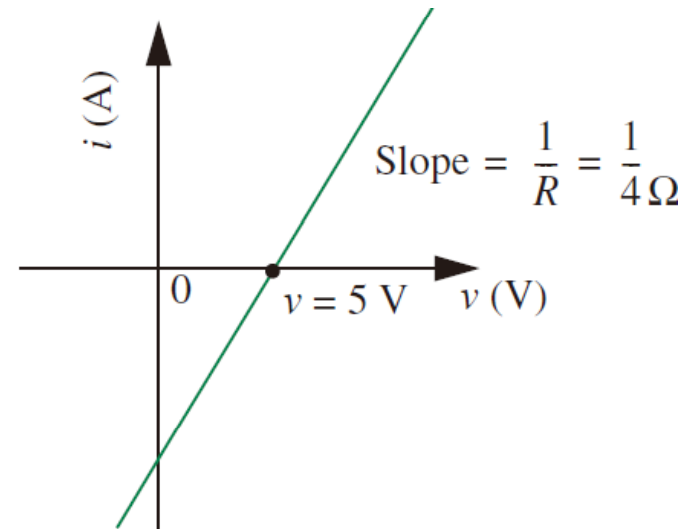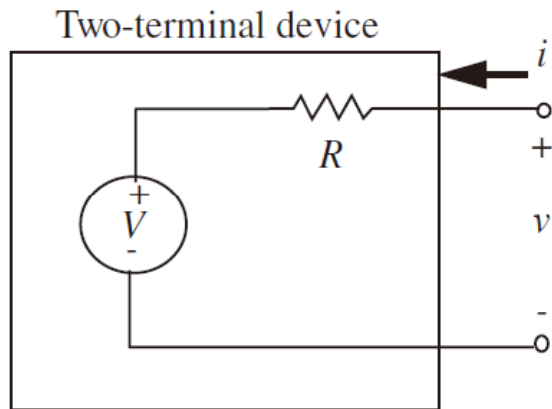

- Test circuit

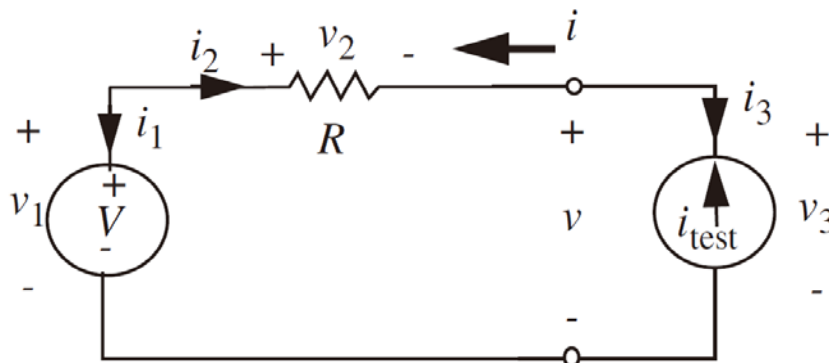

$$v = V + i_{test} R$$

$$i = \frac{v - V}{R}$$

Conclusion



- KVL and KCL

$$\sum_j v_j = 0 \text{ for Loop}$$

$$\sum_j i_j = 0 \text{ for Node}$$

- KVL, KCL method of circuit analysis
- Element combination rules