

Energy Storage Elements

Chenhsin Lien and Po-Tai Cheng

CENTER FOR ADVANCED POWER TECHNOLOGIES

Dept. of Electrical Engineering

National Tsing Hua University


Hsinchu, TAIWAN





CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN



Motivation

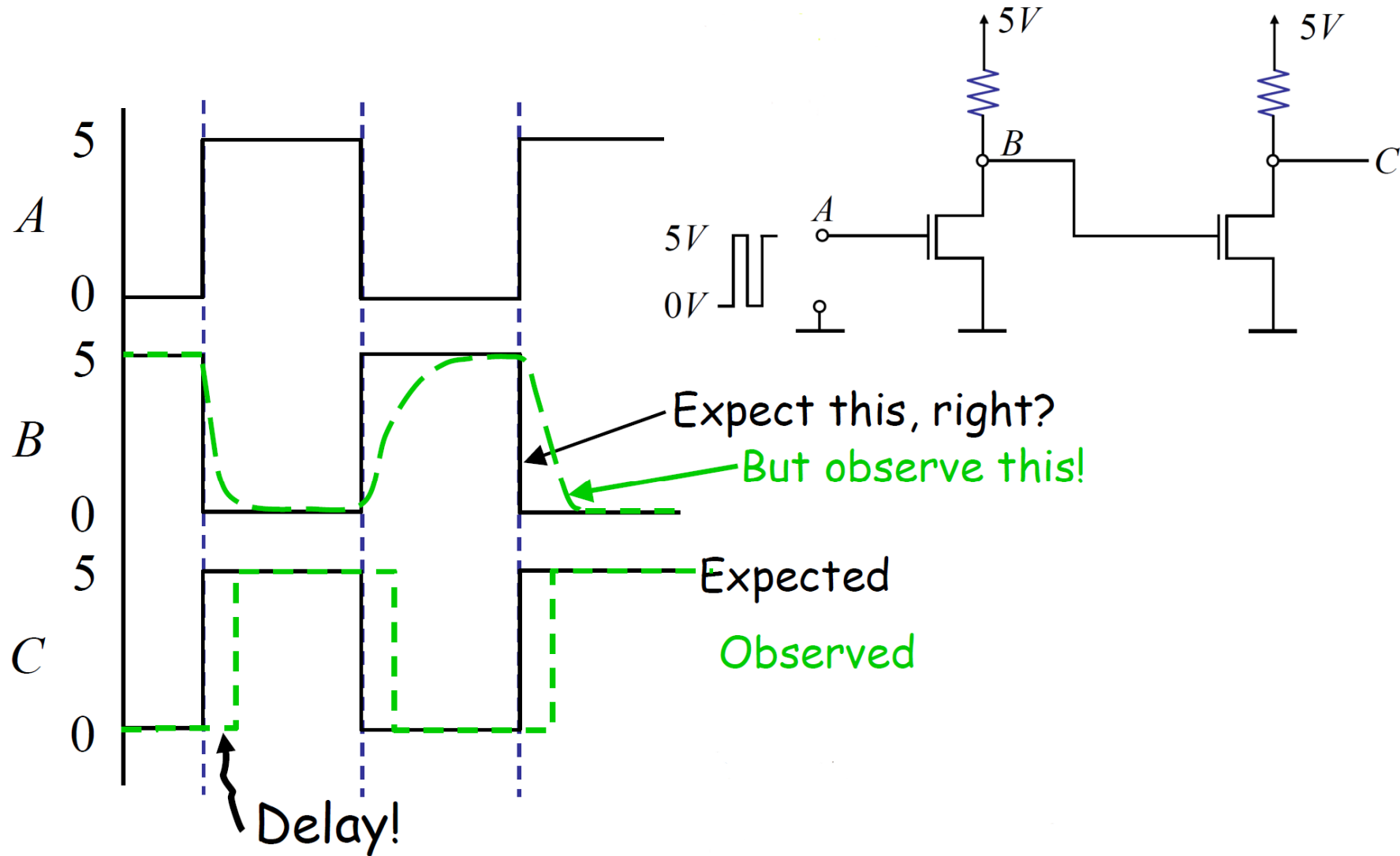


The Gate to Source Capacitor

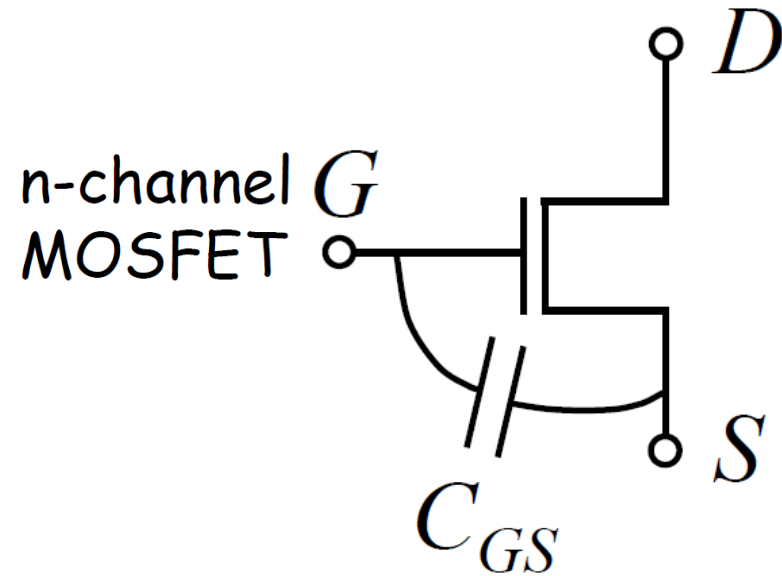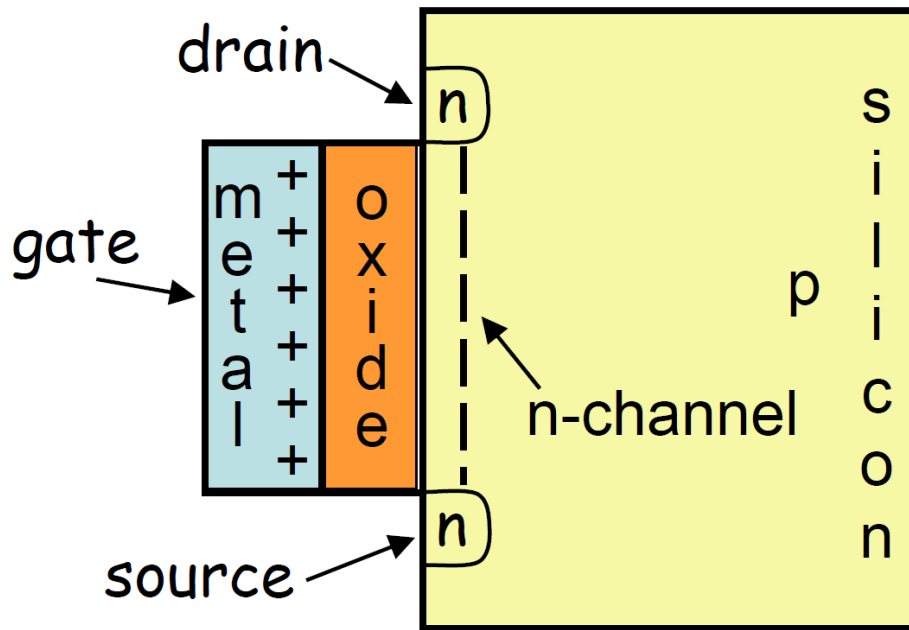

Capacitors, C

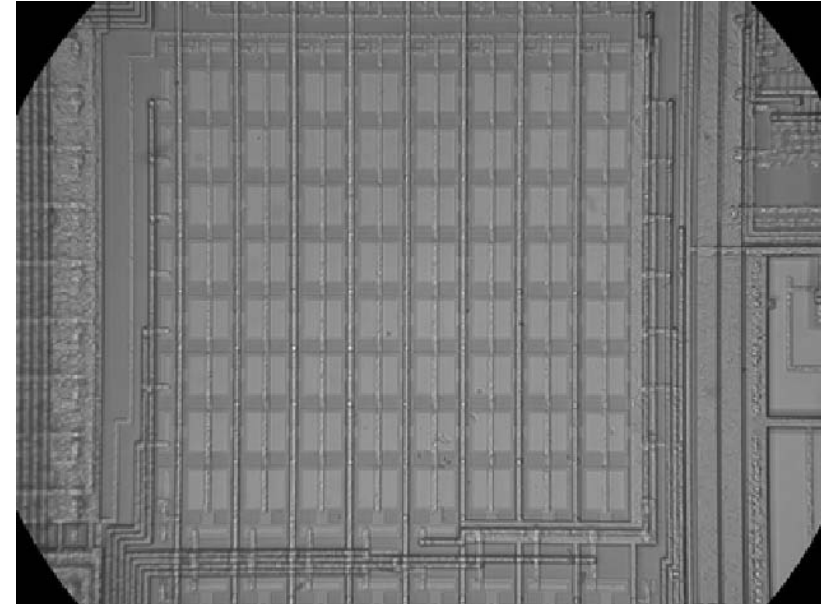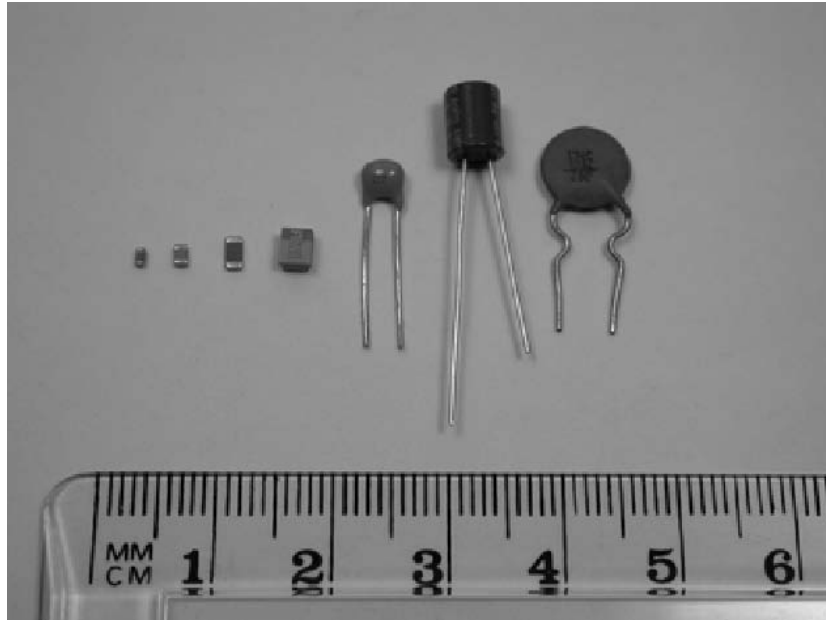

Polyester capacitor

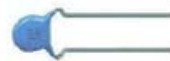

Ceramic capacitor



Electrolytic capacitor





Tantalum capacitor



AC Motor capacitors



Capacitor

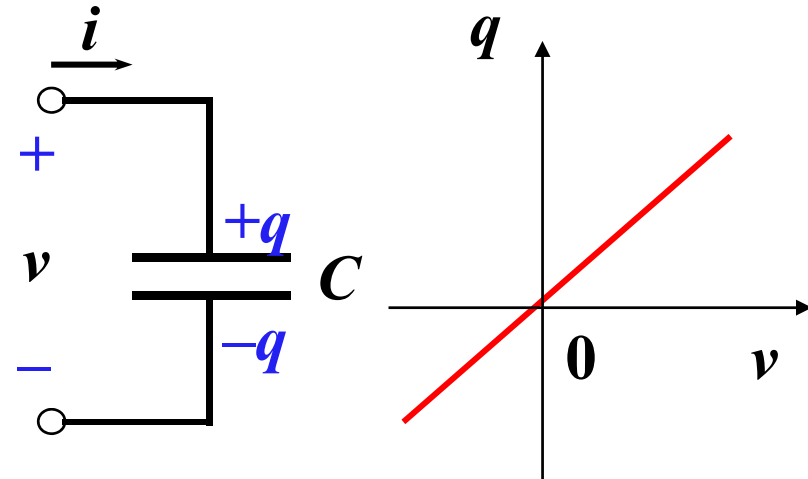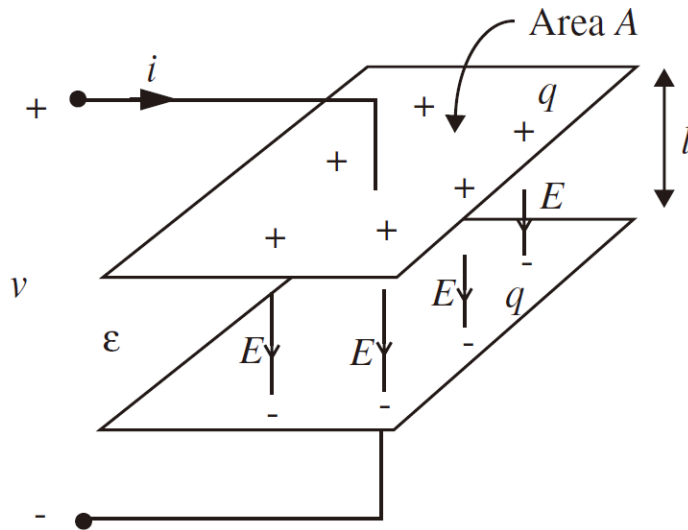

- Ideal linear capacitor

$$E = \frac{1}{\epsilon} D = \frac{1}{\epsilon} \frac{q}{A} \text{ and } v = lE \Rightarrow q = \epsilon \frac{A}{l} v \Rightarrow q = Cv$$

$$q = Cv$$

$$C = \epsilon \frac{A}{l}$$

- The unit of capacitance is Coulombs/Volt, or Farads (F). Name after Michael Faraday (1781-1867), an English physics and chemist.

Element law for a capacitor




- The capacitance is defined as

$$C = \frac{dq}{dv} \quad \text{or} \quad dq = Cdv$$

- The element law of a capacitor can be found as:

$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

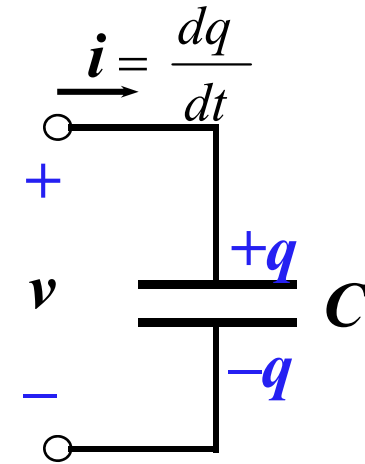

- The branch voltage of a capacitor depends on the entire past history of its branch current, which is the essence of *memory*.

$$v(t) = \frac{1}{C} \int_{-\infty}^t id\tau = \frac{1}{C} \int_{-\infty}^{t_0} id\tau + \frac{1}{C} \int_{t_0}^t id\tau$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t id\tau$$

$$q(t) = q(t_0) + \int_{t_0}^t id\tau$$

Switch and Initial Condition




- $t = 0^-$ and $t = 0^+$

- Switching at $t = 0$

$$v_C(0^-) = \lim_{\substack{t \rightarrow 0 \\ t < 0}} v_C(t) \quad v_C(0^+) = \lim_{\substack{t \rightarrow 0 \\ t > 0}} v_C(t)$$

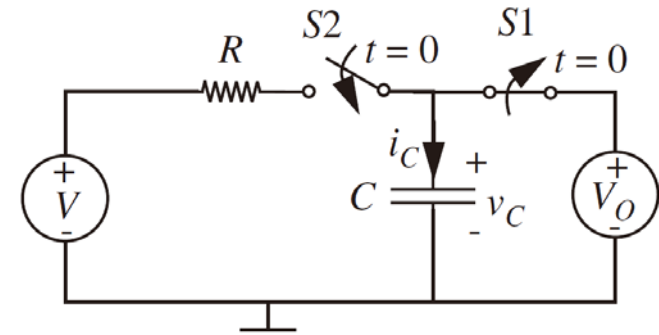- $v_C(0^+)$ is the initial condition for v_C .



$$v_C(t) = v_C(0^-) + \frac{1}{C} \int_{0^-}^t i_C(\tau) d\tau$$

$$v_C(0^+) = v_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_C(\tau) d\tau$$

- When $i_C(\tau)$ is finite,

$$v_C(0^+) = v_C(0^-)$$

$$q_C(0^+) = q_C(0^-)$$



Electric Energy Storage

- Associated with the ability to exhibit memory is the property of energy storage, which is often exploited by circuits that process energy.
- The energy is stored in the form of electric field.
- Electric energy w_E stored in a capacitor

$$P_E = iv \Rightarrow \frac{dw_E}{dt} = iv \Rightarrow \frac{dw_E}{dt} = v \frac{dq}{dt} \Rightarrow dw_E = vdq$$

$$w_E = \int_0^q vdq' = \int_0^q \frac{q'}{C} dq' = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} Cv^2$$

- Unlike a resistor, a capacitor *stores energy* rather than dissipates it.

$$w_E = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} Cv^2$$

i-v Behaviors of Capacitor



- Its current depends on the *changing rate* of voltage v .
- Steady state characteristics
 - The capacitor is an *open circuit to DC* at steady state.

$$i_{c_{dc}} = C \frac{dv_{c_{dc}}}{dt} = 0$$

- The capacitor is a *short circuit to high frequency* signals at steady state.

Assume $v_c = V \sin(\omega t)$,

$$i_c = C \frac{dv_c}{dt} = \omega CV \cos(\omega t) \quad \text{As } \omega \rightarrow \infty, i_c \rightarrow \infty, \text{ similar to a short-circuit.}$$


- ***The voltage on a capacitor does not change abruptly.*** Discontinuous change in the capacitor voltage requires an infinite current.
- For finite current, $v_C(0^+) = v_C(0^-)$

The Inverter Chain



- Apply node method:
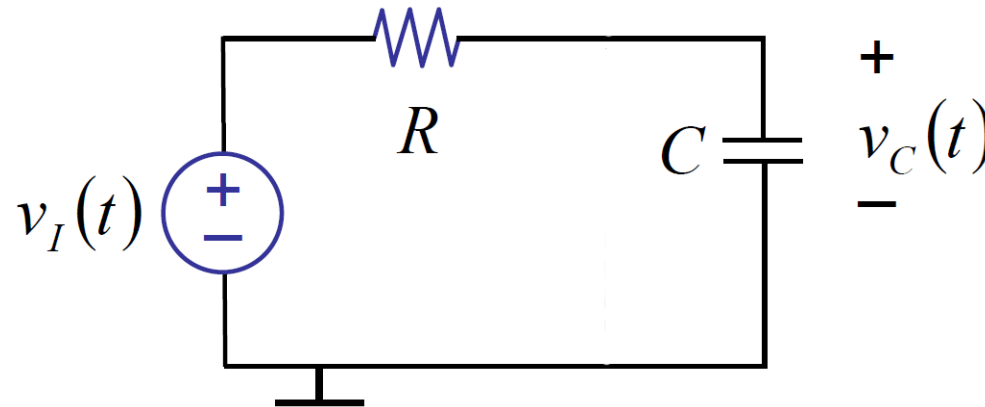
$$\frac{v_C - v_I}{R} + C \frac{dv_C}{dt} = 0$$




Given:

$$v_I(t) = V_I = 5 \text{ V for } t \geq 0$$


$v_C(0) = V_0 = 0 \text{ V}$ is the given initial state value of the capacitor.

$$RC \frac{dv_C}{dt} + v_C = V_I = 5 \text{ V The input drive switch from 0 to 5V for } t \geq 0$$
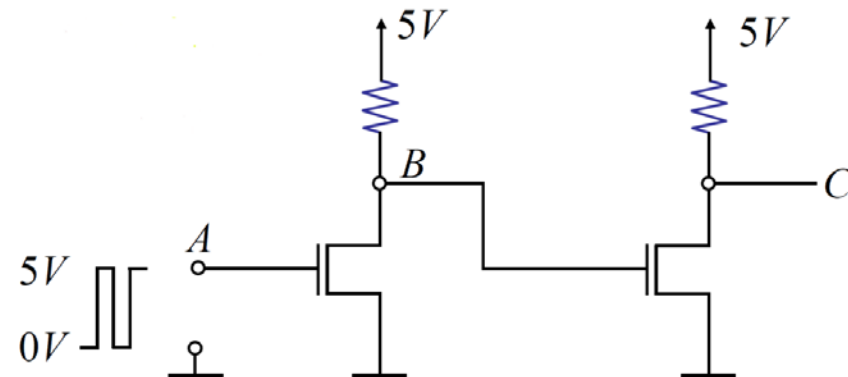
$$RC \frac{dv_C}{dt} + v_C = V_I = 5 \text{ V for } t \geq 0$$




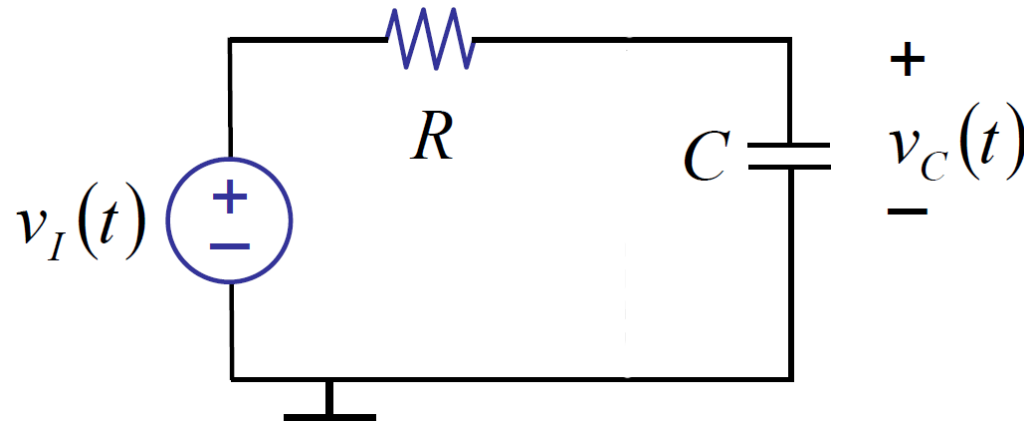Method of homogeneous and particular solutions



- Find the particular solution, v_{CP} .
- Find the homogeneous solution, v_{CH} .
- The total solution is the sum of the particular and homogeneous solutions, $v_C = v_{CP} + v_{CH}$.
- Use the initial conditions to solve for the remaining constants.

The Particular solution v_{CP}

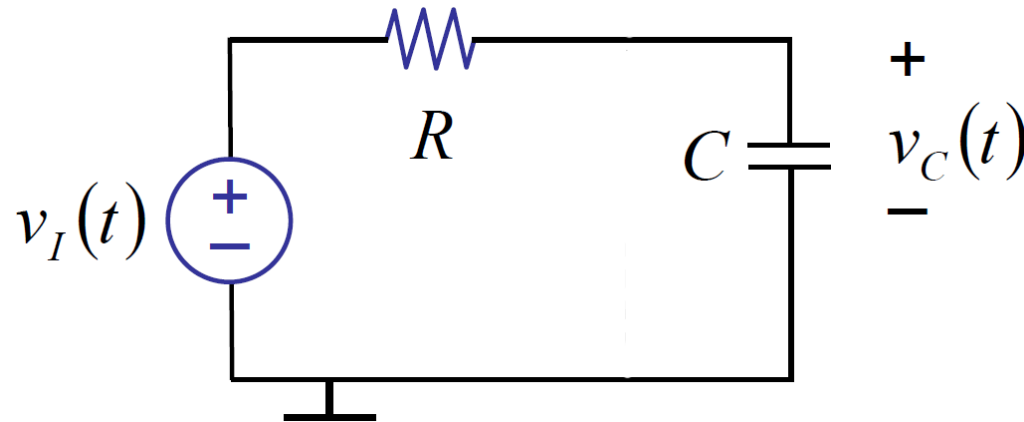

- Find the particular solution, v_{CP} .
- v_{CP} : any solution that satisfies the original equation $RC \frac{dv_{CP}}{dt} + v_{CP} = 5 \text{ V}$
- Use trial and error : Try $v_{CP} = 5 \text{ V}$,

$$RC \frac{dv_{CP}}{dt} + v_{CP} = 5 \text{ V} \Rightarrow RC \frac{d5}{dt} + 5 = 5 \text{ Worked!!!}$$

The Homogeneous Solution



- Find the homogeneous solution, v_{CH} .
- v_{CH} : solution to the homogeneous equation by setting the input drive v_I to 0.
- Assume solution is of this form: $v_{CH} = Ae^{st}$


$$RC \frac{dv_{CH}}{dt} + v_{CH} = 0$$

$$RC \frac{dAe^{st}}{dt} + Ae^{st} = 0 \Rightarrow RCsAe^{st} + Ae^{st} = 0 \Rightarrow RCs + 1 = 0$$

- Characteristic equation $RCs + 1 = 0 \Rightarrow s = -\frac{1}{RC} = -\frac{1}{\tau}$
- The homogeneous solution, v_{CH} :

$$v_{CH} = Ae^{-\frac{t}{RC}}$$

- RC is called time constant τ .

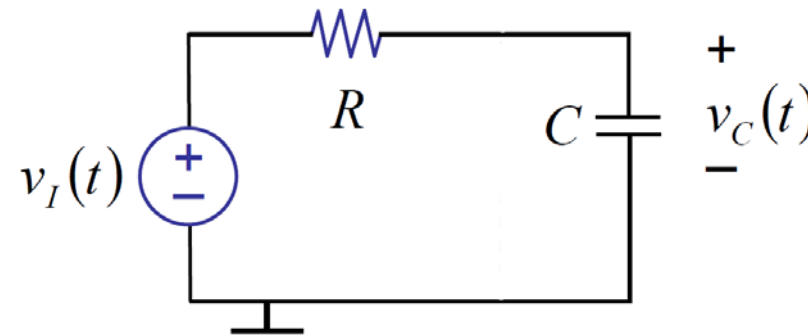

The Total solution



- The total solution is the sum of the particular and homogeneous solutions:


$$v_C = v_{CP} + v_{CH} = 5 + Ae^{-\frac{t}{RC}}$$

- Use the initial conditions:

$$v_C(0) = V_0 = 0 \text{ V}$$

to solve for the remaining constants.
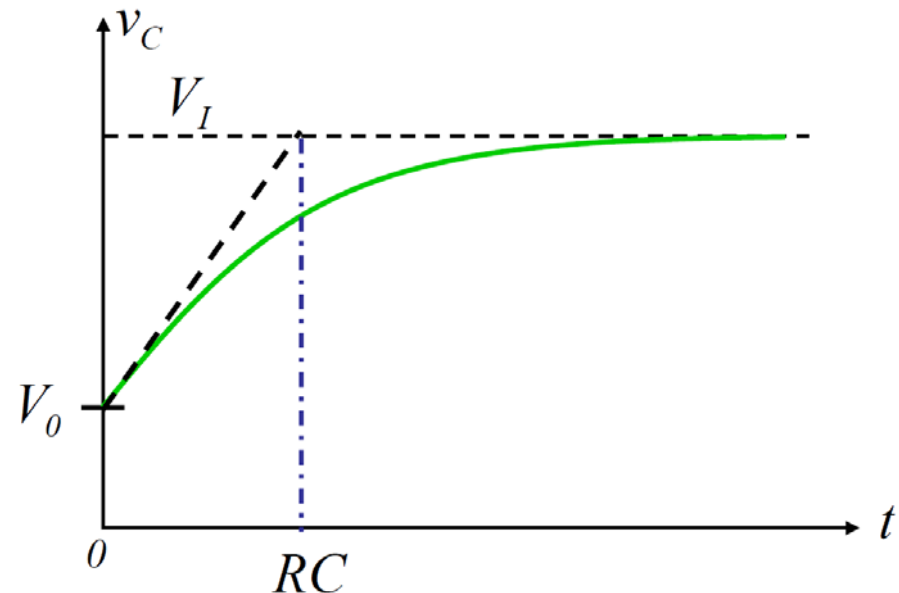
$$V_0 = 0 = V_I + Ae^{-\frac{0}{RC}} = 5 + Ae^{-\frac{0}{RC}}$$
$$\Rightarrow A = V_0 - V_I = 0 - 5 = -5 \text{ V}$$




- The total solution v_C :

$$v_C = V_I + (V_0 - V_I)e^{-\frac{t}{RC}} = 5 + (0 - 5)e^{-\frac{t}{RC}} = 5 \left(1 - e^{-\frac{t}{RC}} \right)$$

Capacitors, C




- Parallel connection

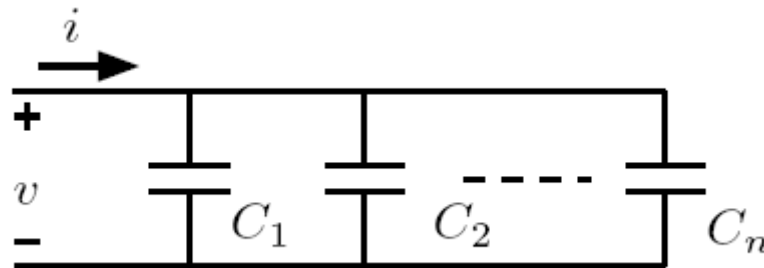

$$\begin{aligned} i &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt} \\ &= \left(\sum_{k=1}^n C_k \right) \frac{dv}{dt} \\ &\rightarrow C_{eq} = \sum_{k=1}^n C_k \end{aligned}$$

- Series connection

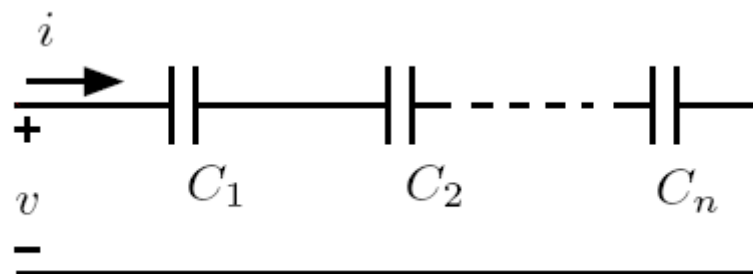

$$\begin{aligned} v &= \frac{1}{C_1} \int_0^t idt + \dots + \frac{1}{C_n} \int_0^t idt \\ &= \left(\sum_{k=1}^n \frac{1}{C_k} \right) \int_0^t idt \\ &\rightarrow \frac{1}{C_{eq}} = \sum_{k=1}^n \frac{1}{C_k} \end{aligned}$$

Inductor, L



CAPT
Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN



Toroid inductor



Wound inductor



Transformer






AC line inductor



AC shunt inductor

Inductor

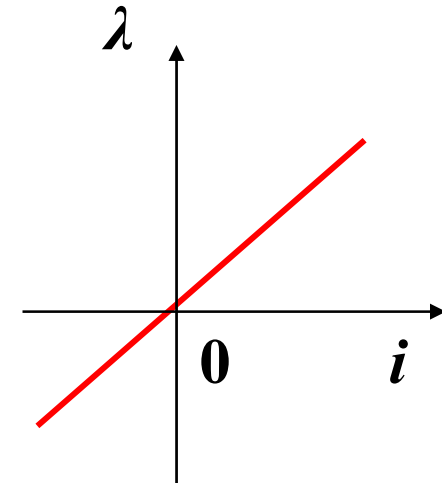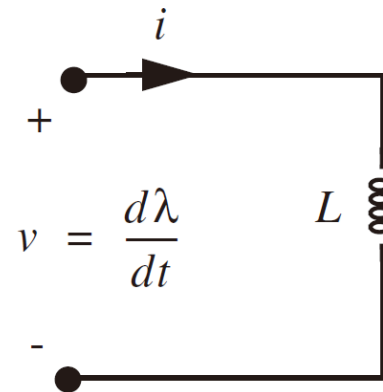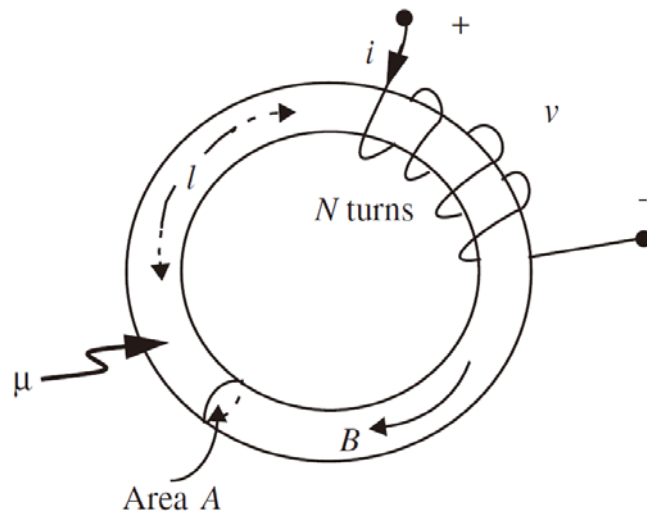

- Total Flux linkage λ

$$\lambda = N\Phi = NAB = NA\mu\frac{Ni}{l} = \mu\frac{N^2A}{l}i$$
$$L = \mu\frac{N^2A}{l}$$

$$\lambda = Li$$

- L has the units of Webers/Ampere, or Henrys (H). Name after Joseph Henry (1797-1878), an American physics.

Element law for an inductor



CAPT

Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- The inductance is defined as

$$L = \frac{d\lambda}{di} \quad \text{or} \quad d\lambda = L di$$

- The element law of an inductor can be found as:


$$v = \frac{d\lambda}{dt} = L \frac{di}{dt}$$

- The branch current of an inductor depends on the entire past history of its branch voltage, which is the essence of *memory*.

$$i(t) = \frac{1}{L} \int_{-\infty}^t v d\tau = \frac{1}{L} \int_{-\infty}^{t_0} v d\tau + \frac{1}{L} \int_{t_0}^t v d\tau$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v d\tau$$
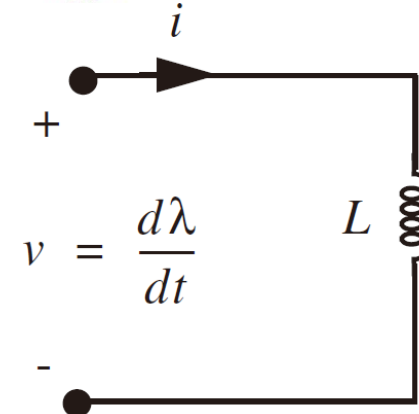
$$\lambda(t) = \lambda(t_0) + \int_{t_0}^t v d\tau$$



Switch and Initial Condition




- $t = 0^-$ and $t = 0^+$

- Switching at $t = 0$

$$i_L(0^-) = \lim_{\substack{t \rightarrow 0 \\ t < 0}} i_L(t) \quad i_L(0^+) = \lim_{\substack{t \rightarrow 0 \\ t > 0}} i_L(t)$$

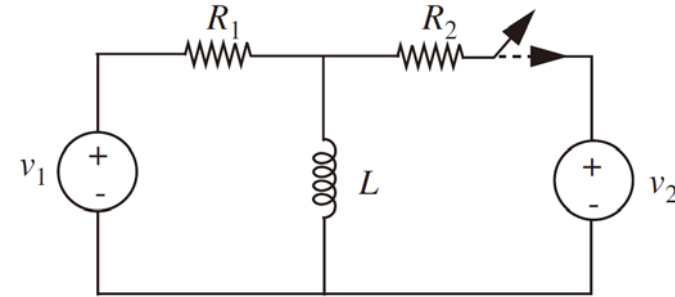- $v_C(0^+)$ is the initial condition for v_C .



$$i_L(t) = i_L(0^-) + \frac{1}{C} \int_{0^-}^t v_L(\tau) d\tau$$

$$i_L(0^+) = i_L(0^-) + \frac{1}{C} \int_{0^-}^{0^+} v_L(\tau) d\tau$$

- When $i_C(\tau)$ is finite,

$$i_L(0^+) = i_L(0^-)$$

$$\lambda_L(0^+) = \lambda_L(0^-)$$



Magnetic Energy Storage

- Associated with the ability to exhibit memory is the property of energy storage, which is often exploited by circuits that process energy.
- The energy is stored in the form of magnetic field.
- Magnetic energy w_M stored in an inductor

$$P_M = iv \Rightarrow \frac{dw_M}{dt} = iv \Rightarrow \frac{dw_M}{dt} = i \frac{d\lambda}{dt} \Rightarrow dw_M = id\lambda$$

$$w_M = \int_0^\lambda id\lambda' = \int_0^q \frac{\lambda'}{L} dq' = \frac{1}{2} \frac{\lambda^2}{L} = \frac{1}{2} Li^2$$

- Unlike a resistor, an *inductor stores energy* rather than dissipates it.

$$w_M = \frac{1}{2} \frac{\lambda^2}{L} = \frac{1}{2} L i^2$$

i-v Behaviors of Inductor



- Its voltage depends on the *changing rate* of current i .
- Steady state characteristics
 - The inductor is ***a short circuit to DC*** at steady state.

$$v_{L_{dc}} = L \frac{di_{L_{dc}}}{dt} = 0$$

- The inductor is an ***open circuit to high frequency*** signals at steady state.

Assume $i_L = I \sin(\omega t)$,

$$v_L = L \frac{di_L}{dt} = \omega LI \cos(\omega t)$$


As $\omega \rightarrow \infty, v_L \rightarrow \infty$ similar
to an open-circuit.

- ***The current through an inductor does not change abruptly.*** A discontinuous change of the inductor current requires an infinite voltage.
- For finite voltage, $i_L(0^+) = i_L(0^-)$

Inductors, L




- Parallel connection

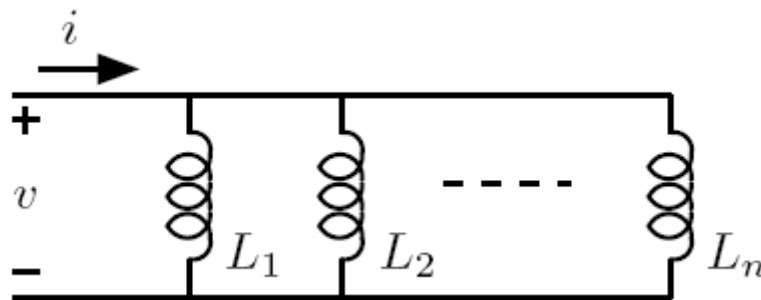

$$\begin{aligned} i &= \frac{1}{L_1} \int_0^t v dt + \dots + \frac{1}{L_n} \int_0^t v dt \\ &= \left(\sum_{k=1}^n \frac{1}{L_k} \right) \int_0^t v dt \\ &\rightarrow \frac{1}{L_{eq}} = \sum_{k=1}^n \frac{1}{L_k} \end{aligned}$$

- Series connection

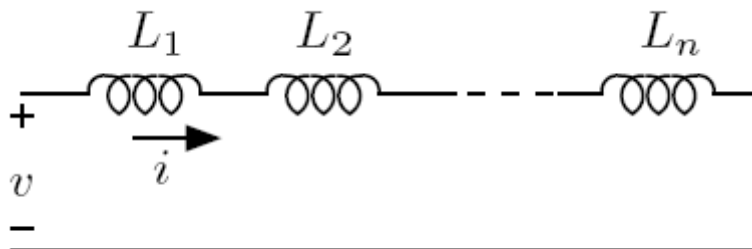


$$\begin{aligned} v &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt} \\ &= \left(\sum_{k=1}^n L_k \right) \frac{di}{dt} \\ &\rightarrow L_{eq} = \sum_{k=1}^n L_k \end{aligned}$$


Excitations



- Step function;

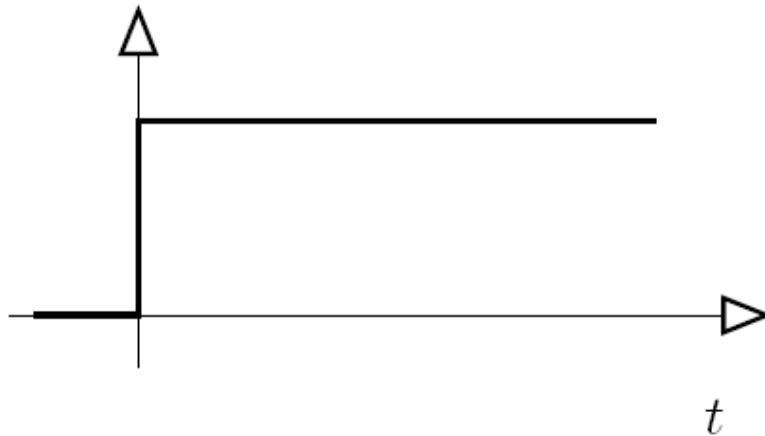
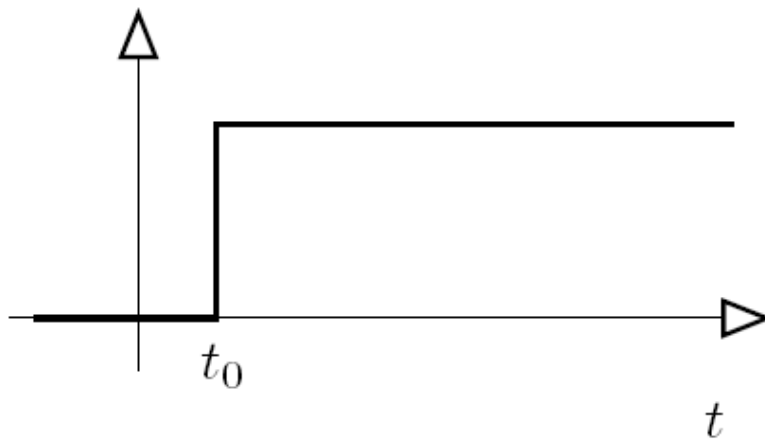
$$u(t) = \begin{cases} 0 & \text{if } t < 0 \\ 1 & \text{if } t \geq 0 \end{cases}$$




$$u(t - t_0) = \begin{cases} 0 & \text{if } t < t_0 \\ 1 & \text{if } t \geq t_0 \end{cases}$$


Excitations



- Pulse

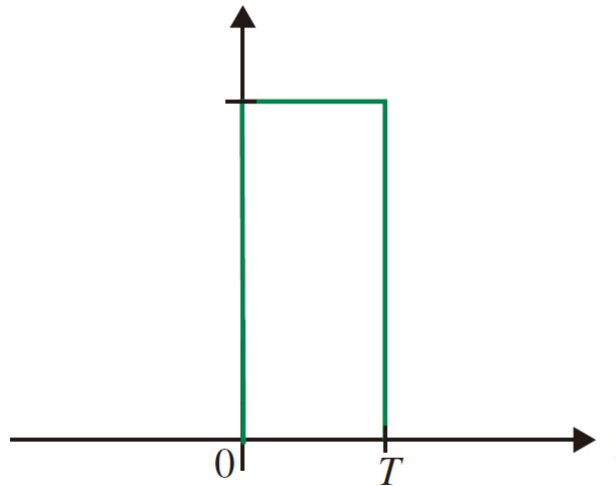

- Ramp function

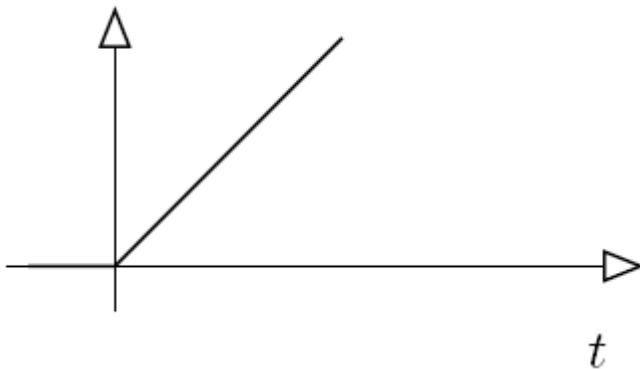


$$r(t) = \int u(t)dt = \begin{cases} 0 & \text{if } t < 0 \\ t & \text{if } t \geq 0 \end{cases}$$

Excitations



- Impulse;


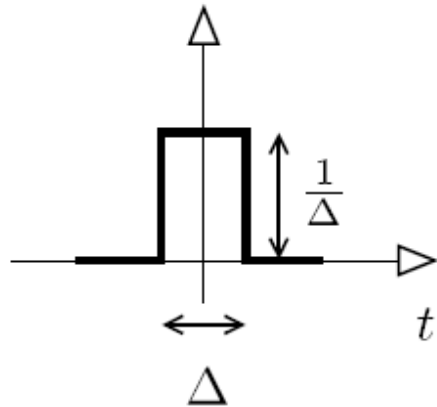


$$\delta(t) = \frac{du(t)}{dt} = \begin{cases} 0 & t > \frac{\Delta}{2}, t < -\frac{\Delta}{2}, \Delta \rightarrow 0. \\ \frac{1}{\Delta} & -\frac{\Delta}{2} < t < \frac{\Delta}{2}, \Delta \rightarrow 0. \end{cases}$$

$$\int_{-\frac{\Delta}{2}}^{\frac{\Delta}{2}} \delta(t) dt = 1$$


- Since $i_C(0) = \infty$

$$v_C(0^+) - v_C(0^-) = V_0$$

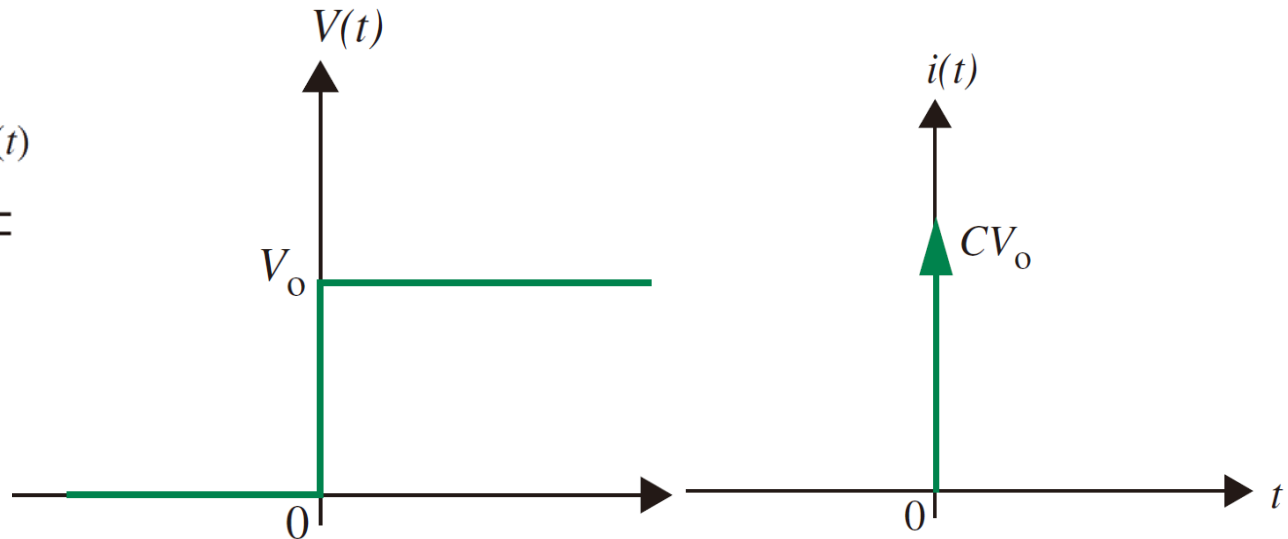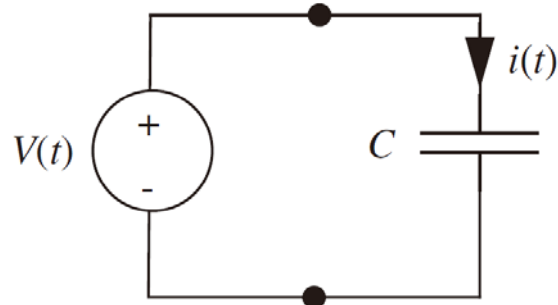



Impulse

- Inductor

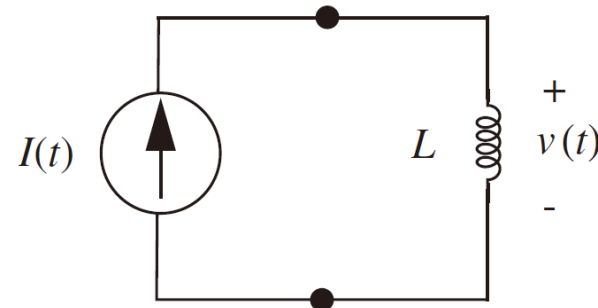


- Since $v_L(0) = \infty$

$$i_L(0^+) - i_L(0^-) = I_0$$

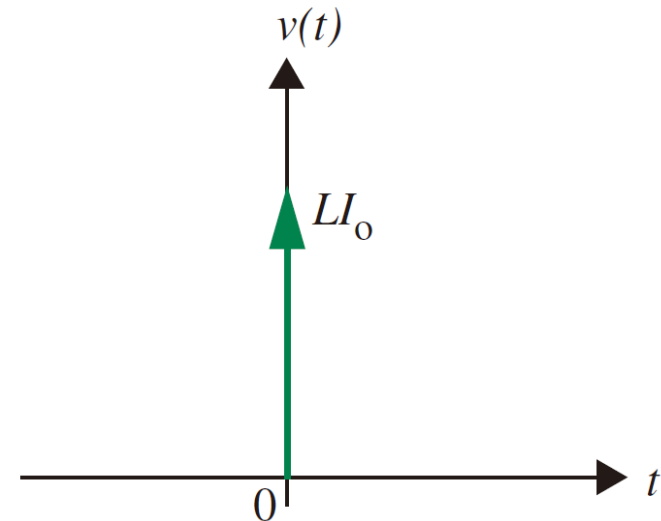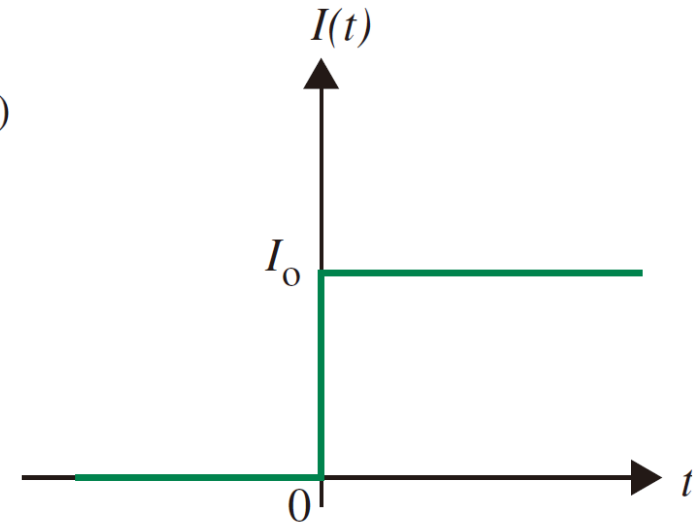


Boost converter

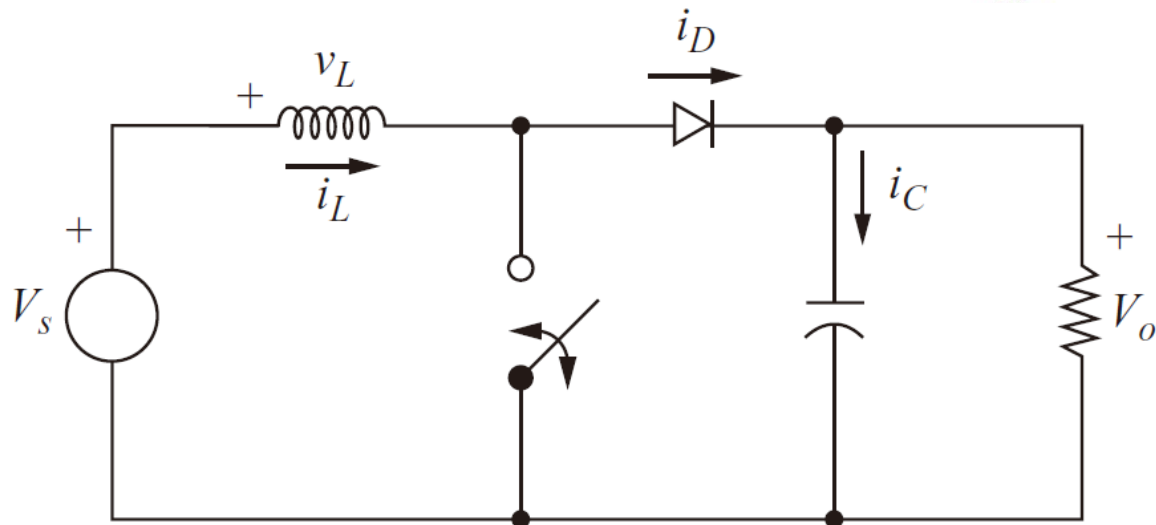


$$v_L = V_S - V_o$$


Switch Open

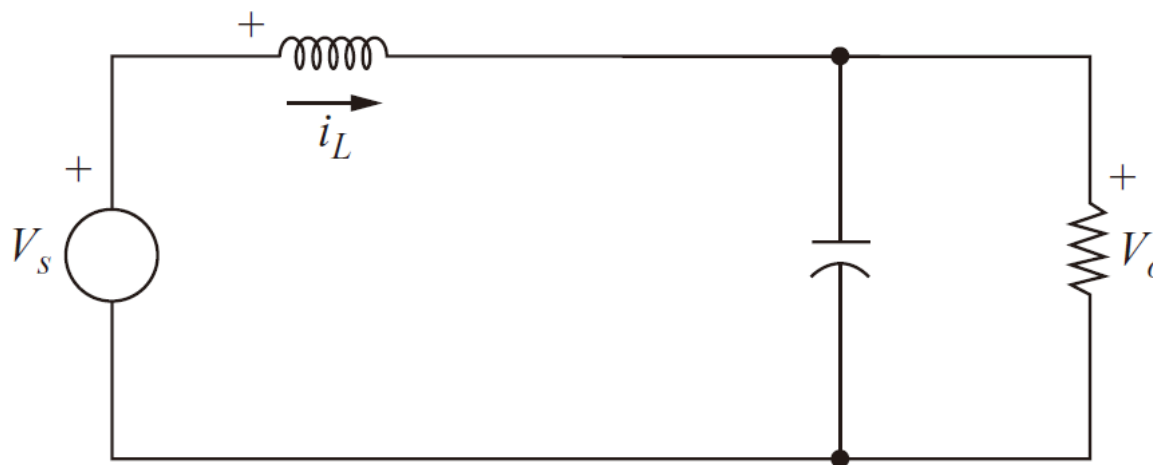

Boost converter

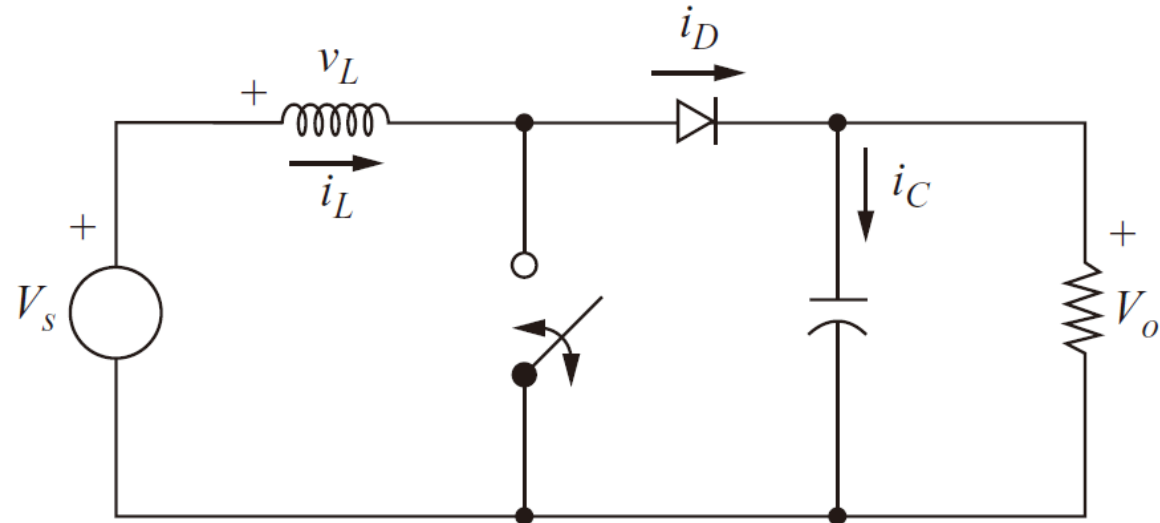

Switch Closed

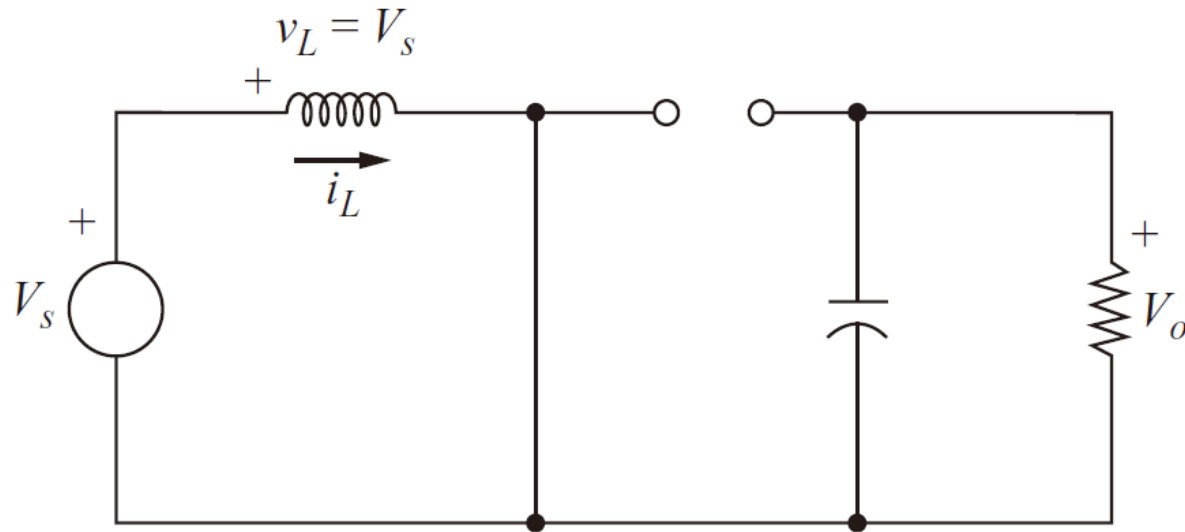


Boost converter



CAPT
Center for Advanced Power Technologies
National Tsing Hua University, TAIWAN

- The analysis assumes the following:
- The switching period is T , and the switch is closed for time DT and open for $(1 - D)T$.
- The inductor current is continuous (always positive).
- The capacitor is very large, and the output voltage is held constant at voltage V_o .
- Steady-state conditions exist.
- The components are ideal.


When Switch is Open

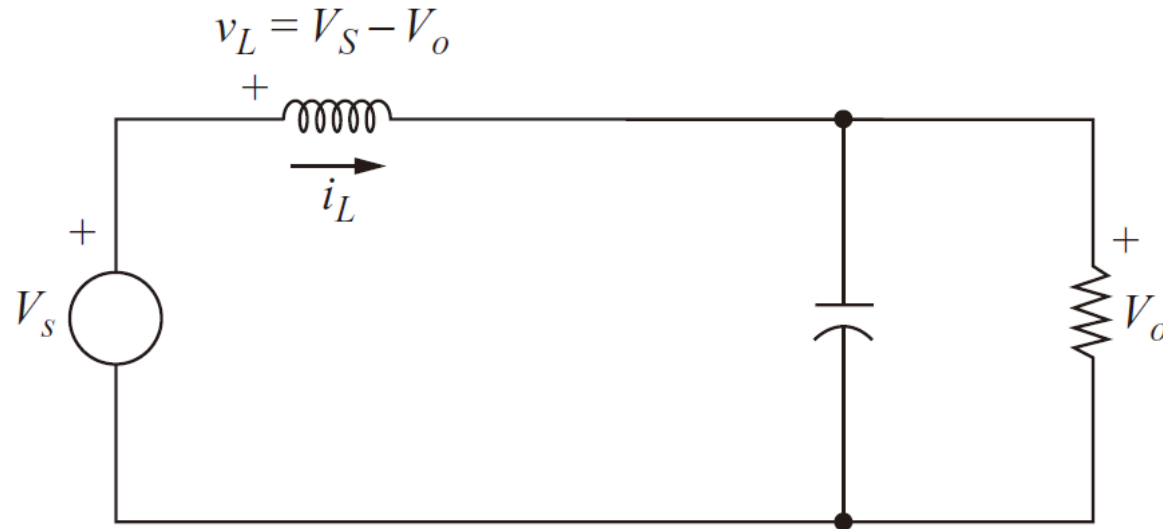

$$v_L = V_s - V_o = L \frac{di_L}{dt} \quad \frac{di_L}{dt} = \frac{V_s - V_o}{L} \quad \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{V_s - V_o}{L}$$

$$(\Delta i_L)_{open} = \frac{(V_s - V_o)(1-D)T}{L}$$

When Switch is Closed

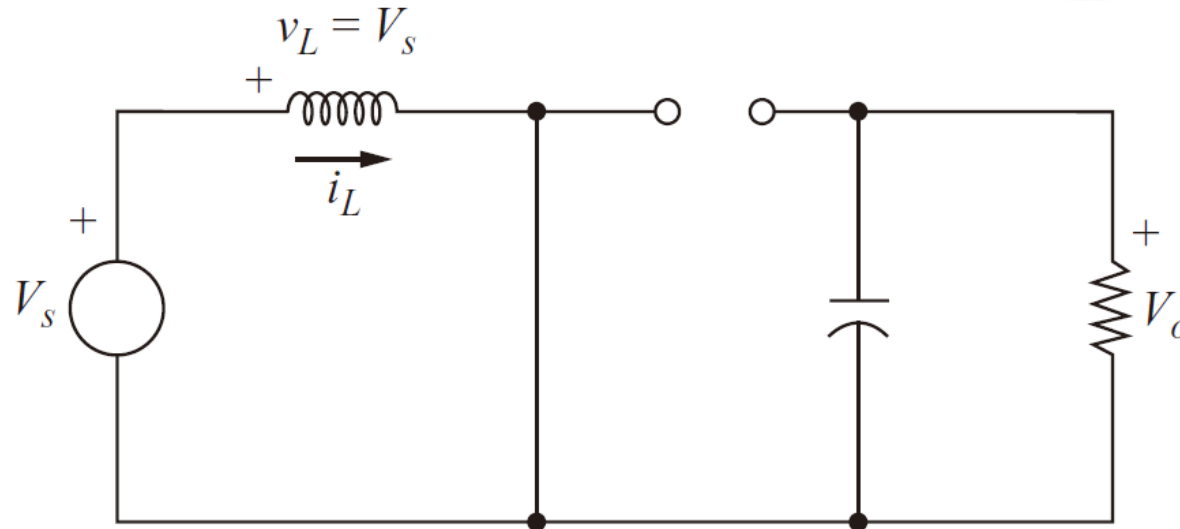



$$v_L = V_s = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{V_s}{L}$$

$$\frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_s}{L}$$

$$(\Delta i_L)_{closed} = \frac{V_s DT}{L}$$

Boost converter

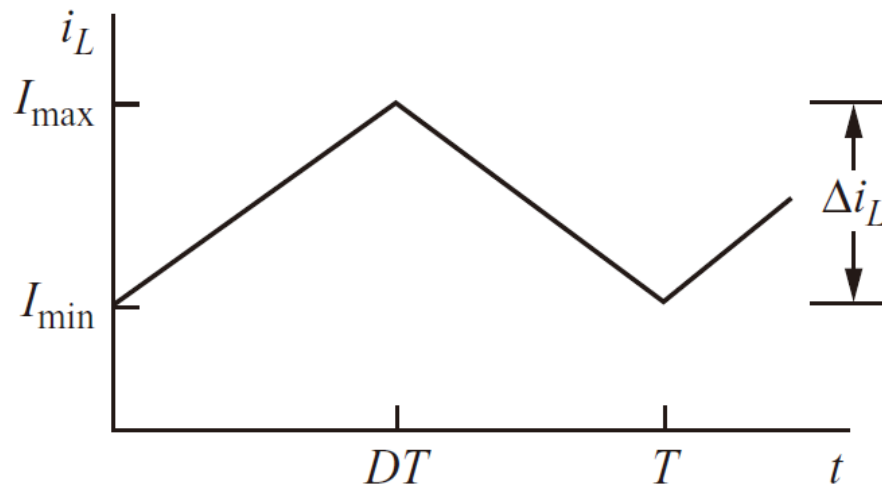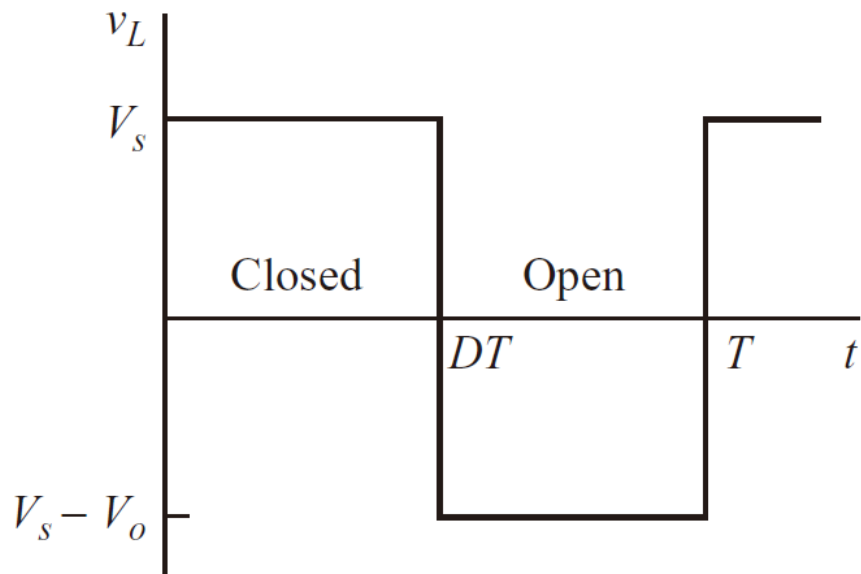

$$(\Delta i_L)_{open} + (\Delta i_L)_{open} = 0 \quad \frac{(V_s - V_o)(1-D)T}{L} + \frac{V_s DT}{L} = 0$$

$$V_o = \frac{V_s}{1-D}$$

Summary



	R	C	L
$v - i$	$v_R = i_R R$	$v_C = \frac{1}{C} \int_{t_0}^t i_C dt$	$v_L = L \frac{di_L}{dt}$
$i - v$	$i = \frac{v_R}{R}$	$i_C = C \frac{dv_C}{dt}$	$i_L = \frac{1}{L} \int_{t_0}^t v_L dt$
Power, Energy	$p_R = i_R^2 R = \frac{v_R^2}{R}$	$W_C = \frac{1}{2} C v_C^2$	$W_L = \frac{1}{2} L i_L^2$
Series	$R_{eq} = \sum R_k$	$\frac{1}{C_{eq}} = \sum \frac{1}{C_k}$	$L_{eq} = \sum L_k$
Parallel	$\frac{1}{R_{eq}} = \frac{1}{R_k}$	$C_{eq} = \sum C_k$	$\frac{1}{L_{eq}} = \frac{1}{L_k}$
DC steady state	(same)	open-circuit	short-circuit
Continuity	(no restriction)	v_C	i_L

Fundamental Circuit Variables and Elements



- **4 fundamental circuit variables:** current, i ; voltage, v ; charge, q ; magnetic flux linkage, λ (φ instead λ of is adopted in this slide).
- **6 mathematical relations** (or Elements) might be construed to connect pairs of these 4 fundamental circuit variables.

