

電路學(EE2210)第一次期中考

2013年10月28日

時間：2 小時

Close Book


學號： _____

姓名： _____

- There are 11 pages in this midterm exam, including this cover page. Please check that you have them all.
- Please write your 學號 姓名 in the space provided above.
- **IMPORTANT:** The problems in this exam vary in difficulty; moreover, questions of different levels of difficulty are distributed throughout the exam. If you find yourself spending a long time on a question, consider moving on to later problems in the exam, and then working on the challenging problems after you have finished all of the easier ones.
- Do your work and enter your answer for each question within the boundaries of that question. You may do your work on the back of the preceding page.
- Remember to include the sign and units for all numerical answers.
- This is a closed-book exam, but you may use a calculator.
- You have 2 hours to complete this exam.
- Good luck!


1.	2.	3.	4.	5.
6.	7.	8.	9.	10.
11.	12.			
<i>Total Grade</i>				

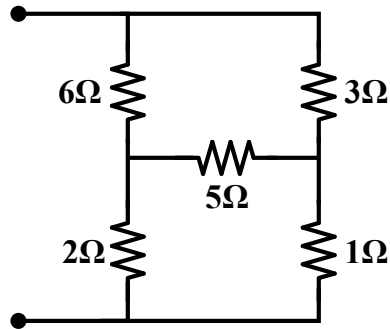1. Find the equivalent resistance R_{eq} between the indicated terminals (all resistances in ohms) in following Figure. (5%)



$R_{eq} =$ _____.

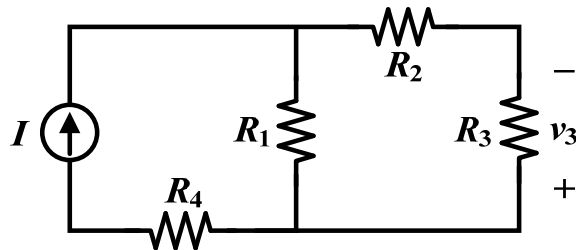2. Determine explicitly the voltage v_3 in the following circuit in terms of $R_1, R_2, R_3, R_4,$ and $I.$ (5%)




$v_3 =$ _____.


3. Measurements made on terminals BB' of a linear circuit as shown, which is known to be made up only of independent voltage sources and current sources, and resistors, yield the current-voltage characteristics as shown.

(a) Find the Thévenin equivalent of the circuit. (5%)

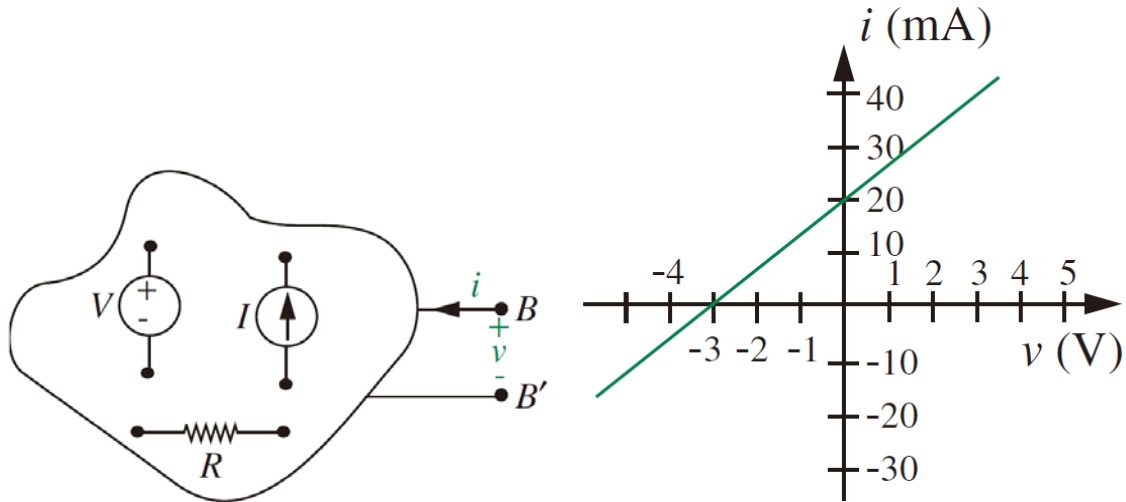(b) Over what quadrants, if any, of the i - v characteristics does this circuit absorb power? (5%)



(a) Thévenin equivalent circuit:

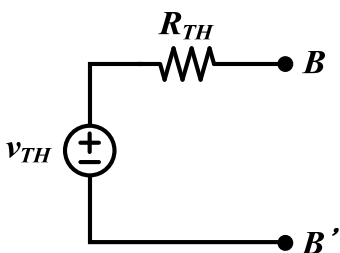


$v_{TH} =$ _____, $R_{TH} =$ _____.

(b) Please circle the answer.

Quadrants (You can choose more than one): 1st, 2nd, 3rd, 4th, none.

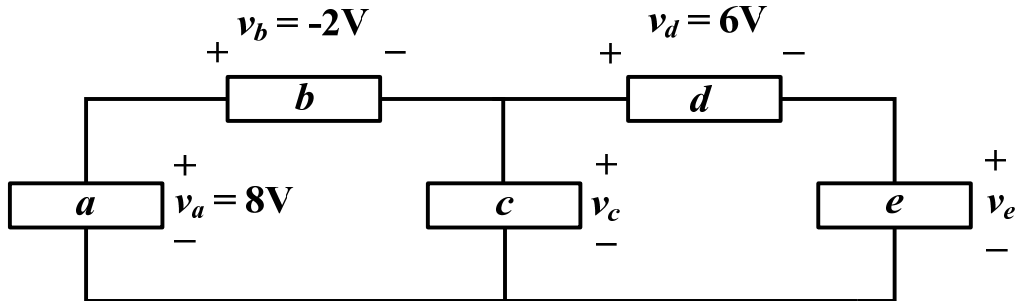4. For the circuit as shown below, there are five elements which observe the *Associated Variables Convention*. Among the five elements, the voltages for three elements are given on the figure. The current for element b is $i_b = 2\text{A}$ and for element d is $i_d = 3\text{A}$. By using the KVL and KCL, please find (i) the current of element a , (ii) the voltage, the current and the power of element c , (iii) the voltage of element e . (10%)




(i) $i_a =$ _____.

(ii) $v_c =$ _____, $i_c =$ _____, $p_c =$ _____.

(iii) $v_e =$ _____.

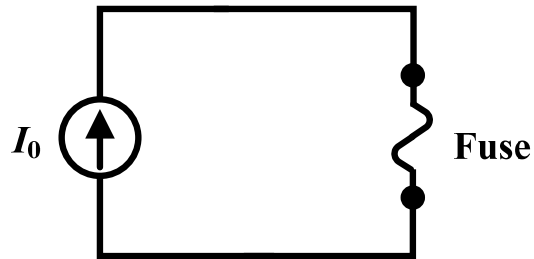5. A fuse is a wire with a positive temperature coefficient of resistance (in other words, its resistance increases with temperature). When a current is passed through the fuse, power is dissipated in the fuse, which raises its temperature.



Use the following data to determine the current I_{max} at which the fuse will blow (i.e., its temperature goes up without limit). (10%)

Fuse Resistance:

$$R = 1 + aT \text{ } (\Omega)$$

$$a = 0.001 \text{ } (\Omega/^\circ\text{C})$$

$T = \text{Temperature rise above ambient}$

Temperature rise:


$$T = \beta P$$

$$\beta = 1/0.225 \text{ } (^\circ\text{C}/\text{W})$$

$P = \text{power dissipated in fuse}$


$I_{max} = \underline{\hspace{10em}}$

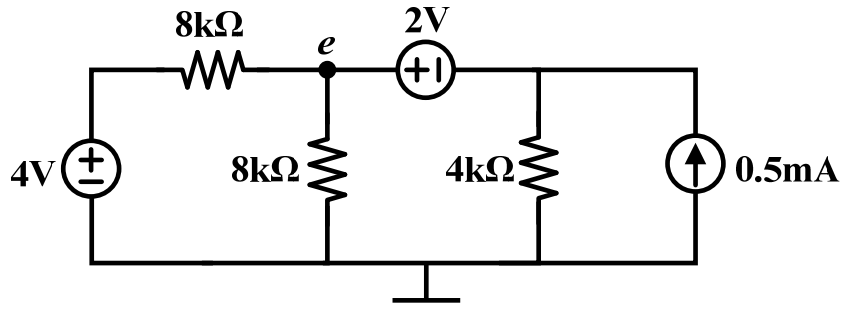6. Find the node potential e in the following circuit. (5%)




$e =$ _____.

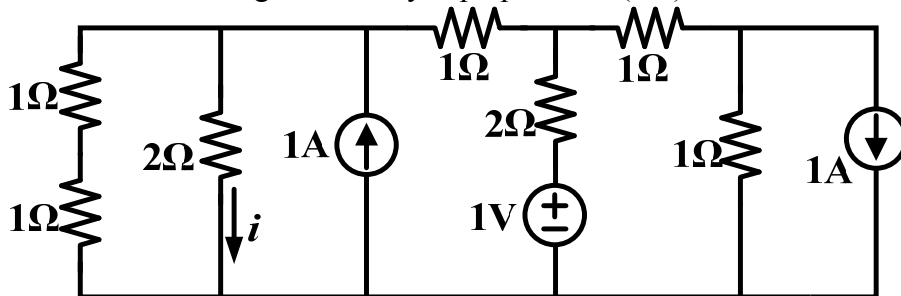7. Find the current i of the following network by superposition. (5%)




$i =$ _____.

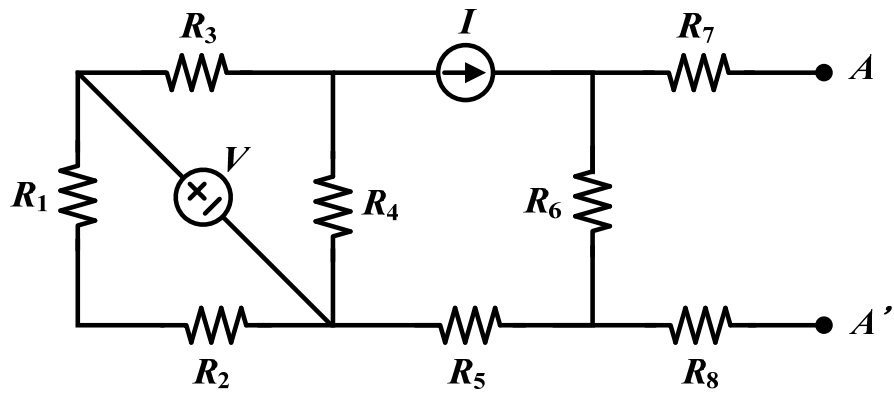8. Find the Thévenin equivalent of the circuit for the terminals marked AA' . (10%)




Thévenin equivalent circuit:

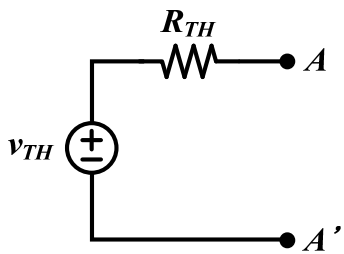

$v_{TH} =$ _____, $R_{TH} =$ _____.

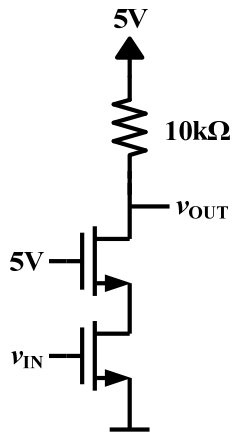
9. Draw the voltage transfer characteristics for the NAND gate circuit shown. Can this gate be operated in a digital system characterized by a static discipline with the voltage thresholds below? (10%)



For both MOSFET: $V_T = 2.1 \text{ V}$
 $R_{on} = 1 \text{ k}\Omega$

Static Discipline: $V_{OL} = 1 \text{ V}$ $V_{OH} = 4 \text{ V}$
 $V_{IL} = 2 \text{ V}$ $V_{IH} = 3 \text{ V}$


Voltage transfer characteristic (VTC):

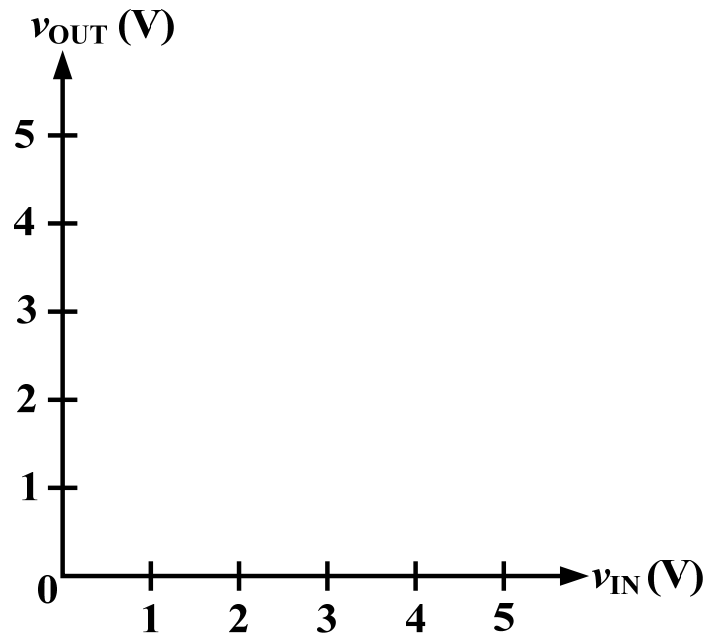


Can this gate be operated in a digital system characterized by the a static discipline? Explain.

Answer: _____.

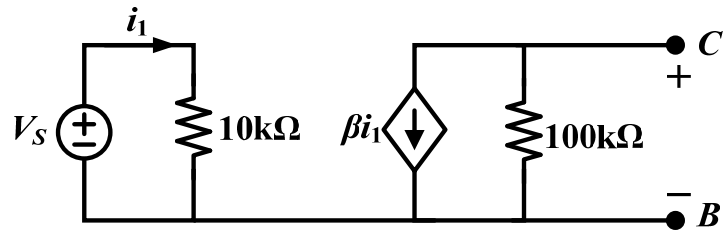
10. (a) Find the Thévenin equivalent for the network at the terminals CB . The current source is a controlled source. (8%)



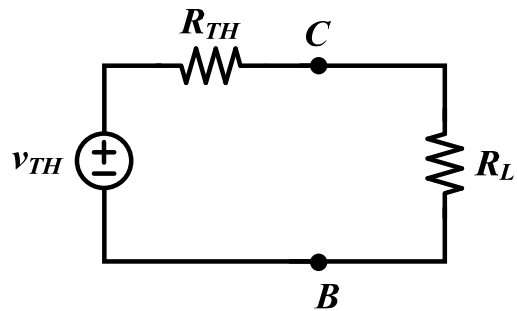(b) Now suppose you connect a load resistor across the output of your equivalent circuit as shown. Find the value of R_L which will provide the maximum power transfer to the load. (2%)




(a) Thévenin equivalent circuit:

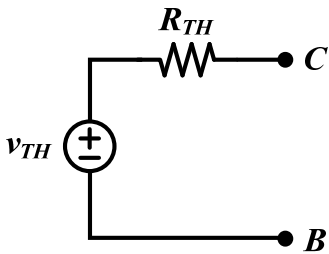

$v_{TH} =$ _____, $R_{TH} =$ _____.

(b) $R_L =$ _____.

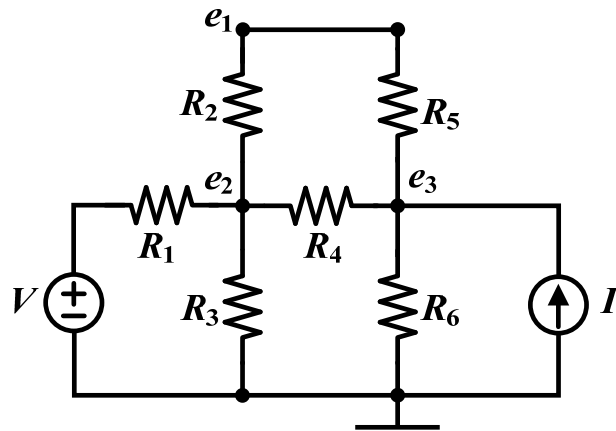11. The network shown below has three nodes with unknown node voltages e_1 , e_2 and e_3 . Use conductance instead of resistance to write the node equations. Simplify the equations by collecting terms and arranging them in the “standard” form for n linear equations in n unknowns. Express these n linear equations in matrix form as shown below. (Do not solve the equations.) (15%)




Matrix Form:
$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} S_1 \\ S_2 \\ S_3 \end{bmatrix}$$

$G_{11} = \underline{\hspace{2cm}}, G_{12} = \underline{\hspace{2cm}}, G_{13} = \underline{\hspace{2cm}}, S_1 = \underline{\hspace{2cm}},$

$G_{21} = \underline{\hspace{2cm}}, G_{22} = \underline{\hspace{2cm}}, G_{23} = \underline{\hspace{2cm}}, S_2 = \underline{\hspace{2cm}},$

$G_{31} = \underline{\hspace{2cm}}, G_{32} = \underline{\hspace{2cm}}, G_{33} = \underline{\hspace{2cm}}, S_3 = \underline{\hspace{2cm}},$

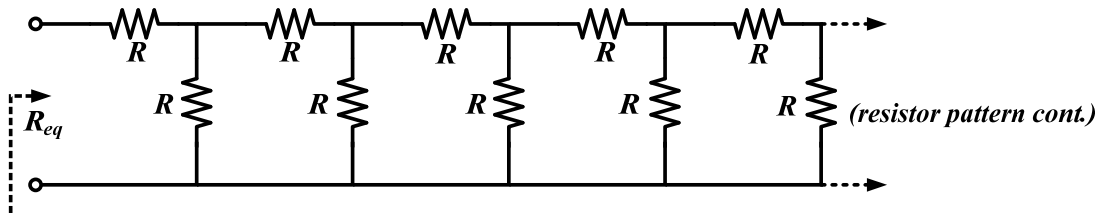12. Find the equivalent resistance R_{eq} between the indicated terminals. (5%)



$R_{eq} =$ _____.