

電路學(10320EE221000)第一次期中考

2015年4月22日

時間：2 小時

Close Book

學號： _____


姓名： _____

- There are 9 pages in this midterm exam, including this cover page. Please check that you have them all.
- Please write your 學號 姓名 in the space provided above.
- **IMPORTANT:** The problems in this exam vary in difficulty; moreover, questions of different levels of difficulty are distributed throughout the exam. If you find yourself spending a long time on a question, consider moving on to later problems in the exam, and then working on the challenging problems after you have finished all of the easier ones.
- Do your work and enter your answer for each question within the boundaries of that question. You may do your work on the back of the preceding page. Give a brief explanation if you are asked to explain.
- Remember to include the sign and units for all numerical answers.
- This is a closed-book exam, but you may use a calculator.
- You have 2 hours to complete this exam.
- Good luck!

Table of grades:


1.	2.	3.	4.	5.
6.	7.	8.	9.	10.
11.	Total Grade:			

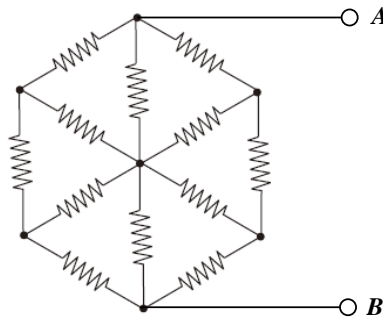1. Find the voltage drop between nodes A and B (V_{AB}) in following figure. Assume that all of the resistors have a value of $1\text{k}\Omega$, and that 1mA current flows into node A and out of node B . (6%)




$V_{AB} =$ _____.

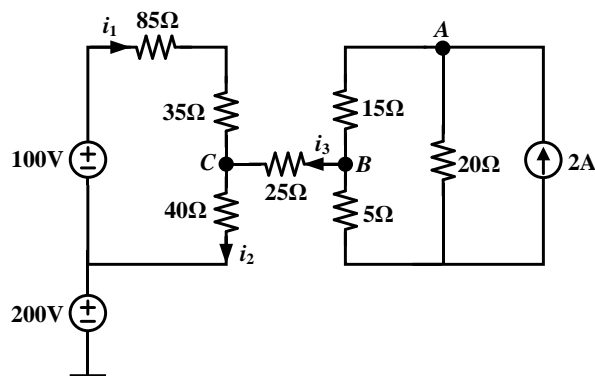2. Find the voltage at node C with respect to the ground node. (7%)



$V_C =$ _____.

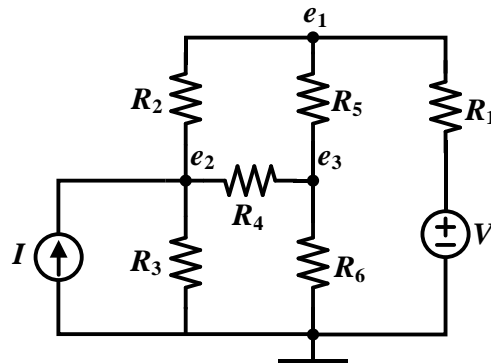3. The network shown below has three nodes with unknown node voltages e_1 , e_2 and e_3 . Use conductance instead of resistance to write the node equations. Simplify the equations by collecting terms and arranging them in the “standard” form for n linear equations in n unknowns. Express these n linear equations in matrix form as shown below. (Do not solve the equations.) (12%)



Matrix Form:
$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} S_1 \\ S_2 \\ S_3 \end{bmatrix}$$

$G_{11} =$ _____, $G_{12} =$ _____, $G_{13} =$ _____,


$G_{21} =$ _____, $G_{22} =$ _____, $G_{23} =$ _____,

$G_{31} =$ _____, $G_{32} =$ _____, $G_{33} =$ _____,

$S_1 =$ _____, $S_2 =$ _____, $S_3 =$ _____.

4. For the circuit as shown below, there are five elements which observe the *Associated Variables Convention*. Among the five elements, the voltages for three elements are given on the figure. The current for element b is $i_b = -5\text{A}$, for element d is $i_d = 4\text{A}$, and for element e is $i_e = -1\text{A}$. By using the KVL and KCL, please find

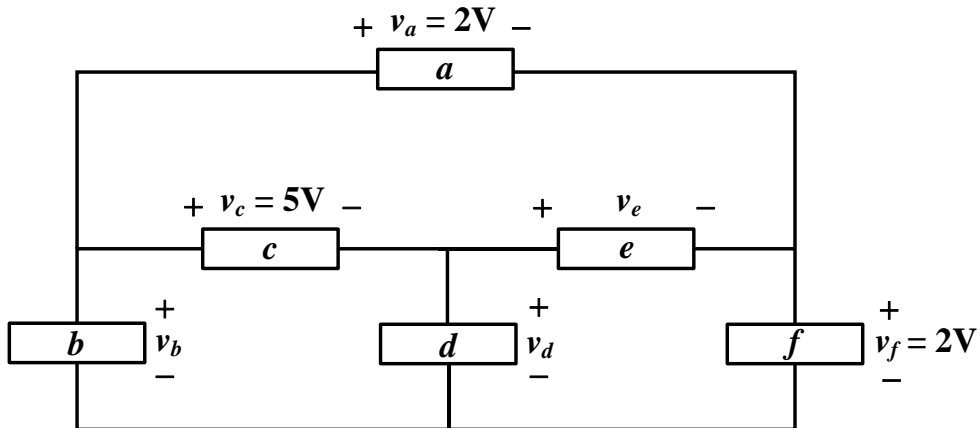- (i) the voltages of element d and e (v_d and v_e), (4%)
- (ii) the currents of element a and f (i_a and i_f), (4%)
- (iii) the power of element d (p_d). (2%)



(i) $v_d =$ _____, $v_e =$ _____,


(ii) $i_a =$ _____, $i_f =$ _____,

(iii) $p_d =$ _____.

5. Prove that in a network containing only linear resistors, every branch voltage and branch current must be zero. If a proof is not possible, illustrate the failure with a counter-example and restate the theorem with a suitable restriction so it can be proved. (10%)

Proof:

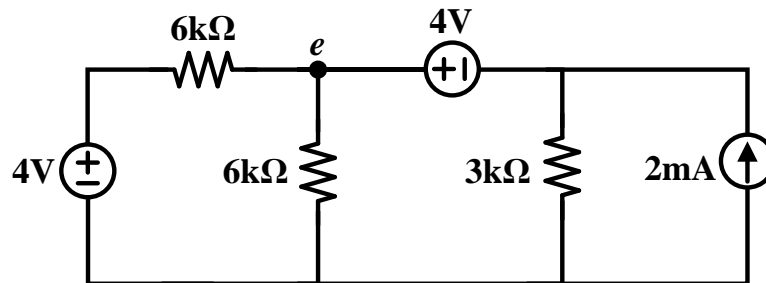
6. Find the node potential e in the following circuit. (7%)



$v_e =$ _____.

7. Find the current i of the following network by superposition.


(7%)

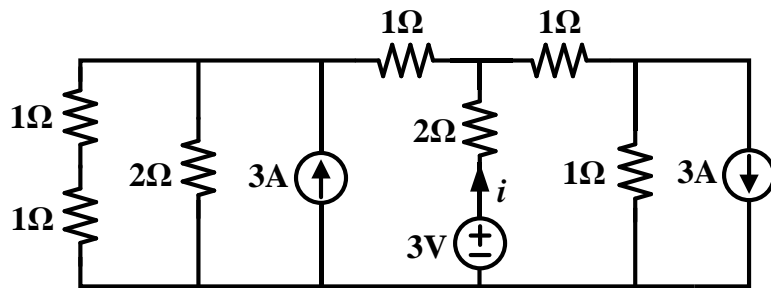

$i =$ _____.


8. Find the Norton equivalent of the circuit for the terminals marked AA' .

(10%)

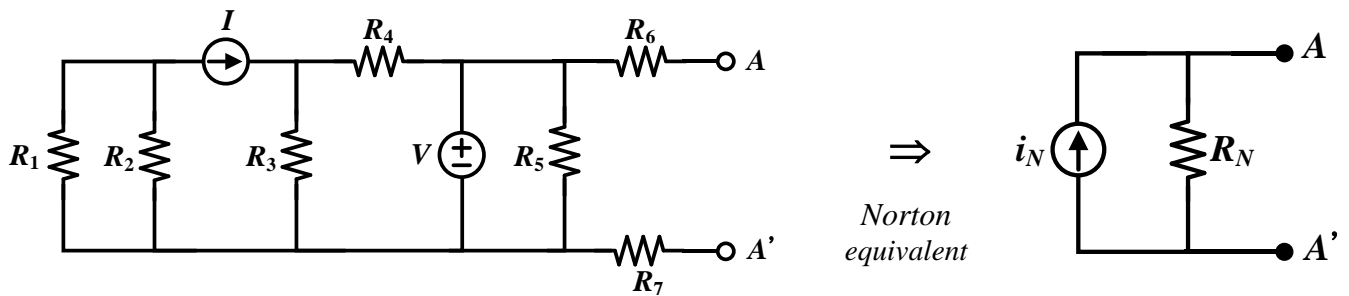


$i_N =$ _____, $R_N =$ _____.

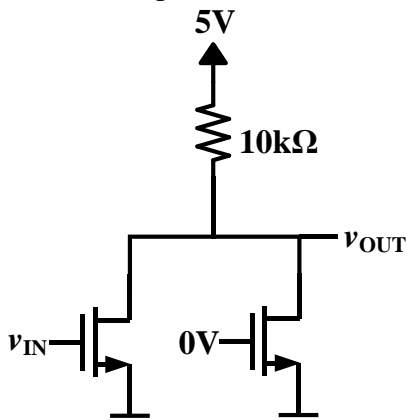9. (a) Draw the voltage transfer characteristics for the NOR gate circuit shown. (5%)
 (b) Can this gate be operated in a digital system characterized by a static discipline with the voltage thresholds below? **Explain.** (5%)
 (c) Compute the worst-case power ($p_{worst-case}$) consumed by this NOR gate. (5%)



For both MOSFET: $V_T = 2.1 \text{ V}$
 $R_{on} = 2 \text{ k}\Omega$

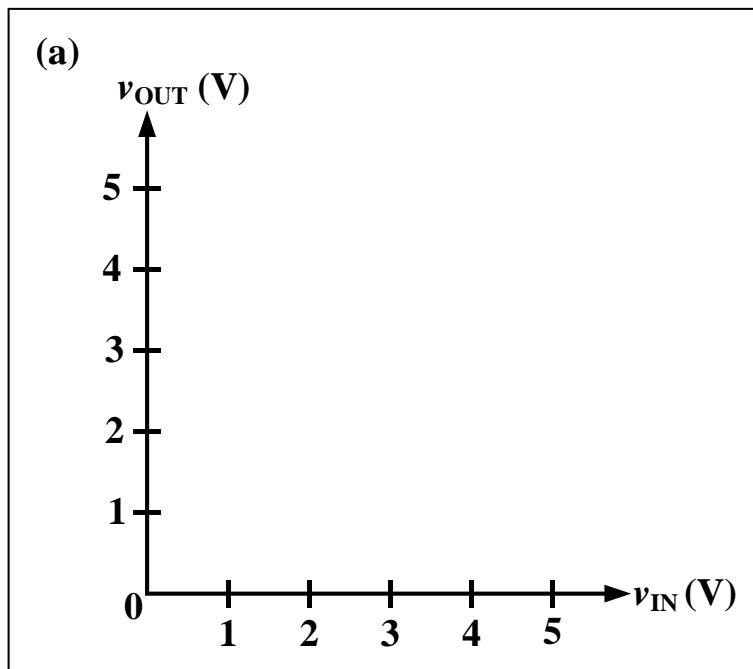Static Discipline: $V_{OL} = 1 \text{ V}$ $V_{OH} = 4 \text{ V}$
 $V_{IL} = 2 \text{ V}$ $V_{IH} = 3 \text{ V}$




(b) Can this gate be operated in a digital system characterized by the a static discipline? **Explain.**

Answer: _____.

(c) $p_{worst-case} =$ _____.

10. Find the Thévenin equivalent for the network at the terminals DS .


(8%)

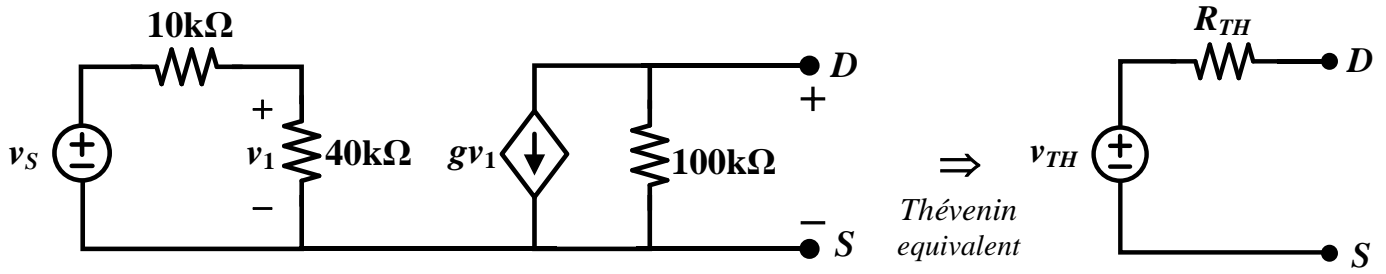

\Rightarrow
Thévenin
equivalent

$v_{TH} =$ _____, $R_{TH} =$ _____.

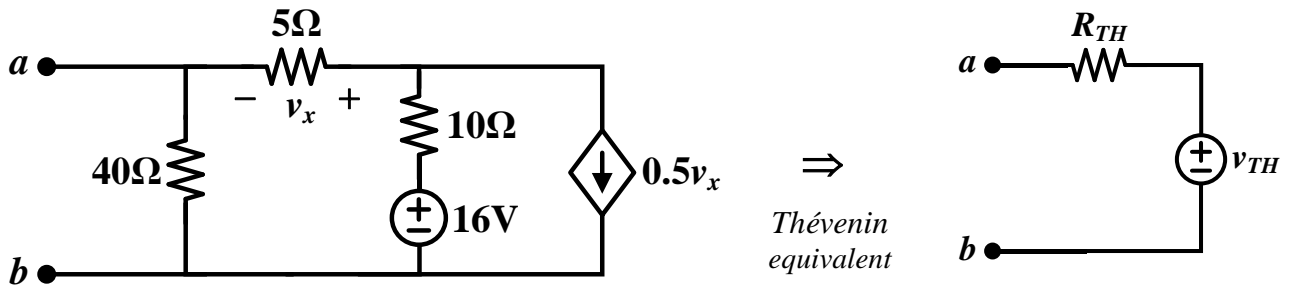11. Find the Thévenin equivalent parameters, v_{TH} and R_{TH} , for the port ab of the network shown in the following figure. (8%)



$v_{TH} =$ _____, $R_{TH} =$ _____.