

電路學(10410EE221002)第二次期中考

2015年12月09日

時間：2 小時

Close Book

學號： _____













姓名： _____

- There are 12 pages in this midterm exam, including this cover page. Please check that you have them all.
- Please write your 學號 姓名 in the space provided above.
- **IMPORTANT:** The problems in this exam vary in difficulty; moreover, questions of different levels of difficulty are distributed throughout the exam. If you find yourself spending a long time on a question, consider moving on to later problems in the exam, and then working on the challenging problems after you have finished all of the easier ones.
- Do your work and enter your answer for each question within the boundaries of that question. You may do your work on the back of the preceding page. Give a brief explanation if you are asked to explain.
- Remember to include the sign and units for all numerical answers.
- This is a closed-book exam, but you may use a calculator.
- You have 2 hours to complete this exam.
- Good luck!

Table of grades:


1.	2.	3.	4.	5.
6.	7.	8.	9.	
Total Grade:				

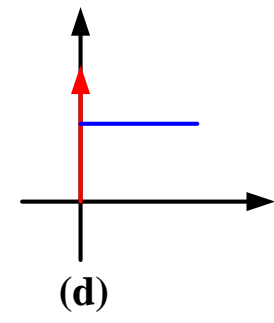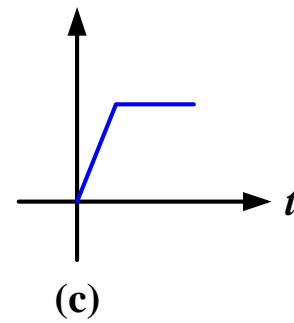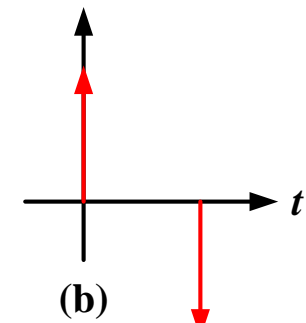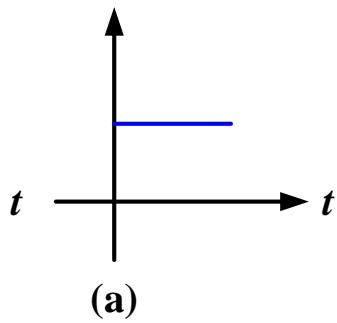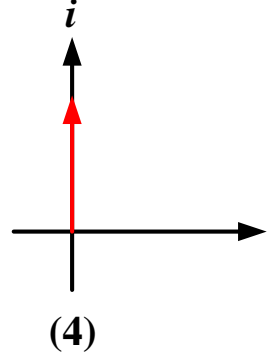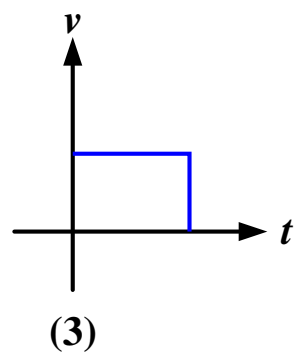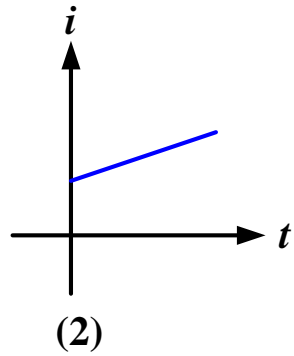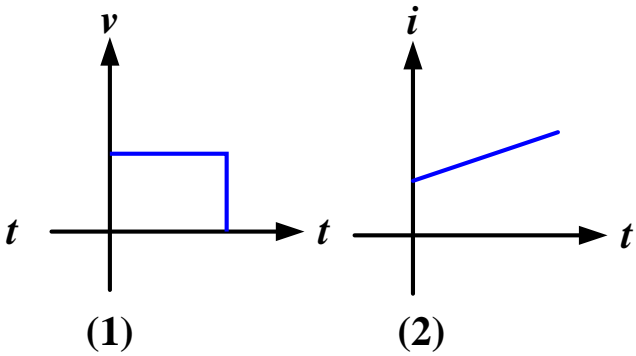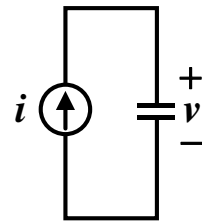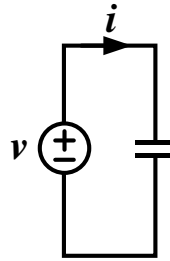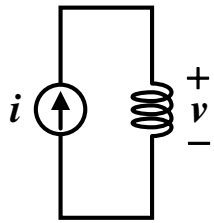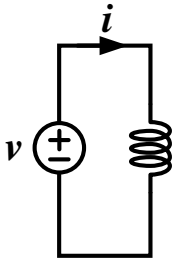1. The following figures show four circuits, labeled "(1)" through "(4)", together with the waveform for the source in each circuit. The figures also show four branch-variable waveforms, labeled "(a)" through "(d)", that could correspond to branch currents i or branch voltages v labeled in circuits. Match the branch variable waveform (a to d) to the appropriate circuit and source waveform (1 to 4). (8%)




(1) → c , (2) → d , (3) → b , (4) → a .

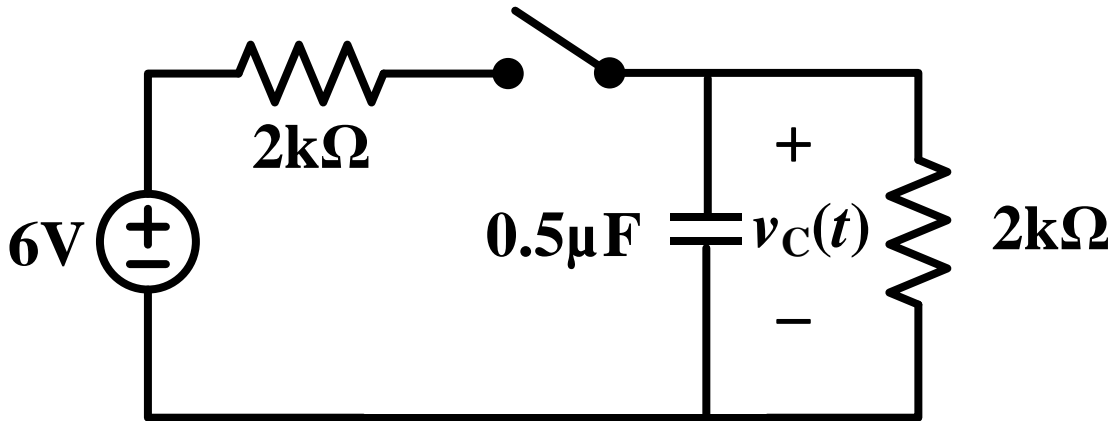2. For the circuit as shown, the switch was opened for a long time before it was closed at time $t = 0$ and opened at $t = 2.5$ msec. Find $v_C(t)$ for $t \geq 0$. (12%)




$\tau_1(0 < t < 2.5\text{ms}) = \underline{0.5\text{ms}}$ (2%), $\tau_2(t > 2.5\text{ms}) = \underline{1\text{ms}}$ (2%),

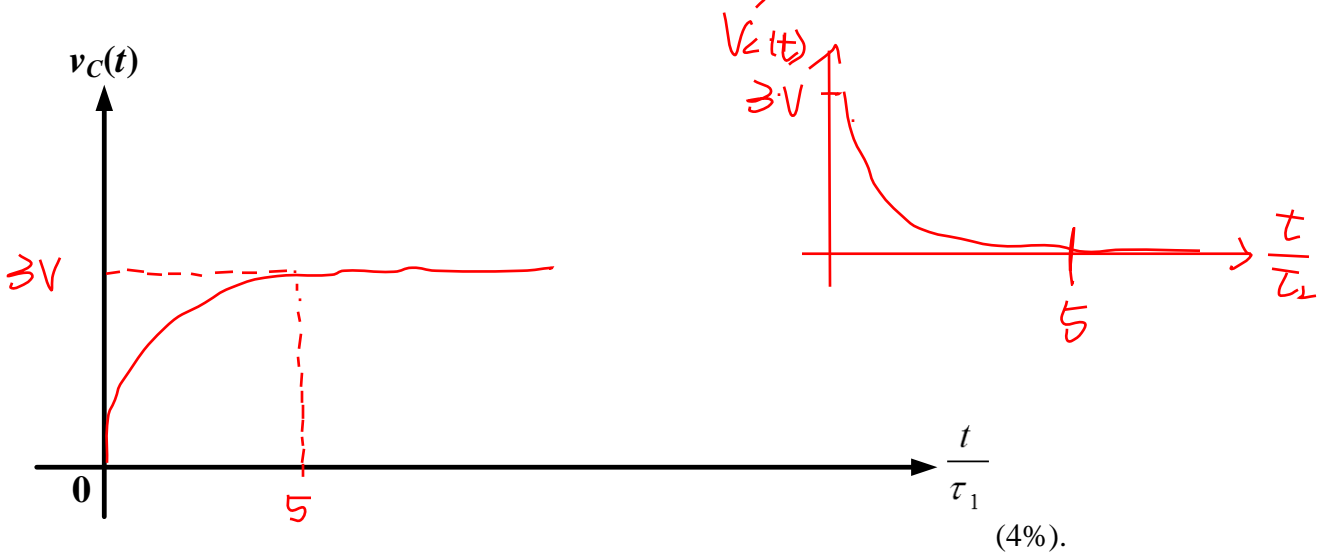$v_C(t) = \underline{3 - 3e^{-\frac{t}{0.5\text{ms}}}}$ (for $0 < t \leq 2.5\text{ms}$), $\underline{3e^{-\frac{t}{1\text{ms}}}}$ for $t > 2.5\text{ms}$ (4%).




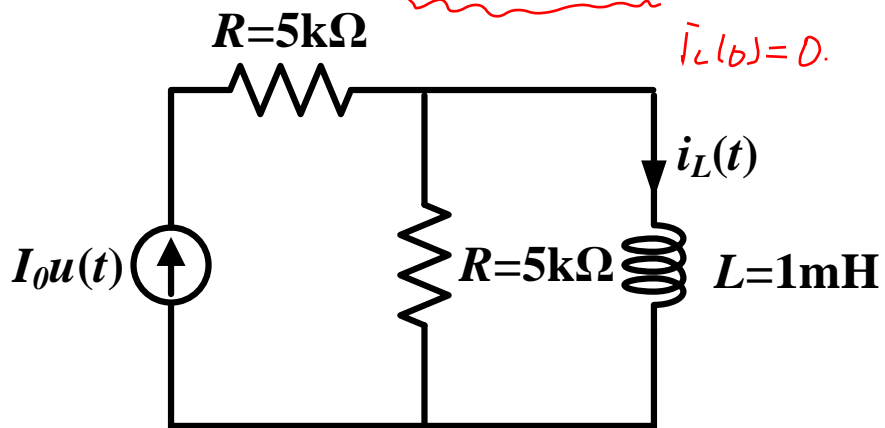3. For the circuit as shown, find and sketch the zero state response $i_L(t)$ for $t \geq 0$. (10%)





$\tau = \frac{L}{R} = 2 \times 10^{-7} \text{ s}$ (2%),

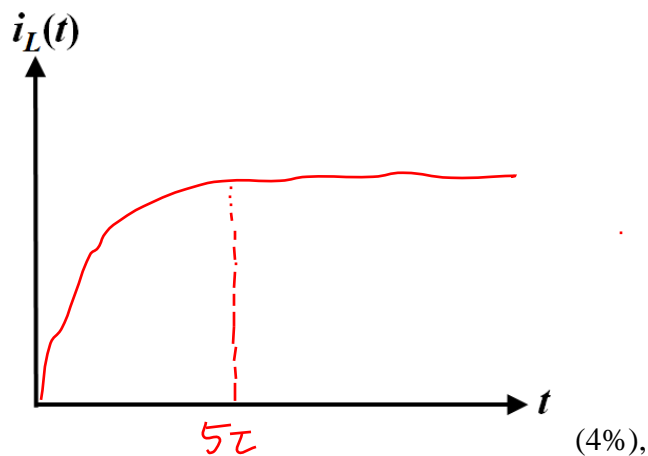$i_L(t) = I_0 - I_0 e^{-\frac{t}{L/R}}$ (4%),



4. Find the time constant τ of the circuit as shown.

(8%)

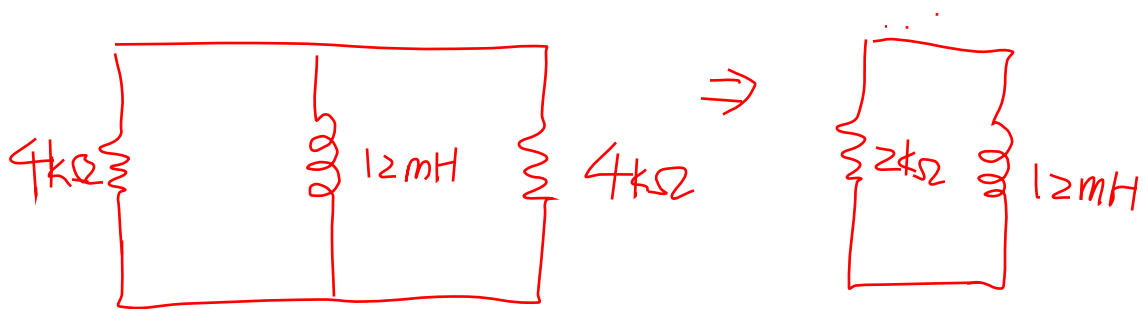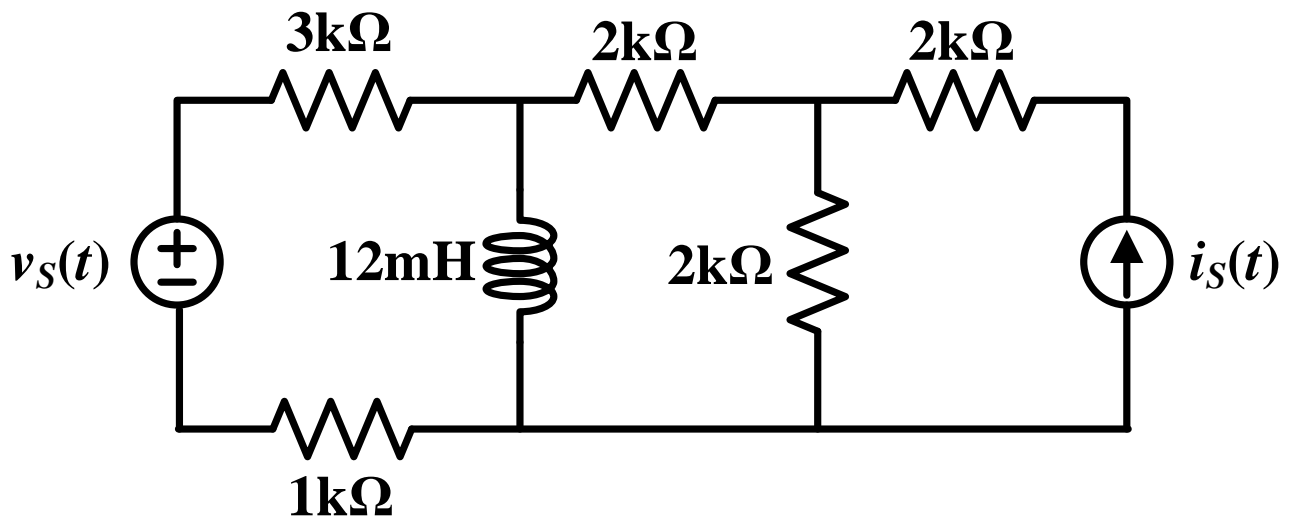


$$\tau = \frac{L}{R} = \frac{12\text{mH}}{2\text{k}\Omega} = 6 \times 10^{-6} \text{ s}$$

$\tau =$ _____

5. Find the time constant τ of the circuit show.


(10%)

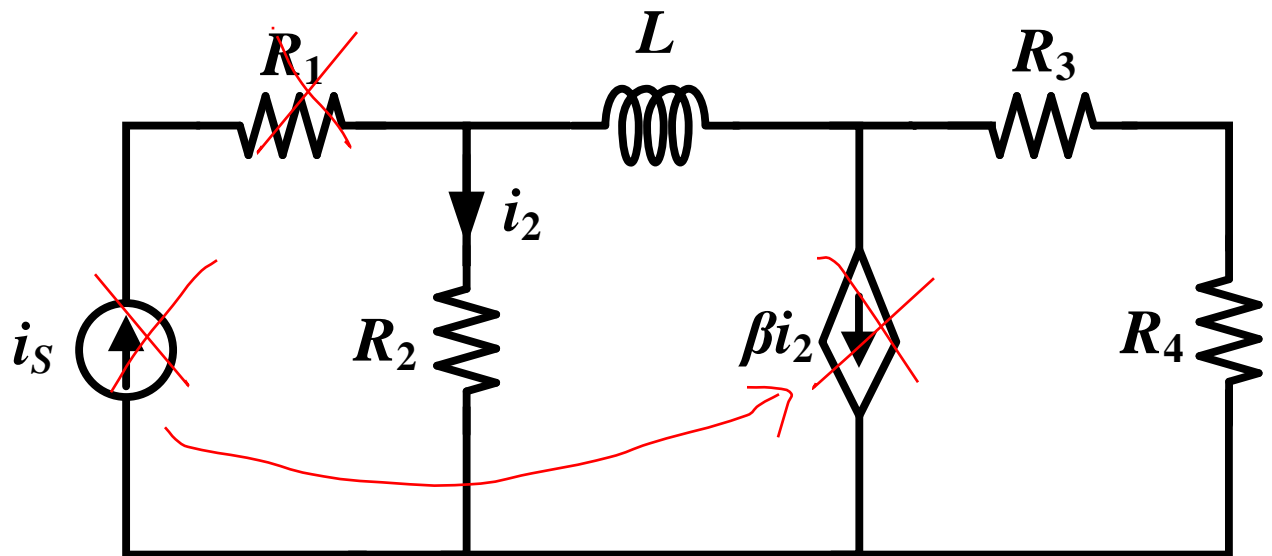

$$\therefore \tau = \frac{L}{R} = \frac{L}{R_2 + R_3 + R_4}$$

$\tau =$ _____

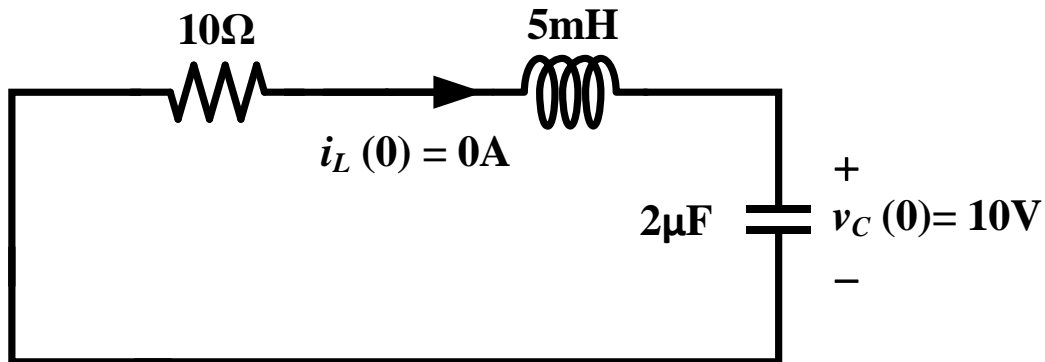
6. For the following circuit as shown, assume the initial state of the capacitor $v_C(0)$ is 10V and that of inductor $i_L(0) = 0$ A, answer that following questions. (16%)



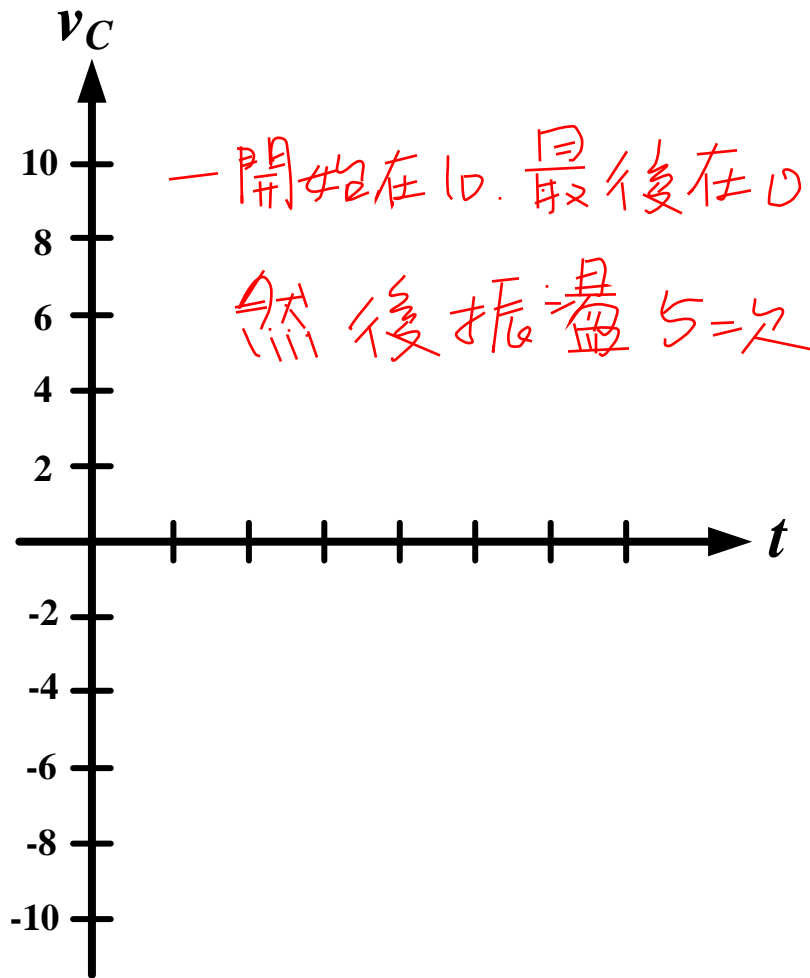
- (1) Find the undamped natural frequency, ω_0 . (2%)
- (2) Find the damping factor, α . (2%)
- (3) Find the approximate damped-natural frequency, ω_d . (2%)
- (4) Find the approximate period of the ringing, T . (2%)
- (5) Find the quality factor, Q . (2%)
- (6) Find $v_C(0^+)$. (1%)
- (7) Find $\frac{dv_C(0^+)}{dt}$. (1%)
- (8) Sketch the zero-input response $v_C(t)$ for $t \geq 0$. (4%)

$$\omega_0 = 10^4 \text{ rad/s}, \alpha = 10^3, \omega_d \approx 9950, T \approx 6315 \times 10^{-4} \text{ s}$$

$$Q = \frac{\omega_0}{2\alpha} = 5, v_C(0^+) = V_C(0) = 10, \frac{dv_C(0^+)}{dt} = \frac{i_C(0^+)}{C} = 0$$



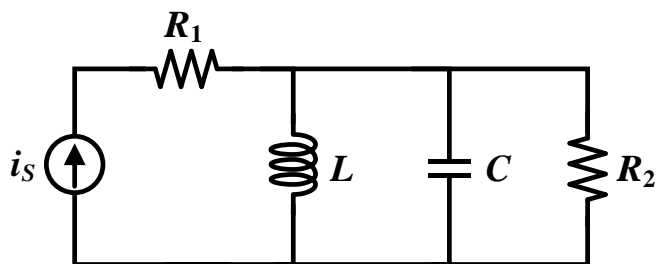7. Is the zero-input response of the following circuit under-damped, over-damped, or critically-damped assuming $L = 2\text{mH}$, $C = 0.2\mu\text{F}$, and $R_1 = R_2 = 50\ \Omega$? (10%)





$\alpha = 5 \times 10^4$ (3%), $\omega_0 = 5 \times 10^4$ (3%),

Answer: critically damped (4%).

8. For the RLC circuits as shown, this circuit is under a 125 Hz square wave excitation. The excitation and the response of the capacitor are also shown in the figure below. It is known that the capacitance is equal to $10\ \mu\text{F}$. From the information given, answer the following questions.

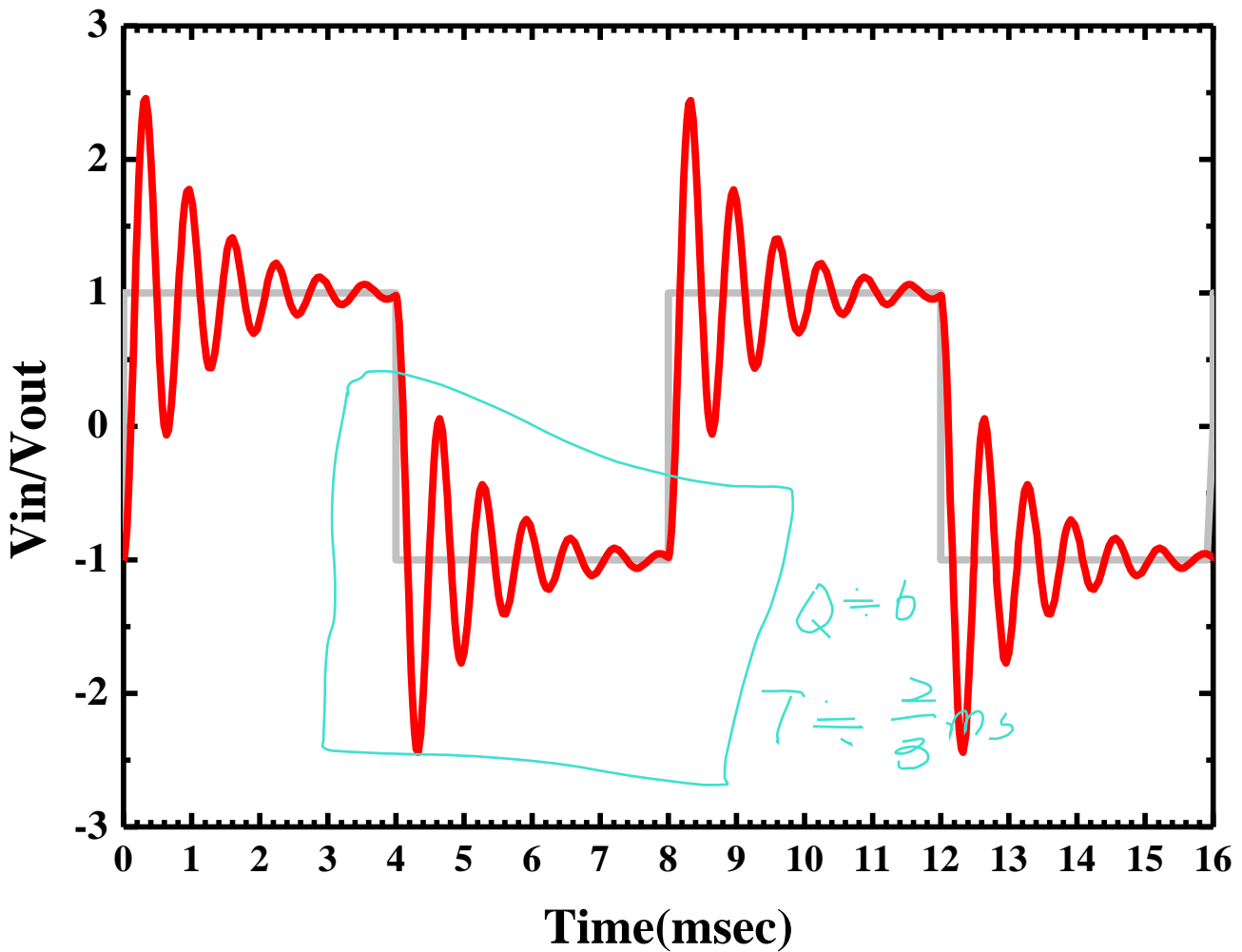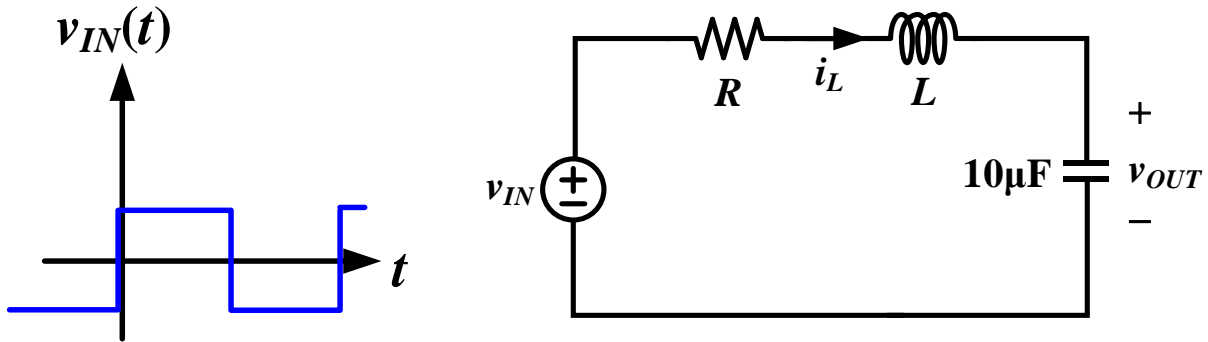
- (a) What is the resistance (approximately) of the resistor that is in the circuit? (6%)
- (b) What is the inductance (approximately) of the inductor that is in the circuit? (6%)




(a) $R = 1.7685 \Omega$

(b) $L = 1.126 \text{ mH}$

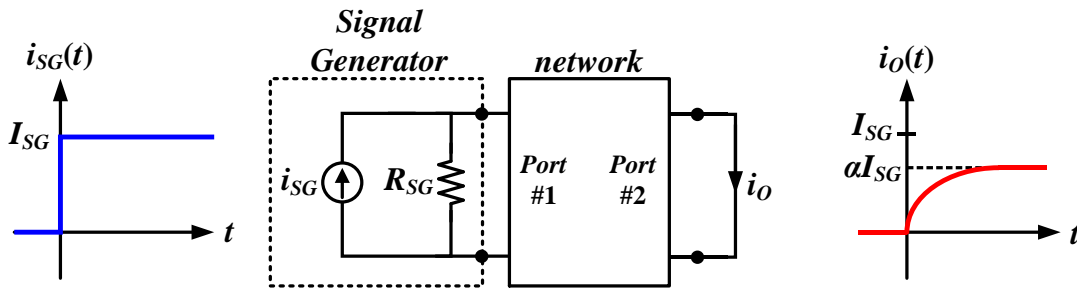9. A signal generator having Norton resistance R_{SG} is connected to Port #1 of a two-port network as shown below. At $t = 0$, the Norton current $i_{SG}(t)$ of the signal generator takes a step from zero to I_{SG} , and the current $i_o(t)$ is measured at Port #2 as shown below with the port short-circuited. Note that α is a unitless constant satisfying $0 < \alpha < 1$, and τ is a time constant. Assume that the Norton current of the signal generator is zero for a very long time prior to the step.



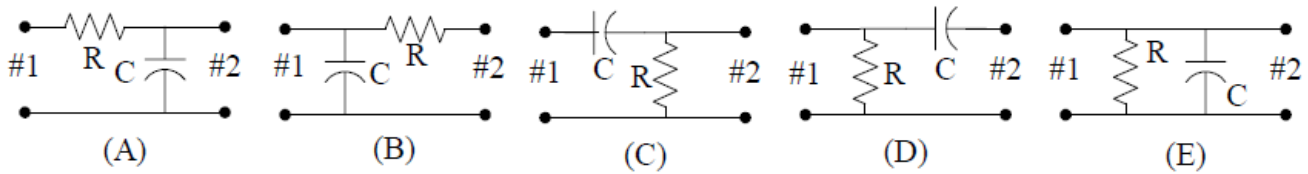(a) Which of the following could be the two-port network? (4%)



(a) Network (circle one): A **B** C D E

(b) Determine the values of R and C in the network you chose in Part (a). Express the values in terms of R_{SG} , α and τ . (10%)

$$R = \frac{1-\alpha}{\alpha} R_{SG}$$

$$C = \frac{\tau}{R // R_{SG}}$$

(b) $R =$ _____, $C =$ _____.