

EE2210 Electric Circuits, Spring 2018
Practice problems (Lecture11-Lecture14)

1. Find the magnitude and phase of each of the following expression:

$$(8 + j7)(5e^{j30^\circ})(e^{-j39^\circ})(0.3 - j0.1)$$

2. Find the real and imaginary parts of the following expressions:


(a)

$$(3 + j5)(4e^{j50^\circ})(7e^{-j20^\circ})$$


(b)

$$(10e^{j50^\circ})(e^{j20^\circ})$$

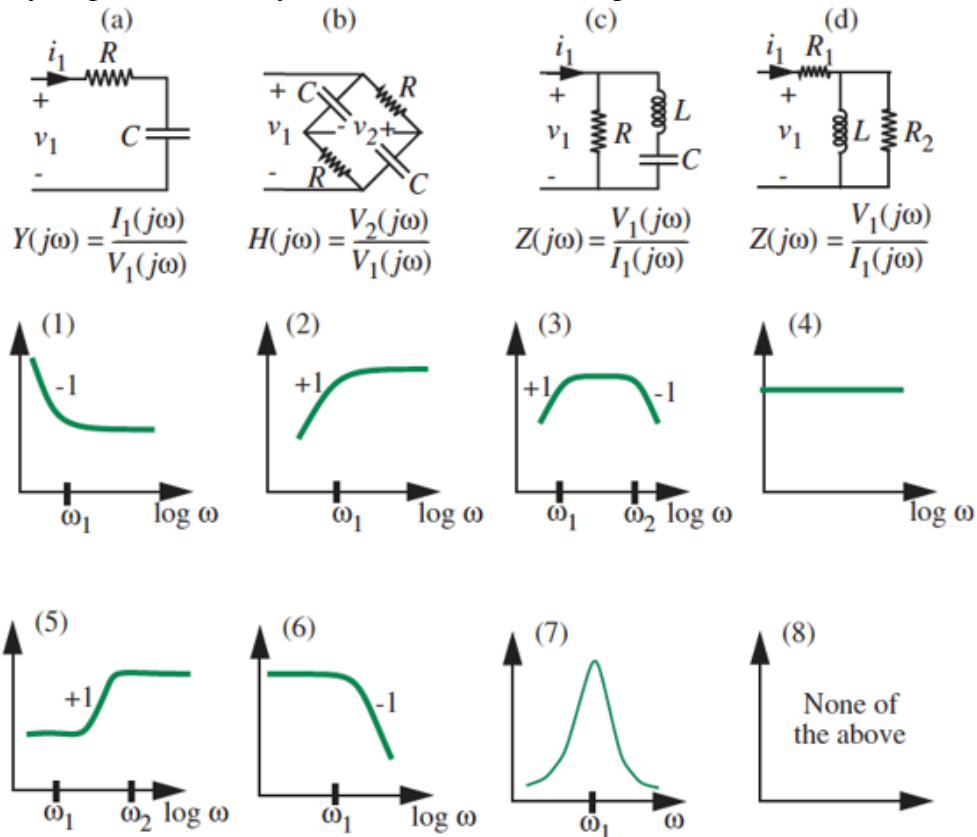
3. For each of the circuits shown in the following figures, select the magnitude of the frequency response for the system function (that is, impedance, admittance)




4. Write expressions for $H(j\omega) = V_o/V_i$, its magnitude $|H(j\omega)|$, and its phase angle $\angle H(j\omega)$, as a function of ω in the following figure.

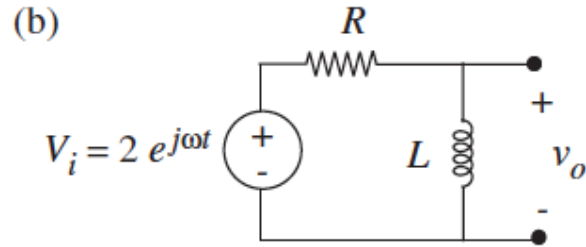

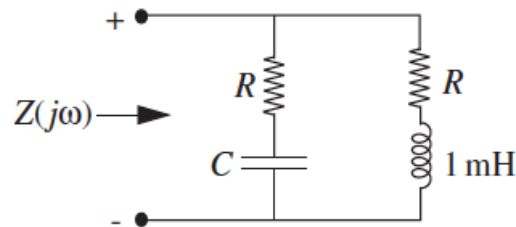
5. The impedance of the network shown in Figure is found to be $2\text{ k}\Omega$ and is purely real all frequencies. The value of the inductor is 1 mH as shown. What are the values of R and C ?



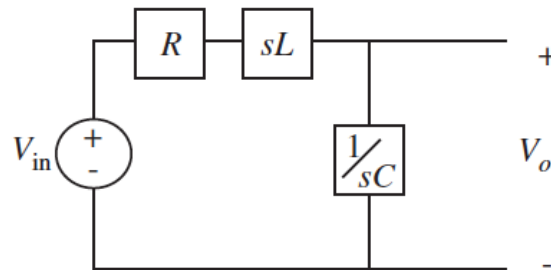
6. The circuit shown in Figure has an input voltage $v_{in}(t) = V_1 \cos(120\pi t)$, and $L = 500\text{ mH}$, $C = 80\text{ }\mu\text{F}$, and $R = 50\text{ }\Omega$. Compute the transfer function $H(s) = V_o(s)/V_{in}(s)$.



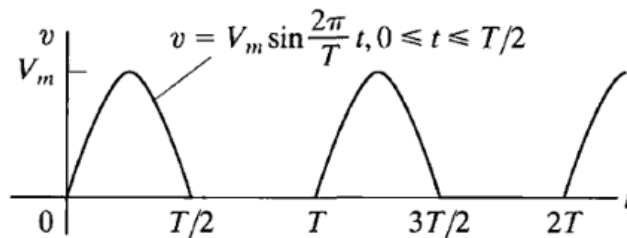
7. Find the rms value of the half-wave rectified sinusoidal voltage shown.



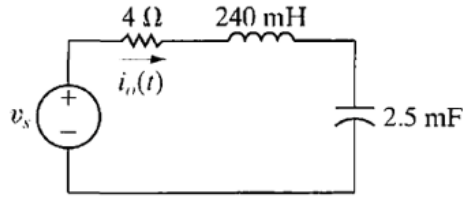8. Find the steady-state expression for $i_o(t)$ in the circuit in the following figure if $v_s = 100\sin 50t\text{ mV}$.



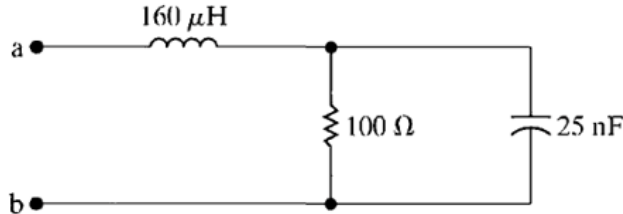- 9.
- For the circuit shown in the figure below, find the frequency (in radians per second) at which the impedance Z_{ab} is purely resistive.
 - Find the value of Z_{ab} at the frequency of (a).



10. A resistor denoted as R_L is connected in parallel with the capacitor in the circuit in the following Figure 14.7. The loaded low-pass filter circuit is shown in the following Figure 14.7.

- Derive the expression for the voltage transfer function $\frac{v_o}{v_i}$.
- At what frequency will the magnitude of $H(j\omega)$ be maximum?
- What is the maximum value of the magnitude of $H(j\omega)$?
- At what frequency will the magnitude of $H(j\omega)$ equal its maximum value divided by $\sqrt{2}$?
- Assume a resistance of $10 \text{ k}\Omega$ is added in parallel with the 100 nF capacitor in the circuit in Fig 14.4.

Find ω_c , $H(j0)$, $H(j\omega_c)$, $H(j0.1\omega_c)$, and $H(j10\omega_c)$.

Figure P14.7

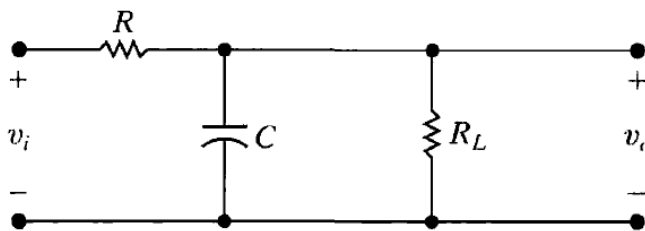


Figure P14.4

